# **Combinational Logic**

Prof. Usagi



# **Recap: Logic Design?**

Logic design

https://www.britannica.com/technology/logic-design

COMPUTER TECHNOLOGY

WRITTEN BY: The Editors of Encyclopaedia Britannica See Article History

Logic design, Basic organization of the circuitry of a digital computer. All digital computers are based on a two-valued logic system—1/0, on/off, yes/no (see <u>binary code</u>). Computers perform calculations using components called logic gates, which are made up of integrated circuits that receive an input signal, process it, and change it into an output signal. The components of the gates pass or block a clock pulse as it travels through them, and the output bits of the gates control other gates or output the result. There are three basic kinds of logic gates, called "and," "or," and "not." By connecting logic gates together, a device can be constructed that can perform basic arithmetic functions.











#### Recap: Why are digital computers more popular now?

- Please identify how many of the following statements explains why digital computers are now more popular than analog computers.
  - The cost of building systems with the same functionality is lower by using digital computers.
  - Digital computers can express more values than analog computers.
  - Ø Digital signals are less fragile to noise and defective/low-quality components.
  - Ø Digital data are easier to store.
  - A. 0
  - B. 1
  - C. 2



computers. quality components.

## Recap: The basic idea of a number system

- Each position represents a quantity; symbol in position means how many of that quantity
  102 101 100
  - Decimal (base 10)
    - Ten symbols: 0, 1, 2, 3, 4, 5, 6, 7, 8, 9
    - More than 9: next position
    - Each position is incremented by power of 10
  - Binary (base 2)
    - Two symbols: 0, 1
    - More than 1: next position
    - Each position is incremented by power of 2





- Two types of logics
- The theory behind combinational logics
- The building blocks of combinational logics

# **Types of circuits**

## **Combinational v.s. sequential logic**

- Combinational logic
  - The output is a pure function of its current inputs
  - The output doesn't change regardless how many times the logic is triggered — Idempotent
- Sequential logic
  - The output depends on current inputs, previous inputs, their history



# **Theory behind each**

- A Combinational logic is the implementation of a **Boolean Algebra** function with only Boolean Variables as their inputs
- A Sequential logic is the implementation of a **Finite-State Machine**

# **Boolean Algebra**

## **Boolean algebra (disambiguation)**

- Boolean algebra George Boole, 1815—1864
  - Introduced binary variables
  - Introduced the three fundamental logic operations: AND, OR, and NOT
  - Extended to abstract algebra with set operations: intersect, union, complement
- Switching algebra Claude Shannon, 1916—2001
  - Wrote his thesis demonstrating that electrical applications of Boolean algebra could construct any logical numerical relationship
  - Disposal of the abstract mathematical apparatus, casting switching • algebra as the two-element Boolean algebra.
  - We now use switching algebra and boolean algebra interchangeably in EE, but not doing that if you're interacting with a mathematician.



## **Basic Boolean Algebra Concepts**

- {0, 1}: The only two possible values in inputs/outputs
- Basic operators
  - AND (•) a b
    - returns 1 only if both a **and** b are 1s
    - otherwise returns 0
  - OR (+) a + b
    - returns 1 if a **or** b is 1
    - returns 0 if none of them are 1s
  - NOT (') a'
    - returns 0 if a is 1
    - returns 1 if a is 0



## **Truth tables**

 A table sets out the functional values of logical expressions on each of their functional arguments, that is, for each combination of values taken by their logical variables

Inp	Output	
Α	В	Output
0	0	0
0	1	0
1	0	0
1	1	1

#### **AND**

Ing	Output	
Α	В	Ουιραι
0	0	0
0	1	1
1	0	1
1	1	1

#### NOT

Input A	Output
0	1
0	1
1	0
1	0

## **Derived Boolean operators**

- NAND (a b)'
- NOR (a + b)'
- XOR (a + b) (a' + b') or ab' + a'b
- XNOR (a + b') (a' + b) or ab + a'b'

#### NAND

#### NOR

XOR

Inp	out	Output	Input		Input Input Input		out	Output	Input		Output
Α	В	Output	Α	В	Output	Α	В	Output	Α	В	Output
0	0	1	0	0	1	0	0	0	0	0	1
0	1	1	0	1	0	0	1	1	0	1	0
1	0	1	1	0	0	1	0	1	1	0	0
1	1	0	1	1	0	1	1	0	1	1	1



#### **XNOR**

# Express Boolean Operators/ Functions in Circuit "Gates"



## How to express y = e(ab+cd)









#### We can also make everything NOR!

Original

NAND





## How to express y = e(ab+cd)





У

# a

b

C

e





# How gates are implemented?

# Two type of CMOSs

- nMOS
  - Turns on when G = 1
  - When it's on, passes 0s, but not 1s
  - Connect S to ground (0)
  - Pulldown network
- pMOS
  - Turns on when G = 0
  - When it's on, passes 1s, but not 0s
  - Connect S to Vdd (1)
  - Pullup network

( -)

S

#### NOT Gate (Inverter) Vdd

Input	NMOS (passes 0	PMOS (passes 1	Output
Α	when on G=1)	when on G=0)	Output
0	OFF	ON	1
1	ON	OFF	0













NMOS2 (passes 0 when on G=1)	PMOS2 (passes 1 when on G=0)	Output
OFF	ON	1
ON	OFF	1
OFF	ON	1
ON	OFF	0

# Why use NAND?

- NAND and NOR are "universal gates" you can build any circuit with everything NAND or NOR
- Simplifies the design as you only need one type of gate
- NAND only needs 4 transistors gate delay is smaller than OR/AND that needs 6 transistors
- NAND is slightly faster than NOR due to the physics nature

## How about total number of transistors?







#### Now, only 5 gates and 4 transistors each — 20 transistors!



# Can We Get the Boolean Equation from a Truth Table?

## **Definitions of Boolean Function Expressions**

- Complement: variable with a bar over it or a ' A', B', C'
- Literal: variable or its complement A, A', B, B', C, C'
- Implicant: product of literals ABC, AC, BC
- Implicate: sum of literals (A+B+C), (A+C), (B+C)
- Minterm: AND that includes all input variables ABC, A'BC, AB'C
- Maxterm: OR that includes all input variables (A+B+C), (A'+B+C), (A'+B'+C)



## **Canonical form — Sum of "Minterms"**





#### **XNOR**





С	anc	onical	form — Product of "				
Inp	Input						
X	Y	Output	f(X,Y) =( <u>X+Y</u> ) ( <u>X + Y')</u>				
0	0	0					
0	1	0					
1	0	1					
1	1	1					
	XNO	R					
In	put	Output					
Α	В	Output					
0	0	1	T(A,B) = (A+B) (A+B)				
0	1	0	]f				
1	0	0					
1	1	1	10				
	Inc X 0 0 1 1 1 1 1 0 0 0 0 0 1 1 1	Canc     Input     X   Y     0   0     0   1     1   0     1   1     X   Y     0   1     1   0     X   Y     0   1     X   Y     Q   0     X   Y     X   Y     Q   0     X   Y     X   Y     Q   0     X   Y     X   Y     X   Y     X   Y     X   Y     X   Y     X   Y     X   Y     X   Y     X   Y     X   Y     X   Y     X   Y     X   Y     X   Y     X   Y     X   Y     X   Y     X <th>Input   Output     X   Y   Output     0   0   0     0   1   0     1   0   1     1   1   1     1   1   1     1   1   1     1   1   1     1   1   1     1   1   1     1   1   1     1   1   1     0   0   1     0   0   1     0   1   0     1   0   1     0   1   0     1   0   0     1   0   0</th>	Input   Output     X   Y   Output     0   0   0     0   1   0     1   0   1     1   1   1     1   1   1     1   1   1     1   1   1     1   1   1     1   1   1     1   1   1     1   1   1     0   0   1     0   0   1     0   1   0     1   0   1     0   1   0     1   0   0     1   0   0				



#### – Product of maxterms

# Let's design a circuit!



## **Binary addition**



#### full adder — adder with without a carry as an input a carry as an input

3 + 2 = 5carry 0 +00'100101

	npu	t	Out	tput
Α	В	Cin	Out	Cout
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	1	1

# half adder — adder

Input		Ou	tput
Α	В	Out	Cout
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

## Half adder



Input		Output	
Α	В	Out	Cout
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

#### Cout

## sum-of-products/product-of-sums

- They can be used interchangeably
- Depends on if the truth table has more 0s or 1s in the result
- Neither forms give you the "optimized" equation. By optimized, we mean — minimize the number of operations



# Can we simplify these functions?

# Laws in Boolean Algebra

OR

Associative laws	(a+b)+c=a+(b+c)
<b>Commutative laws</b>	a+b=b+a
<b>Distributive laws</b>	a+(b·c)=(a+b)·(a+c)
Identity laws	a+0=a
<b>Complement laws</b>	a+a'=1

Duality: We swap all operators between (+,.) and interchange all elements between (0,1). For a theorem if the statement can be proven with the laws of Boolean algebra, then the duality of the statement is also true.



#### AND

## Some more tools

	OR	
DeMorgan's Theorem	(a + b)' = a'b'	
<b>Covering Theorem</b>	a(a+b) = a+ab = a	ab -
<b>Consensus Theorem</b>	ab+ac+b'c = ab+b'c	(a+b)(
<b>Uniting Theorem</b>	a (b + b') = a	
Shannon's Expansion	f(a,b,c) = a'b' + bc f(a,b,c) = a f(1, b, c) +	



$$a'b' = (a + b)'$$

#### (a+c)(b'+c) = (a+b)(b'+c)

$$(a+b)\cdot(a+b')=a$$

c + ab'c - a' f(0,b,c)