
 


# Datapath Components (4) — Those Who Can “Remember” Things

Prof. Usagi

# Recap: D flip-flop

 


# Outline

- Volatile Memory
  - Registers
  - SRAM
  - DRAM
- Non-volatile Memory

# Registers

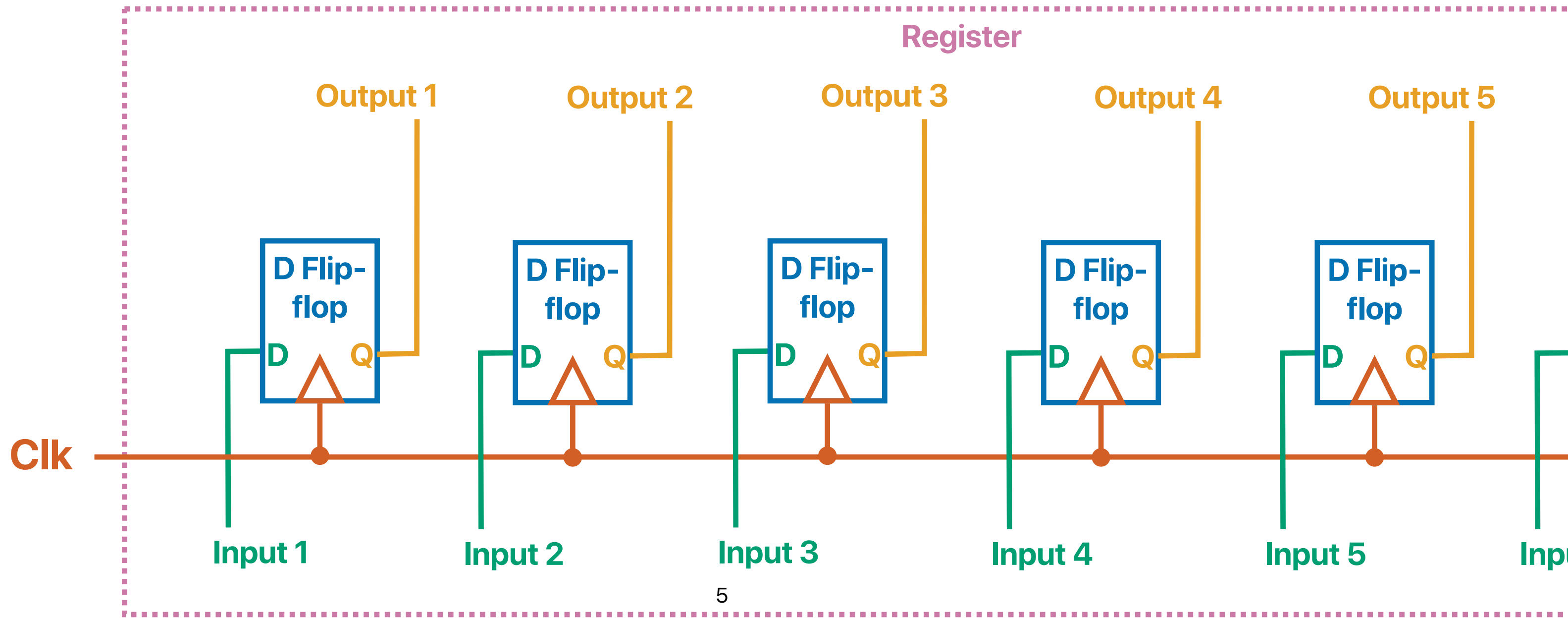
# Registers

- Register: a sequential component that can store multiple bits
- A basic register can be built simply by using multiple D-FFs



# Shift register


- Holds & shifts samples of input

 

# Pattern Recognizer


- Combinational function of input samples

We can recognize 1001!

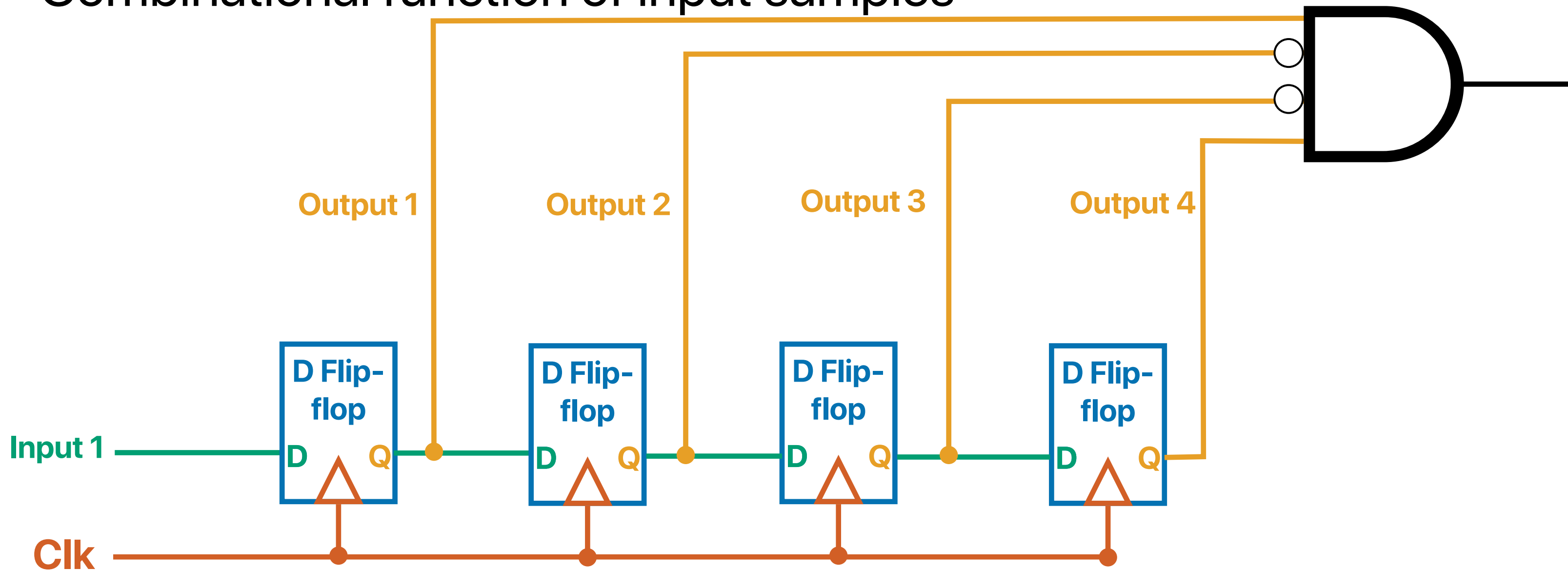
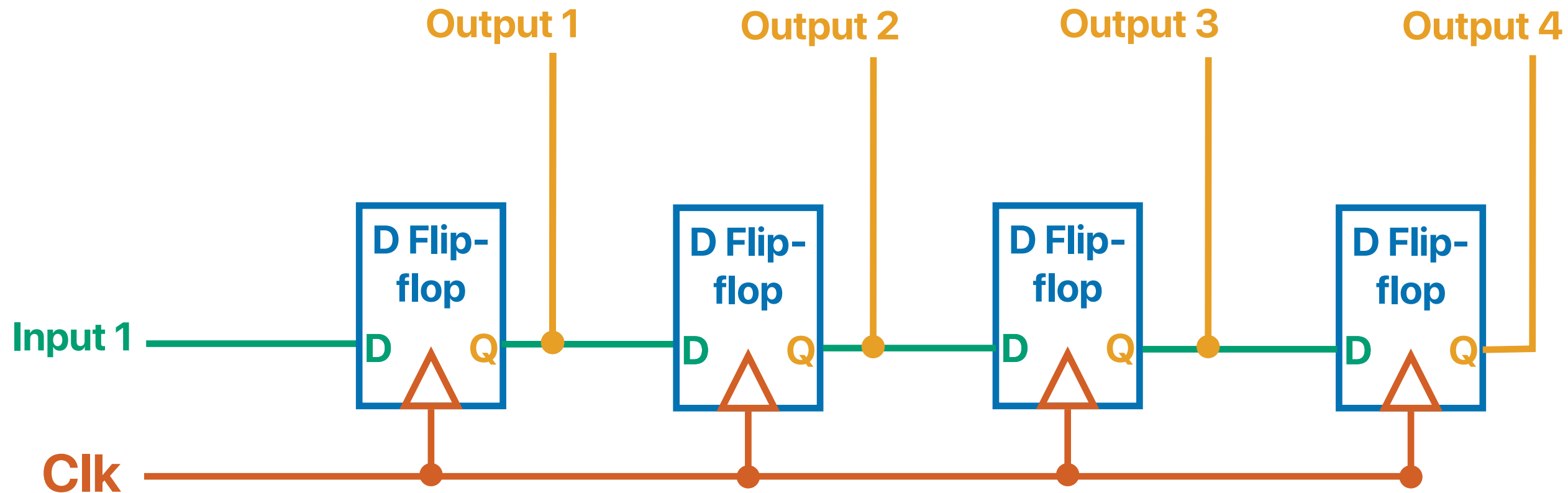
# Counters


- Sequences through a fixed set of patterns
- Note: definition is general
- For example, the one in the figure is a type of counter called Linear Feedback Shift Register (LFSR)






# **Static Random Access Memory (SRAM)**


# A Classical 6-T SRAM Cell

 


# Write "1" to an SRAM Cell

 


# Write "0" to an SRAM Cell

 

# Reading from an SRAM Cell

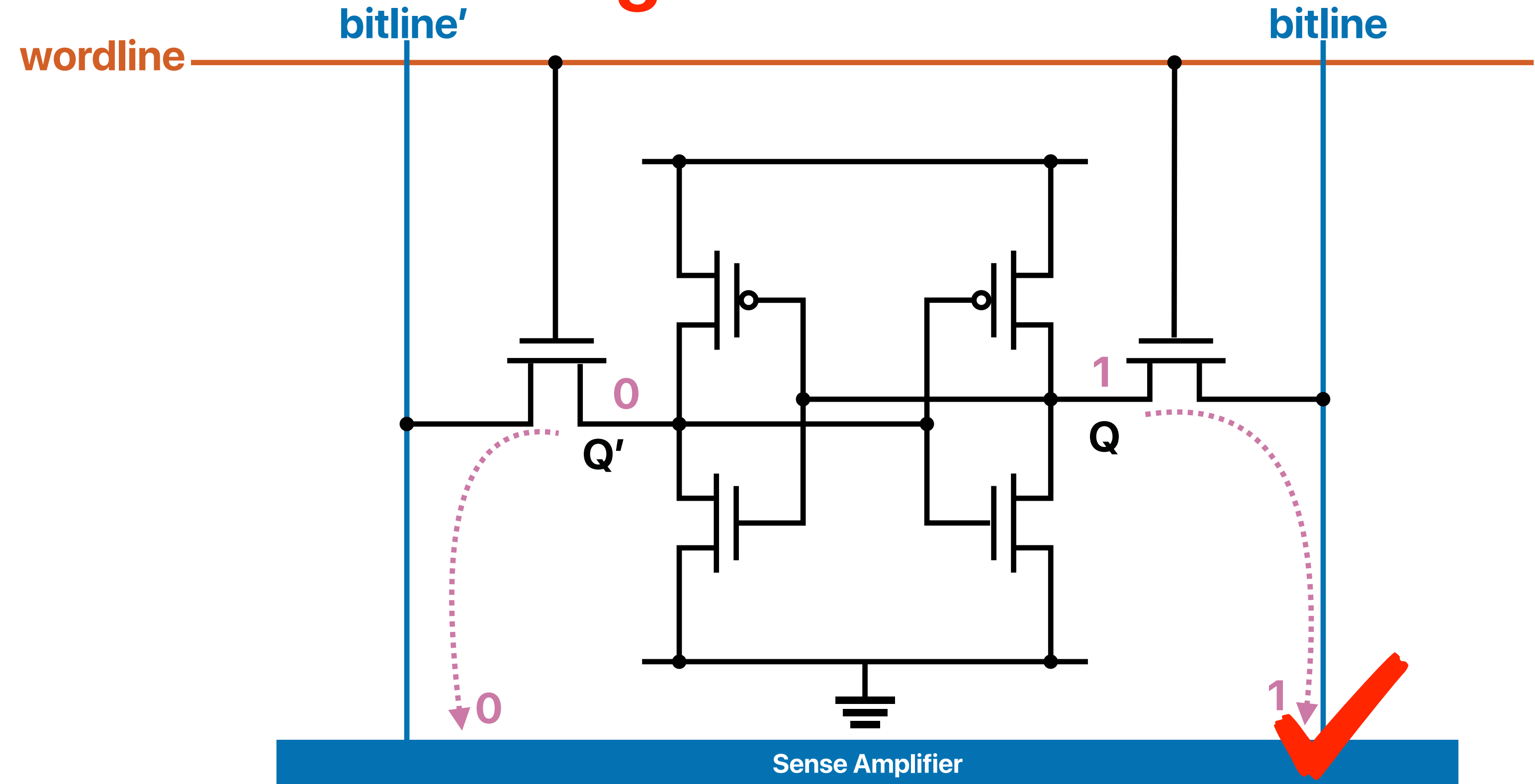


# SRAM array

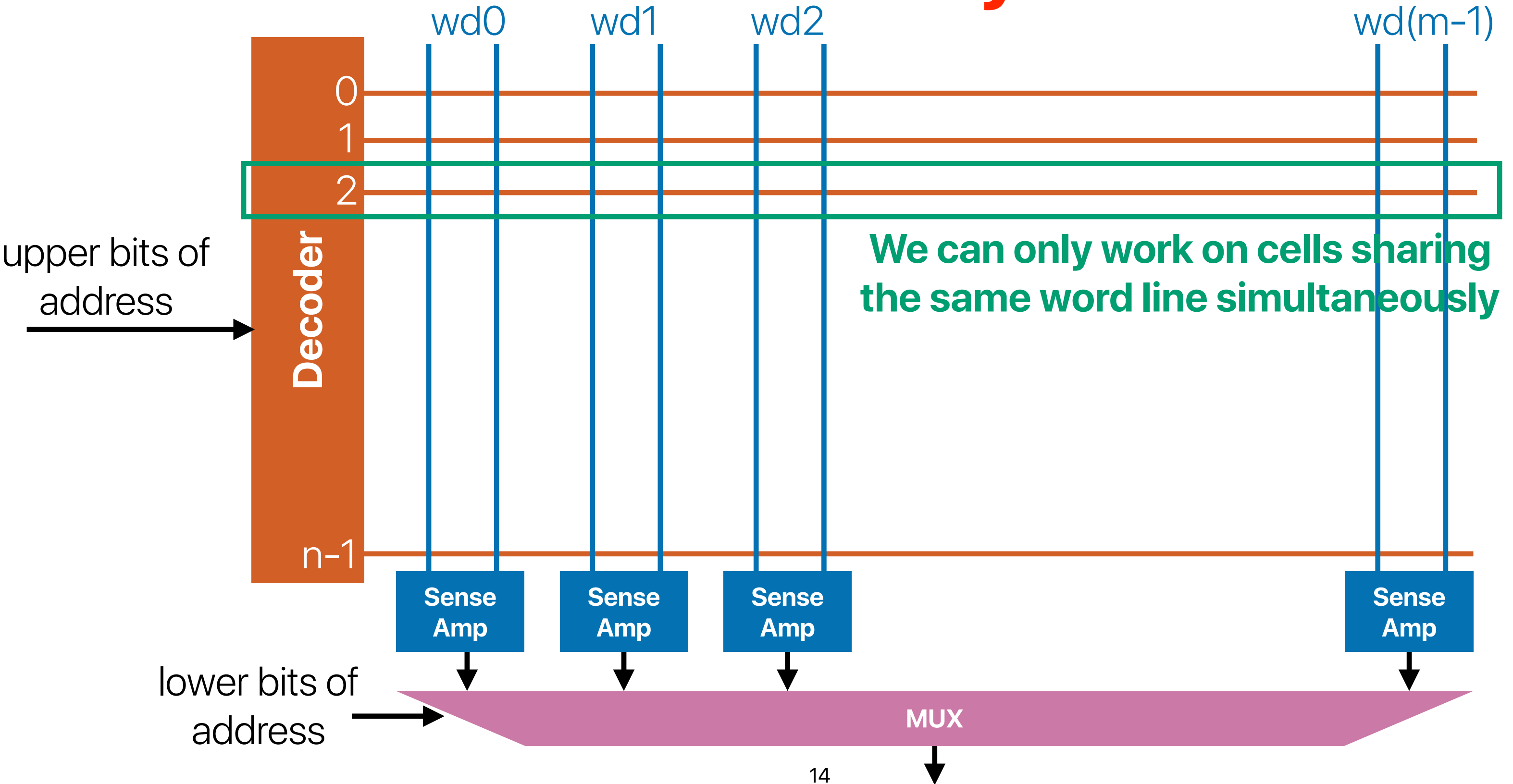

# **Dynamic Random Access Memory (DRAM)**


# An DRAM cell

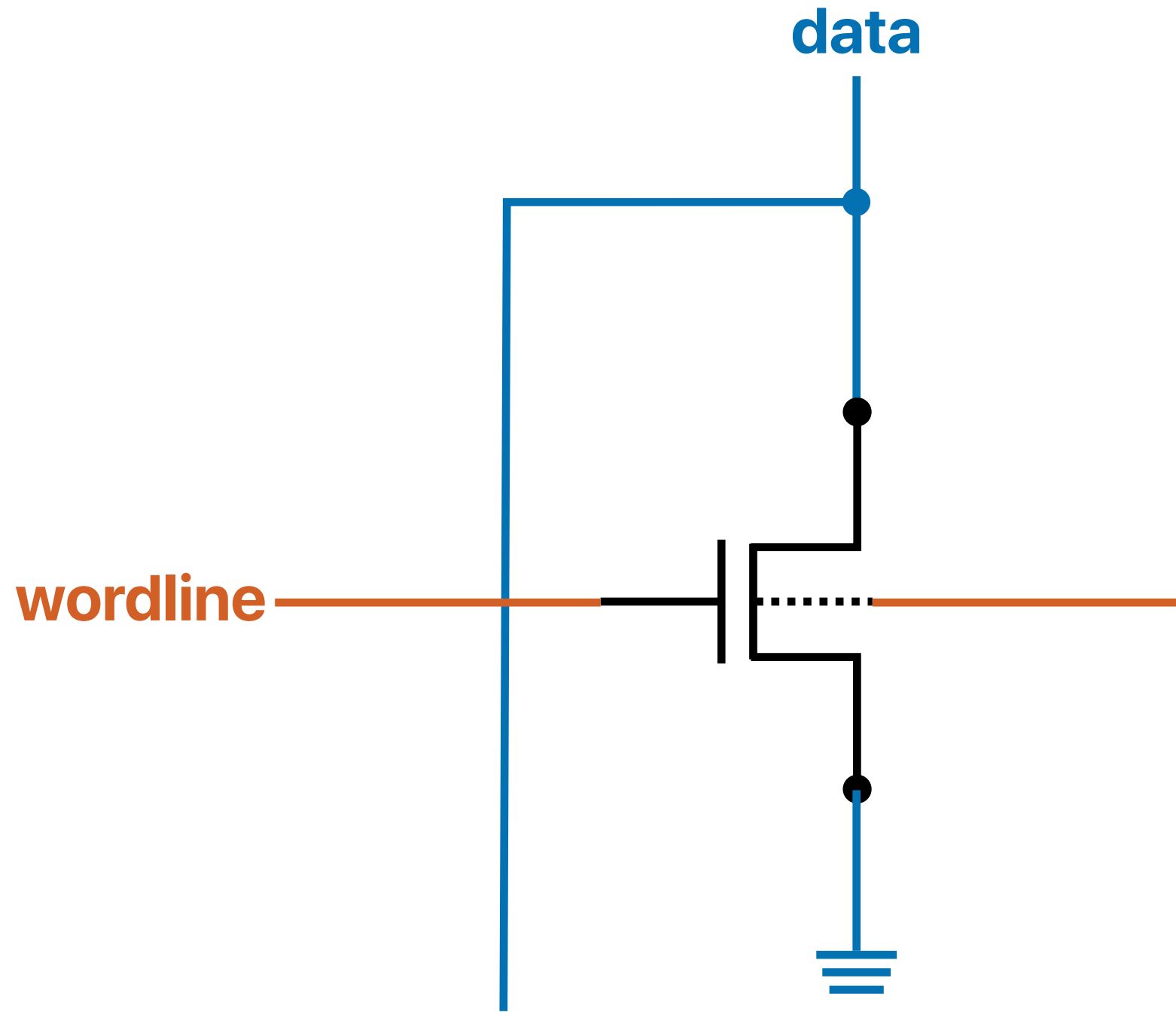


- 1 transistor (rather than 6)
- Relies on large capacitor to store bit
  - Write: transistor conducts, data voltage level gets stored on top plate of capacitor
  - Read: look at the value of d
- Problem: Capacitor discharges over time
  - Must "refresh" regularly, by reading d and then writing it right back



# DRAM array

 

# RC charging

 


$$V_b = V_R + V_C$$

$$V_b = IR + \frac{Q}{C}$$

As charging progresses,

$$V_b = IR + \frac{Q}{C}$$

 current decreases and  
charge increases.



At  $t = 0$

$$Q = 0$$

$$V_C = 0$$

$$I = \frac{V_b}{R}$$

As  $t \rightarrow \infty$

$$Q \rightarrow CV_b$$

$$V_C \rightarrow V_b$$

$$I \rightarrow 0$$

# Latency of volatile memory

	Size (Transistors per bit)	Latency (ns)
Register	18T	~ 0.1 ns
SRAM	6T	~ 0.5 ns
DRAM	1T	50-100 ns


# **Non-volatile memory**

# Volatile v.s. Non-volatile


- Volatile memory
  - The stored bits will vanish if the cell is not supplied with electricity
  - Register, SRAM, DRAM
- Non-volatile memory
  - The stored bits will not vanish “immediately” when it’s out of electricity — usually can last years
  - Flash memory, PCM, MRAM, STTRAM
 
# Flash memory

- Floating gate made by polycrystalline silicon trap electrons
- The voltage level within the floating gate determines the value of the cell
- The floating gates will wear out eventually



# Basic flash operations

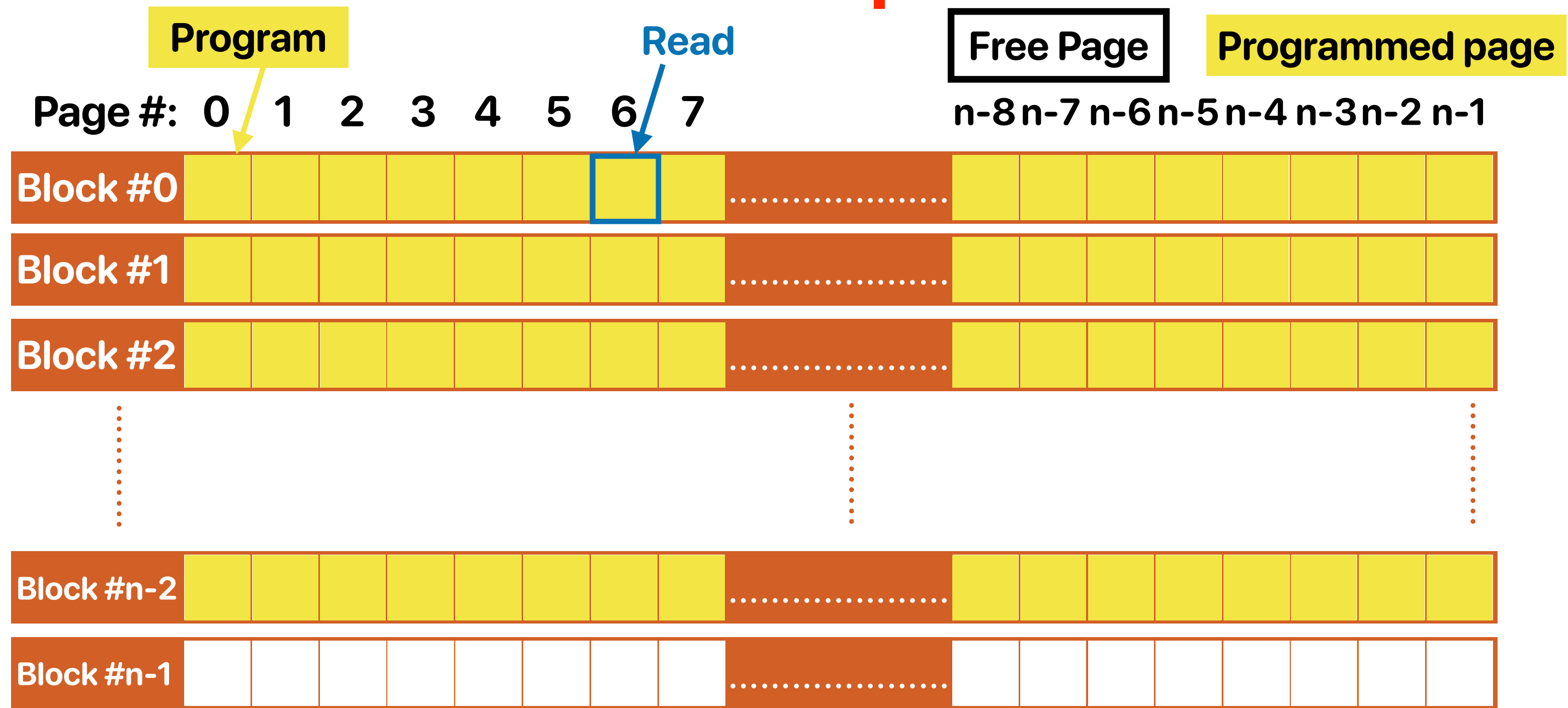

# Types of Flash Chips

2 voltage levels,  
1-bit



**Single-Level Cell  
(SLC)**

4 voltage levels,  
2-bit



**Multi-Level Cell  
(MLC)**

8 voltage levels,  
3-bit



**Triple-Level Cell  
(TLC)**

16 voltage levels,  
4-bit



**Quad-Level Cell  
(QLC)**



# Programming in MLC

4 voltage levels,  
2-bit




**Multi-Level Cell  
(MLC)**

**3.14000000000000001243449787580**

**= 0x40091EB851EB851F**

 
**= 01000000 00001001 00011110 10111000 01010001 11101011 10000101 00011111**



**3 Cycles/Phases to finish programming**


# Programming in MLC

4 voltage levels,  
2-bit

 

**Multi-Level Cell  
(MLC)**

 **3.140000000000000000001243449787580**  
**= 0x40091EB851EB851F**  
**= 01000000 00001001 00011110 10111000 01010001 11101011 10000101 00011111**



**1 Phase to finish programming the first page!**



# Programming the 2nd page in MLC

3.140000000000000000001243449787580

= 0x40091EB851EB851F

= 01000000 00001001 00011110 10111000 01010001 11101011 10000101 00011111

  
= 01000000 00001001 00011110 10111000 01010001 11101011 10000101 00011111




2 Phase to finish programming the second page!

# Optimizing 1st Page Programming in MLC

4 voltage levels,  
2-bit

 

 3.140000000000000000001243449787580  
= 0x40091EB851EB851F  
= 01000000 00001001 00011110 10111000 01010001 11101011 10000101 00011111




1 Phase to finish programming the first page!

28 — the phase is shorter now
 
# 2nd Page Programming in MLC

2<sup>nd</sup> page 4 voltage levels,  
2-bit





Multi-Level Cell  
(MLC)

3.140000000000000000001243449787580

= 0x40091EB851EB851F

= 01000000 00001001 00011110 10111000 01010001 11101011 10000101 00011111

  
= 01000000 00001001 00011110 10111000 01010001 11101011 10000101 00011111




2 Phase to finish programming the second page!

Not a good practice


# Flash performance

 

**Reads:**  
less than 150us

 

**Program/write:**  
less than 2ms

 


**Erase:**  
less than 3.6ms

**Similar relative performance for reads, writes and erases**

Laura M. Grupp, Adrian M. Caulfield, Joel Coburn, Steven Swanson, Eitan Yaakobi, Paul H. Siegel, and Jack K. Wolf.  
Characterizing flash memory: anomalies, observations, and applications. In MICRO 2009.

# Basic flash operations

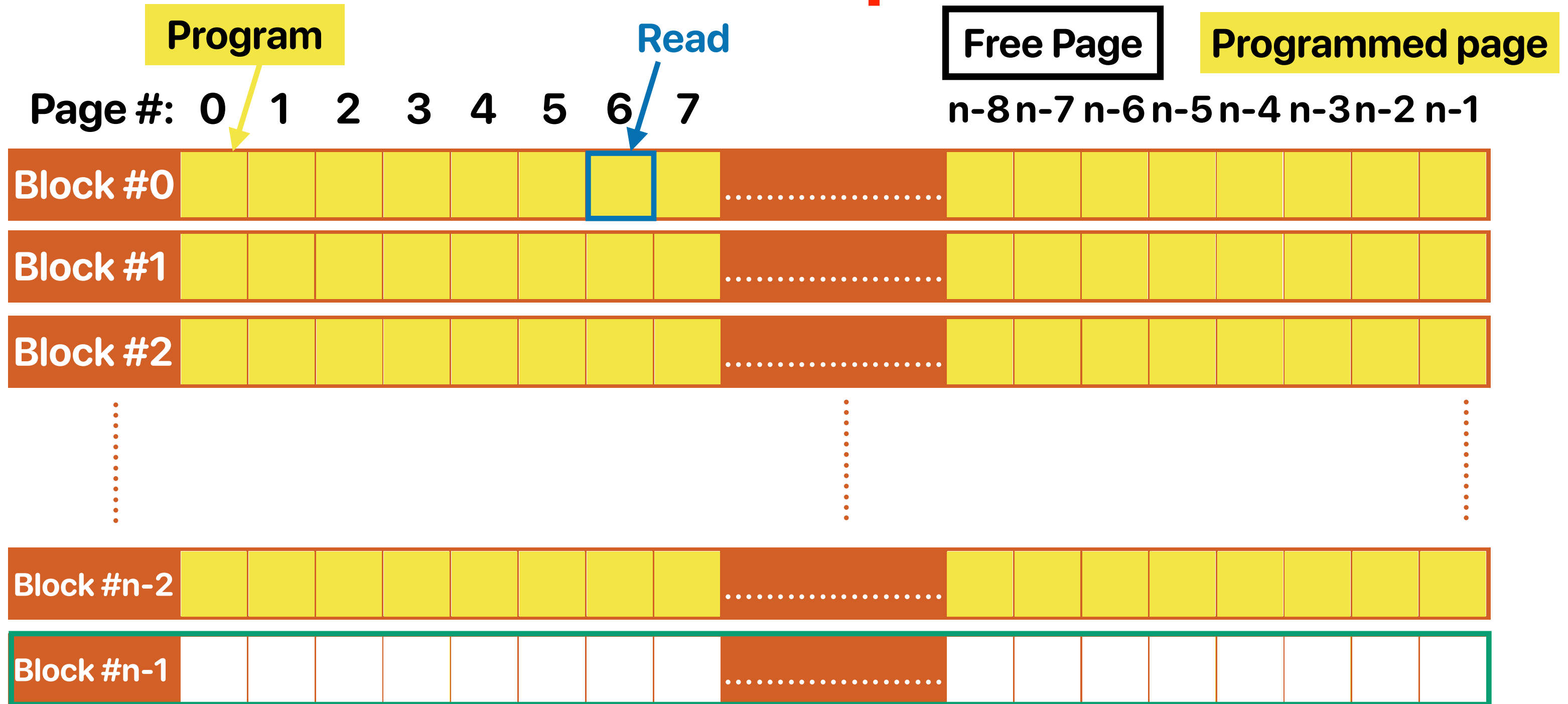

- Flash pages must be erased in "blocks"

# If programmer doesn't know flash "features"

- Software designer should be aware of the characteristics of underlying hardware components

## Spotify is writing massive amounts of junk data to storage drives

Streaming app used by 40 million writes hundreds of gigabytes per day.

DAN GOODIN - 11/10/2016, 7:00 PM




[Enlarge](#) / SSD modules like this one are being abused by Spotify.

204

For almost five months—possibly longer—the Spotify music streaming app has been assaulting users' storage devices with enough data to potentially take years off their expected lifespans. Reports of tens or in some cases hundreds of gigabytes being written in an hour aren't uncommon, and occasionally the recorded amounts are measured in terabytes. The overload happens even when Spotify is idle and isn't storing any songs locally.



# Non-volatile memory technologies

 

	H.D.D	Flash	Optane	STT-MRAM
Latency	~ 10-15 ms	~ 100 us (read) ~ 1 ms (write)	7 us (read) 18 us (write)	35 ns
Bandwidth	~200 MB/Sec	3.5 GB/sec (read) 2.1 GB/sec (write)	1.35 GB/sec (read) 290 MB/sec (write)	
Dollar/GB	0.0295	0.583	2.18	

**Flash is still the most convincing technology for now**

# Announcement

- Assignment #4 due next Tuesday — **Chapter 4.8-4.9 & 5.2-5.4**
- Lab 5 is up — due next Thursday
  - Start early & plan your time carefully
  - Watch the video and read the instruction BEFORE your session
  - There are links on both course webpage and iLearn lab section
  - Submit through iLearn > Labs
- Check your grades in iLearn

# Electrical Computer Science Engineering

# 120A

# つづく

