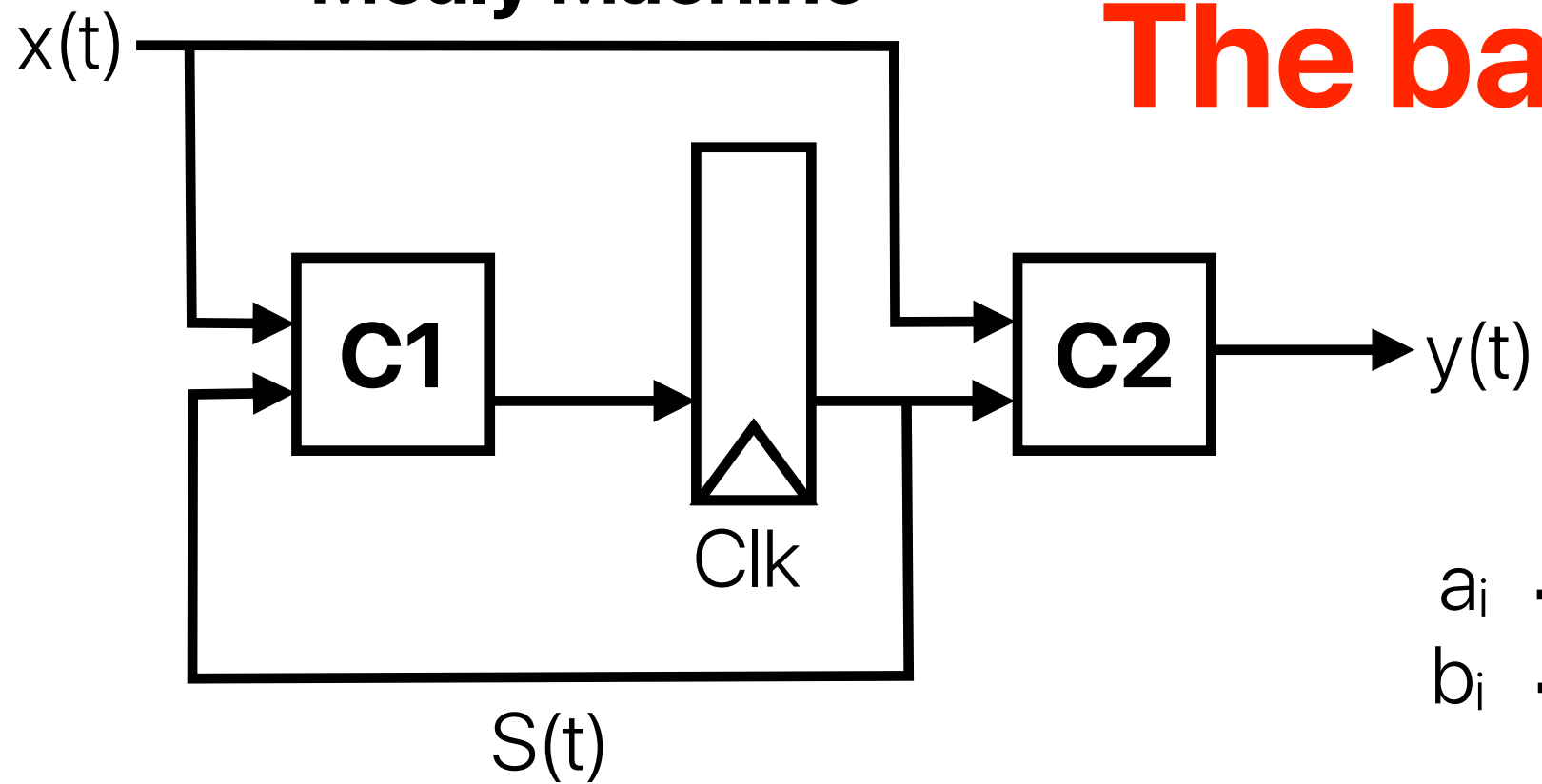


When sequential circuits meet datapath components (3)


Prof. Usagi

Serial Addder

Mealy Machine



The basic idea

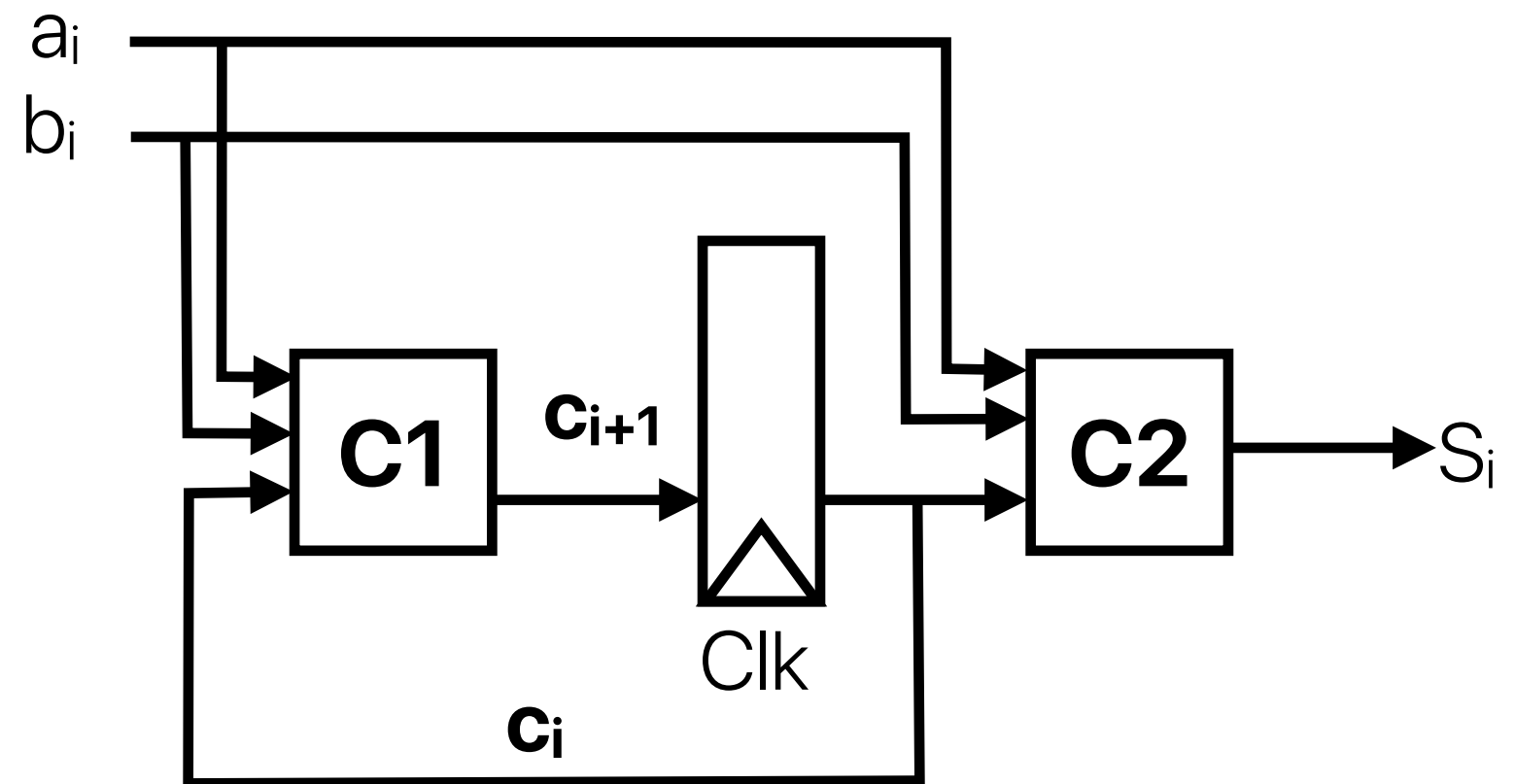


Feed a_i and b_i and generate s_i at time i . Where is c_i and c_{i+1} ?

Excitation Table of Serial Adder

a_i	b_i	c_i	c_{i+1}	s_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Excitation Table of Serial Adder


a_i	b_i	c_i	c_{i+1}	s_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

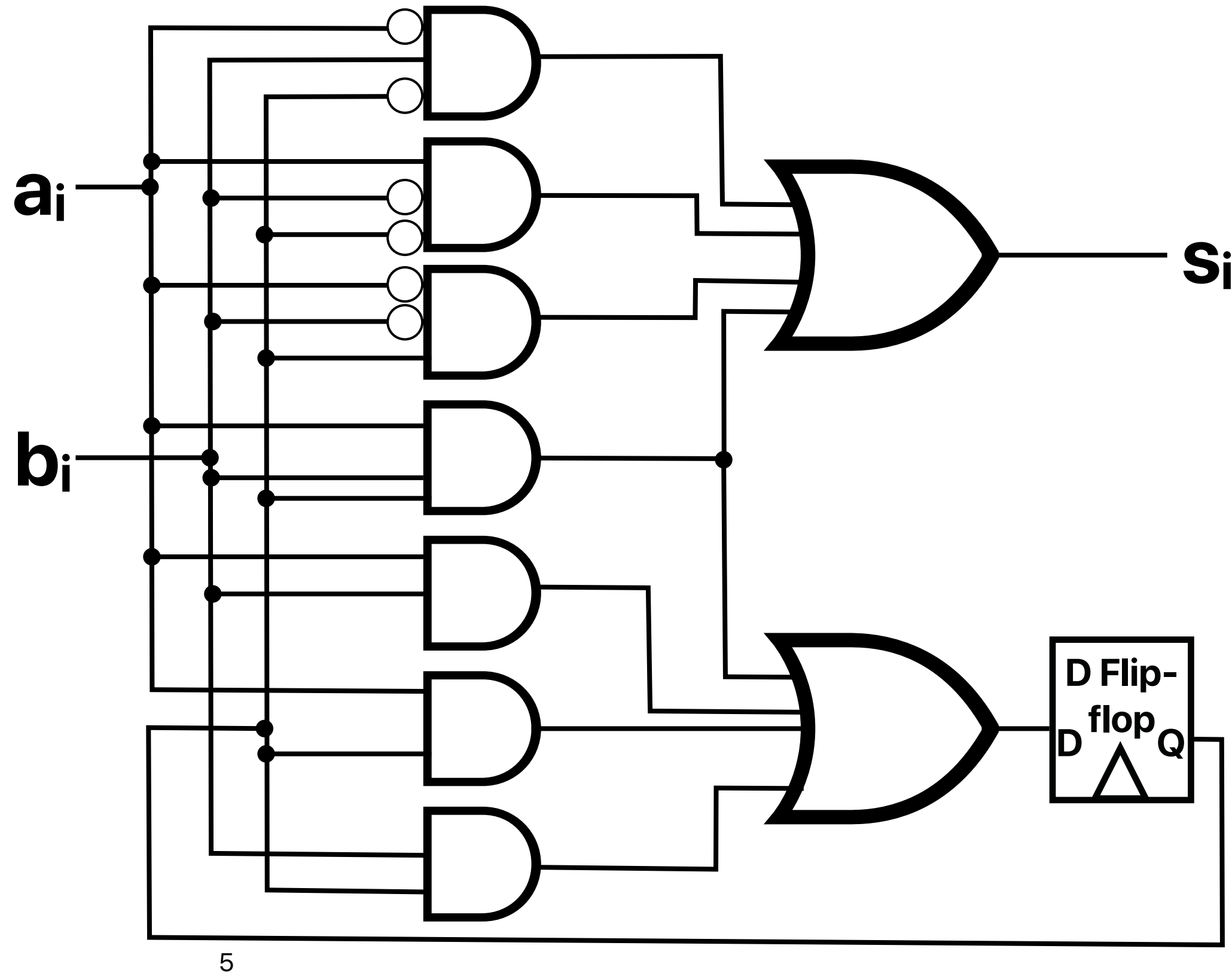


Pipelining

- Different parts of the hardware works on different requests/ commands simultaneously
- A clock signal controls and synchronize the beginning and the end of each part/**stage** of the work
- A **pipeline register** between different parts of the hardware to keep intermediate results necessary for the upcoming work
 - Register is basically an array of flip-flops!

Pipelining

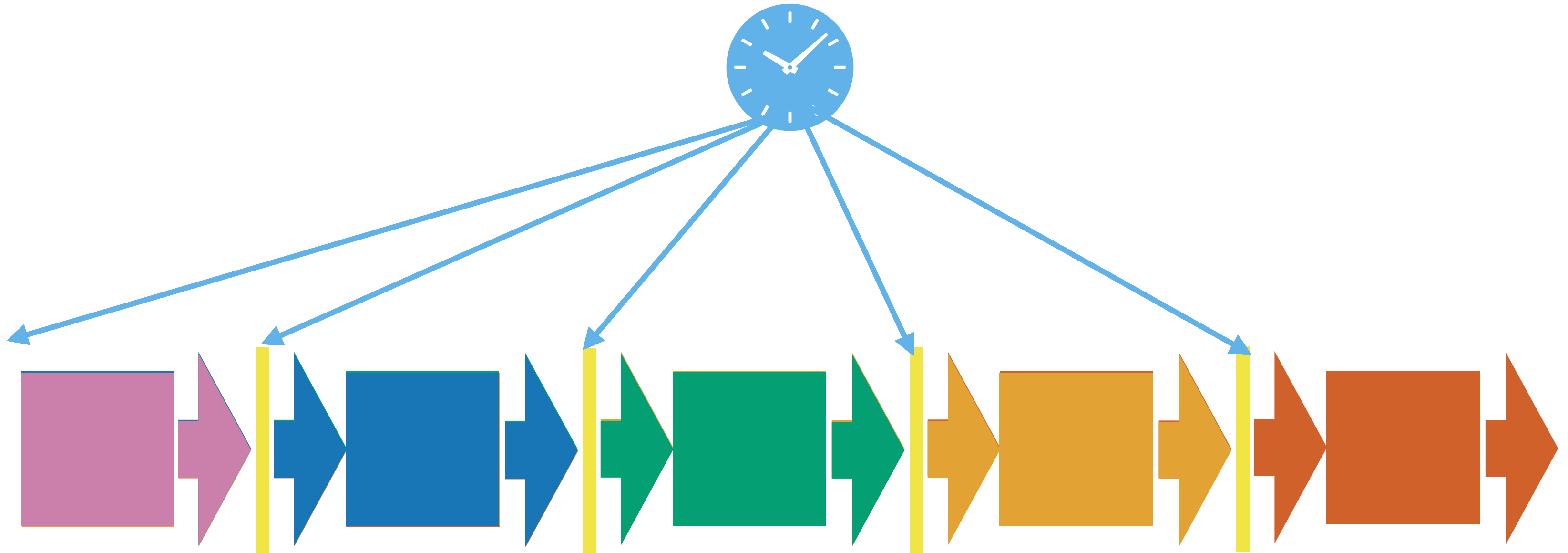


Pipelining a 4-bit serial adder

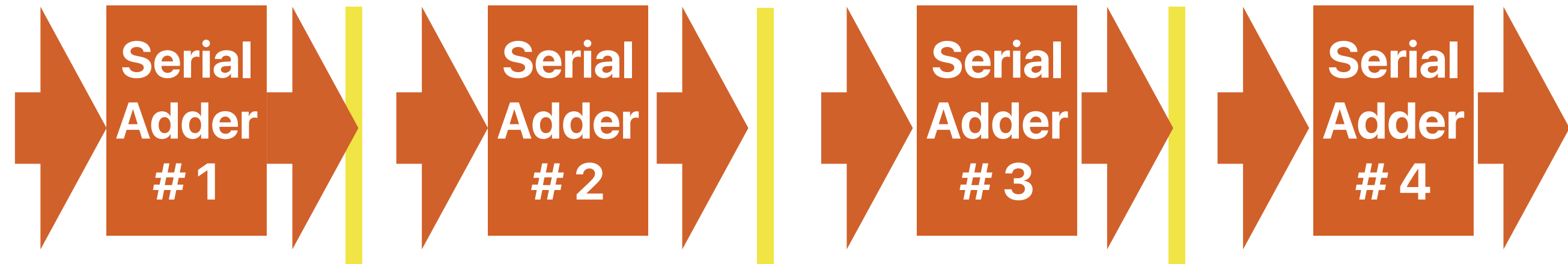

Pipelining a 4-bit serial adder

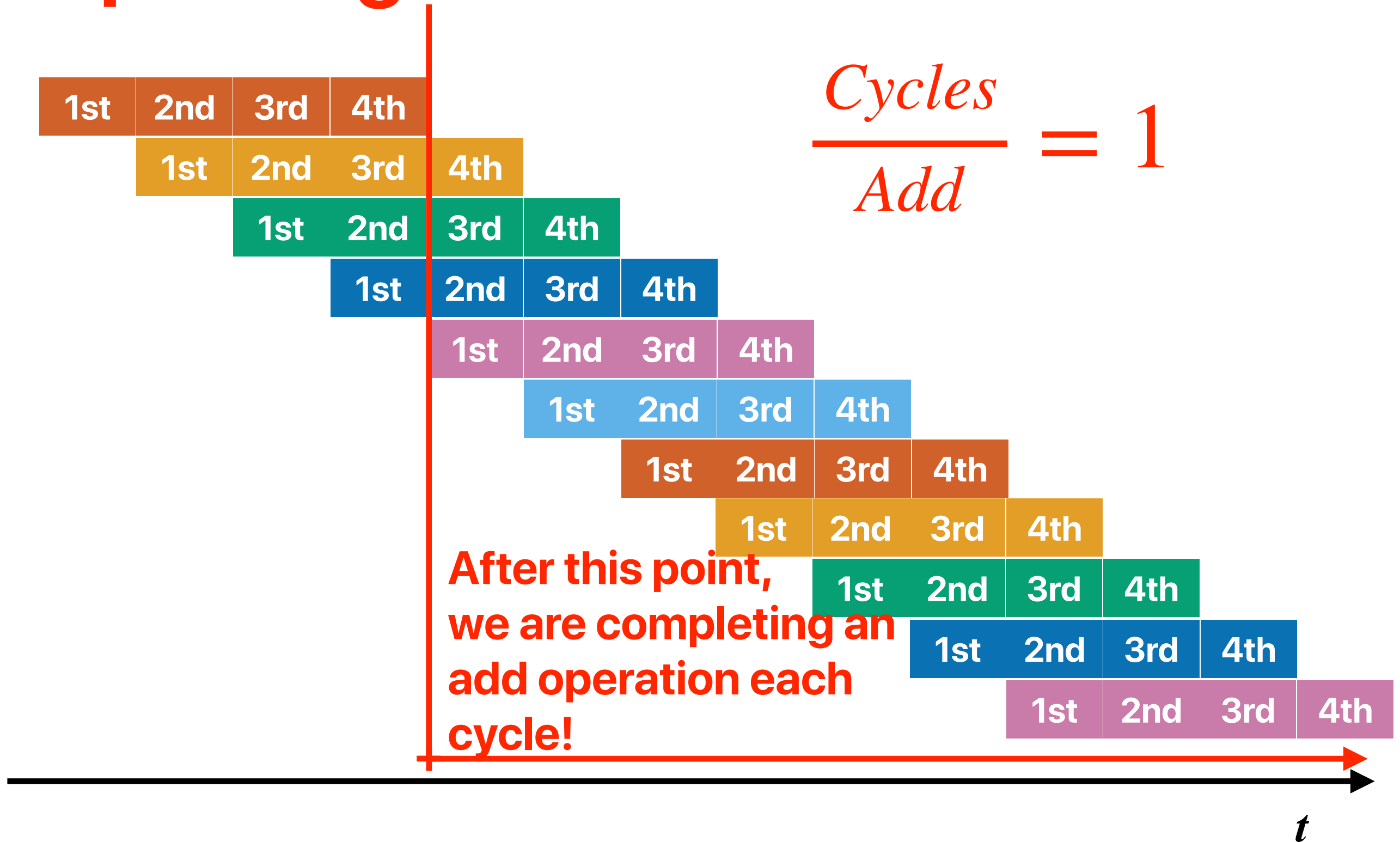

add a, b
add c, d
add e, f
add g, h
add i, j
add k, l
add m, n
add o, p
add q, r
add s, t
add u, v




Latency/Delay v.s. Bandwidth/Throughput

- Latency — the amount of time to finish an operation
 - access time
 - response time
- Throughput — the amount of work can be done within a given period of time
 - bandwidth (MB/Sec, GB/Sec, Mbps, Gbps)
 - IOPs
 - MFLOPs

Latency/Delay v.s. Throughput

	Toyota Prius	100 Gb Network
	<ul style="list-style-type: none">• 100 miles (161 km) from UCSD• 75 MPH on highway!• Max load: 374 kg = 2,770 hard drives (2TB per drive) 	<ul style="list-style-type: none">• 100 miles (161 km) from UCSD• Lightspeed! — $3 \times 10^8 \text{ m/sec}$• Max load: 4 lanes operating at 25GHz 
bandwidth	290GB/sec	100 Gb/s or 12.5GB/sec
latency	3.5 hours	2 Peta-byte over 167772 seconds = 1.94 Days
response time	You see nothing in the first 3.5 hours	You can start watching the movie as soon as you get a frame!

Recap: Shift "Right"

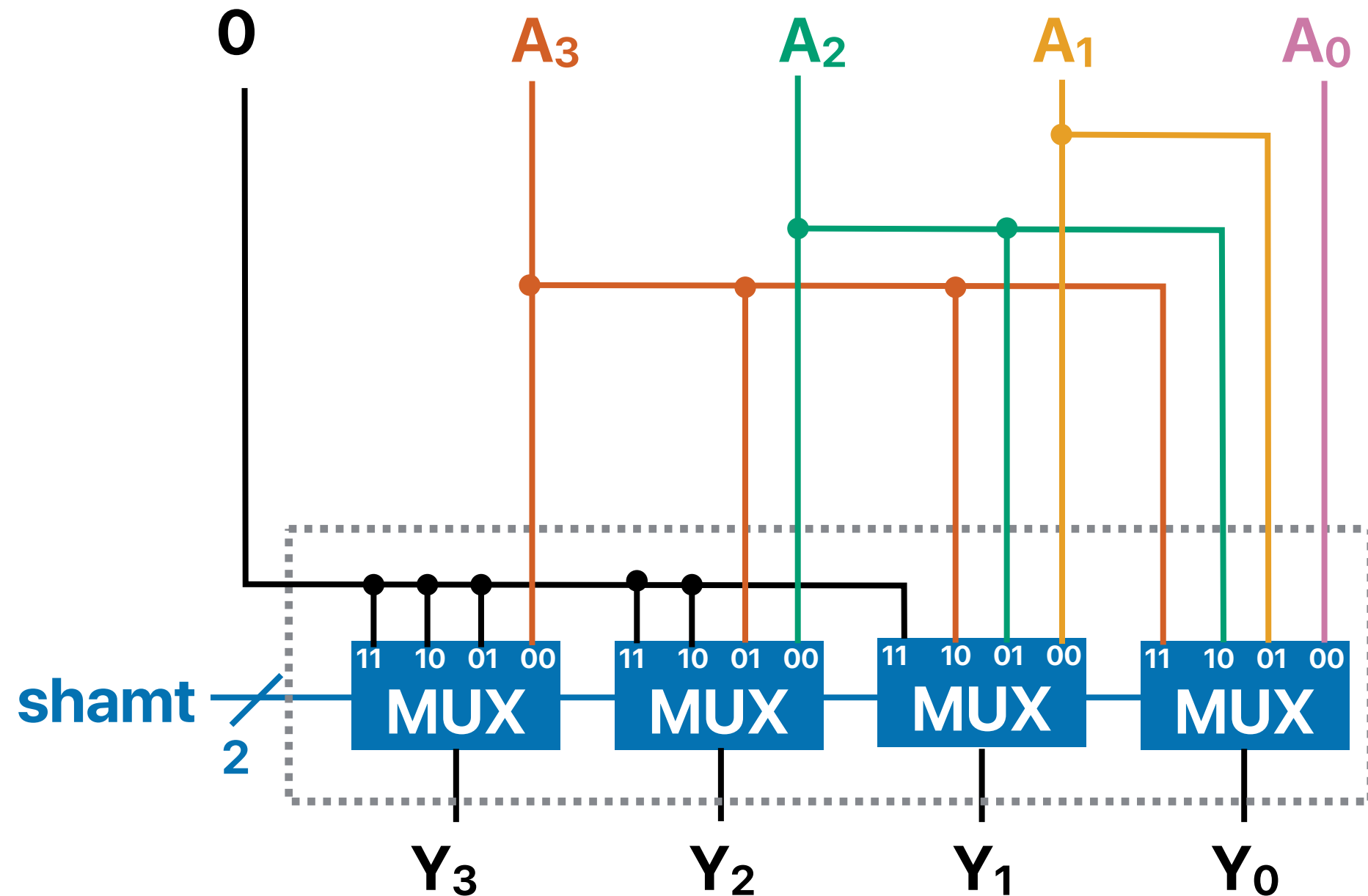

Based on the value of the selection input (shamt = shift amount)

Example:
if S = 11
then
Y₃ = 0
Y₂ = 0
Y₁ = 0
Y₀ = A₃

Example:
if S = 10
then
Y₃ = 0
Y₂ = 0
Y₁ = A₃
Y₀ = A₂

Example:
if S = 01
then
Y₃ = 0
Y₂ = A₃
Y₁ = A₂
Y₀ = A₁

The "chain" of multiplexers determines how many bits to shift


Shifters

Shift "Left"


Example:
if $S = 01$
then
 $Y_3 = A_2$
 $Y_2 = A_1$
 $Y_1 = A_0$
 $Y_0 = 0$

Example:
if $S = 10$
then
 $Y_3 = A_1$
 $Y_2 = A_0$
 $Y_1 = 0$
 $Y_0 = 0$

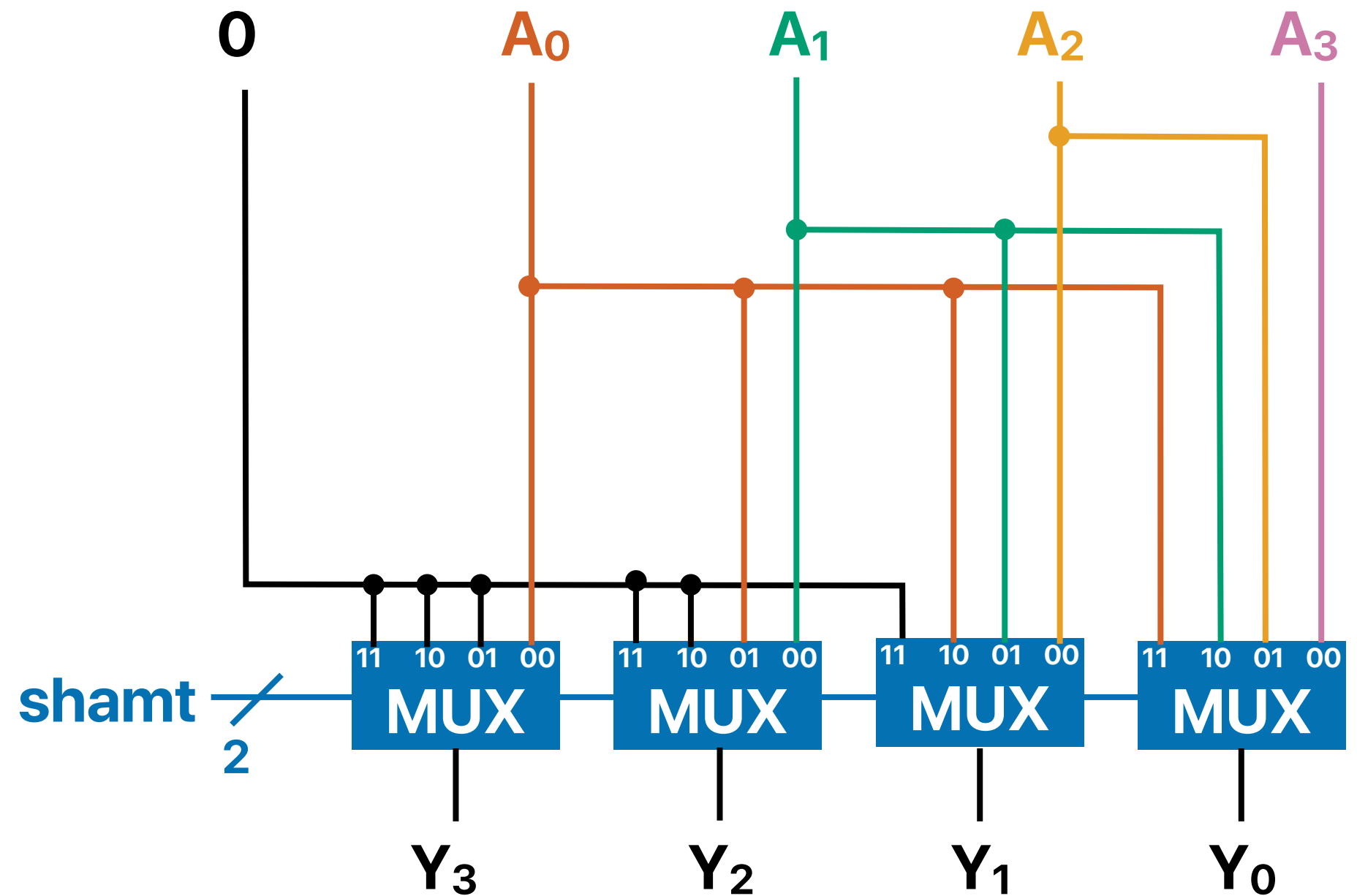Example:
if $S = 11$
then
 $Y_3 = A_0$
 $Y_2 = 0$
 $Y_1 = 0$
 $Y_0 = 0$



Generic Shifter

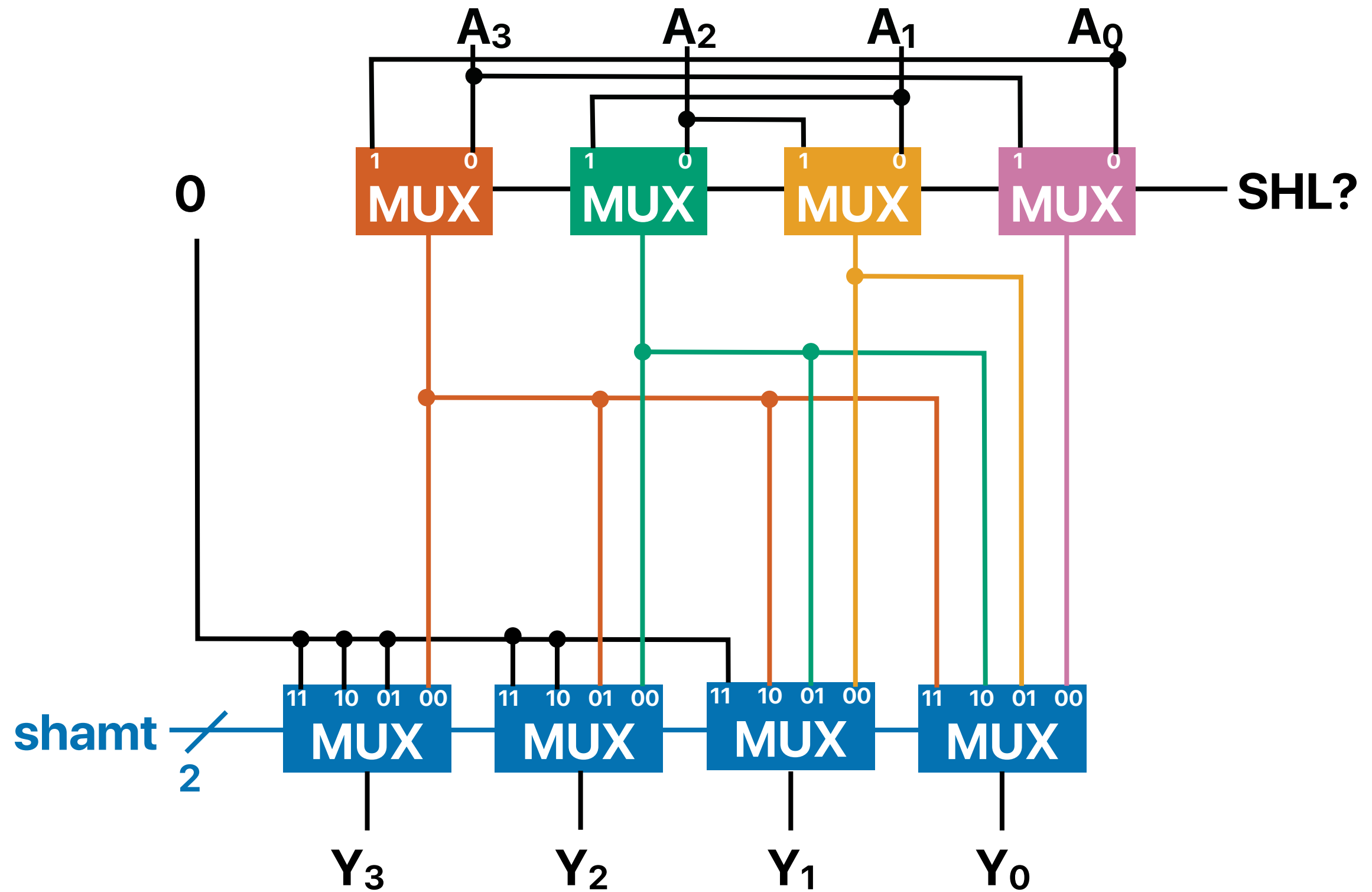

Multiplier


Binary multiplication

- Thinking about how you do this by hand in decimal!

				1	2	3	4							0	1	1	1
				×	5	6	7	8					×	1	1	0	0
<hr/>								<hr/>									
					9	8	7	2						0	0	0	0
				8	6	3	8						0	0	0	0	
		7	4	0	4							0	1	1	1		
6	1	7	0								0	1	1	1			
<hr/>								<hr/>									
7	0	0	6	6	5	2			1	0	1	0	1	0	0		

				a_3	a_2	a_1	a_0		
			\times	b_3	b_2	b_1	b_0		
pp1				a_3b_0	a_2b_0	a_1b_0	a_0b_0		
pp2				a_3b_1	a_2b_1	a_1b_1	a_0b_1	\emptyset	
pp3				a_3b_2	a_2b_2	a_1b_2	a_0b_2	\emptyset	\emptyset
pp4	a_3b_3	a_2b_3	a_1b_3	a_0b_3	\emptyset	\emptyset	\emptyset		
	p_7	p_6	p_5	p_4	p_3	p_2	p_1	p_0	

Shift and add

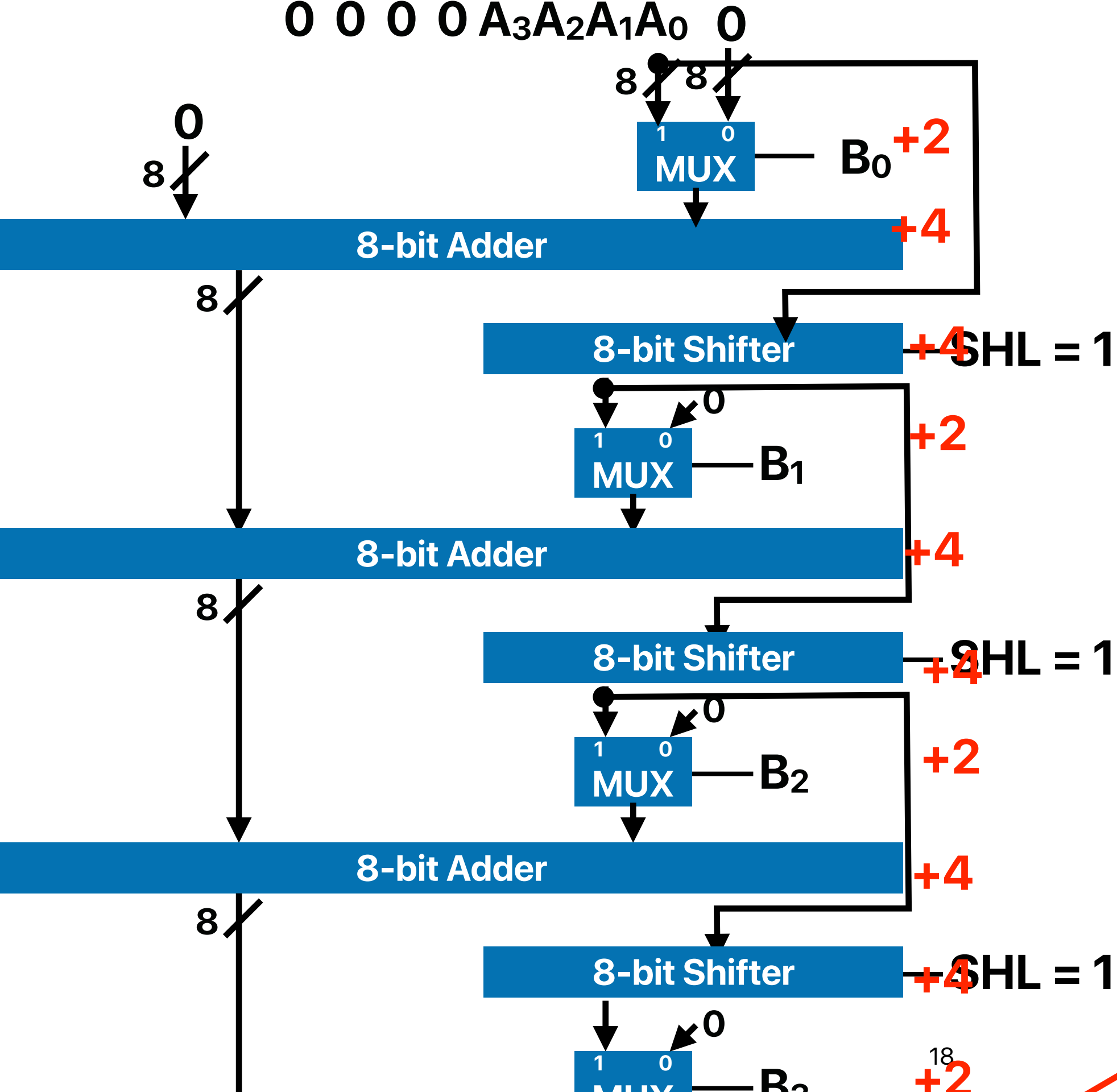


			a_3	a_2	a_1	a_0	
			\times	b_3	b_2	b_1	b_0
				a_3b_0	a_2b_0	a_1b_0	a_0b_0
				a_3b_1	a_2b_1	a_1b_1	a_0b_1
				a_3b_2	a_2b_2	a_1b_2	a_0b_2
				a_3b_3	a_2b_3	a_1b_3	a_0b_3
7	p_6	p_5	p_4	p_3	p_2	p_1	p_0

— 36 gate delays


+4

+2


4-bit serial shift-and-add multiplier

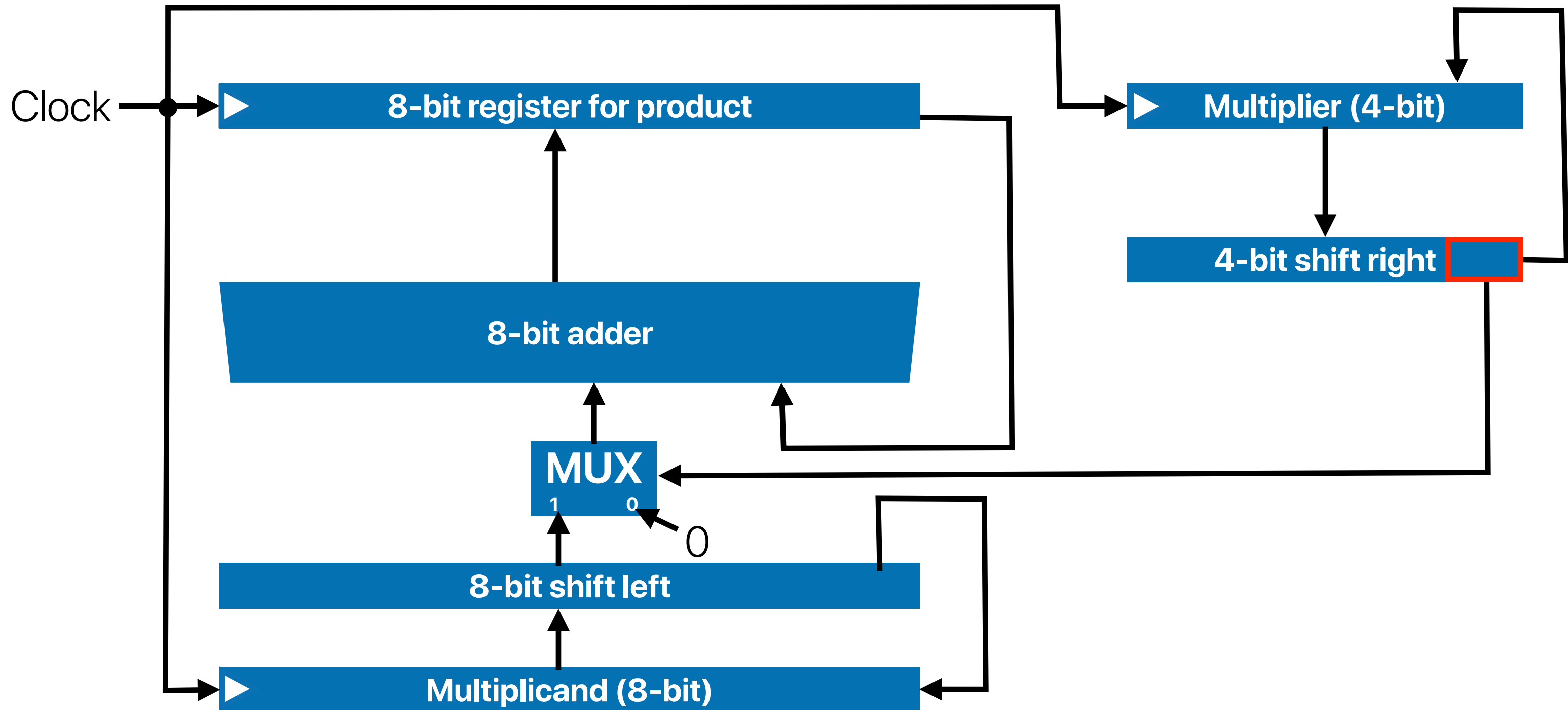

Array style

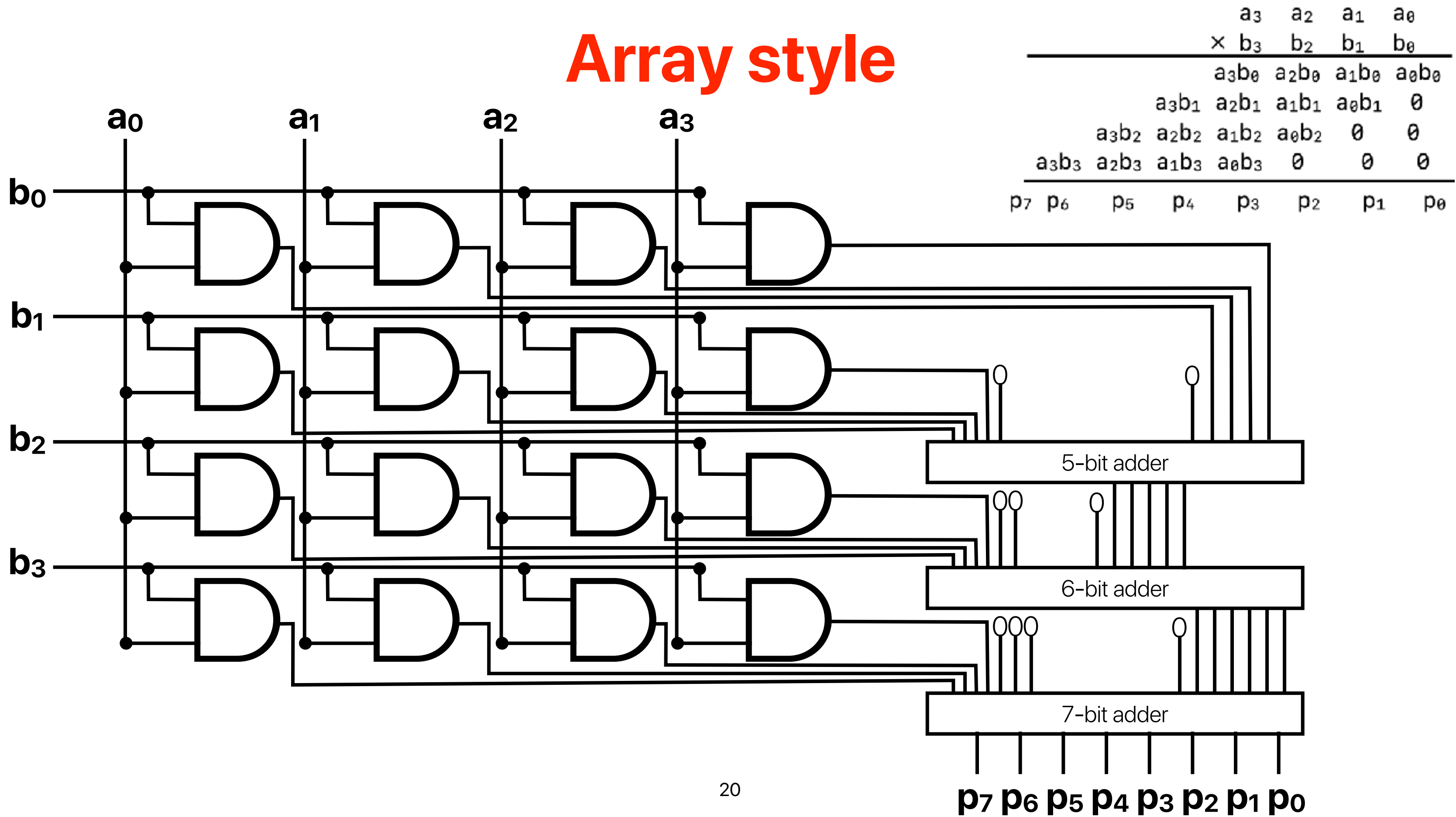

Parallel-tree Multiplier

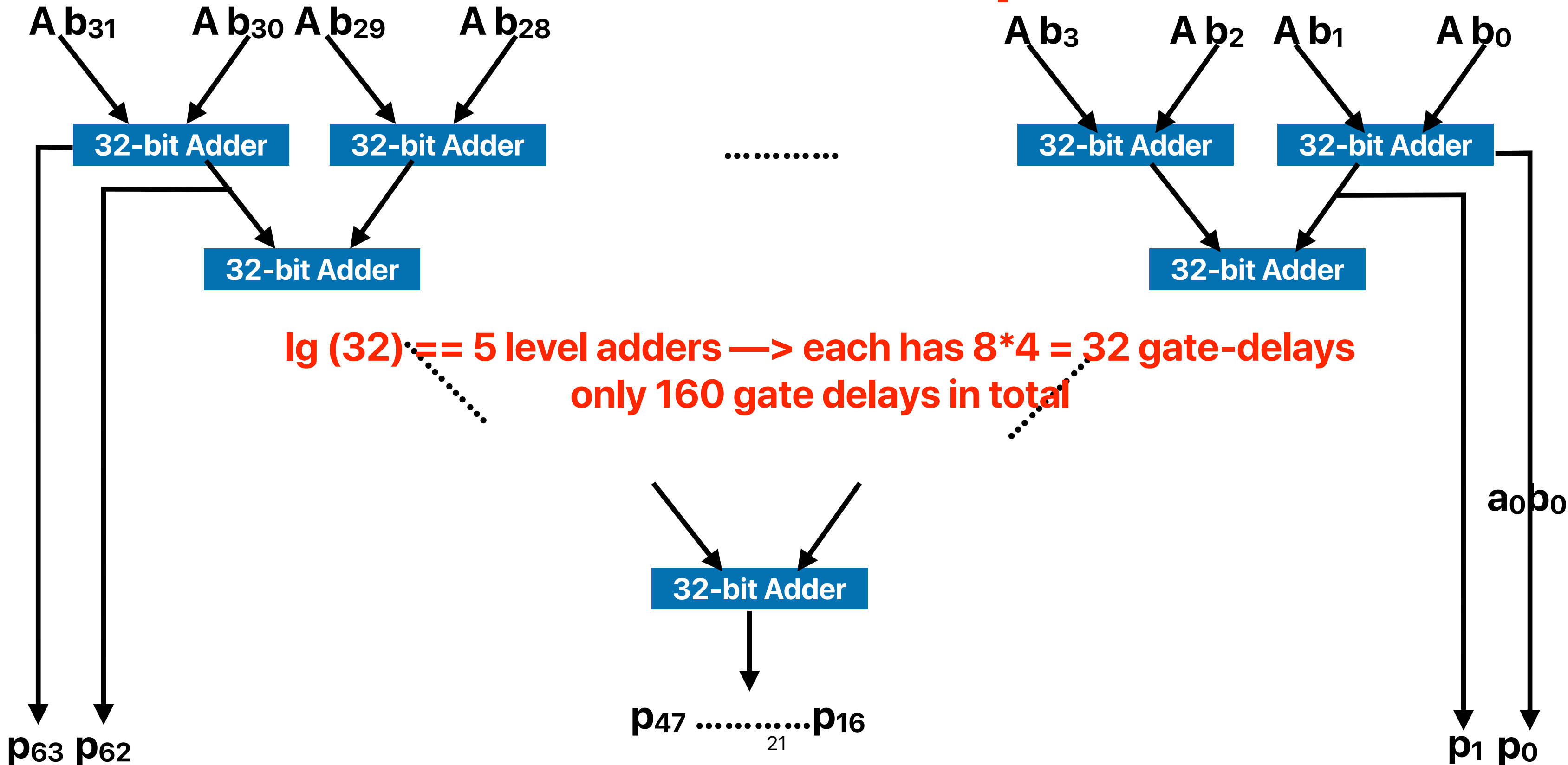

Divider

Division of positive binary numbers

- Repeated subtraction
 - Set quotient to 0
 - Repeat while (dividend \geq divisor)
 - Subtract divisor from dividend
 - Add 1 to quotient
 - When dividend $<$ divisor:
 - Remainder = dividend
 - Quotient is correct

Put everything all together!
ALU — arithmetic logic unit

Announcement

- Assignment 2 due **TONIGHT**
 - All challenge questions up to **3.5**
- Reading quiz 5 due 4/28 **BEFORE** the lecture
 - Under iLearn > reading quizzes
- Lab 3 due 4/30
 - Watch the video and read the instruction **BEFORE** your session
 - There are links on both course webpage and iLearn lab section
 - Submit through iLearn > Labs
- Midterm on 5/7 during the lecture time, access through iLearn — no late submission is allowed — make sure you will be able to take that at the time
- Check your grades in iLearn

Electrical Computer Science Engineering

120A

つづく

