

Verilog

Prof. Usagi

Turn a design into Verilog

Verilog

- Verilog is a Hardware Description Language (HDL)
 - Used to describe & model the operation of digital circuits.
 - Specify simulation procedure for the circuit and check its response — simulation requires a logic simulator.
 - Synthesis: transformation of the HDL description into a physical implementation (transistors, gates)
 - When a human does this, it is called logic design.
 - When a machine does this, it is called synthesis.
- In this class, we use Verilog to implement and verify your processor.
- C/Java like syntax

Data types in Verilog

- Bit vector is the only data type in Verilog
- A bit can be one of the following
 - 0: logic zero
 - 1: logic one
 - X: unknown logic value, don't care
 - Z: high impedance, floating
- Bit vectors expressed in multiple ways
 - 4-bit binary: 4 ' b11_10 (_ is just for readability)
 - 16-bit hex: 16 ' h034f
 - 32-bit decimal: 32 ' d270


Operators

Arithmetic		Logical		Bitwise		Relational	
+	addition	!	not	~	not	>	greater than
-	substraction	&&	and	&	and	<	less than
*	multiplication		or		or	>=	greater or equal
/	division			^	xor	<=	less or equal
%	modulus			~^	xnor	==	equal (doesn't work if there is x, z)
**	power			<<	shift left	!=	not equal
				>>	shift right	===	really equal
Concatenation		{ } (e.g., {1b'1,1b'0} is 2b'10)		Replication		{ { } } (e.g., {4{1b'0}} is 4b'0)	
Conditional		condition ? value_if_true : value_if_false					

Wire and Reg

- wire is used to denote a hardware net — “continuously assigned” values and do not store
 - single wire
`wire my_wire;`
 - array of wires
`wire[7:0] my_wire;`
- reg is used for procedural assignments — values that store information until the next value assignment is made.
 - again, can either have a single reg or an array
`reg[7:0] result; // 8-bit reg`
 - reg is not necessarily a hardware register
 - you may consider it as a variable in C

Revisit the 4-bit adder

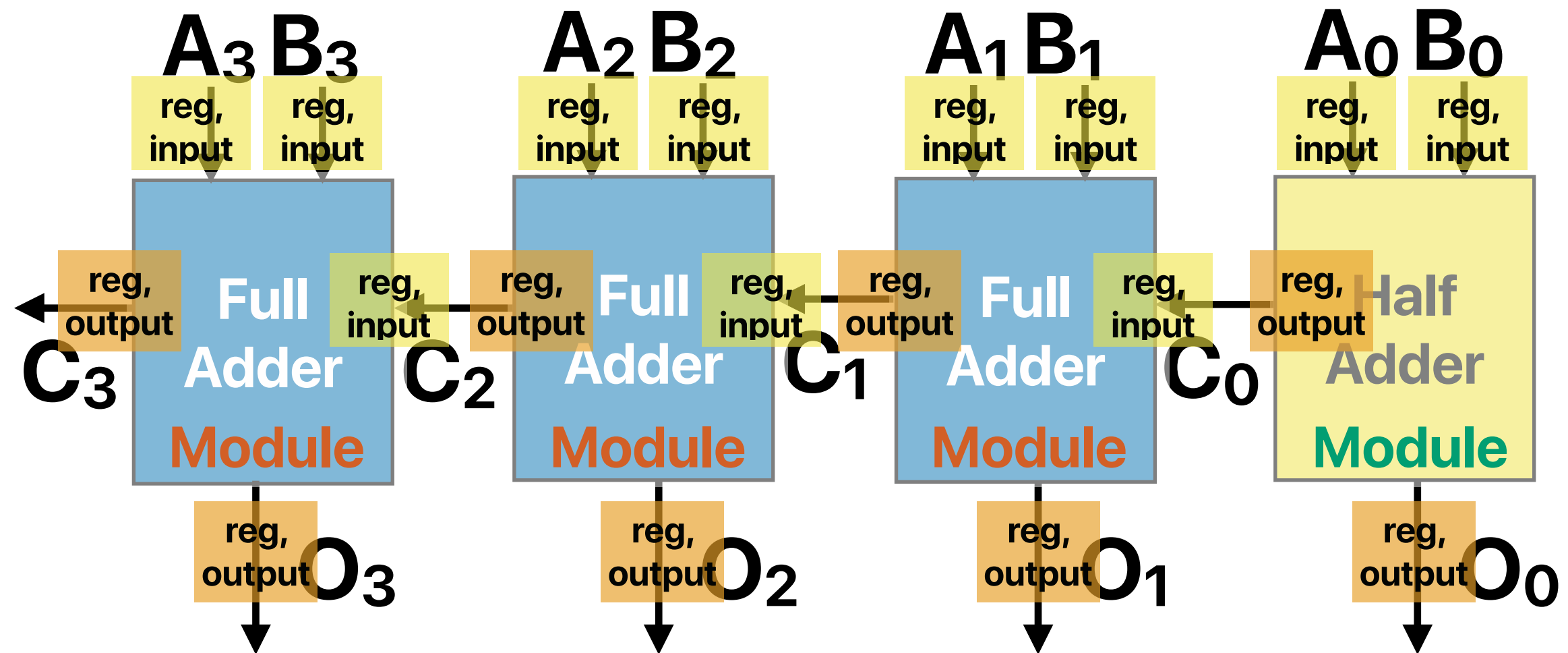

Half adder

Input		Output	
A	B	Out	Cout
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$\text{Out} = A'B + AB'$$
$$\text{Cout} = AB$$

```
module HA(
    input a,
    input b,
    output cout,
    output out );
    assign out = (~a & b) | (a & ~b);
    assign cout = a&b;
endmodule
```

Input ports

Output ports

Full adder


$$\text{Out} = A'BCin' + AB'cin' + A'B'cin + ABCin$$

$$\text{Cout} = ABCin' + A'BCin + AB'cin + ABCin$$

Input			Output	
A	B	Cin	Out	Cout
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	1	1

```
module FA( input a,
            input b,
            input cin,
            output cout,
            output out );
    assign out = (~a&b&~cin)|(a&~b&~cin)|(~a&~b&cin)|(a&b&cin);
    assign cout = (a&b&~cin)|(~a&b&cin)|(a&~b&cin)|(a&b&cin);;
endmodule
```

The Adder

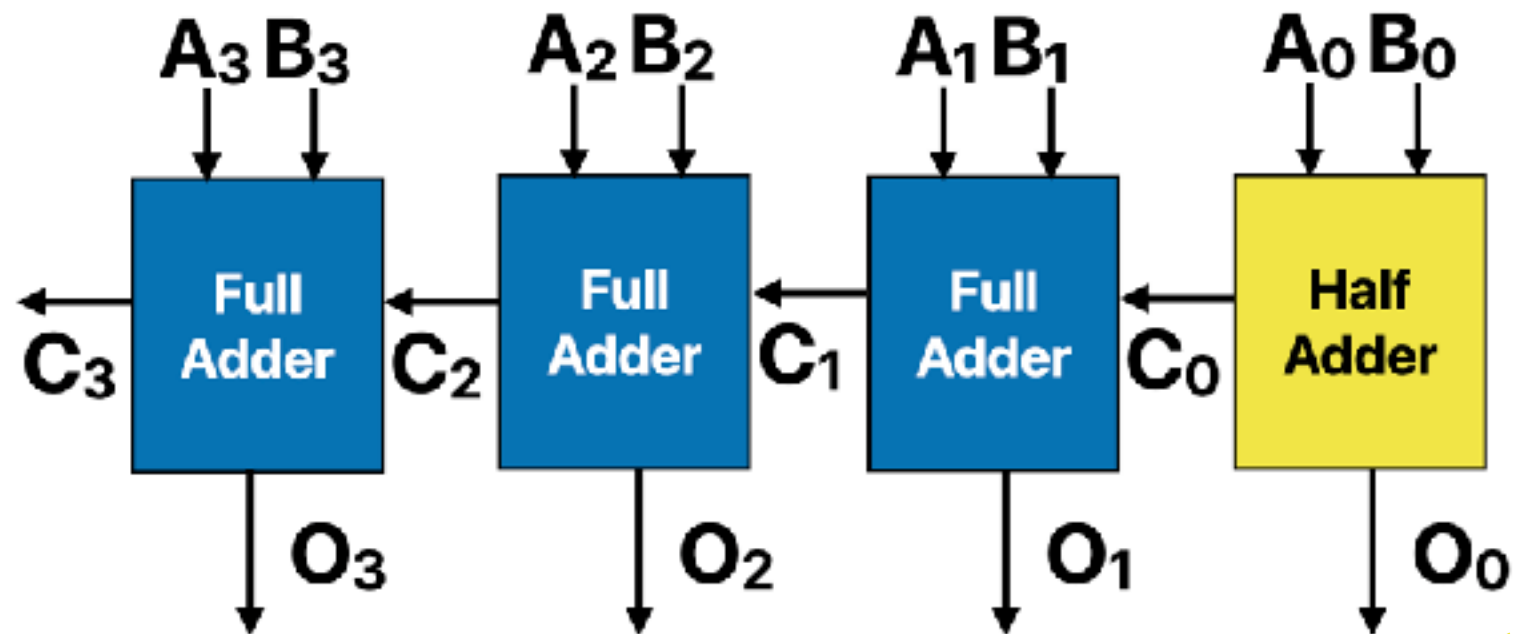

```
module FA( input a,
           input b,
           input cin,
           output cout,
           output out );
    assign out = (~a&b&~cin)|(a&~b&~cin)|(~a&~b&cin)|(a&b&cin);
    assign cout = (a&b&~cin)|(~a&b&cin)|(a&~b&cin)|(a&b&cin);;
endmodule
```

```
module HA( input a,
           input b,
           output cout,
           output out );
    assign out = (~a & b)|(a & ~b);
    assign cout = a&b;
endmodule
```

```
module adder( input[3:0] A,
              input[3:0] B,
              output[3:0] O,
              output cout);
```

```
    wire [2:0] carries;
```

```
    HA ha0(.a(A[0]), .b(B[0]), .out(O[0]), .cout(carries[0]));
```

```
    FA fa1(.a(A[1]), .b(B[1]), .cin(carries[0]), .out(O[1]), .cout(carries[1]));
```

```
    FA fa2(.a(A[2]), .b(B[2]), .cin(carries[1]), .out(O[2]), .cout(carries[2]));
```

```
    FA fa3(.a(A[3]), .b(B[3]), .cin(carries[2]), .out(O[3]), .cout(cout));
```

```
endmodule
```

Connecting ports by name yields clearer and less buggy code.

Always block — combinational logic

- Executes when the condition in the sensitivity list occurs

```
module FA( input a,
           input b,
           input cin,
           output cout,
           output out );
always@(a or b or cin)
begin          // the following block changes outputs when a, b or cin changes
assign out = (~a&b&~cin)|(a&~b&~cin)|(~a&~b&cin)|(a&b&cin);
assign cout = (a&b&~cin)|(~a&b&cin)|(a&~b&cin)|(a&b&cin);;
end
endmodule
```

Always block — sequential logic

- Executes when the condition in the sensitivity list occurs

```
always@(posedge clk) // the following block only triggered by a positive clock
begin
...
...
end
```

Blocking and non-blocking

- Inside an always block, = is a blocking assignment
 - assignment happens immediately and affect the subsequent statements in the always block
- <= is a non-blocking assignment
 - All the assignments happens at the end of the block
- Assignment rules:
 - The left hand side, LHS, must be a reg.
 - The right hand side, RHS, may be a wire, a reg, a constant, or expressions with operators using one or more wires, regs, and constants.

Initially, a = 2, b = 3

```
reg a[3:0];
reg b[3:0];
reg c[3:0];
always @(posedge clock)
begin
a <= b;
c <= a;
end
Afterwards: a = 3 and c = 2
```

```
reg a[3:0];
reg b[3:0];
reg c[3:0];
always @(*)
begin
a = b;
c = a;
end
Afterwards: a = 3 and c = 3
```

"Always blocks" permit more advanced sequential idioms

```
module mux4( input a,b,c,d,
             input [1:0] sel,
             output out );

reg out;
always @( * )
begin
    if ( sel == 2'd0 )
        out = a;
    else if ( sel == 2'd1 )
        out = b;
    else if ( sel == 2'd2 )
        out = c;
    else if ( sel == 2'd3 )
        out = d;
    else
        out = 1'bx;
    end
endmodule
```

```
module mux4( input a,b,c,d,
             input [1:0] sel,
             output out );

reg out;
always @( * )
begin
    case ( sel )
        2'd0 : out = a;
        2'd1 : out = b;
        2'd2 : out = c;
        2'd3 : out = d;
        default : out = 1'bx;
    endcase
end
endmodule
```

Initial block

- Executes only once in beginning of the code

```
initial
```

```
begin
```

```
...
```

```
...
```

```
end
```

Testing the adder!

```
`timescale 1ns/1ns // Add this to the top of your file to set time scale
module testbench();
reg [3:0] A, B;
reg C0;
wire [3:0] S;
wire C4;
adder uut (.B(B), .A(A), .sum(S), .cout(C4)); // instantiate adder

initial
begin
A = 4'd0; B = 4'd0; C0 = 1'b0;
#50 A = 4'd3; B = 4'd4; // wait 50 ns before next assignment
#50 A = 4'b0001; B = 4'b0010; // don't use #n outside of testbenches
end

endmodule
```


Parameterize your module

```
module adder #(parameter WIDTH=32)(  
    input[WIDTH-1:0]  A,  
    input[WIDTH-1:0]  B,  
    output[WIDTH-1:0] O,  
    output cout);  
  
endmodule
```

Coding guides

- When modeling sequential logic, use nonblocking assignments.
- When modeling latches, use nonblocking assignments.
- When modeling combinational logic with an always block, use blocking assignments.
- When modeling both sequential and combinational logic within the same always block, use nonblocking assignments.
- Do not mix blocking and nonblocking assignments in the same always block.
- Do not make assignments to the same variable from more than one always block.
- Use \$strobe to display values that have been assigned using nonblocking assignments.
- Do not make assignments using #0 delays.

http://www.sunburst-design.com/papers/CummingsSNUG2000SJ_NBA.pdf