

# Sequential Circuits (2)

Prof. Usagi

# Recap: Combinational v.s. sequential logic

- Combinational logic
  - The output is a pure function of its current inputs
  - The output doesn't change regardless how many times the logic is triggered — Idempotent
- Sequential logic
  - The output depends on current inputs, previous inputs, their history





**Sequential circuit has memory!**

# Recap: Theory behind each


- A **Combinational logic** is the implementation of a **Boolean Algebra** function with only Boolean Variables as their inputs
- A **Sequential logic** is the implementation of a **Finite-State Machine**
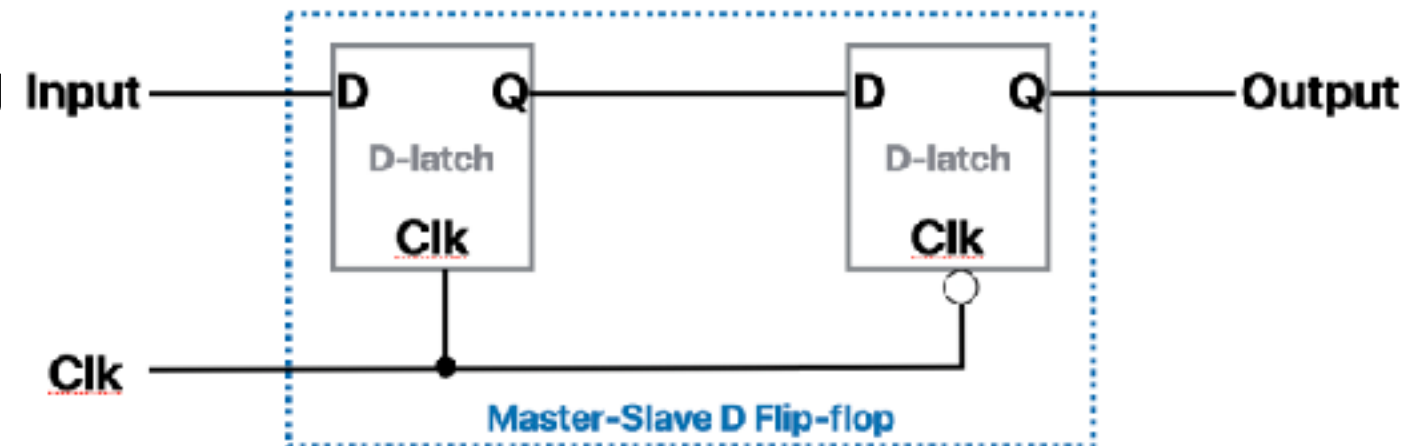   
# Recap: 4-different types of bit storage


- SR-latch
  - $S = 1$  sets  $Q = 1$
  - $R = 1$  sets  $Q = 0$
  - Problem:  $S = 1, R = 1, Q = \text{undefined}$
- Level-sensitive SR-latch
  - $S, R$  only become effective when  $C = 1$
  - Problem: avoid the case of signal oscillation, but cannot avoid the "intensional" 1,1 inputs
- D-latch
  - SR can never be 11 if the Clk is set appropriately
  - Problem: D signal needs to be stably long enough to set the memory
- D-flip-flop
  - Only loads the value into memory in the beginning of the rising edge. Values can hold for a complete clock cycle
  - Problem: more gates



# Positive-edge-triggered D flip-flop

 

# Recap: Clock signal

 

- Clock -- Pulsing signal for enabling latches; ticks like a clock
- Synchronous circuit: sequential circuit with a clock
- Clock period: time between pulse starts
  - Above signal: period = 20 ns
- Clock cycle: one such time interval
  - Above signal shows 3.5 clock cycles
- Clock duty cycle: time clock is high
  - 50% in this case
- Clock frequency:  $1/\text{period}$ 
  - Above :  $\text{freq} = 1 / 20\text{ns} = 50\text{MHz}$ ;

# Outline






- From FSM to circuit
- Canonical forms of FSMs
- When sequential circuits meets datapath components

**Let's learn how to design  
sequential circuits!**








Poll close in 1:30
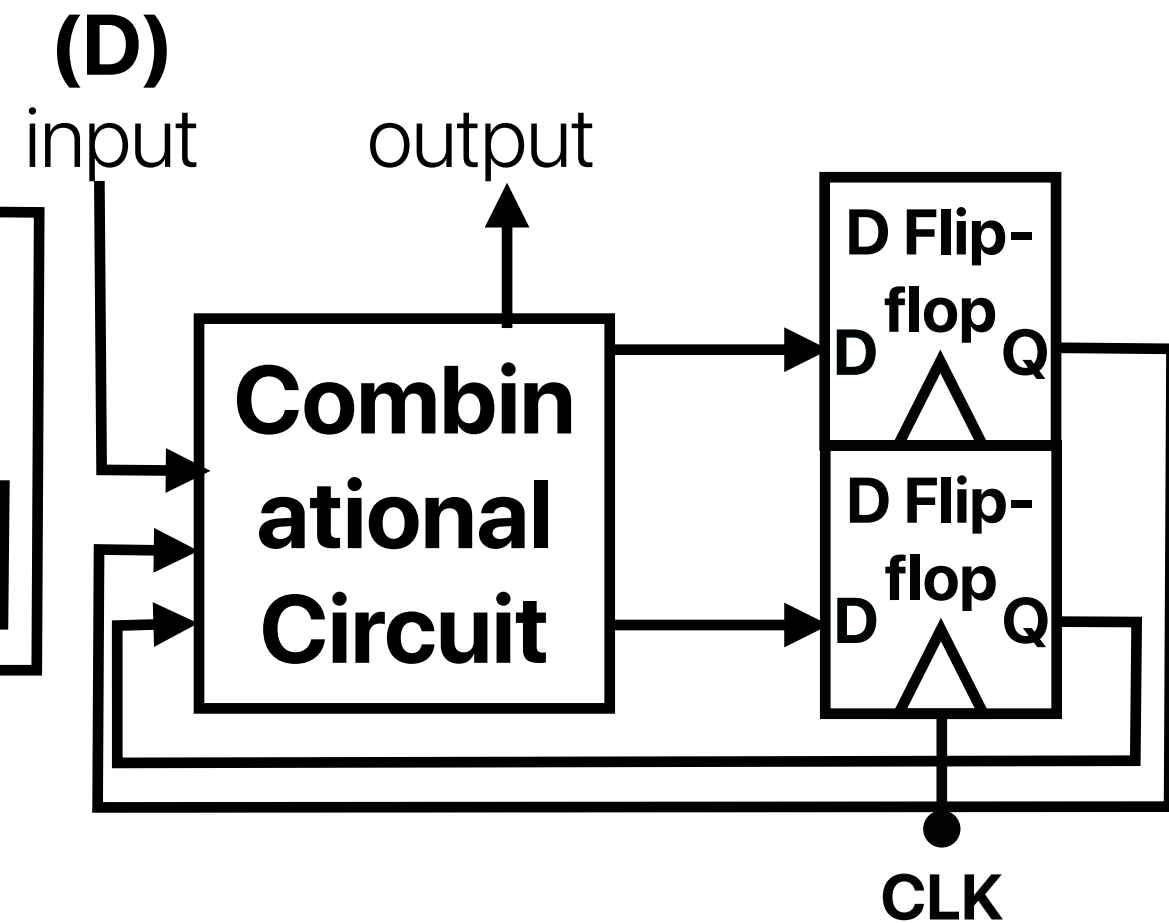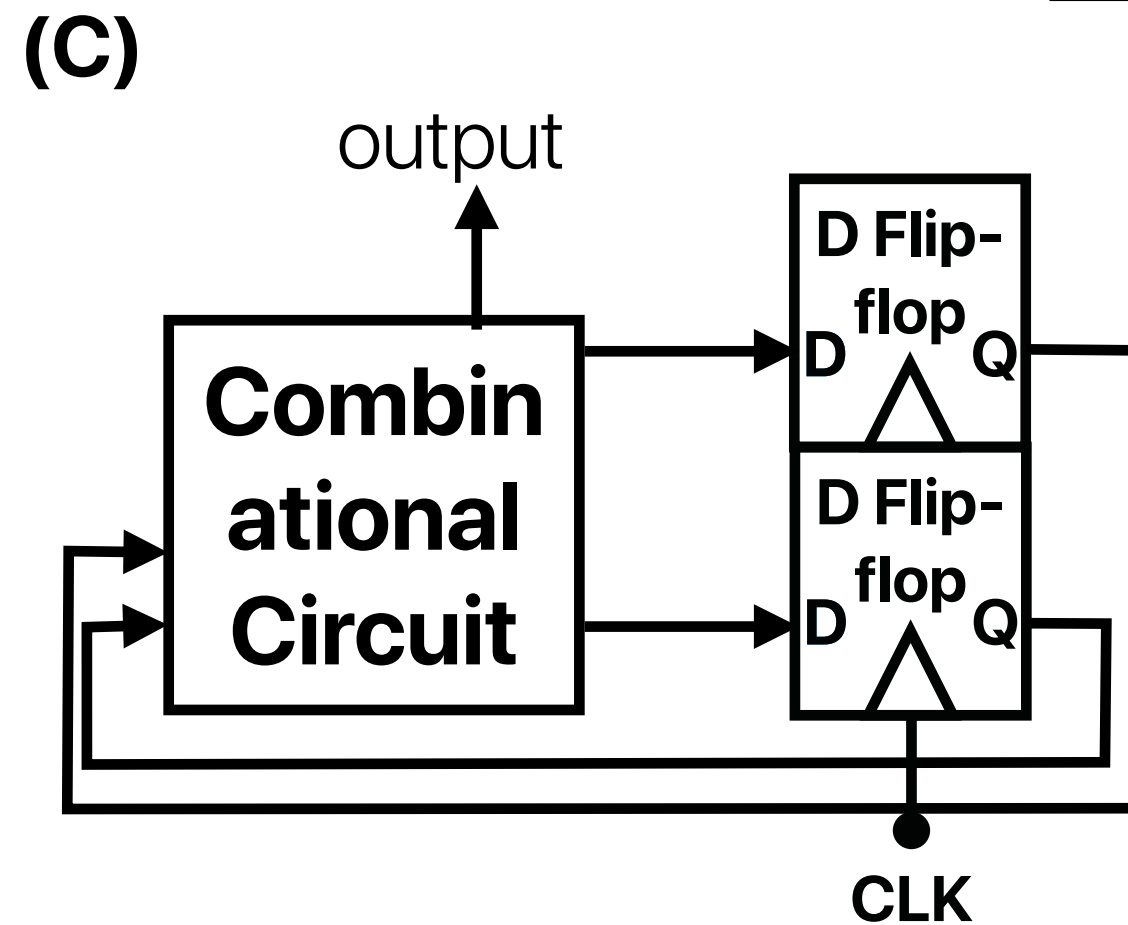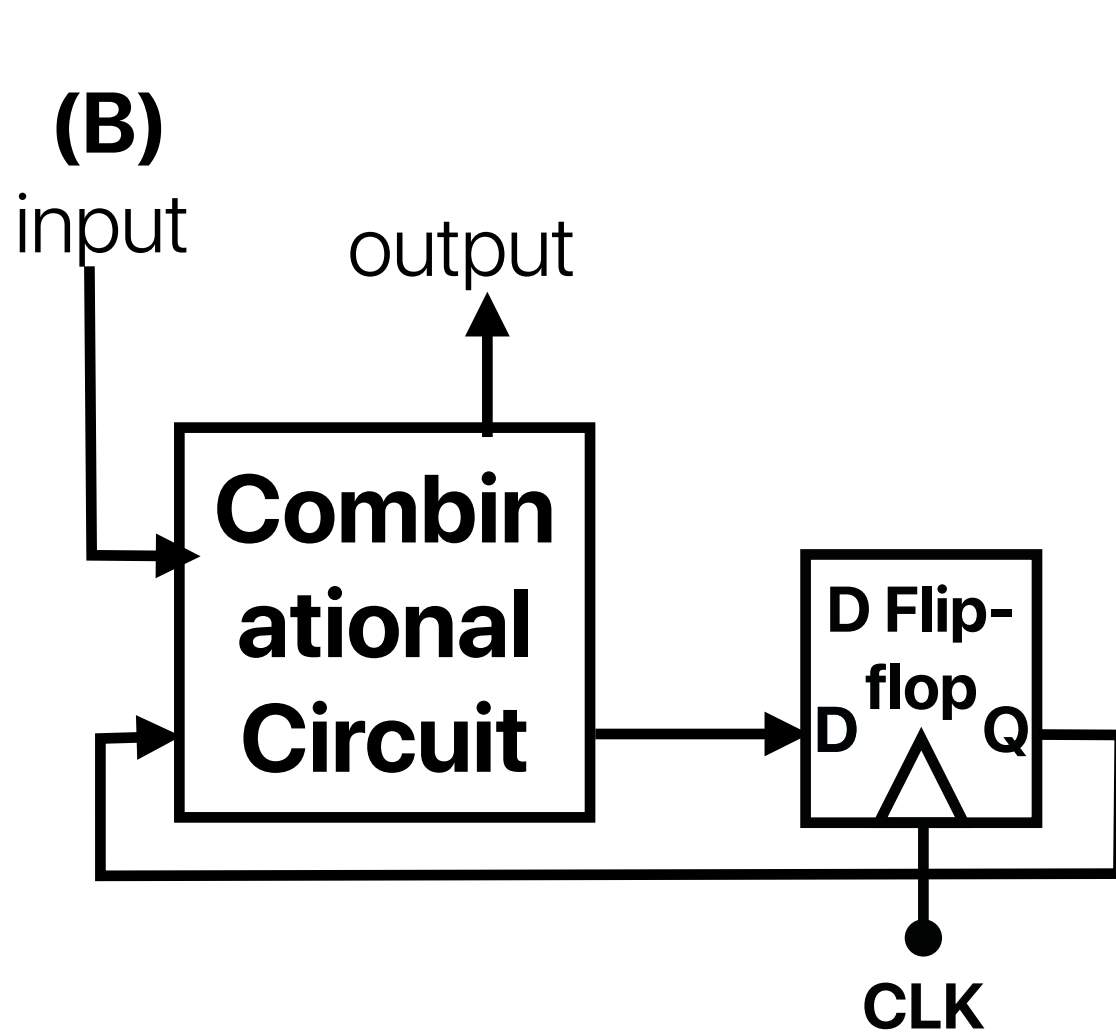  
# Which is the most likely circuit realization of Life on Mars


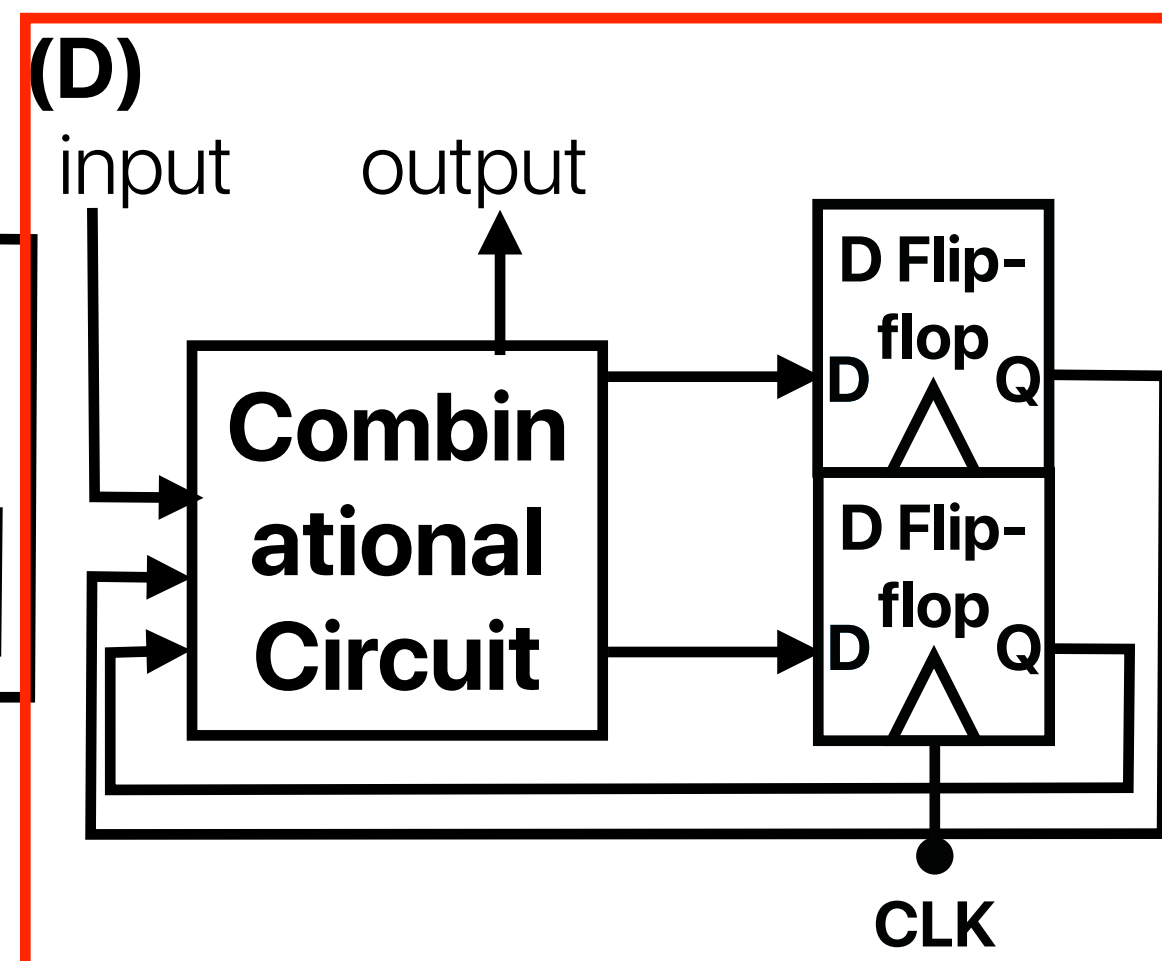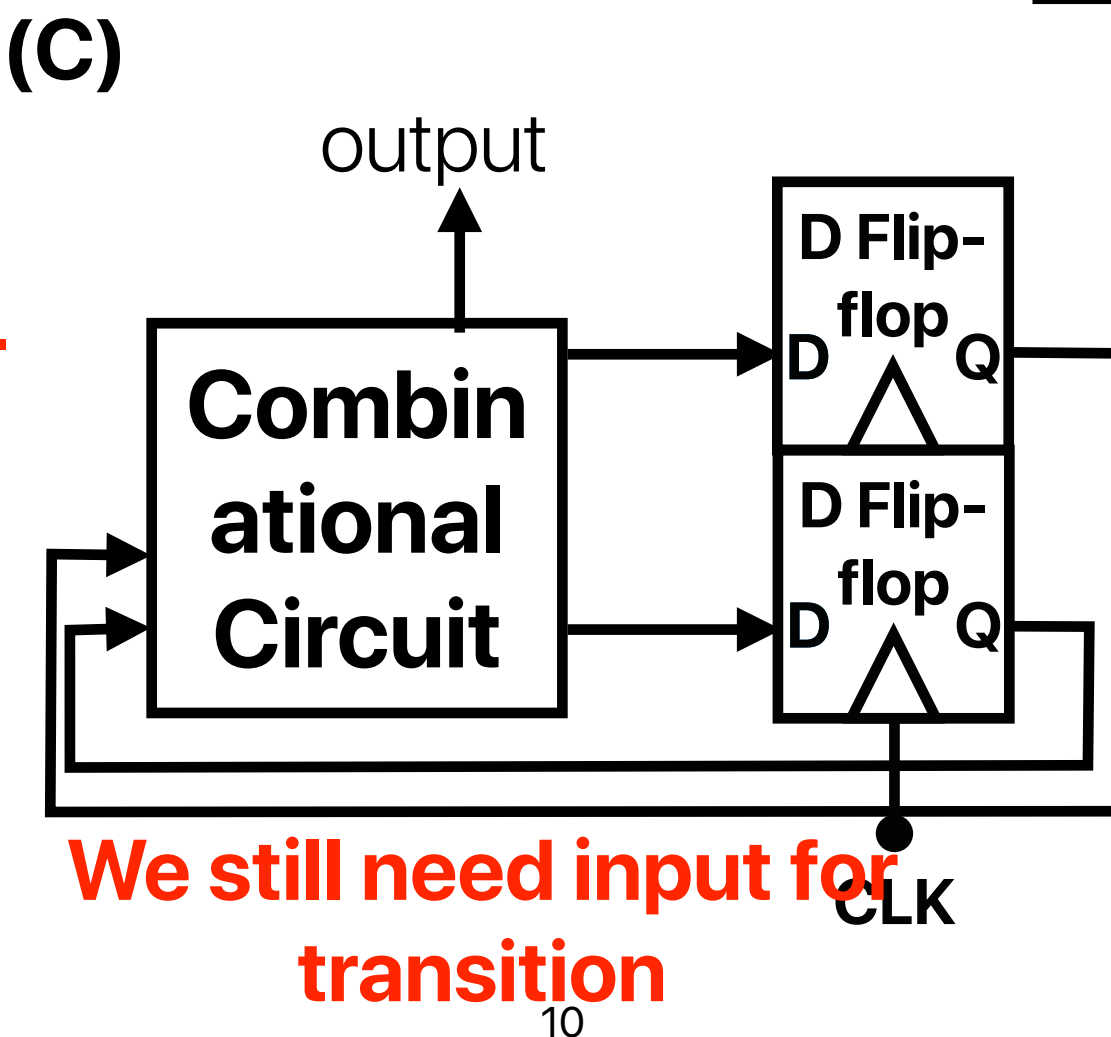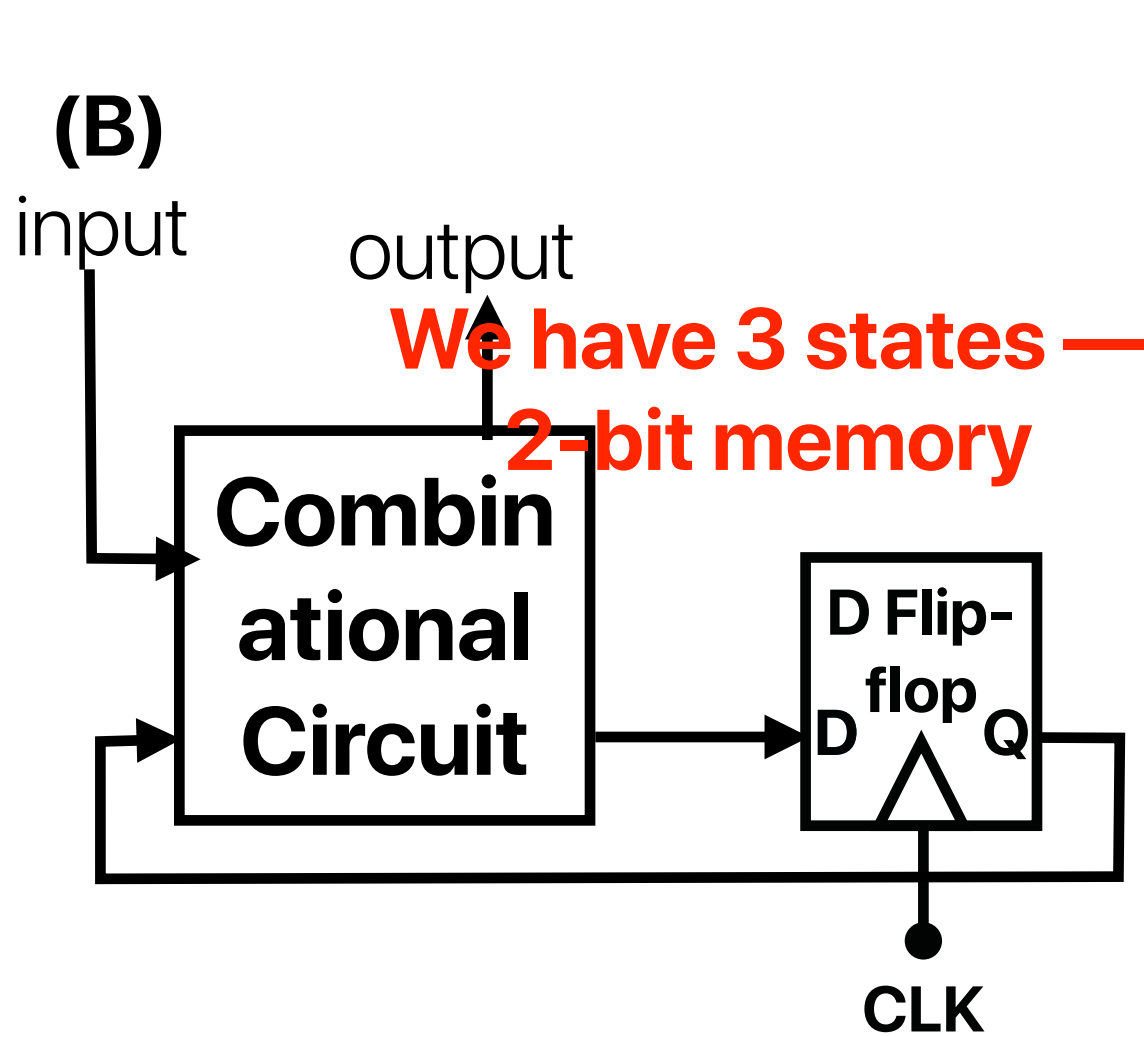  
# Which is the most likely circuit realization of Life on Mars




# Sequential Circuit Design Flow

- Input Output Relation
- State Diagram (Transition of states)
  - State minimization (Reduction)
  - Finite state machine partitioning
- State Assignment (Map states into binary code)
  - Binary code, Gray encoding, One hot encoding, Coding optimization
- State Table (Truth table of states)
- Excitation Table (Truth table of FF inputs)
  - K Map, Minimal Expression
  - Logic Diagram


# Life on Mars

State Diagram

 


State Diagram

Current State	Next State, Output	
	Input 0	Input 1
S0	S1, 0	S0, 0
S1	S2, 0	S0, 0
S2	S2, 0	S0, 1

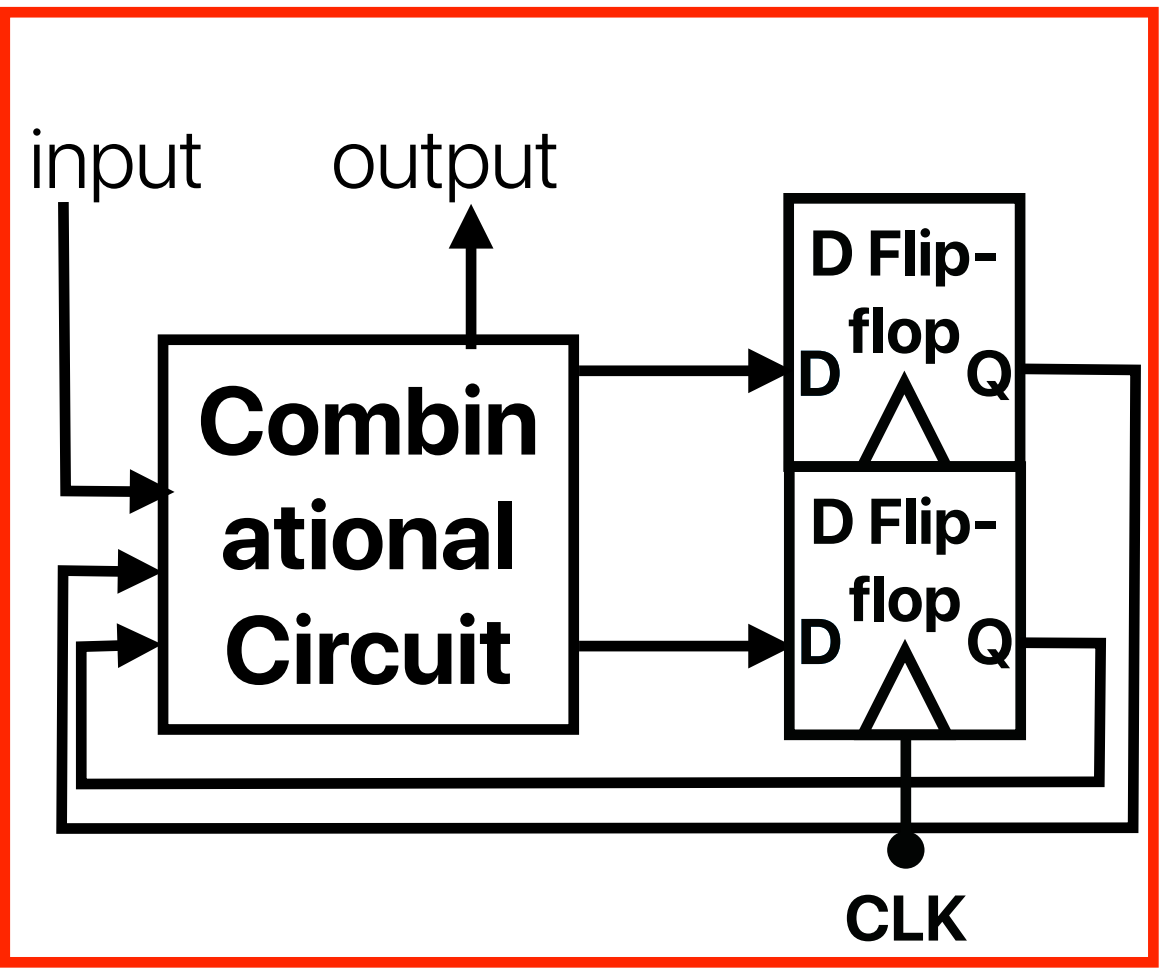

# Life on Mars

State Diagram

 


State Diagram

Current State	Next State, Output	
	Input 0	Input 1
S0	S1, 0	S0, 0
S1	S2, 0	S0, 0
S2	S2, 0	S0, 1


State Assignment

S0	00
S1	01
S2	10

 

# Life on Mars

State Diagram

 

State Diagram


Current State	Next State, Output	
	Input 0	Input 1
S0	S1, 0	S0, 0
S1	S2, 0	S0, 0
S2	S2, 0	S0, 1

State Assignment

S0	00
S1	01
S2	10


State Truth Table

State\Input	0	1
00	01, 0	00, 0
01	10, 0	00, 0
10	10, 0	00, 1

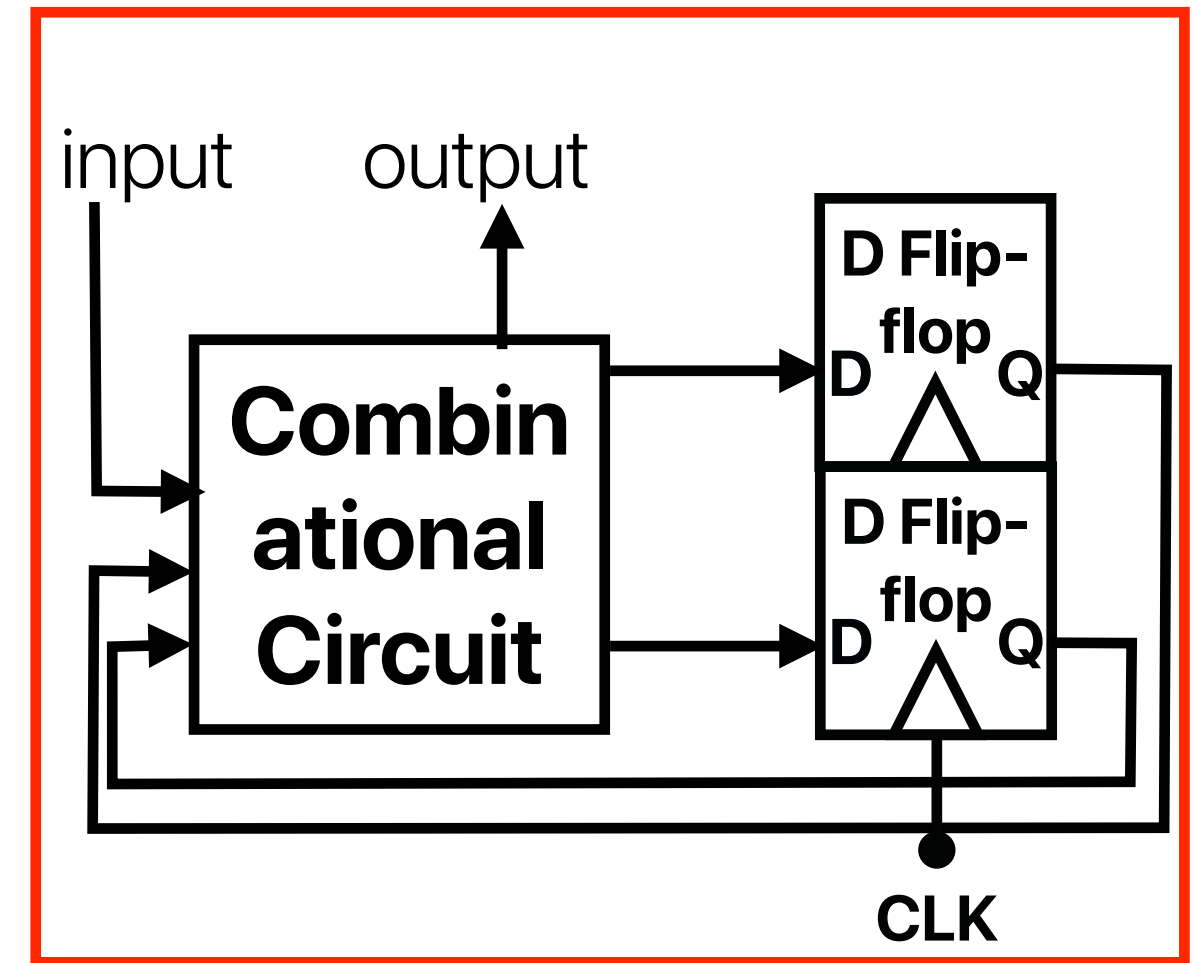
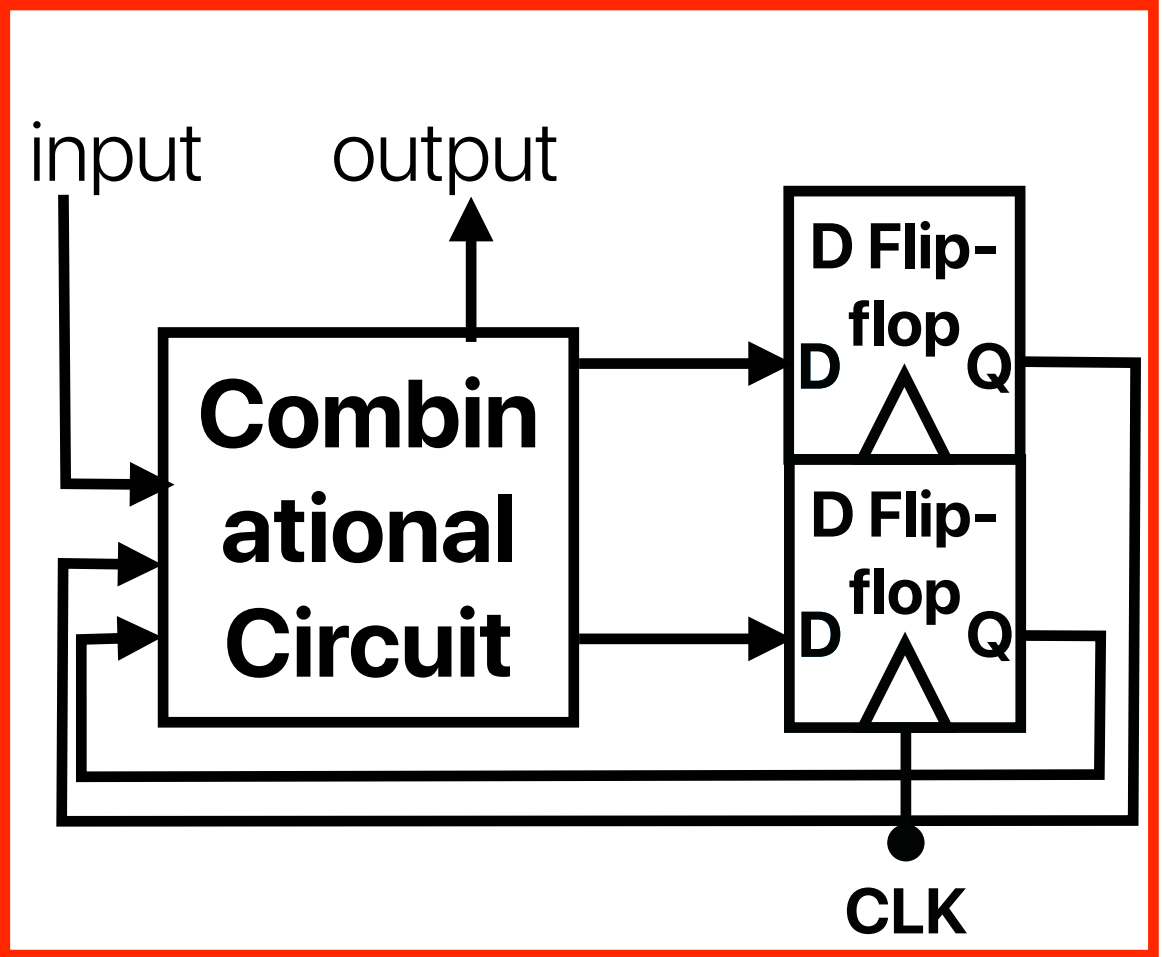
# Excitation Table

- Excitation table is basically the truth table describing the combinational circuit that provides inputs for the flip-flops in the sequential circuit. How many rows are there in the excitation table of Life on Mars?
  - A. 2
  - B. 3
  - C. 4
  - D. 8
  - E. 32



# Excitation Table

- Excitation table is basically the truth table describing the combinational circuit that provides inputs for the flip-flops in the sequential circuit. How many rows are there in the excitation table of Life on Mars?


A. 2

B. 3

C. 4

D. 8

E. 32

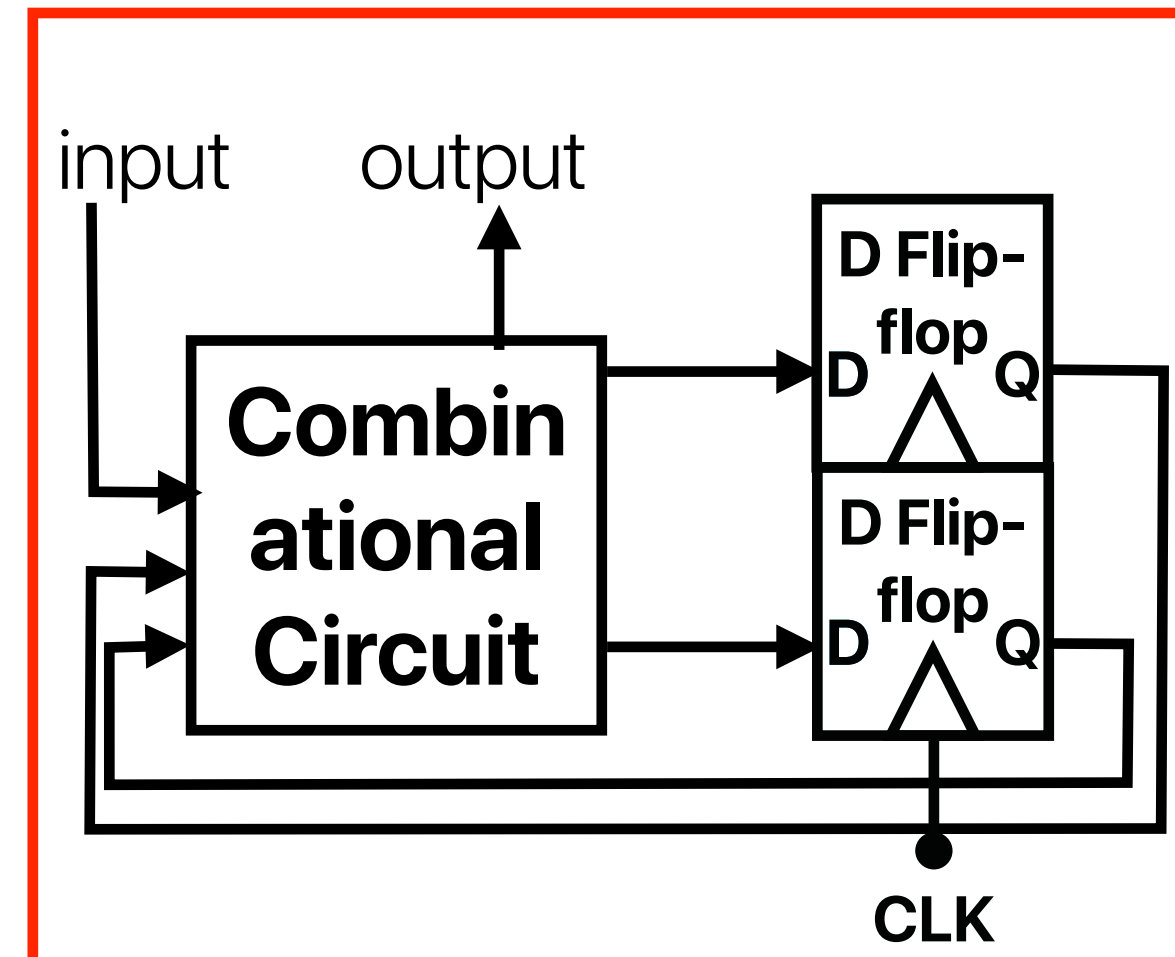




# Life on Mars

State Truth Table

State\Input	0	1
00	01, 0	00, 0
01	10, 0	00, 0
10	10, 0	00, 1

Excitation Table

NextStateOput StateInput	D1	D0	y
000	0	1	0
001	0	0	0
010	1	0	0
011	0	0	0
100	1	0	0
101	0	0	1
110	X	X	X
111	X	X	X

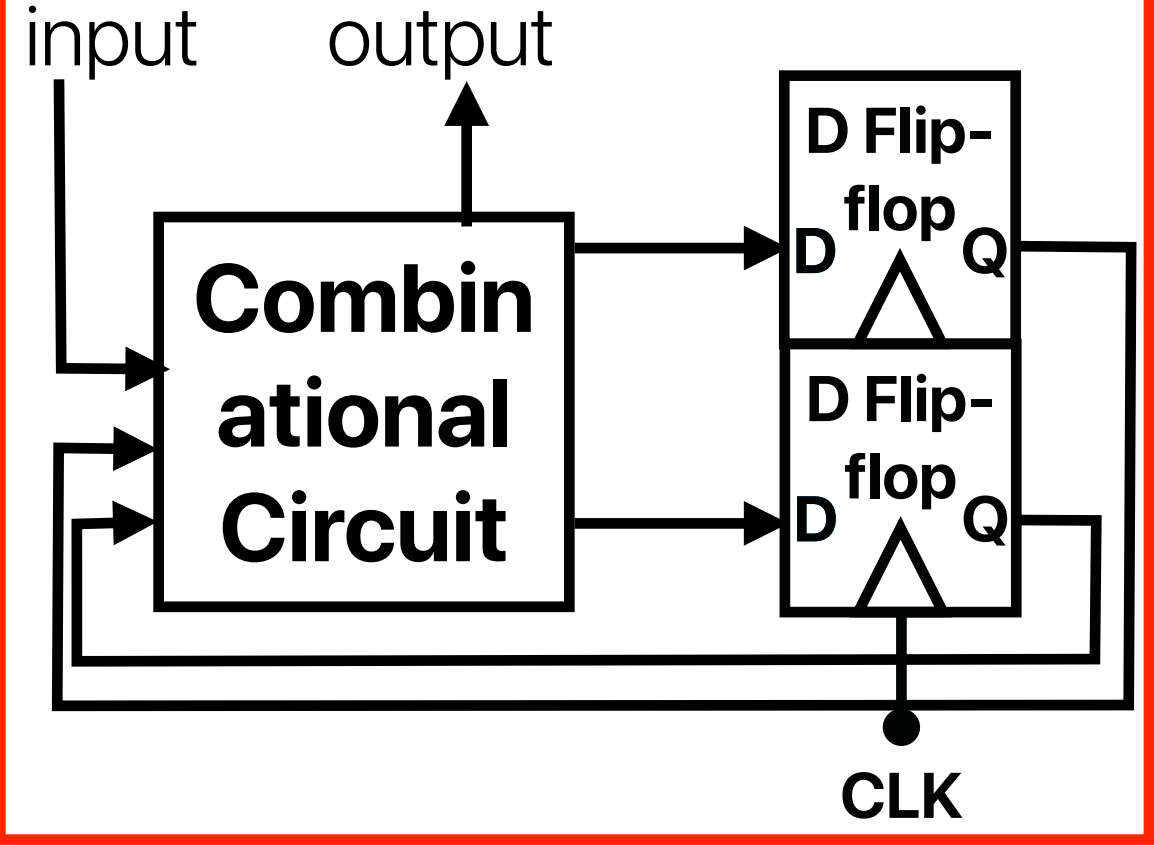


State Truth Table

State\Input	0	1
00	01, 0	00, 0
01	10, 0	00, 0
10	10, 0	00, 1

Excitation Table

NextStateOput StateInput	D1	D0	y
000	0	1	0
001	0	0	0
010	1	0	0
011	0	0	0
100	1	0	0
101	0	0	1
110	X	X	X
111	X	X	X

Life on Mars

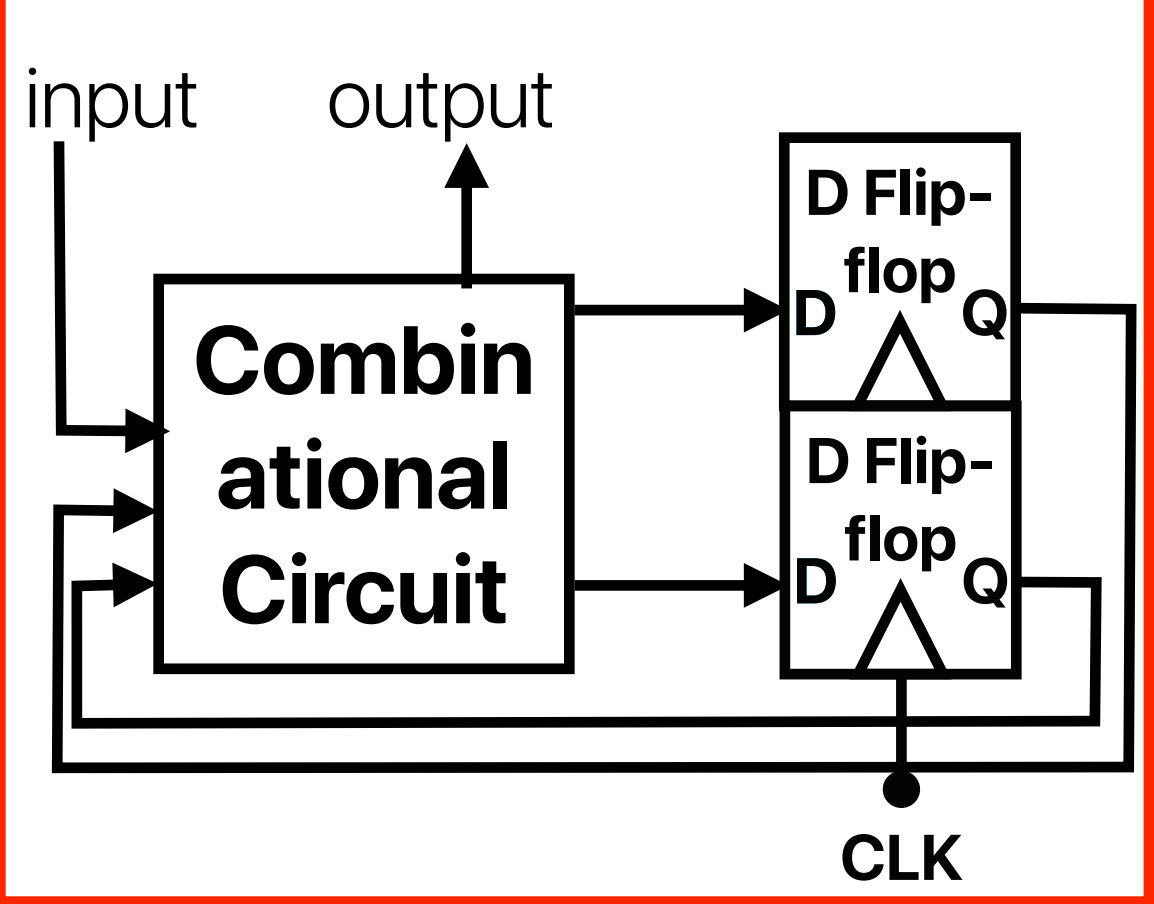

K-Map — D1

	0,0	0,1	1,1	1,0
0	0	1	X	1
1	0	0	X	0

$D1 = x'Q_0 + x'Q_1$

K-Map — D0

	0,0	0,1	1,1	1,0
0	1	0	X	0
1	0	0	X	0

$D0 = Q_0'Q_1'x'$

K-Map — y

	0,0	0,1	1,1	1,0
0	0	0	X	0
1	0	0	X	1



$y = Q_1'x$

# Circuit — Life on Mars

$$D1 = x'Q_0 + x'Q_1$$

$$D0 = Q_0'Q_1'x'$$



$$y = Q_1'x$$

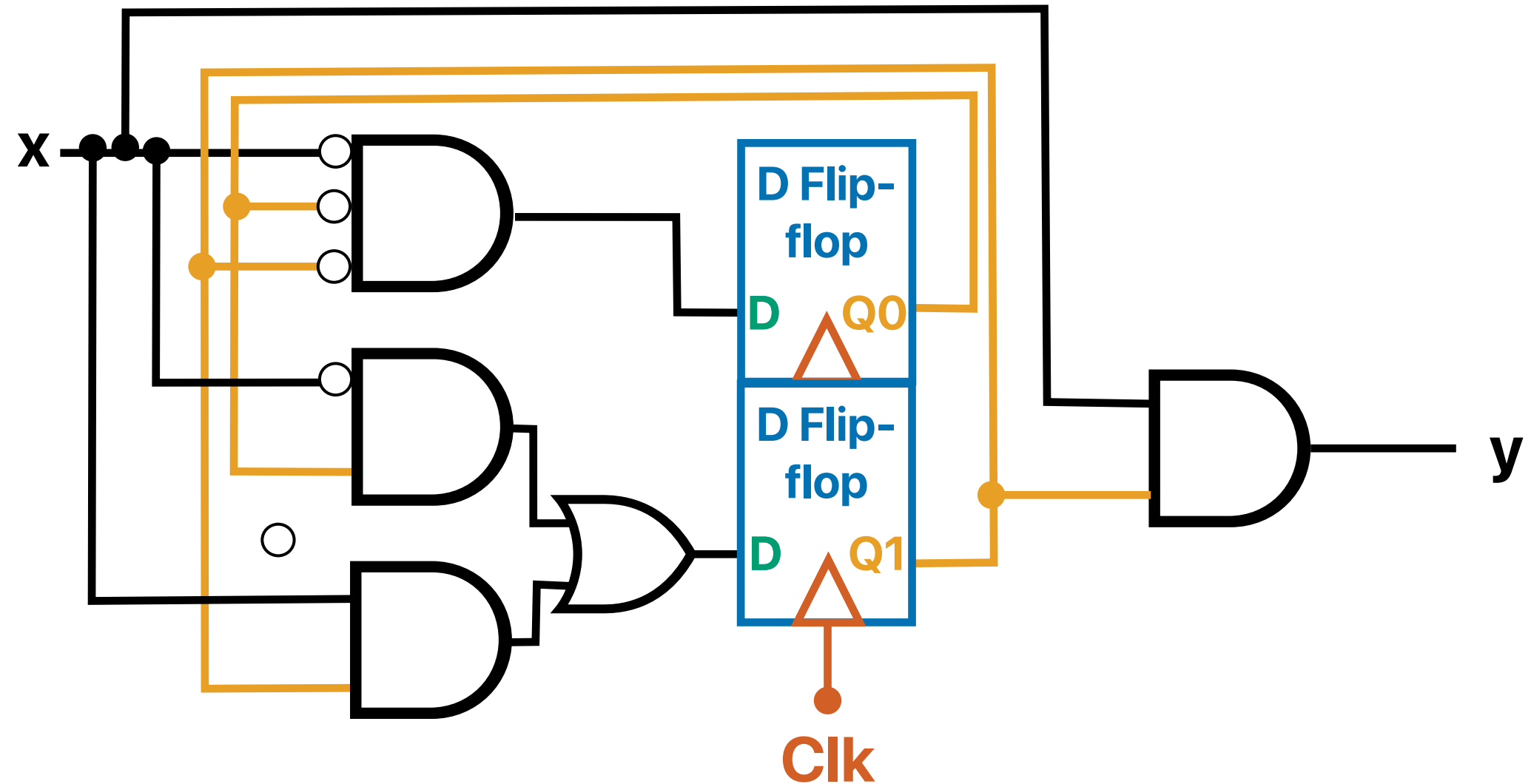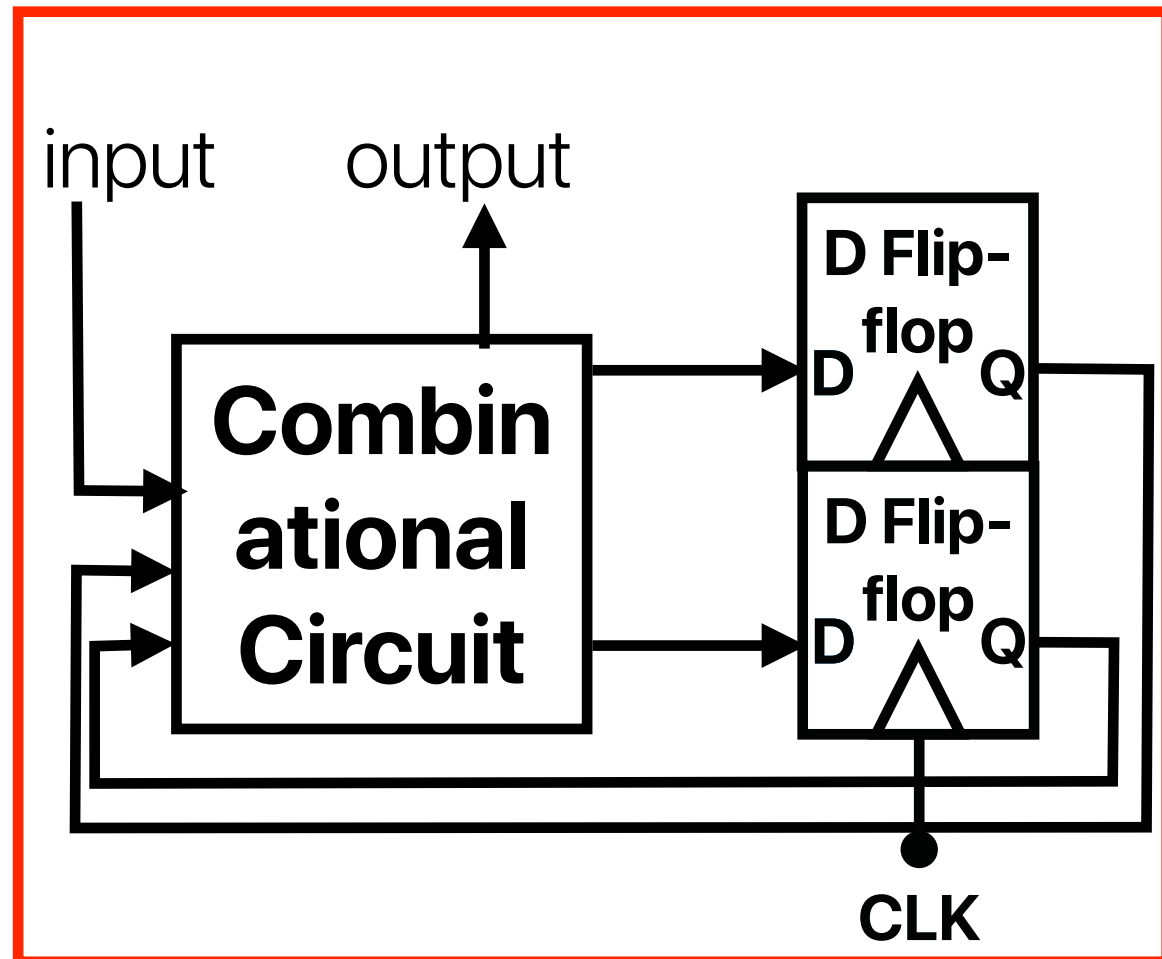

# Canonical Form: Mealy and Moore Machines



# Canonical Form: Mealy and Moore Machines

## Mealy Machine

 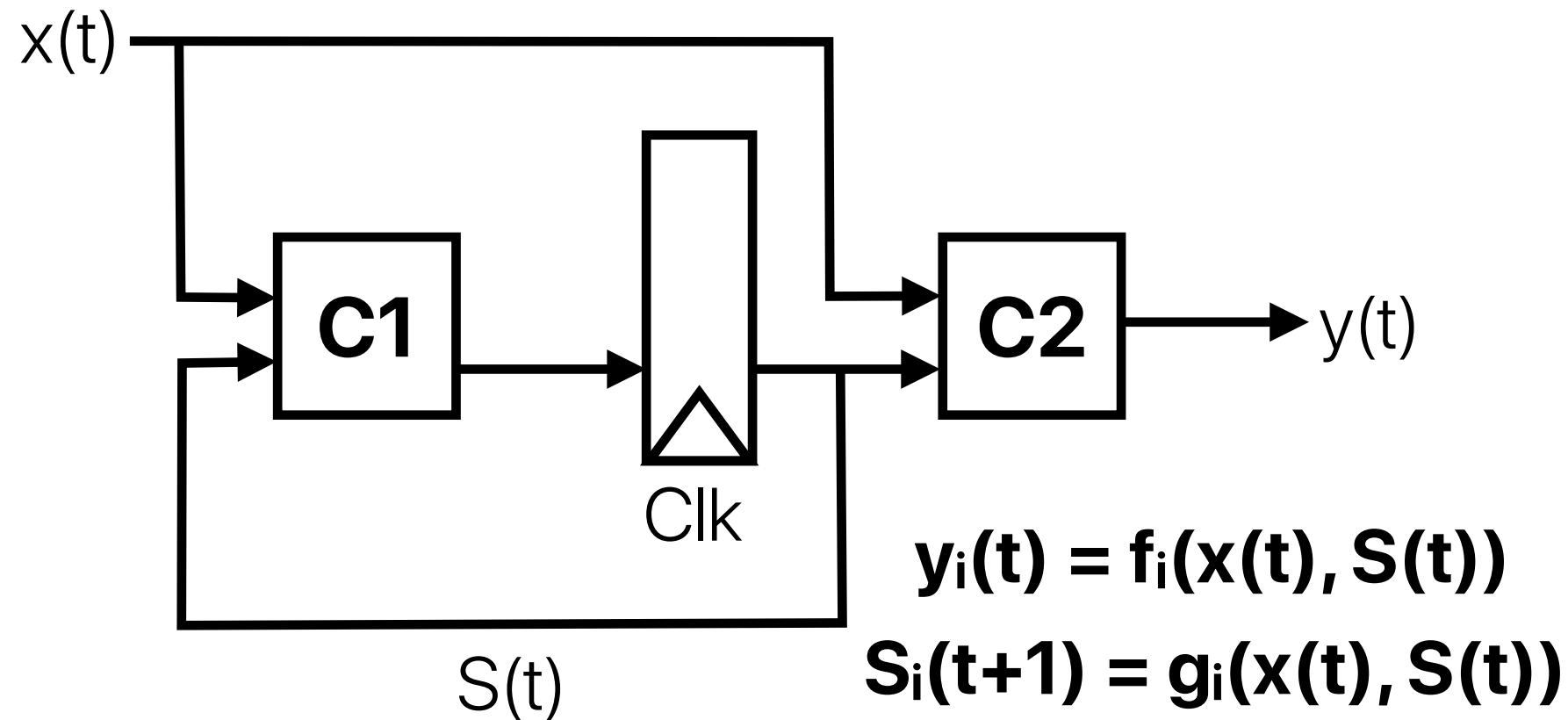

**Result depends on both input and the current state**

## Moore Machine

 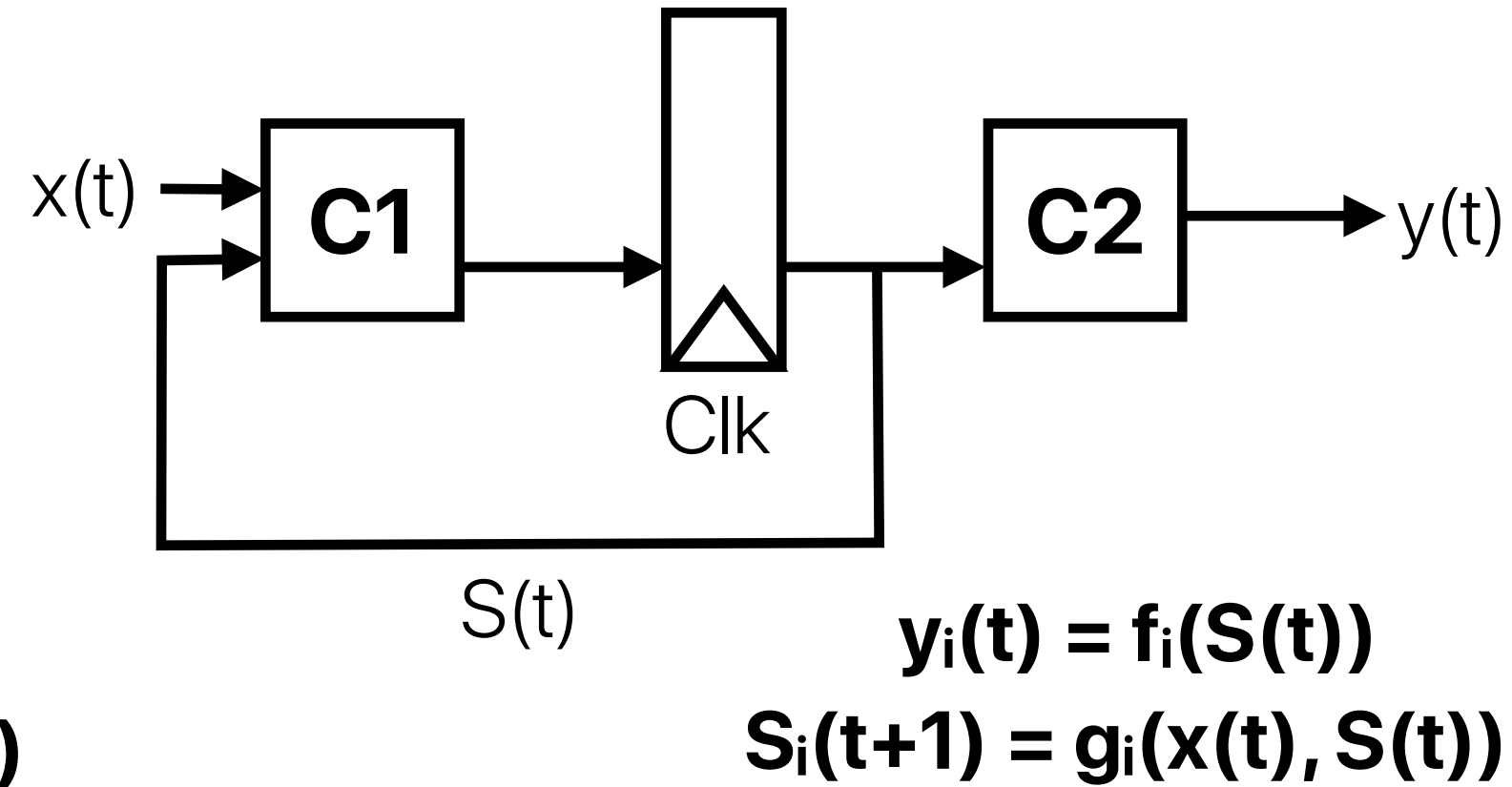


**Result only depends on the current state**

# Moore or Mealy? — Life on Mars

• Which type of state machine can describe the “Life on Mars” pattern recognizer of “001”.

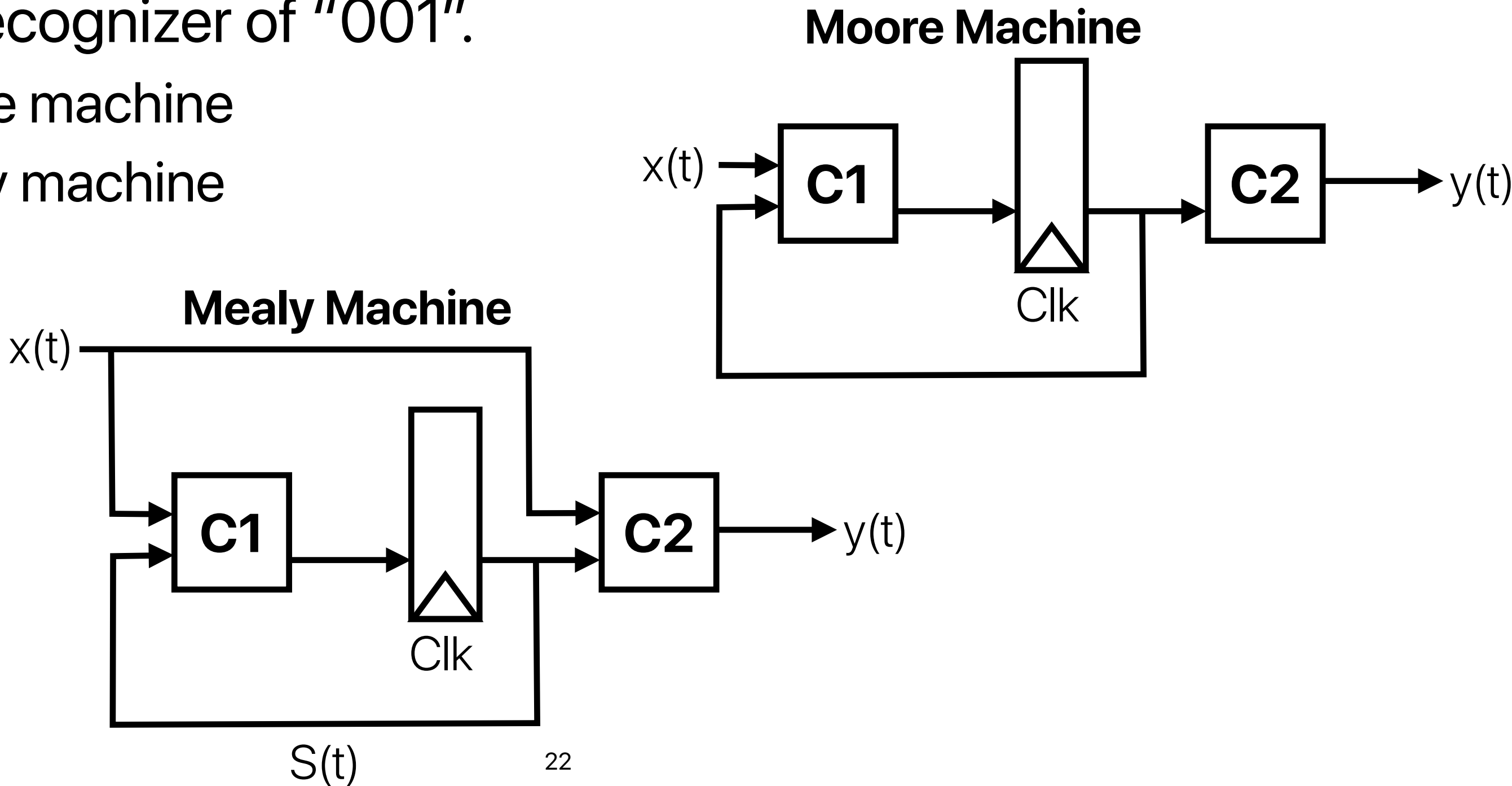- A. Moore machine
- B. Mealy machine
- C. Both
- D. None



# Moore or Mealy? — Life on Mars

- Which type of state machine can describe the “Life on Mars” pattern recognizer of “001”.


A. Moore machine

B. Mealy machine


C. Both

D. None

Moore Machine

 


Mealy Machine

 
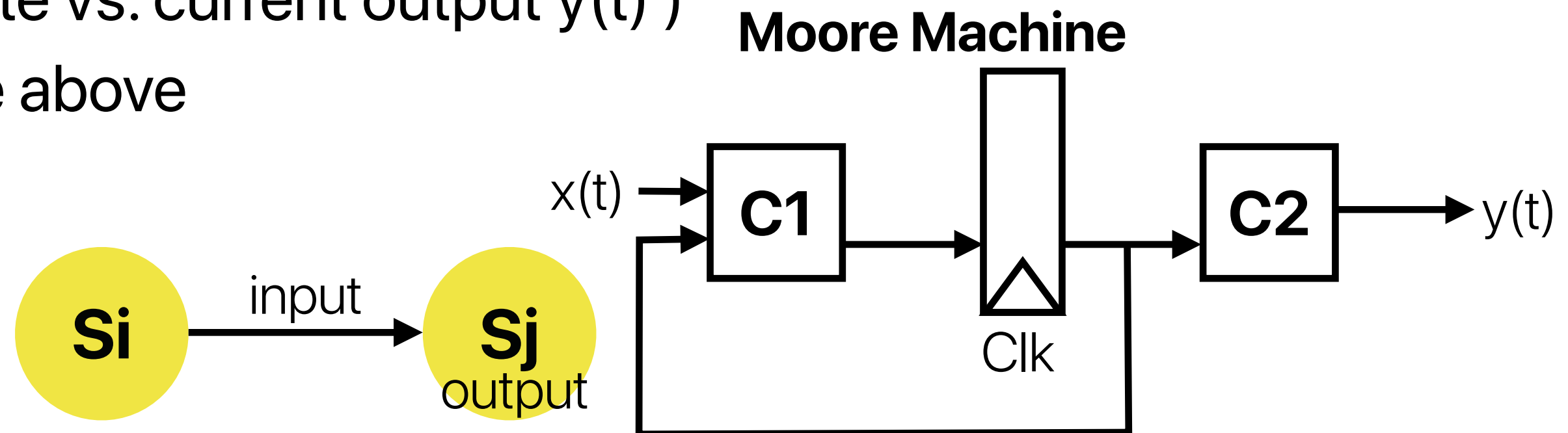
# Moore machine for Life on Mars


- What does state table need to show to design controls of C2 to implement pattern recognizer "001"?
  - A. (current input  $x(t)$ , current state  $S(t)$  vs. next state,  $S(t+1)$ )
  - B. (current input, current state vs. current output  $y(t)$ )
  - C. (current state vs. current output  $y(t)$  and next state)
  - D. (current state vs. current output  $y(t)$  )
  - E. None of the above




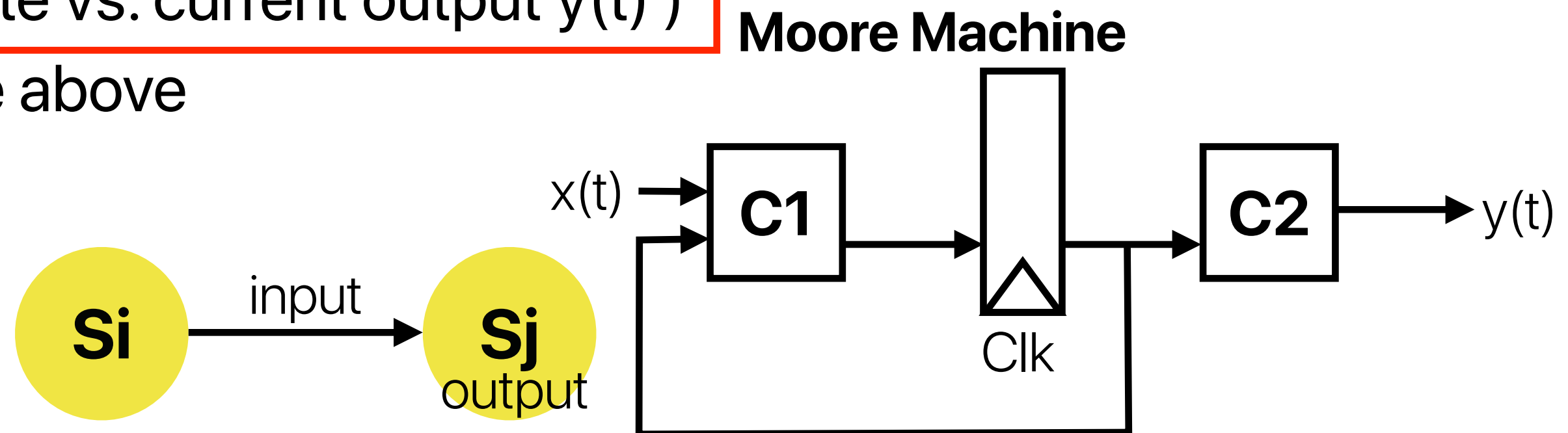
# Moore machine for Life on Mars

- What does state table need to show to design controls of C2 to implement pattern recognizer "001"?
  - A. (current input  $x(t)$ , current state  $S(t)$  vs. next state,  $S(t+1)$ )
  - B. (current input, current state vs. current output  $y(t)$ )
  - C. (current state vs. current output  $y(t)$  and next state)
  - D. (current state vs. current output  $y(t)$ )**
  - E. None of the above



# Conversion from Mealy to Moore

- ① Identify distinct (Next State, y) pair
- ② Replace each distinct (Next State, y) pair with distinct new states
- ③ Insert rows of present state = new states
- ④ Append each present state with its output y

Current State	Next State Input	
	0	1
S0	S1, 0	S0, 0
S1	S2, 0	S0, 0
S2	S2, 0	<b>S0, 1</b>

Current State	Next State Input		Output
	0	1	
S0	S1	S0	0
S1	S2	S0	0
S2	S2	<b>S3</b>	0
S3			

# Conversion from Mealy to Moore

- ① Identify distinct (Next State, y) pair
  - ② Replace each distinct (Next State, y) pair with distinct new states
  - ③ Insert rows of present state = new states
  - ④ Append each present state with its output y
- For the given Moore machine, what are the next states with respect to present state S3?
    - A. S2, S3, 1
    - B. S2, S0, 1
    - C. S1, S0, 1
    - D. S1, S0, 0
    - E. None of the above.

Current State	Next State Input	
	0	1
S0	S1, 0	S0, 0
S1	S2, 0	S0, 0
S2	S2, 0	<b>S0, 1</b>

Current State	Next State Input		Output
	0	1	
S0	S1	S0	0
S1	S2	S0	0
S2	S2	<b>S3</b>	0
S3			

# Conversion from Mealy to Moore

- ① Identify distinct (Next State, y) pair
  - ② Replace each distinct (Next State, y) pair with distinct new states
  - ③ Insert rows of present state = new states
  - ④ Append each present state with its output y
- For the given Moore machine, what are the next states with respect to present state S3?
    - A. S2, S3, 1
    - B. S2, S0, 1
    - C. S1, S0, 1
    - D. S1, S0, 0
    - E. None of the above.

Current State	Next State Input	
	0	1
S0	S1, 0	S0, 0
S1	S2, 0	S0, 0
S2	S2, 0	<b>S0, 1</b>

Current State	Next State Input		Output
	0	1	
S0	S1	S0	0
S1	S2	S0	0
S2	S2	<b>S3</b>	0
S3	<b>S1</b>	<b>S0</b>	<b>1</b>

# Conversion from Mealy to Moore

- ① Identify distinct (Next State, y) pair
- ② Replace each distinct (Next State, y) pair with distinct new states
- ③ Insert rows of present state = new states
- ④ Append each present state with its output y

Current State	Next State Input	
	0	1
S0	S1, 0	S0, 0
S1	S2, 0	S0, 0
S2	S2, 0	<b>S0, 1</b>

Current State	Next State Input		Output
	0	1	
S0	S1	S0	0
S1	S2	S0	0
S2	S2	<b>S3</b>	0
S3	<b>S1</b>	<b>S0</b>	<b>1</b>

# State tables for C1 and C2


Current State	Next State		Output
	Input 0	Input 1	
S0	S1	S0	0
S1	S2	S0	0
S2	S2	S3	0
S3	S1	S0	1

C1

CurrentState-Input	D1	D0
000	0	1
001	0	0
010	1	0
011	0	0
100	1	0
101	1	1
110	0	1
111	0	0

State	y
00	0
01	0
10	0
11	1

C2

 

# State tables for C1 and C2

Current State	Next State		Output
	Input 0	Input 1	
S0	S1	S0	0
S1	S2	S0	0
S2	S2	S3	0
S3	S1	S0	1


C1

C2

CurrentState-Input	D1	D0
000	0	1
001	0	0
010	1	0
011	0	0
100	1	0
101	0	0
110	0	1
111	0	0

State	y
00	0
01	0
10	0
11	1

Moore Machine

 

K-Map — D1

	0,0	0,1	1,1	1,0
0	0	1	0	1
1	0	0	0	1

$D1 = x'Q_1'Q_0 + Q_1Q_0'$

K-Map — D0

	0,0	0,1	1,1	1,0
0	1	0	1	0
1	0	0	0	1

$D0 = Q_0'Q_1'x' + Q_0Q_1x' + Q_0'Q_1x'$

K-Map — y

	0	1
0	0	0
1	0	1

$y = Q_0Q_1$


# **When sequential circuits meet datapath components (3)**



# The delay is determined by the "critical path"

Available in the very beginning


Only this is available in the beginning

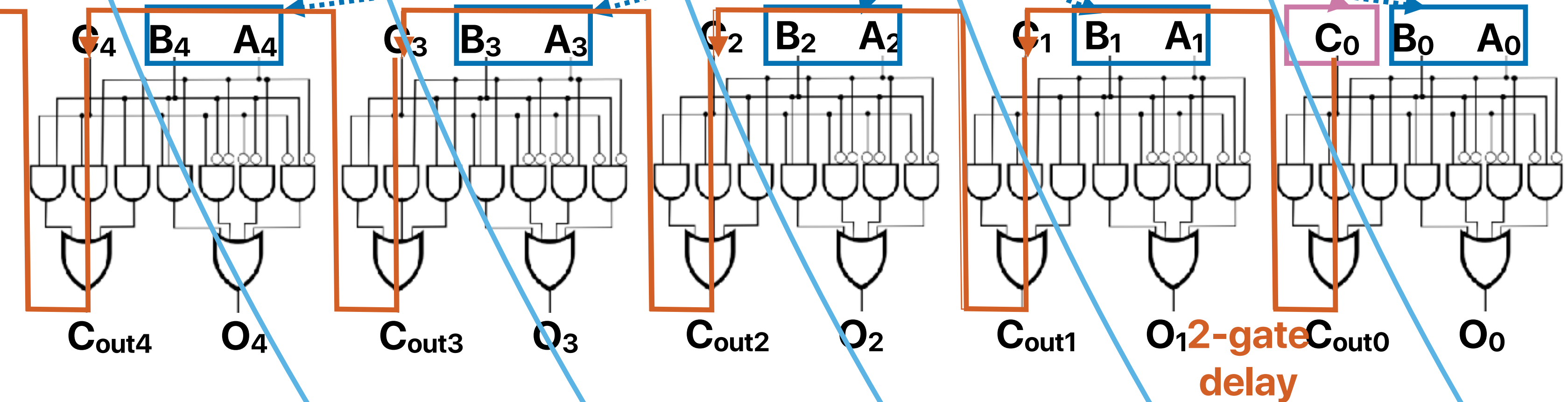

## Carry-Ripple Adder
 
# CLA (cont.)

- All "G" and "P" are immediately available (only need to look over  $A_i$  and  $B_i$ ), but "c" are not (except the  $c_0$ ).



$$G_i = A_i B_i$$

$$P_i = A_i \text{ XOR } B_i$$

$$C_1 = G_0 + P_0 C_0$$

$$C_2 = G_1 + P_1 C_1 = G_1 + P_1 (G_0 + P_0 C_0) \\ = G_1 + P_1 G_0 + P_1 P_0 C_0$$

$$C_3 = G_2 + P_2 C_2$$

$$= G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$$

$$C_4 = G_3 + P_3 C_3$$

$$= G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 \\ + P_3 P_2 P_1 P_0 C_0$$

# CLA v.s. Carry-ripple

- Size:

- 32-bit CLA with 4-bit CLAs — requires 8 of 4-bit CLA
  - Each requires 116 for the CLA  $4 \times (4 \times 6 + 8)$  for the  $A+B$  — 244 gates
  - 1952 transistors
- 32-bit CRA
  - 1600 transistors **Win!**


**Area-Delay Trade-off!**

- Delay


- 32-bit CLA with 8 4-bit CLAs
  - 2 gates \* 8 = 16 **Win!**
- 32-bit CRA
  - 64 gates

# Serial Addder

## Mealy Machine

 

**The basic idea**

 


Feed  $a_i$  and  $b_i$  and generate  $s_i$  at time  $i$ . Where is  $c_i$  and  $c_{i+1}$ ?

# Excitation Table of Serial Adder


$a_i$	$b_i$	$c_i$	$c_{i+1}$	$s_i$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

# Excitation Table of Serial Adder


$a_i$	$b_i$	$c_i$	$c_{i+1}$	$s_i$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

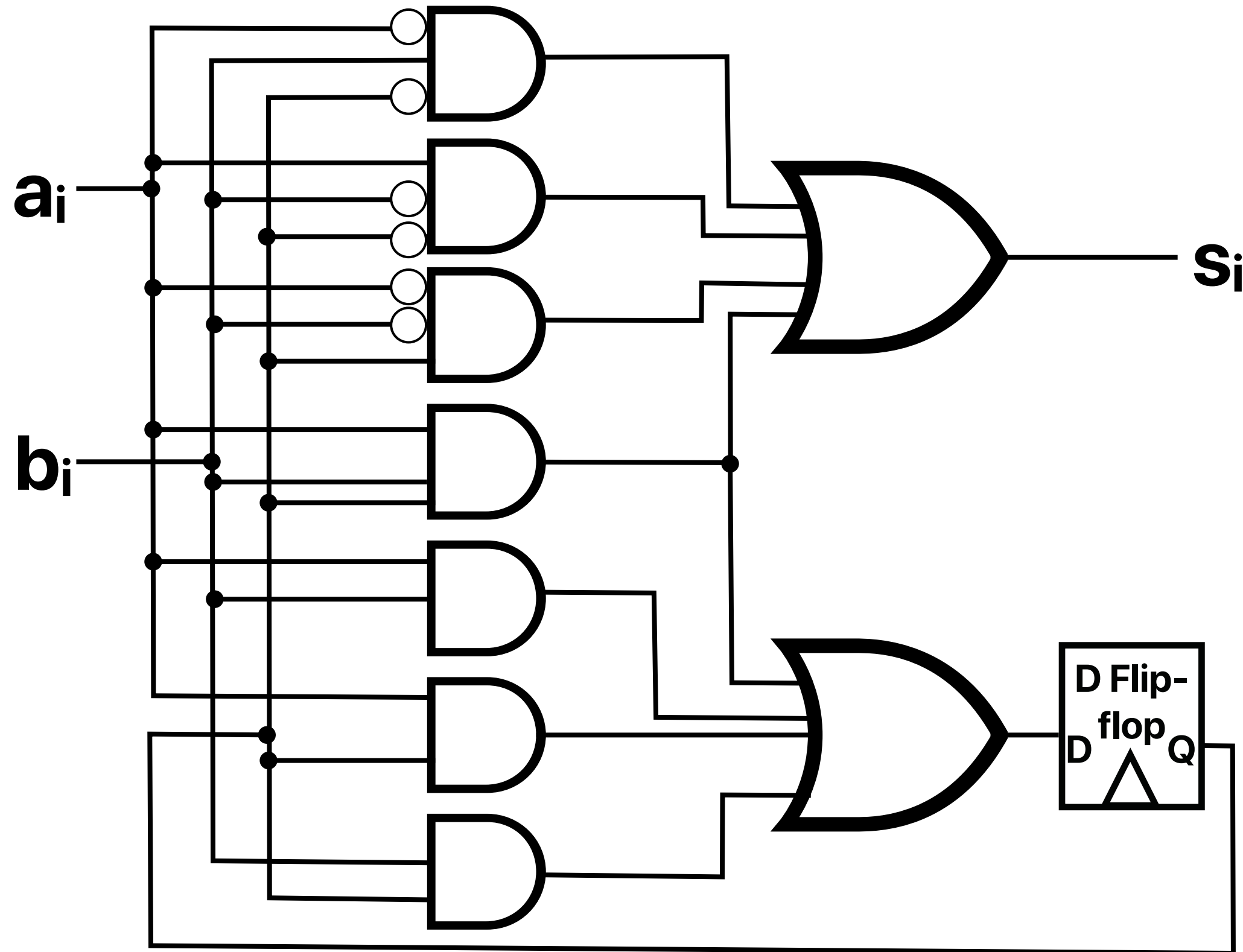

# EXCUSE

 



 

Google

How Often Do People Lie

Q All News Images Videos Shopping More Settings Tools

About 267,000,000 results (0.54 seconds)

The study, published in the journal's June issue, found that 60 percent of **people lied** at least once during a 10-minute conversation and told an average of two to three lies. "**People** tell a considerable number of lies in everyday conversation. Jun 10, 2002

UMass researcher finds most people lie in everyday ...  
[https://www.eurekalert.org/pub\\_releases/uoma-urf061002](https://www.eurekalert.org/pub_releases/uoma-urf061002)

Politics 45 Congress SCOTUS Facts First 2020 2019 Elections LIVE TV Edition

# Did Trump lie more often than you wash your hands every day

by [Chris Cillizza](#), CNN Editor-at-large

4:56 PM ET, Mon June 10, 2019

"A lie doesn't become truth, wrong doesn't become right and evil doesn't become good, just because it is accepted by a majority."

*–Rick Warren*

Honesty is the best policy

–*Benjamin Franklin*







Better three hours too soon, than one minute too late.

*–William Shakespeare*


In truth, people can generally make time for what they choose to do; it is not really the time but the will that is lacking.

*—Sir John Lubbock*

Don't over-commit


*–Prof. Usagi*

# Midterm

 


 
# Weighted Total — what really decides your final grades



# Announcement

- Lab 4 — due tonight
- Reading quiz due this Thursday
- Assignment #4 due next Tuesday — **Chapter 4.8-4.9 & 5.2-5.4**
- Lab 5 is up — due next Thursday
  - Start early & plan your time carefully
  - Watch the video and read the instruction BEFORE your session
  - There are links on both course webpage and iLearn lab section
  - Submit through iLearn > Labs
- Check your grades in iLearn

# Electrical Computer Science Engineering

# 120A

# つづく

