

# Datapath Components (3) — Those Who “Remember” Things



Prof. Usagi

# Recap: Combinational v.s. sequential logic


- Combinational logic
  - The output is a pure function of its current inputs
  - The output doesn't change regardless how many times the logic is triggered — Idempotent
- Sequential logic
  - The output depends on current inputs, previous inputs, their history

**Sequential circuit has memory!**

# Recap: D flip-flop

  
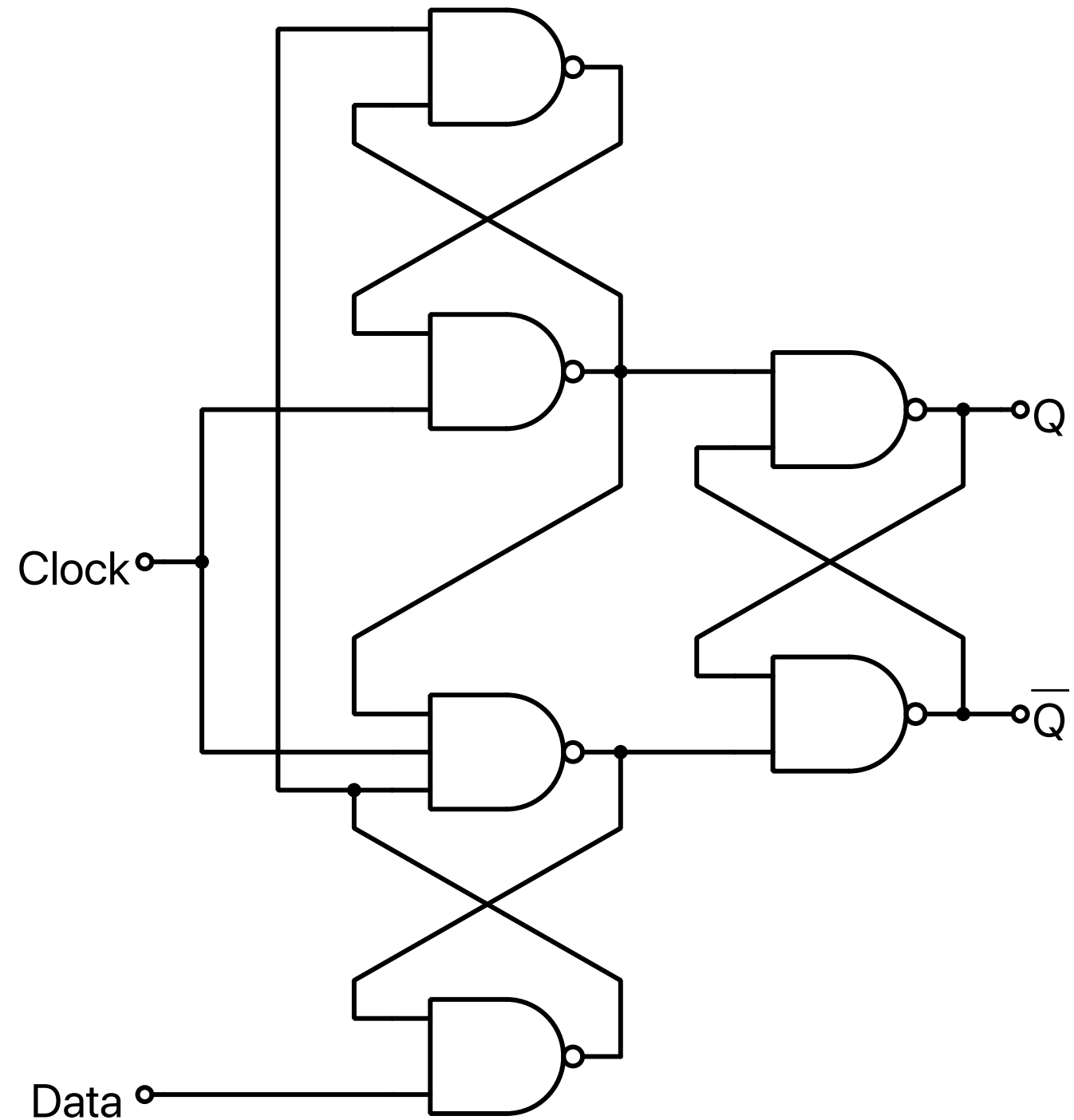
# Recap: Positive-edge-triggered D flip-flop




# Outline

- Volatile Memory
  - Registers
  - SRAM
  - DRAM
- Programming and memory
- Non-volatile Memory


# Registers
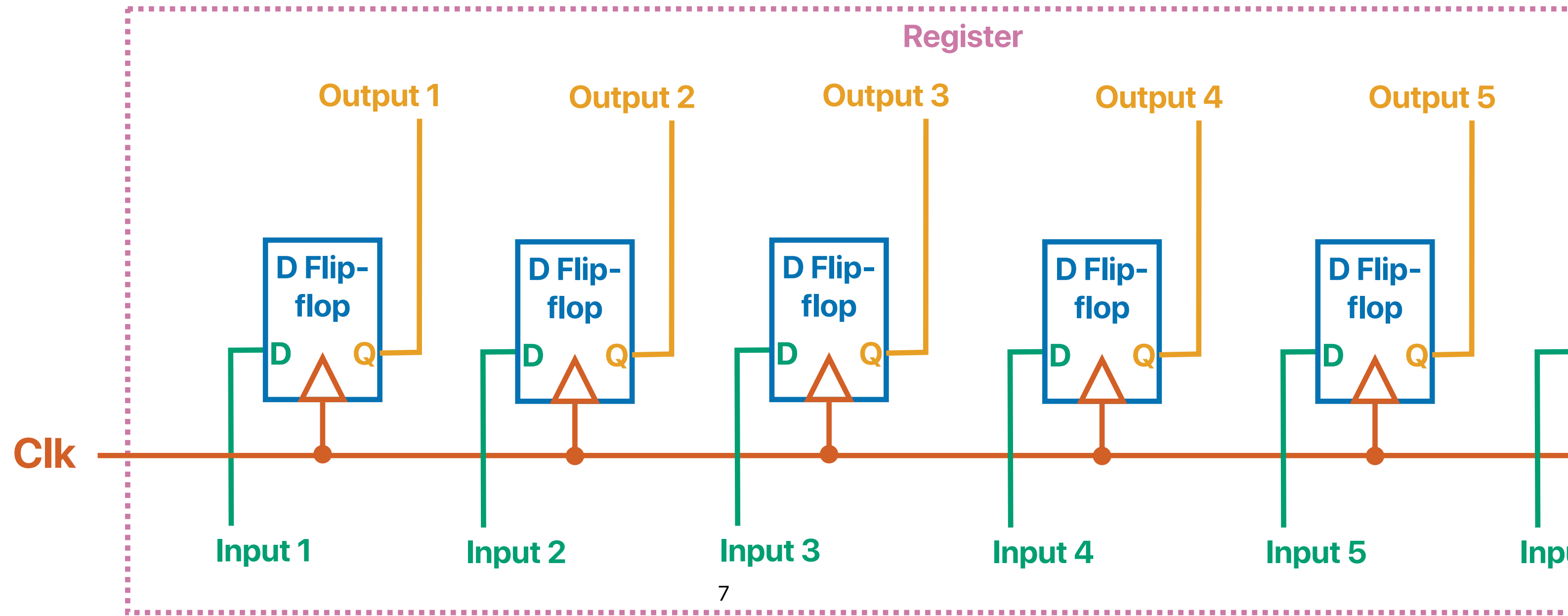
# Registers

- Register: a sequential component that can store multiple bits
- A basic register can be built simply by using multiple D-FFs




# What will we output 4 cycles later?

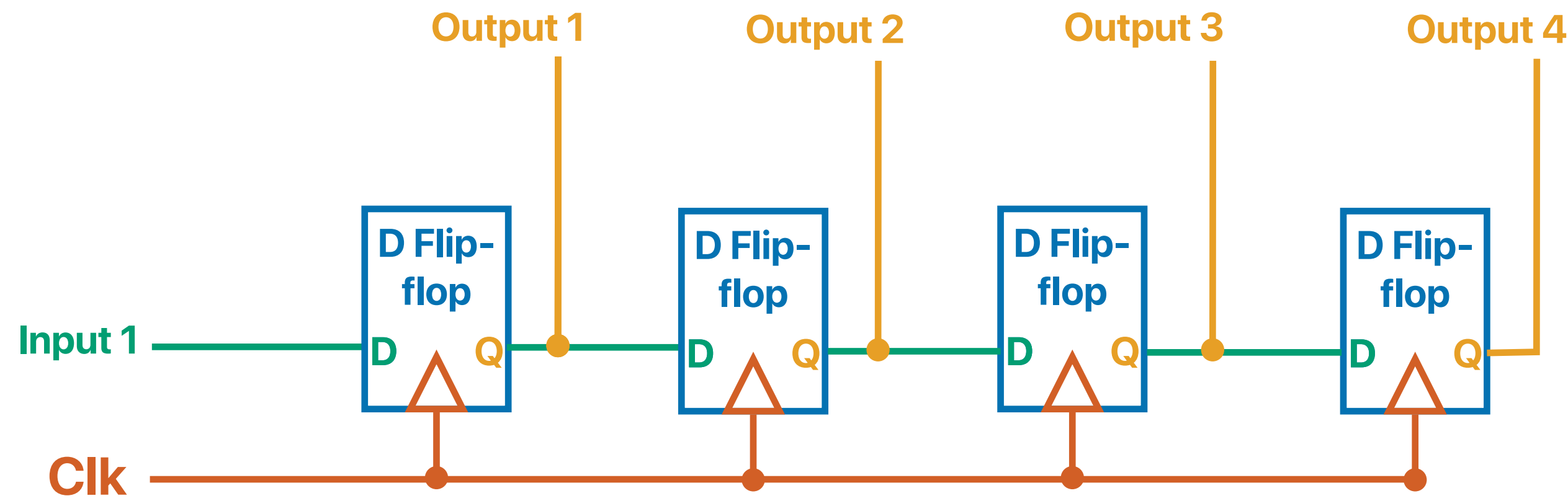

- For the above D-FF organization, what are we expecting to see in (O1,O2,O3,O4) in the beginning of the 5th cycle after receiving (1,0,1,1)?
  - A. (1,1,1,1)
  - B. (1,0,1,1)
  - C. (1,1,0,1)
  - D. (0,0,1,0)
  - E. (0,1,0,0)




# What will we output 4 cycles later?

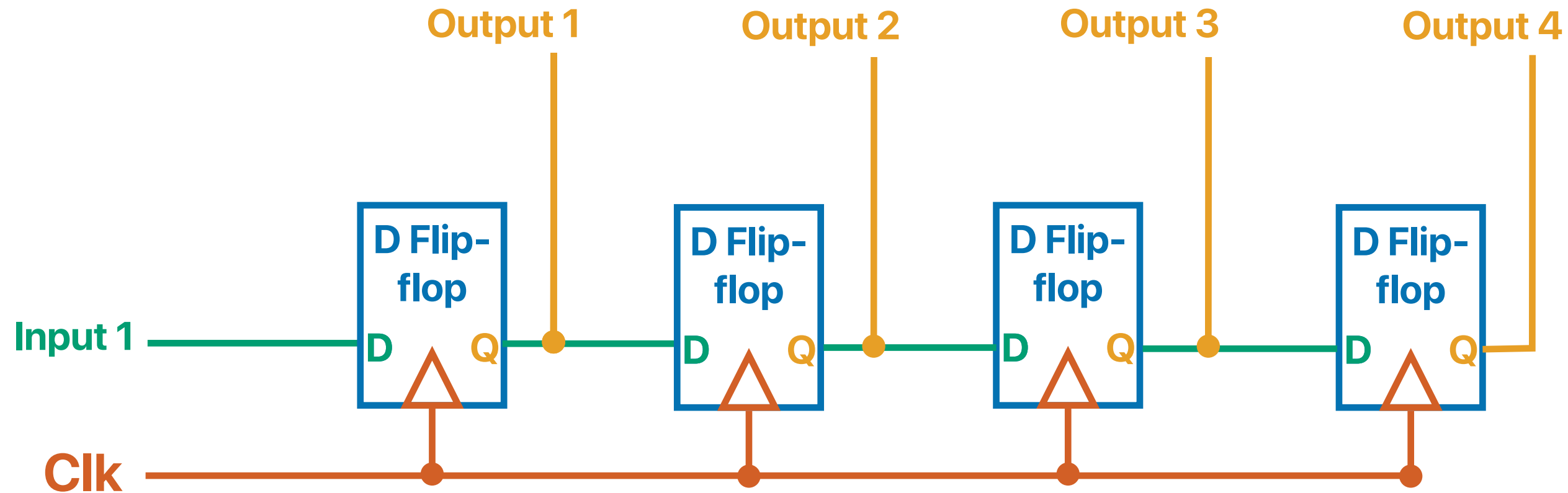


- For the above D-FF organization, what are we expecting to see in (O1,O2,O3,O4) in the beginning of the 5th cycle after receiving (1,0,1,1)?
  - A. (1,1,1,1)
  - B. (1,0,1,1)
  - C. (1,1,0,1)**
  - D. (0,0,1,0)
  - E. (0,1,0,0)

# Shift register

- Holds & shifts samples of input

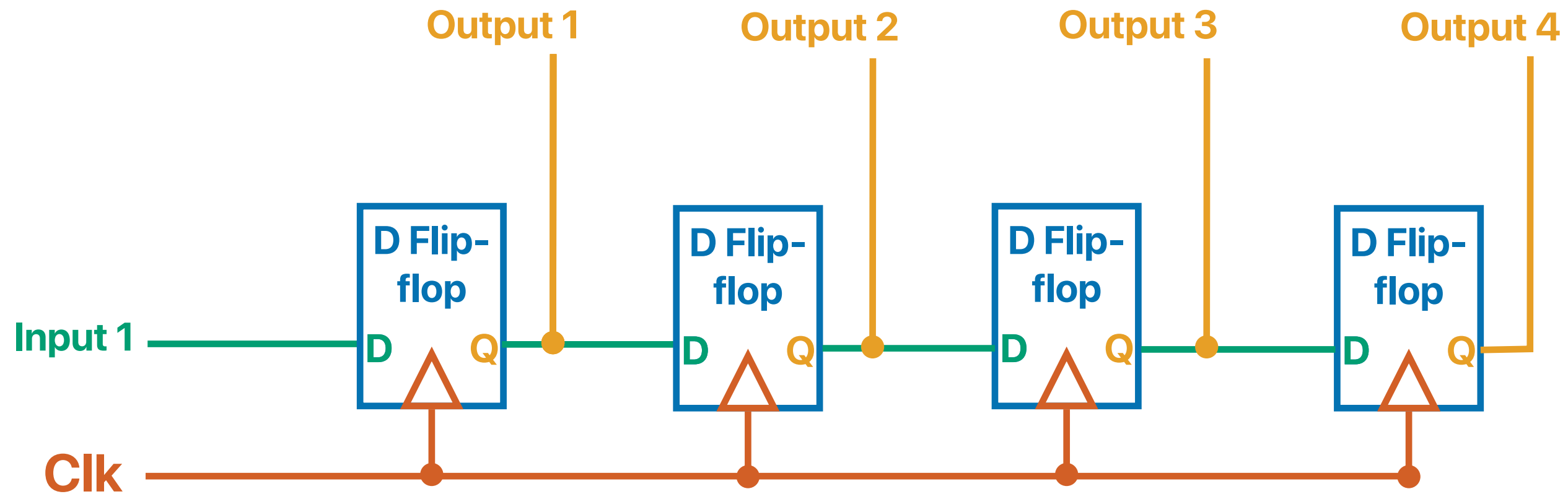

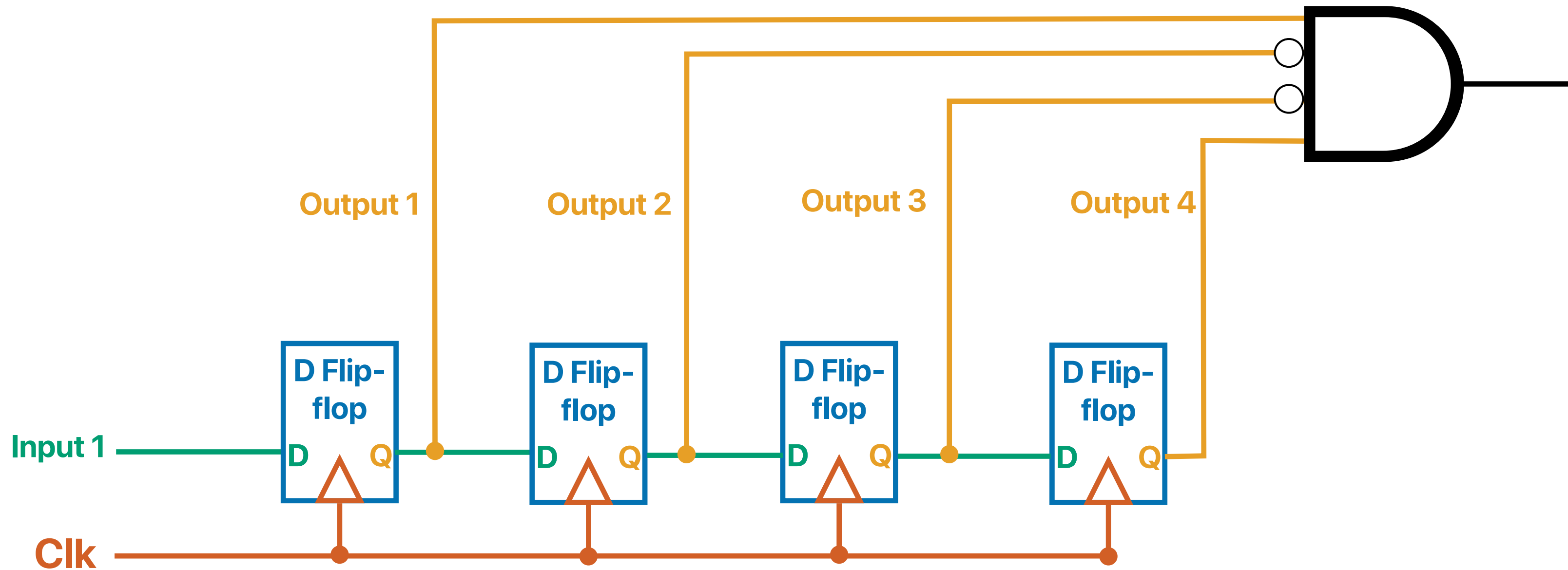
# Let's play with the shift register more...



# Let's play with the shift register more...

- For the extended shift register, what sequence of input will let the circuit output "1"?

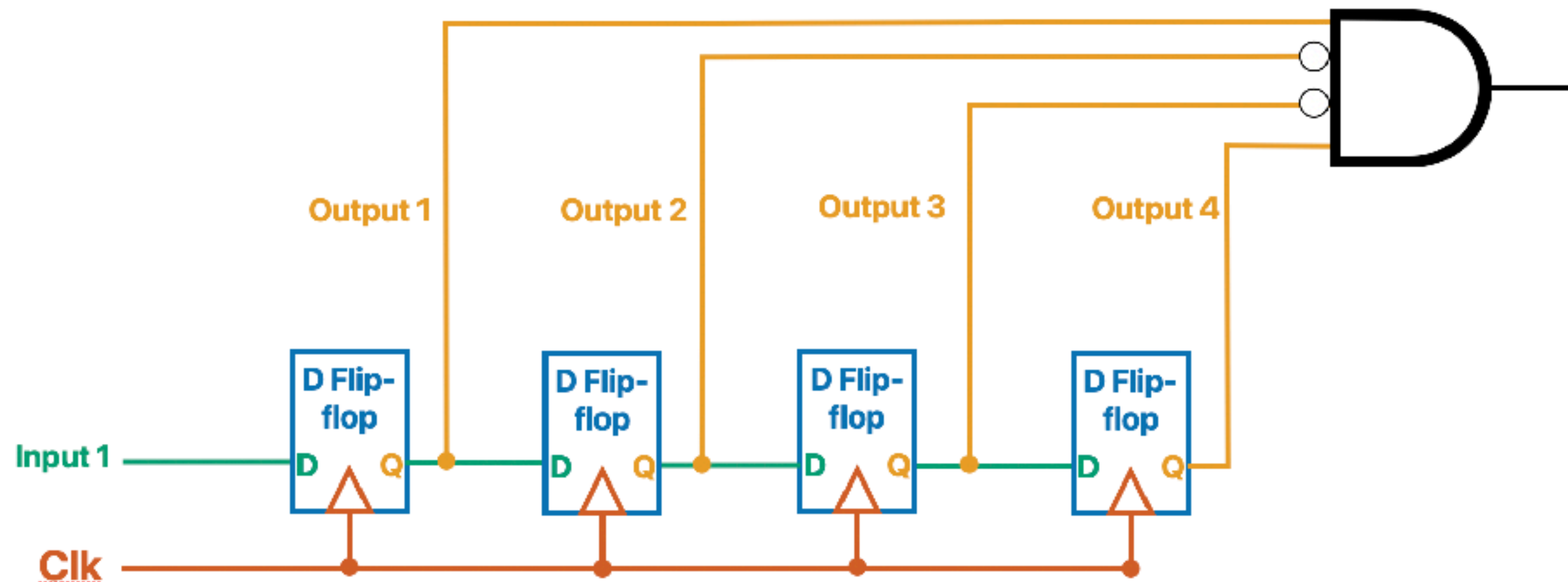
- A. (1, 1, 1, 1)
- B. (0, 1, 0, 1)
- C. (1, 0, 1, 0)
- D. (0, 1, 1, 0)
- E. (1, 0, 0, 1)



# Let's play with the shift register more...

- For the extended shift register, what sequence of input will let the circuit output "1"?

 
- A. (1, 1, 1, 1)
- B. (0, 1, 0, 1)
- C. (1, 0, 1, 0)
- D. (0, 1, 1, 0)
- E. (1, 0, 0, 1)**



# Pattern Recognizer


- Combinational function of input samples

We can recognize 1001!

 
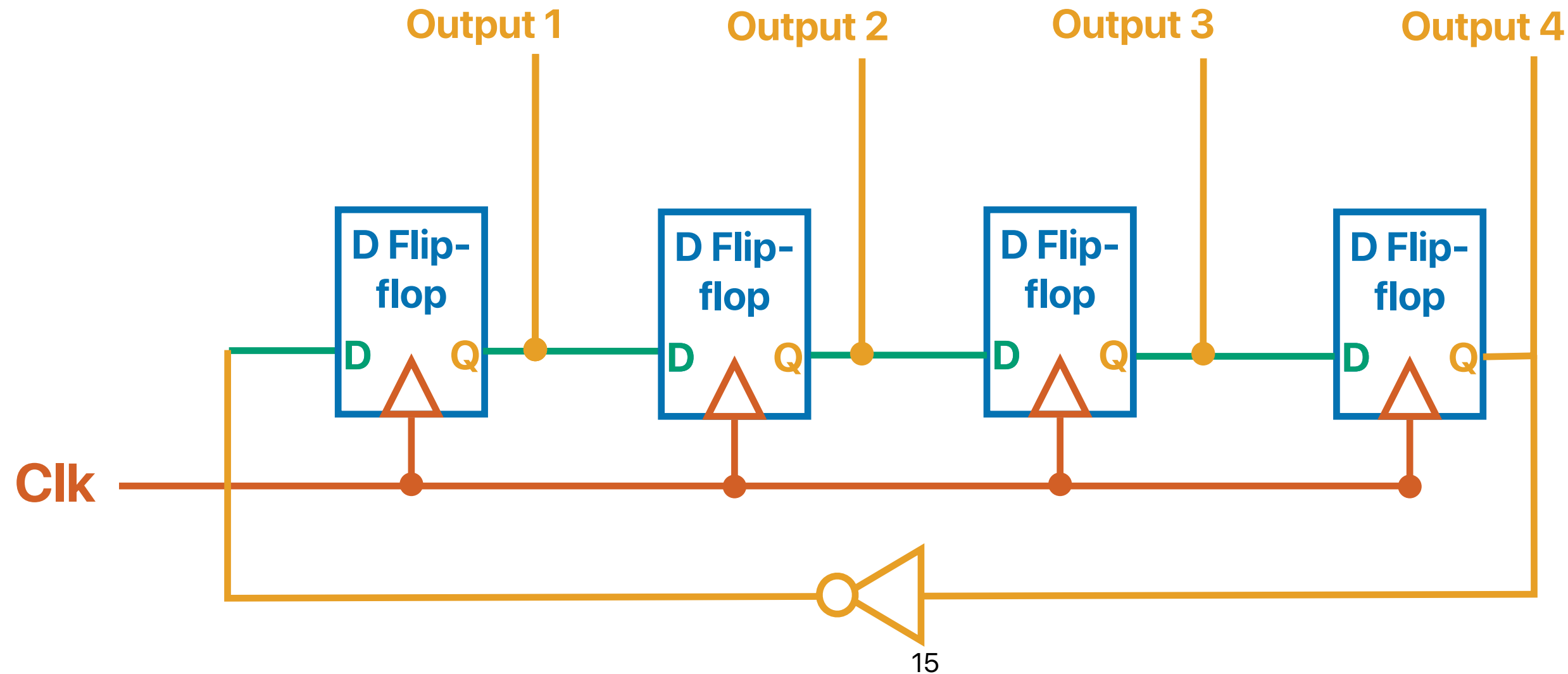
# Counters


- Sequences through a fixed set of patterns
- Note: definition is general
- For example, the one in the figure is a type of counter called Linear Feedback Shift Register (LFSR)




# **Static Random Access Memory (SRAM)**




# A Classical 6-T SRAM Cell

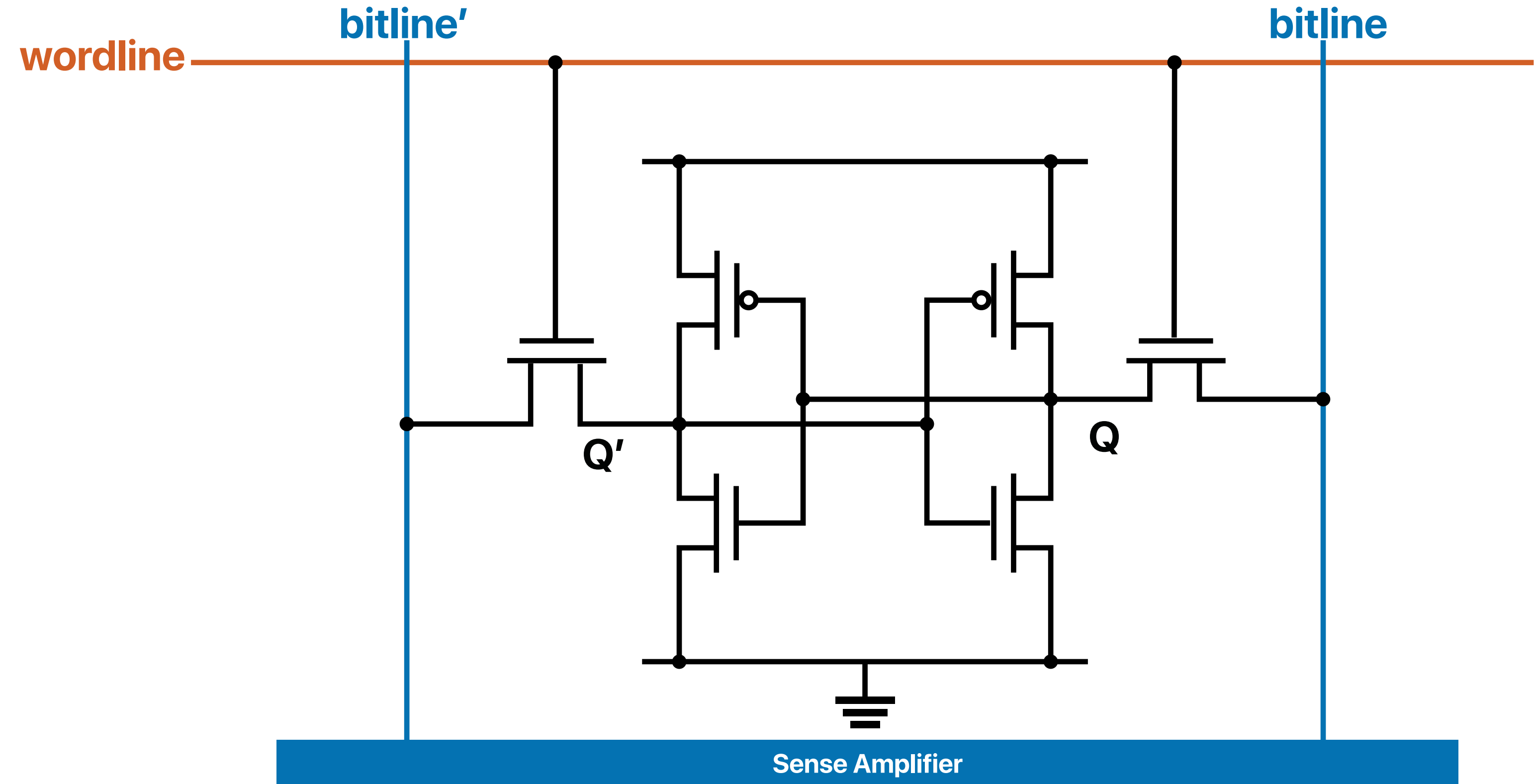


# A Classical 6-T SRAM Cell

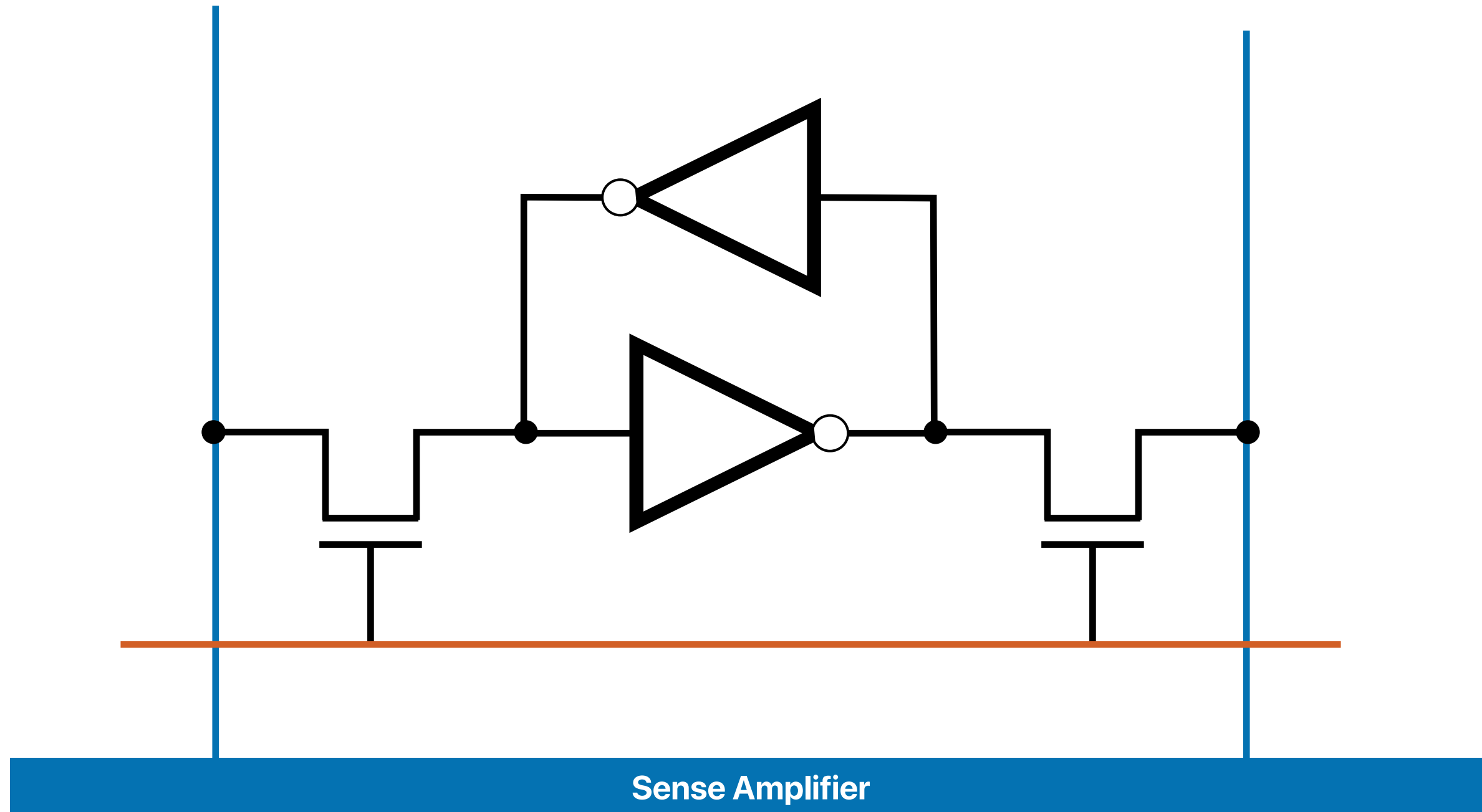


# Write "1" to an SRAM Cell

 


# Write "0" to an SRAM Cell

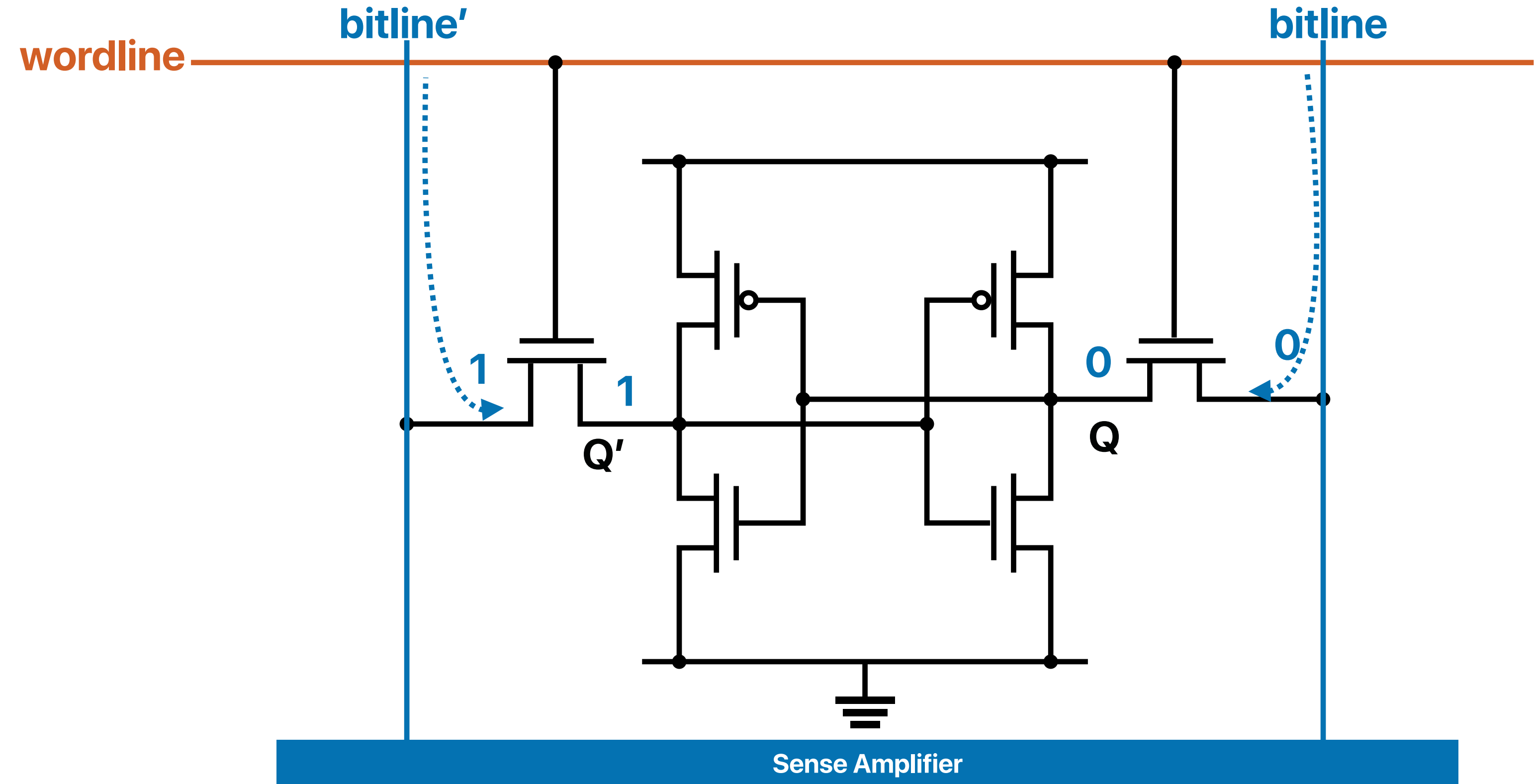

# Reading from an SRAM Cell

 


# SRAM array

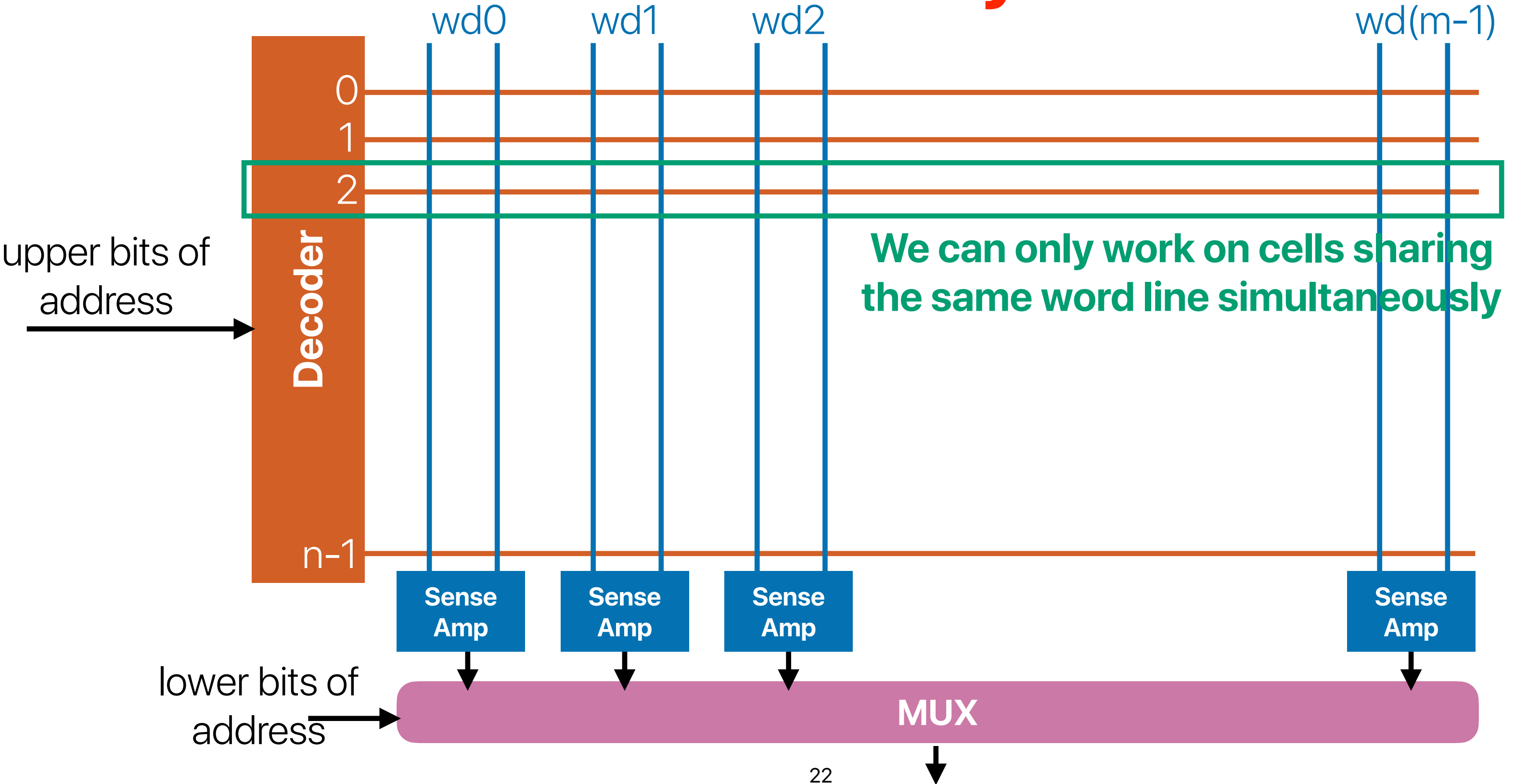

# **Dynamic Random Access Memory (DRAM)**


# An DRAM cell

 

- 1 transistor (rather than 6)
- Relies on large capacitor to store bit
  - Write: transistor conducts, data voltage level gets stored on top plate of capacitor
  - Read: look at the value of d
- Problem: Capacitor discharges over time
  - Must "refresh" regularly, by reading d and then writing it right back



# DRAM array

 

# Register v.s. DRAM v.s. SRAM

- Consider the following memory elements
  - ① 64\*64-bit Registers
  - ② 512B SRAM
  - ③ 512B DRAM
- A. Area: (1) > (2) > (3) Delay: (1) < (2) < (3)
- B. Area: (1) > (3) > (2) Delay: (1) < (3) < (2)
- C. Area: (3) > (1) > (2) Delay: (1) < (3) < (2)
- D. Area: (3) > (2) > (1) Delay: (3) < (2) < (1)
- E. Area: (2) > (3) > (1) Delay: (2) < (3) < (1)

# Register v.s. DRAM v.s. SRAM

- Consider the following memory elements

① 64\*64-bit Registers

② 512B SRAM

③ 512B DRAM

A. Area: (1) > (2) > (3) Delay: (1) < (2) < (3)


B. Area: (1) > (3) > (2) Delay: (1) < (3) < (2)

C. Area: (3) > (1) > (2) Delay: (1) < (3) < (2)

D. Area: (3) > (2) > (1) Delay: (3) < (2) < (1)

E. Area: (2) > (3) > (1) Delay: (2) < (3) < (1)

# RC charging

 


$$V_b = V_R + V_C$$

$$V_b = IR + \frac{Q}{C}$$

As charging progresses,

$$V_b = IR + \frac{Q}{C}$$

 current decreases and  
charge increases.



At  $t = 0$

$$Q = 0$$

$$V_C = 0$$

$$I = \frac{V_b}{R}$$

As  $t \rightarrow \infty$

$$Q \rightarrow CV_b$$

$$V_C \rightarrow V_b$$


$$I \rightarrow 0$$

# Latency of volatile memory

	Size (Transistors per bit)	Latency (ns)
Register	18T	~ 0.1 ns
SRAM	6T	~ 0.5 ns
DRAM	1T	50-100 ns

# Programming and memory
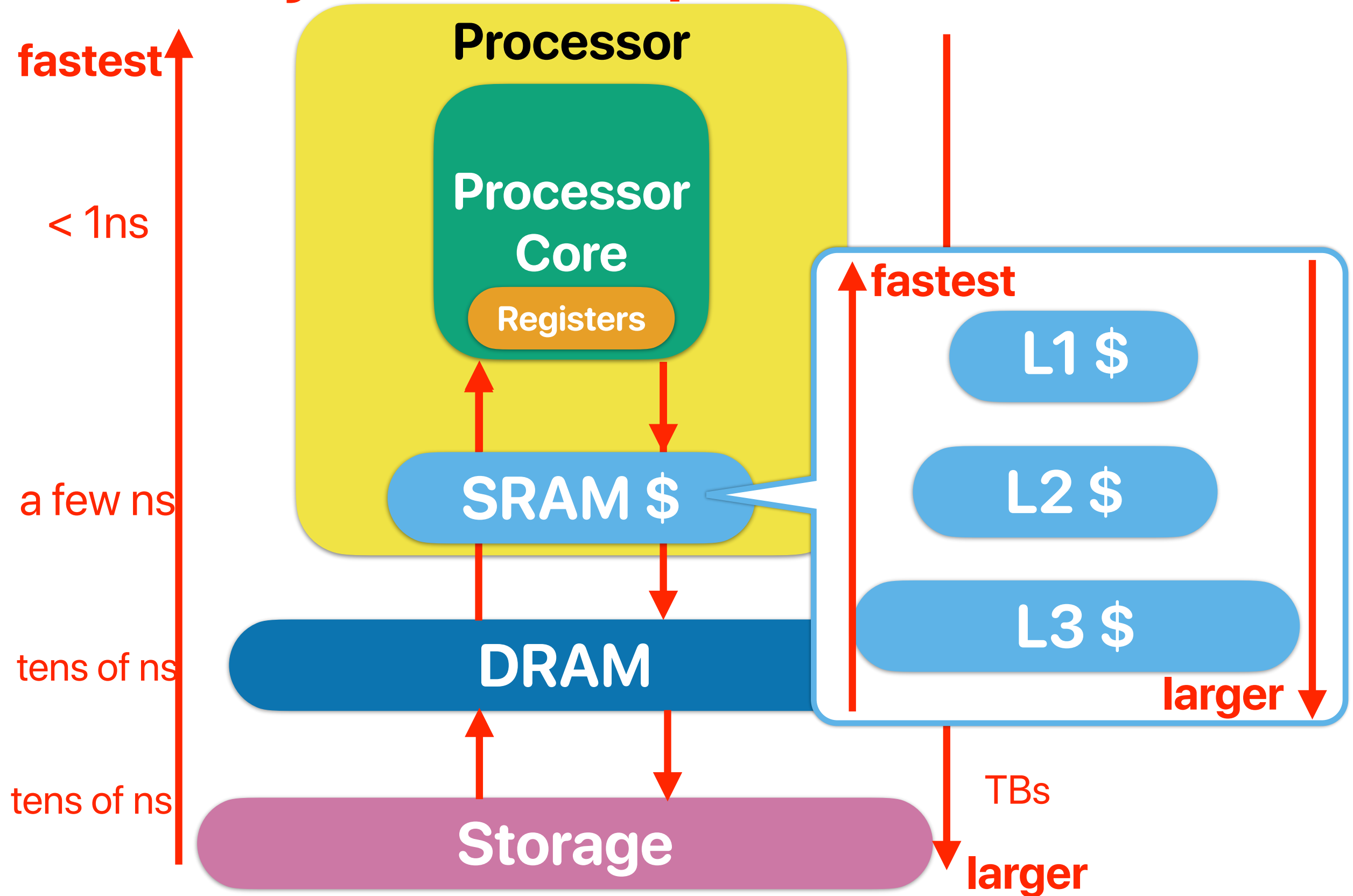
# Memory "hierarchy" in modern processor architectures



# Thinking about programming

```

struct student_record
{
    int id;
    double homework;
    double midterm;
    double final;
};

int main(int argc, char **argv)
{
    int i,j;
    double midterm_average=0.0;
    int number_of_records = 10000000;
    struct timeval time_start, time_end;
    struct student_record *records;
    records = (struct
student_record*)malloc(sizeof(struct
student_record)*number_of_records);
    init(number_of_records,records);

    for (j = 0; j < 100; j++)
        for (i = 0; i < number_of_records; i++)
            midterm_average+=records[i].midterm;

    printf("average: %lf\n",midterm_average/
number_of_records);
    free(records);
    return 0;
}

```

```

int main(int argc, char **argv)
{
    int i,j;
    double midterm_average=0.0;
    int number_of_records = 10000000;
    struct timeval time_start, time_end;
    id = (int*)malloc(sizeof(int)*number_of_records);
    midterm = (double*)malloc(sizeof(double)*number_of_records);
    final = (double*)malloc(sizeof(double)*number_of_records);
    homework = (double*)malloc(sizeof(double)*number_of_records);
    init(number_of_records);

    for (j = 0; j < 100; j++)
        for (i = 0; i < number_of_records; i++)
            midterm_average+=midterm[i];

    free(id);
    free(midterm);
    free(final);
    free(homework);
    return 0;
}

```

- Which side is faster in executing the for-loop?
  - A. Left
  - B. Right
  - 32C. About the same



# Thinking about programming

```
struct student_record
{
    int id;
    double homework;
    double midterm;
    double final;
};

int main(int argc, char **argv)
{
    int i,j;
    double midterm_average=0.0;
    int number_of_records = 10000000;
    struct timeval time_start, time_end;
    struct student_record *records;
    records = (struct
student_record*)malloc(sizeof(struct
student_record)*number_of_records);
    init(number_of_records,records);

    for (j = 0; j < 100; j++)
        for (i = 0; i < number_of_records; i++)
            midterm_average+=records[i].midterm;

    printf("average: %lf\n",midterm_average/
number_of_records);
    free(records);
    return 0;
}
```

```
int main(int argc, char **argv)
{
    int i,j;
    double midterm_average=0.0;
    int number_of_records = 10000000;
    struct timeval time_start, time_end;
    id = (int*)malloc(sizeof(int)*number_of_records);
    midterm = (double*)malloc(sizeof(double)*number_of_records);
    final = (double*)malloc(sizeof(double)*number_of_records);
    homework = (double*)malloc(sizeof(double)*number_of_records);
    init(number_of_records);

    for (j = 0; j < 100; j++)
        for (i = 0; i < number_of_records; i++)
            midterm_average+=midterm[i];

    free(id);
    free(midterm);
    free(final);
    free(homework);
    return 0;
}
```

**More row buffer hits in the  
DRAM, more SRAM hits**

- Which side is faster in executing the for-loop?

A. Left

B. Right

33 C. About the same

# Thinking about programming (2)

```

struct student_record
{
    int id;
    double homework;
    double midterm;
    double final;
};

int main(int argc, char **argv)
{
    int i,j;
    double midterm_average=0.0;
    int number_of_records = 10000000;
    struct timeval time_start, time_end;
    struct student_record *records;
    records = (struct
student_record*)malloc(sizeof(struct
student_record)*number_of_records);
    init(number_of_records,records);

    for (j = 0; j < 100; j++)
        for (i = 0; i < number_of_records; i++)
            midterm_average+=records[i].midterm;

    printf("average: %lf\n",midterm_average/
number_of_records);
    free(records);
    return 0;
}

```

```

int main(int argc, char **argv)
{
    int i,j;
    double midterm_average=0.0;
    int number_of_records = 10000000;
    struct timeval time_start, time_end;
    id = (int*)malloc(sizeof(int)*number_of_records);
    midterm = (double*)malloc(sizeof(double)*number_of_records);
    final = (double*)malloc(sizeof(double)*number_of_records);
    homework = (double*)malloc(sizeof(double)*number_of_records);
    init(number_of_records);

    for (j = 0; j < 100; j++)
        for (i = 0; i < number_of_records; i++)
            midterm_average+=midterm[i];

    free(id);
    free(midterm);
    free(final);
    free(homework);
    return 0;
}

```

- Which side is consuming less memory?
  - A. Left
  - B. Right
  - C. About the same


# Thinking about programming (2)

```
struct student_record
{
    int id;
    double homework;
    double midterm;
    double final;
};

int main(int argc, char **argv)
{
    int i,j;
    double midterm_average=0.0;
    int number_of_records = 10000000;
    struct timeval time_start, time_end;
    struct student_record *records;
    records = (struct
student_record*)malloc(sizeof(struct
student_record)*number_of_records);
    init(number_of_records,records);

    for (j = 0; j < 100; j++)
        for (i = 0; i < number_of_records; i++)
            midterm_average+=records[i].midterm;

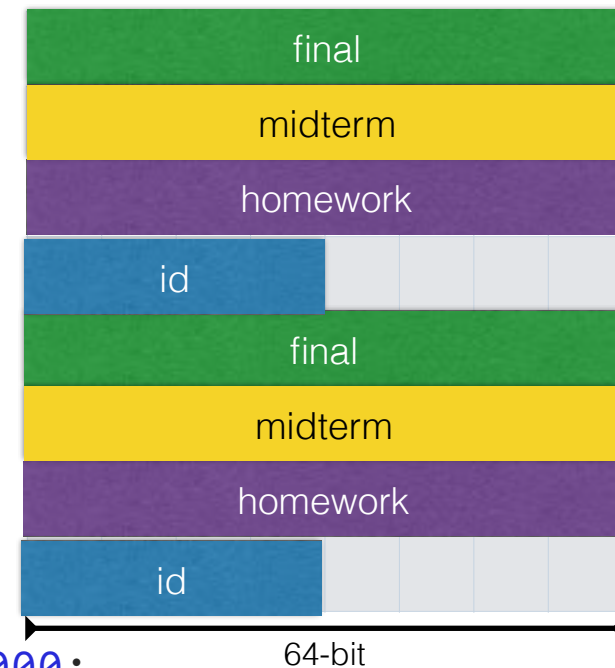    printf("average: %lf\n",midterm_average/
number_of_records);
    free(records);
    return 0;
}
```



```
int main(int argc, char **argv)
{
    int i,j;
    double midterm_average=0.0;
    int number_of_records = 10000000;
    struct timeval time_start, time_end;
    id = (int*)malloc(sizeof(int)*number_of_records);
    midterm = (double*)malloc(sizeof(double)*number_of_records);
    final = (double*)malloc(sizeof(double)*number_of_records);
    homework = (double*)malloc(sizeof(double)*number_of_records);
    init(number_of_records);

    for (j = 0; j < 100; j++)
        for (i = 0; i < number_of_records; i++)
            midterm_average+=midterm[i];

    free(id);
    free(midterm);
    free(final);
    free(homework);
    return 0;
}
```

- Which side is consuming less memory?

A. Left

B. Right

C. About the same


# **Non-volatile memory**

# Volatile v.s. Non-volatile


- Volatile memory
  - The stored bits will vanish if the cell is not supplied with electricity
  - Register, SRAM, DRAM
- Non-volatile memory
  - The stored bits will not vanish “immediately” when it’s out of electricity — usually can last years
  - Flash memory, PCM, MRAM, STTRAM
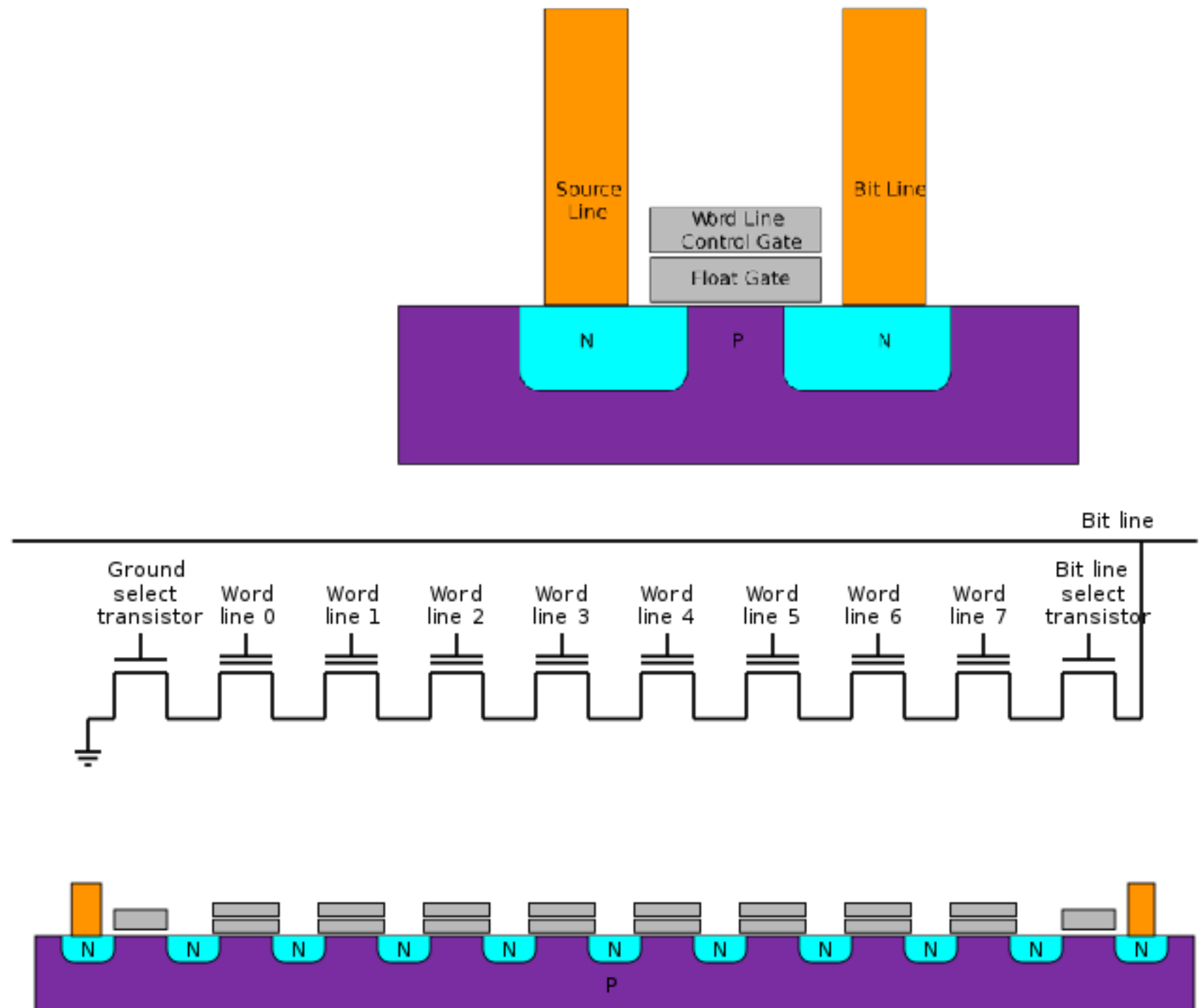
# Flash memory

- Floating gate made by polycrystalline silicon trap electrons
- The voltage level within the floating gate determines the value of the cell
- The floating gates will wear out eventually



# Basic flash operations

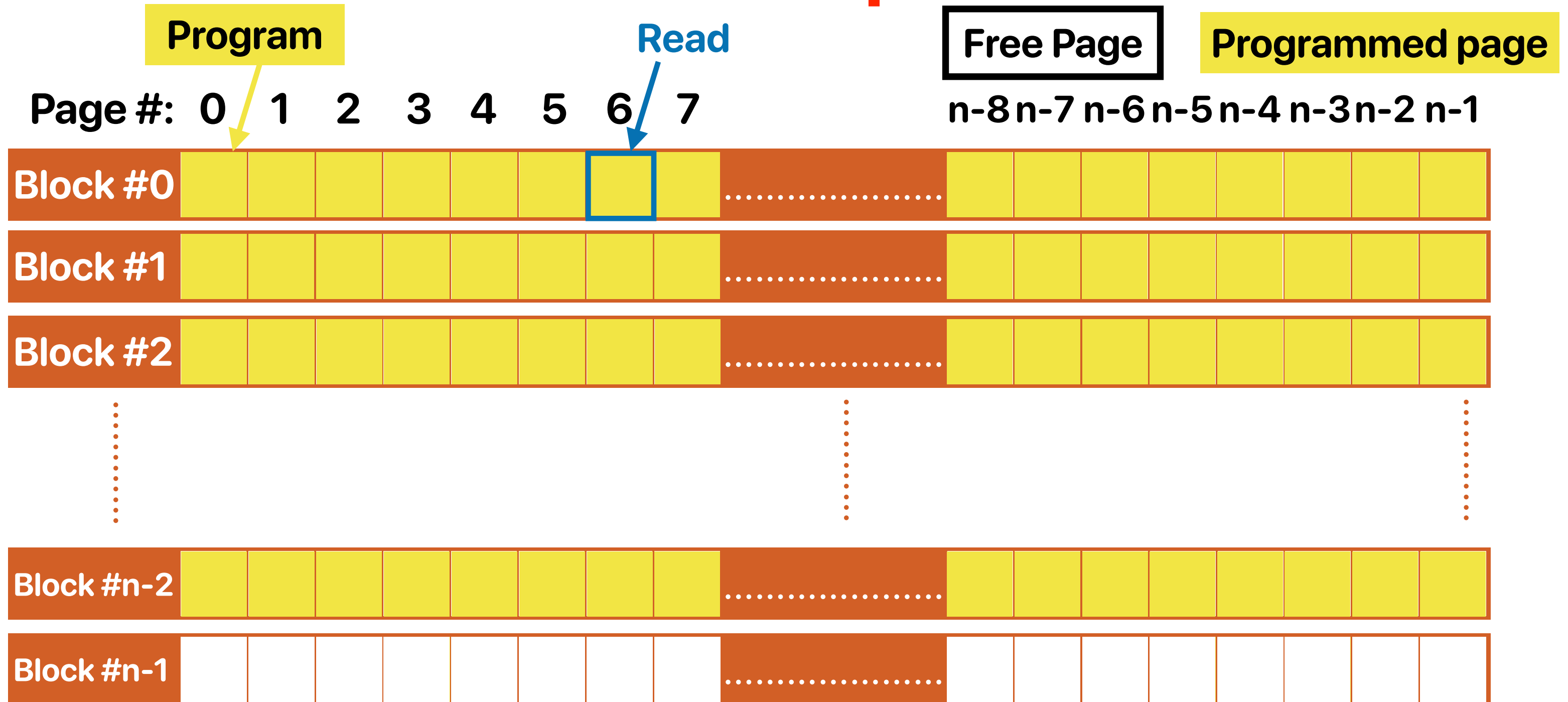

# Types of Flash Chips

2 voltage levels,  
1-bit



**Single-Level Cell  
(SLC)**

4 voltage levels,  
2-bit



**Multi-Level Cell  
(MLC)**

8 voltage levels,  
3-bit



**Triple-Level Cell  
(TLC)**

16 voltage levels,  
4-bit




**Quad-Level Cell  
(QLC)**



# Programming in MLC

4 voltage levels,  
2-bit

 


**Multi-Level Cell  
(MLC)**

**3.14000000000000001243449787580**

**= 0x40091EB851EB851F**

 **= 01000000 00001001 00011110 10111000 01010001 11101011 10000101 00011111**



**3 Cycles/Phases to finish programming**

# Announcement

- Assignment #4 due next Tuesday — **Chapter 4.8-4.9 & 5.2-5.4**
- Lab 5 is up — due next Thursday
  - Start early & plan your time carefully
  - Watch the video and read the instruction BEFORE your session
  - There are links on both course webpage and iLearn lab section
  - Submit through iLearn > Labs
- Check your grades in iLearn

# Electrical Computer Science Engineering

# 120A

# つづく

