

ME 133 lecture 11 2/10/2022


Digital circuits Ch-6

- Input signal processing
 - digital controller
 - Display.
-

Today :

- digital representations
- Combinational logic
- Timing Diagrams

What is an analog signal?

 

- changes continuously
- infinite values
- 'analog' → signal represents some other physical quantity



Digital Signals

- Can only take discrete values



→ Binary signal

[on/off
true/false
0, 1

→ Boolean logic

→ binary numbers

Digital Representation

What does base of a number system mean?

Base = # of possible symbols to represent a digit

10 $\rightarrow$ 0, 1, 2, 3, 4, 5, 6, 7, 8, 9

Base 10:

$$\begin{aligned} d_{n-1} \dots d_3 d_2 d_1 d_0 &= d_{n-1} \cdot 10^{n-1} \\ &+ \vdots \\ &+ d_3 \cdot 10^3 \\ &+ d_2 \cdot 10^2 \\ &+ d_1 \cdot 10^1 \\ &+ d_0 \cdot 10^0 \end{aligned}$$

$$\begin{aligned} \text{Ex. } 123 &= 1 \times 10^2 + 2 \cdot 10^1 + 3 \times 10^0 \\ &\quad 100 \quad + 20 \quad + 3 \\ &= 123 \end{aligned}$$

→ you can include fractions!
 $(d_{-1}, d_{-2}, \dots)$

Binary Representation (Base 2)

Why? → fundamental operation of digital device can only be on or off (we are using transistors)

$$d_{n-1} \dots d_3 d_2 d_1 d_0 = d_{n-1} \cdot 2^{n-1}$$

+
 $\vdots$

$$\begin{aligned} &+ d_3 2^3 + d_2 2^2 \\ &+ d_1 2^1 + d_0 2^0 \end{aligned}$$

$$\boxed{d_i = 1 \text{ or } 0}$$

Ex.

$$\begin{array}{cccc} & 1 & 1 & 0 & 1 \\ & \swarrow & \downarrow & \downarrow & \swarrow \\ d_3 & d_2 & d_1 & d_0 & \end{array} \quad 1101 = 1 \cdot 2^3 + 1 \cdot 2^2 + 0 \cdot 2^1 + 1 \cdot 2^0$$
$$= 8 + 4 + 0 + 1$$
$$= \underline{\underline{13}}$$

Digit in binary called Bits.

MSB: most significant bit
furthest left
highest power of 2.

LSB: least significant bit.

Byte: 8 bits

→ typically smallest
unit used in hardware
e.g. for addresses

From Wiki:

Byte - basic characters (A, B, C ...)
256

Kilobyte - 1024
(2^{10}) Bytes
"Jabberwocky"

megabyte - (2^{20}) Bytes
Harry Potter

gigabyte - (2^{30}) Bytes
half hour video

terabyte - (2^{40}) Bytes
→ largest consumer harddrive
in 2001

petabyte - (2^{50})
2000 years of MP3
music.

Binary Arithmetic

$$\begin{array}{r} 9 \\ + 3 \\ \hline 12 \end{array}$$

$$9 = 1 \cdot 2^3 + 0 \cdot 2^2 + 0 \cdot 2^1 + 1 \cdot 2^0$$
$$1001$$

$$3 = 0011$$

$$\begin{array}{r} 11 \\ 1001 \\ + 0011 \\ \hline 1100 \end{array} \rightarrow$$

$$1 \cdot 2^3 + 1 \cdot 2^2 = \underline{12}$$

$$\begin{array}{r} 9 \\ \times 3 \\ \hline 27 \end{array}$$

$$\begin{array}{r} 1001 \\ \times 0011 \\ \hline 1001 \\ 1001 \\ 0000 \\ 0000 \\ \hline 11011 \rightarrow 27 \end{array}$$

Binary is annoying to write ;
read

Hexadecimal is extensively used
for programming devices

base 16 { 0, ..., 9,

A, B, C, D, E, F
10 11 12 13 14 15

$$9A = 9 \cdot 16^1 + 10 \cdot 16^0$$

$$123_{10} = \underbrace{0111}_7 \underbrace{1011}_B_2 = \underbrace{0x7B}$$


ASCII: American Standard Code
for Information Interchange



for example :

char myvar = 'a'
myvar == 56.

Combinational logic

 


"gates" → control flow of signals

Truth Table

- a way to display
all possible combos of input/output


0. Inverter

Inverter

 

A	C
0	1
1	0


AND

 

$$C = A \cdot B$$

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1


NAND

 

$$C = \overline{A \cdot B}$$

A	B	C
0	0	1
0	1	1
1	0	1
1	1	0


OR

 

$$C = A + B$$

A	B	C
0	0	0
0	1	1
1	0	1
1	1	1


NOR

 

$$C = \overline{A + B}$$

A	B	C
0	0	1
0	1	0
1	0	0
1	1	0

XOR

 


$$C = A \oplus B$$

$$= A \cdot \overline{B} + \overline{A} \cdot B$$

A	B	C
0	0	0
0	1	1
1	0	1
1	1	0

Buffer

 

A	C
0	0
1	1

- used to increase current
- important to drive multiple input with single output


'fanout'

→ max # of inputs
driven by single output

- all gates are manufactured
as integrated circuits

Example

A B C

 

$$D = A \cdot B$$

$$E = D + \bar{C} = (A \cdot B) + \bar{C}$$

$$F = \overline{E \cdot \bar{C}}$$

$$F = \overline{[(A \cdot B) + \bar{C}] \cdot \bar{C}}$$

$$D = A \cdot B$$


$$E = D + \bar{C} = (A \cdot B) + \bar{C}$$

$$F = \overline{E \cdot \bar{C}}$$

$$F = \overline{[(A \cdot B) + \bar{C}] \cdot \bar{C}}$$

A	B	C	D	E	F
0	0	0	0	1	0
0	0	1	0	0	1
0	1	0	0	1	0
0	1	1	0	0	1
1	0	0	0	1	0
1	0	1	0	0	1
1	1	0	1	1	0
1	1	1	1	1	1

AND gate w/ transistor

 


$V_A = \text{Low} \Rightarrow T_1 \text{ open}$
 $V_C = \text{Low}$

$V_B = \text{Low} \Rightarrow T_2 \text{ open}$
 $V_C = \text{Low}$

iff $V_A = V_B = \text{High}$
 $V_C = \text{High}$

V_A	V_B	V_C
0	0	0
1	0	0
0	1	0
1	1	1

OR gate

 

$V_A = \text{high}$

$V_C = \text{high}$

$V_B = \text{high}$

$V_C = \text{high}$

V_A	V_B	V_C
0	0	0
0	1	1
1	0	1
1	1	1

Timing Diagram

