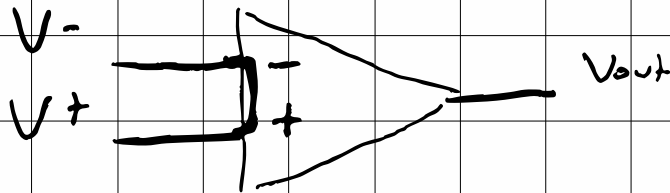


Last time:

- stepper motors
- op amps

## Ideal op-amps



$$V_{out} = A_{ol} (V_+ - V_-)$$

$\uparrow$   
 $\infty$

(1) infinite input impedance

$$I_+ = I_- = 0$$


(2) infinite gain

$$V_+ = V_-$$

(3) zero output impedance

$V_{out}$  is independent of  $I_{out}$


Example : Inverting Amplifier

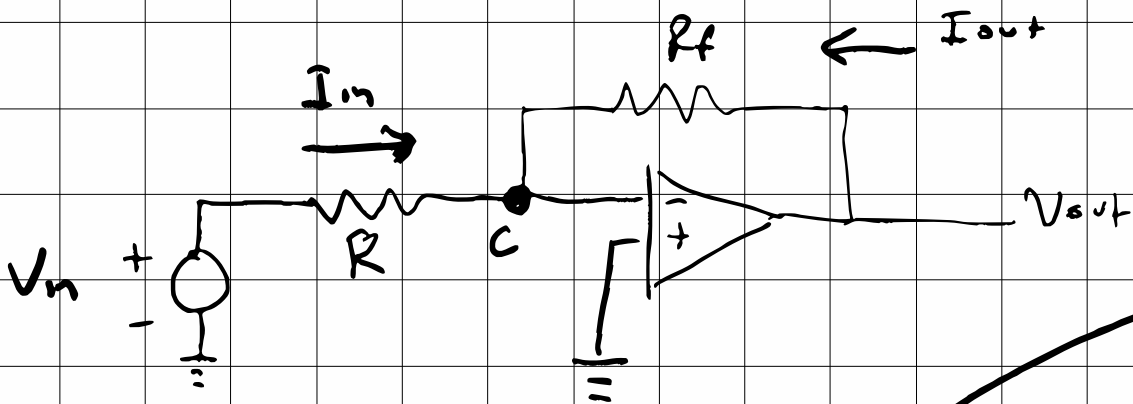

```

Node C

```

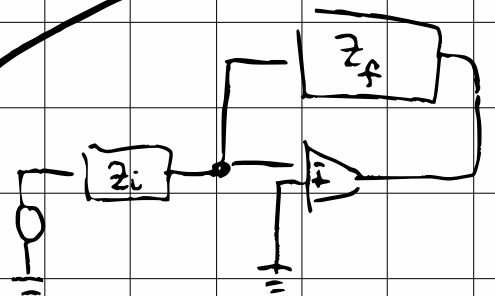

$$\begin{cases} I_{in} = -I_{out} \\ V_L = 0 \end{cases}$$

$$\frac{V_{out}}{V_{in}} = - \frac{Z_f}{Z_i}$$



$$\frac{V_{in}}{R} = I_{in}$$

$$\frac{V_{out}}{R_f} = I_{out}$$

$$\frac{V_{in}}{R} = - \frac{V_{out}}{R_f}$$

$$\frac{V_{out}}{V_{in}} = - \frac{R_f}{R}$$

# Example : non-inverting Amp 1.1er

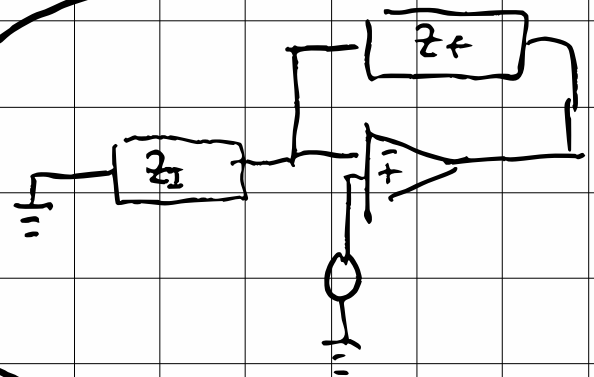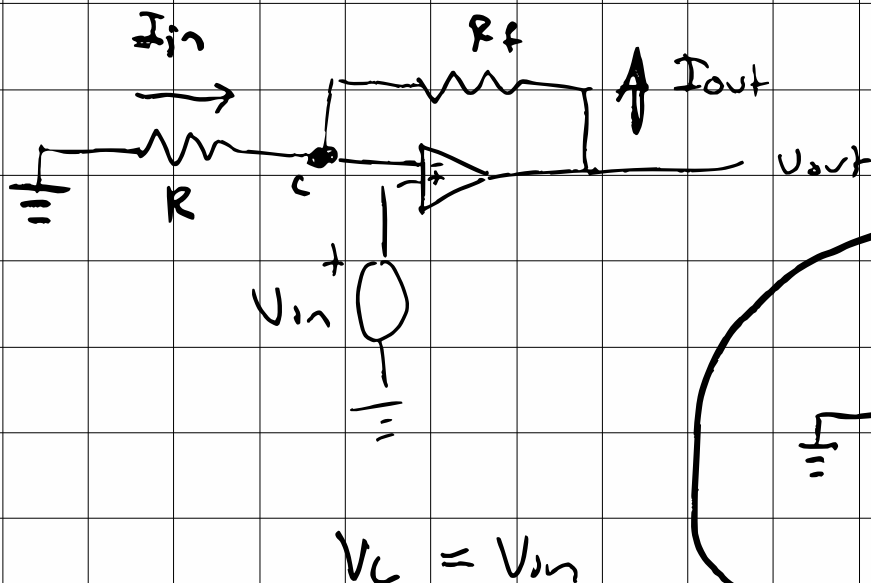

KCL @ C :  $I_{in} = -I_{out}$

$$\frac{V_{out}}{V_{in}} = \left(1 + \frac{Z_f}{Z_1}\right)$$


$$I_{in} = -\frac{V_c}{R} = -\frac{V_{in}}{R}$$

$$I_{out} = \frac{V_{out} - V_{in}}{R_f}$$

$$-\frac{V_{in}}{R} = -\frac{(V_{out} - V_{in})}{R_f}$$


$$\boxed{\frac{V_{out}}{V_{in}} = \left(1 + \frac{R_f}{R}\right)}$$

Example : Buffer.

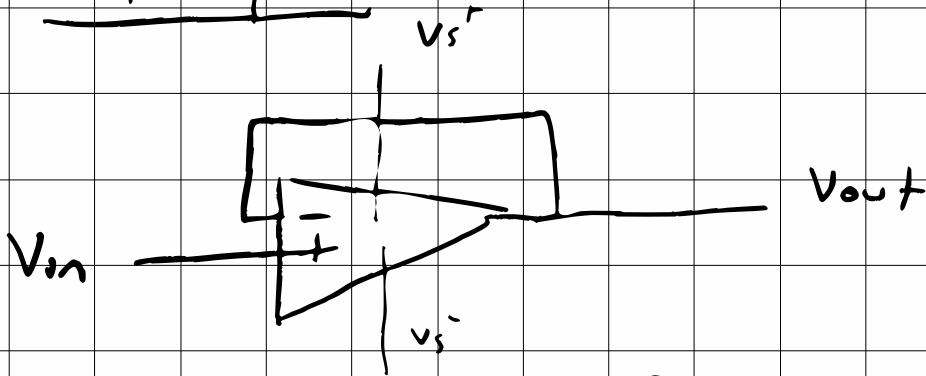


$$\frac{V_{out}}{V_{in}} = \left( 1 + \frac{R_f}{R} \right) = 1$$

$$\frac{R_f}{R} \rightarrow 0$$

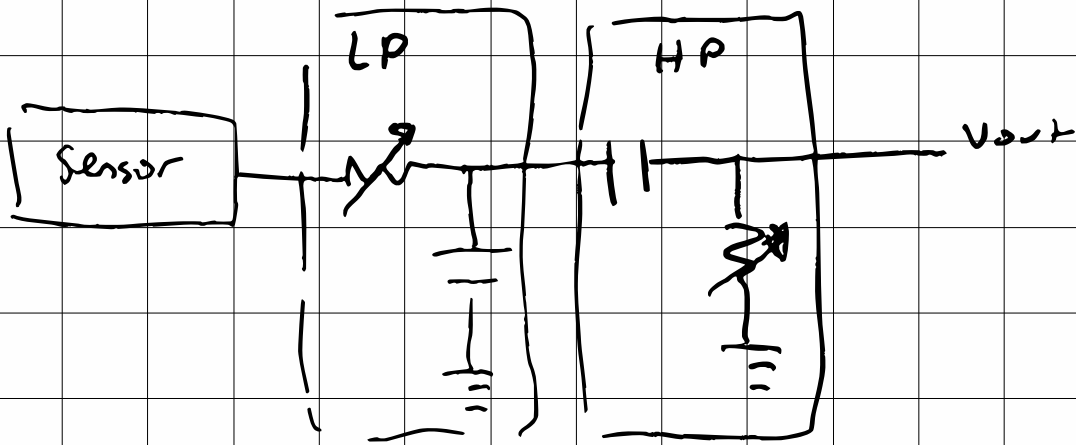


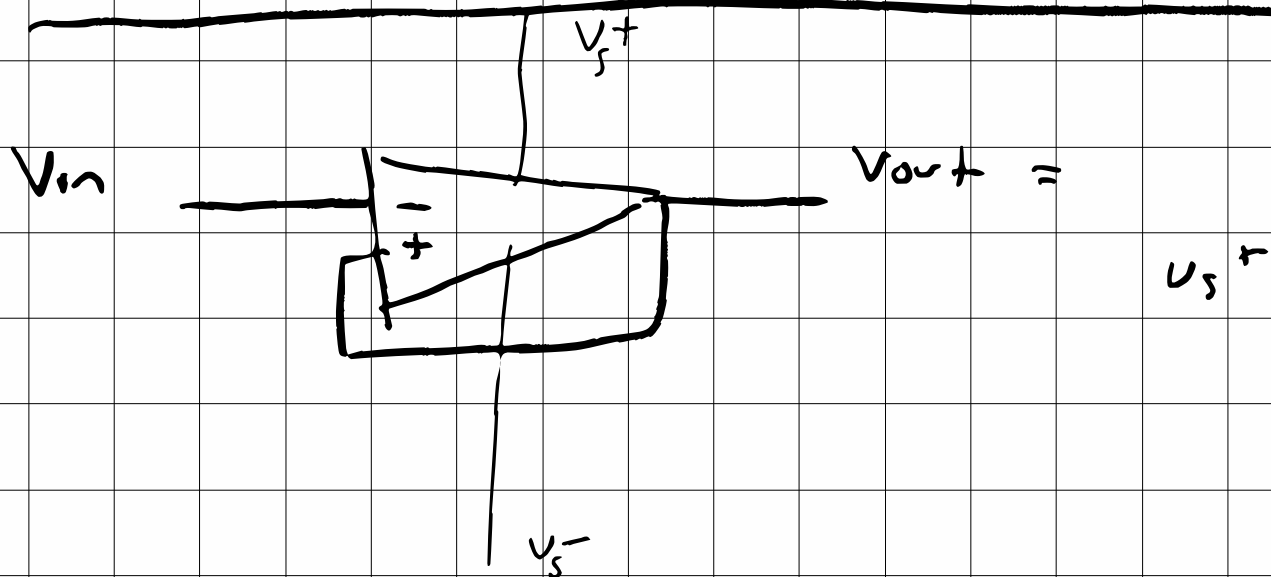\* Buffers isolate output stage from input stage and therefore doesn't load the upstream circuits




What's an example of positive feedback?

Example: summer

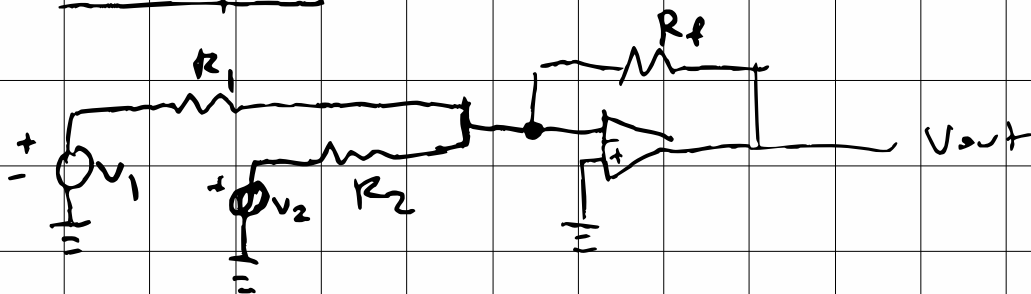

Example :

Summer

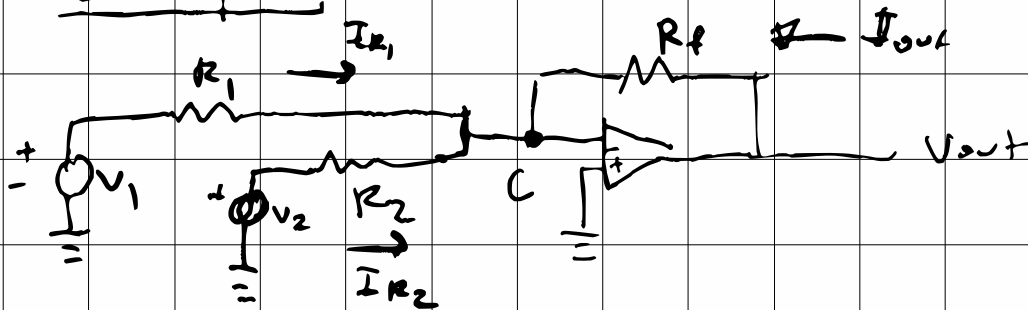

$$V_c = 0$$


KCL @ Node C :

$$\rightarrow I_{R1} + I_{R2} = -I_{out}$$

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} = -\frac{V_{out}}{R_f}$$

$$V_{out} = -\left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2\right)$$

## Example: Integrator

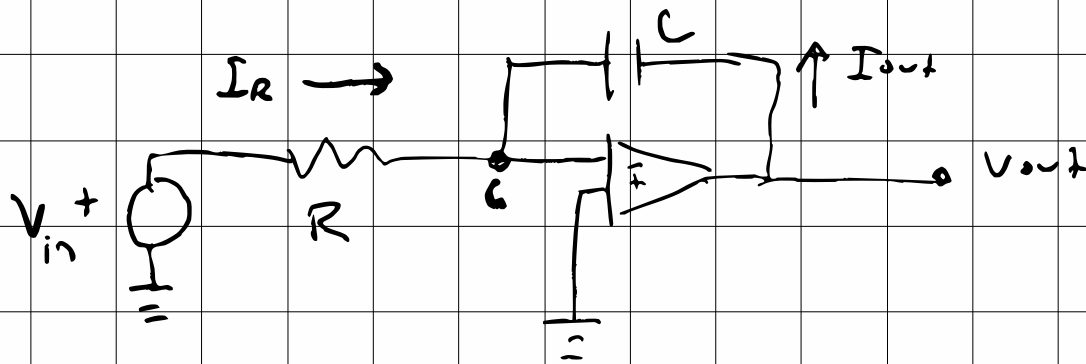

$$V_c = 0$$

KCL:  $I_R = -I_{out}$


$$\Rightarrow \frac{V_{in}}{R} = -C \frac{dV_{out}}{dt}$$

$$\Rightarrow \frac{dV_{out}}{dt} = -\frac{1}{RC} \cdot V_{in}$$

$$V_{out} = -\frac{1}{RC} \int_0^t V_{in} dt$$

$$V_{out}(t) = -\frac{1}{RC} \int_0^t V_{in}(\tau) d\tau$$

## Example: Differentiator

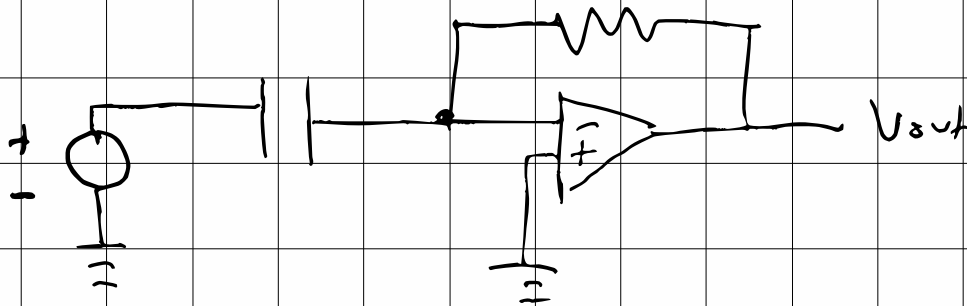


$$V_{out} = -RC \dot{V}_{in}$$

---



## Comparator


No feedback

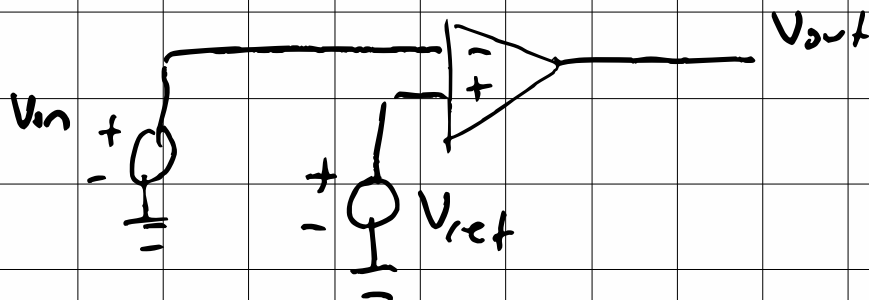

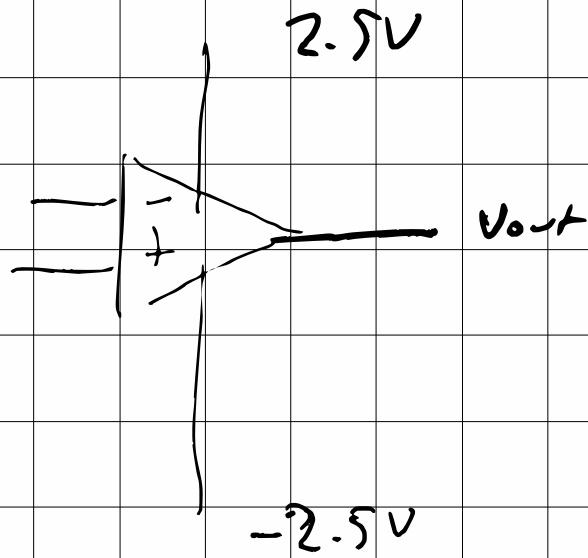
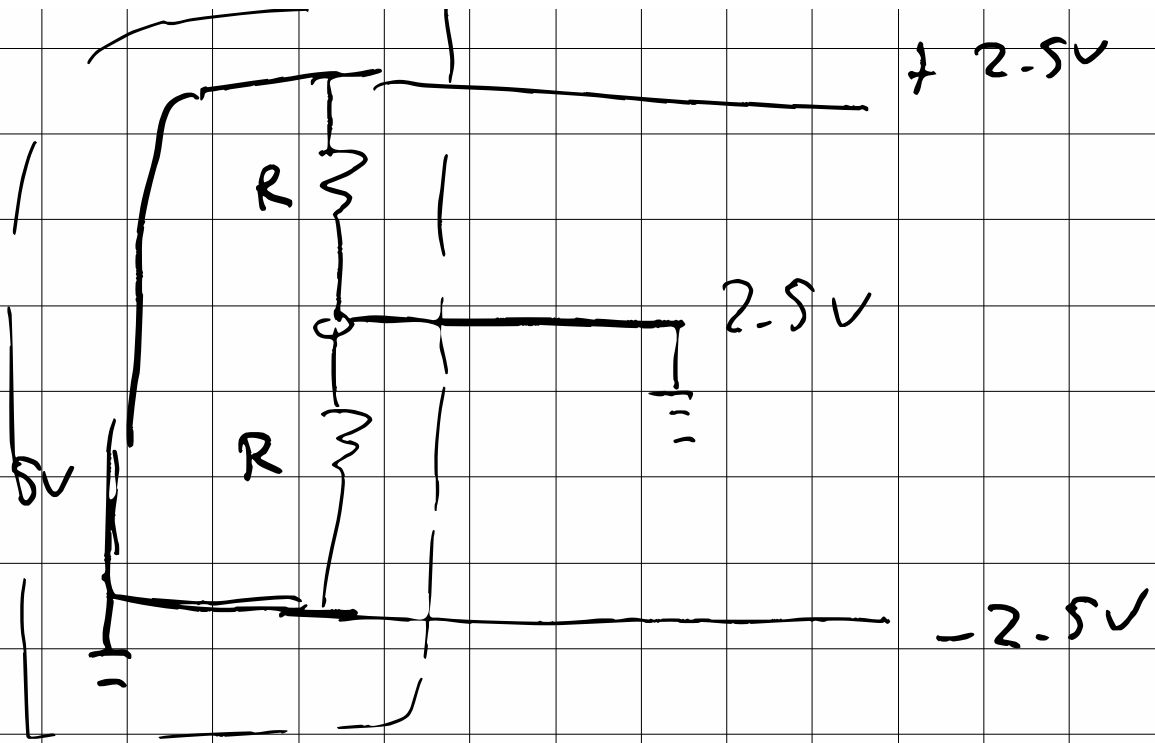
$$V_{out} = \begin{cases} +V_{sat} & V_{in} > V_{ref} \\ -V_{sat} & V_{in} < V_{ref} \end{cases}$$





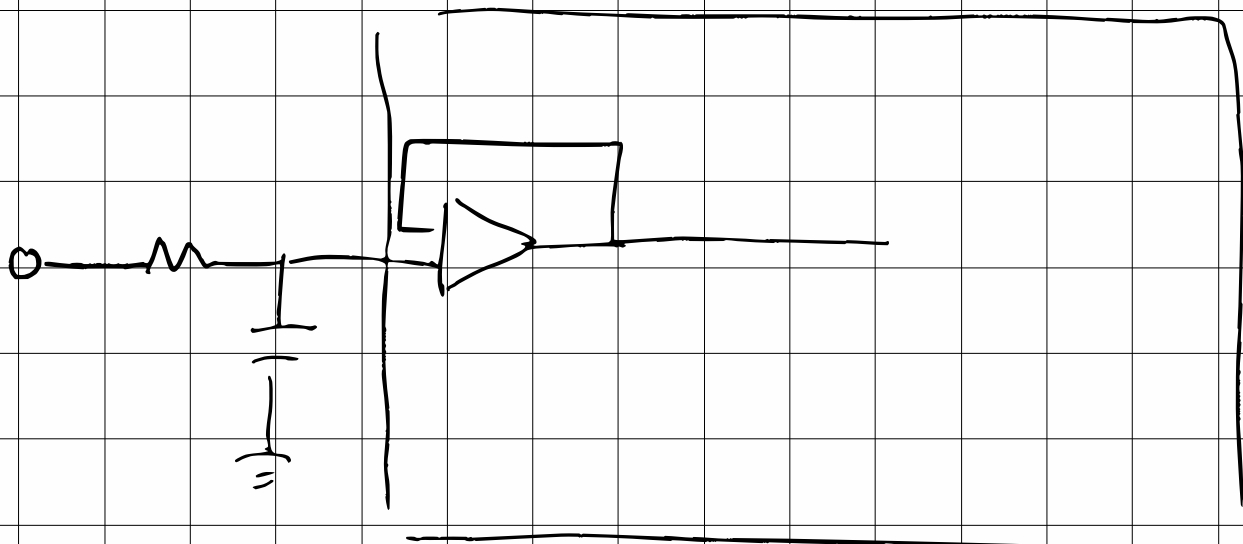

## Active Filters

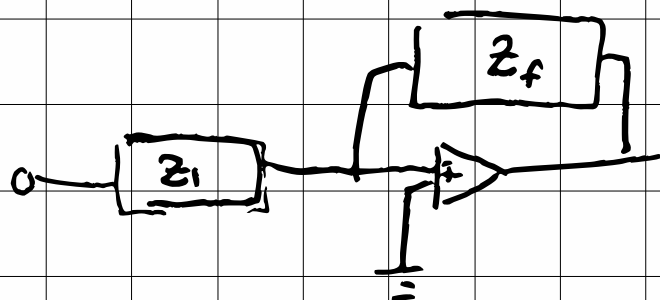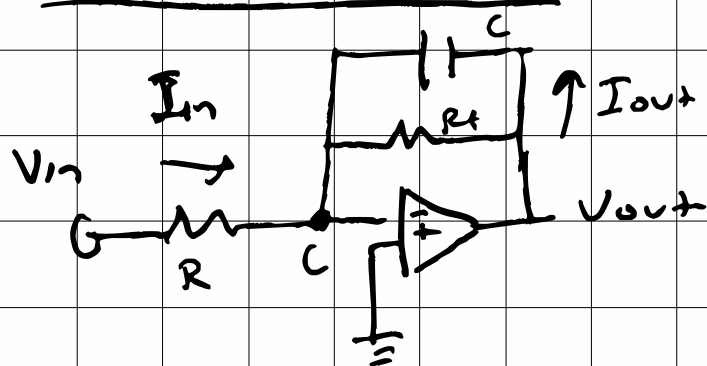


$$I_{in} = -I_{R_f} - I_C$$

$$\frac{V_{in}}{R} = -\frac{V_{out}}{R_f} - Cj\omega V_{out}$$

...

$$\frac{V_{out}}{V_{in}} = -\frac{R_f}{R} \left( \frac{1}{1 + CRj\omega} \right)$$

# Sample & Hold circuit

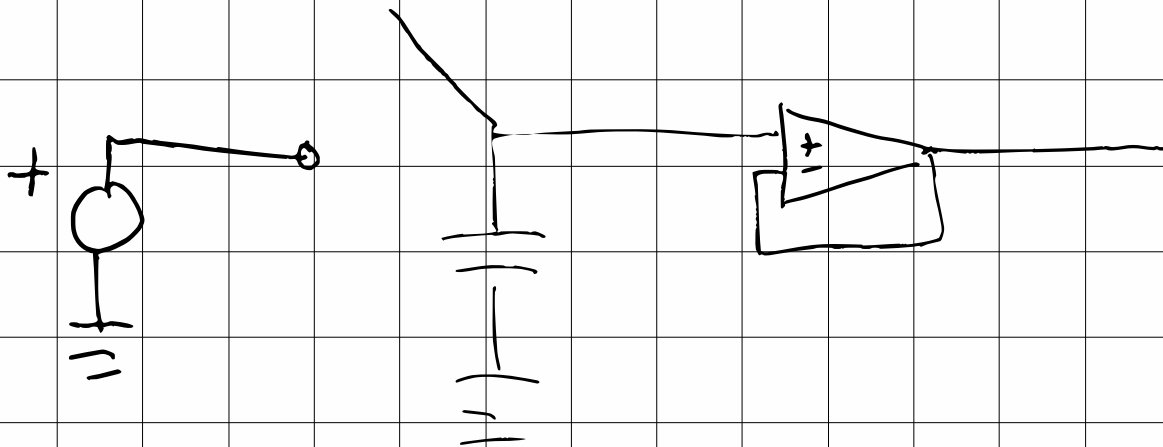


$$V_{out}(t) = V_{in}(t) \quad \text{Switch closed}$$

$$V_{out}(t - t_{sample}) = V_{in}(t_{sample})$$

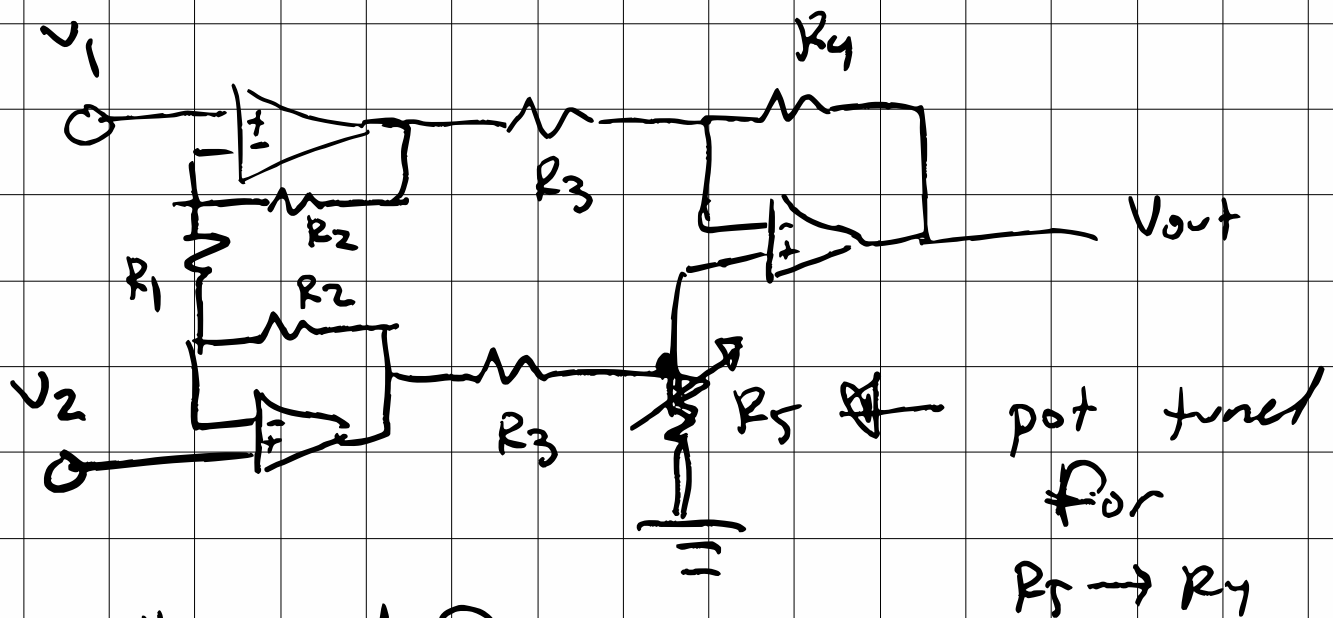
# Instrumentation Amplifier

\* most important amplifier for differential measurement



really good @

Common mode rejection

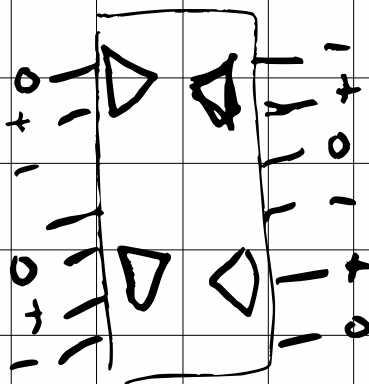

Example package.