

ME 133 lecture 17.

3/3

Final

March 14 8am - 11am


SKZ

last time

→ sensors

ADC


Analog to digital Converter

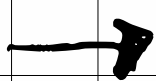


most widely used

successive approximation

ADC overview :

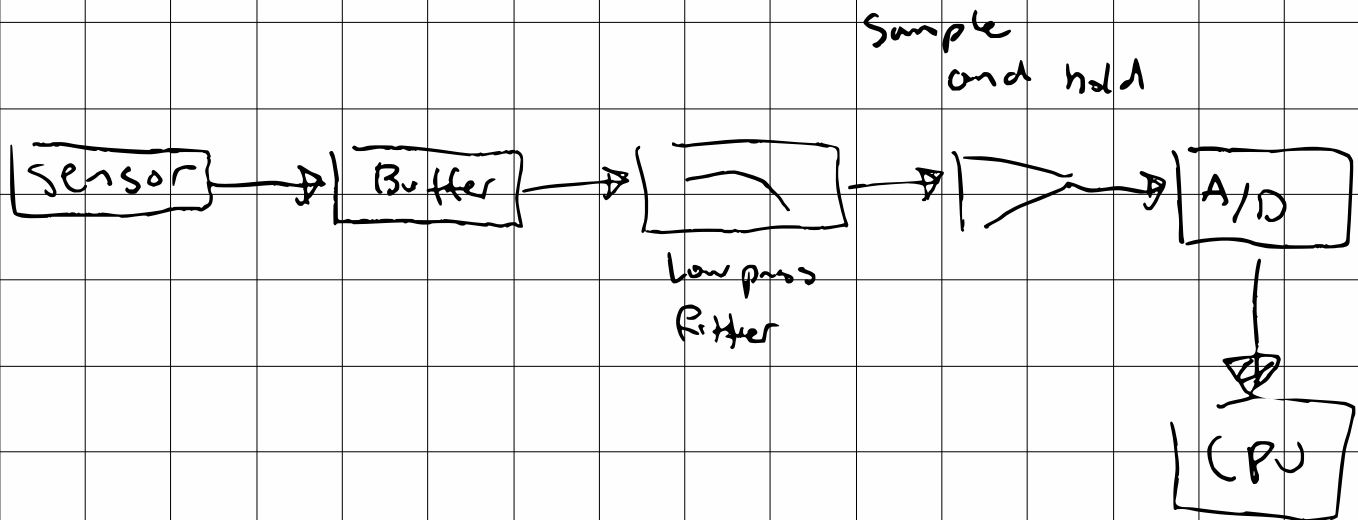

Successive approximation

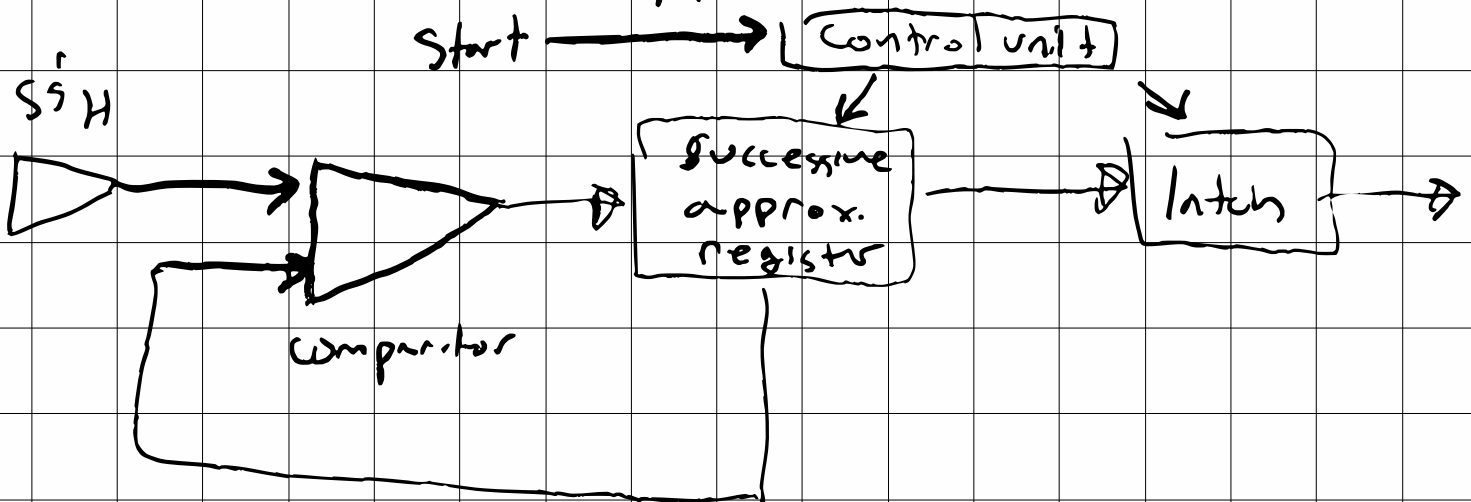

Exam Structure

- 4-5 problems (1 hr 20 mins)
 - no numerical calculations
 - two sheets of notes
 - mix of conceptual & symbolic derivations
-

Ch. 6 Digital Circuits

- digital vs analog signals
- Binary number
- Boolean logic

• Numerical Representation

$$d_{n-1} \dots d_2 d_1 d_0 = d_{n-1} \cdot 10^{n-1}$$

$$+ \vdots$$

base 10

$$+ d_2 \cdot 10^2$$

$$+ d_1 \cdot 10^1$$

$$+ d_0 \cdot 10^0$$

$$d_{n-1} \dots d_2 d_1 d_0 = d_{n-1} \cdot 2^{n-1}$$

$$\vdots$$

$$+ d_2 \cdot 2^2$$

$$+ d_1 \cdot 2^1$$

$$+ d_0 \cdot 2^0$$

- Bits

- MSB vs LSB


- Byte

- Binary Arithmetic







$$\begin{array}{r} \overset{1}{1} \overset{1}{0} \overset{1}{0} \overset{1}{1} \\ + \quad 0011 \\ \hline 1100 \end{array} \rightarrow 12$$


$$\begin{array}{r} 9 \\ + 3 \\ \hline 12 \end{array}$$

Combinational Logic

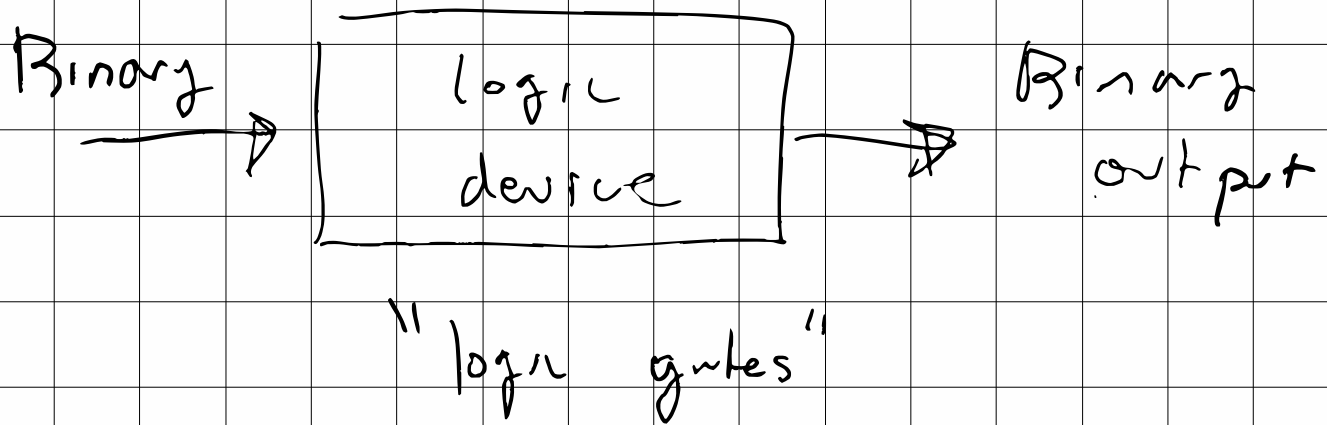

logic gates

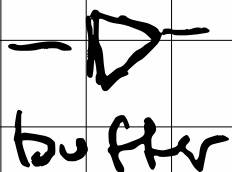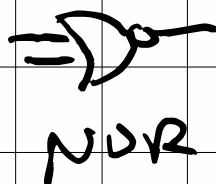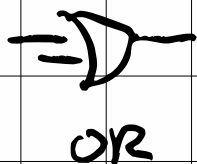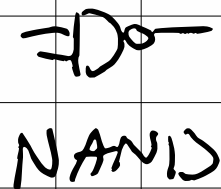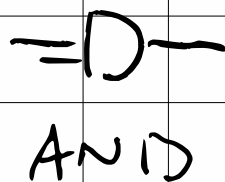
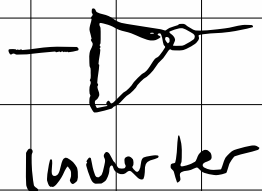


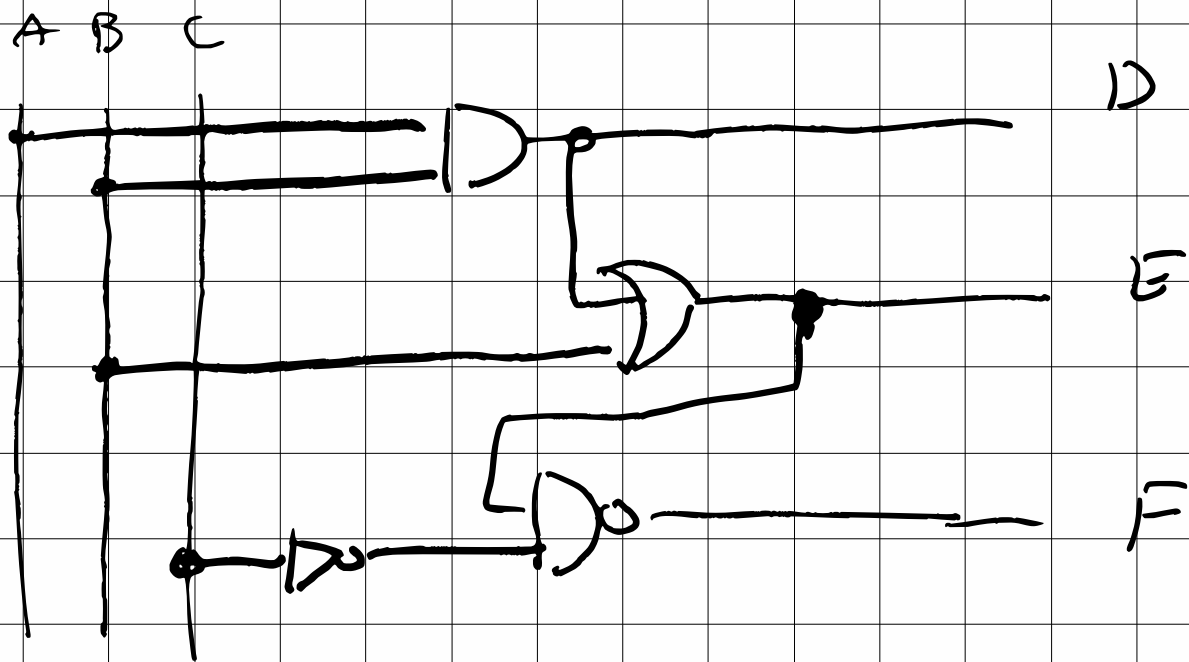

D = ? E = ? F = ?

• Truth tables

• Timing Diagram

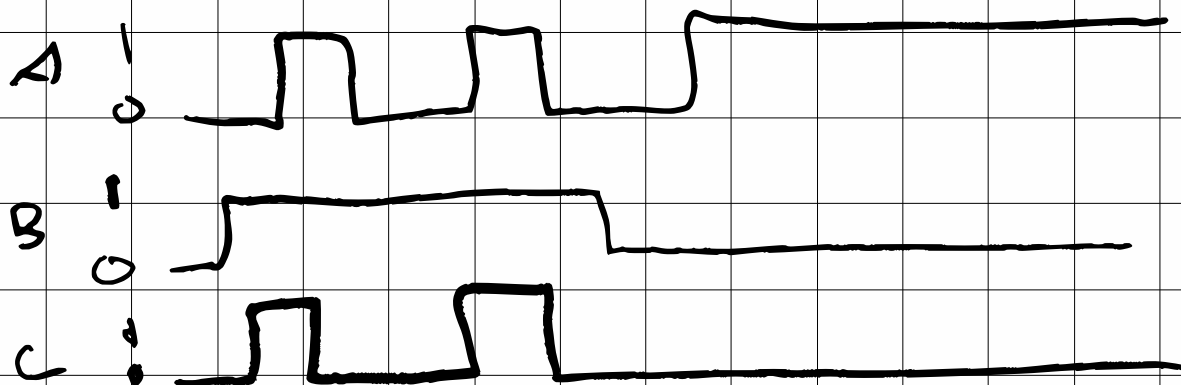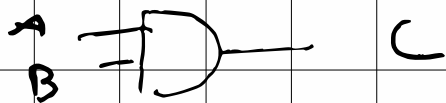

Boolean Algebra

- Fundamental Laws

- Commutative law

- Associative

- Distributive

- De Morgan's Laws


- Design logic Network

→ like the alarm
example

Ch. 10 Actuators

- Identify different actuators
 - solenoids
 - electric motors
-


- Fundamental principle

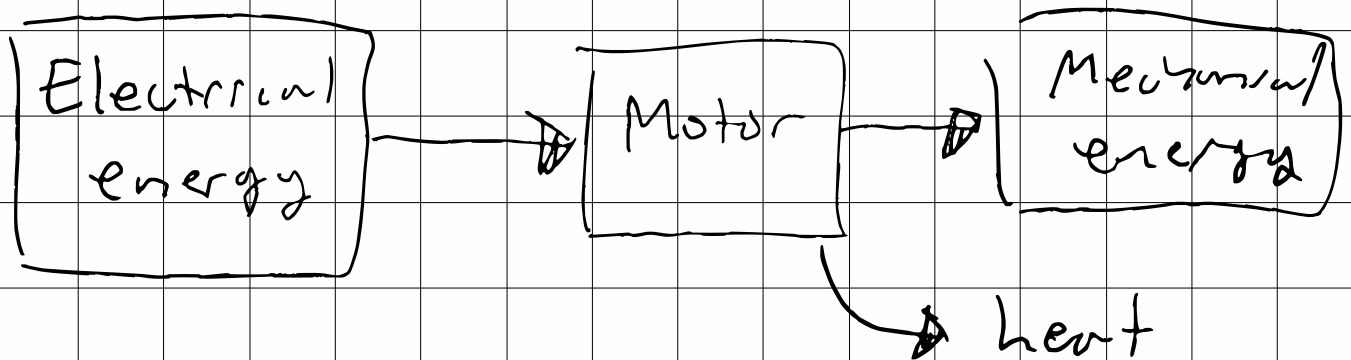


$$P_{in} = P_{out}$$

$$\eta \quad V \cdot I = \tau \cdot \omega$$


Components of DC Motor

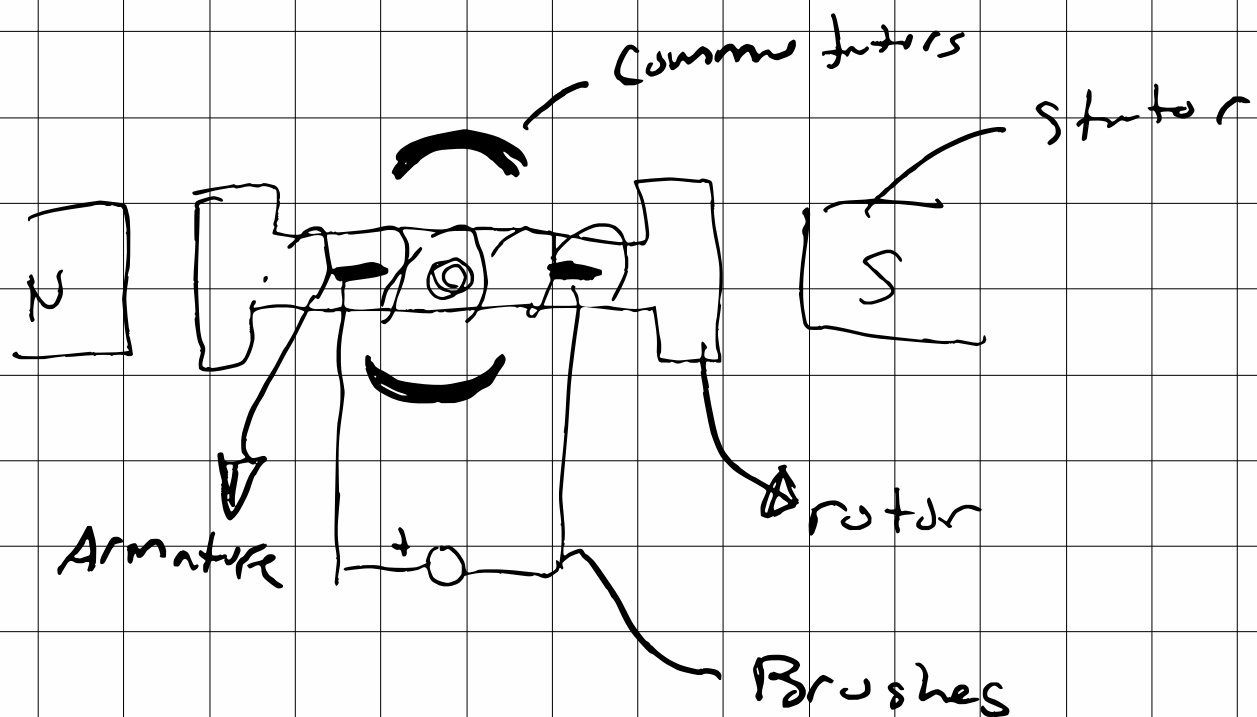

DC motor model

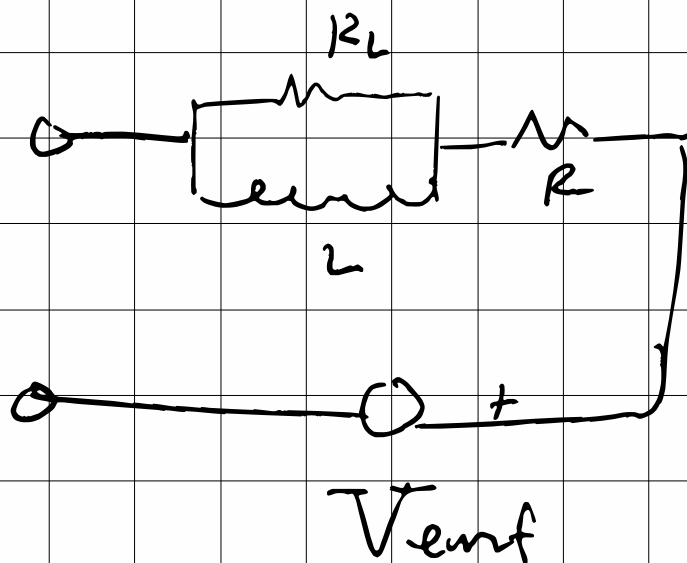

$$R_L \gg R$$

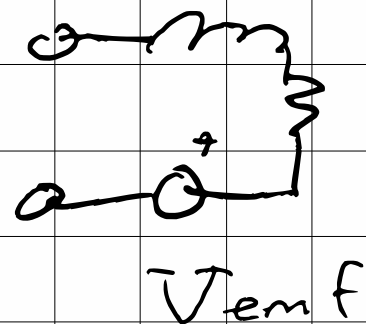

$$V_{in} = L \dot{I}_n + R I_n + \underline{k_e \omega}$$

Torque constant

$$T = k_T I_{in}$$


Mechanical Model: rotor + load inertia

$$T = (\underbrace{J_a + J_L}_{\text{rotor + load inertia}}) \frac{d\omega}{dt}$$

$$+ \underbrace{T_f + T_L}_{\text{"losses"}}$$

Steady state behavior

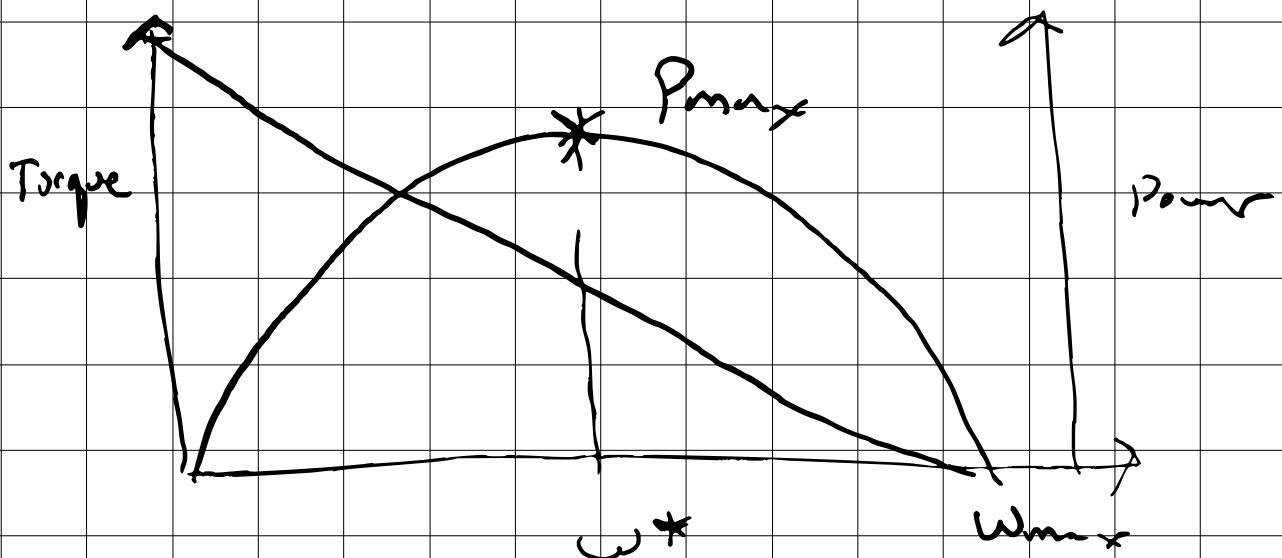
$$T = \left(\frac{k_T}{R} \right) V_{in} - \left(\frac{k_e k_T}{R} \right) \omega$$



$$W^* = \frac{1}{2} W_{max}$$

know why!!


Stepper Motors

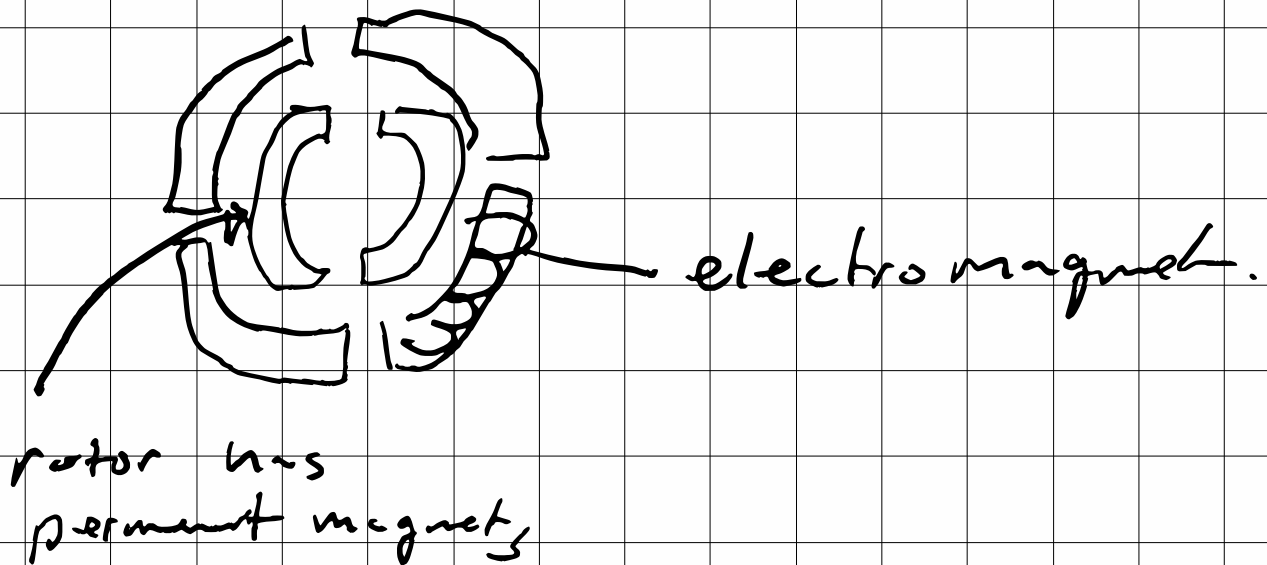

locked step mode vs slewing mode

Ch. 5 Analog Signal Processing

→ Why?

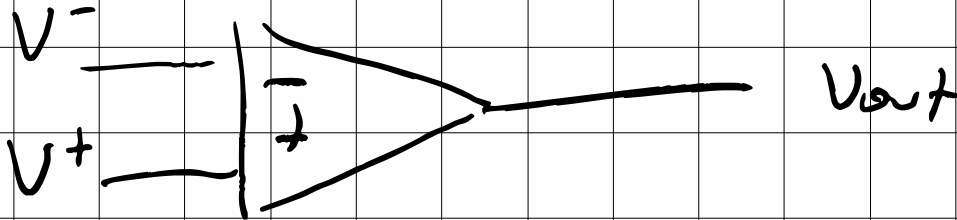

$$V_{out} = A_{OL} (V^+ - V^-)$$

Ideal op amp Assumptions

① Infinite input impedance

$$\rightarrow I^- = I^+ = 0$$

② Infinite gain

$$\rightarrow V^+ = V^-$$

$$\begin{aligned} V &= IR \\ R &= \frac{V}{I} \\ Z &= \frac{V}{I} \end{aligned}$$

③ output impedance is zero
 V_{out} is independent of I_{out}

[Know how to analyze
op amp circuits]

- Inverting Amp
- Non-inverting Amp
- Buffer
- Summer
- Integrator
- differentiator
- comparator
- Active filter
- Sample & hold

Sensors Ch. 9

- Position & Speed

conceptual {

- photoemitter - detector
- switches
- potentiometer
- LVDT
- encoders


- Stress & strain

* Wheatstone Bridge!

- Temperature Sensors

→ basic

- Vibration & Accelerations

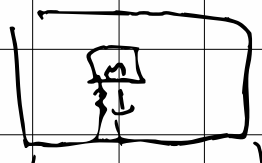

Ch. 8 Data Acquisition

- Shannon's sampling Theorem
- ADC successive approximation

op Amp

