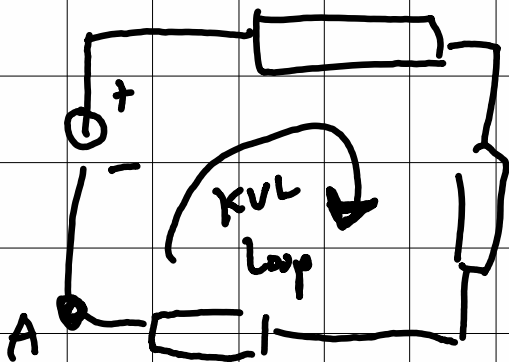


Last time:

- electrical elements
- I-V characteristics
- Kirchhoff's laws


$$\text{KVL: } \sum_i^N V_i = 0$$

sum of V around closed loop




$$\text{KCL: } \sum_i^N I_i = 0$$

sum of I flowing into
a node = 0

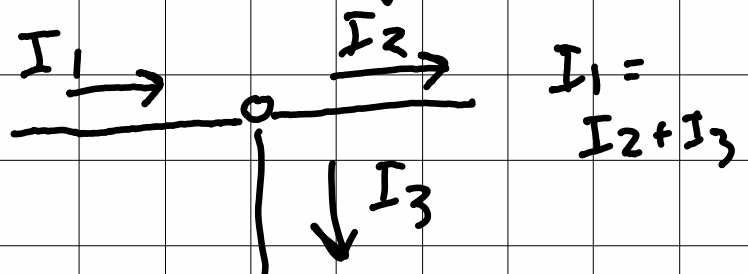


- Equivalent series resistance

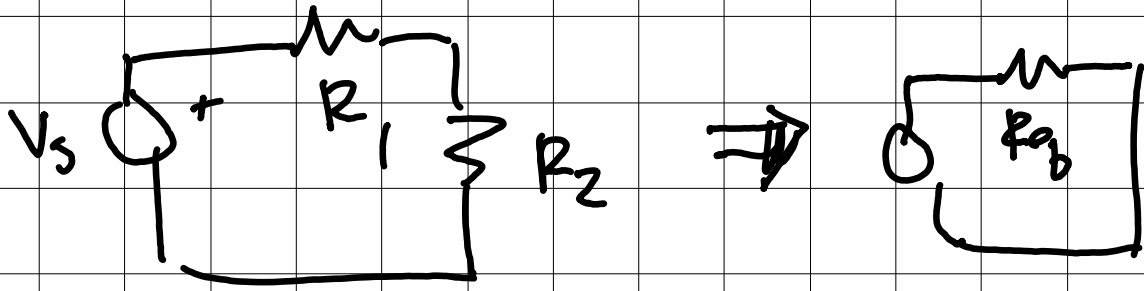

$$R_{eq} = R_1 + R_2$$

- Voltage divider sensor circuit

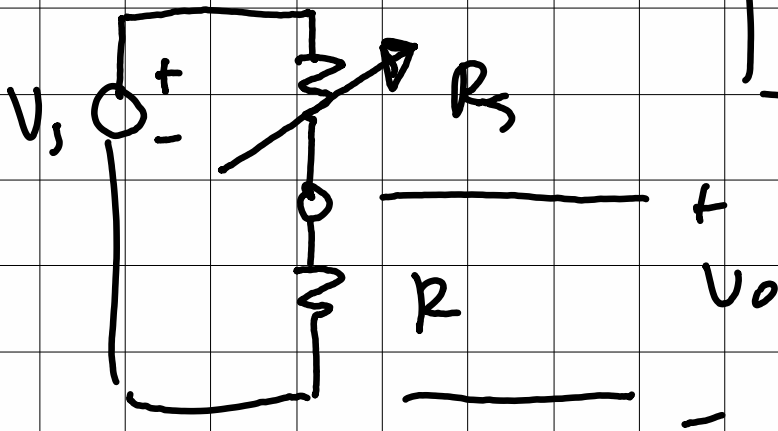

$$V_o = \frac{R}{R_s + R} V_s$$


Today:

- Equivalent series & parallel circuits
- Sources & meters
- Thevenin & Norton Eq.
- Power
- Impedance

Thursday

- AC circuits
- Transformer

Series Capacitors

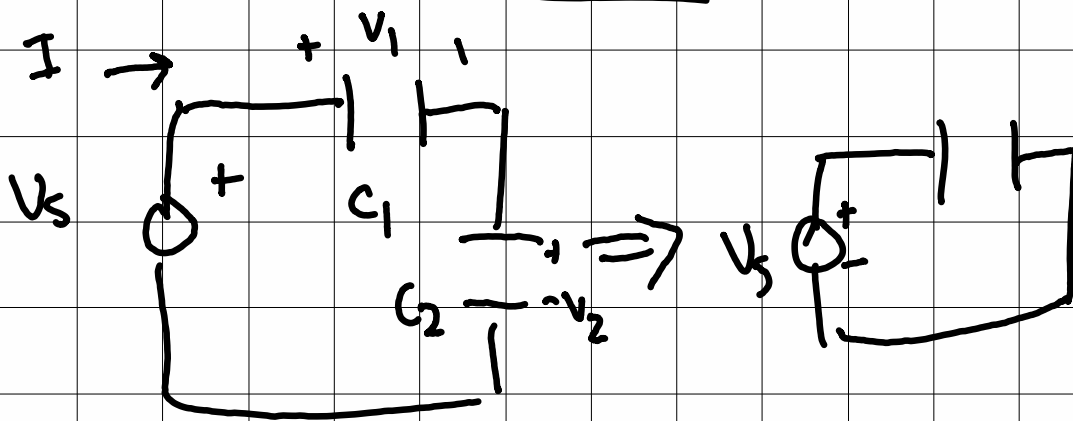

$$\text{KVL: } V_s = V_1 + V_2$$

$$\rightarrow \frac{d}{dt} V_s = \frac{d}{dt} V_1 + \frac{d}{dt} V_2$$

$$\dot{V}_s = \dot{V}_1 + \dot{V}_2$$

$$I = C \dot{V} \quad \dot{V}_s = \underline{I} + \underline{I} = \left(\frac{C_1 + C_2}{C_1 C_2} \right) I$$


$$\dot{V}_s = \left(\frac{C_1 + C_2}{C_1 C_2} \right) I$$

$$\Rightarrow I = C_{eq} \dot{V}_s$$

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$


$$C_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}}$$

Series Inductors

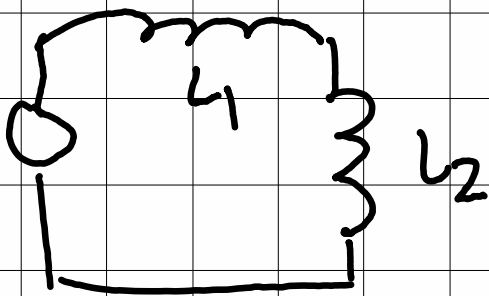


$$L_{eq} = L_1 + L_2$$

Parallel Resistance

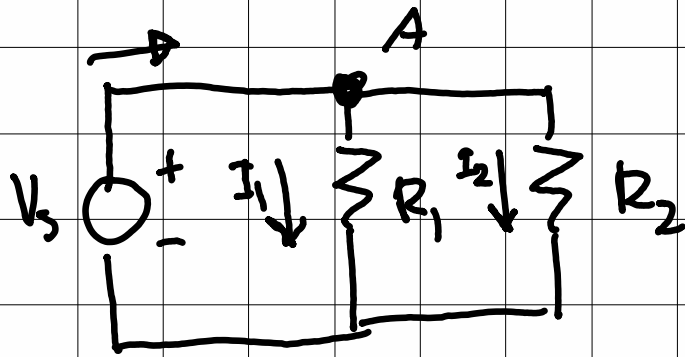

$\Rightarrow$

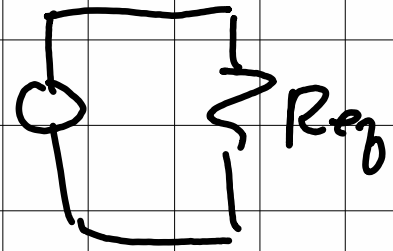

$$\text{KCL: } I = I_1 + I_2$$

$$V = IR$$

$$\text{KVL: } V_s = V_1 = V_2$$


$$I = \frac{V_1}{R_1} + \frac{V_2}{R_2} = \frac{V_s}{R_1} + \frac{V_s}{R_2}$$

$$I = \left(\frac{R_2 + R_1}{R_1 R_2} \right) V_s$$

$$V_s = \underbrace{\left(\frac{R_1 R_2}{R_1 + R_2} \right)}_{R_{eq}} I$$


$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$

Current Divider Circuit

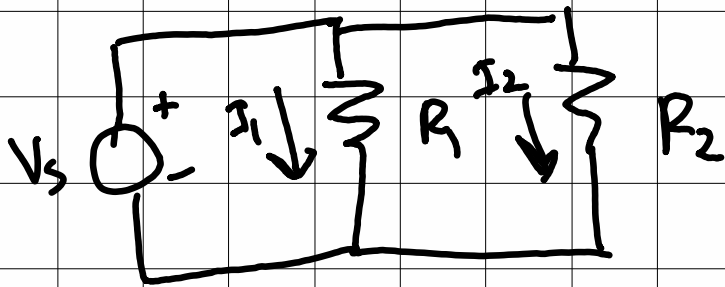


$$I_1 = \frac{R_2}{R_1 + R_2} I$$

Capacitor in Parallel

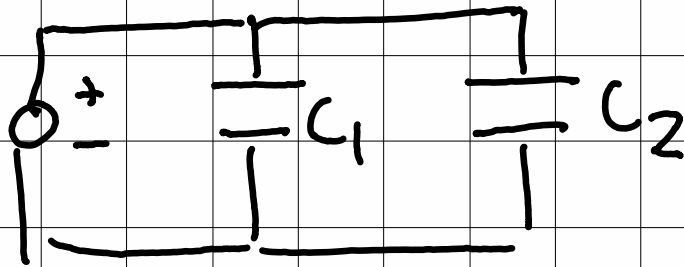


$$C_{eq} = C_1 + C_2$$

Inductor in Parallel

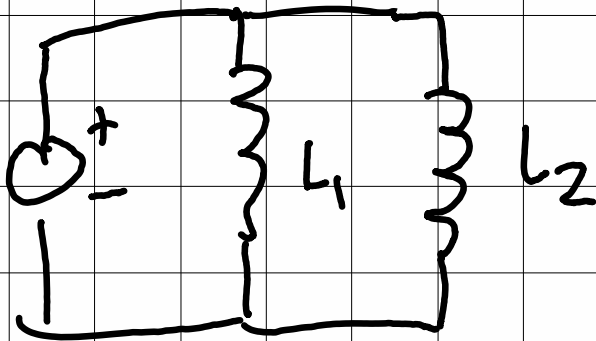

$$L_{eq} = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2}}$$
$$= \frac{L_1 L_2}{L_1 + L_2}$$

Example 2.4

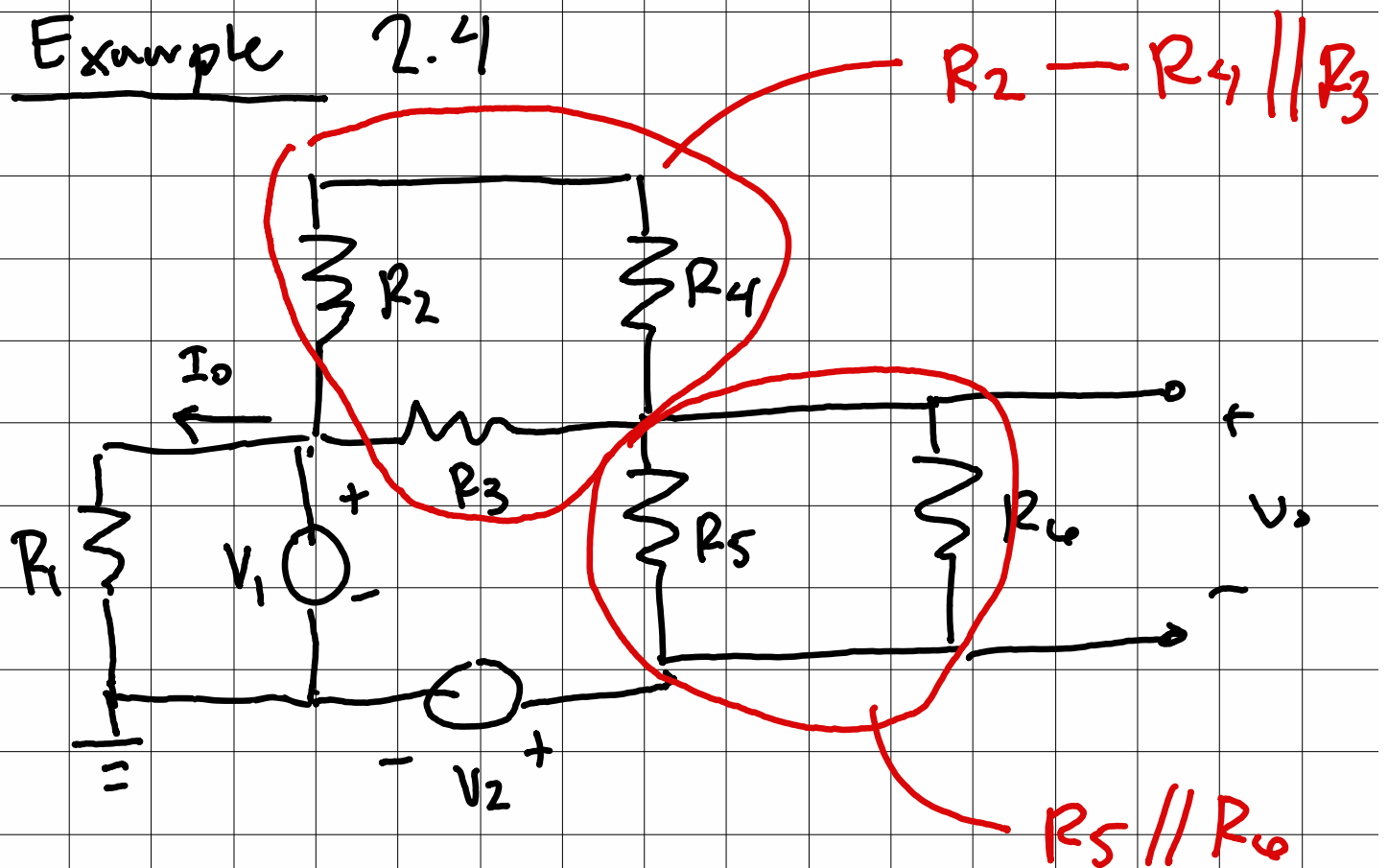


Find I_0 & V_0

$$0 \quad (R_2 - R_4) // R_3 : R_{234}$$

$$0 \quad (R_5 // R_6) : R_{56}$$
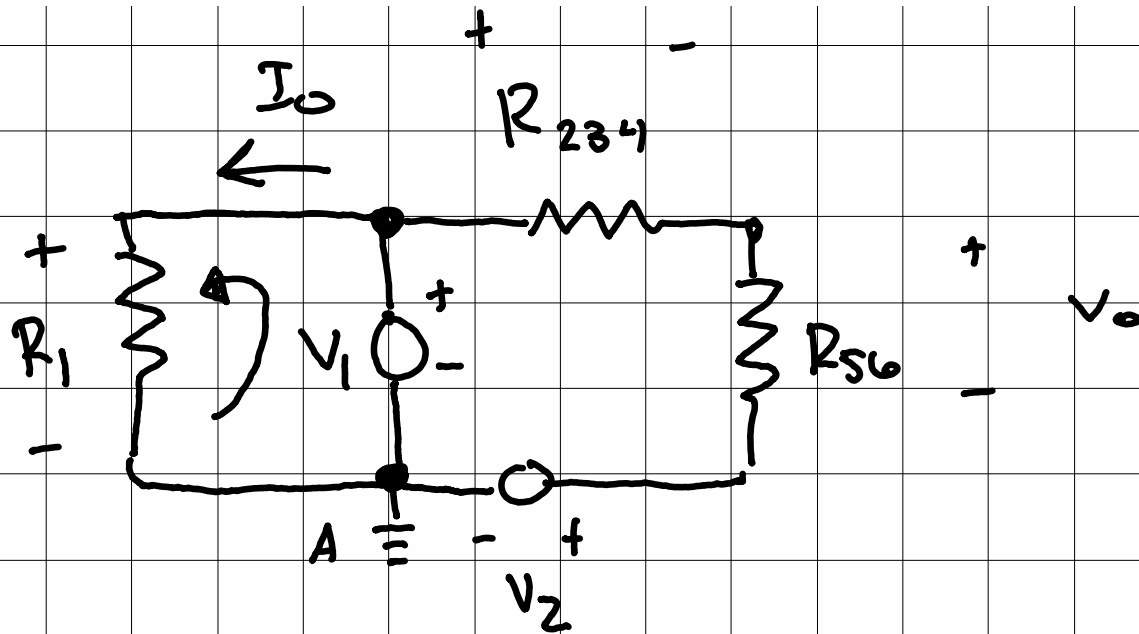
$$\Rightarrow R_{234} = \frac{(R_2 + R_4) \cdot R_3}{R_2 + R_4 + R_3}$$




Find I_0 & V_0

KVL (Left Loop): $-V_1 + V_{R_1} \Rightarrow V_1 = V_{R_1}$

$$V_{R_1} = I_0 R_1 = V_1$$

$$I_0 = \frac{V_1}{R_1}$$

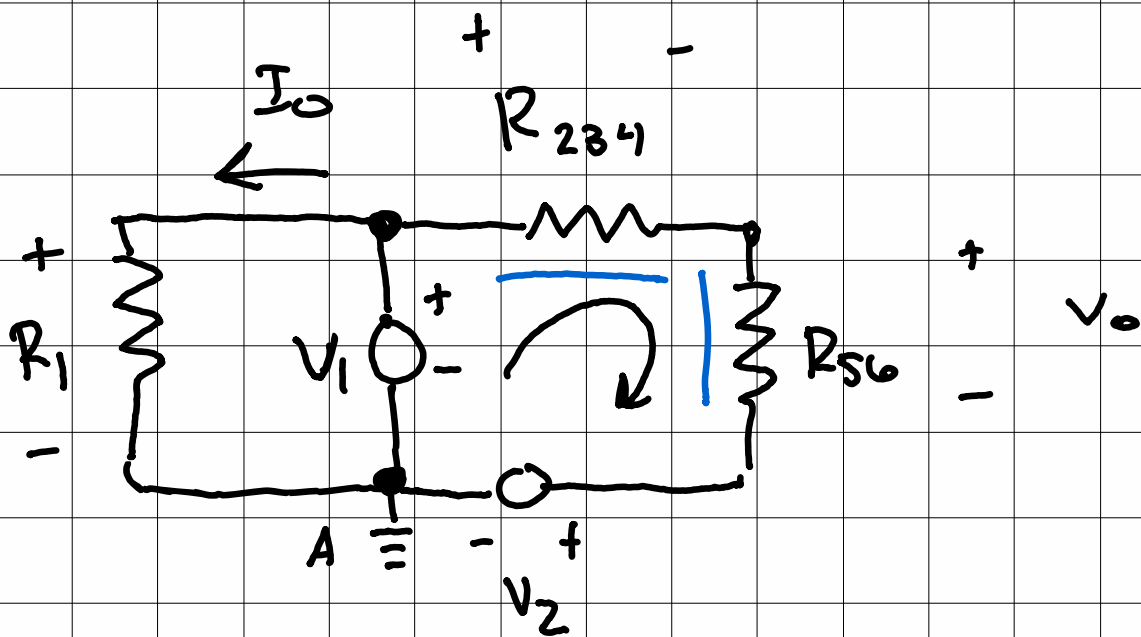

Find V_o :

$$\text{KVL (right loop)} : -V_1 + \overbrace{V_{234} + V_{56} + V_2}^{V_{23456}} = 0$$

$$V_{23456} = V_1 - V_2$$

Voltage divider:

$$V_{234} = \left(\frac{R_{234}}{R_{234} + R_{56}} \right) (V_1 - V_2)$$

V_o is equal to V_1 minus voltage drop from R_{234} :

$$\therefore V_o = V_1 - V_{234}$$


Sources & Meters

Voltage source

- ideal source
 - zero output impedance
 - ∞ current

generalize
resistance

- real source

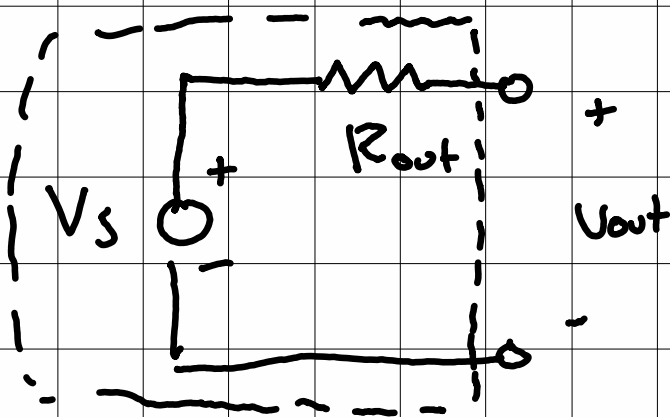

real voltage source

R_{out} : output impedance
 V_s : ideal voltage

$$V_{out} \neq V_s$$

$$R_{out} \ll 1$$


Current source

- Ideal current source
 - ∞ output impedance
 - ∞ voltage




$$R_{out} \ll \infty$$

TRUE FOR METER!

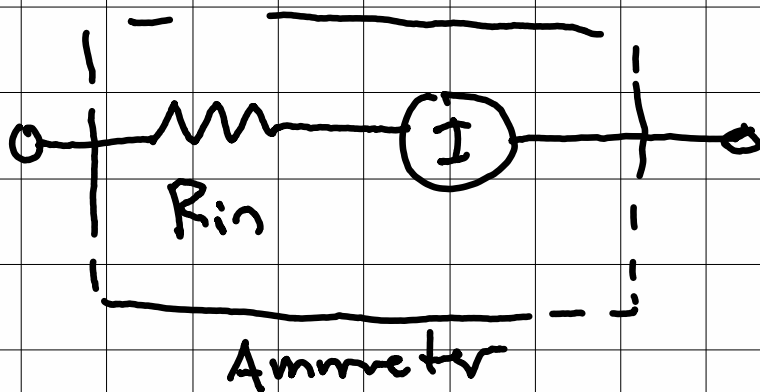

R_{in} : input impedance

Ammeter

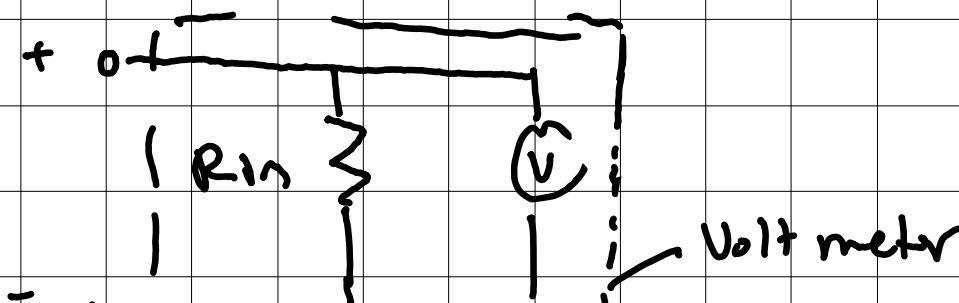


Volt meter

Why should we care about input/output impedance?

→ Loading effect:


the effect a measurement system (or source) impacts the rest of the circuit

Example 2.5

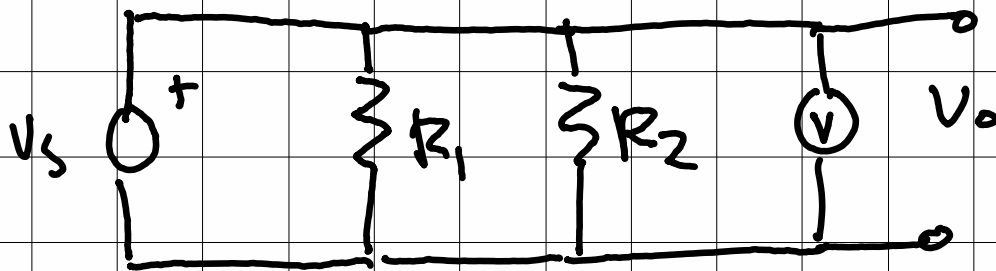


• ideal case



$$V_o = V_s$$

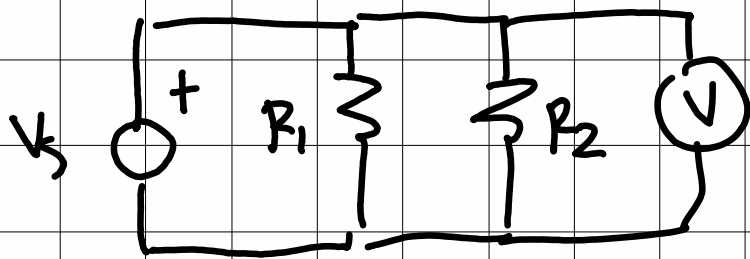


$$R_{eq} = R_1 // R_2$$

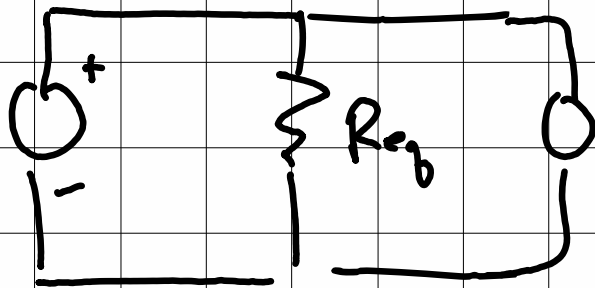

Non-ideal :

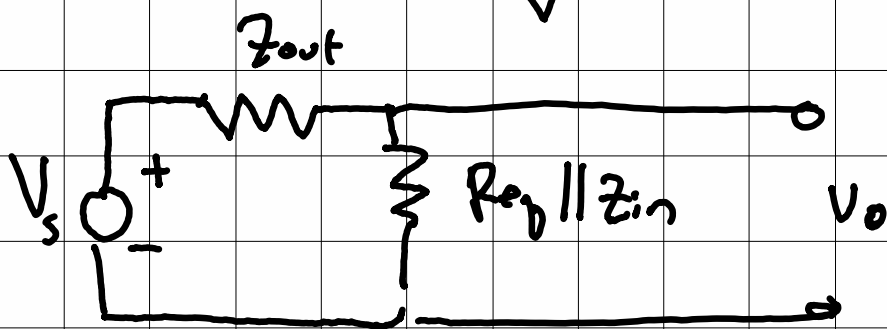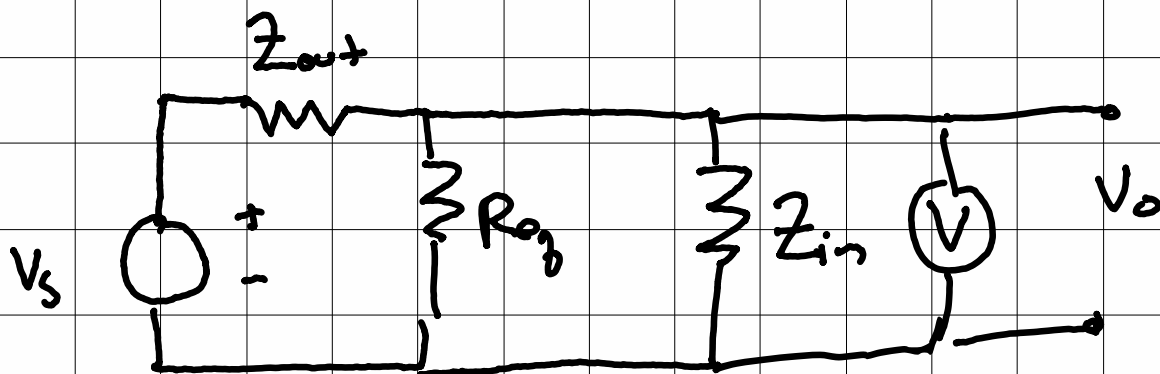

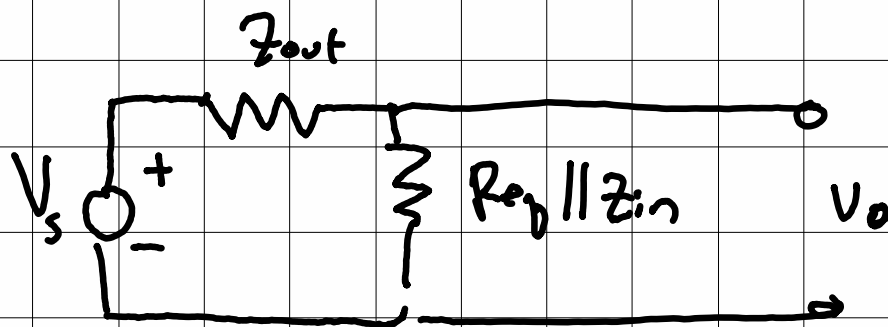

$$V_o = \left(\frac{R_{eq} \parallel Z_{in}}{Z_{out} + R_{eq} \parallel Z_{in}} \right) V_s$$



loading effect

Take away: designer/engineer must be cognizant of input/output impedance characteristics


Thevenin & Norton Equivalent Circuits

Thevenin Eq.

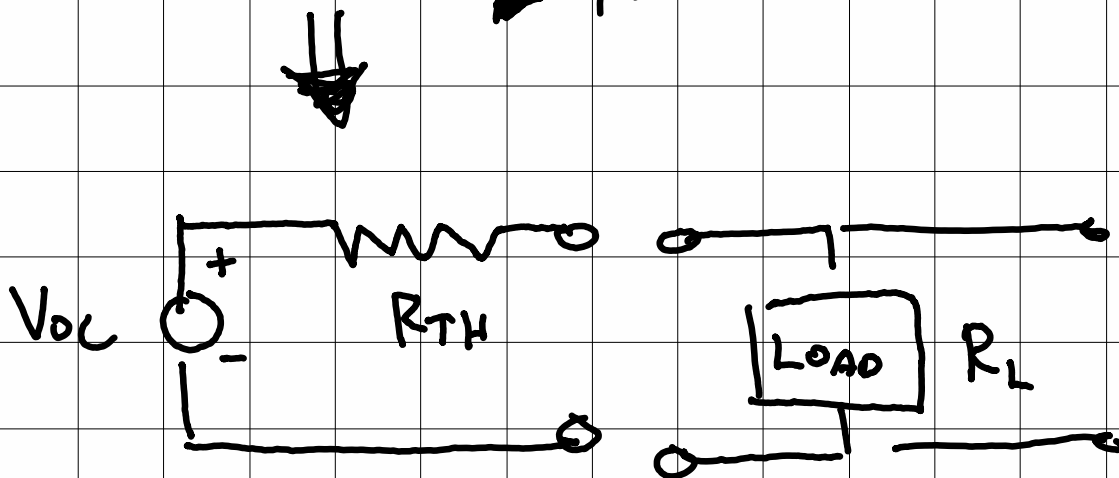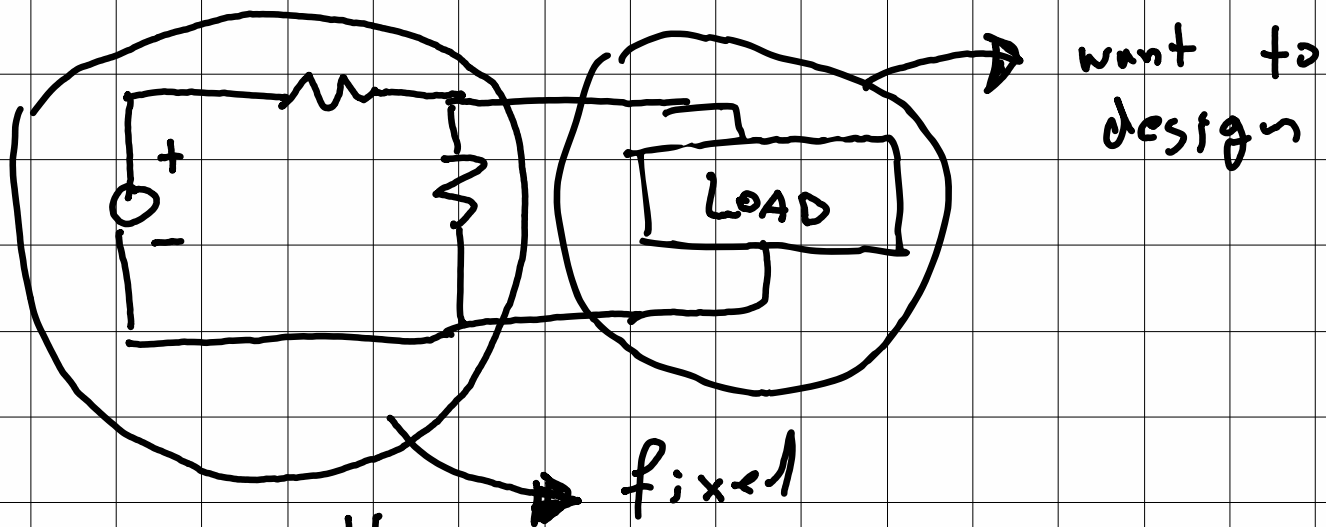- to simplify complex circuits by replacing voltage source & part of the network with an equivalent V source & series resistor



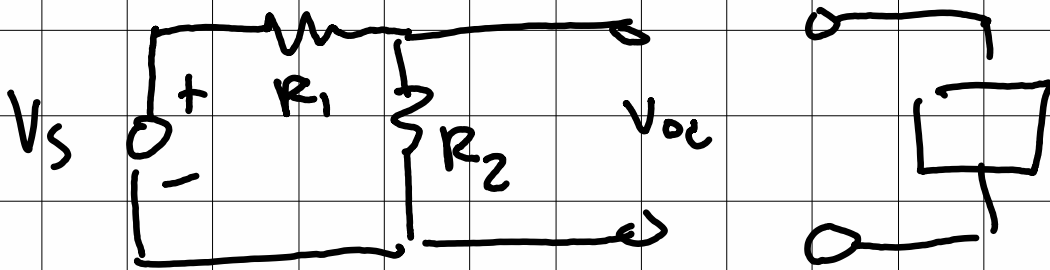- ① Find open circuit voltage V_{oc}
- disconnect "rest of circuit"
 - ↳ find voltage across open terminal



$$V_{oc} = \frac{R_2}{R_1 + R_2} V_S$$

- ② To find Thevenin eq. resistance
- short V_S ($V_S = 0$)

$$\Rightarrow R_{TH} = R_1 // R_2 = \frac{R_1 R_2}{R_1 + R_2}$$


The diagram shows two resistors, R_1 and R_2 , connected in parallel. An arrow points from this diagram to the equation for R_{TH} .

- ③ Analyze:



Norton Equivalent

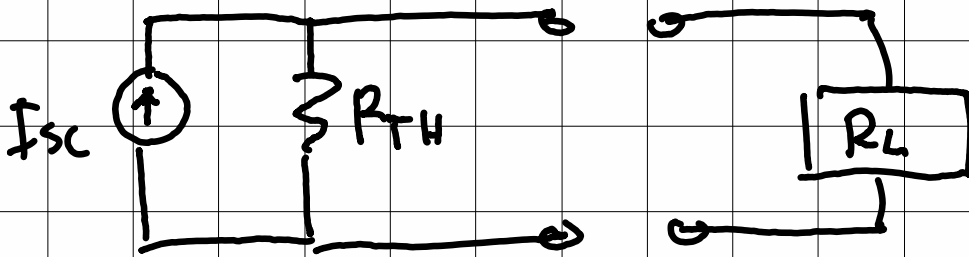- Network is replaced by ideal current source I_{sc} & Thevenin Resistance R_{TH} in parallel




① Find I_{sc}

- calculating the current when short the load terminals

② Find R_{TH} (same as previous)

③ Analyze circuit:

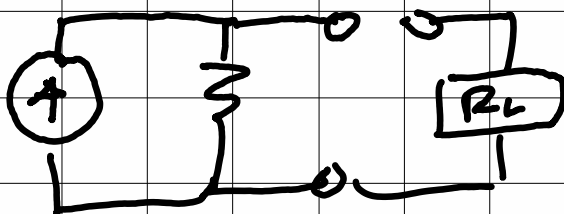

$$I_L = \left(\frac{R_{th}}{R_{TH} + R_L} \right) I_{sc}$$

- Why all the trouble?

- Thevenin / Norton equivalents are independent of the load

- we can make changes (e.g. design) without reanalyzing whole circuit

Power in Circuits

$$P = VI$$


- for any element power consumed or generated is the product of voltage across $\hat{v}$ current through that element

P negative: dissipation / storage

P positive: generation


For resistor : $P = VI = I^2R = \frac{V^2}{R}$

Impedance Matching

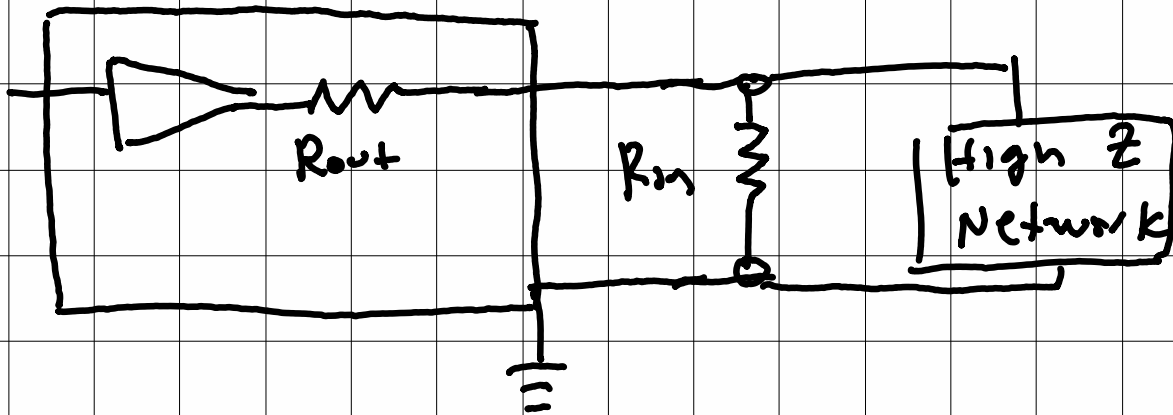

$R_{out} = R_{in}$ matching impedance

Why? String analogy

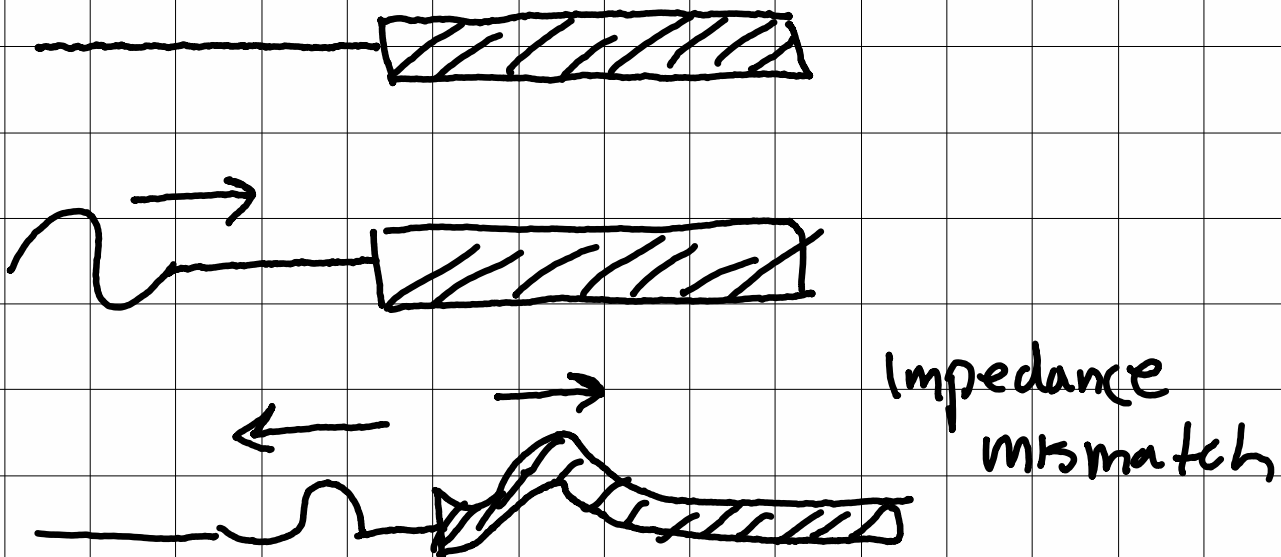

- impedance matching is important for transmitting maximum power



$R_L = R_s$ maximizes power

How? home work

Hint:

$$\frac{dP_L(R_L)}{dR_L} = 0$$

Next time:

- AC circuits
- transformers
- CH. 3