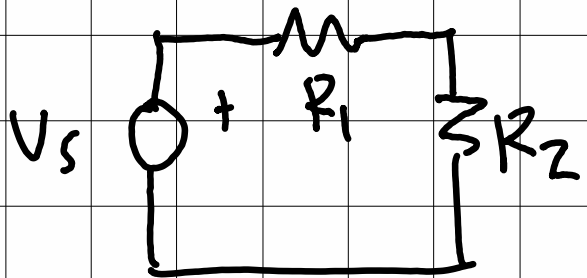


ME133 Lecture 4

1/13/2022


Last time:

• Series & Parallel circuits



$$V_2 = \frac{R_2}{R_1 + R_2} V_s$$


Voltage divider

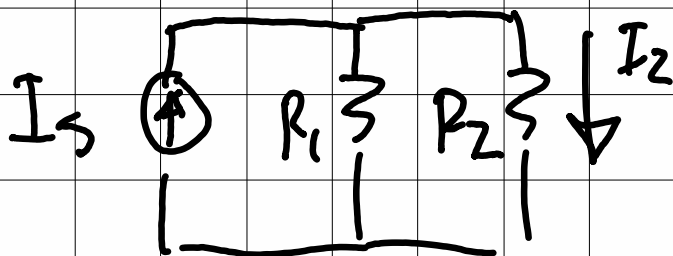

$$I_2 = \frac{R_1}{R_1 + R_2} I_s$$


Current divider

Thevenin Eq:

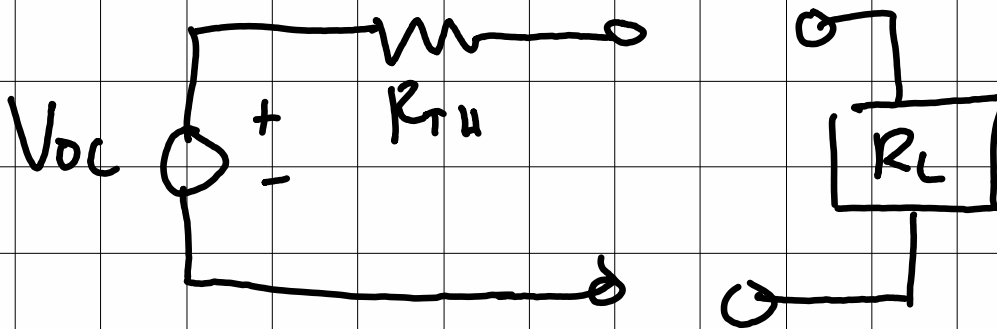

$$V_L = \frac{R_L}{R_{TH} + R_L} V_{oc}$$

Norton Eq.

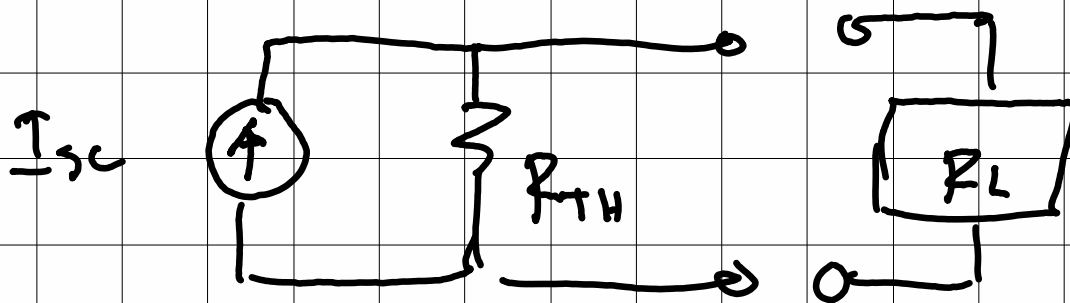

$$I_L = \frac{R_{TH}}{R_L + R_{TH}} I_{sc}$$

Today :

- AC Circuits
 - Transformer
- } CH-2

- Today
- Semiconductor Physics
 - Junction Diodes
 - Bipolar
 - Field effect
- } transistors



AC circuits

Why?


- most electrical signals are not pure DC ($V=C$)
→ even when your system is powered by DC.

Example:

≈ 0

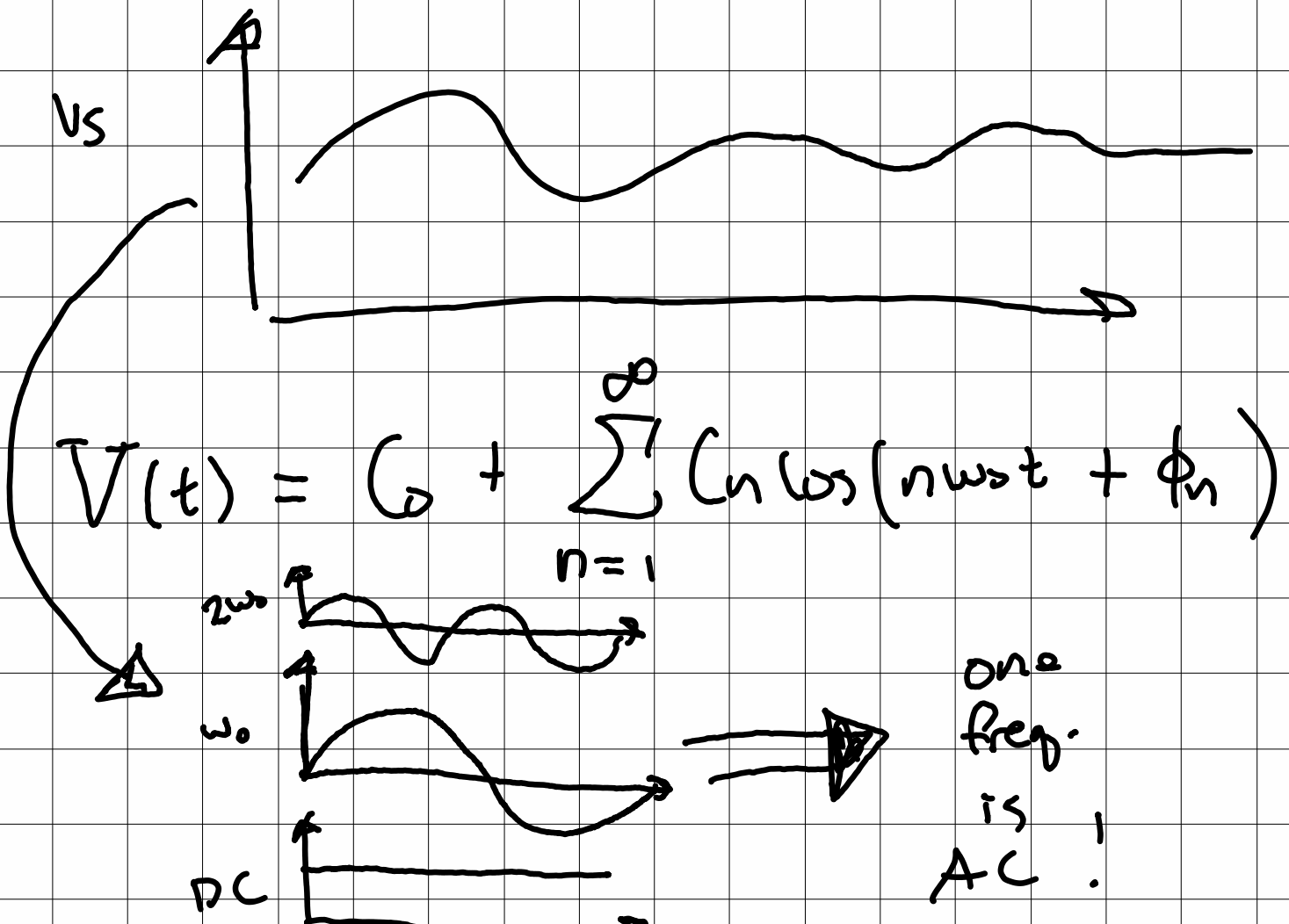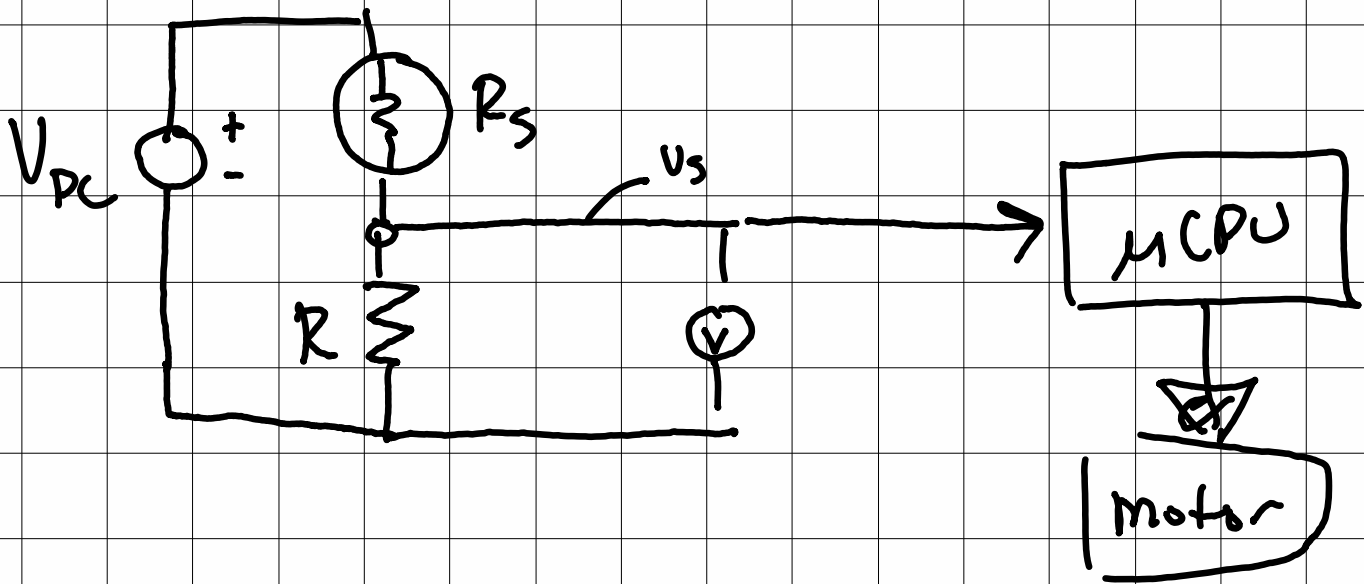
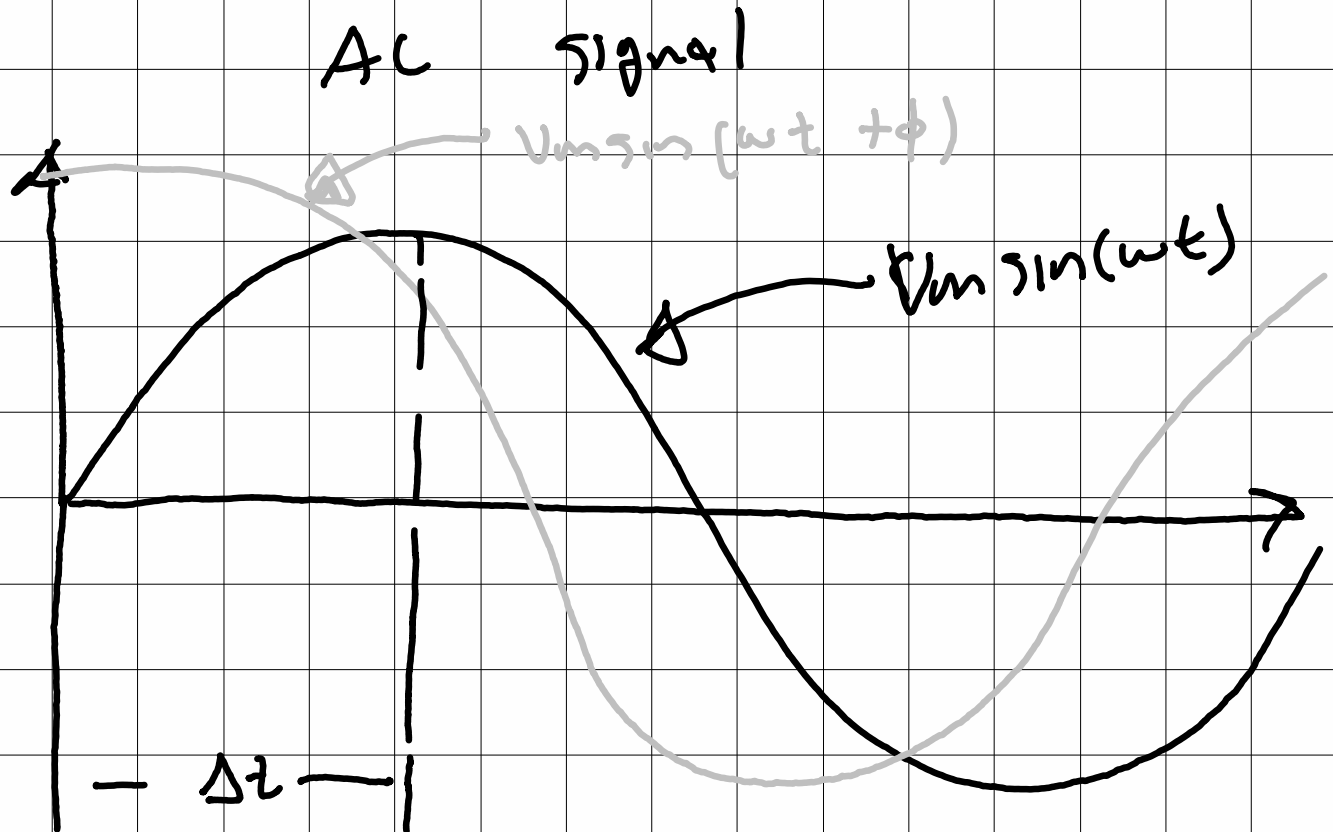
$$\underline{\hat{V}(t) = V_m \sin(\omega t + \phi)}$$



$$\phi = \omega \Delta t \quad (\text{rad})$$

- AC power is more efficient for transmission over long distances
- AC power is easy to generate with rotating machinery

- AC power is easy to use for driving rotating machines

Let's focus on steady state analysis: current & voltage of every element are AC signals with the same freq. as the excitation freq.

Euler's formula:

$$e^{j(\omega t + \phi)} = \cos(\omega t + \phi) + j \sin(\omega t + \phi)$$

$$j = \sqrt{-1}$$

→ phasor


phase vector represents
sinusoids

We can treat $\vec{V}$, I in AC circuits as phasors:

$$V = V_m e^{j(\omega t + \phi)} \quad (\text{exp. form})$$

$$= V_m \angle \phi \quad (\text{phasor form})$$
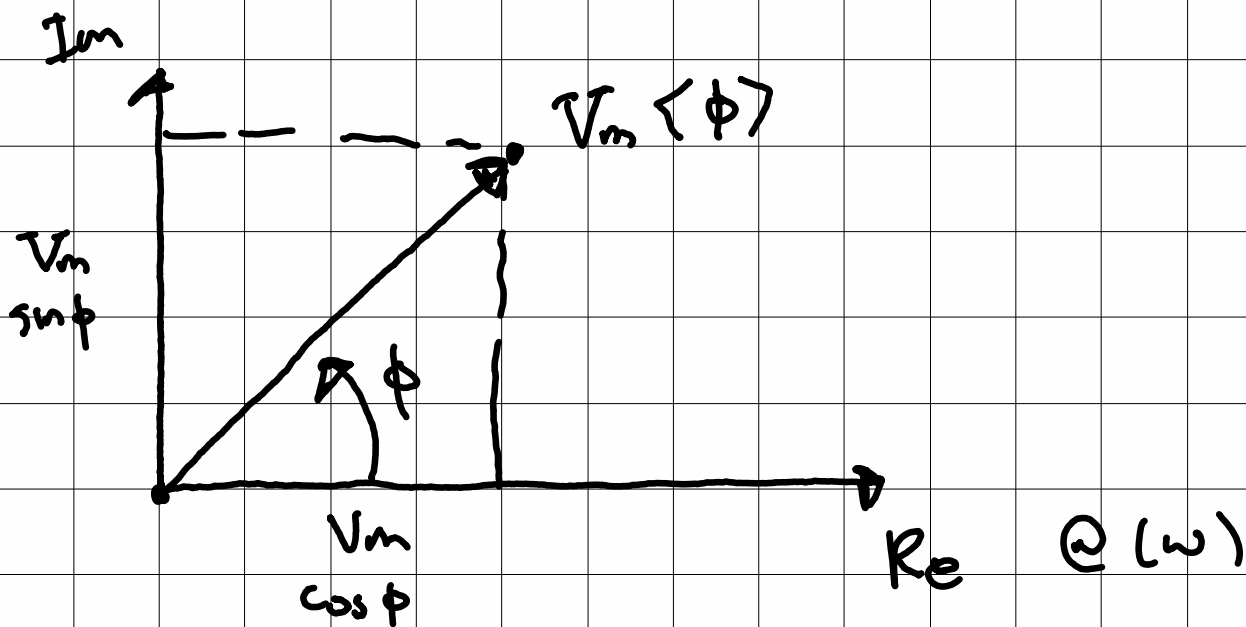
$$= V_m [\cos(\omega t + \phi) + j \sin(\omega t + \phi)]$$



Ohm's law can be generalized for AC:

$$V = R I$$

$$\rightarrow V = Z I$$

↑ impedance

in general impedance is a function of freq.

$$Z = f(\omega)$$

Resistor: $V = R I$

$$\uparrow Z \equiv R \quad (\text{no freq. dependence})$$

Inductor: $V = L \dot{I}$

$$\rightarrow I = I_m e^{j(\omega t + \phi)}$$

$$\dot{I} = j\omega I_m e^{j(\omega t + \phi)}$$

$$\therefore V = L \dot{I} = L j\omega I_m e^{j(\omega t + \phi)}$$

$$\begin{aligned}\therefore V &= L \dot{I} = L j \omega \underbrace{I_m e^{j(\omega t + \phi)}} \\ &= \underbrace{L j \omega}_{Z_L} I\end{aligned}$$

$$Z_L = j \omega L$$

$$e^{j\phi} = \cos(\phi) + j \sin(\phi)$$

$$\text{if } \phi = 90^\circ$$

$$e^{j(90^\circ)} = 0 + j$$

$$\therefore Z_L = \omega L \angle 90^\circ$$

$$\frac{V}{I} = Z_L$$







Voltage leads
current by 90°

$$Z_L = \omega L \angle 90^\circ$$

$$\omega \rightarrow 0 \text{ (DC)} \quad Z_L \rightarrow 0$$

inductor acts like a short circuit
at low frequency.
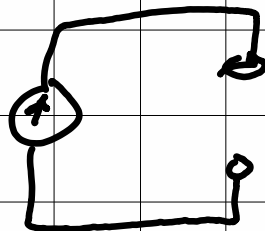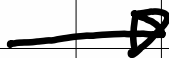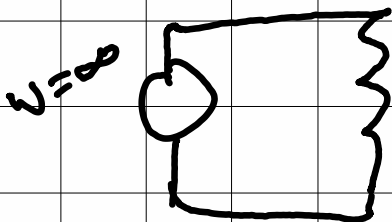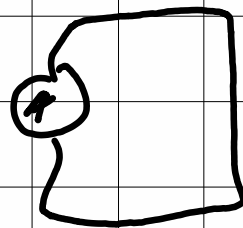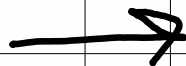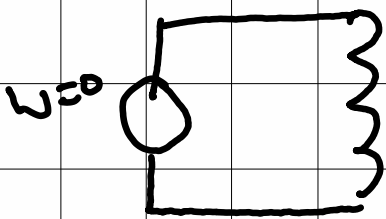
$$\omega \rightarrow \infty \quad Z_L \rightarrow \infty \text{ (open circuit)}$$



Capacitor:

$$I = C \dot{V} = C \frac{dV}{dt}$$

$$V = V_m e^{j(\omega t + \phi)}$$

$$\Rightarrow \dot{V} = j\omega V_m e^{j(\omega t + \phi)} \\ = j\omega V$$

$$I = j\omega C V$$


$$V = \frac{1}{C j\omega} I$$

$$Z_c$$

$$Z_c = \frac{1}{\omega C} \angle -90^\circ$$


$$V = Z_c I$$

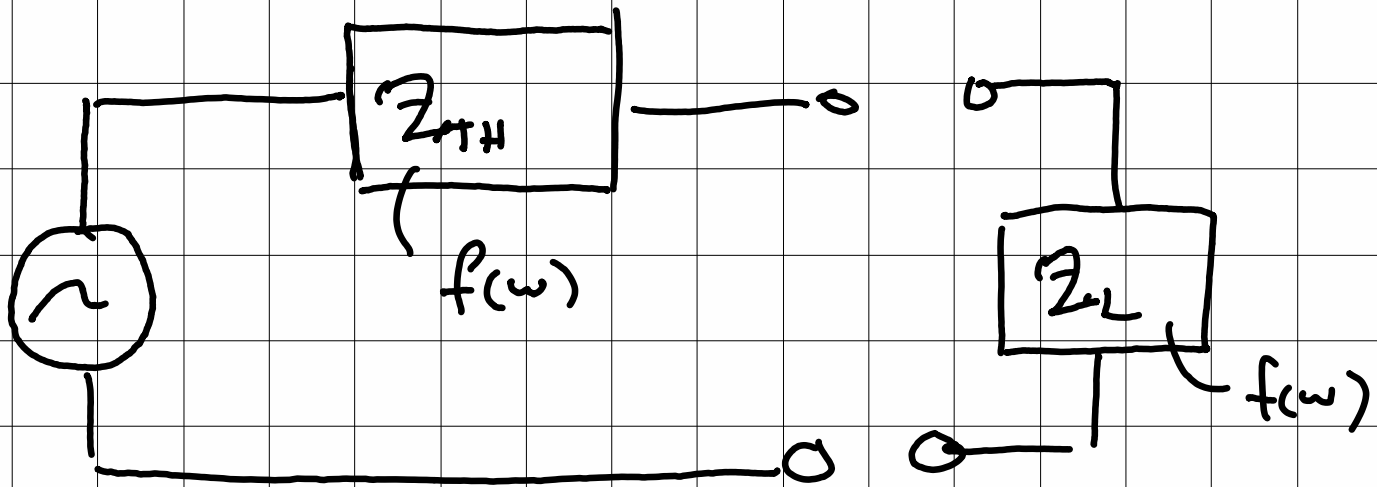Everything we discuss (Norton & Thevenin)
applies to AC circuits



Transformers

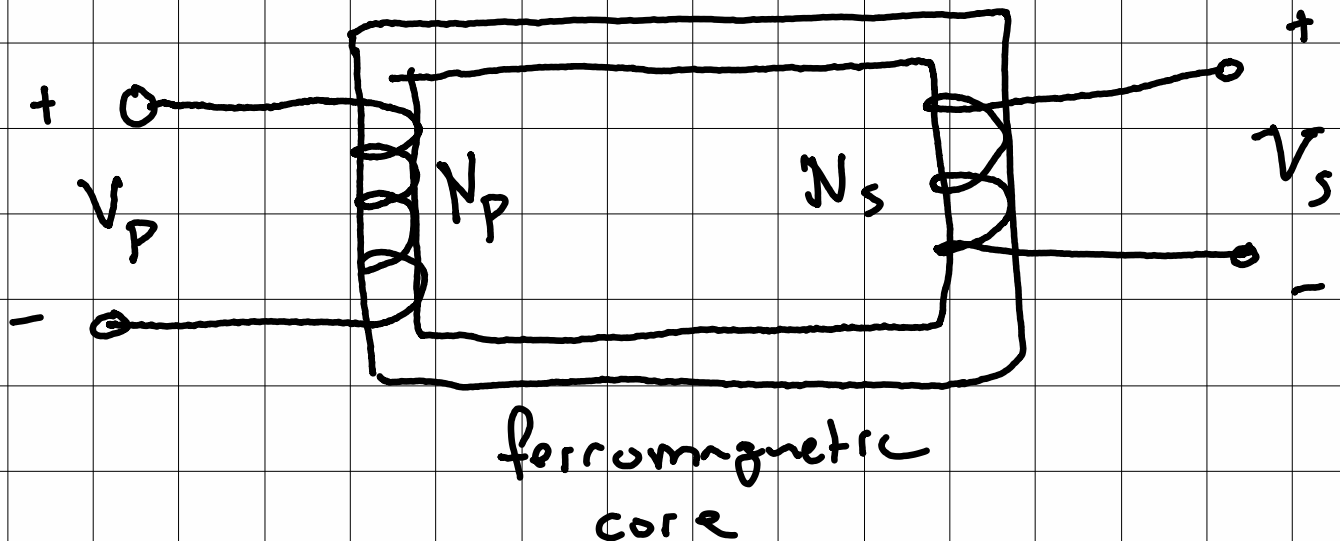- Changes the relative amplitude of voltage/current in AC circuit



$$\frac{V_p}{N_p} = \frac{V_s}{N_s} = - \frac{d\phi}{dt} \quad \leftarrow \text{flux}$$

$$\boxed{\therefore V_s = \frac{N_s}{N_p} V_p}$$

like gears in a mechanical system

$$N_s > N_p \rightarrow \frac{N_s}{N_p} > 1 \quad \text{Step-up trans.}$$

$$N_s < N_p \rightarrow \frac{N_s}{N_p} < 1 \quad \text{Step-down}$$

From conservation of energy:

$$\boxed{P_{in} = P_{out}} \rightarrow \underline{\text{ideal}} \quad \eta \quad P_{in} = P_{out}$$

$$V_p I_p = V_s I_s \rightarrow I_s = \frac{V_p}{V_s} I_p$$

$$\boxed{V \uparrow \quad I \downarrow}$$

$$\boxed{I_s = \frac{N_p}{N_s} I_p}$$

CH. 3 Semiconductors

- sensors
- signal processing
- display

Focus : diodes
transistor

Physics

- metals (e.g. conductors) have a large number of weakly bound electrons
- under an electric field
voltage
these electron flow! → current.
- other materials (e.g. insulators) have valence electrons which are tightly bound

- therefore under an electric field, no current flows
- semiconductors : have properties somewhere in between conductors & insulators
ex: silicon, germanium
- current-carrying characteristics depend on environmental factors : temp. or light.
- properties of semiconductors can be significantly changed by by doping :
inserts quantities of other elements into the lattice structure of the semiconductor

types of dopants :

- donor : enhances electron conductivity

n-type
(negative)

- acceptor : reduces electron conductivity


p-type
(positive)

The purpose of doping is to control the number of charge carriers


- n-type : charge carrier e^-
- p-type : charge carrier is hole (+)

The interaction of p- & n-type areas forms the basis of semiconductor electronics.


Junction Diode : pn-junction

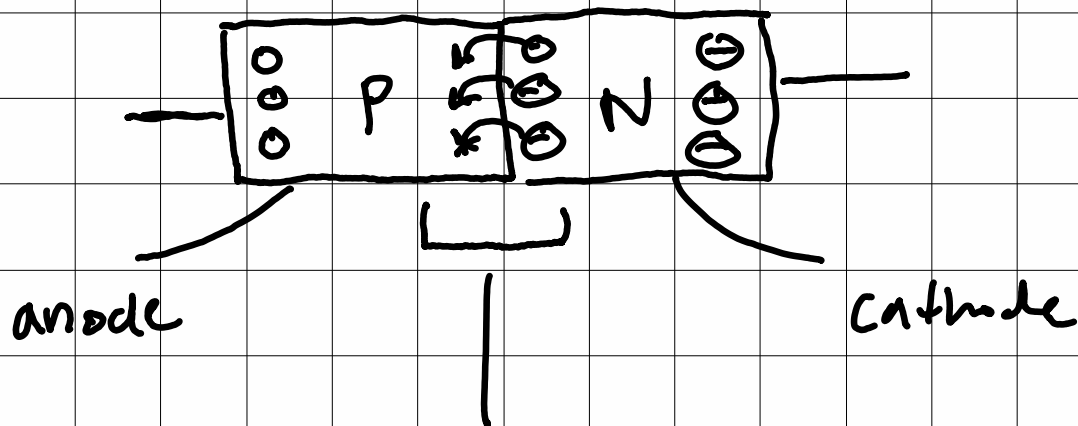

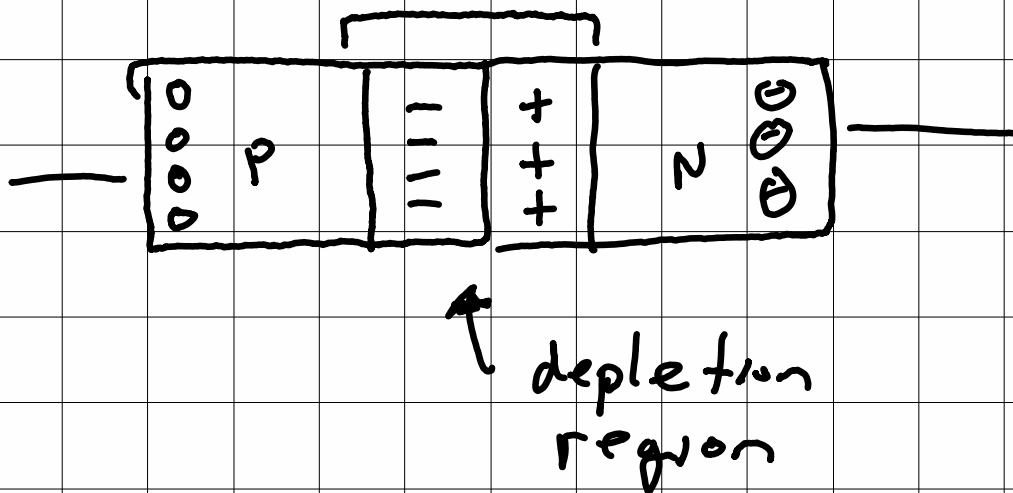electrons from cathode diffuse to occupy the holes in the anode



contact potential $\sim$ silicon 0.7 V

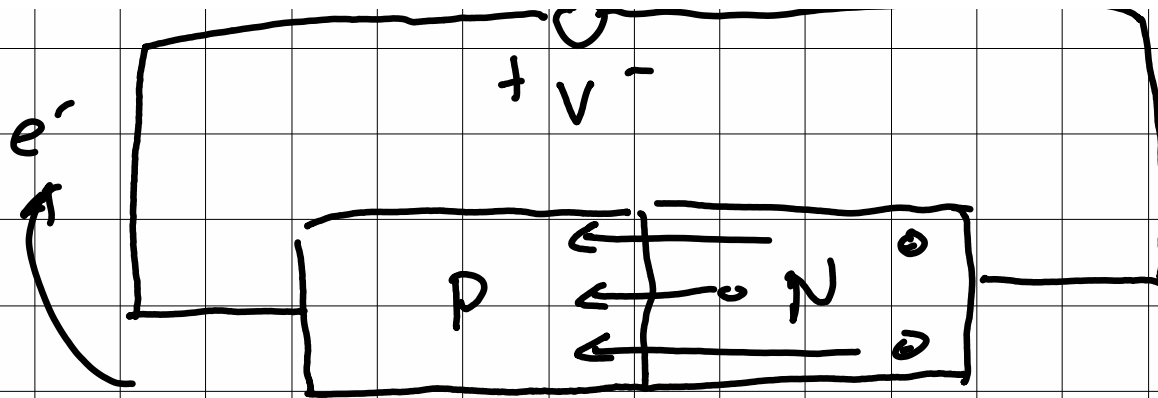

forward bias

- positive V on anode
- $V > 0.7$ (silicon) overcome the contact potential
- depletion region shrinks
- current flow through!

$$I_D = I_0 \left(e^{\frac{qV_0}{kT}} - 1 \right)$$
