

Last time:

- AC circuits

$$\begin{aligned} V &= \bar{V}_m e^{j(\omega t + \phi)} \\ &= V_m \angle \phi \\ &= V_m [\cos(\omega t + \phi) + j \sin(\omega t + \phi)] \end{aligned}$$

- Impedance

$$V = Z I$$

$$\text{generalized resistance} \quad Z = f(\omega)$$

- Transformers

$$V_s = \underbrace{\frac{N_s}{N_p}}_{\text{number of windings}} V_p$$

$$I_s = \frac{N_p}{N_s} I_p$$

- semiconductor introduction

Today :

- Finish Diode


- Zener

- photo

- light emitting

next time [• Transistor

Recall where we left off:

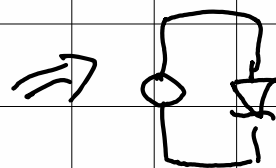

Forward Bias

$$I_D = I_0 \left(e^{\frac{qV_D}{kT}} - 1 \right) \quad (3.1)$$

I_D : current through the diode


I_0 : reverse saturation current

q : electron charge

T : Temp. in Kelvin

k : Boltzmann's constant

V_D : Voltage across diode

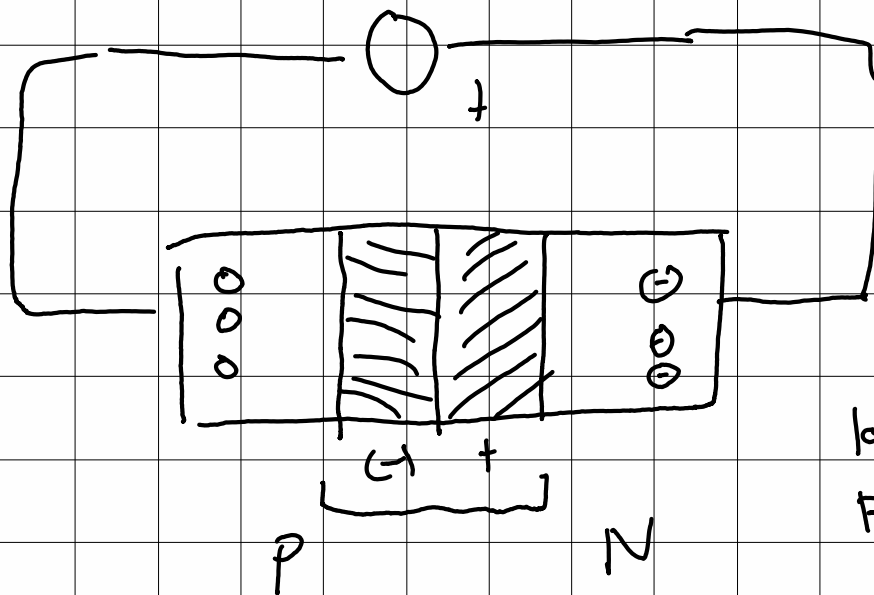

look at
Book Fig 3.2



reverse bias

- if positive voltage is applied to cathode the depletion region is enlarged





- no current flows

very tiny current $I_0 \sim 10^{-9} \text{ (A)}$

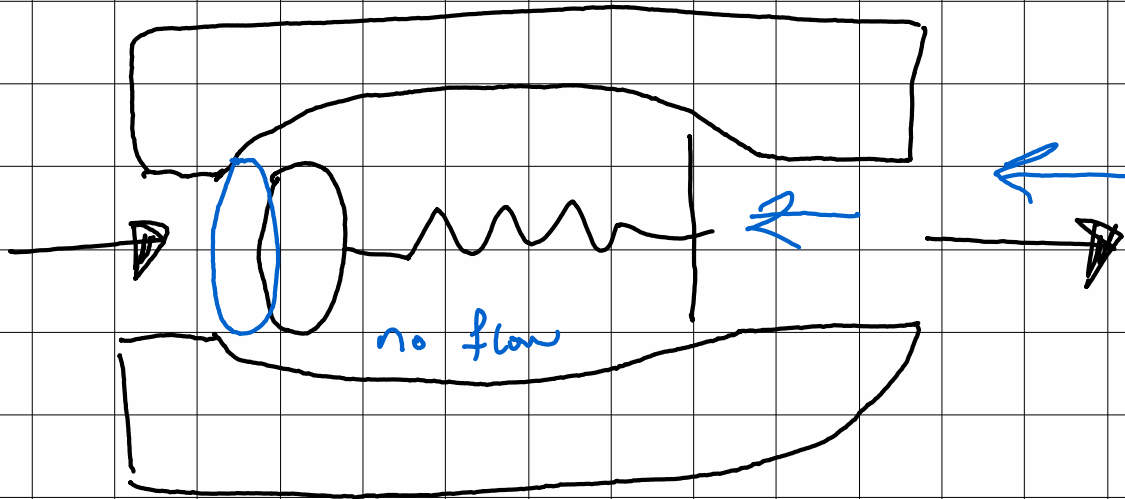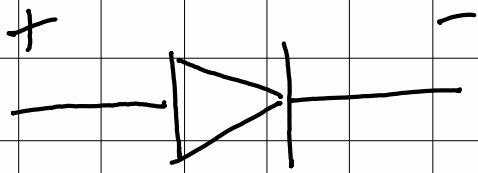Therefore, pn-junction only lets
(diode)
current flow in one direction



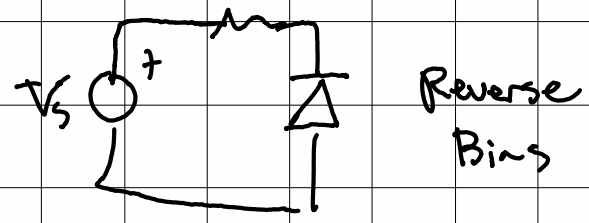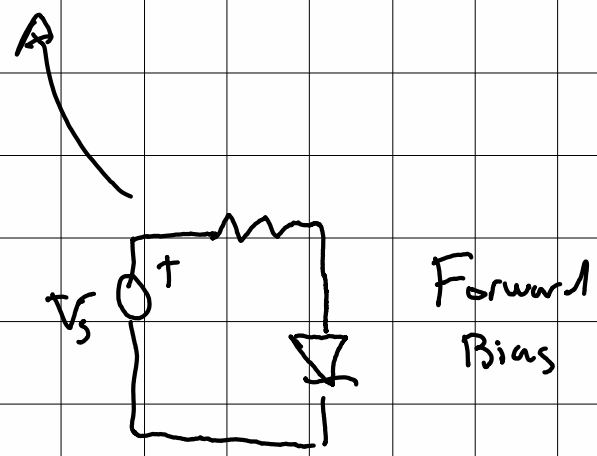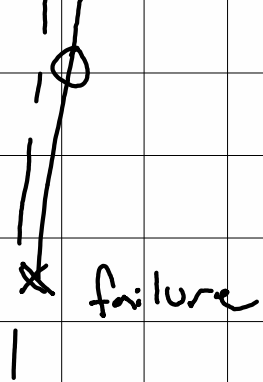
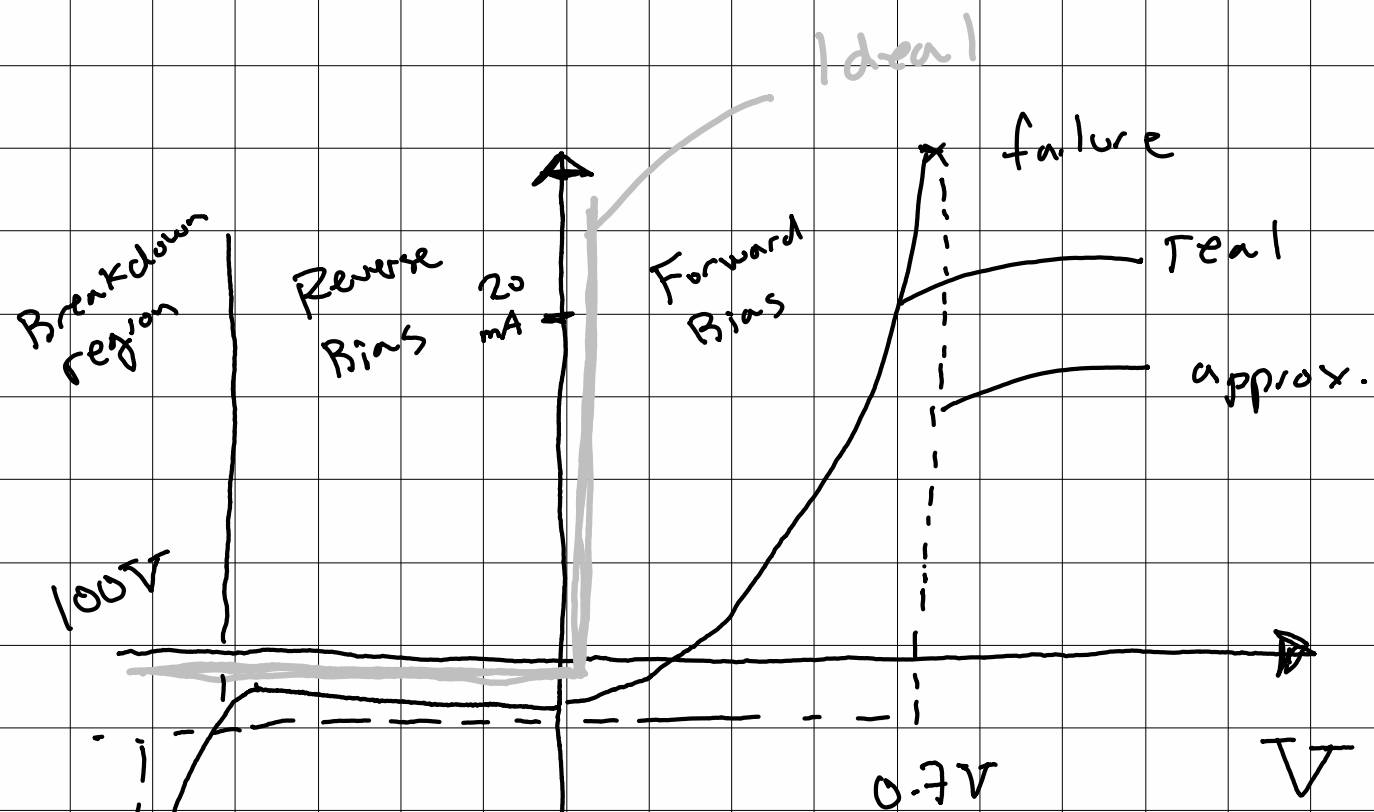
- on-off action of pn-junction is the basis for all digital devices




What are diodes useful for?

- circuit protection
- Half-wave rectifier:

only lets positive voltage through

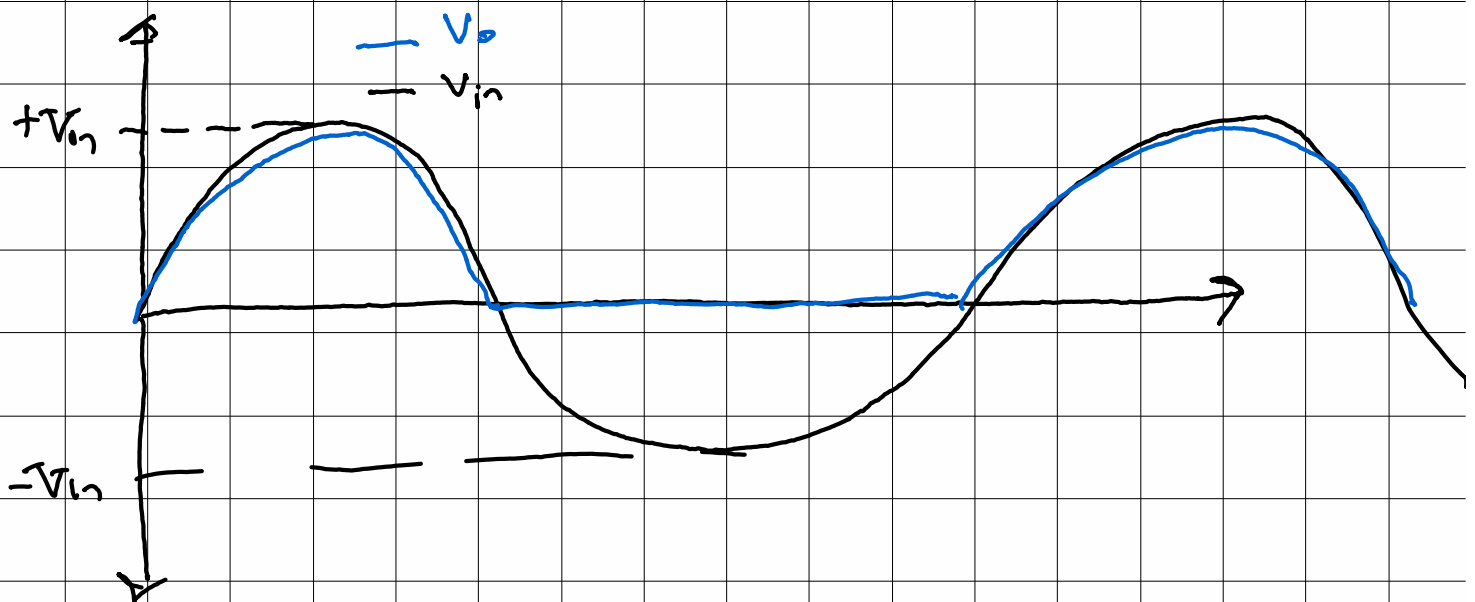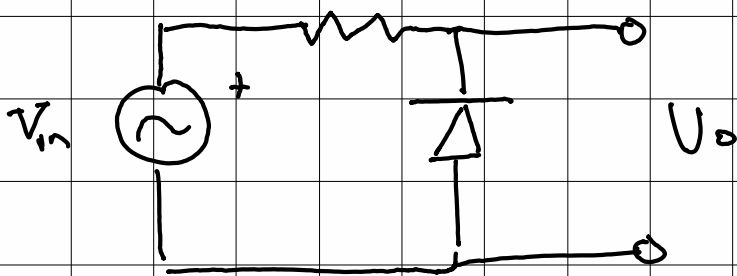

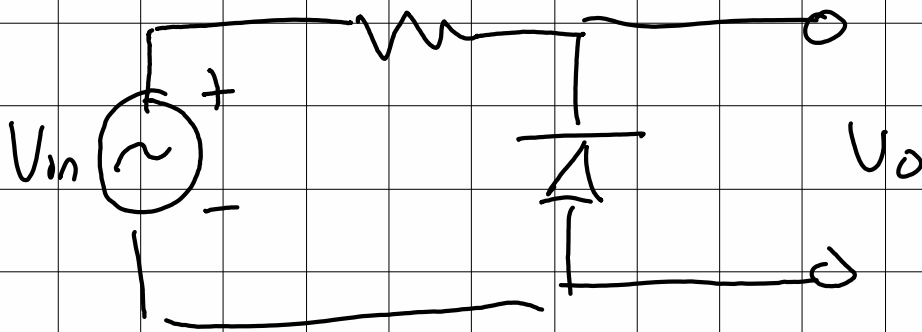


How to analyze?

• split into two circuits

(1) $V_{in} > 0$


(2) $V_{in} < 0$

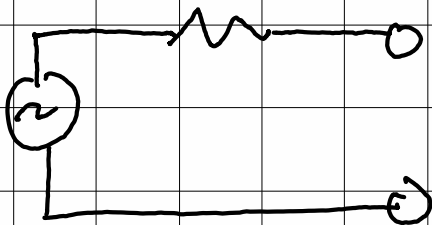(1) $V_{in} > 0$ diode $\rightarrow$ reverse bias
 $\rightarrow$ open circuit




$$V_o = V_{in}$$

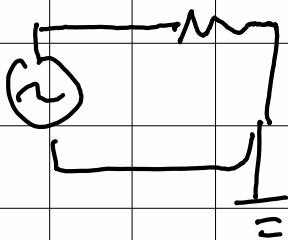(2) $V_{in} < 0$ diode $\rightarrow$ forward bias
 $\rightarrow$ short




$$V_o = 0$$



Peak Detector

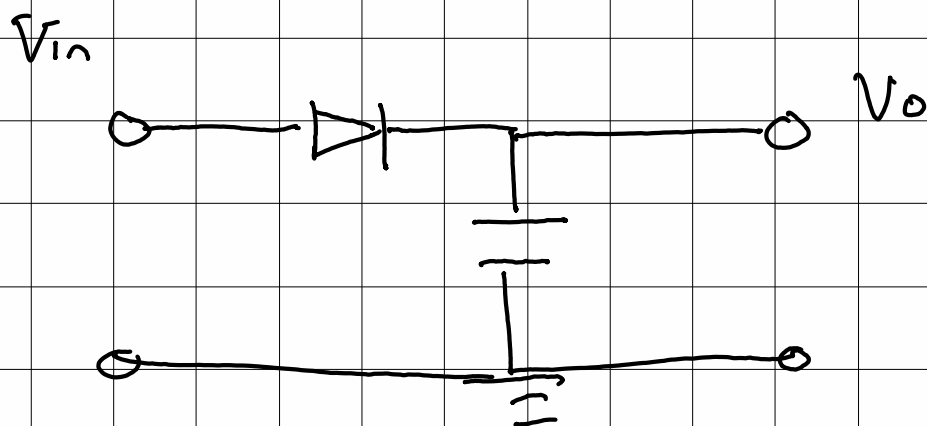

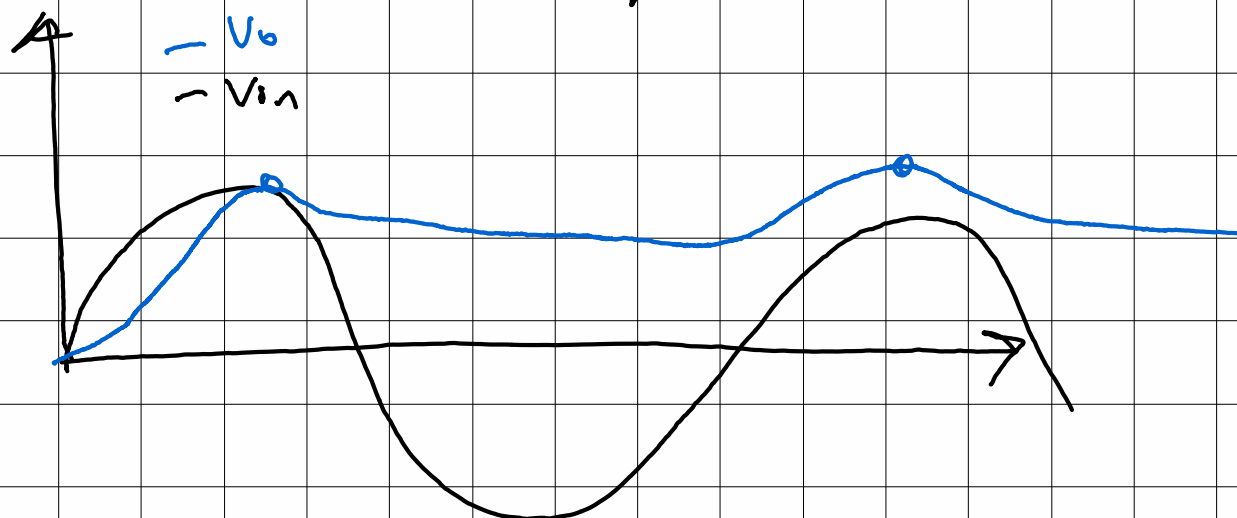- $V_{in} > 0$ forward bias
→ capacitor charges
- $V_{in} < 0$ reverse bias
→ capacitor retains voltage



Clipper

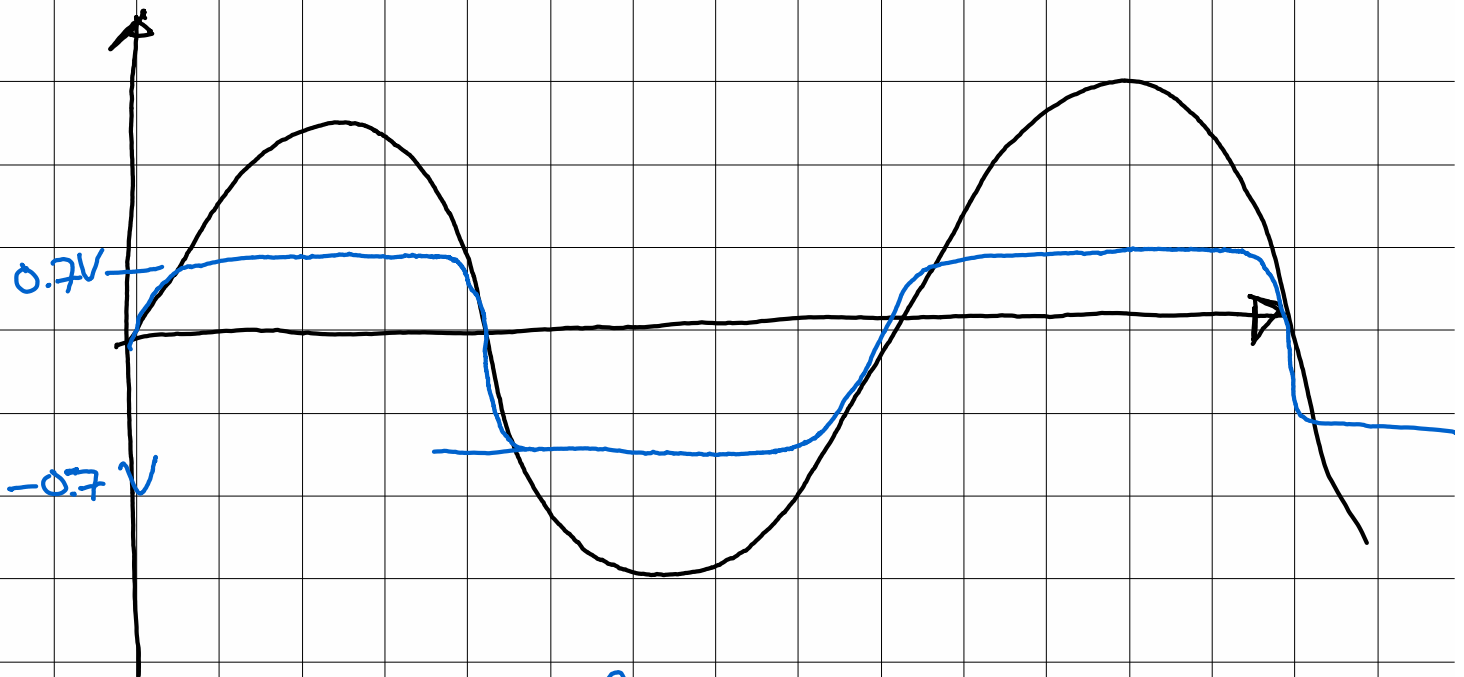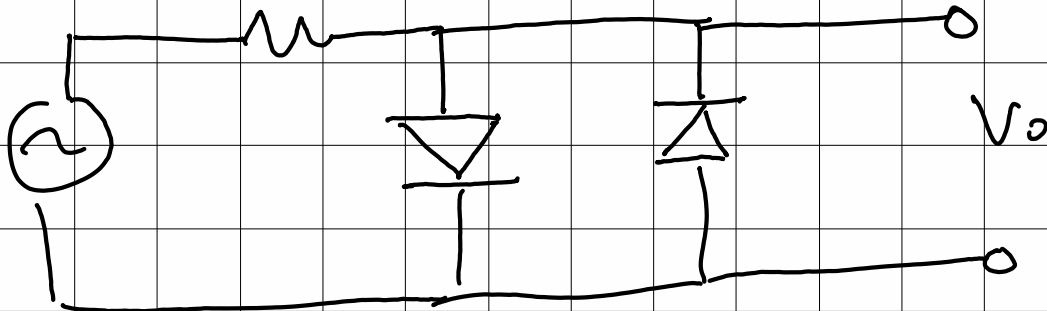


$0.7V \rightarrow$ forward bias voltage


Zener Diodes

- When is reverse-bias a diode can break down with large enough voltage $\sim 50V$

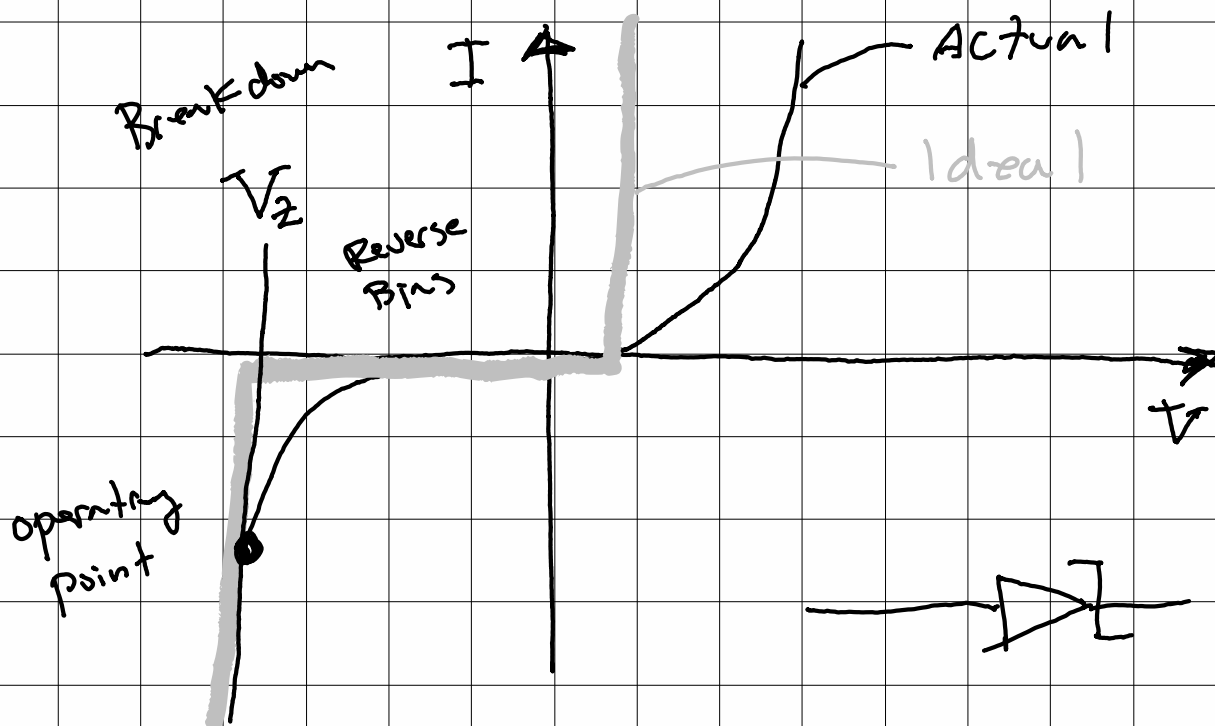- Zener diodes exploit the breakdown behavior (heavily doping)



* good for regulating voltage

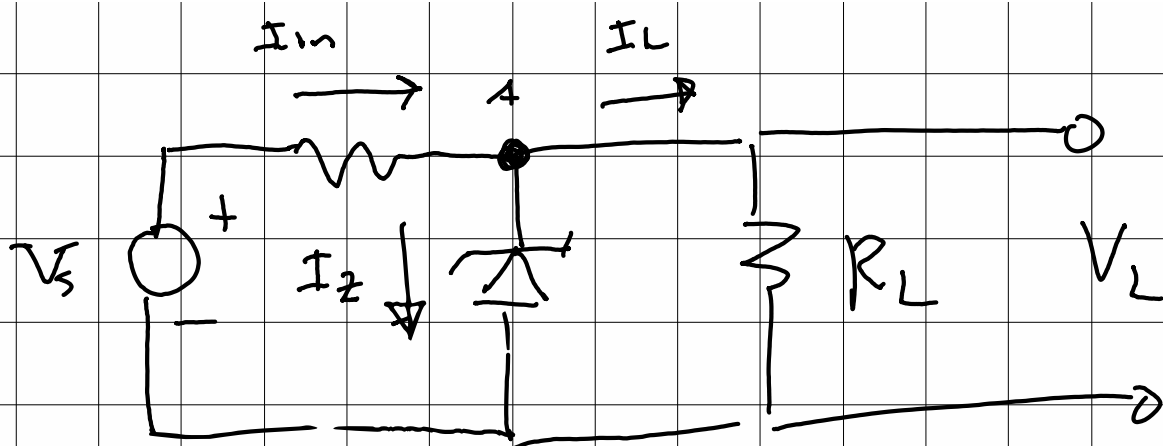

Note $-V_S < V_Z$

the diode is operating in Breakdown

- assume Zener diode is ideal
(current-voltage curve is vertical)

- $V_L = V_Z$

- $I_L = \frac{V_Z}{R_L}$

$$\begin{matrix} V_Z = C \\ R_L = C \end{matrix} \Rightarrow I_L = C$$

- $I_L = I_{in} - I_Z$

$\uparrow I_Z$ 'absorbs'
changes in V_S

- most of the time voltage regulators are constructed from specific IC (integrated circuits)


- Zener diodes are limited

- cannot set specific voltage

- Not good at source ripple

- load change

- LM78 ~~xx~~

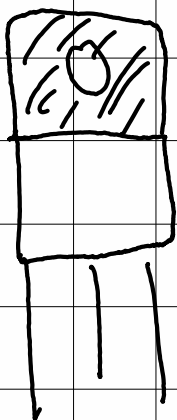



A

05 V

15 V

12 V



Double Clipping Zener

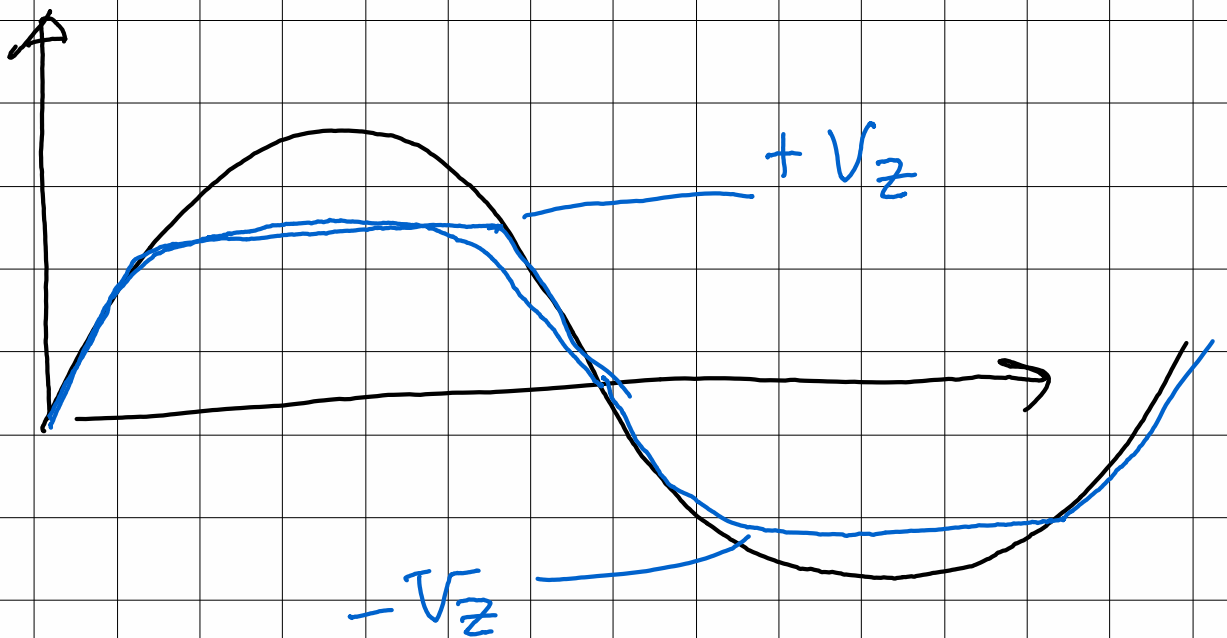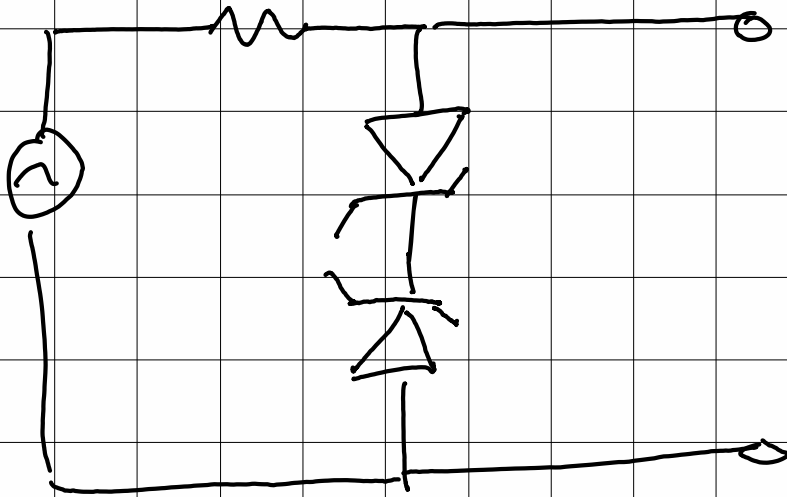

Optoelectric Diodes

LEDs (light emitting diode)

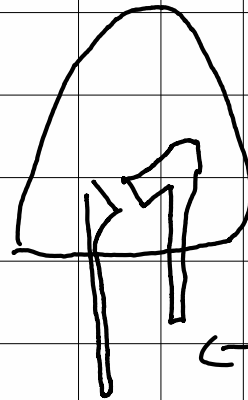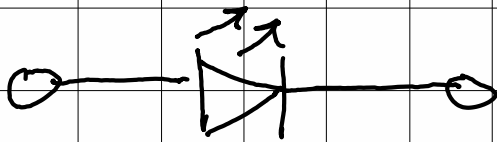
- all diodes emit some light when forward bias, but most times it is not visible
- LED, designed to emit photons when forward bias
- Intensity is related to amount of current flow.



anode

(+)

(-) Cathode

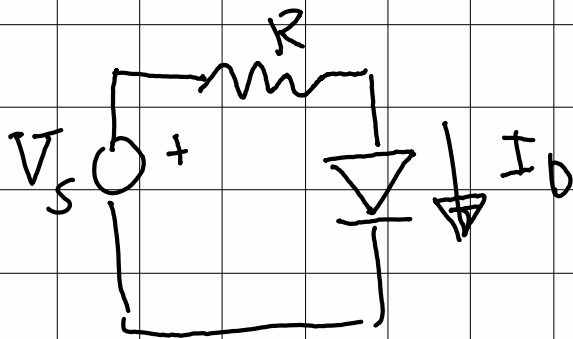

R: current limiting resistor


$$I_D = \frac{V_s}{R}$$

small R $\downarrow$ $\uparrow$ current

- photodiode


- recall that pn junctions (semiconductors in general) have properties that are sensitive to the environment (e.g. light)

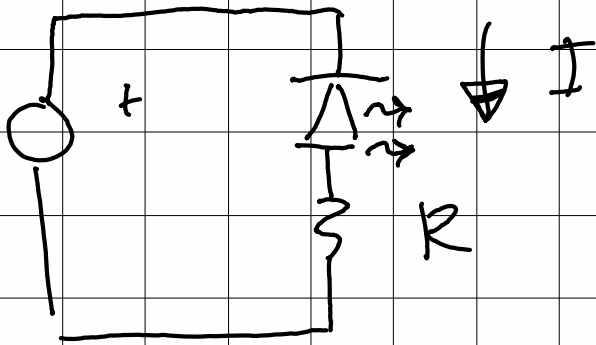- photodiode detect photons (quantum effect)



- photons excite carriers in reverse-bias junction
- very small current flows $\sim$ amount of light

Application : op to coupler

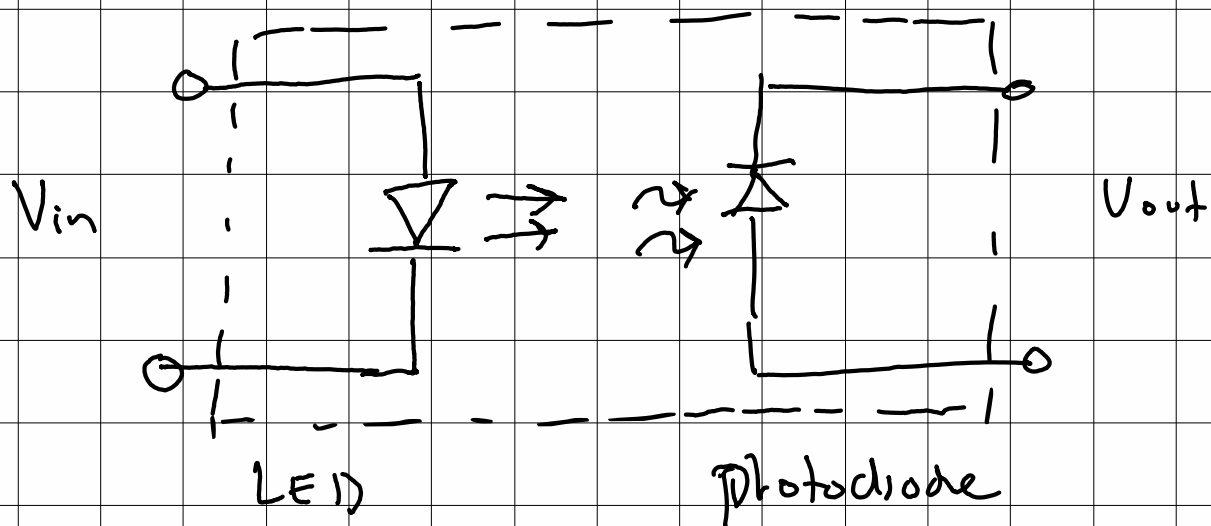

- allows signal transmission between two isolated circuits

Why?

- isolate low-voltage from high voltage circuits