

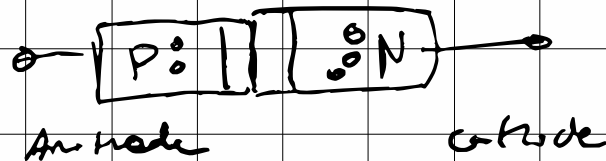


Last time:

- Diodes

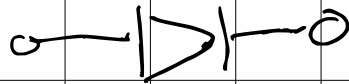


- Zener diodes

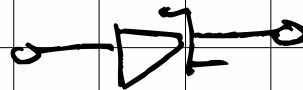

→ operates in Breakdown

- optoelectronic diodes

- LEDs

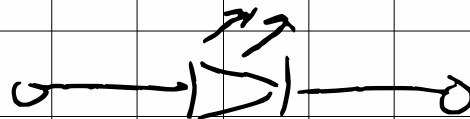


- photo diode



* Main Point : diodes function to
control the flow of current

Correction from last time:

Do diodes act as capacitors?

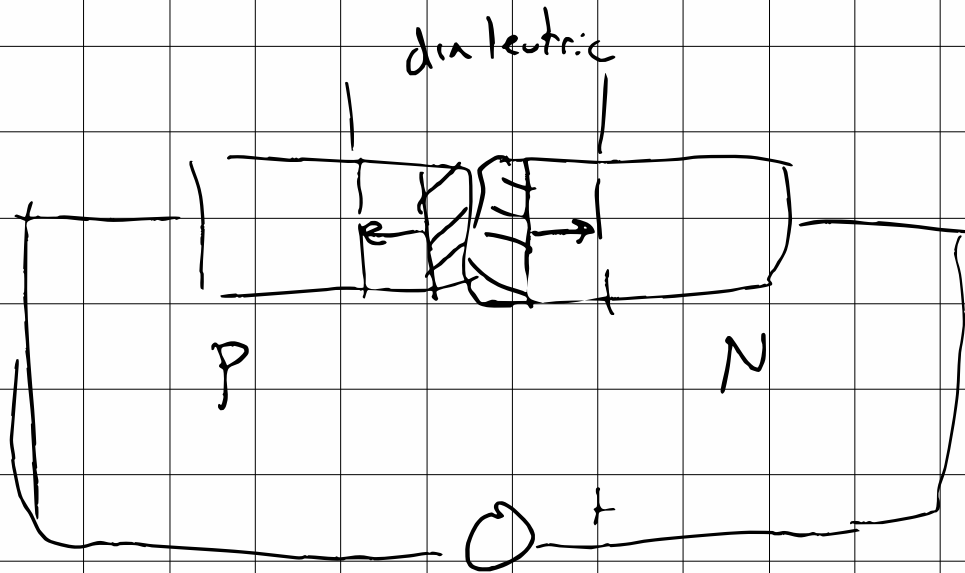

- junction capacitance

- usually ignore it

- also exploit
variable capacitance diodes

Varicap diode

- Variable oscillators


Today :

① quick note on analyzing diodes in circuits

② Transistors


- Bipolar Junctions
 - Field Effect
-

How to analyze diodes in circuits:

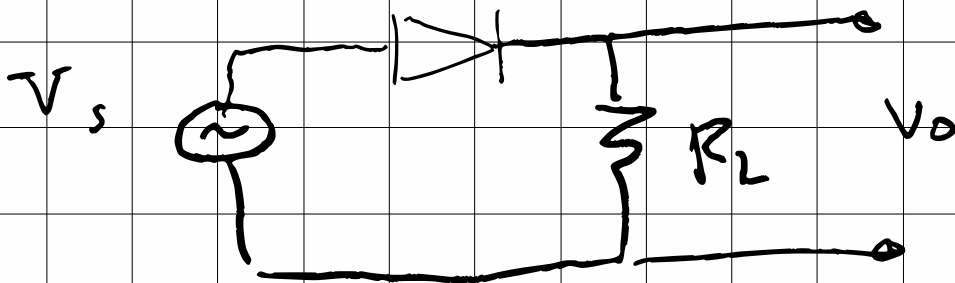


ideal model : $V_s < 0$: open circuit

$V_s > 0$: short circuit

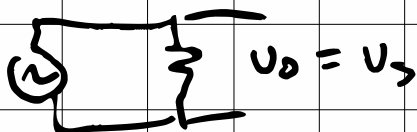


Approximation model (offset model):

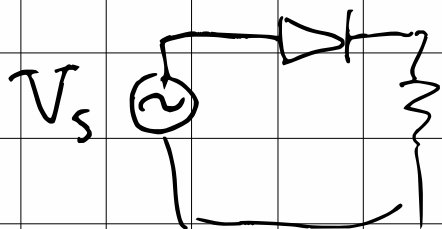

$$V_s < V_D$$




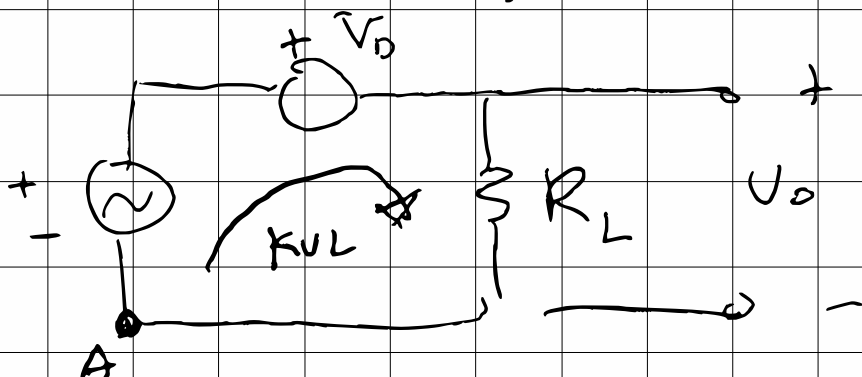$V_s > V_D$: replace diode w/ voltage source = V_D



$$-V_s + V_D + V_o = 0$$

$$V_o = V_s - V_D$$

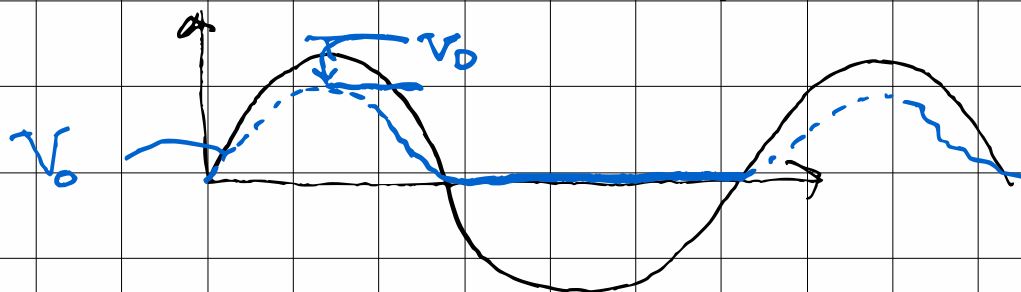

All model are wrong, some models are useful!

Transistors

- these the heart of nearly every electronic device
↳ mechatronic
- the first transistor, bipolar junction, invented in 1948
 - William Shockley, Bell Labs
 - most important technological innovation of the 20th century

Basically Two Functions

- ① Amplification : magnify voltage/current by transferring energy from another source
- ② Switching : control large voltage/current using small voltage/current

Advantages:

① Amplification : transmit tiny signals then amplify them.

② switching : Build logic circuits
Ch. 6

Most Common : BJT, FET

Bipolar Junction

Field Effect

• 3 terminal devices

• 3 terminal Devices



• Two PN junctions

• Channel of doped semiconductor through which current flows



→ conductivity of channel

Bipolar Junction


NPN transistor (n-channel)

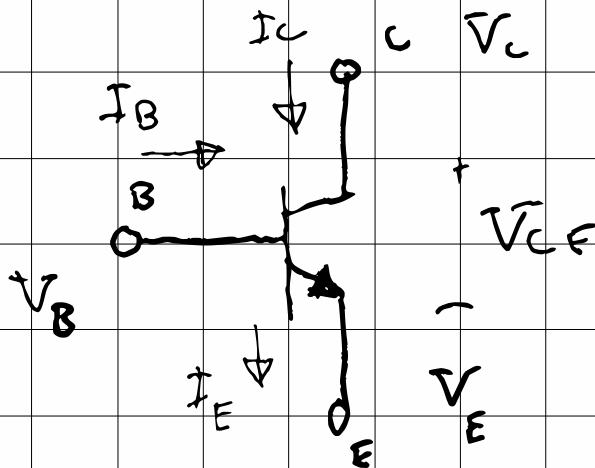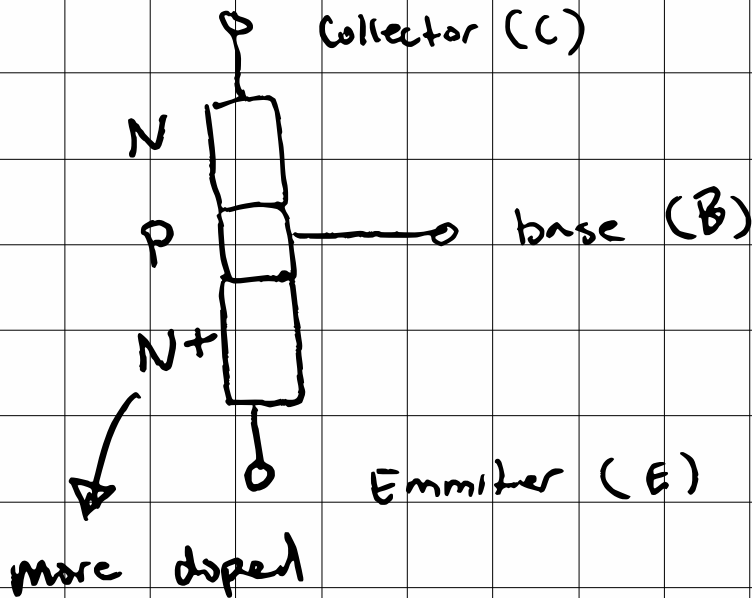

PNP transistor (p-channel)

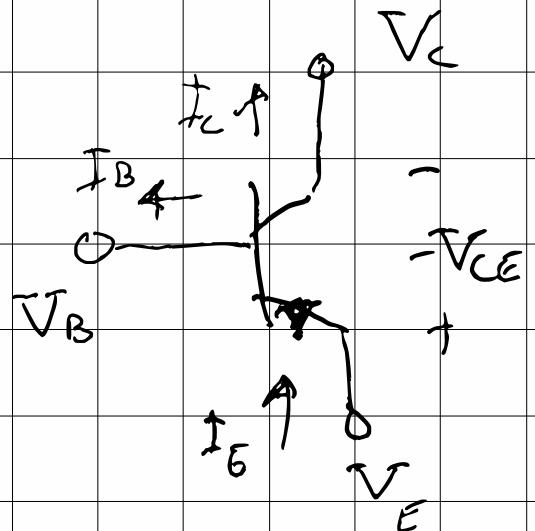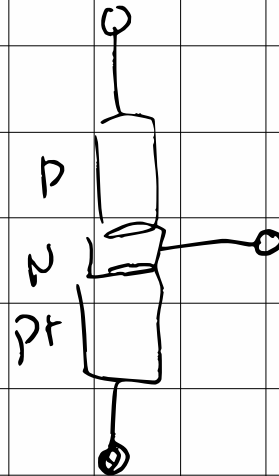

NPN Working Principle

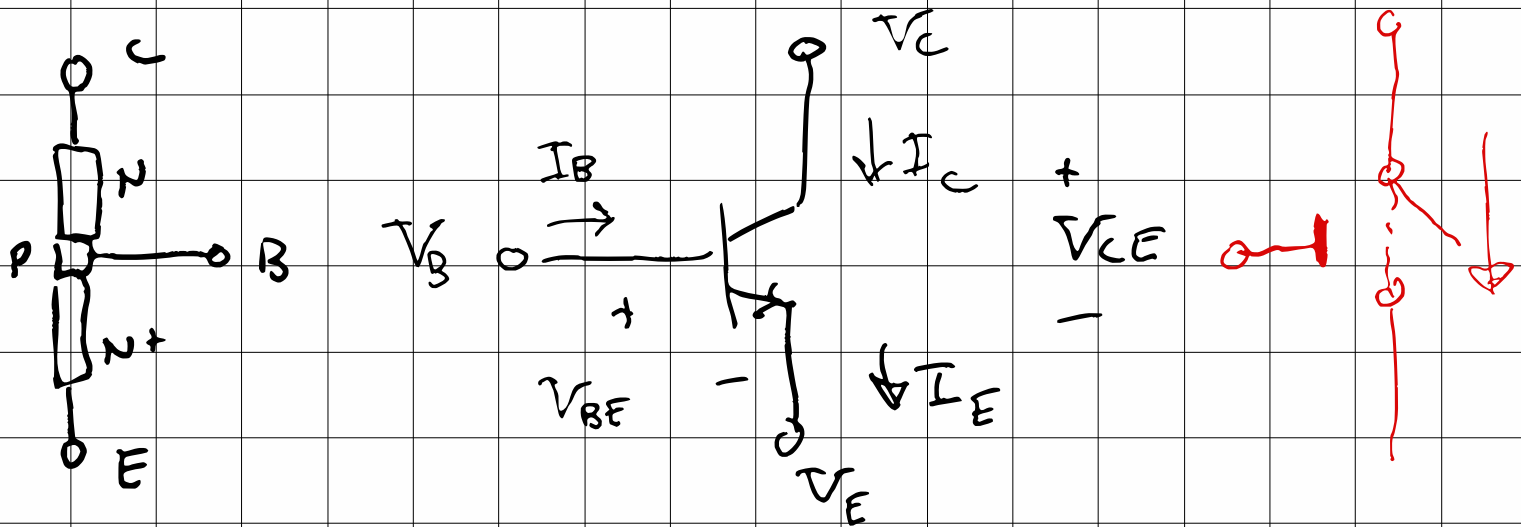


$$\begin{aligned} I_E &= I_C + I_B \\ V_{BE} &= V_B - V_E \\ V_{CE} &= V_C - V_E \end{aligned}$$


For the transistor to be on, base-to-emitter must forward bias

$$V_{BE} = 0.7 \text{ V}$$

$$V_B = V_E + 0.7 \text{ V}$$

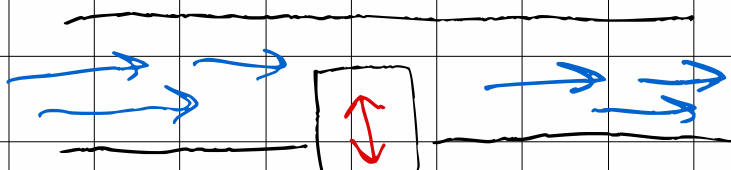- When this is the case, large collector current (I_C) flows, with small base ($I_B \ll I_C$)
- small voltage drop V_{CE}



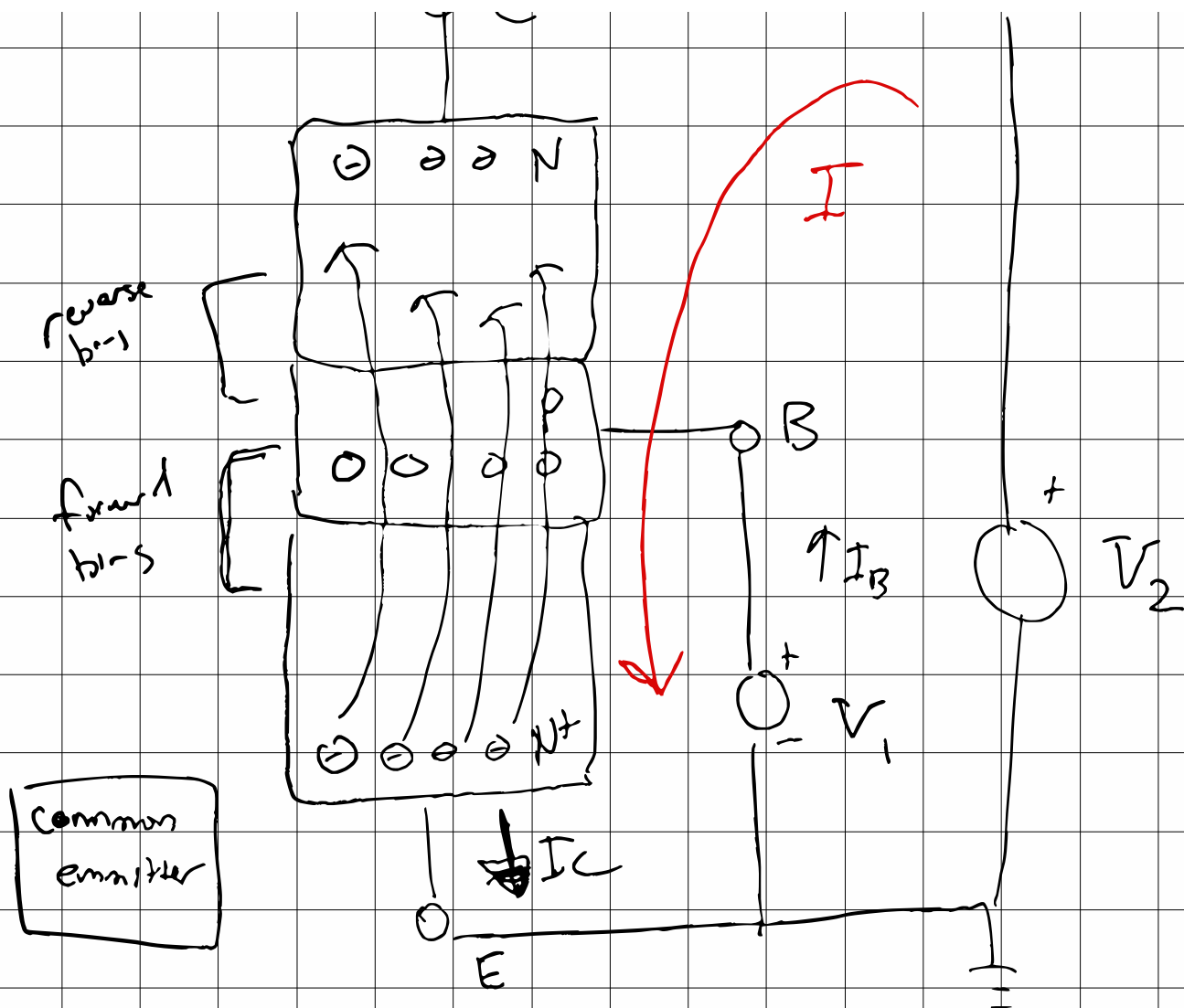

Collector : collects e^- } When transistor is on
 emitter : emits e^-

P-region is small, e^- have enough momentum to cross

Take away: small current I_B allows a larger current I_C to flow

$$I_C = \beta I_B$$

amplification factor -

BJT's have 3 modes

- Active :
- Increase $I_B \rightarrow$ Increase I_C
 - proportional currents

$$\underline{I_C = \beta I_B} \quad (\text{linear growth})$$

- amplifier

Saturation :

$V_{CE} \approx 0$; max current flows

- $I_E \gg I_B \quad I_B \approx I_C$

- both junctions are forward bias


- like a short circuit
(switching behavior)

Cutoff :

- $V_{BE} < 0.7$ no current flows
- open circuit


Fig. 3.18

active region

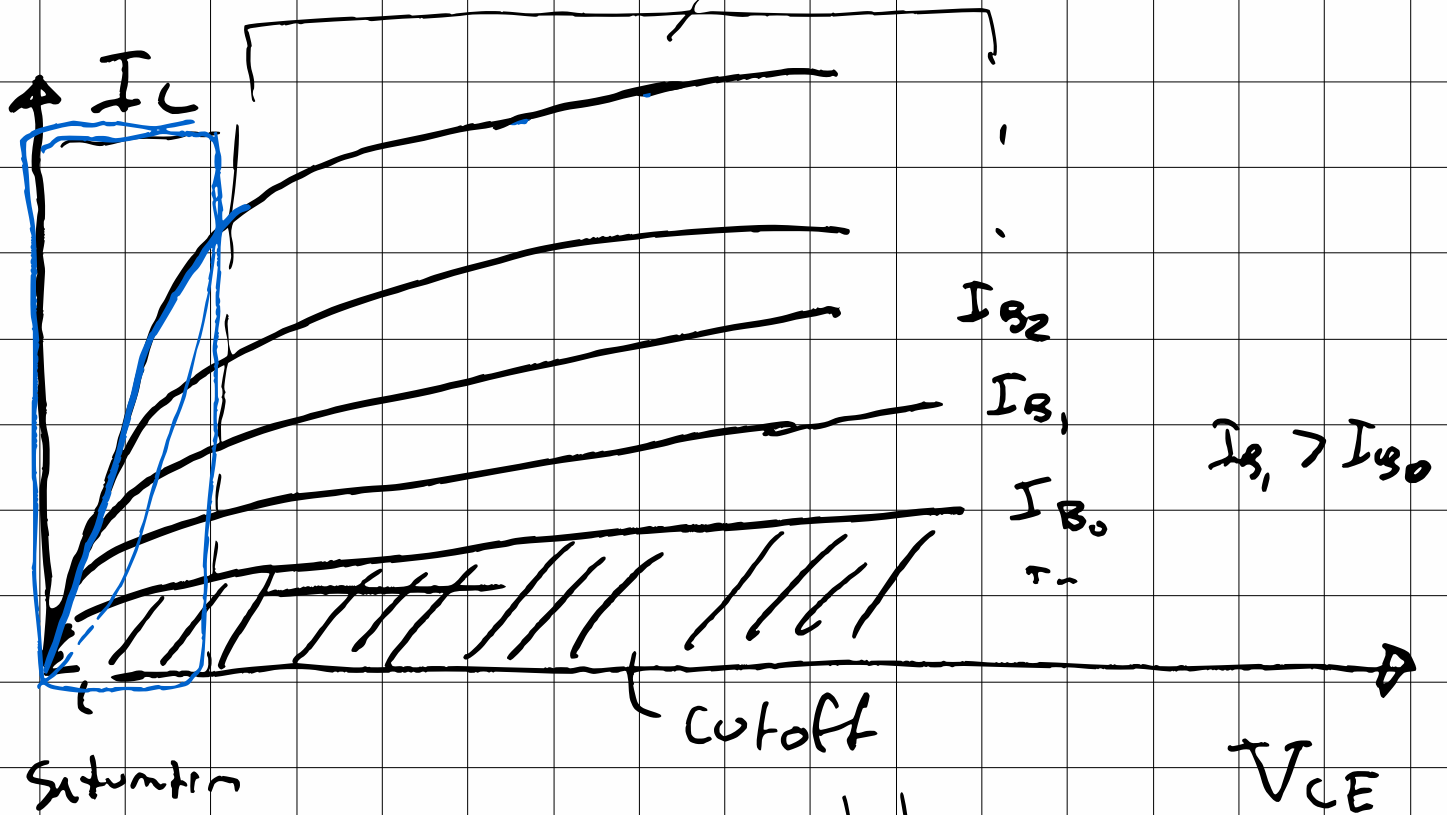


Saturation region

I_C doesn't depend on I_B

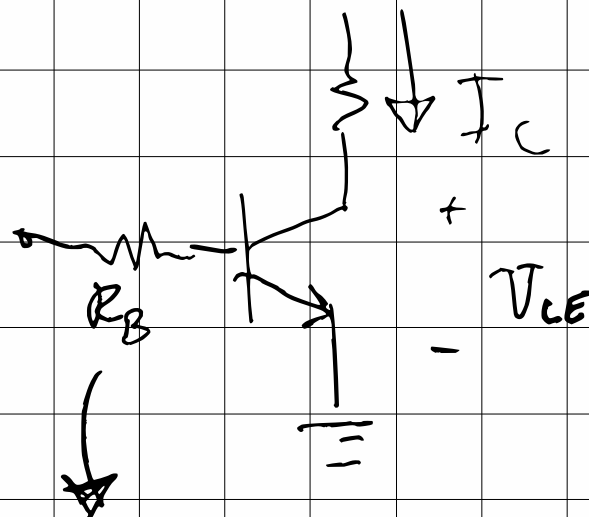


tune R_B to ensure saturation

BJT as a switch

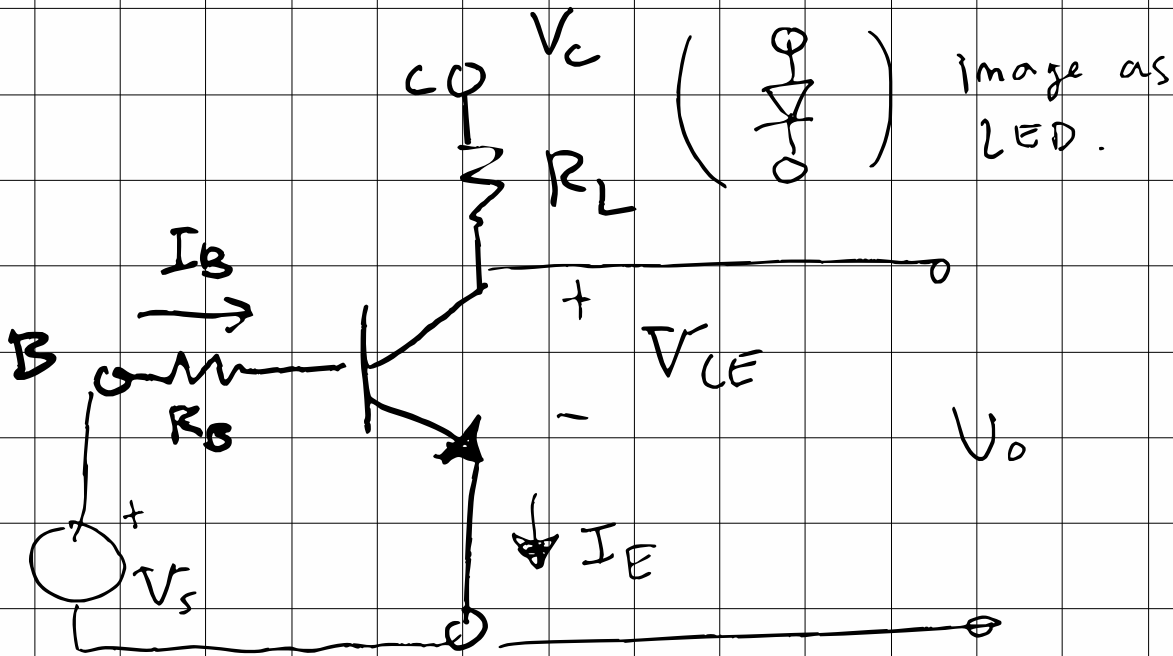

$$V_s < 0.7 \text{ V}$$

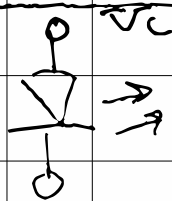collector - emitter $\rightarrow$ open circuit



LED off



LED on

$$V_s > 0.7 \text{ V}$$

collector - emitter $\rightarrow$ short circuit




$$I_B = \frac{V_s - V_{BE}}{R_B}$$

saturation

$R_B \rightarrow$ to ensure saturation.

Application

- power transistors

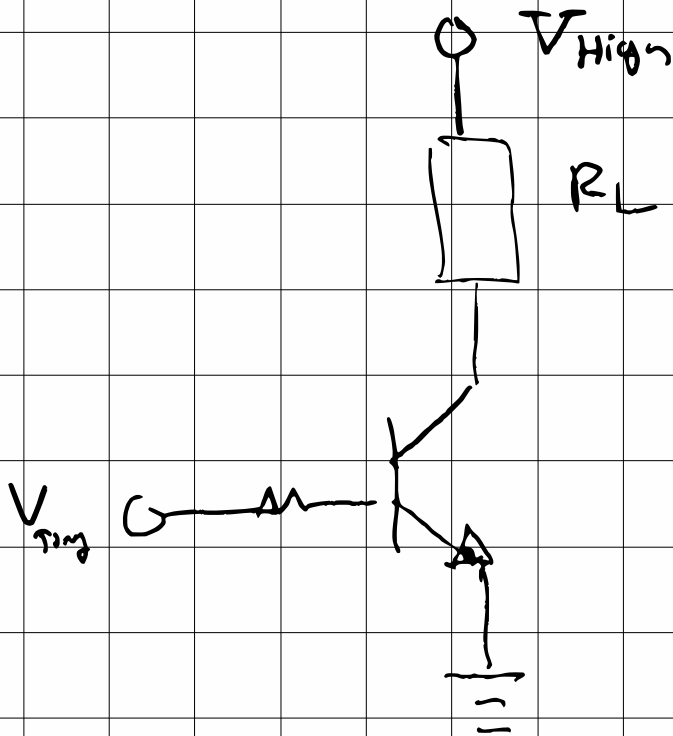


-
- Darlington Pair



Very large
current
gain

power amp / fraction

• Motor Control (H-Bridge)

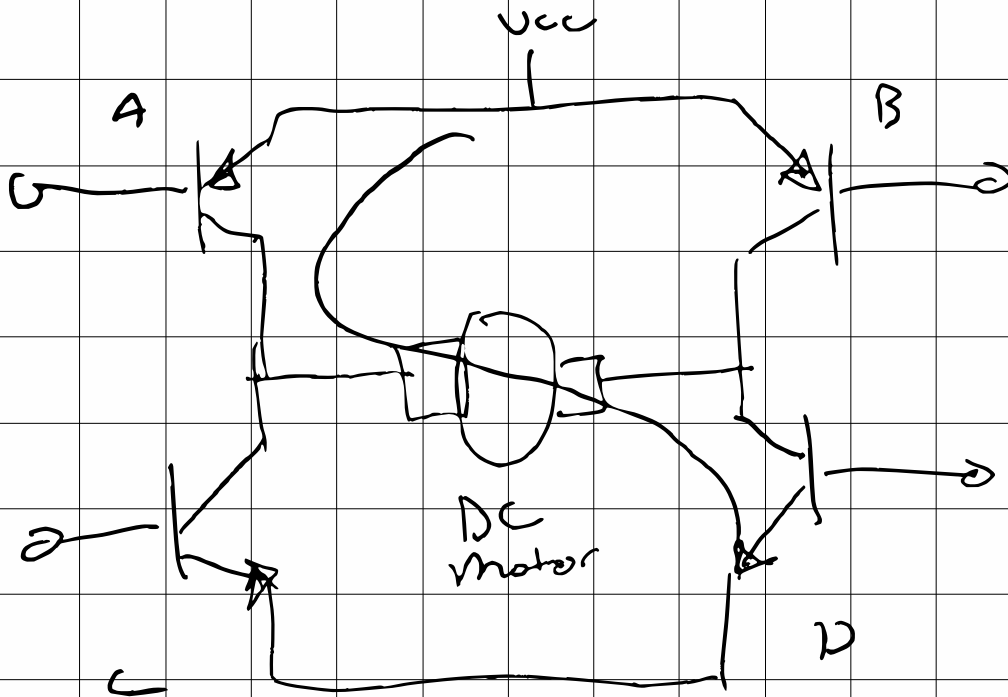

• optoisolators → photo transistor

