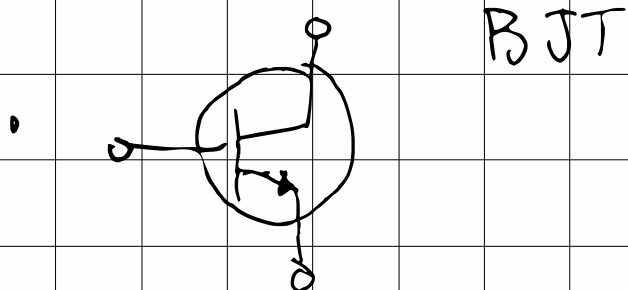


Last time:




- Slight correction : NPN - BJT
(NOT N-channel)
PNP - BJT
(NOT P-channel)

Today :

- ① summarize BJT switch
- ② FET overview

Summary for designing BJT switch

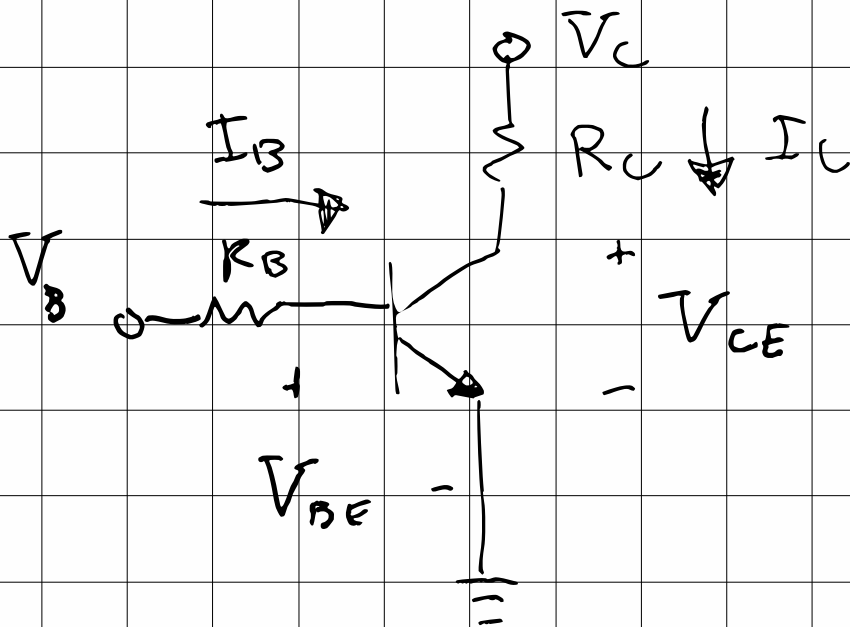

① $V_C > V_B > V_E$

collector must be more positive than
base & emitter

② To turn ON $V_{BE} > 0.7V$ (Typically)


③ I_C is independent of I_B when in
saturation.

④ Minimum base current I_B for saturation
can be found $I_{B_{min}} \approx I_C / \beta \rightarrow I_B = I_{B_{min}} \times 10$

Goal: Design LED switch

Ex. 2.4

PN2222

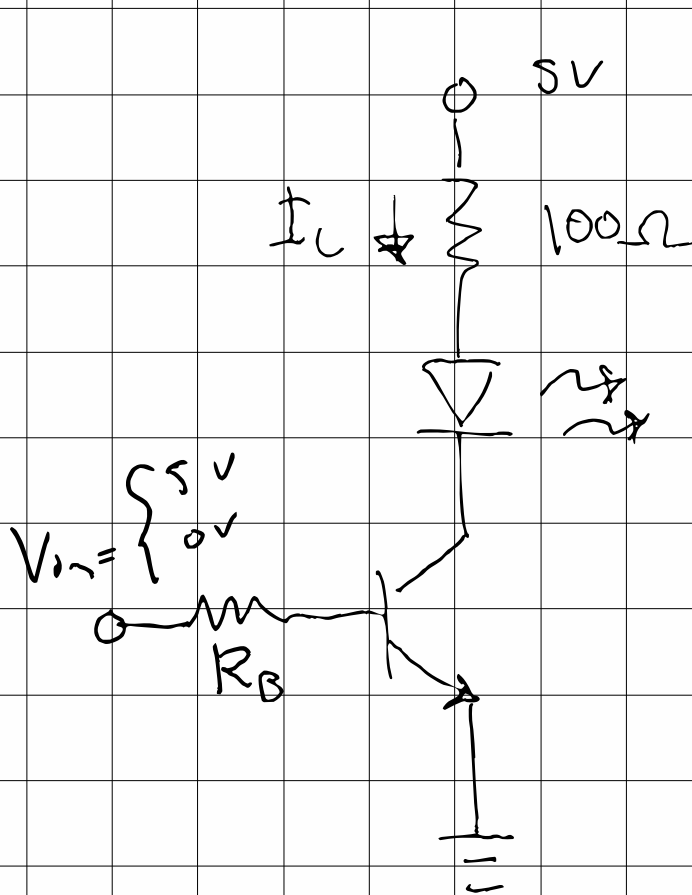

$$V_{BE(sat)} = 0.6V$$

$$V_{CE(sat)} = 0.3V$$

$$\beta = 100$$

$$V_D = 2.0V$$

Assumption about
the voltage of the diode

$$I_C = \frac{V}{R} = \frac{5 - 2 - 0.3V}{100\Omega}$$

$$I_C = 27mA$$

$$I_{B_{min}} \approx \frac{I_C}{\beta} = \frac{I_C}{100} \approx 0.3mA$$

$$I_B = I_{B_{min}} \times 10 = 3mA$$

$$\frac{5V - 0.6V}{R_B} \approx 3mA$$

$$\frac{4.4V}{3mA} = R_B \approx 1.5k\Omega$$

Take away, we design R_B to ensure BJT is in saturation when turned ON.


Field - Effect Transistors (FETs)

- Basic idea:

voltage on one electrode controls the charge carriers in a "channel"

channel: narrow region where current flows

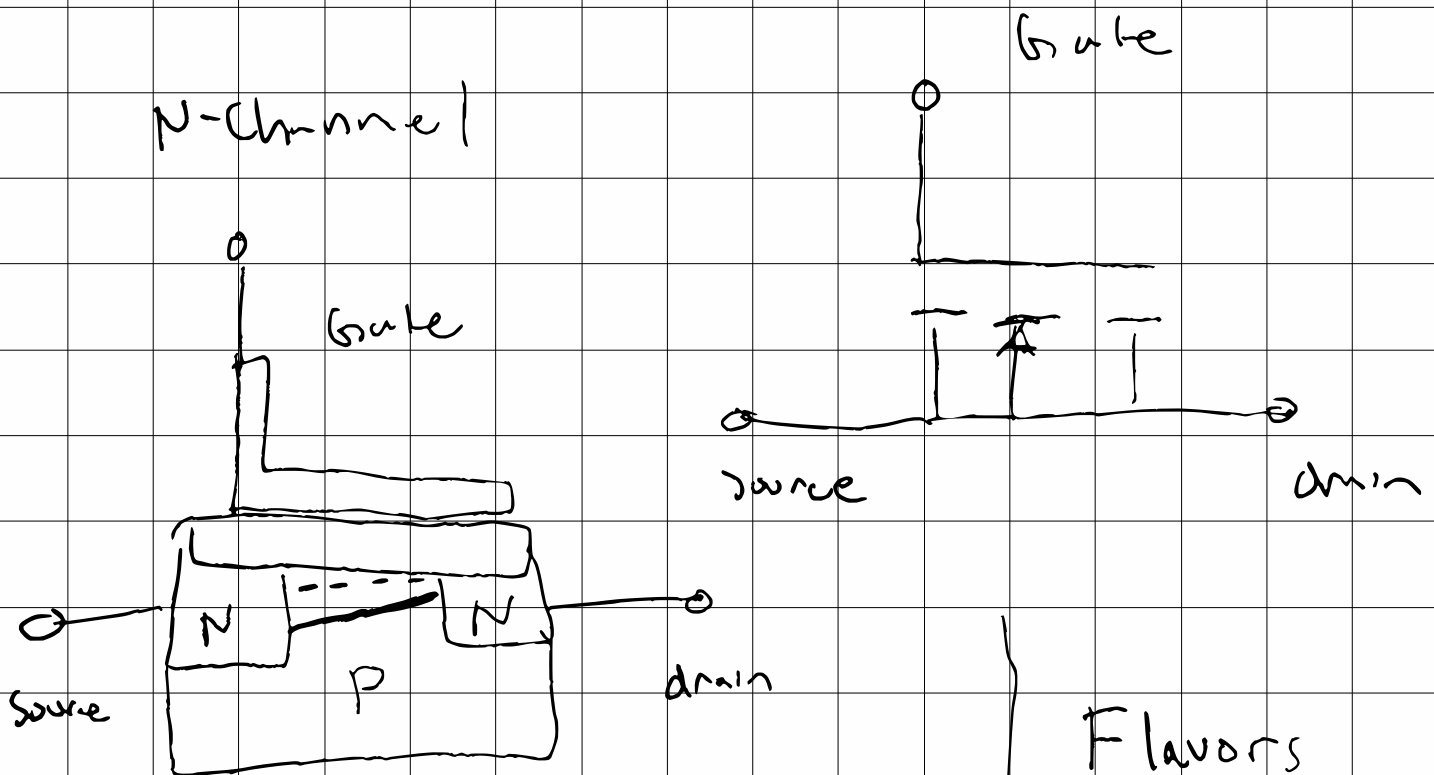- transconductance amplifier
 → output current is
 controlled by input voltage



Analogy with BJT

gate → base
 drain → collector
 source → emitter

Flavors

metal-oxide
 semiconductor
 (MOSFET)

Junction FET

✓ Enhancement mode : off $V_g = 0$
- common for switching

Depletion mode : on $V_g = 0$
- load resistors for logic circuits
JFET are depletion


Which to use?

Case - by - case .


n-Channel enhancement Mode MOSFET

Fig. 3.30

(switch for BJT)

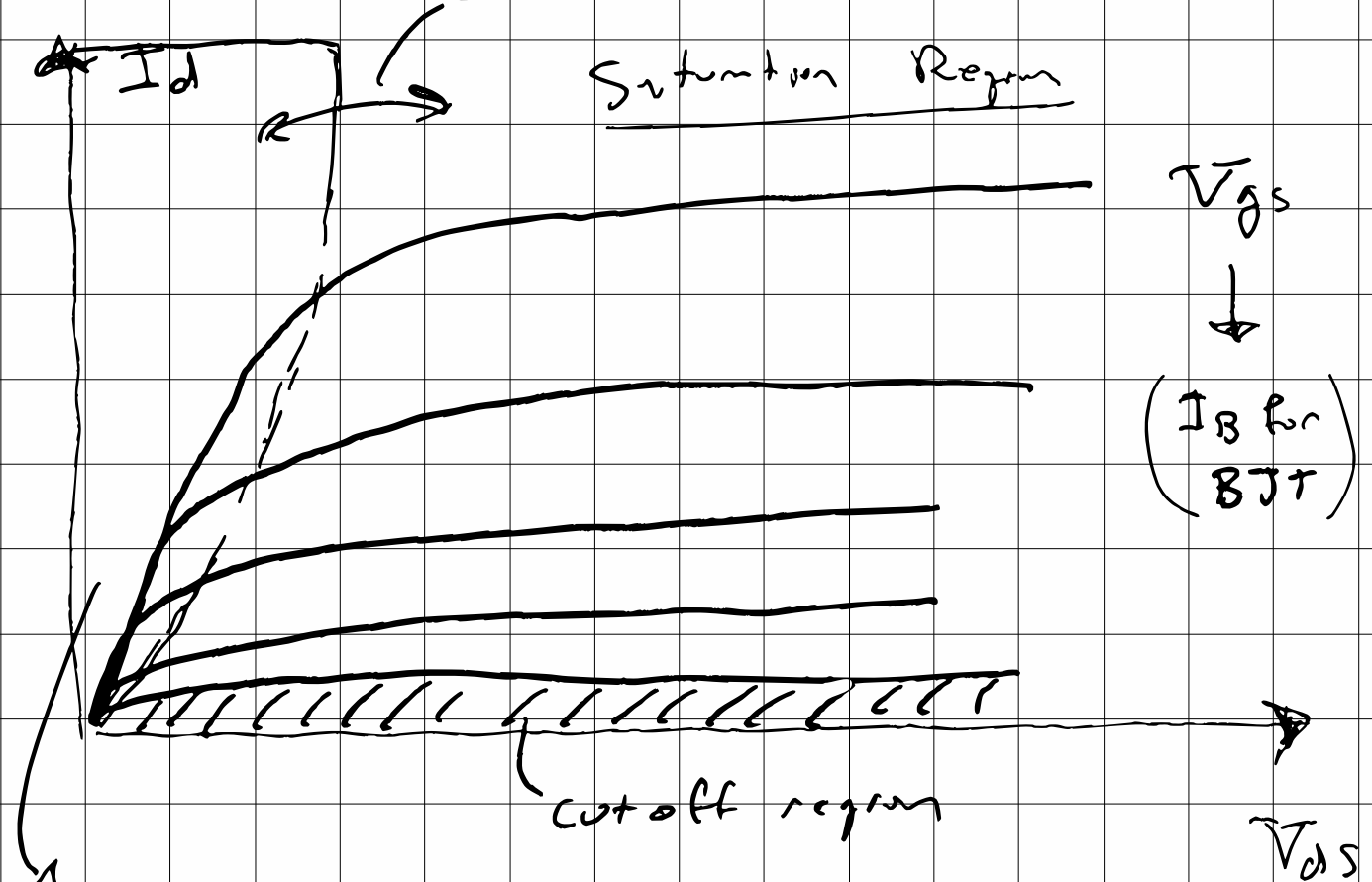

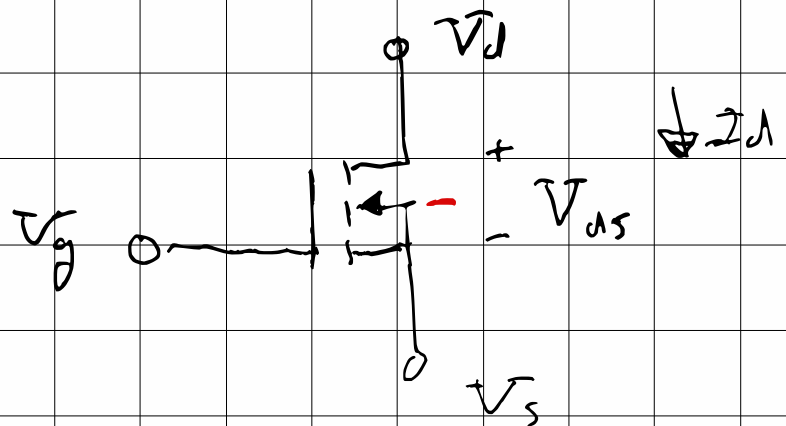active region
(ohmic region)
variable resistor




* Saturation region of MOSFET corresponds to active region of BJT (roughly)


Symbols for FETs

Principle Characteristics

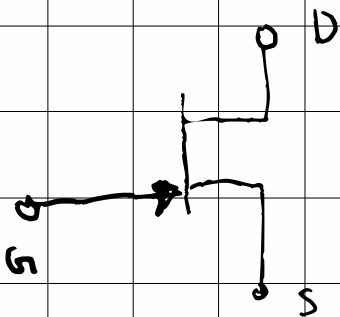- ① Gate/substrate arrow distinguishes between p-channel (arrow out) & n-channel (arrow in)
- ② A separation is shown between gate & source in MOSFET
- ③ Broken line: enhancement mode
Solid line: depletion mode




n-channel JFET

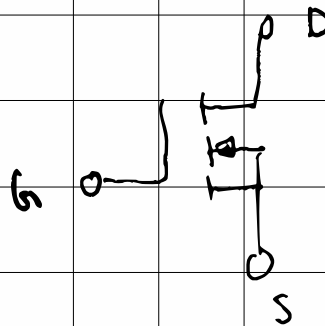


n-channel MOSFET

Fig. 3.33
(3.37 5th ED)

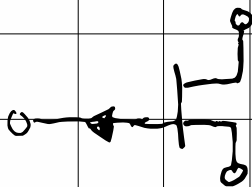

p-channel JFET

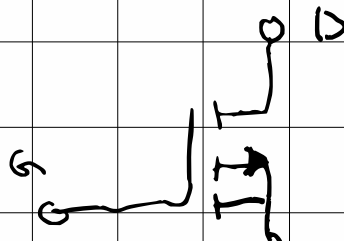

p-channel MOSFET

Applications

- Switching power

→ practically no current @ input!

→ BJT we need to design R_B for saturation

- Analog switch

→ pass analog signals

- memory :
 DRAM
 ROM
 RAM

- Sensors :

gas sensors (GASFET)


pressure sensors (PRESSFET)

•
•
•

- CMOS chips

CMOS

Complementary Metal-Oxide-Semiconductor

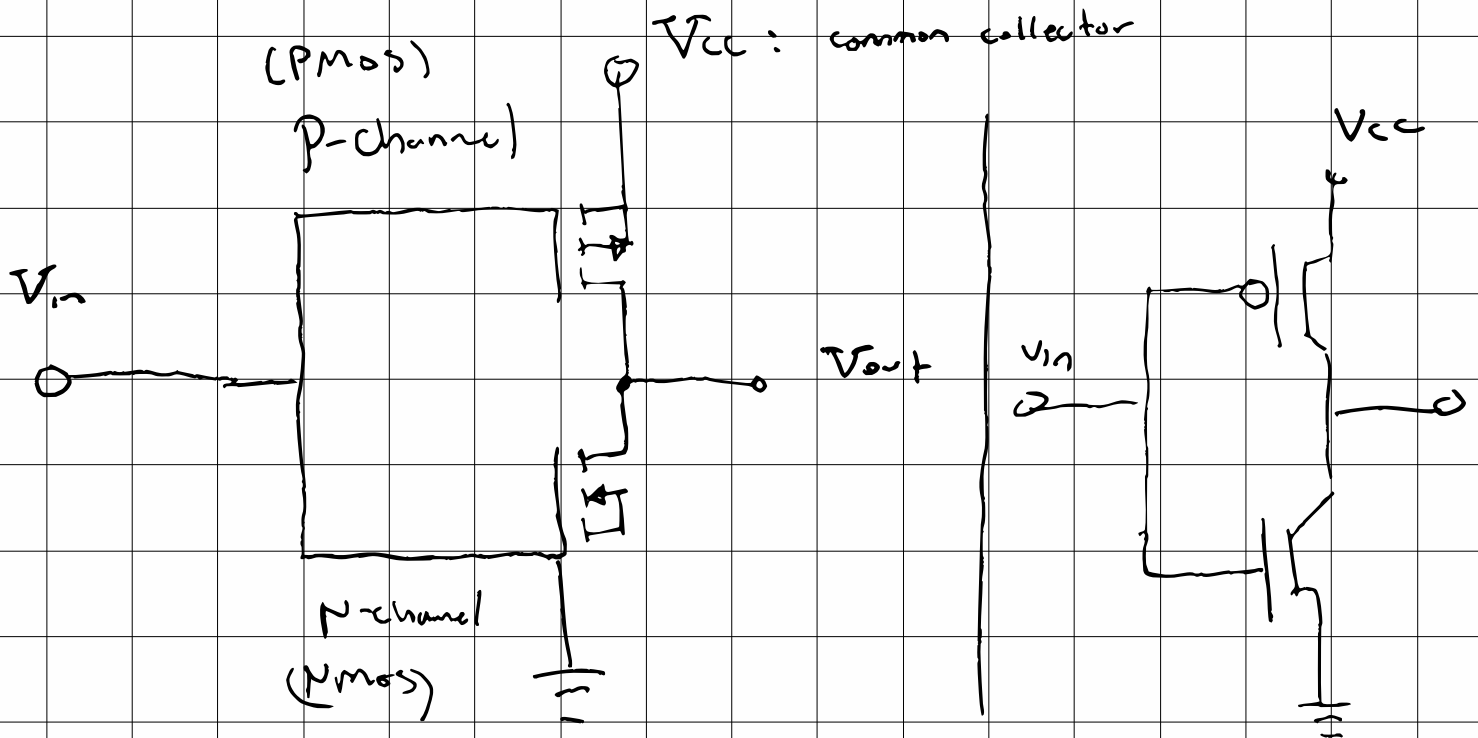


CMOS Inverter : $V_{in} \rightarrow$ common gate input

$V_{in} \approx 0V$, NMOS = OFF, PMOS = ON

$V_o = V_{cc}$ (HIGH - Logic 1)


$V_{in} \approx V_{cc}$, NMOS = ON, PMOS = OFF

$V_o = 0$ (LOW - Logic 0)

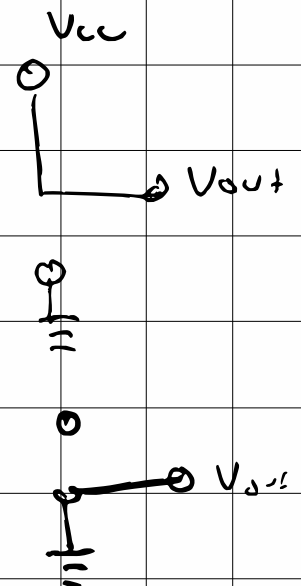

Low circuit

Arduino output

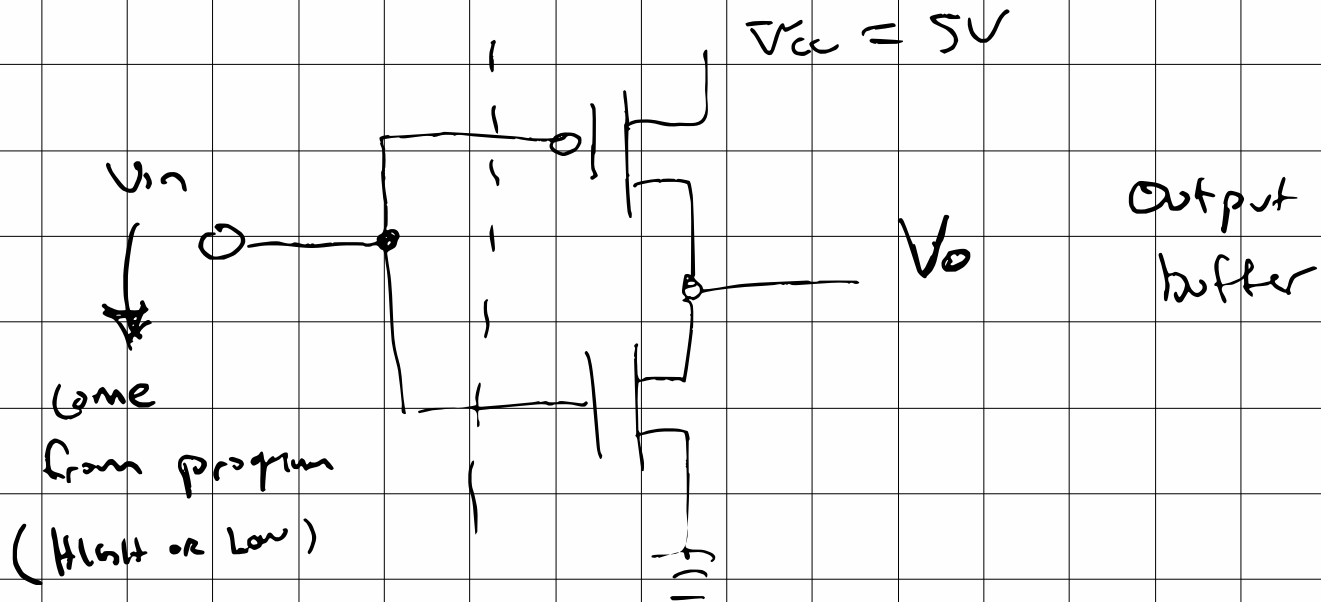

Pin looks like when configure as output

Summary

Control

BJT: current controlled

FET: voltage controlled

Gain

BJT: larger current gain

FET: gain small

Size

BJT: large compared FET

FET: very tiny (Moore's Law)

