

ME 133

2/14/23

## Lecture 10 - midterm Review

### Exam Structure

- 4 - 5 problems
- no numeric calculations
- closed book
- front / back sheet of notes (1 page)
- mix of conceptual & symbolic derivations.


---

OFFICE HOURS by email first  
9-6pm. except. 3-4pm.

# Correction from Last Lecture

Zero-order system example:

Force sensitive resistor

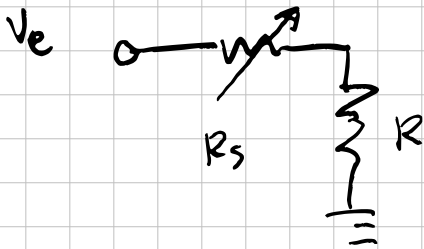


$$\frac{V_o}{V_e} = \frac{R}{R_s + R}$$




$$\frac{V_o}{F_{in}} = \underbrace{\tilde{f}(F_{in})}_{\text{gain}} \cdot V_e$$

gain: nonlinear but static  $\rightarrow$  doesn't change w/ time


# ① Overview of Mechatronics

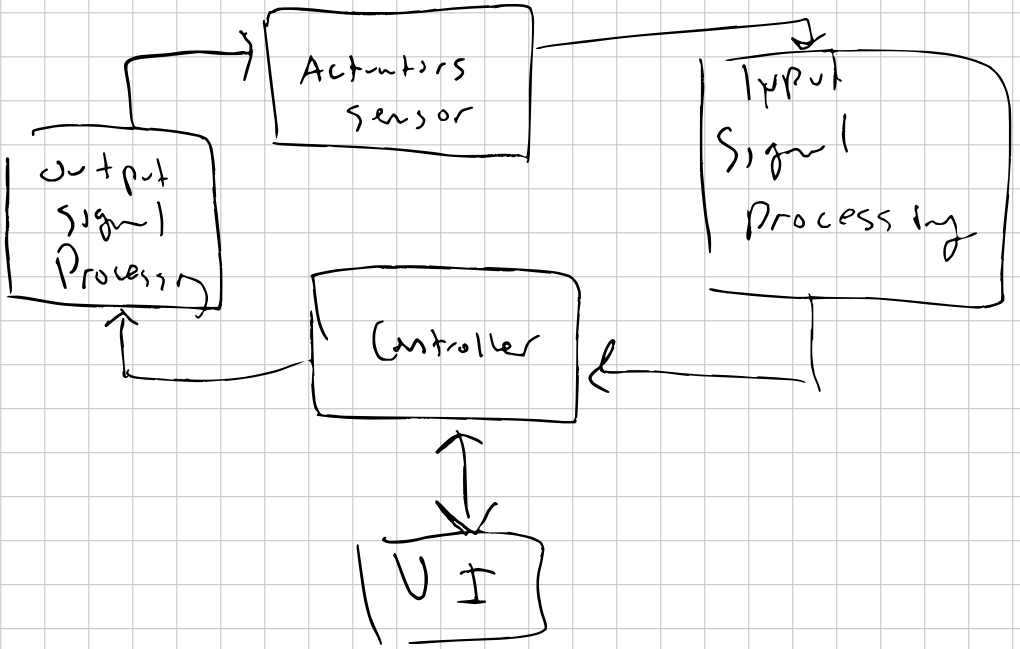

# ② Basic Circuits

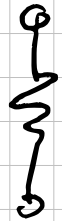


R

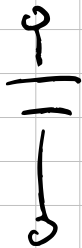

C



L

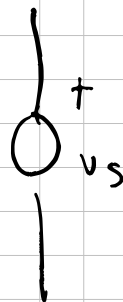


$V_s$



$I_s$


# Kirchoff's Laws

KVL:  $\sum_{i=1}^N V_i = 0$

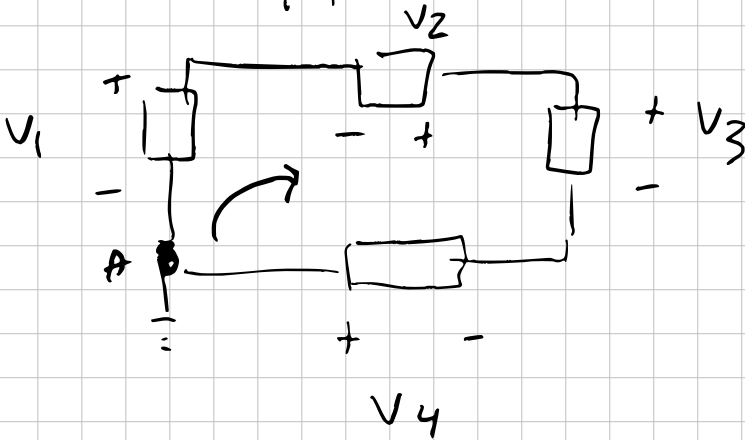


$$-V_1 - V_2 + V_3 - V_4 = 0$$

KCL:  $\sum_{i=1}^N I_i = 0$

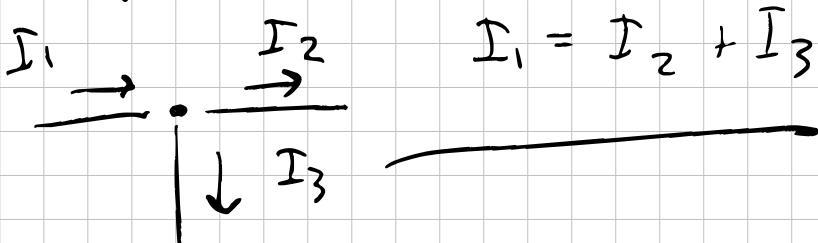

Fond  $V_{out}$ ?

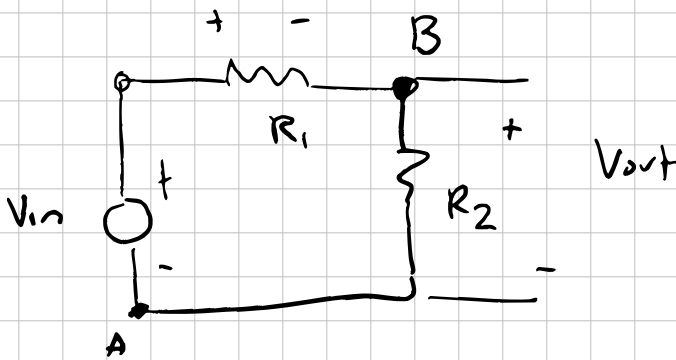

1. KVL:  $-V_{in} + V_{R_1} + \overbrace{V_{R_2}}^{V_{out}} = 0$


2. KCL:  $I_{R_1} = I_{R_2}$

$$\frac{V_{R_1}}{R_1} = \frac{V_{R_2}}{R_2}$$

$$V_{R_1} = \frac{R_1}{R_2} V_{R_2}$$

$$V_{in} = \left( \frac{R_1}{R_2} + 1 \right) V_{out} \Rightarrow \frac{V_{out}}{V_{in}} = \frac{R_2}{R_1 + R_2}$$

## Current Divider

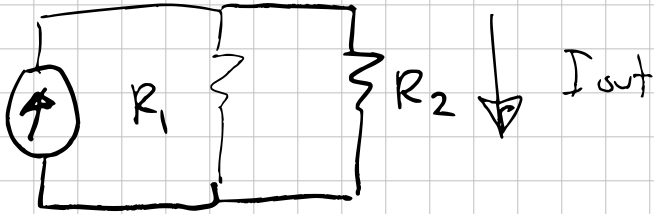

$$\text{KVL: } V_{in} = V_{R_1} = V_{R_2}$$

$$\text{KCL: } I_{in} = I_{R_1} + I_{R_2}$$


$$\frac{I_{out}}{I_{in}} = \frac{R_1}{R_1 + R_2}$$

- Equivalent Circuit Analysis


→ Thevenin

→ Norton

Thevenin :

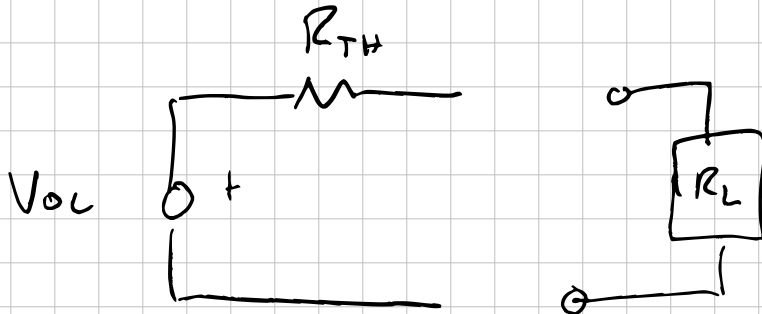

Norton

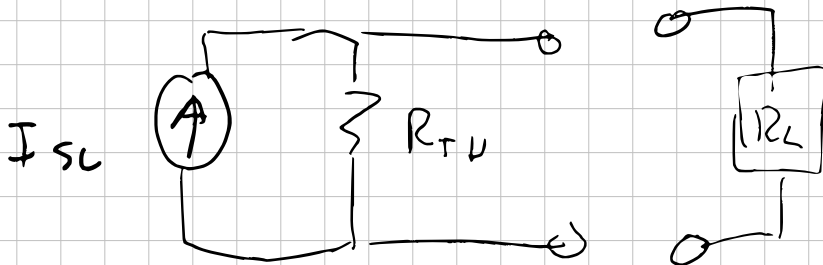

# AC-Analysis

$$\begin{aligned}V &= \vec{V}_m e^{j(\omega t + \phi)} \\&= \vec{V}_m \langle \phi \rangle \\&= \vec{V}_m \sin(\omega t + \phi)\end{aligned}$$

Ohm's Law generalized:

$$V = \underset{\substack{\uparrow \\ \text{Impedance}}}{Z} I$$

$$Z = f(\omega)$$

$$Z_C = \frac{1}{j\omega C}, \quad Z_L = Lj\omega, \quad Z_R = R$$




## Transformers

$$V_s = \frac{N_s}{N_p} V_p$$

$$I_s = \frac{N_p}{N_s} I_p$$

---

## Ch. 3 Semiconductors

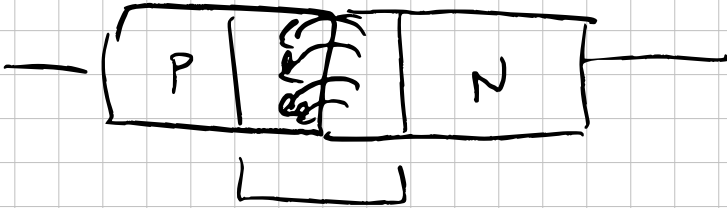


depletion region


contact potential 0.7 V

• Reverse bias vs forward bias

- Know basic circuits

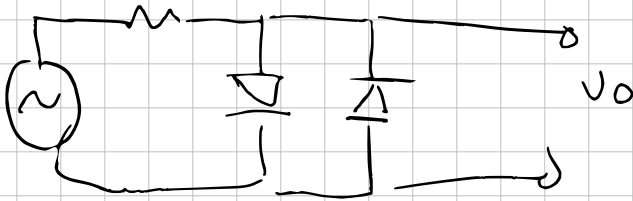

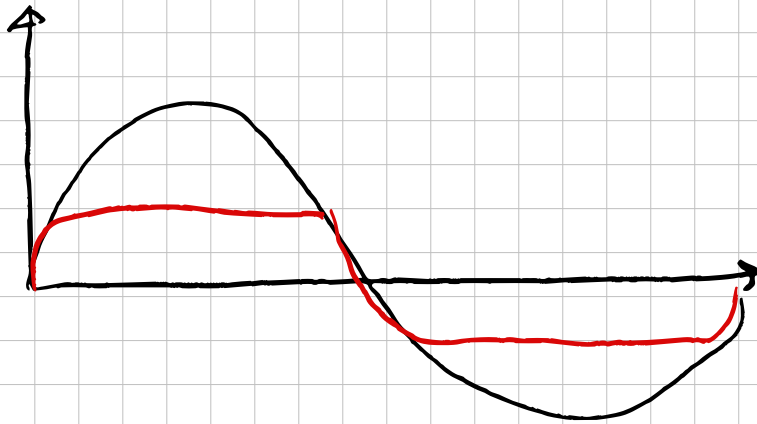Draw the output in  $V_{in} = \sin(\omega t)$



ideal vs approximate model.



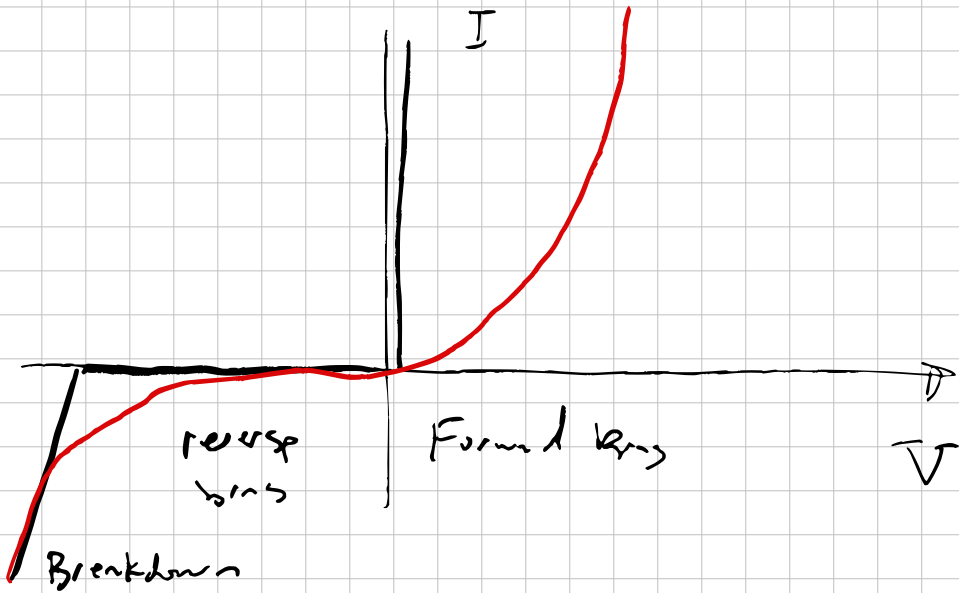


Fig. 3.6

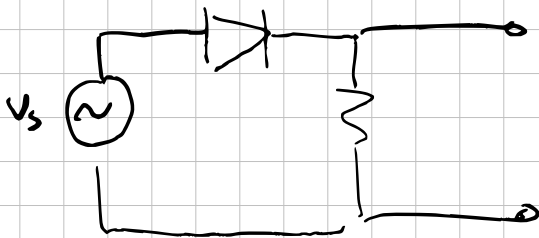

approximate mode

$V_s > V_0$

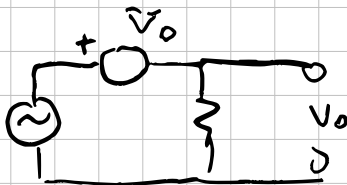

$V_D = V_s - V_0$

0.7V



# • Transistors

→ Function:

\* amplification

\* Switch

→ BJTs    |    FETs


• What's the difference

BJT: current controlled

FET: voltage controlled

only ask about NPN or  
n-channel transistors

# Common-emitter circuit

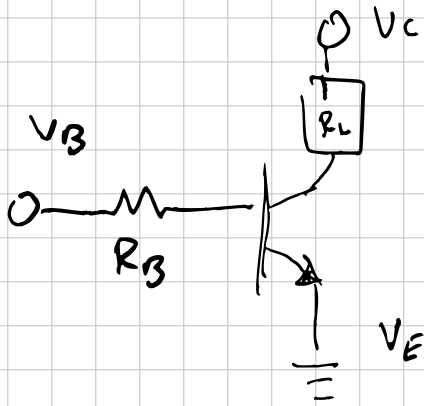


- When is the transistor on?

$$\begin{cases} V_B = V_E + 0.7 \text{ V} \\ V_C \geq V_B \end{cases}$$

- Know how to choose  $R_B$

↳ want to ensure  
that its in saturation
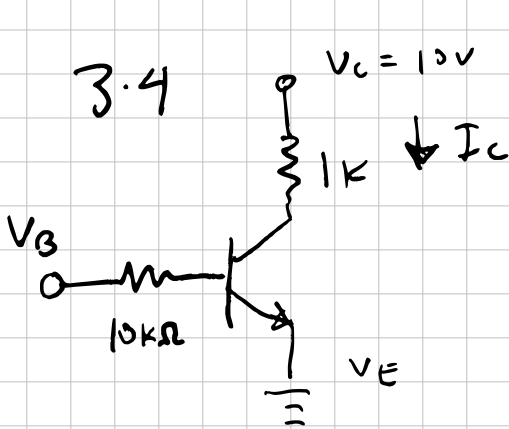
$$I_{B_{\min}} \approx \frac{I_C}{\beta} \quad \text{hFE} \quad (2-5)$$
$$I_B = I_{B_{\min}} \times 10$$



$$V_{CE} = 0.2V$$

$$\beta = 100$$

$$V_{BE} = 0.7V$$

Find  $V_B$  to saturate BJT:

$$I_C = \frac{V_C - V_{CE}}{R_C} = \frac{10V - 0.2V}{1k\Omega}$$


$$= 9.8mA$$

$$I_{Bmin} = \frac{I_C}{\beta} = 0.098mA$$


$$V_{Bmin} = I_{Bmin} \cdot R_B + V_{BE}$$

$$= 1.68V$$

## . FET Basic

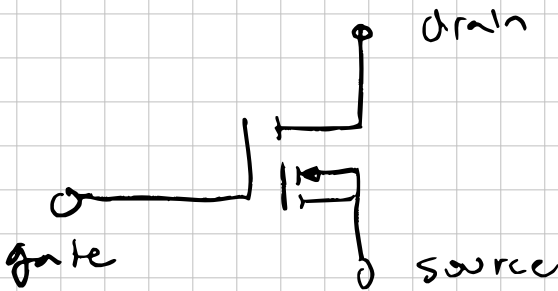

Ch. 4.

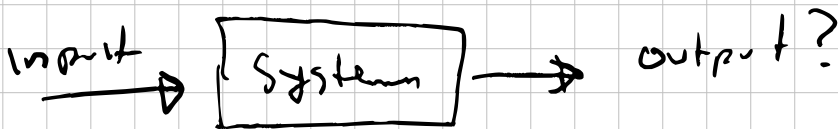

"measurement system"




What makes a good measurement system?

- Amplitude linearity
- Bandwidth
- Phase linearity



## • Fourier Analysis


→ interpret

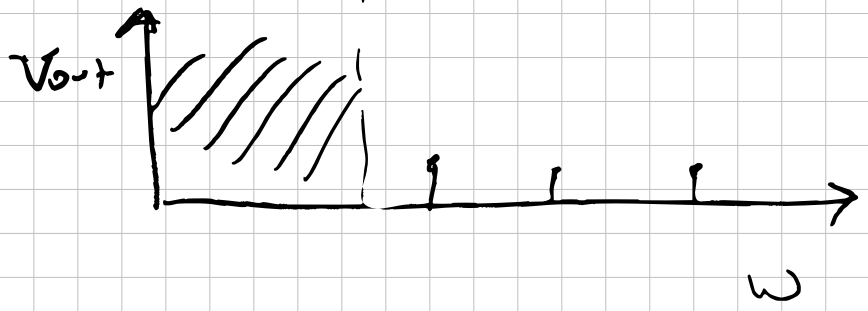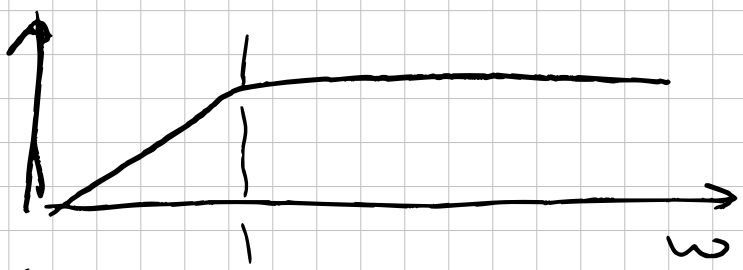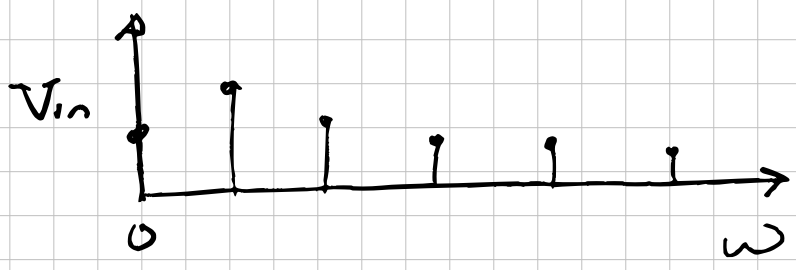



$$\text{dB} = 20 \log \left( \frac{A_{\text{out}}}{A_{\text{in}}} \right)$$
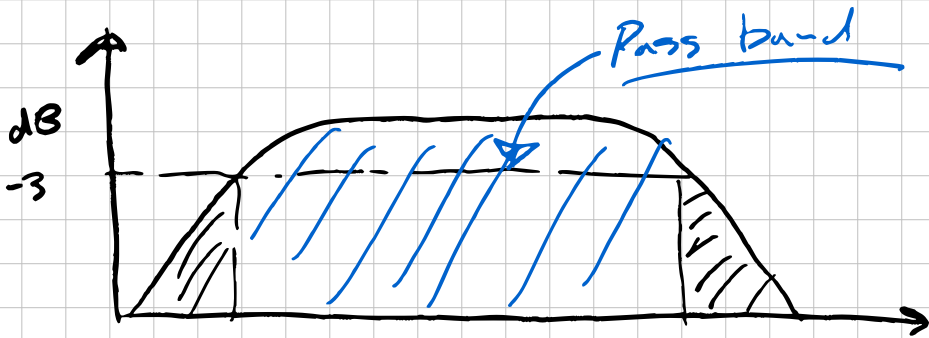
$$60 \text{ dB} \rightarrow A_{\text{out}} = 1000 \cdot A_{\text{in}}$$




• Why -3 dB?

$$\frac{P_{\text{in}}}{P_{\text{out}}} \text{ (Power)} = \frac{1}{2}$$

$$\rightarrow \frac{V_{\text{out}}}{V_{\text{in}}} = \frac{1}{\sqrt{2}} = 0.707$$

Half power point!

Example: what is the cutoff freq?

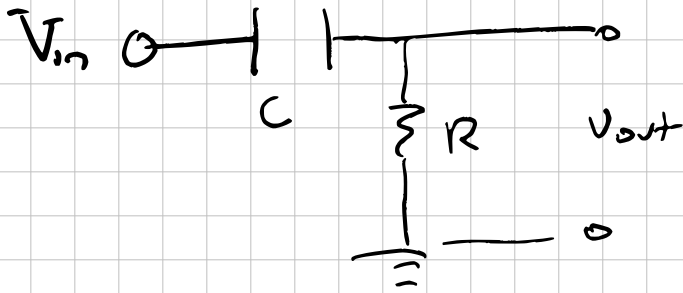

$$\frac{V_{out}}{V_{in}} = \frac{Z_R}{Z_C + Z_R}$$

$$= \frac{R}{\frac{1}{j\omega C} + R} = \frac{j\omega RC}{j\omega RC + 1}$$

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{\omega RC}{\sqrt{1 + (\omega RC)^2}} = \frac{1}{\sqrt{2}}$$

$$\omega = \boxed{\frac{1}{RC} = \omega_c}$$

$$\omega \rightarrow 0 \quad \left| \frac{V_{out}}{V_{in}} \right| \rightarrow 0$$

$$\omega \rightarrow \infty \quad \left| \frac{V_{out}}{V_{in}} \right| \rightarrow 1$$


$$\omega_c = \frac{1}{RC}$$




Should know other filters:



LP

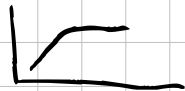

HP

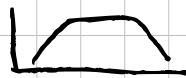

BP



notch

- phase linearity

$$\phi = k \cdot f$$

phase scaled with frequency.

↳ time delay is constant across freq.

---

- zero-order system.

$$X_{out} = \left( \frac{B_0}{A_0} \right) X_{in}$$

↑  
gain or sensitivity

- first order system

$$\tau \dot{X}_{out} + X_{out} = K X_{in}$$

↑  
time constant.

show:  $X_{out} = K_{Am} (1 - e^{-t/\tau})$

Step response



recovery time  $\tau \rightarrow$  system ID