
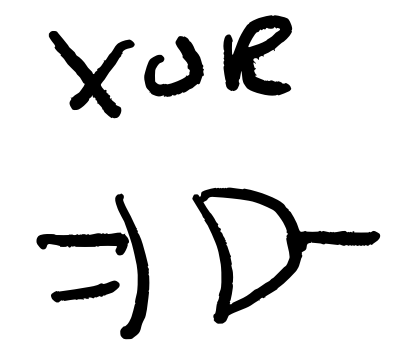
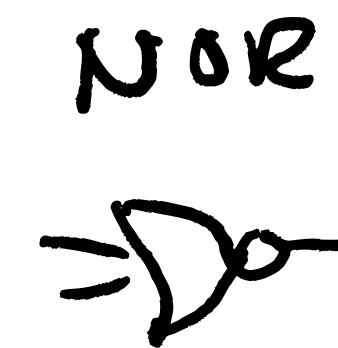
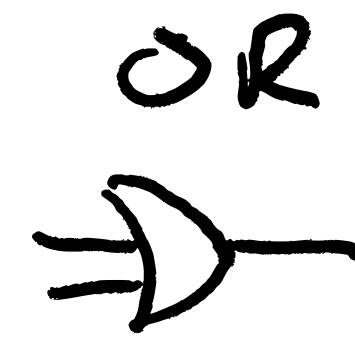
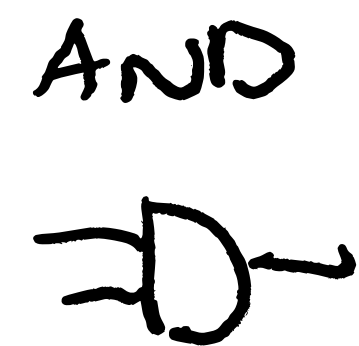


Last time:

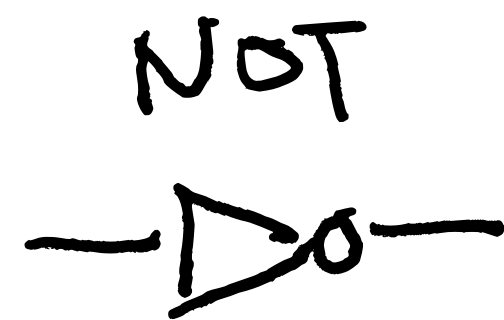- > Digital Signals
- > Representation
- > Combinational Logic



Today:

> Lab project

> Examples

> Timing Diagrams

> Boolean Algebra

MakerSpace opens soon!

Please join the open house
if you're available

MEDDL


Mechanical Engineering Design &
Development Laboratory

BCOE Faculty, Staff and Students
join us for our open house on
February 28th.

Where: Bourns Hall B160
When: 11:30AM-2:30PM.

We will have tours and
demos of the equipment and
facility.

Example

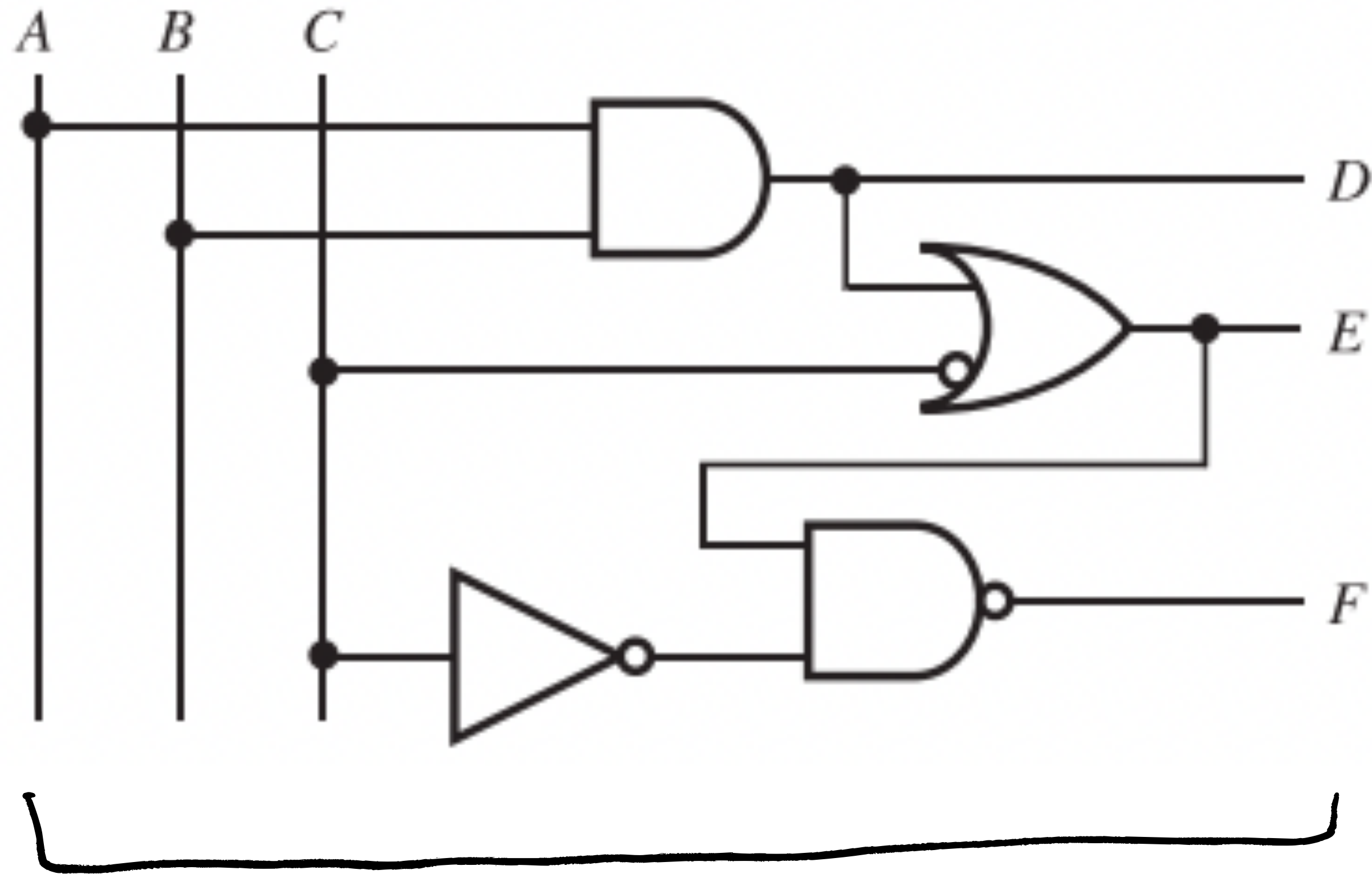

CMOS / transistors


$$D = A \cdot B$$

$$E = D + \bar{C} = (A \cdot B) + \bar{C}$$

$$F = \overline{E \cdot \bar{C}}$$

$$= \overline{[(A \cdot B) + \bar{C}] \cdot \bar{C}}$$

Example

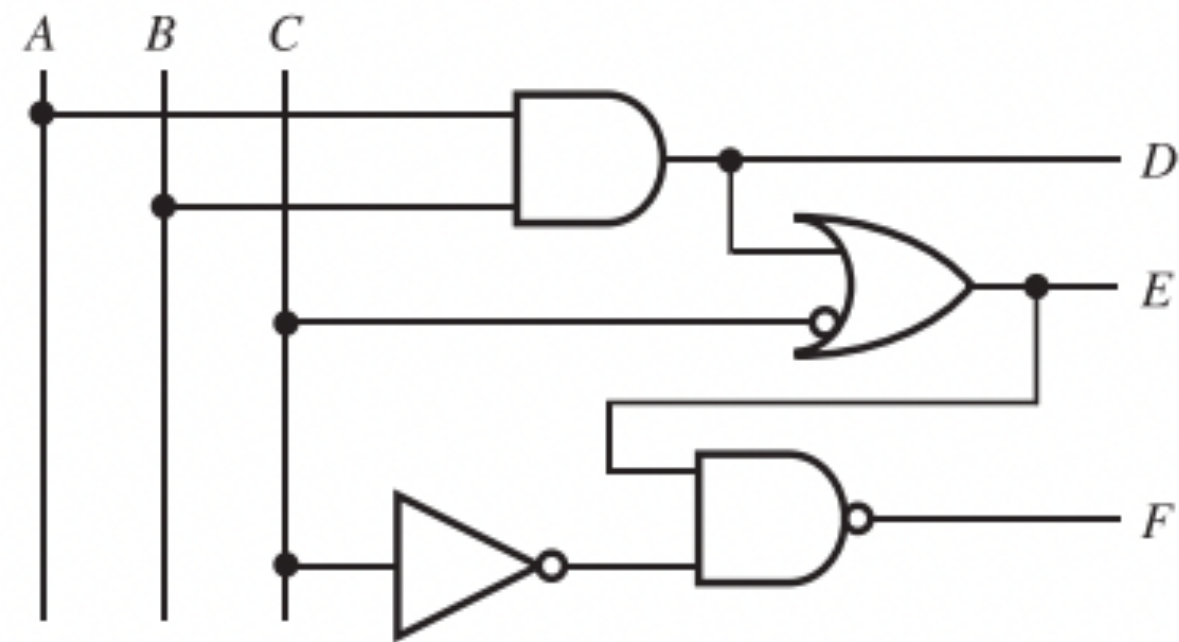

$$D = A \cdot B$$


$$E = D + \bar{C} = (A \cdot B) + \bar{C}$$

$$F = \overline{E \cdot \bar{C}}$$

$$F = \overline{[(A \cdot B) + \bar{C}] \cdot \bar{C}}$$

A	B	C	D	E	F
0	0	0	0	1	0
0	0	1	0	0	1
0	1	0	0	1	0
0	1	1	0	0	1
1	0	0	0	1	0
1	0	1	0	0	1
1	1	0	1	1	0
1	1	1	1	1	1

How to make hardware gates?

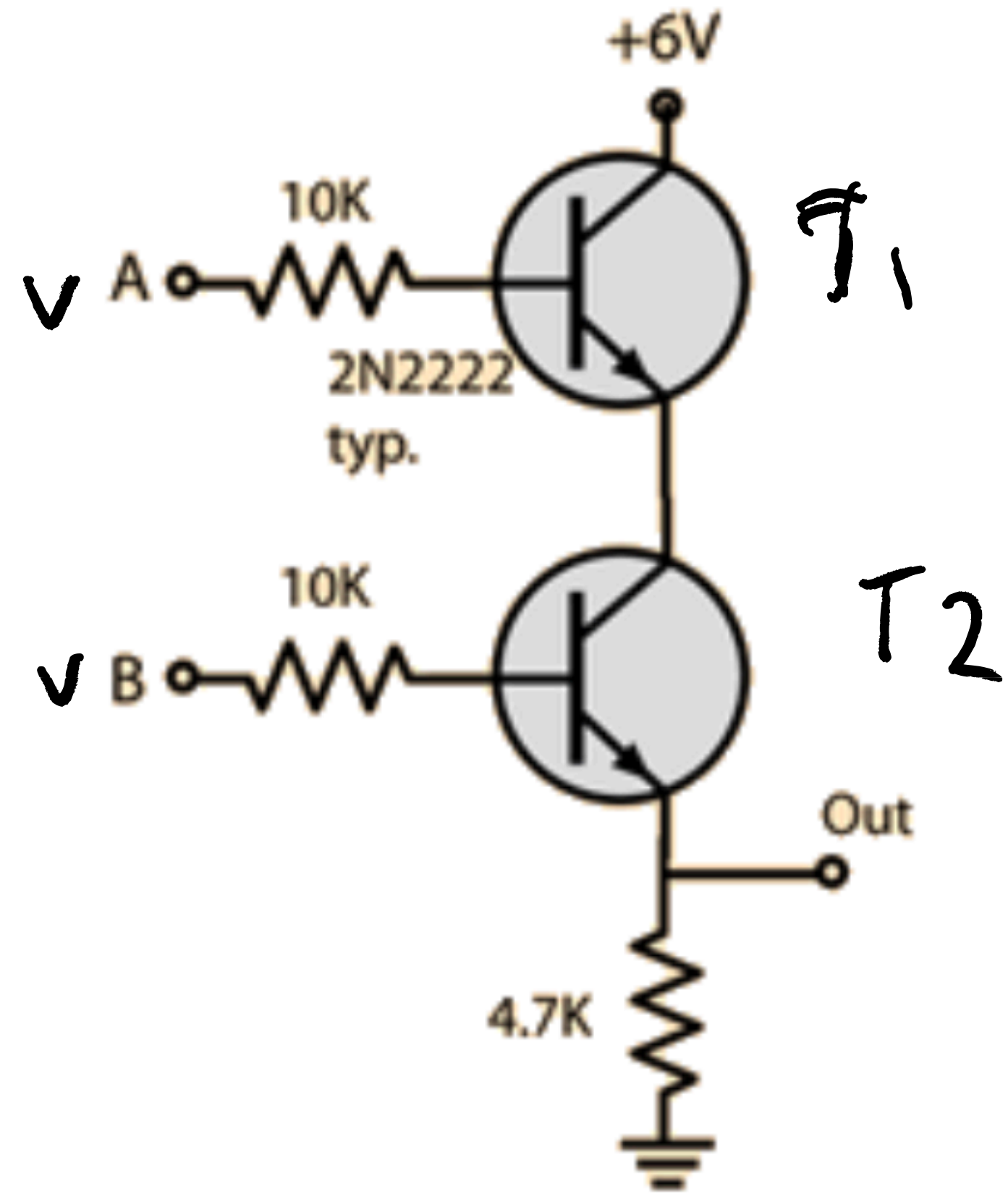


(a) AND gate

$V_A = \text{Low} \Rightarrow T_1 \text{ open}$	
$V_C = \text{Low}$	
<hr/>	
$V_B = \text{Low} \Rightarrow T_2 \text{ open}$	
$V_C = \text{Low}$	
iff $V_A = V_B = \text{High}$	
$V_C = \text{High}$	

V_A	V_B	V_C
0	0	0
1	0	0
0	1	0
1	1	1

How to make hardware gates?



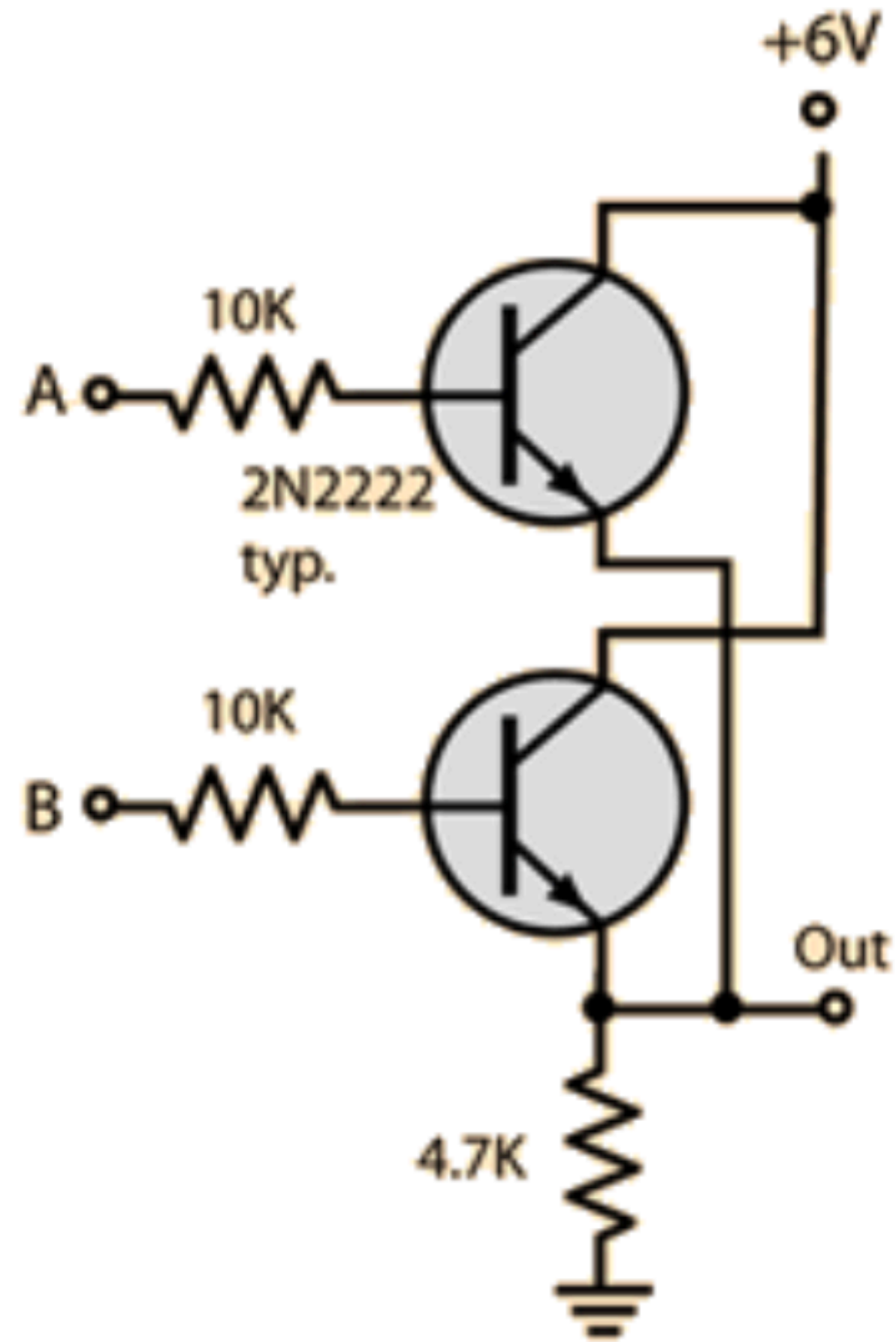


(b) OR gate

$V_A = \text{high}$			
$V_C = \text{high}$			
<hr/>			
$V_B = \text{high}$			
$V_C = \text{high}$			

V_A	V_B	V_C
0	0	0
0	1	1
1	0	1
1	1	1


Timing Diagrams

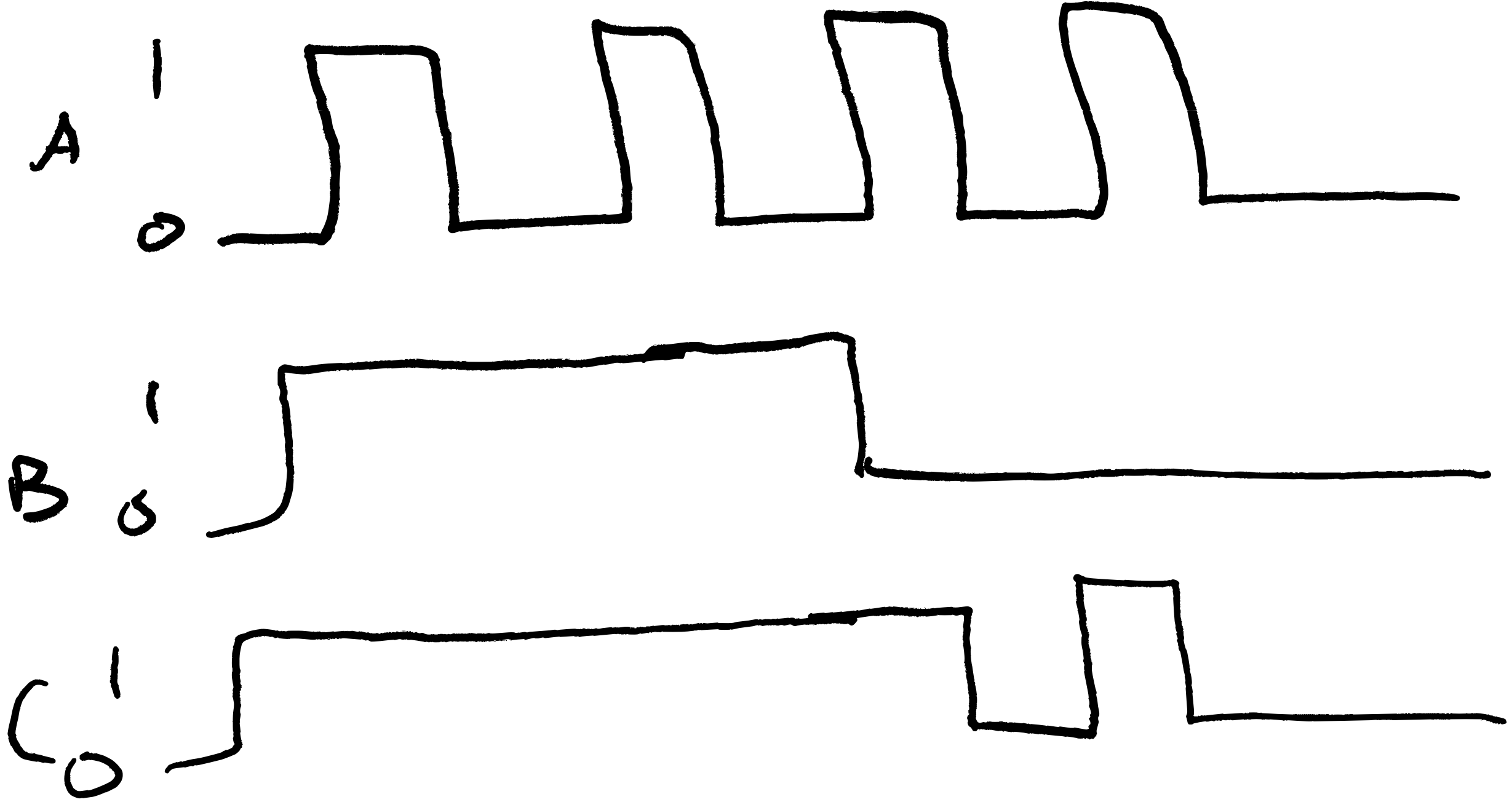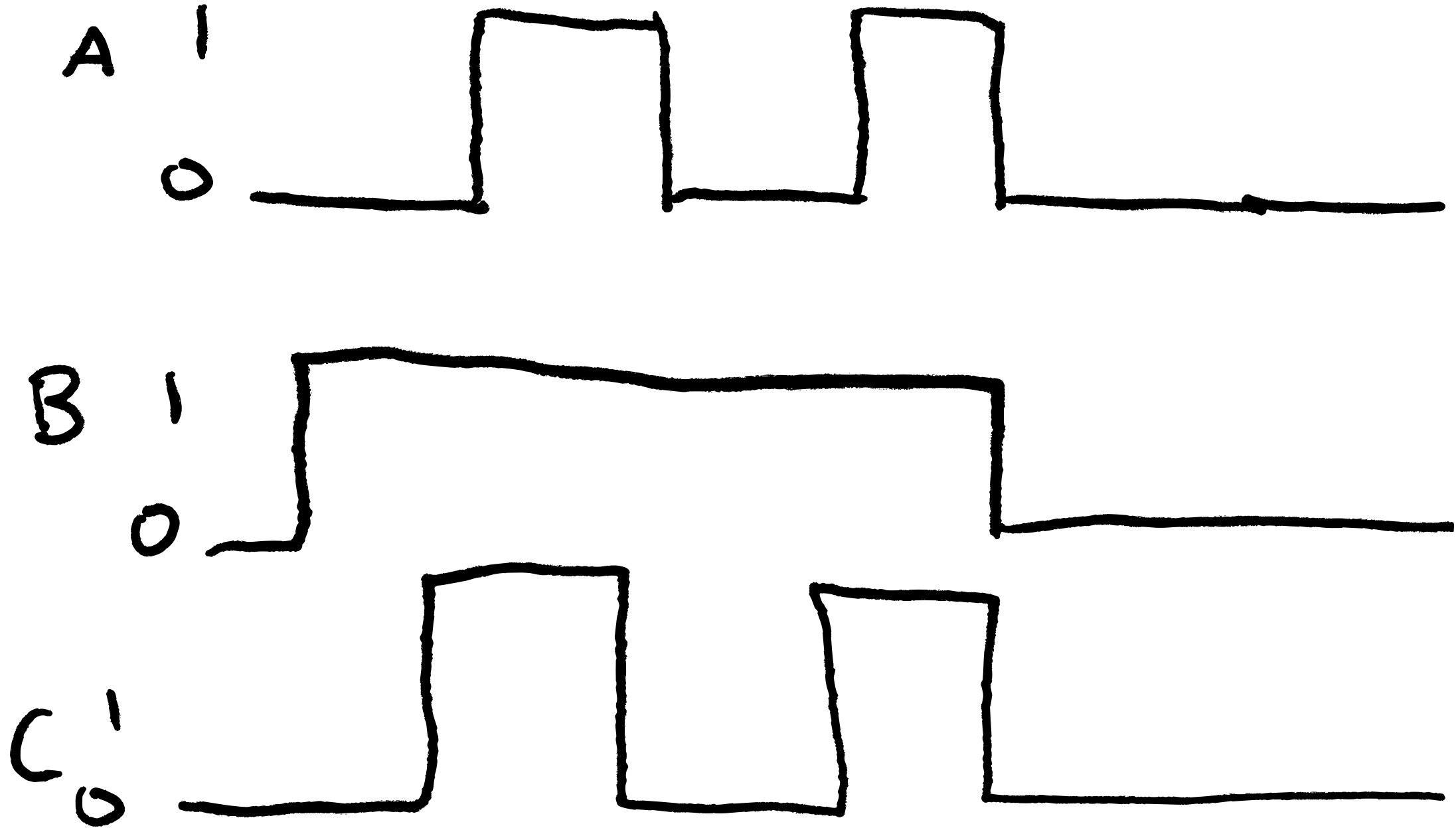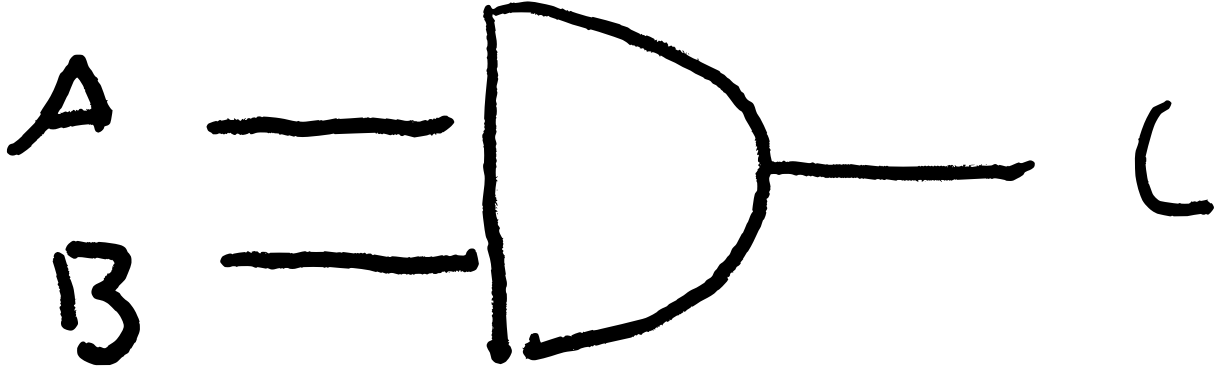

'a' → 52 → 0100,1001

Timing Diagrams

SPI - Serial Peripheral Interface

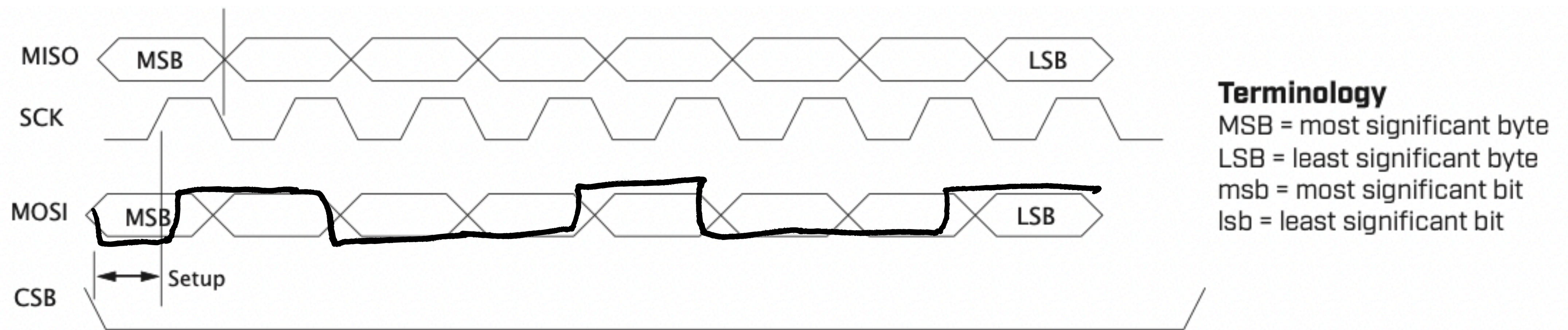

Let's look at real timing diagrams from an encoder with SPI interface

Boolean Algebra

Boolean: binary, usually interpreted as 'TRUE' or 'FALSE'

Algebra: the study of variables & the rules for manipulating these variables in a formula

Boolean Algebra: rules for manipulating binary formulas

Three fundamental logic operators:

AND OR NOT

These can be realized with hardware gates,
or software (logical statements)

Boolean Algebra in Software

Logical Operators

Symbol	Role
&	Find logical AND
	Find logical OR
&&	Find logical AND (with short-circuiting)
	Find logical OR (with short-circuiting)
~	Find logical NOT



$$\underline{A + 0 = A}$$

Fundamental Laws

$A = 0 \text{ or } 1$

	OR	AND	NOT
\rightarrow	$A + 0 = A$	$A \cdot 0 = 0$	
	$A + 1 = 1$	$A \cdot 1 = A$	$\overline{\overline{A}} = A$
	$A + A = A$	$A \cdot A = A$	
	$A + \overline{A} = 1$	$A \cdot \overline{A} = 0$	

Commutative, Associative and Distributive Laws

Commutative

$$A + B = B + A$$

$$A \cdot B = B \cdot A$$

Associative

$$(A + B) + C = A + (B + C)$$

$$(A \cdot B) \cdot C = A \cdot (B \cdot C)$$

Distributive

$$\begin{aligned} A \cdot (B + C) \\ = (A \cdot B) + (A \cdot C) \end{aligned}$$

$$\begin{aligned} A + (B \cdot C) \\ = \end{aligned}$$

$$(A + B) \cdot (A + C)$$

De Morgan's Laws

Can convert ANDs to ORs or vice versa!

$$\overline{A + B + C \dots} = \bar{A} \cdot \bar{B} \cdot \bar{C} \dots$$

$$\overline{A \cdot B \cdot C \dots} = \bar{A} + \bar{B} + \bar{C} \dots$$

$$A + B + C \dots = \overline{\bar{A} \cdot \bar{B} \cdot \bar{C} \dots}$$

$$A \cdot B \cdot C \dots = \overline{\bar{A} + \bar{B} + \bar{C} \dots}$$

Other useful identities 6.17 - 6.24

Example

$$(\cancel{A + \bar{A}}) \cdot (A + B)$$

Prove: $A + (\bar{A} \cdot B) = A + B$

Most straight forward way is to use truth table

A	\bar{A}	B	$\bar{A} \cdot B$	$A + (\bar{A} \cdot B)$	$A + B$
1	0	0	0	1	1
1	0	1	0	1	1
0	1	0	0	0	0
0	1	1	1	1	1

Example

Prove: $A + (\bar{A} \cdot B) = A + B$

Most straight forward way: use a truth table!

A	\bar{A}	B	$\bar{A} \cdot B$	$A + (\bar{A} \cdot B)$	$A + B$
-----	-----------	-----	-------------------	-------------------------	---------

Example: Simplifying a Boolean Expression

Use laws to collect like-terms — just like regular algebra!

$$X = (A \cdot B \cdot C) + (B \cdot C) + (\bar{A} \cdot B)$$

7 operations

→ associative

$$X = A \cdot (B \cdot C) + (B \cdot C) + (\bar{A} \cdot B)$$

→ distributive

$$X = (B \cdot C) \cdot (A + 1) + (\bar{A} \cdot B)$$

→ Fundamental laws $A + 1 = 1$

$$X = (B \cdot C) + (\bar{A} \cdot B) \rightarrow$$

$$X = B \cdot (C + \bar{A})$$

3 operations

Example: Designing a logic network

Let's design a home alarm system using only logic gates

What we want:

1. Alarm to sound if window or doors are disturbed
Mode-1 (sleeping)
2. Alarm to sound if " " " " or motion is detected in house Mode-2 (vacation)
3. A disabled state where alarm is off mode-3 (off)

Assumptions:

That sensors are binary (motion - 1, no motion - 0)
door/window is disturbed - 1, no disturbance 0

Example: Designing a logic network

Let's define our Boolean variables:

- A : state of door/windows
- B : state of motion detector
- Y : output to sound alarm (1 - alarm on, 0 - no sound)
- CD : 2-bit code

$$CD = \begin{cases} 01 & \text{Mode 1} \\ 10 & \text{Mode 2} \\ 00 & \text{mode 3} \end{cases}$$

Example: Designing a logic network

- A : state of the door and window sensors
- B : state of the motion detector
- Y : output used to sound the alarm
- CD : 2-bit code set by the user to select the operating state defined by

$$CD = \begin{cases} 01 & \text{operating state 1} \\ 10 & \text{operating state 2} \\ 00 & \text{operating state 3} \end{cases}$$

Quasi-logic Statement

Activate alarm ($Y=1$) if $A=1$ and $CD=01$ or

$A=1$ or $B=1$ and $CD=10$

Example: Designing a logic network

Translate Quasi-logic Statement into Boolean Expression

Activate alarm ($Y=1$) if $A=1$ and $CD = 01$ or activate the alarm if $A = 1$ or $B = 1$ and $CD = 10$

$$Y = A \cdot (\bar{C} \cdot D) + (A + B) \cdot (C \cdot \bar{D})$$

simplify!

Example: Designing a logic network

Simplify $Y = A \cdot (\bar{C} \cdot D) + (A + B) \cdot (C \cdot \bar{D})$

C	D	$(\bar{C} \cdot D)$	$(C \cdot \bar{D})$
0	0	0	0
1	0	0	1
0	1	1	0

$$(\bar{C} \cdot D) = D \text{ and } (C \cdot \bar{D}) = C$$

$$Y = (A \cdot D) + (A + B) \cdot C$$

Example: Designing a logic network

Convert to single gate: $Y = (A \cdot D) + (A + B) \cdot C$

Example: Designing a logic network

Now we can draw logic circuit:

$$Y = \overline{\overline{A \cdot D} \cdot (\overline{A \cdot B}) \cdot C}$$