

Last time:



> Motors

Today:

> Op Amps and Analog Signal Processing

Power Transistors Design and Control

Unipolar (one power supply)

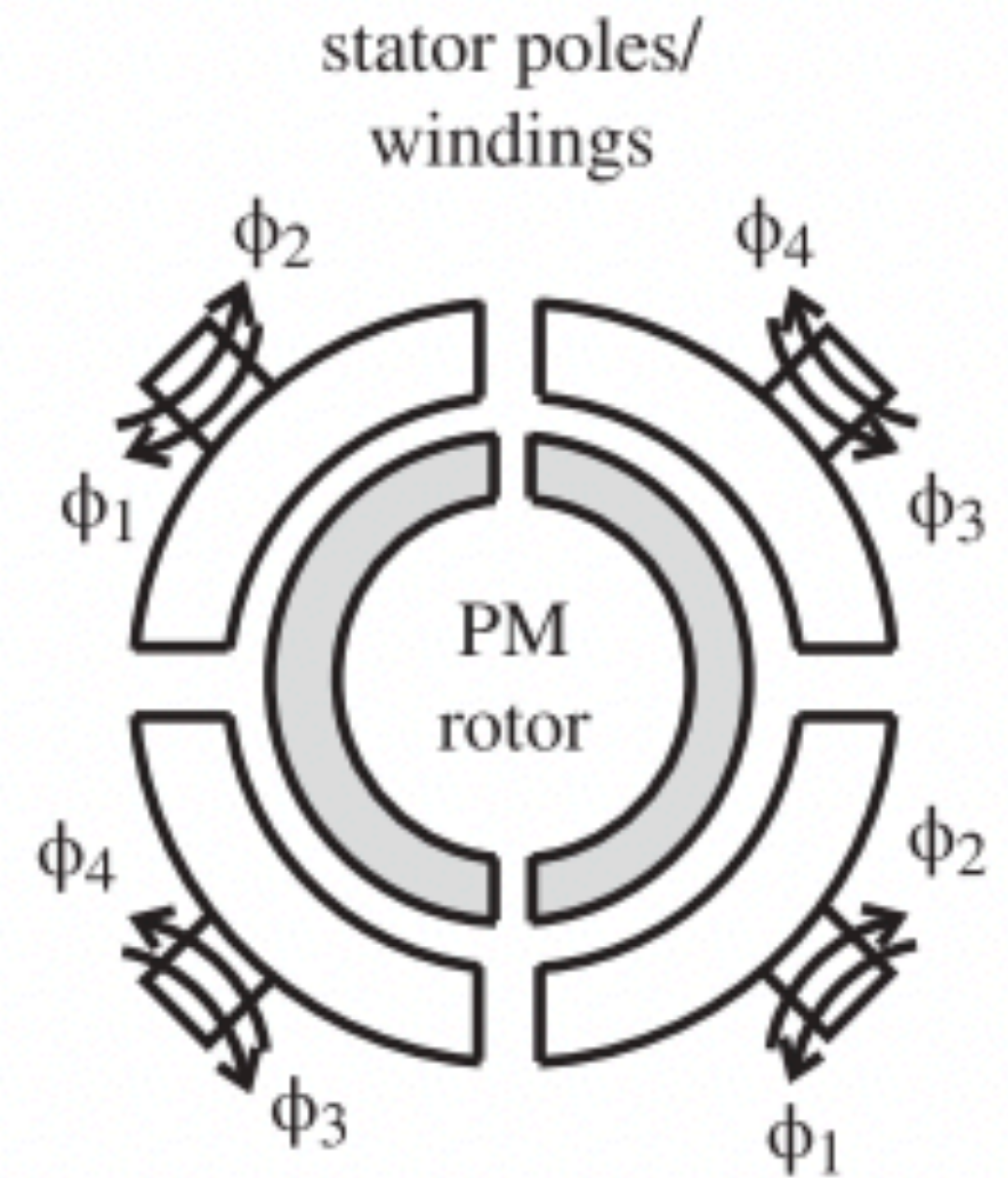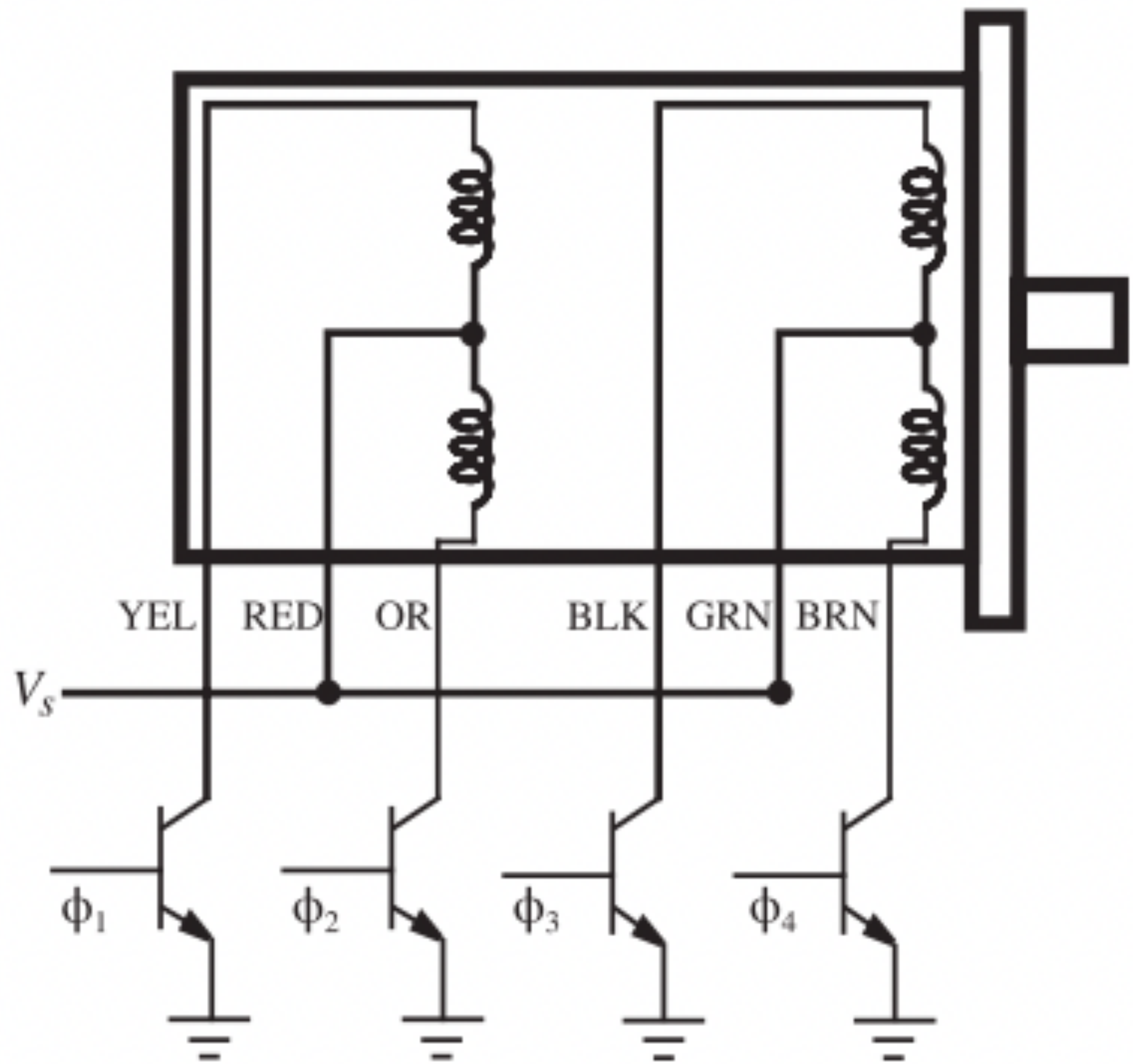

step 1
(ϕ_1, ϕ_3 : ON)

step 1.5
(ϕ_1 : ON)

step 2
(ϕ_1, ϕ_4 : ON)

Step	ϕ_1	ϕ_2	ϕ_3	ϕ_4
1	ON	OFF	ON	OFF
2	ON	OFF	OFF	ON
3	OFF	ON	OFF	ON
4	OFF	ON	ON	OFF

Power Transistors Design and Control

Bipolar (switchable power supply)


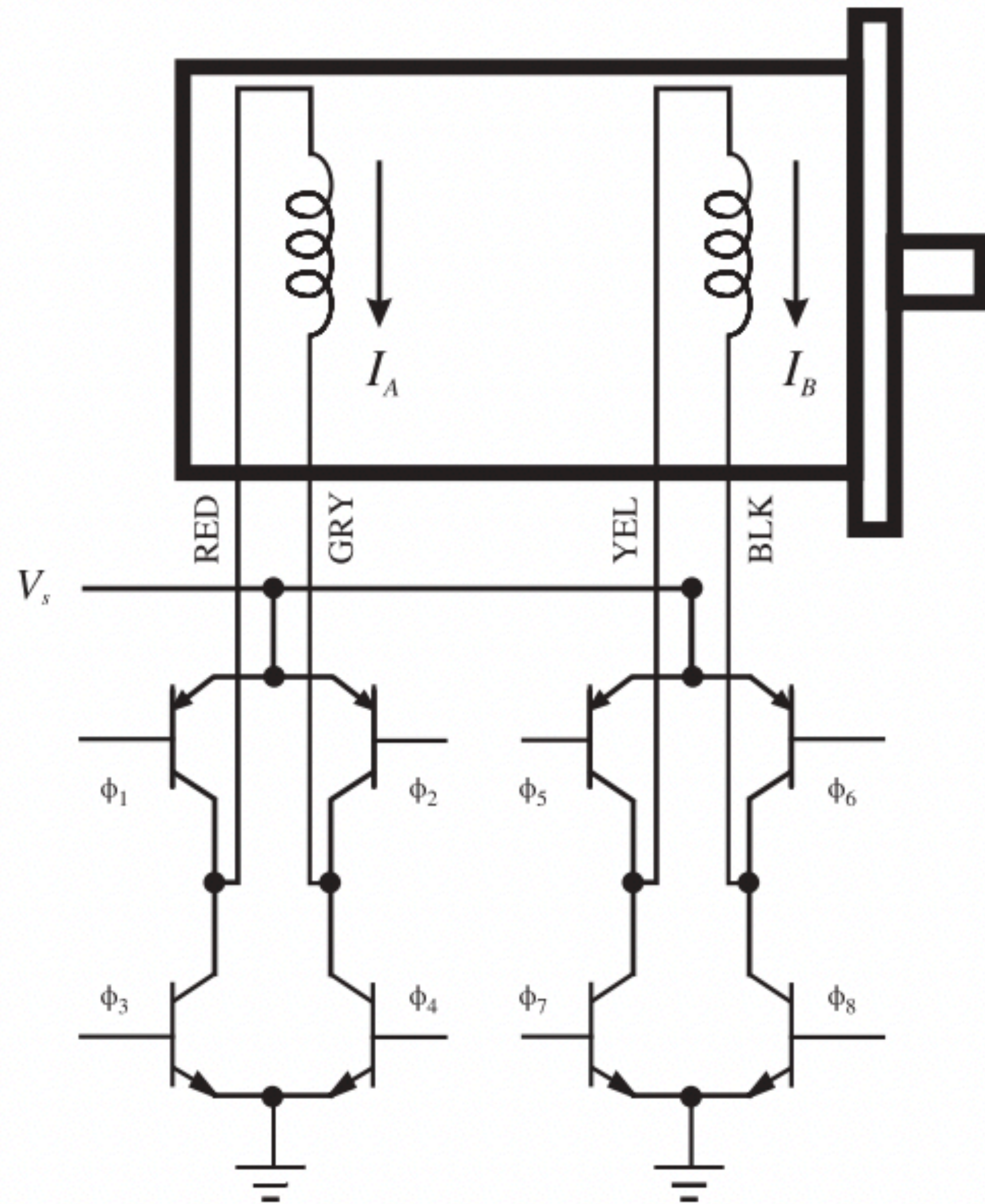


Table 10.3 Bipolar full-step phase sequence

Step	ϕ_1 and ϕ_4	ϕ_2 and ϕ_3	ϕ_5 and ϕ_8	ϕ_6 and ϕ_7
CW ↓	ON	OFF	ON	OFF
2	ON	OFF	OFF	ON
CCW ↑	OFF	ON	OFF	ON
4	OFF	ON	ON	OFF

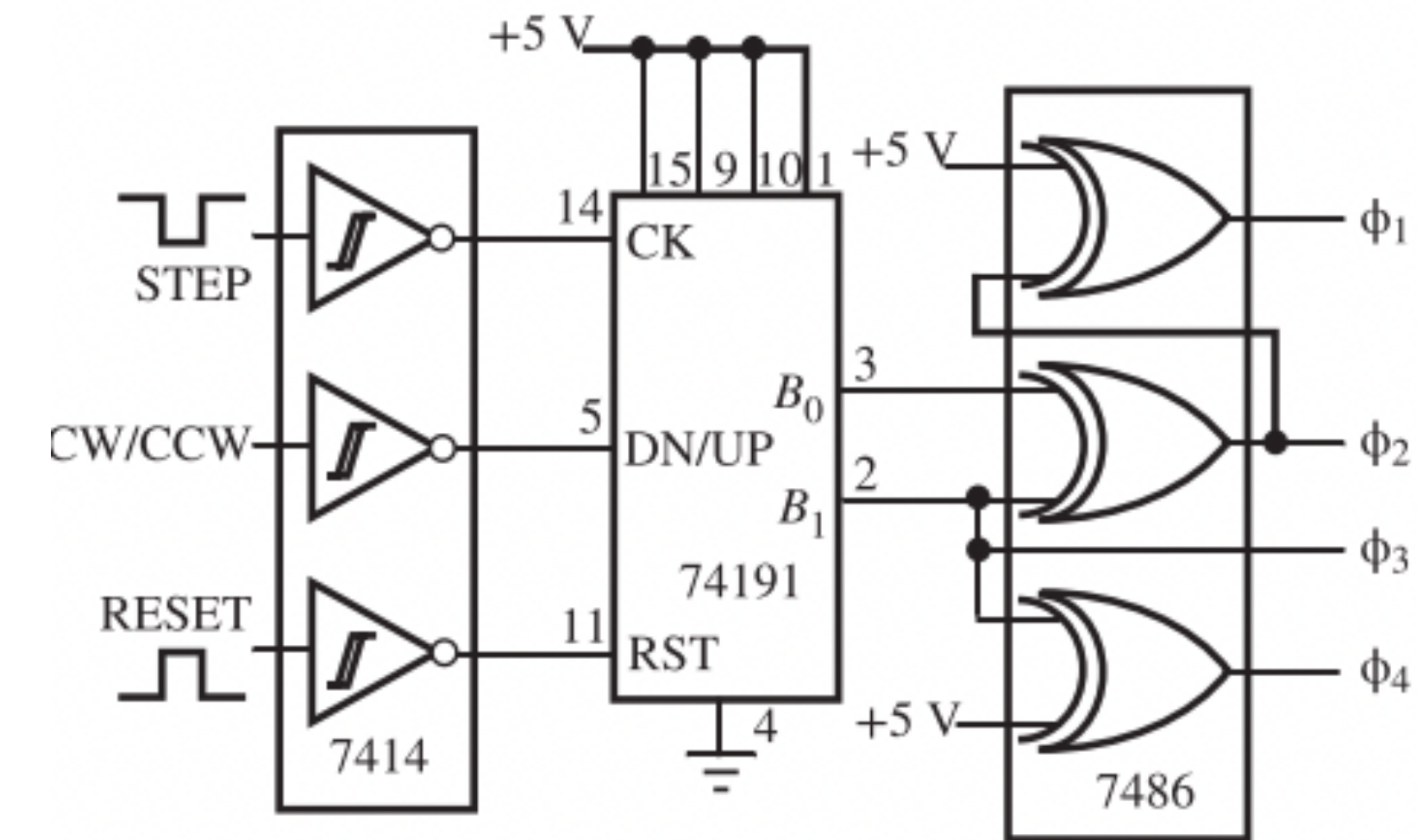For both bipolar and unipolar, there are drive circuits to take care of phasing




Analog Signal Processing Overview

Problem: after sensor outputs & actuator inputs are analog signals that need some form of conditioning (modification).

↳ signal processing.

Conditioning?


- too small
- noisy
- DC offset

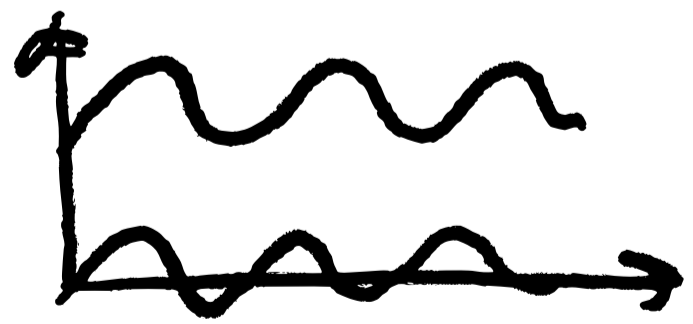

Forms of signal processing

- amplification
- filter (low pass noise)
- differentiation] analog computer
- integration]
- addition
- subtraction

Amplifier Model

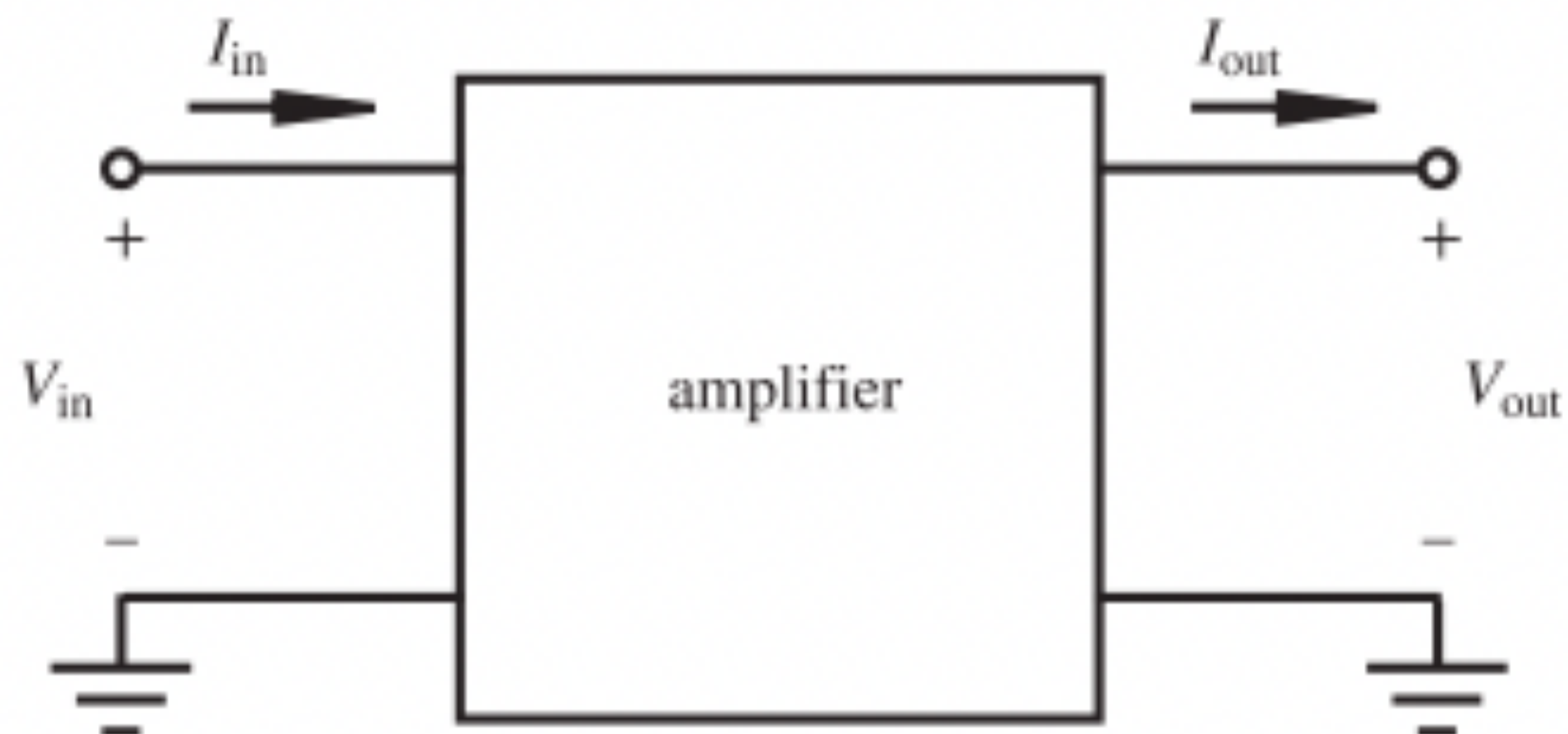

$$V_{out} = A_v V_{in}$$

Ideal amplifier

- linearity
- large bandwidth
- input/output impedance


Characteristics are important!

$Z \rightarrow$ generalization of Ohm's Law. $V = IR \rightarrow R = \frac{V}{I}$


$$Z_{in} = \frac{V_{in}}{I_{in}} \quad \uparrow$$

$$Z_{out} = \frac{V_{out}}{I_{out}} \quad \downarrow$$

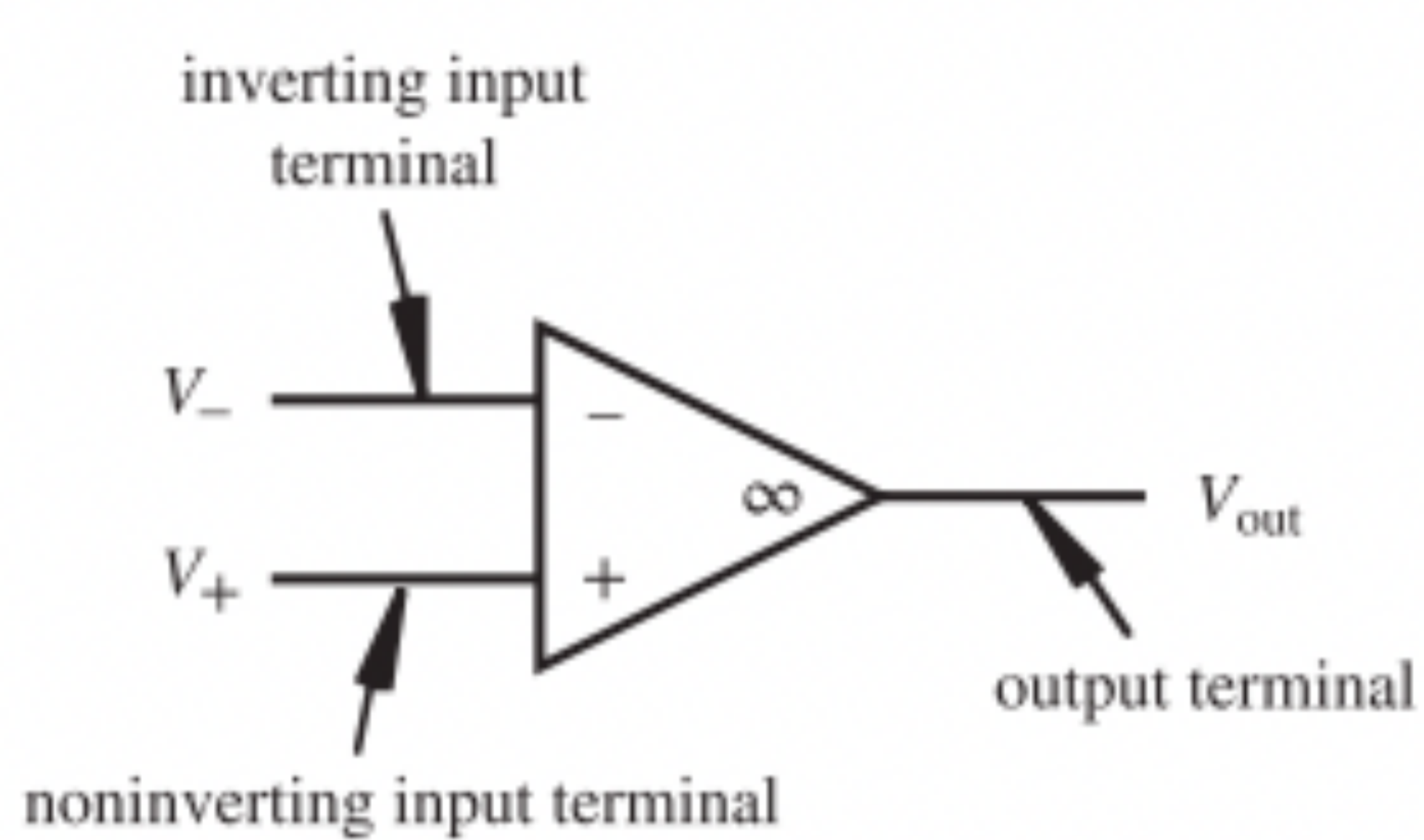Operational Amplifier : most important hardware component for analog signal processing



Open-loop configuration

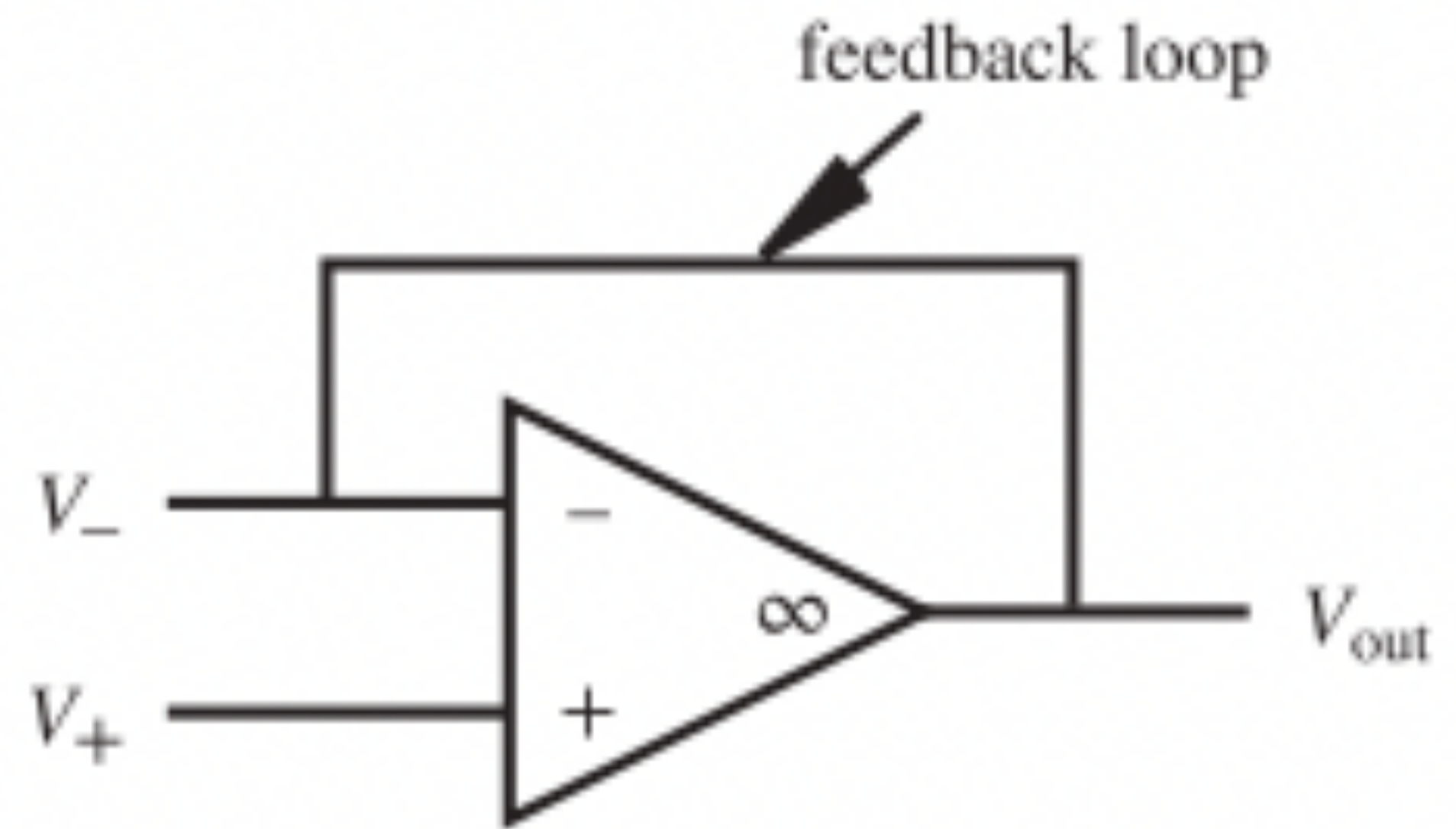


closed form almost always


How are they made?
↓

OpAmps made with transistors!

741 op amp

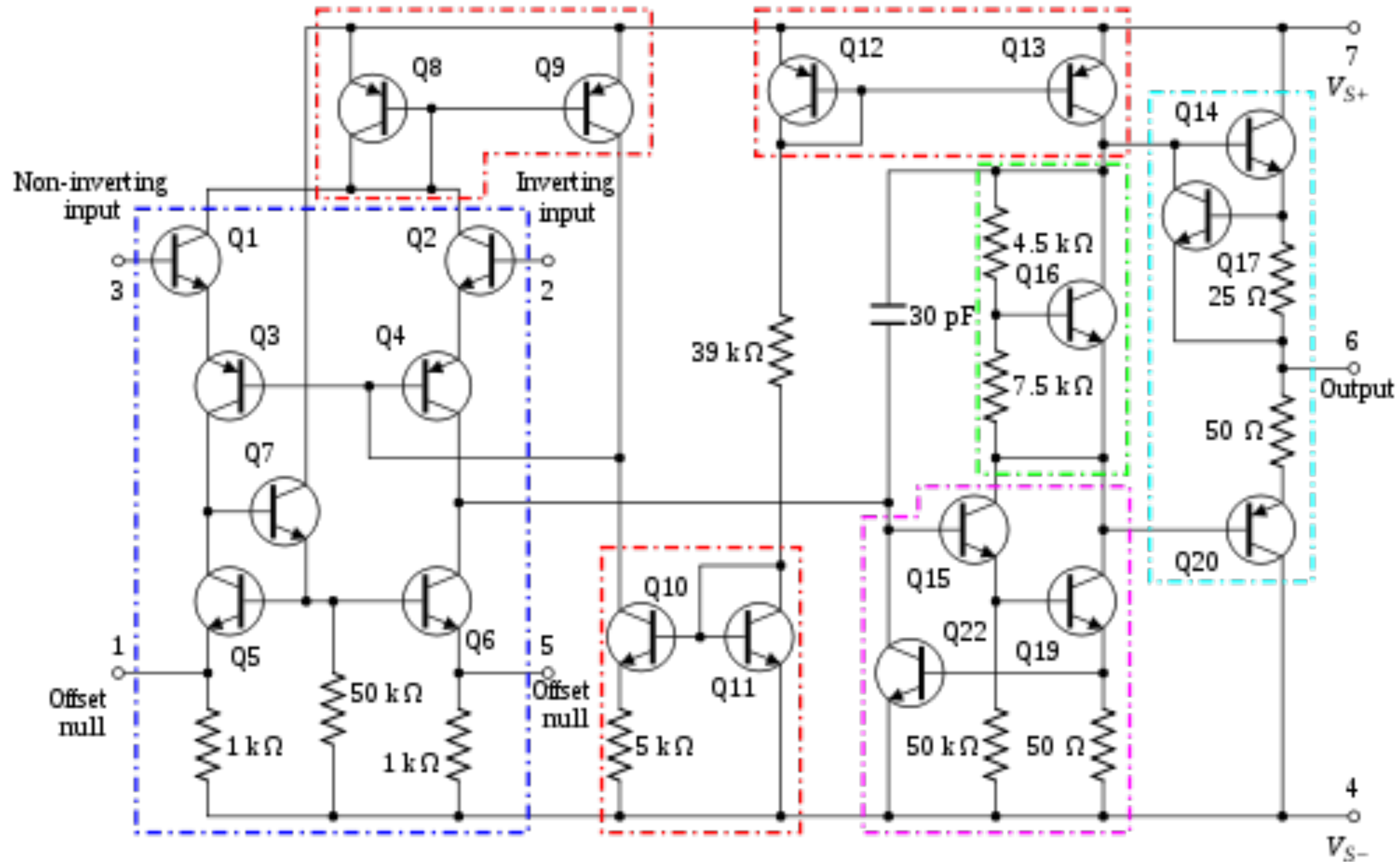

Ideal OpAmp Assumptions

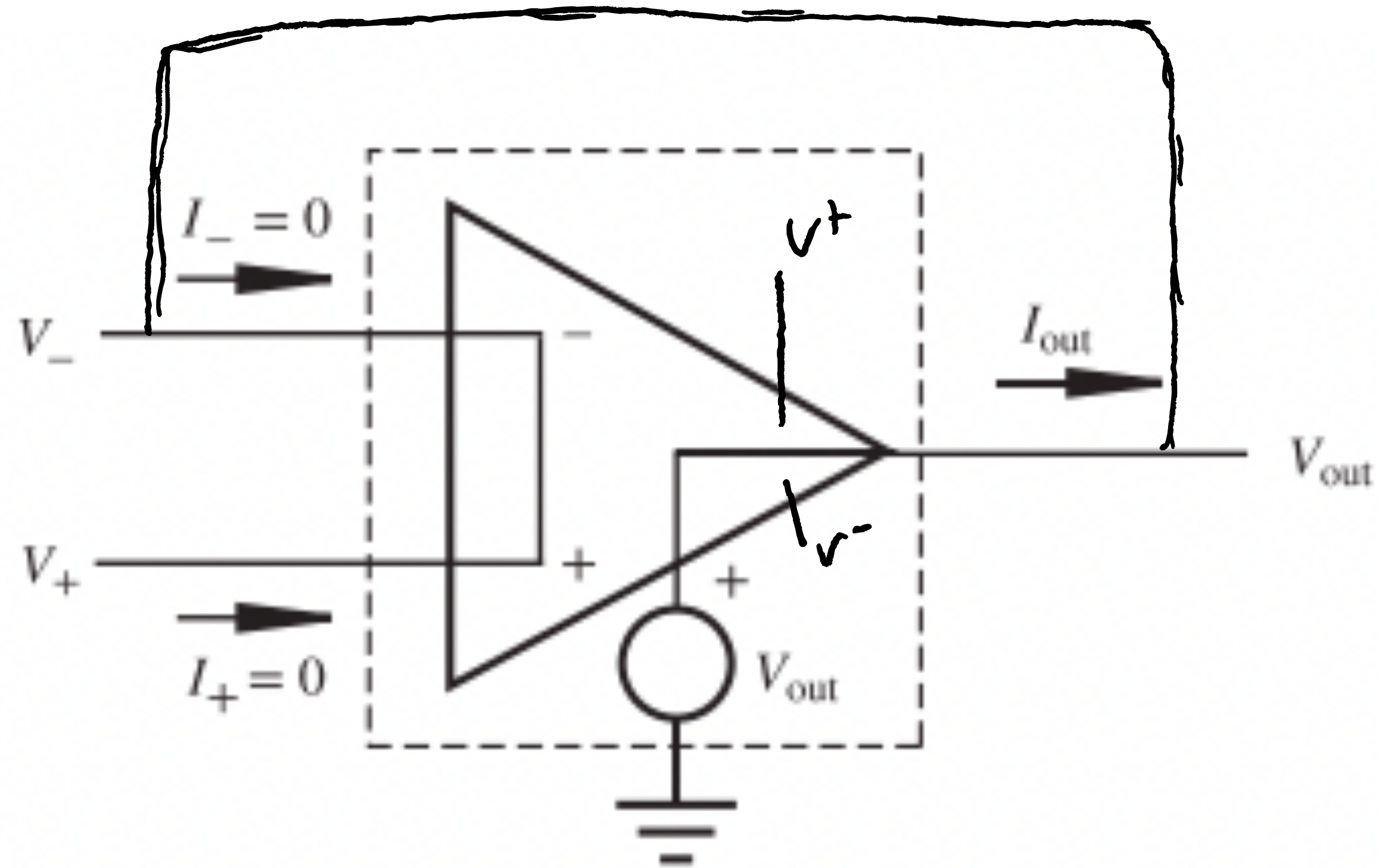

$$V_{out} = A_{OL} (V_+ - V_-)$$

↑
 ∞

┌
open loop gain

① Infinite impedance @ both inputs


$$\underline{I_- = I_+ = 0}$$

② Infinite gain


$$V_+ = V_-$$

③ output impedance is zero:

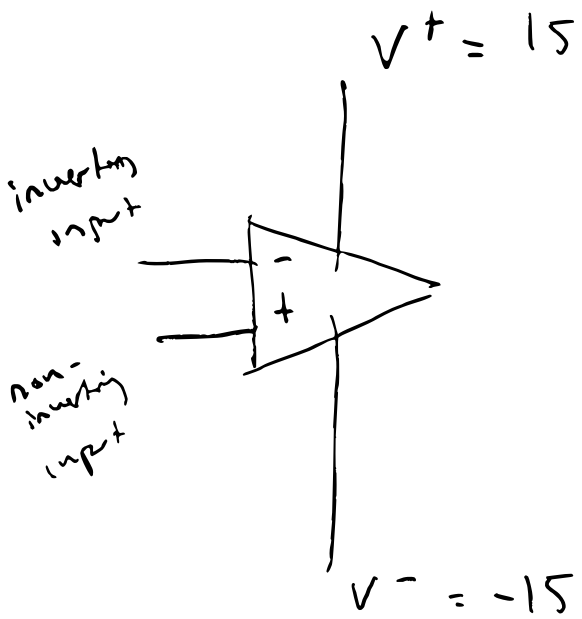$\frac{V_{out}}{I_{out}}$ doesn't depend on



Example: Inverting Amplifier

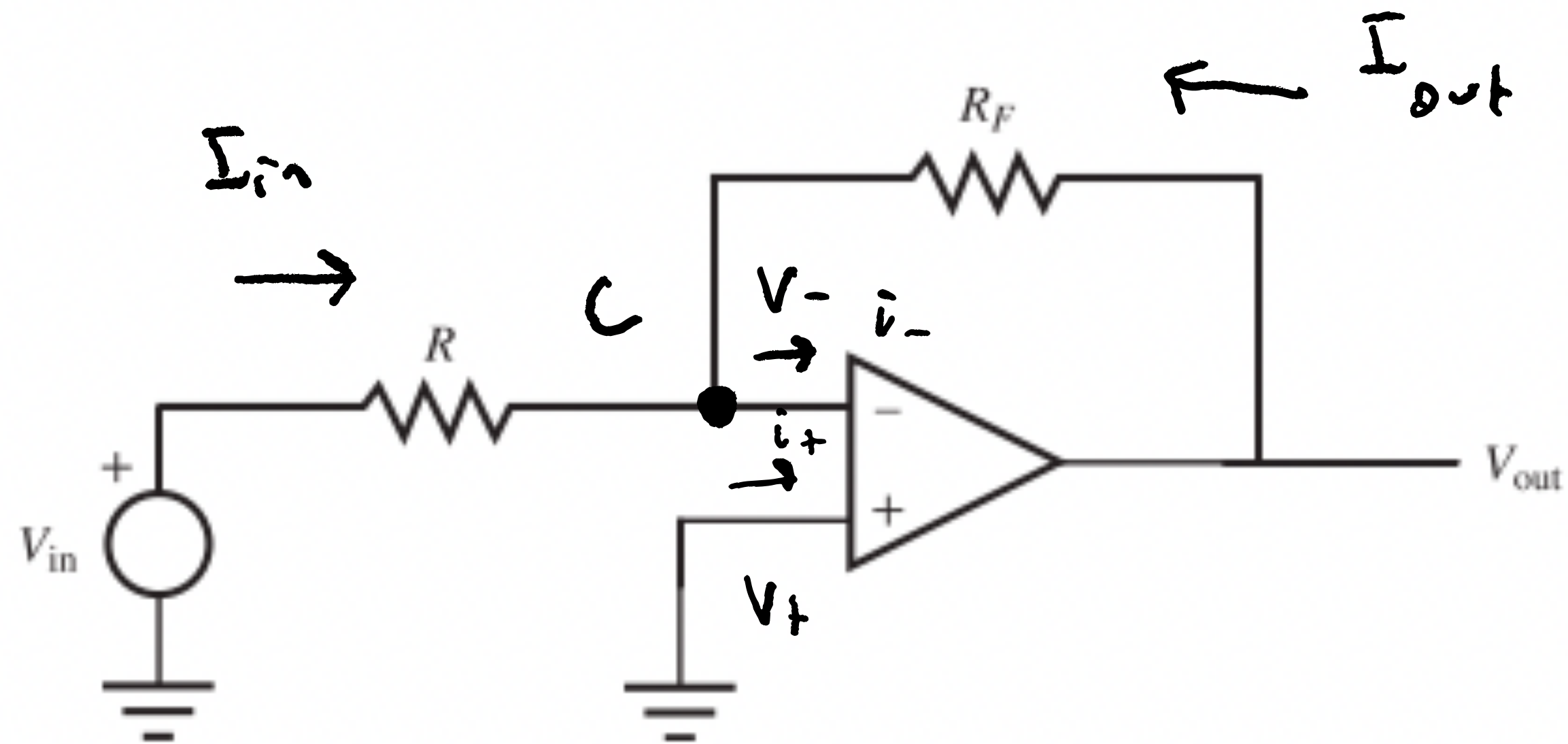

$$V_- = V_+ = 0$$

$$i_- = i_+ = 0$$

$$\begin{array}{l} V = IR \\ I = \frac{V}{R} \end{array}$$

KCL @ Node C



$$i_{in} = -I_{out}$$

$$V_C = V_- = 0$$

$$\frac{V_{in}}{R} = -\frac{V_{out}}{R_f}$$


$$\frac{V_{out}}{V_{in}} = -\frac{R_f}{R}$$

Example: Inverting Amplifier

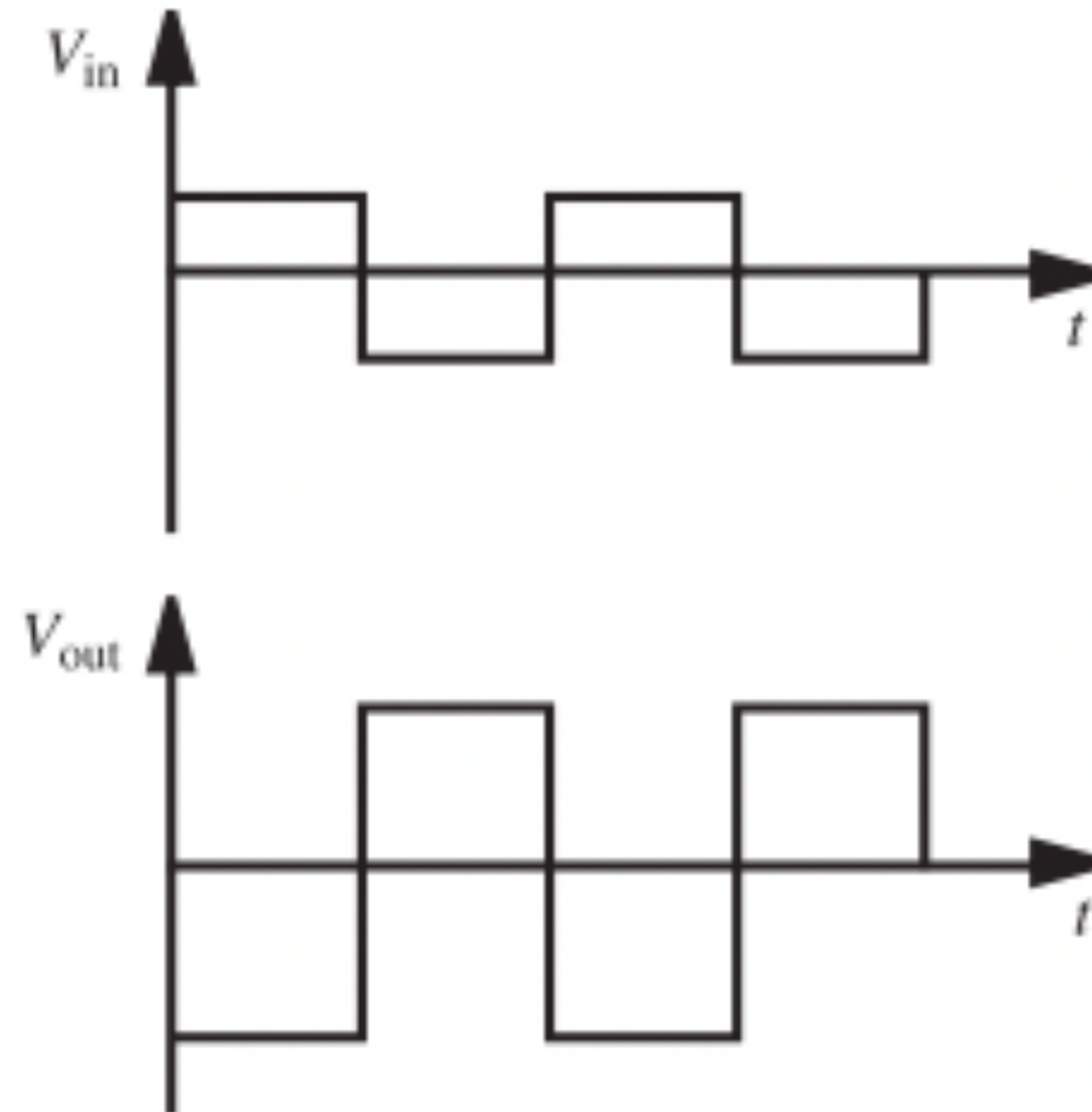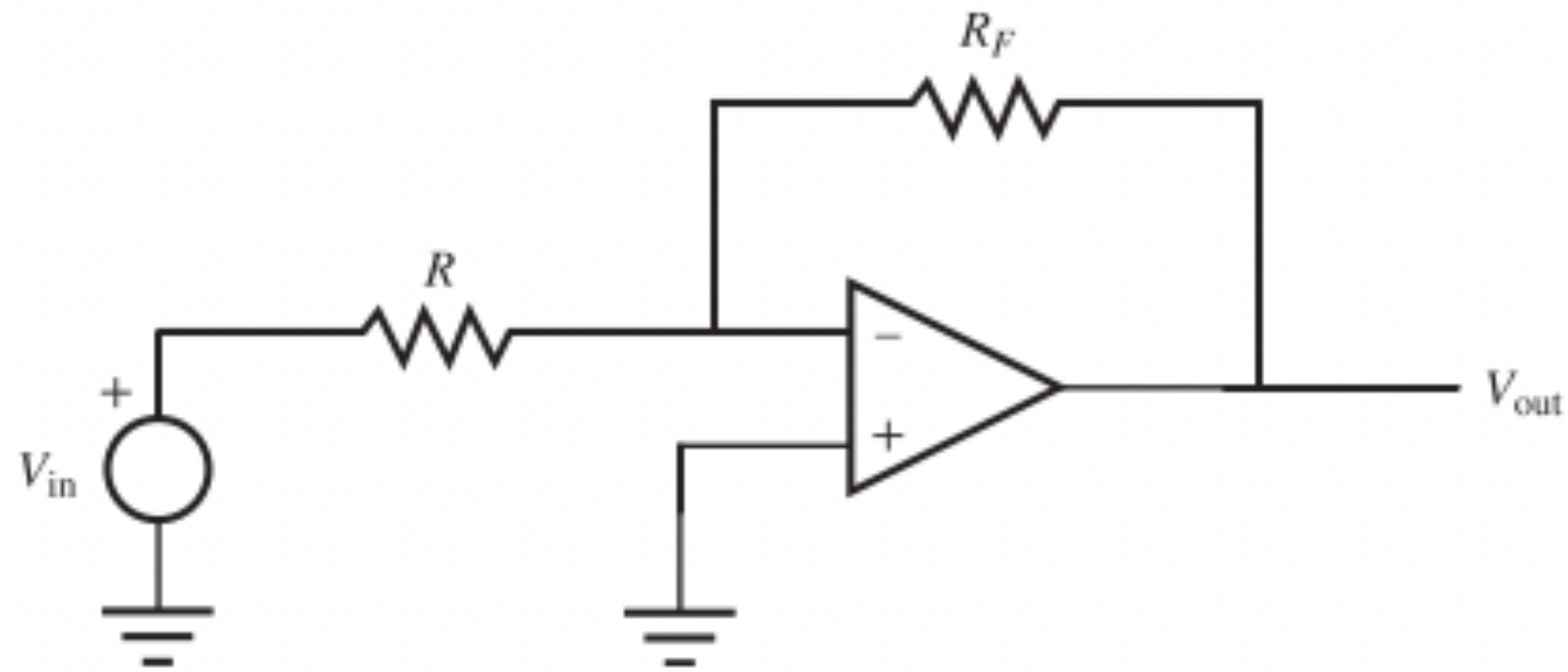


Inverts and scales

Example: Inverting Amplifier

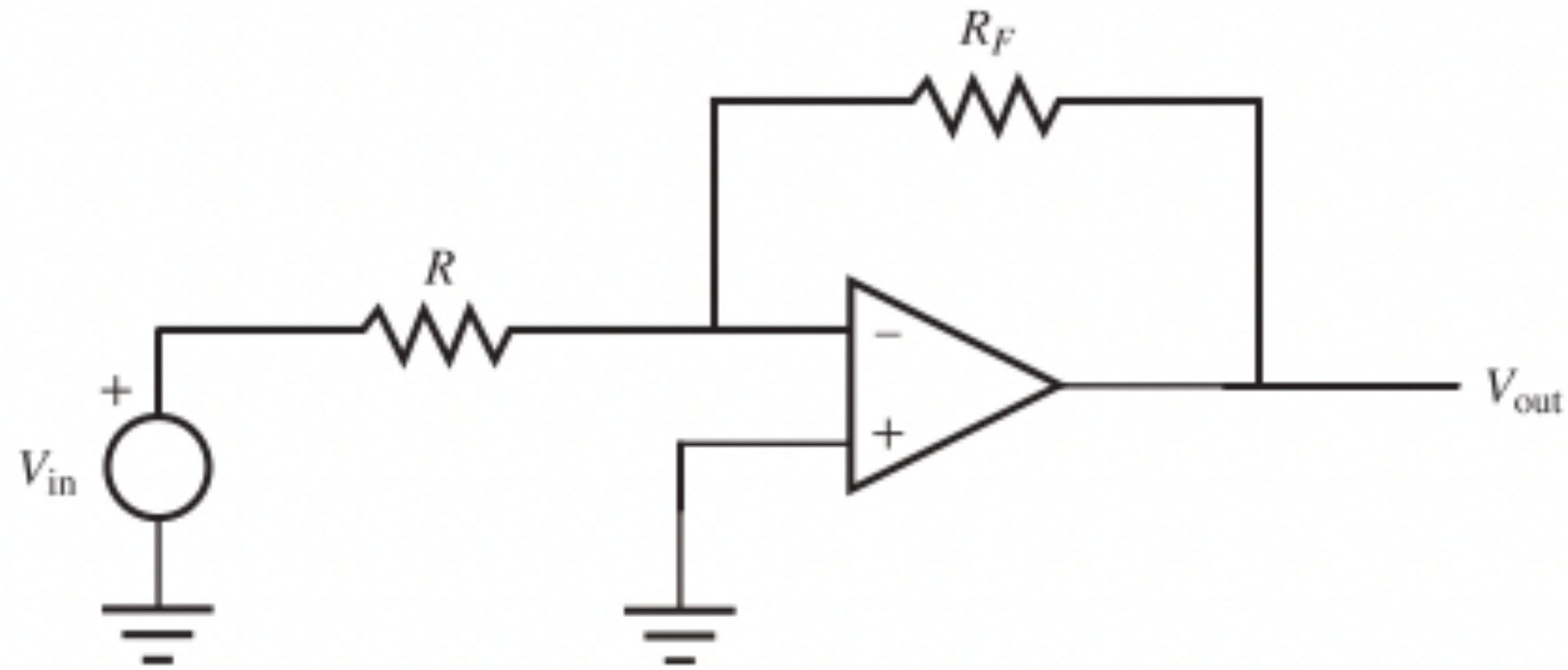


=

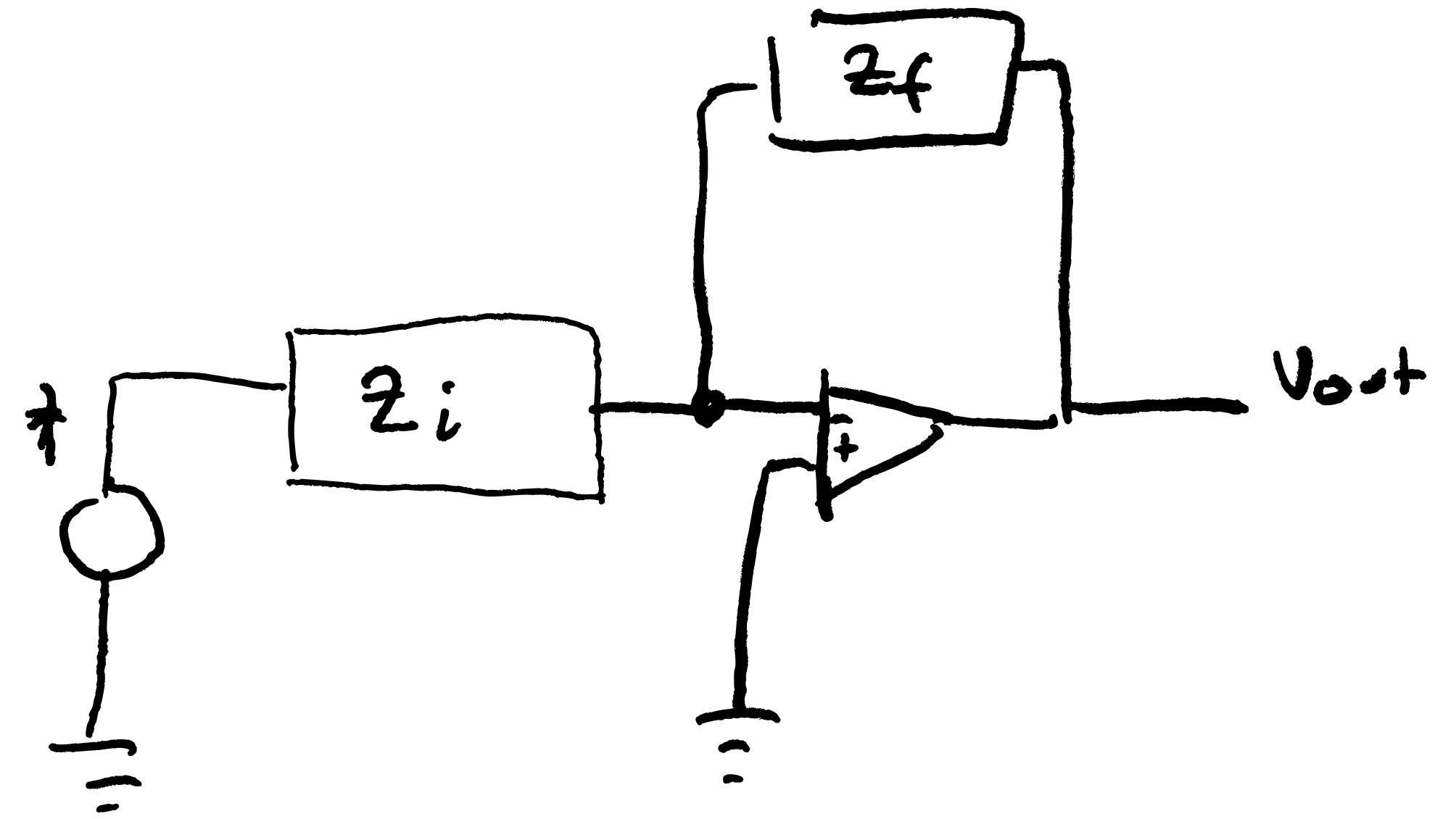

$$\frac{V_{out}}{V_{in}} = - \frac{Z_f}{Z_i}$$

Example: Non Inverting Amplifier

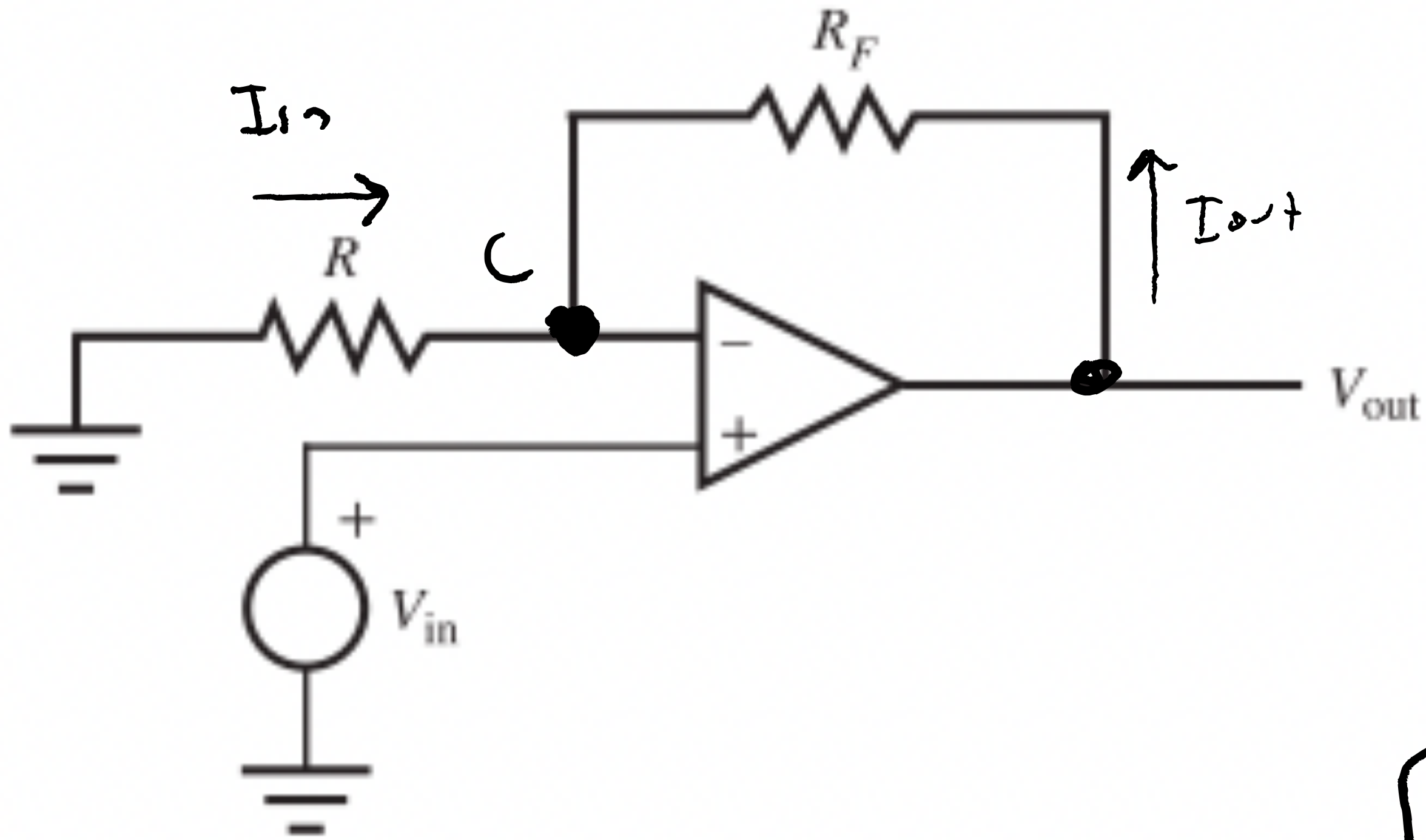

$$\begin{cases} I_- = I_+ = 0 \\ V_- = V_+ = V_{in} \end{cases}$$

KCL @ Node c:

$$\rightarrow I_{in} = -I_{out}$$



$$\begin{cases} I_{in} = -\frac{V_{in}}{R} \\ I_{out} = \frac{V_{out} - V_{in}}{R_f} \end{cases}$$

$$-\frac{V_{in}}{R} = -\frac{(V_{out} - V_{in})}{R_f}$$




$$\boxed{\frac{V_{out}}{V_{in}} = \left(1 + \frac{R_f}{R}\right)}$$

Example: Non Inverting Amplifier

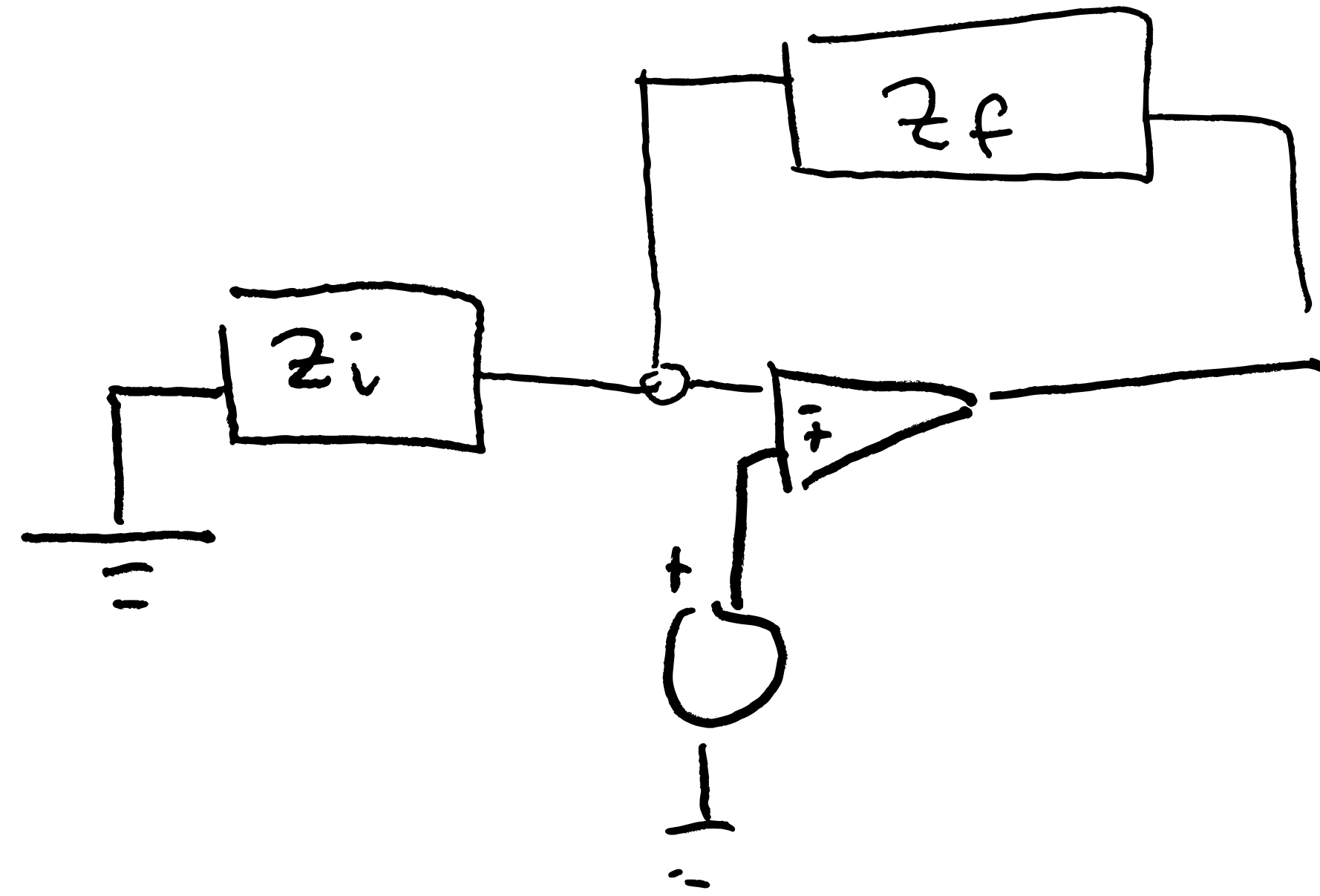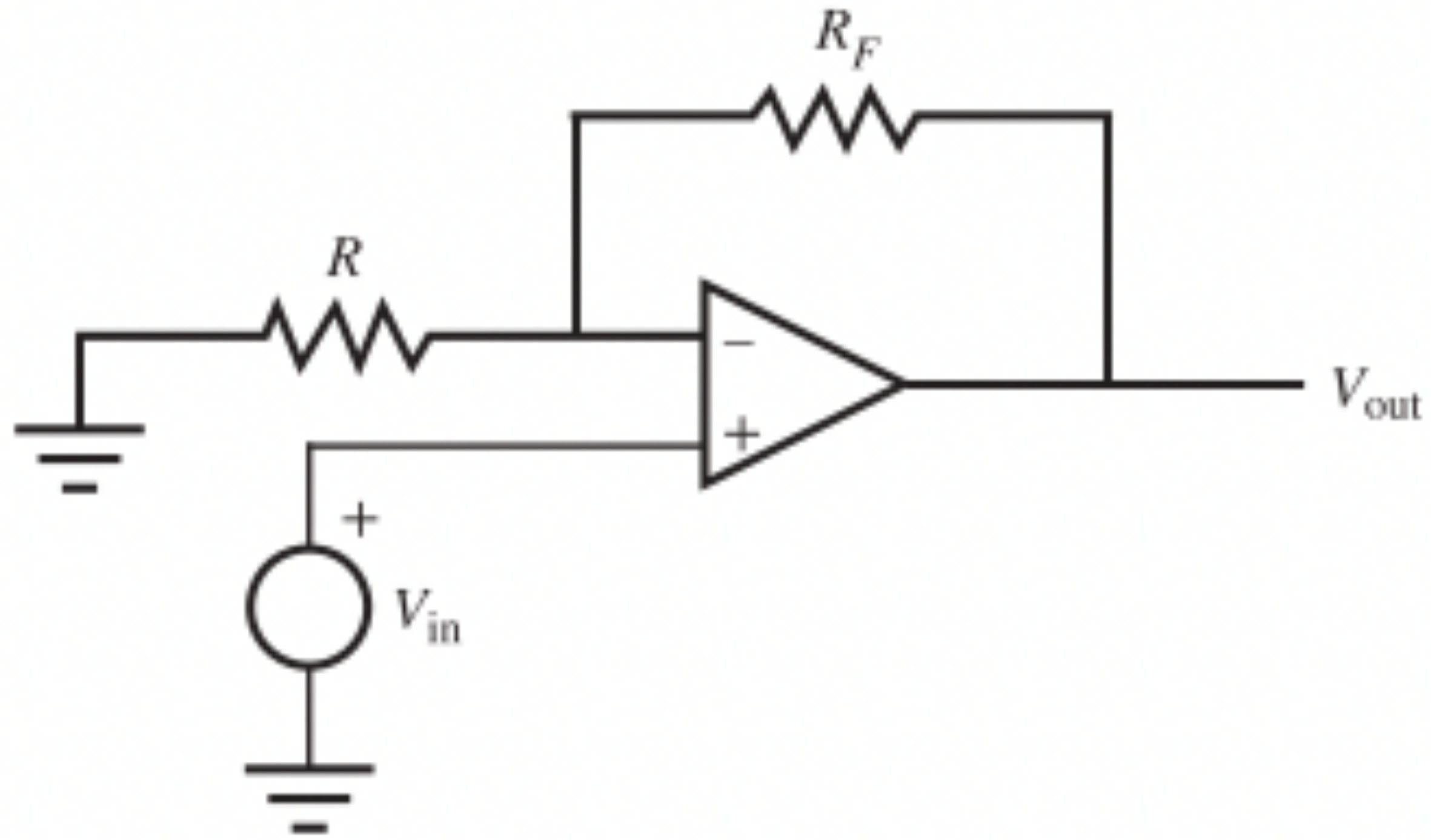


$$\frac{V_{out}}{V_{in}} = \left(1 + \frac{Z_f}{Z_i} \right)$$

Example: Buffer or Voltage Follower



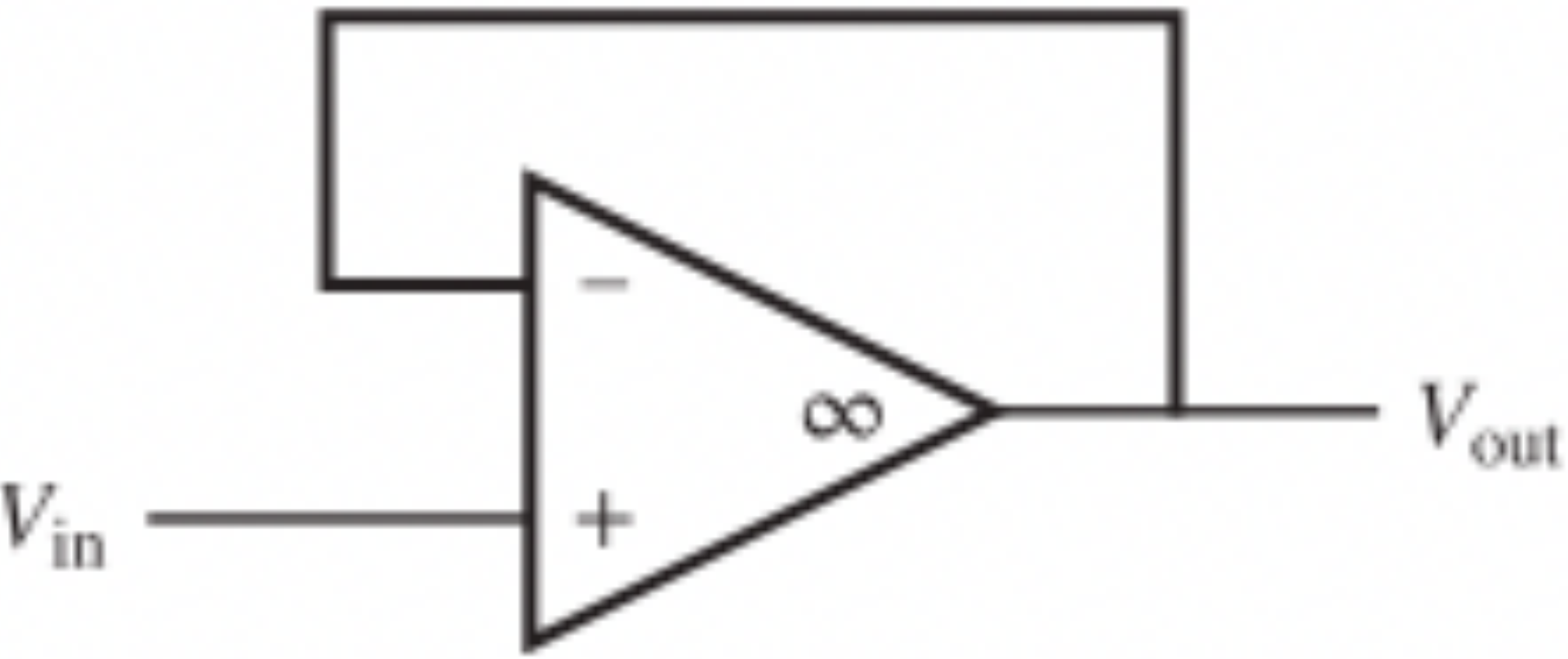


$$\frac{V_{out}}{V_{in}} = \left(1 + \frac{R_f}{R} \right)^{AO} = 1$$

Example: Buffer or Voltage Follower

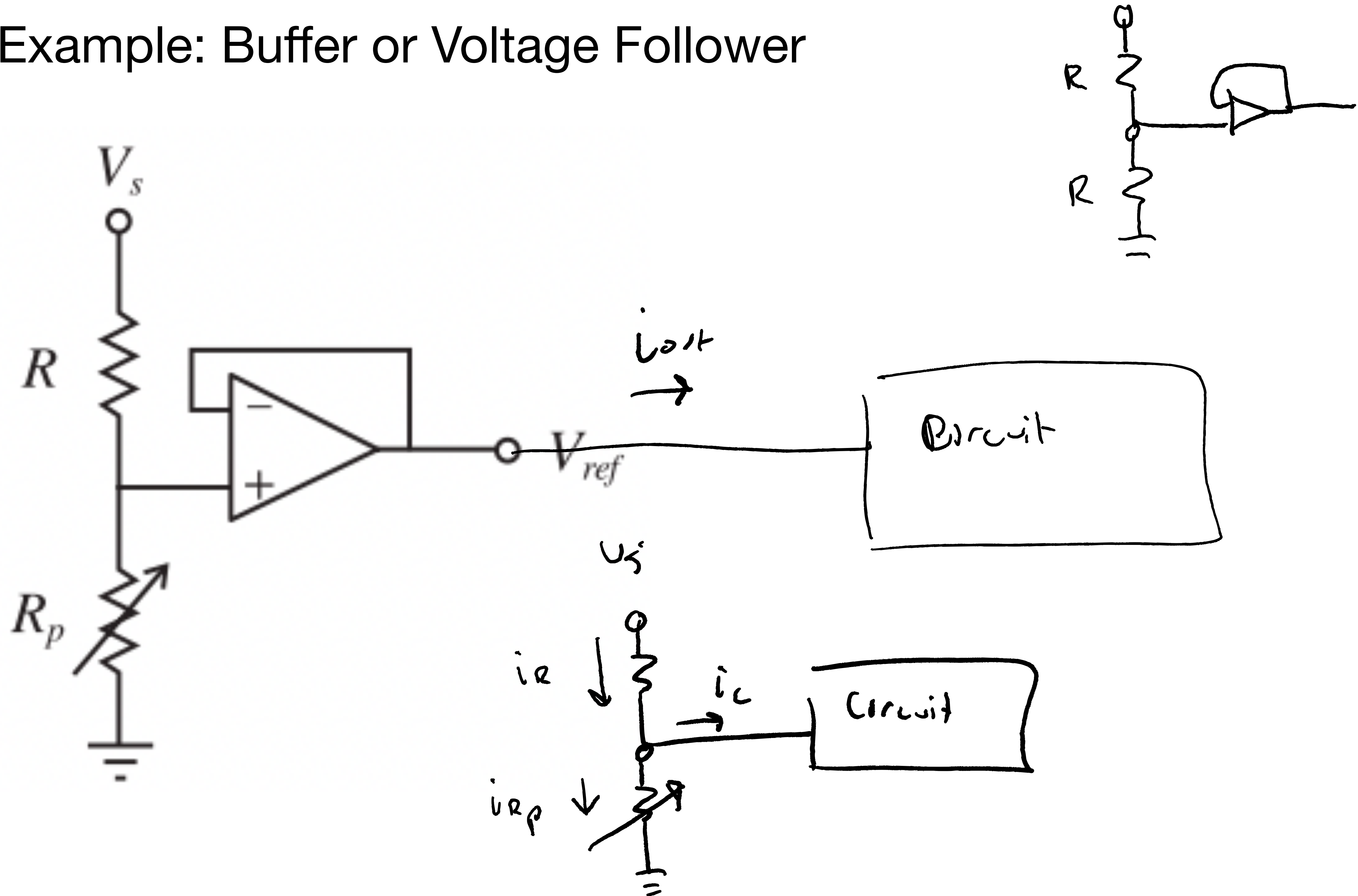

Example: Buffer or Voltage Follower

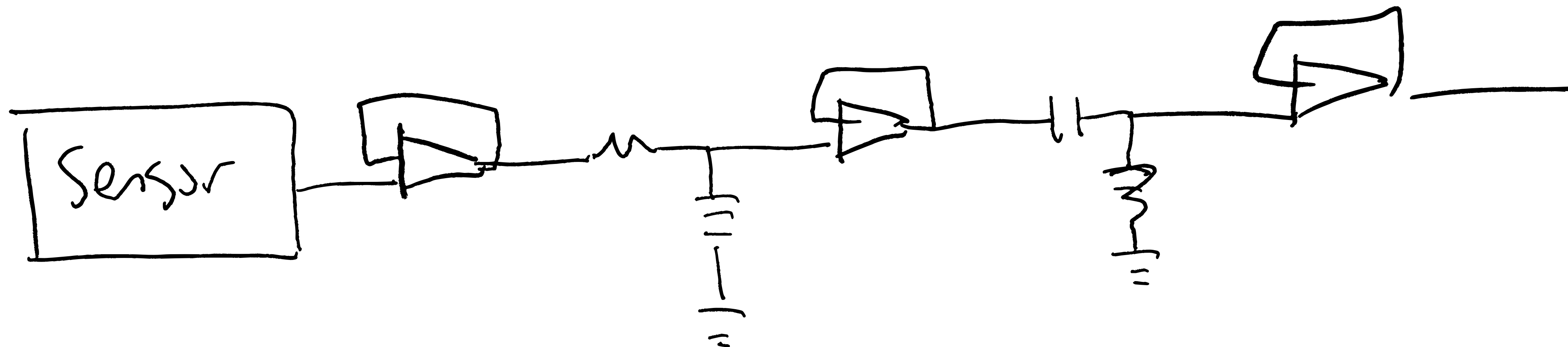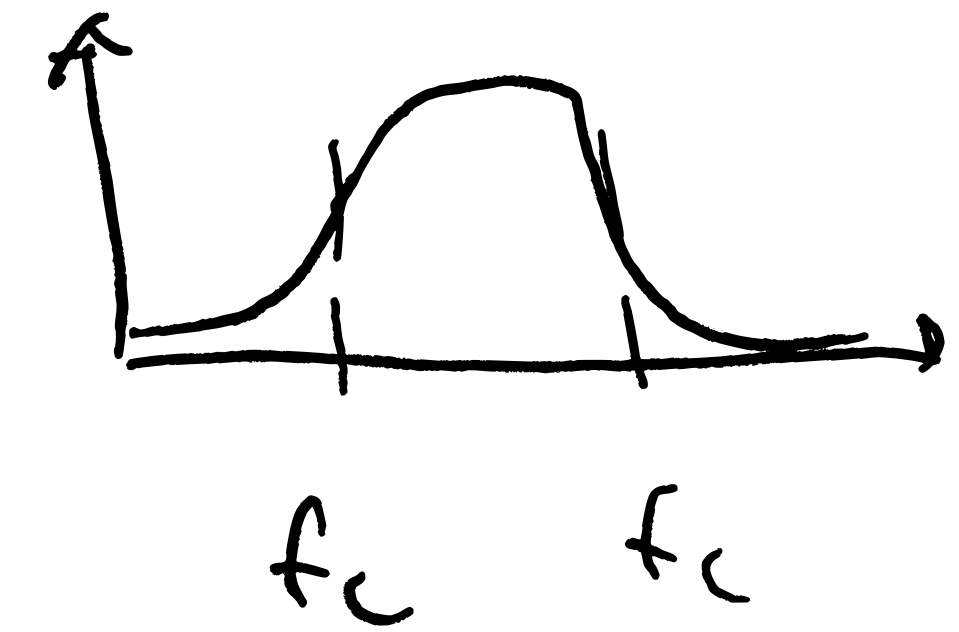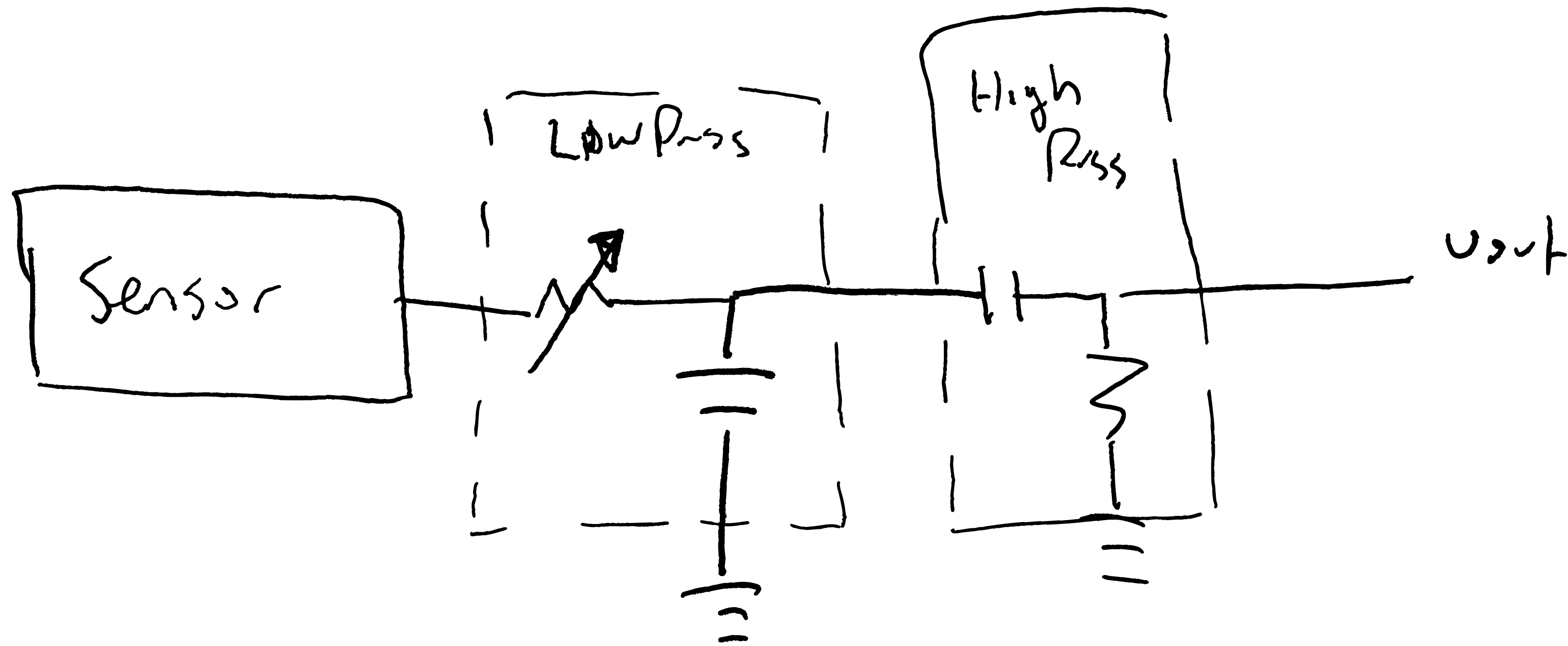

■ CLASS DISCUSSION ITEM 5.3

Example of Positive Feedback


A good example of positive feedback is the effect Jimi Hendrix used to achieve when he would move his guitar close to the front of his amplifier speaker. Describe the effect of this technique and describe what is going on physically. Video Demo 5.5 demonstrates how positive feedback can be used to accentuate string harmonics (modes of vibration), and Video Demo 5.6 shows an example of Jimi's performance style, which was quite unique and impressive.

■ CLASS DISCUSSION ITEM 5.4

Voltage Divider with No Follower

With the voltage-divider follower circuit in Figure 5.13, what effect does the choice of resistance values have? Also, explain in detail what would happen if the follower circuit were not included and the reference voltage were used to source current to another circuit or device.

Example: Summer

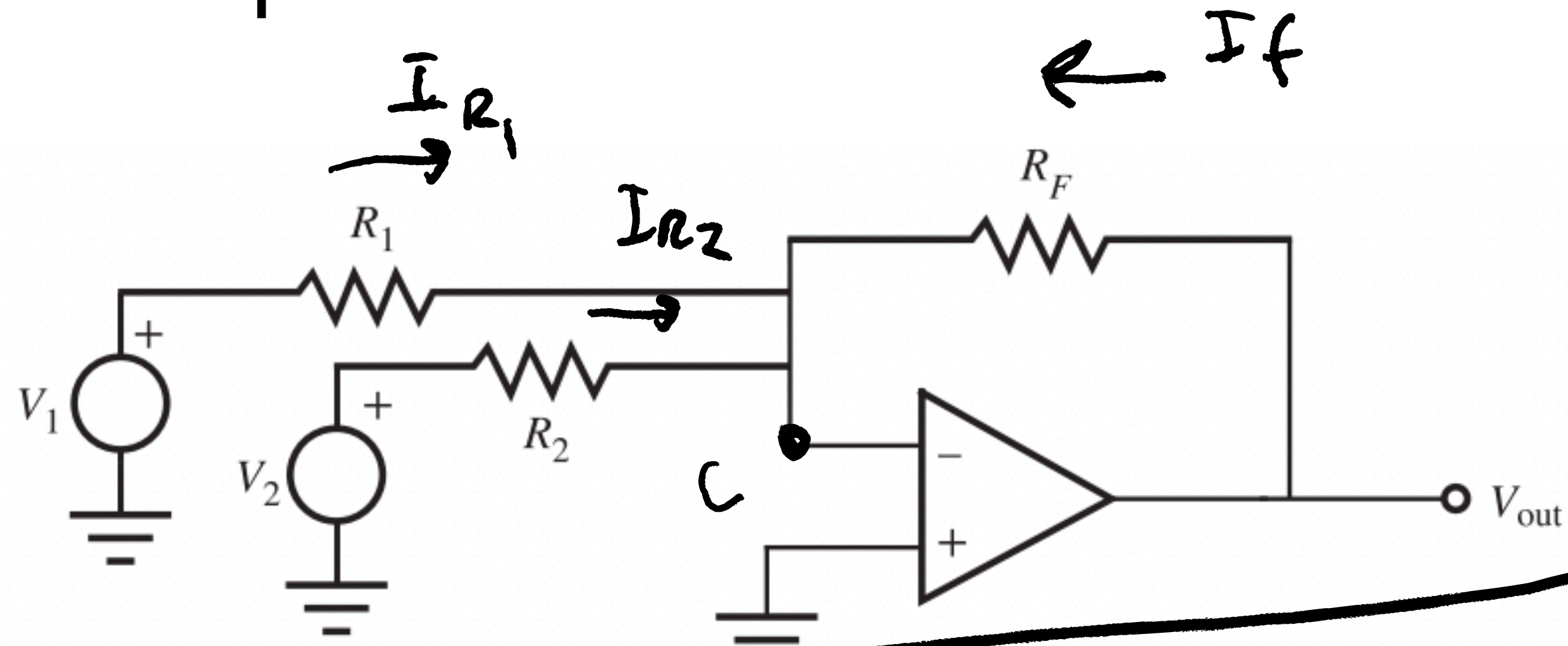

KCL @ Node C:

$$I_{R_1} + I_{R_2} = -I_f$$


$$V_- = V_+ = 0$$

$$I_- = I_+ = 0$$

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} = -\frac{V_{out}}{R_f}$$

$$V_{out} = -\left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2\right)$$

Example: Integrator

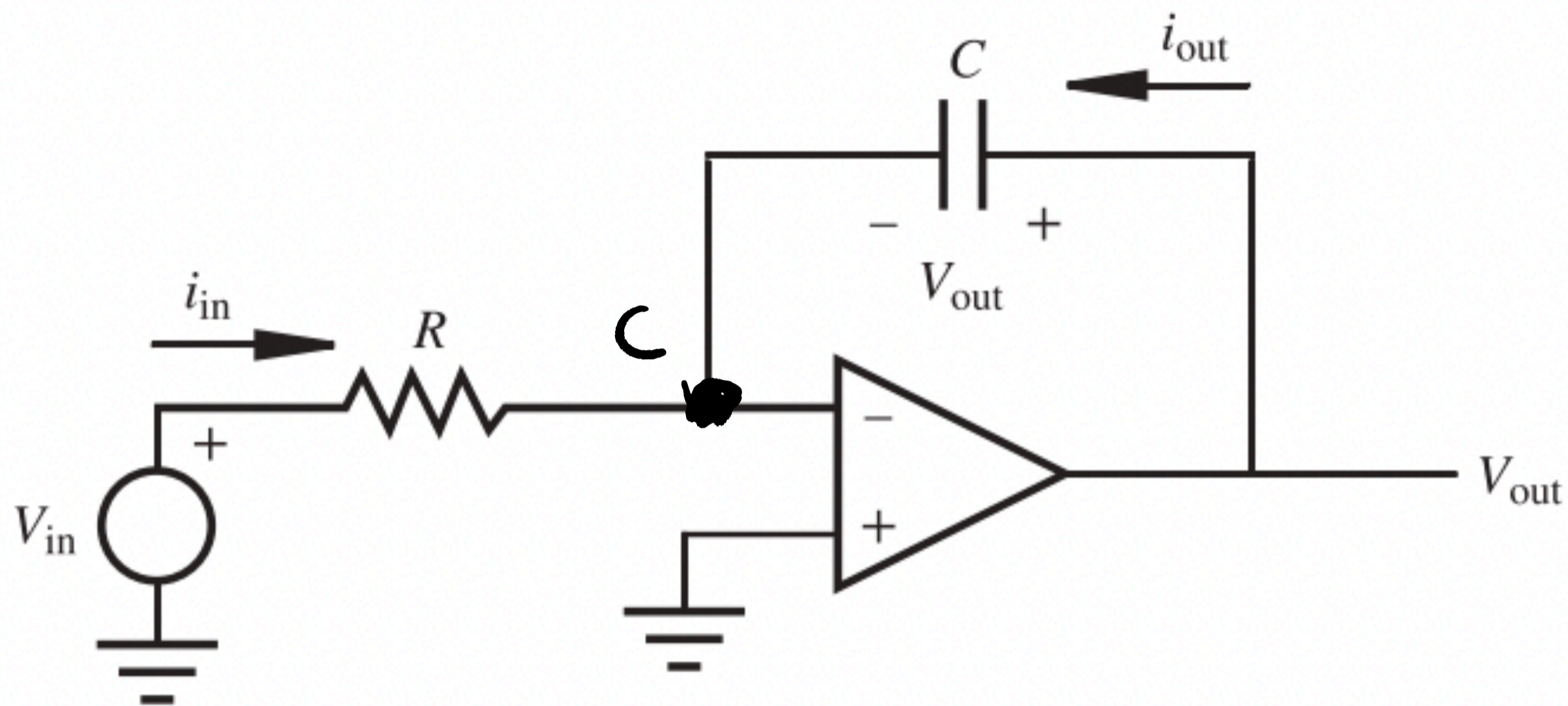

KCL:

$$I_R = -I_{out}$$

$$\frac{V_{in}}{R} = -C \frac{dV_{out}}{dt}$$

$$\dot{V}_{out} = -\frac{1}{RC} \cdot V_{in}$$


$$V_{out} = -\frac{1}{RC} \int_0^t V_{in}(t) dt$$

→ reverse input from serial monitor.


What key do we play?

0, -1

Example: Differentiator

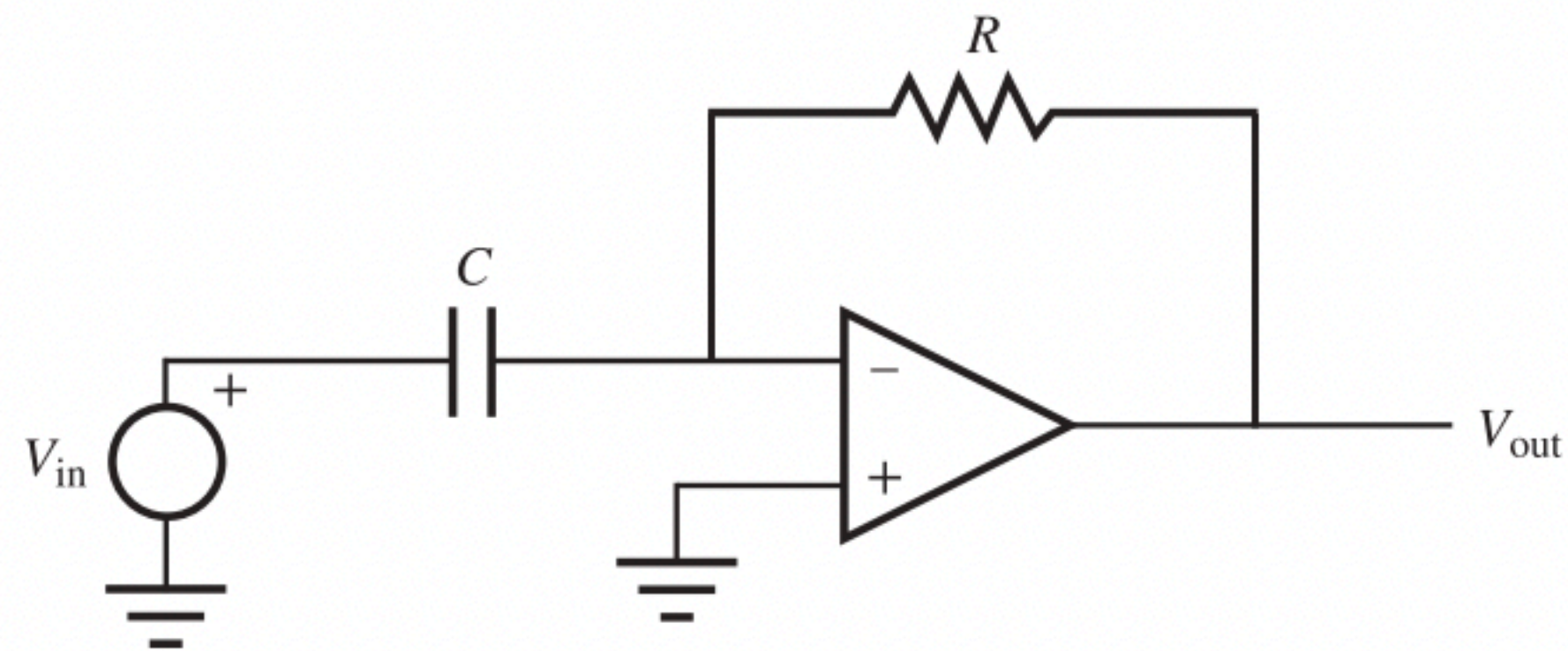


$$\dot{V}_{out} = -RC \dot{V}_{in}$$

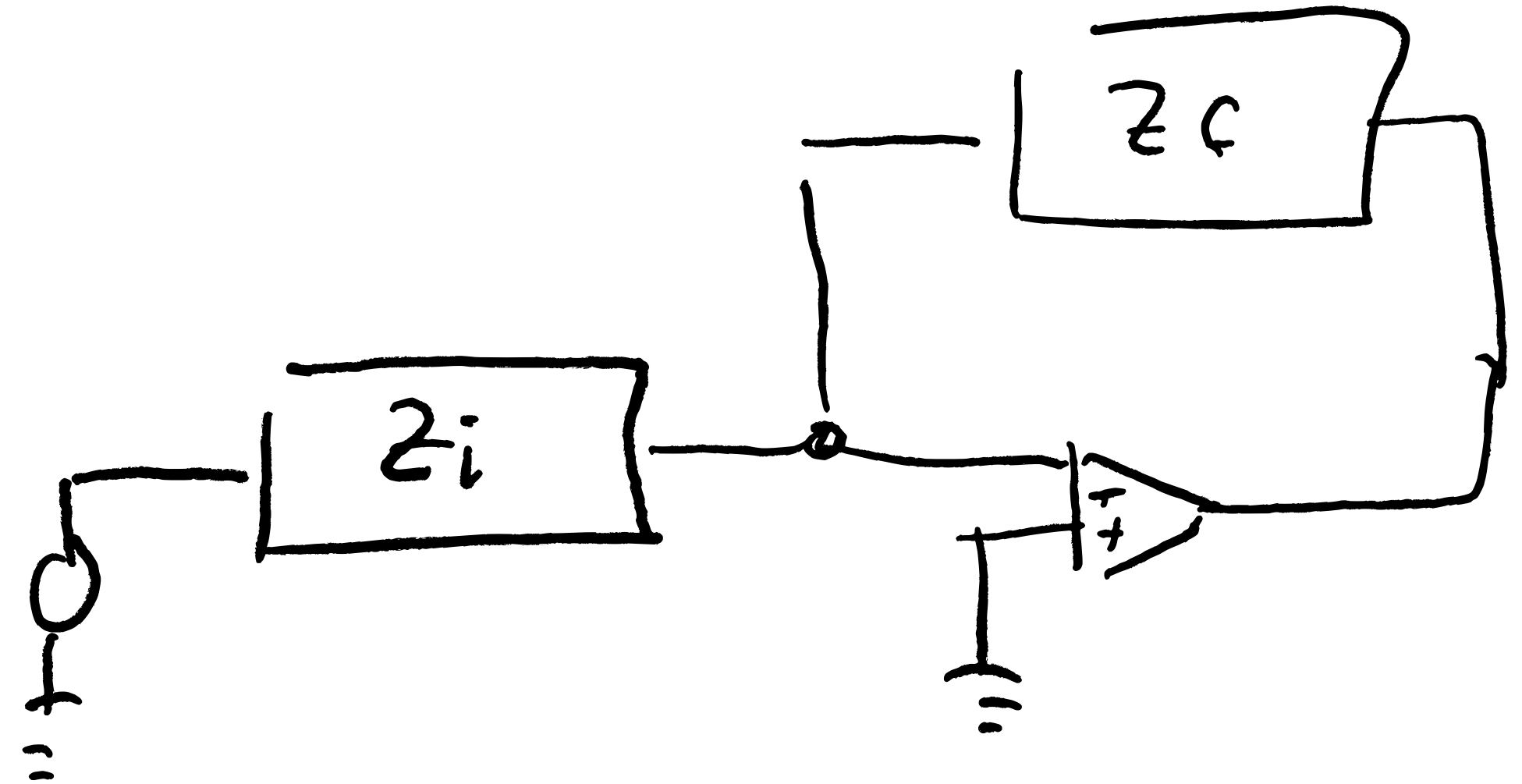

$$\frac{V_{out}}{V_{in}} = -\frac{Z_f}{Z_i}$$


Example: Comparator

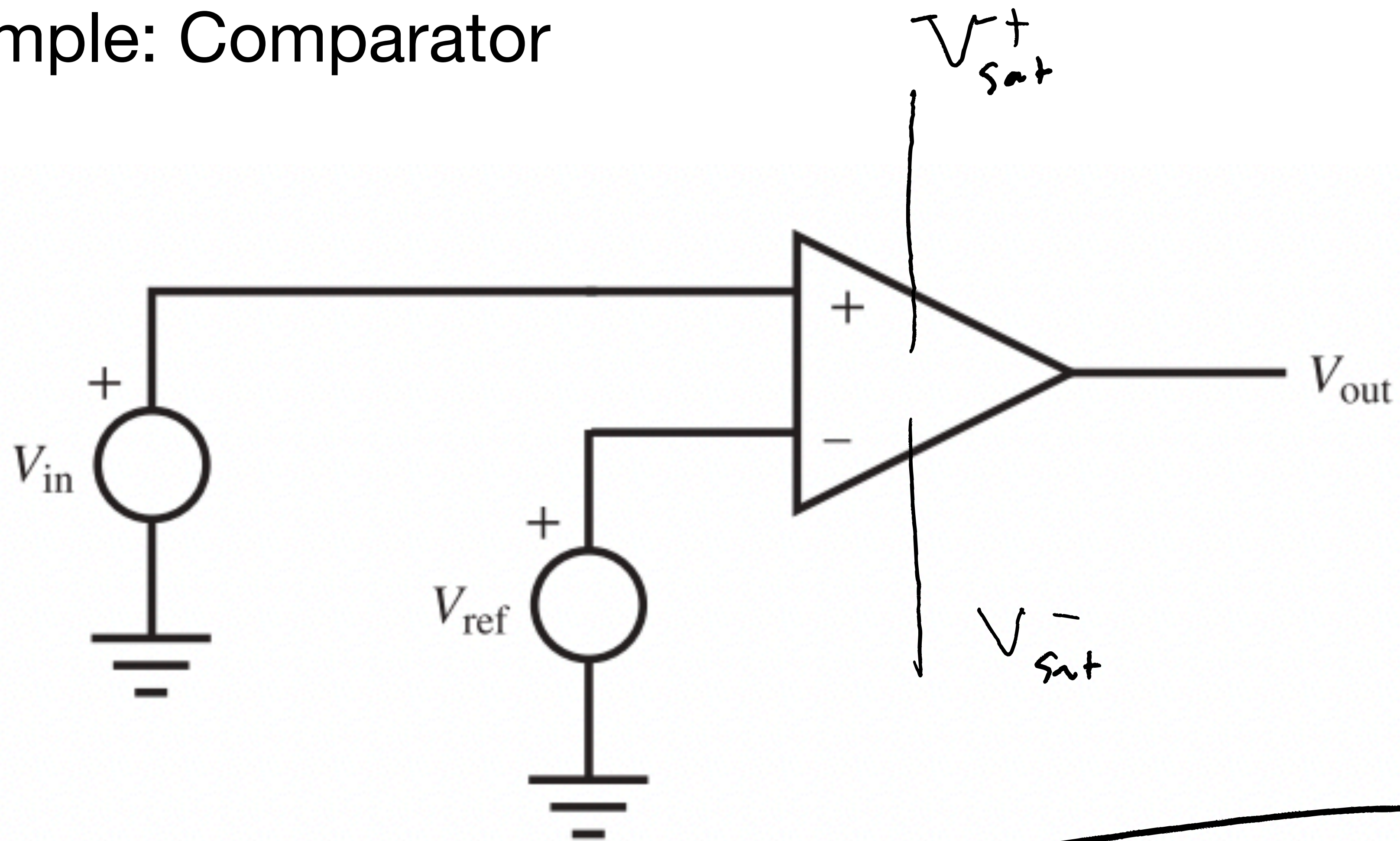

$$V_{out} = \begin{cases} +V_{sat} & V_{in} > V_{ref} \\ -V_{sat} & V_{in} < V_{ref} \end{cases}$$

Example: Active Filters

Example: Sample and Hold

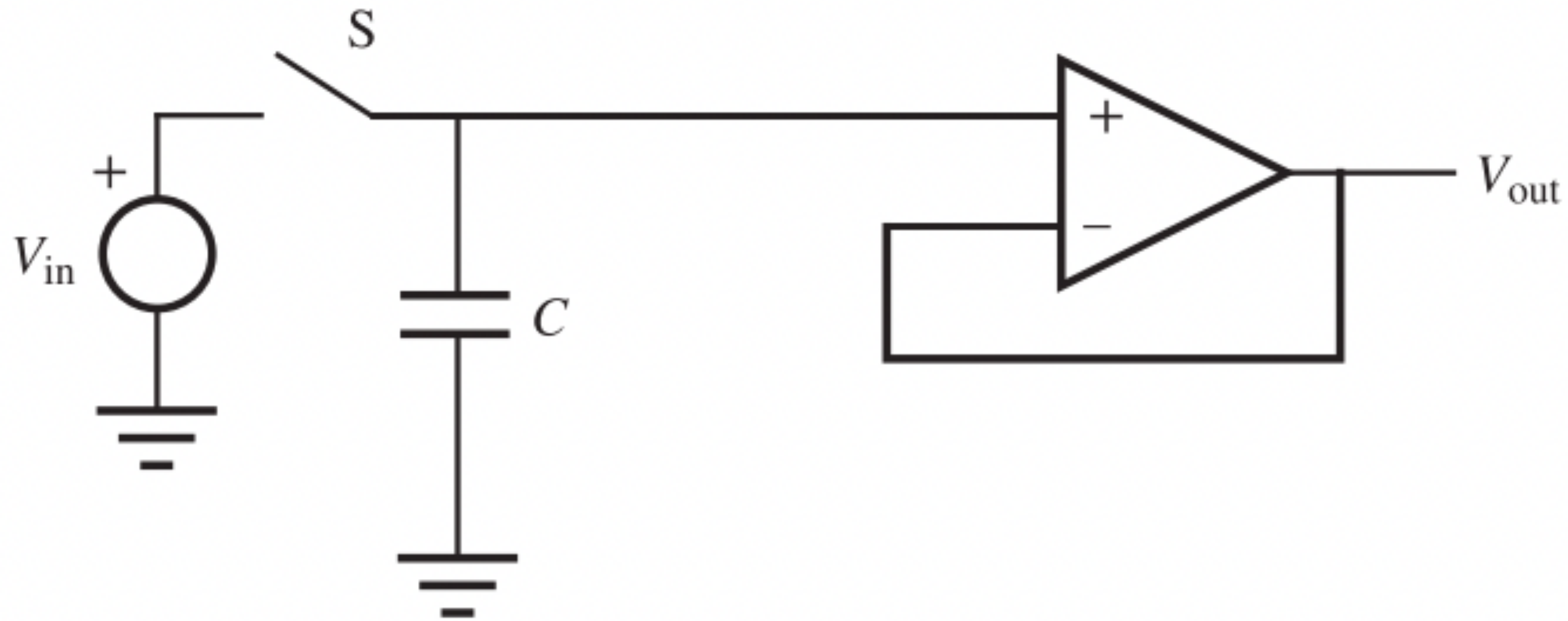

$$V_{out}(t - t_{\text{sampled}}) = V_{in}(t_{\text{sampled}})$$

where t_{sampled} is the time when the switch was last opened.

Example: Instrumentation Amplifier

