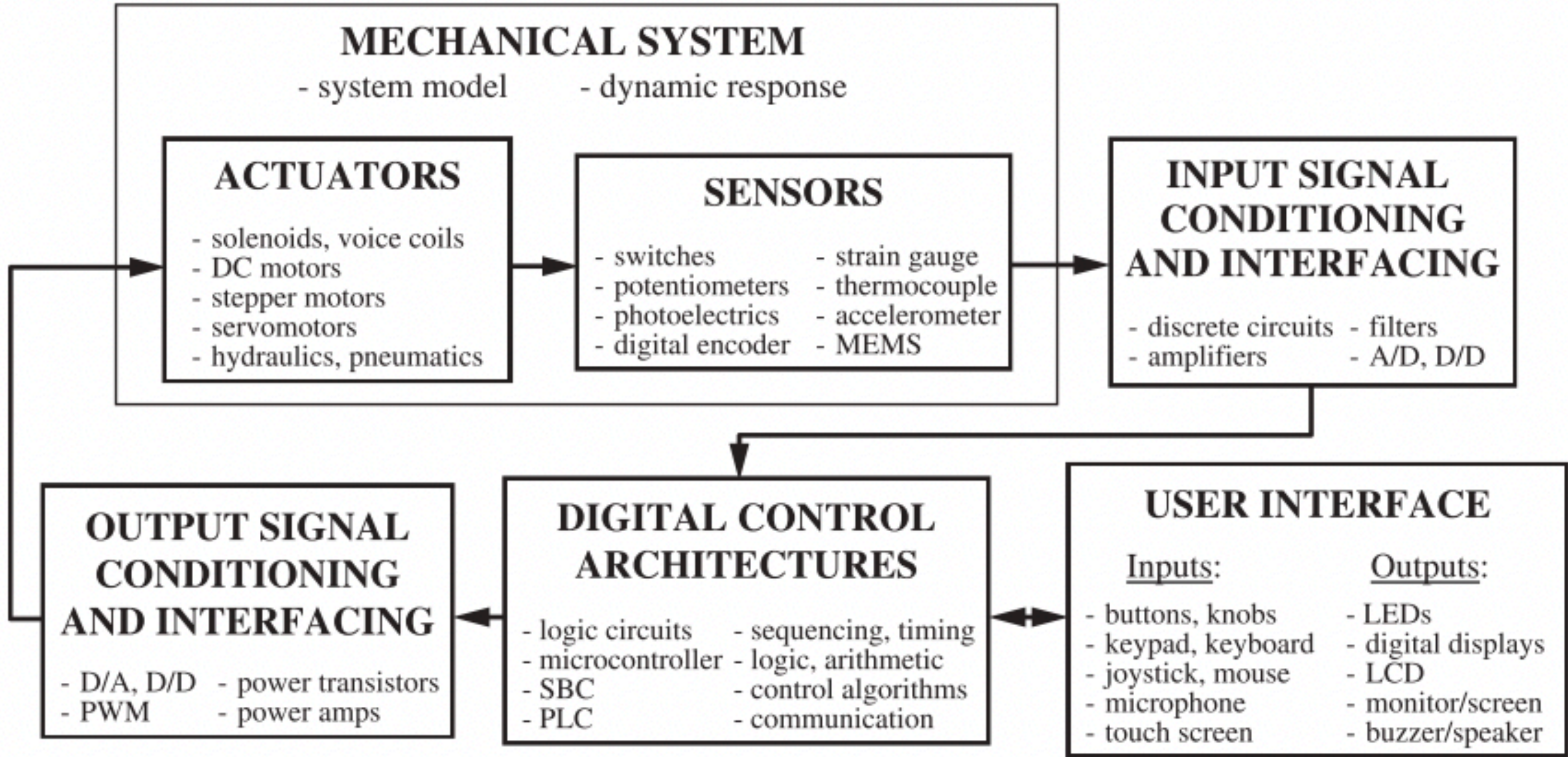


Last time:

> What is mechatronics?



Quick Poll: How many have used ChatGPT?

5

Today:

- Basic electronic components
 - Kirchoff's Laws
 - Examples
-

All mechatronics systems contain electrical circuits

How do circuits work?

Today → Passive components?

- ↳ store or dissipate energy
- ↳ don't external power

Electricity Basics

Voltage: a measure of electric field potential.

→ relative

* analogous to potential energy in gravity field


Current: time rate of "flow of charge"

$$I(t) = \frac{dq}{dt} \begin{array}{l} \rightarrow \text{charge} \\ \rightarrow \text{time} \end{array} \quad (A) \text{ amps}$$

Hydraulic Analogy

Voltage: a measure of electric field potential

Current: time rate of “flow of charge”

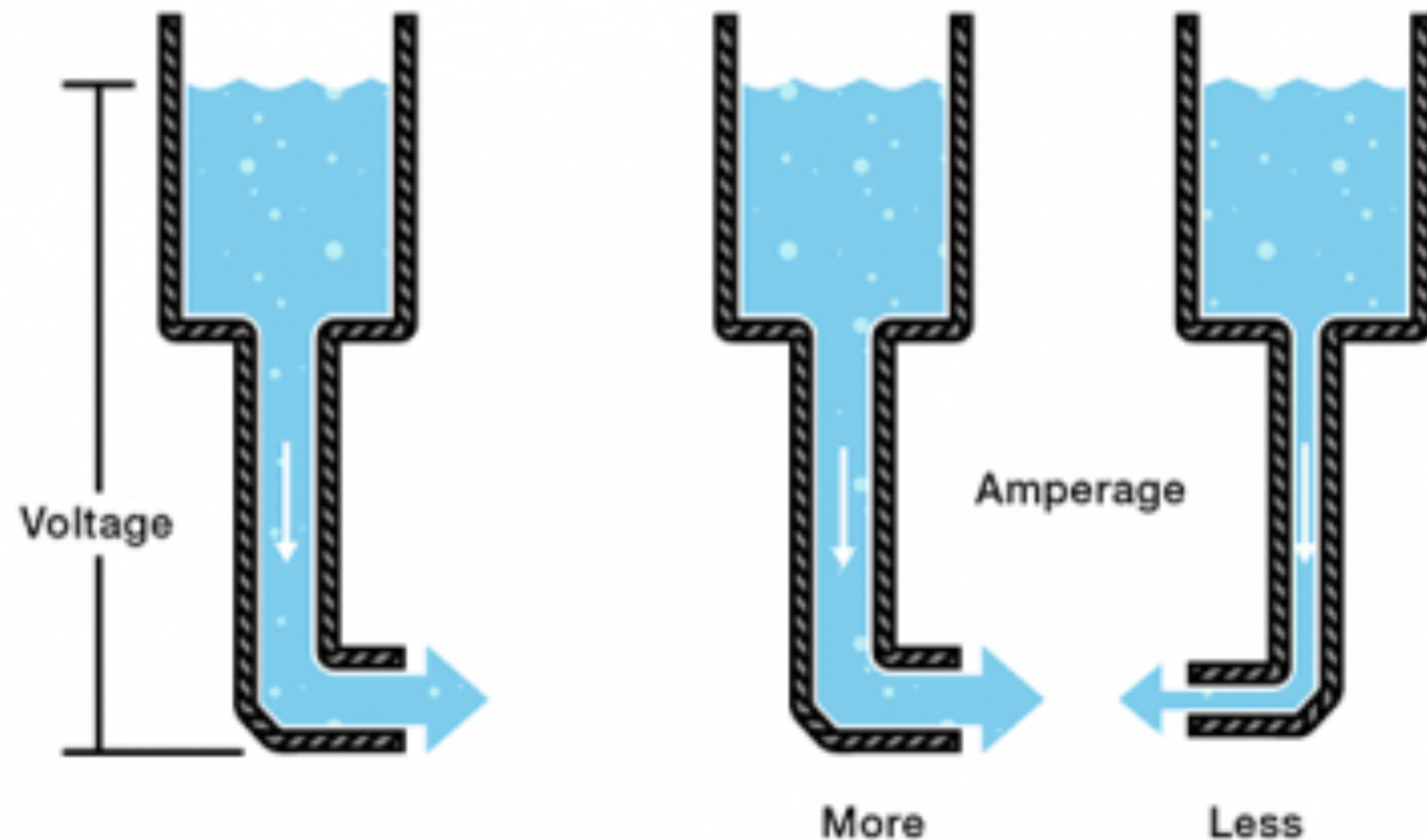

Direct vs Alternating Current

DC: $V = \text{constant}$
 $I = \text{constant}$

Examples: Batteries, USB
Solar cells, Fuel cells


AC: $V = f(t)$
 $I = f(t)$
function of time
(sinusoidal)

Examples: wall plug (outlet)
↳ power lines

Electrical Circuit


allow current to flow

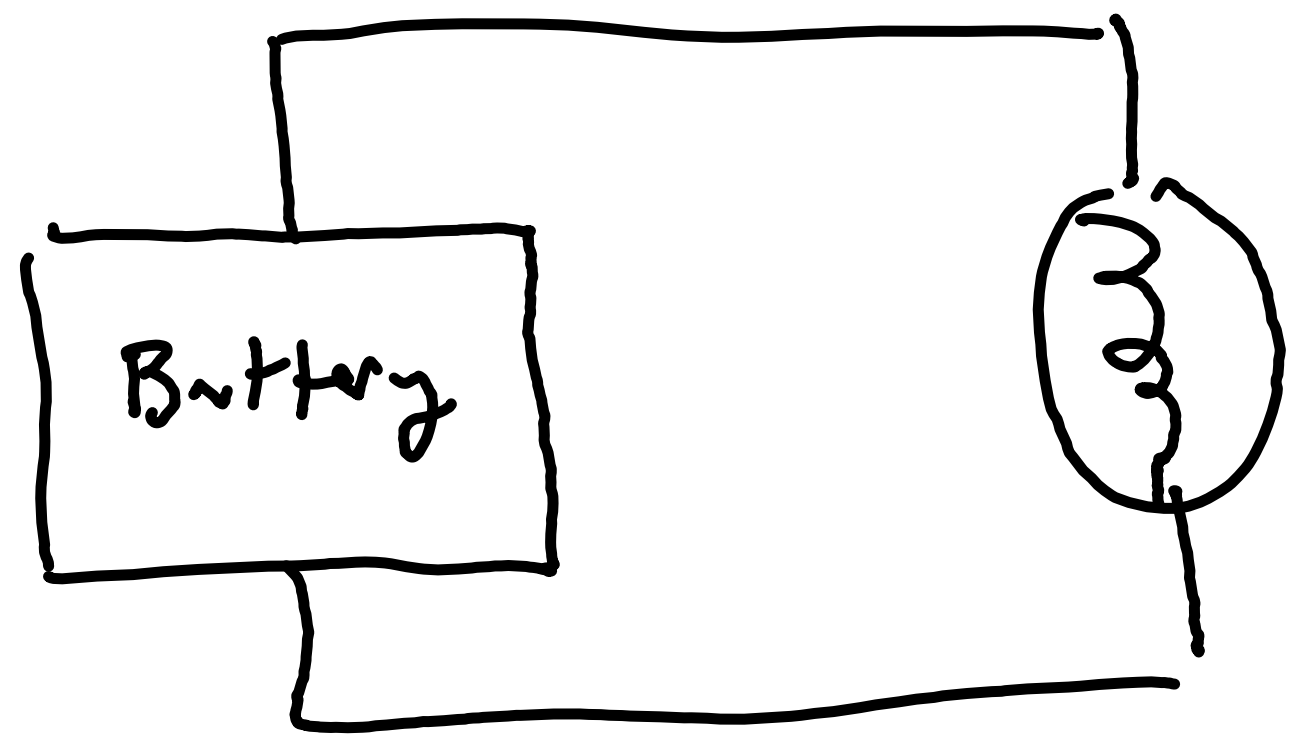Close loop of **conductors** connecting electrical components




DC

light

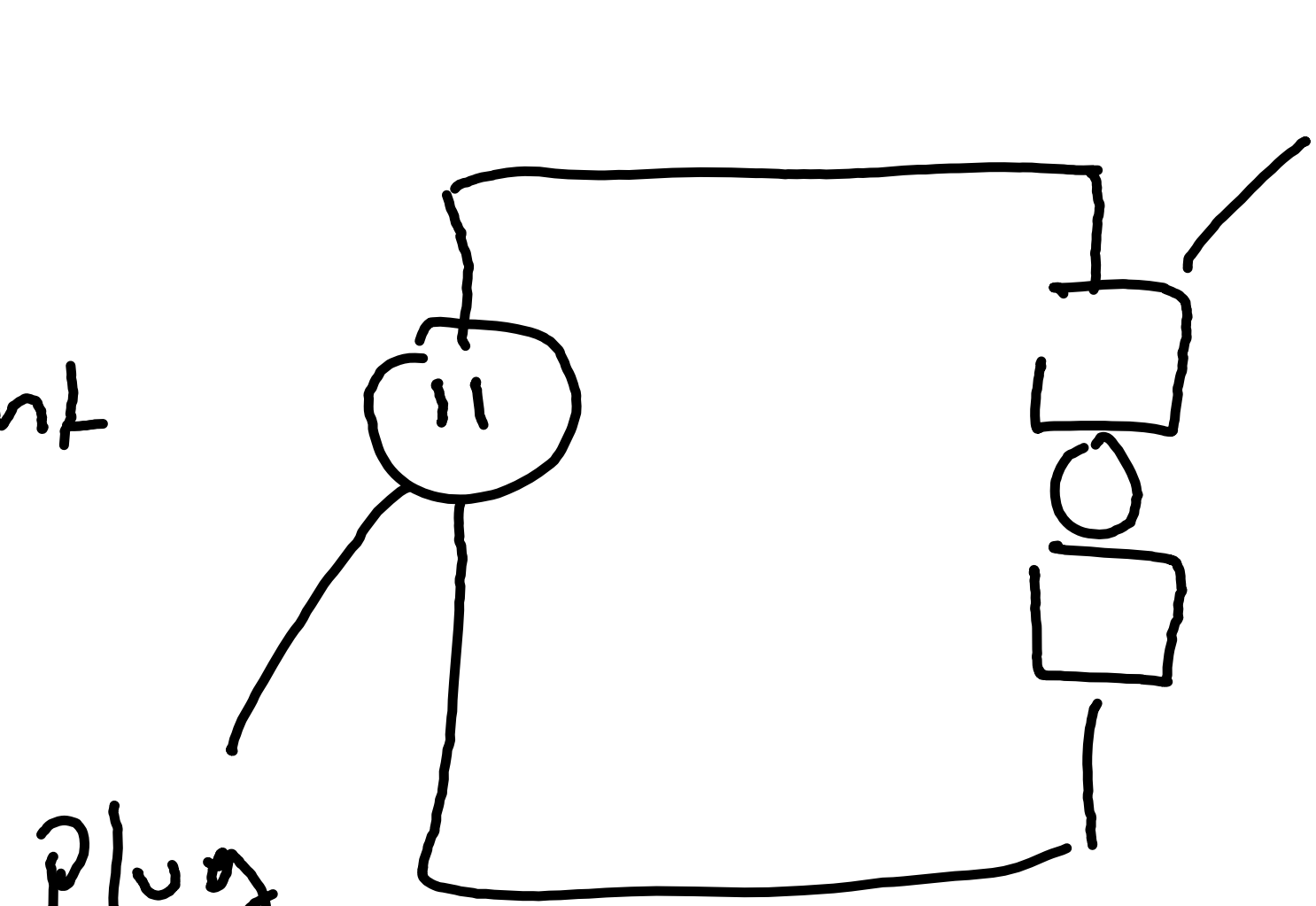

AC


switch

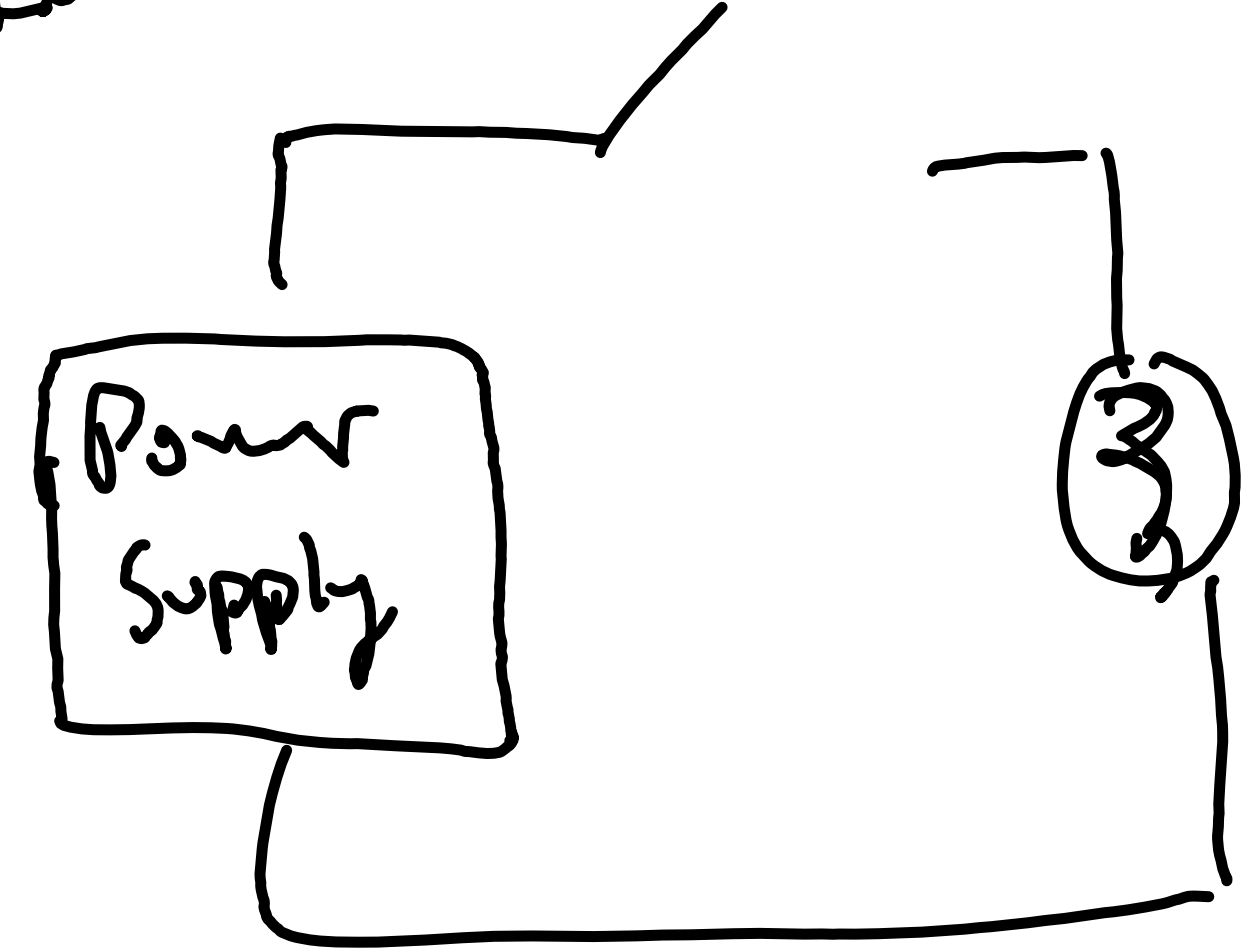


open circuit
until switch
is closed

light

Terminology and Conventions

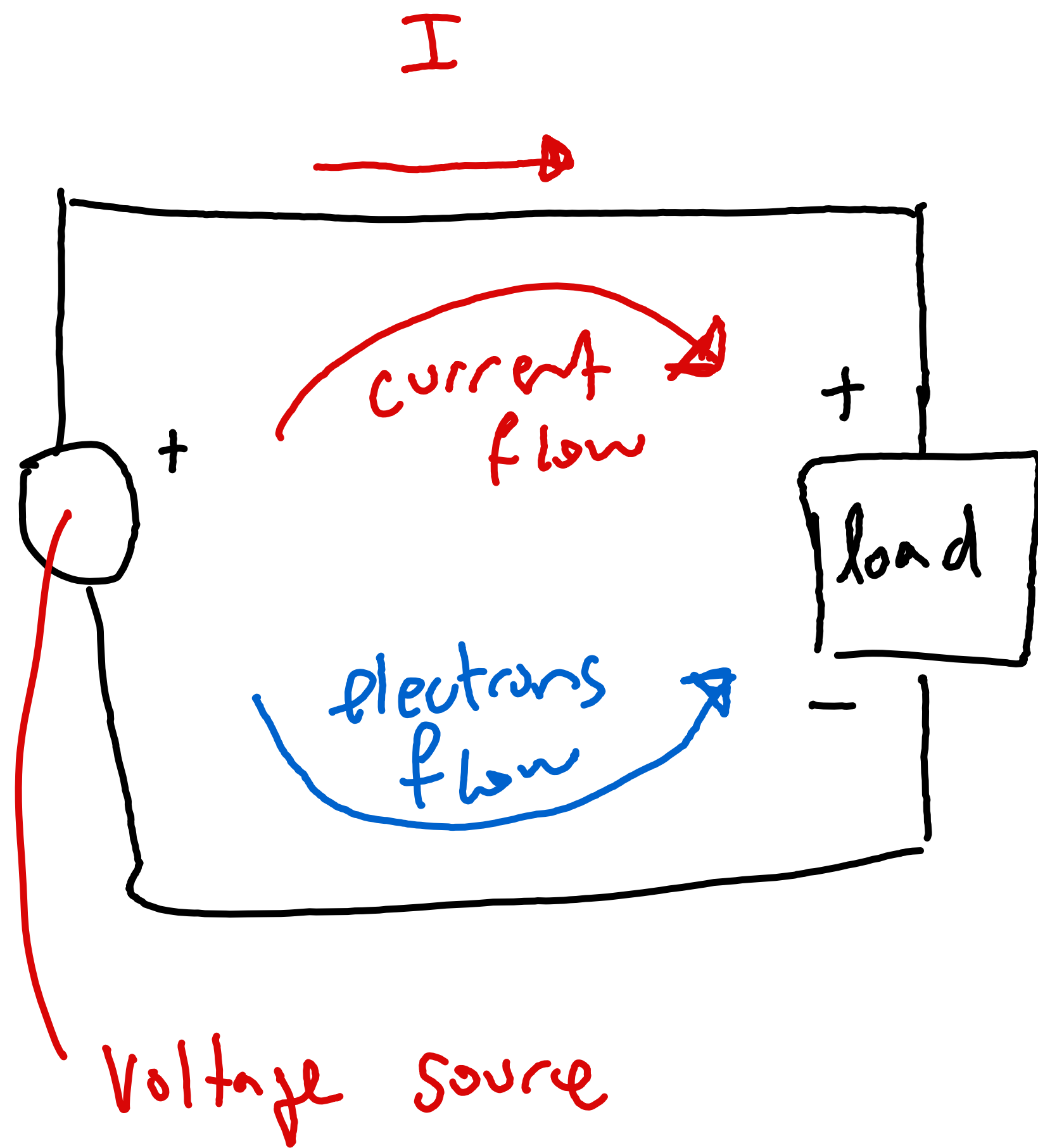

Voltage drop

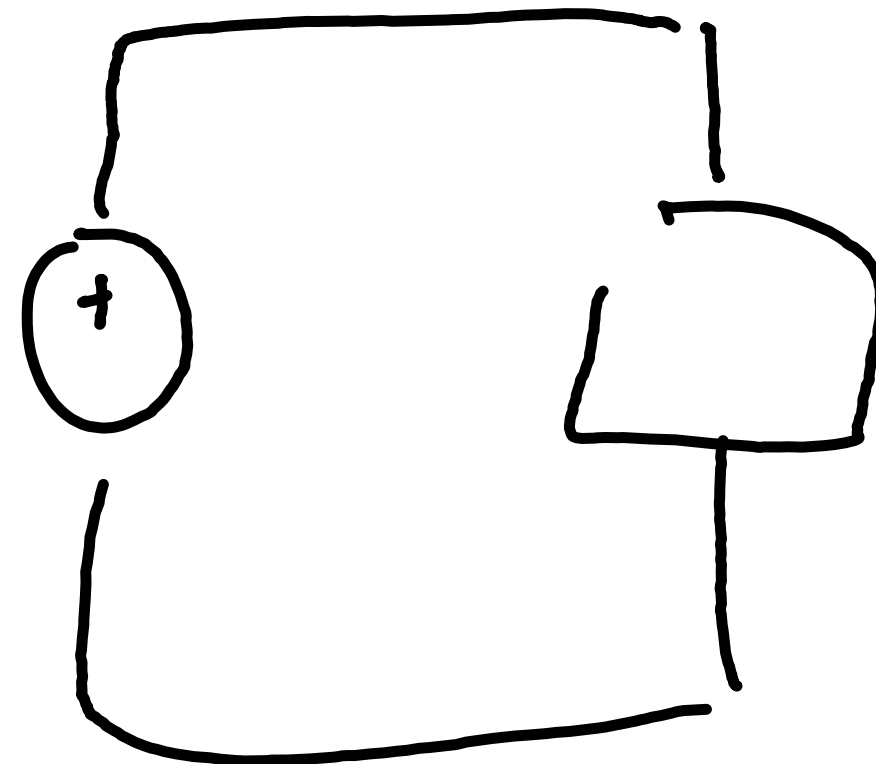

Current

flow of positive charge

Load


network of electrical components that store/dissipate energy

Ground


reference point of circuit where voltage is zero

Basic Ideal Electrical Components

(3 + 2 ideal sources)

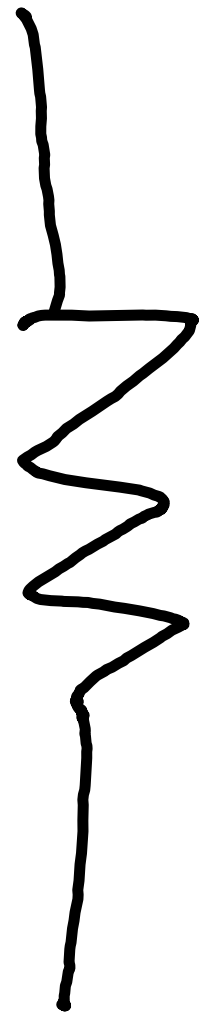


Resistor

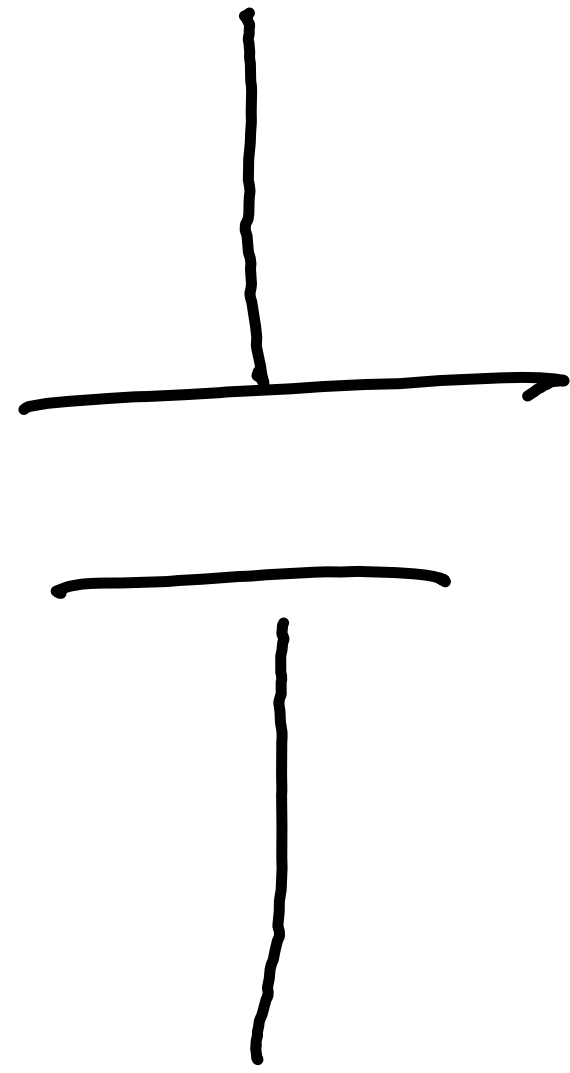


Capacitor



Inductor

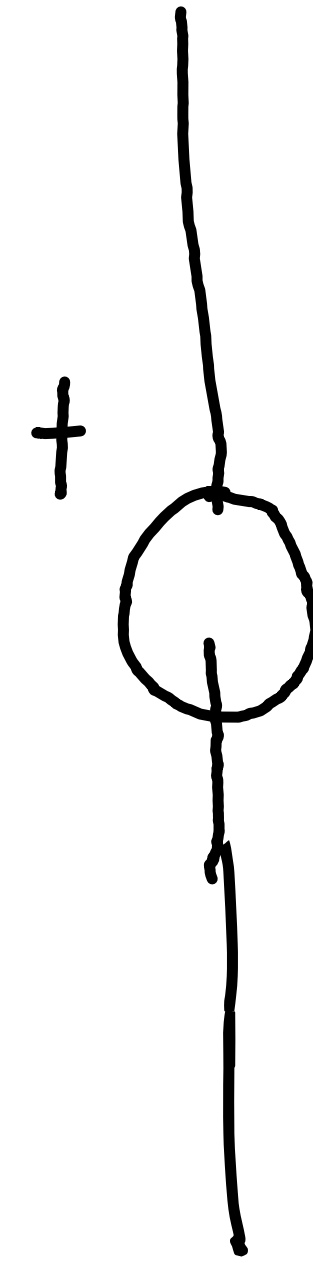

Voltage
source

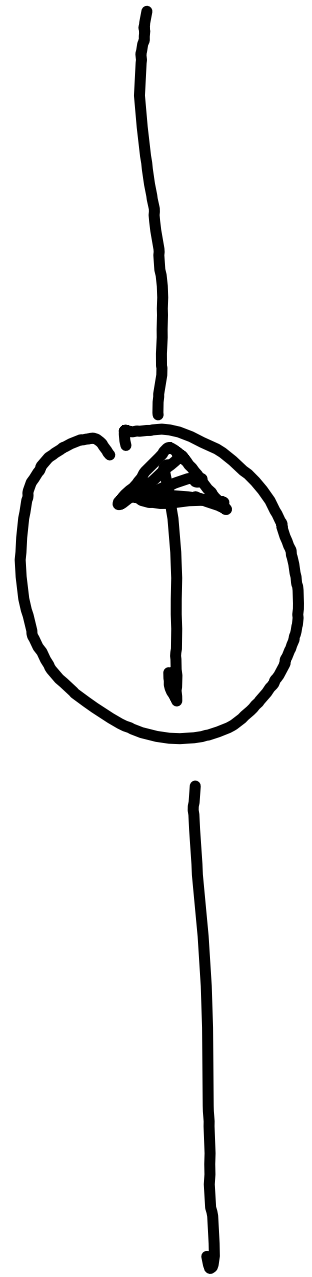


Current
source

Resistor: converts electrical energy into heat
(dissipates energy)



Ohms Law:

$$V = IR$$

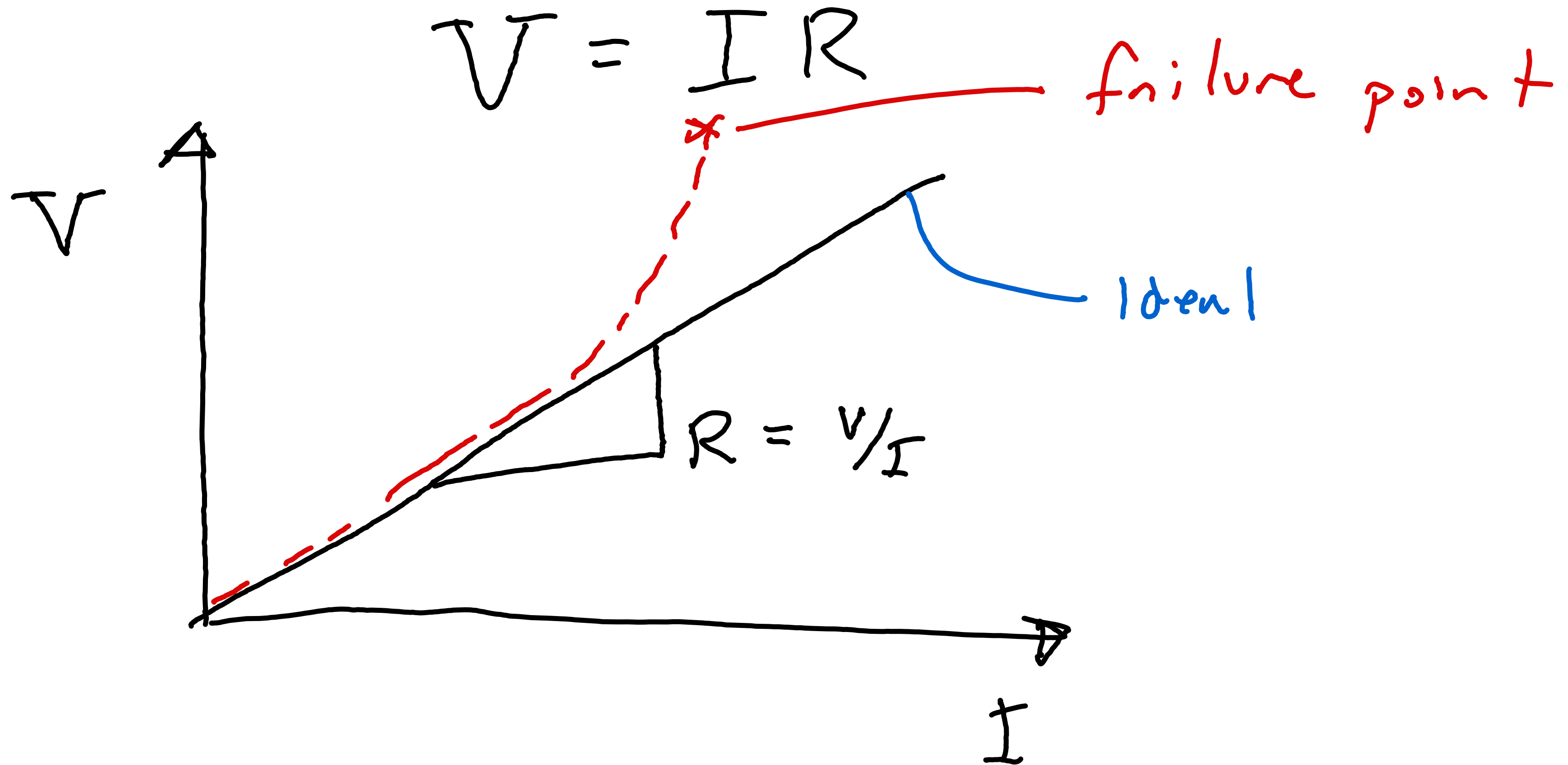

For homogenous material with constant cross-sectional area


$$R = \frac{\rho L}{A}$$

L: length

rho: resistivity

A: cross-sectional area


material property

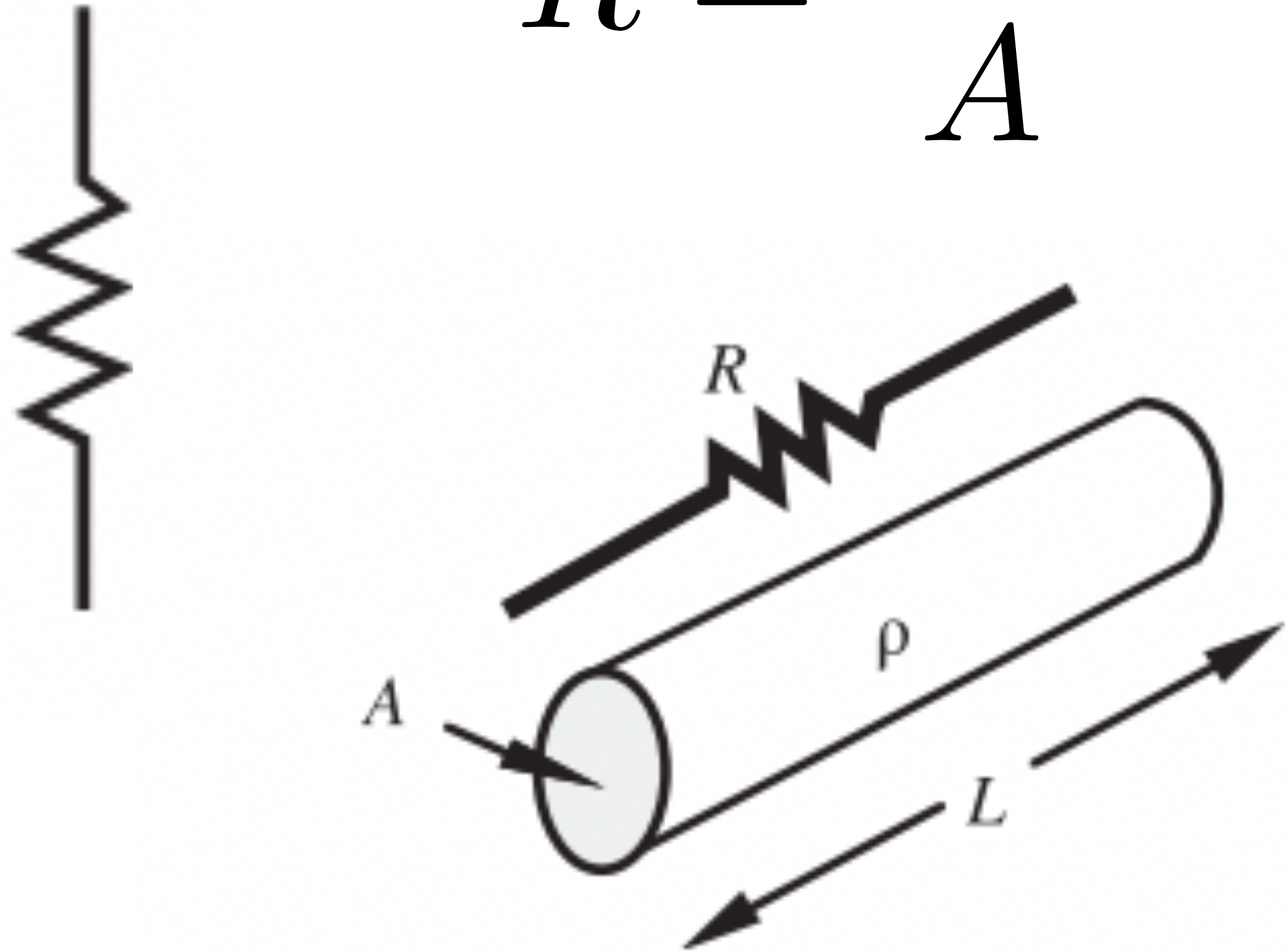

Water Analogy for a resistor

Water Analogy for a resistor



Less resistance

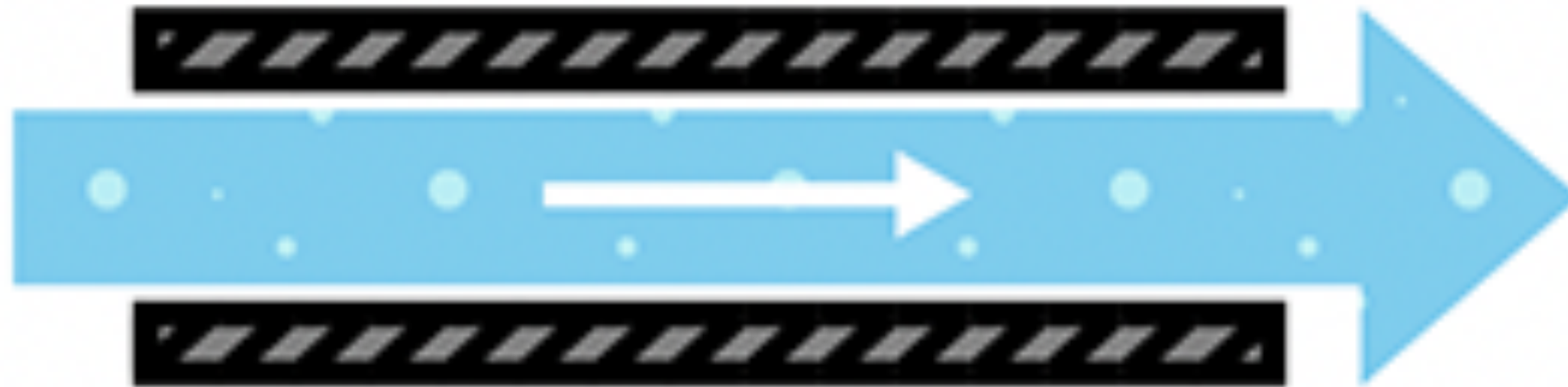

More resistance




Potentiometer: variable resistor

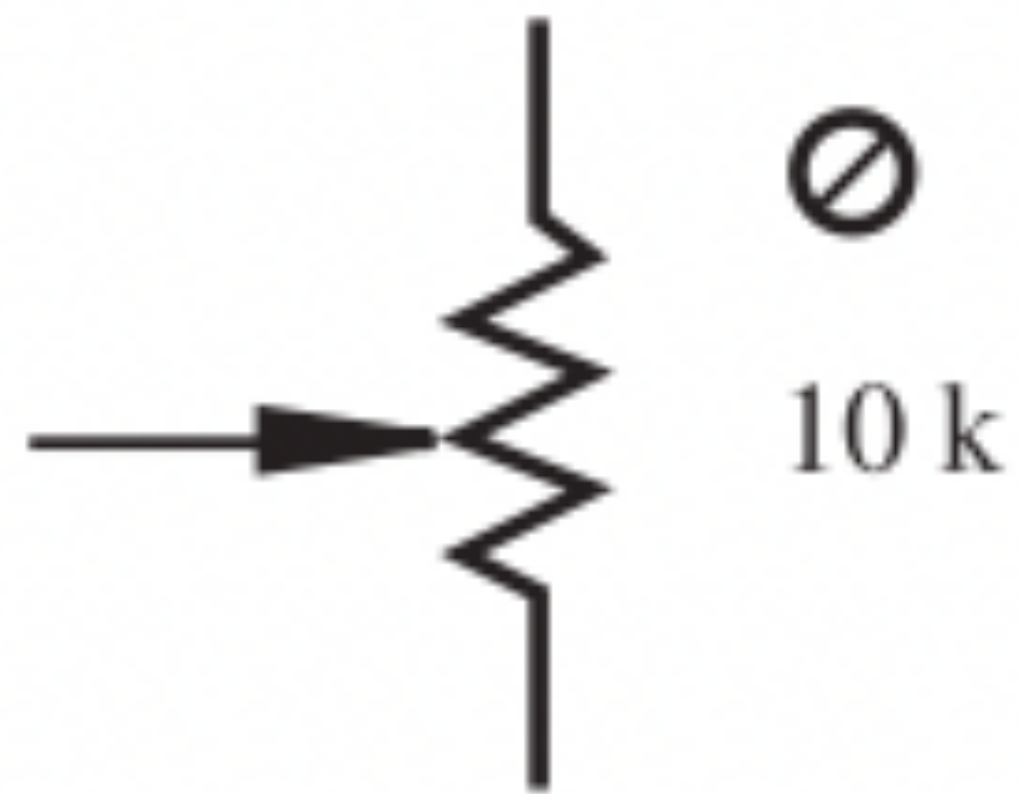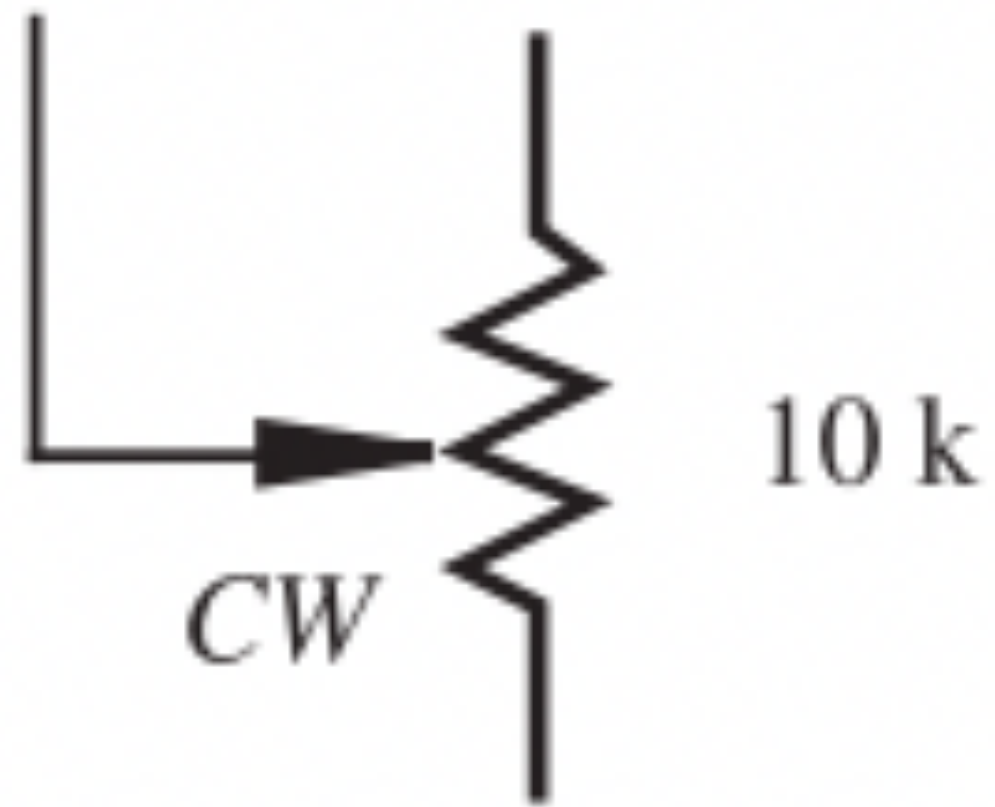

Capacitor: stores energy in the form of an electric field

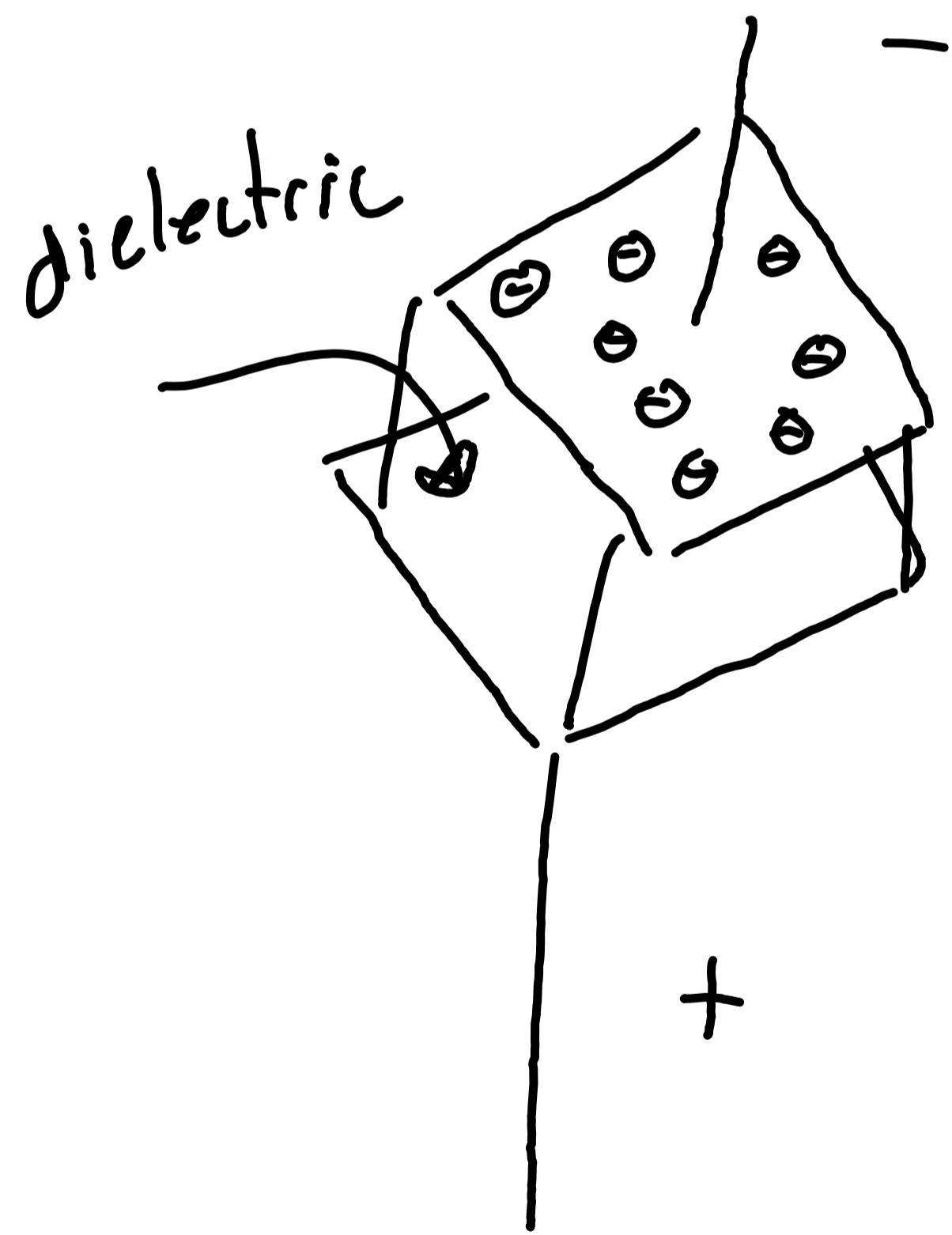simplest is made w/ parallel conductors separated by dielectric material



$$V(t) = \frac{1}{C} \int_0^t I(\tau) d\tau$$

$$= \frac{q(t)}{C}$$

$$\frac{d}{dt} V(t) = \frac{1}{C} \left(\frac{d}{dt} q(t) \right)$$



$$\Rightarrow I(t) = \frac{1}{C} \frac{dV}{dt}$$

$$\Rightarrow I = C \dot{V}$$


C: capacitance

→ material & geometric property Farads


Water Analogy for a capacitor

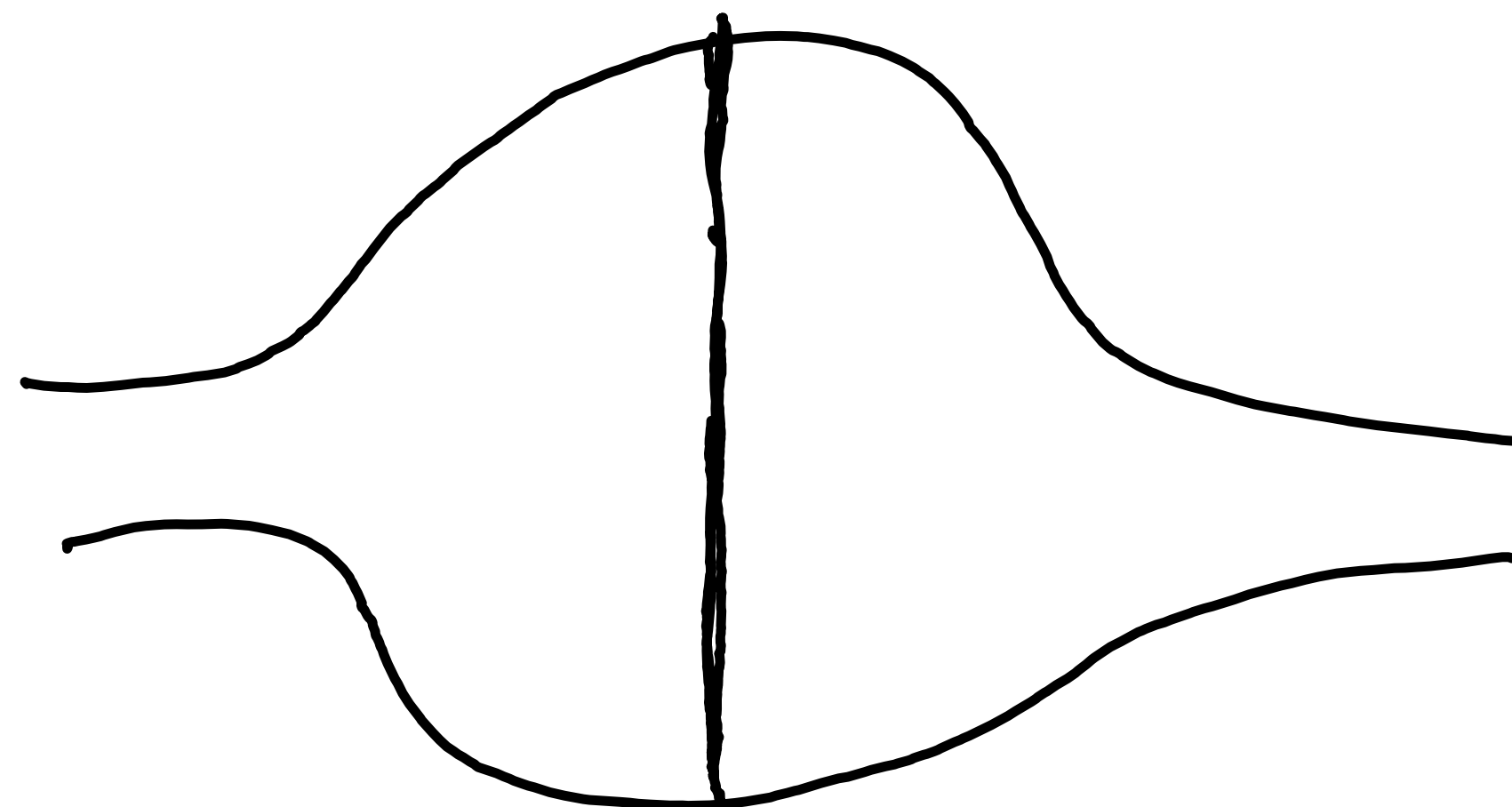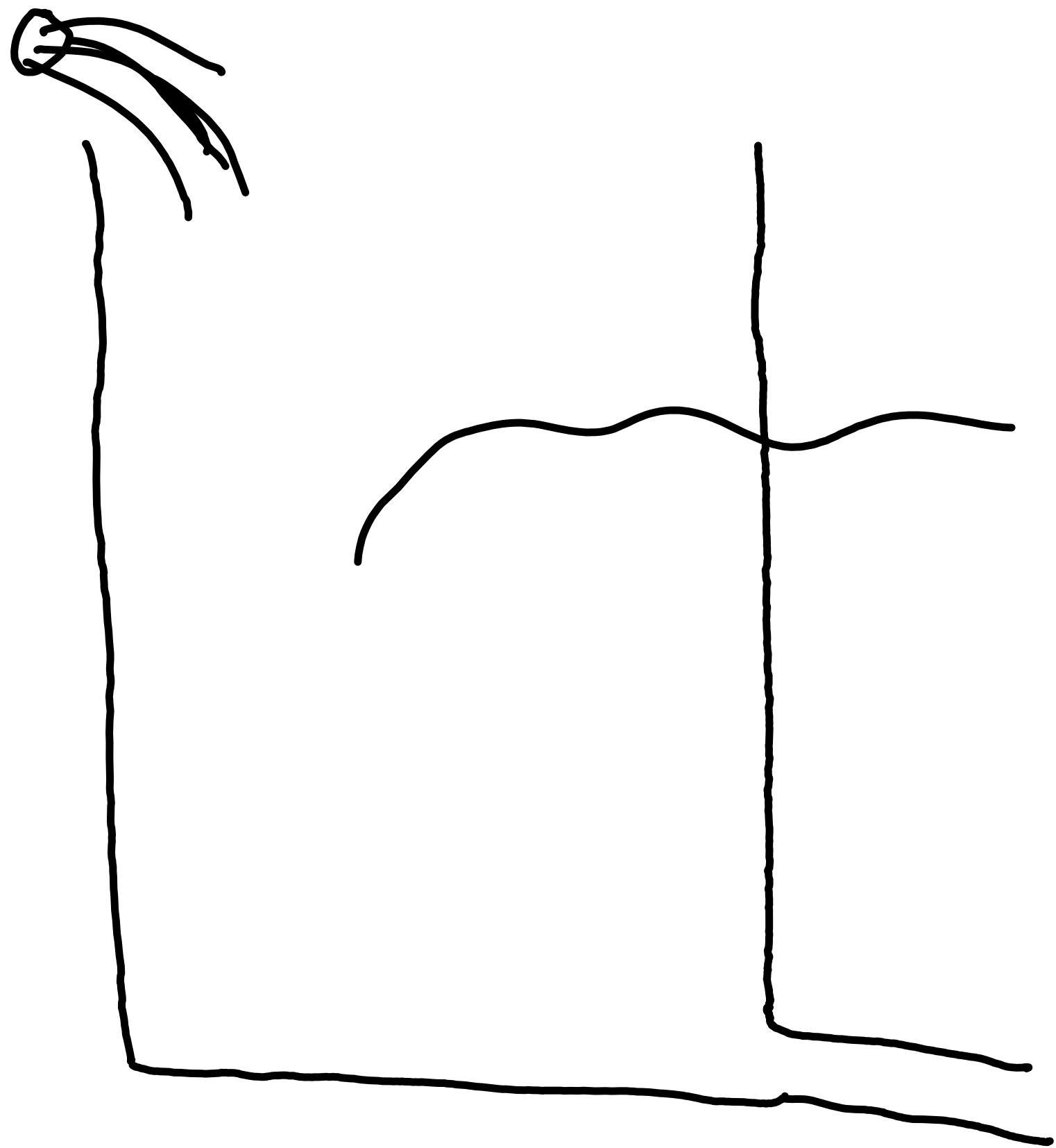

Water Analogy for a capacitor

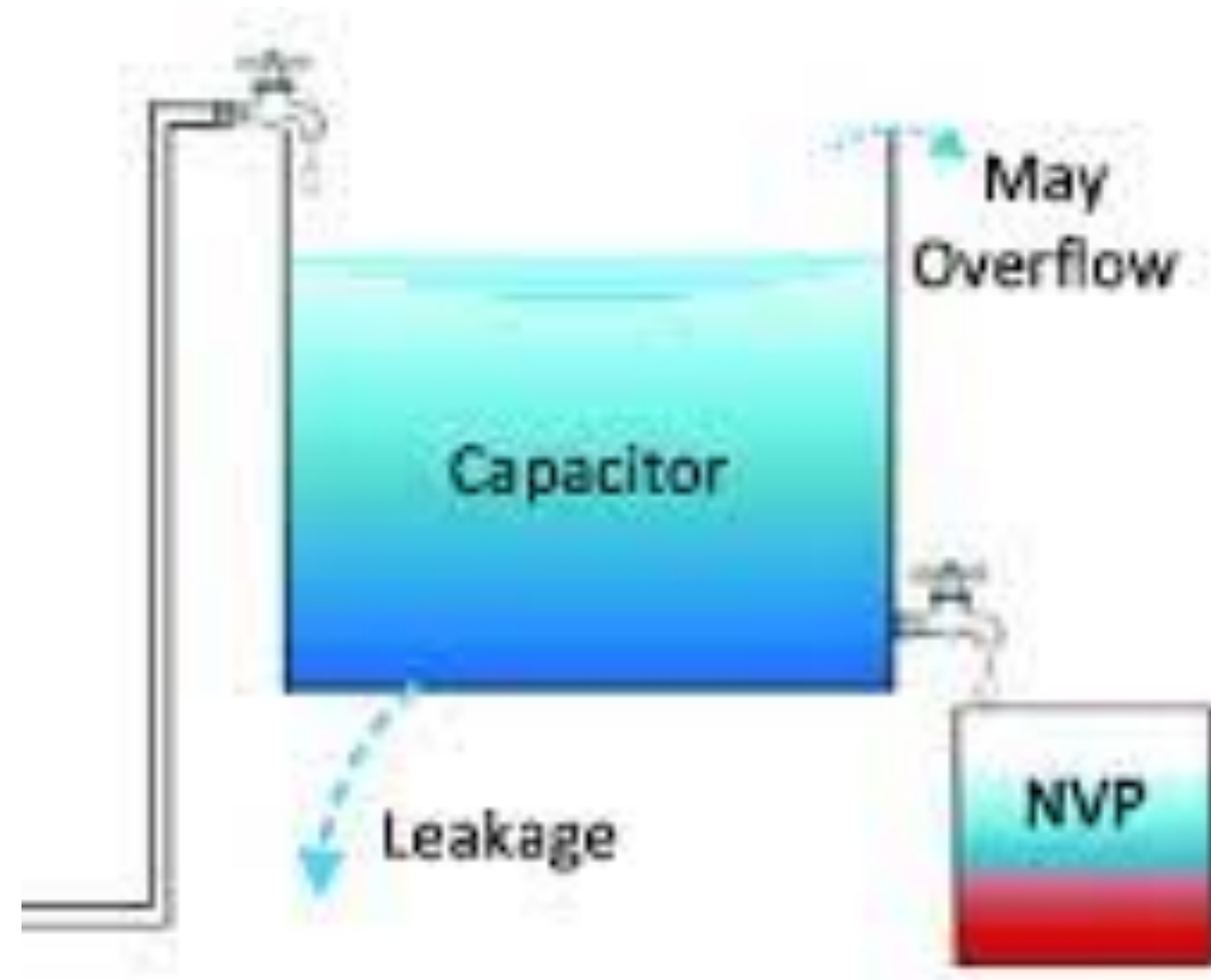

tank analogy

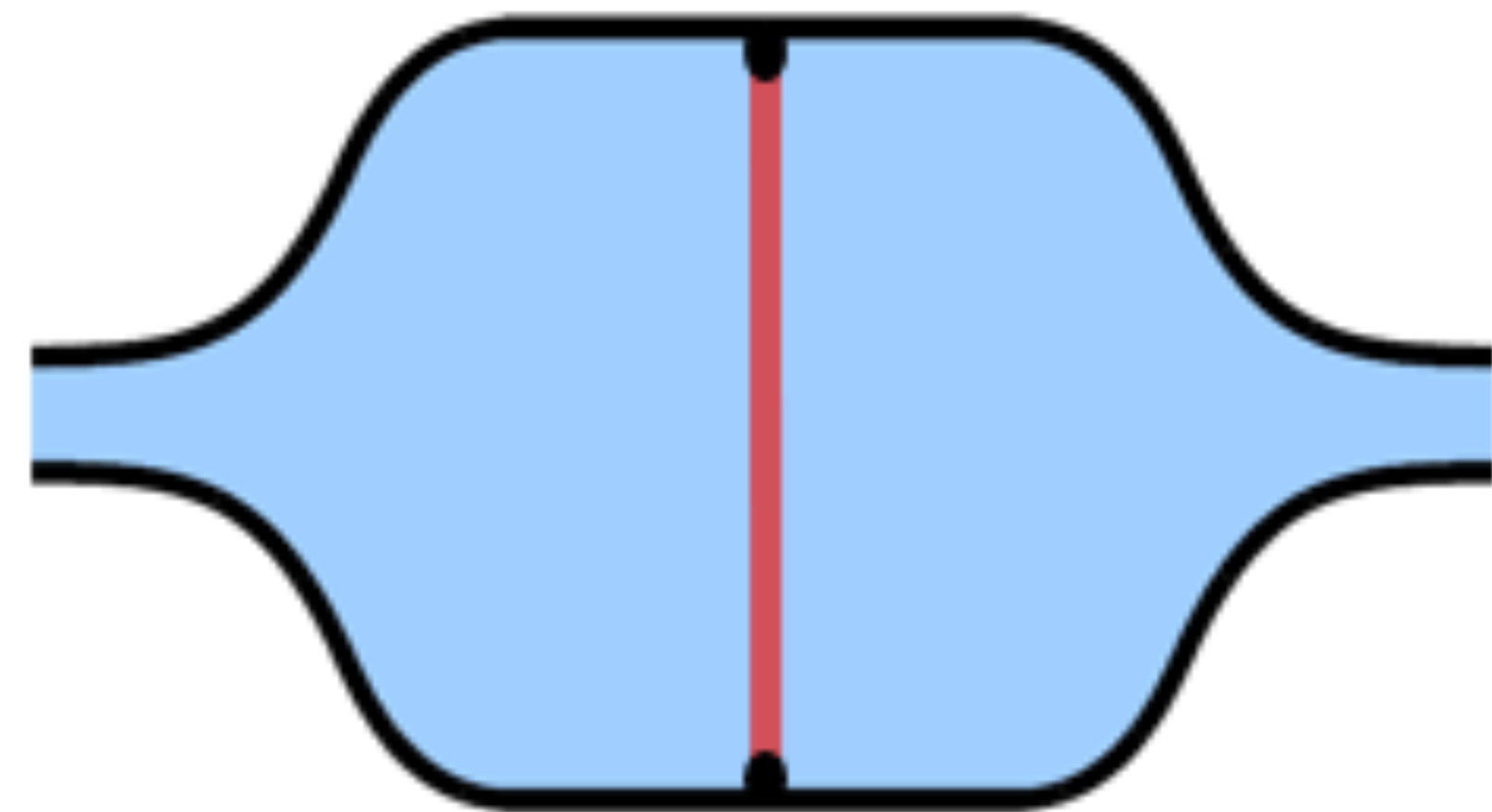


membrane analogy

Inductor: stores energy in the form of a magnetic field

→ coil windings which maintain magnetic field once established

$$V(t) = \frac{d\lambda}{dt}$$

Faraday's Law

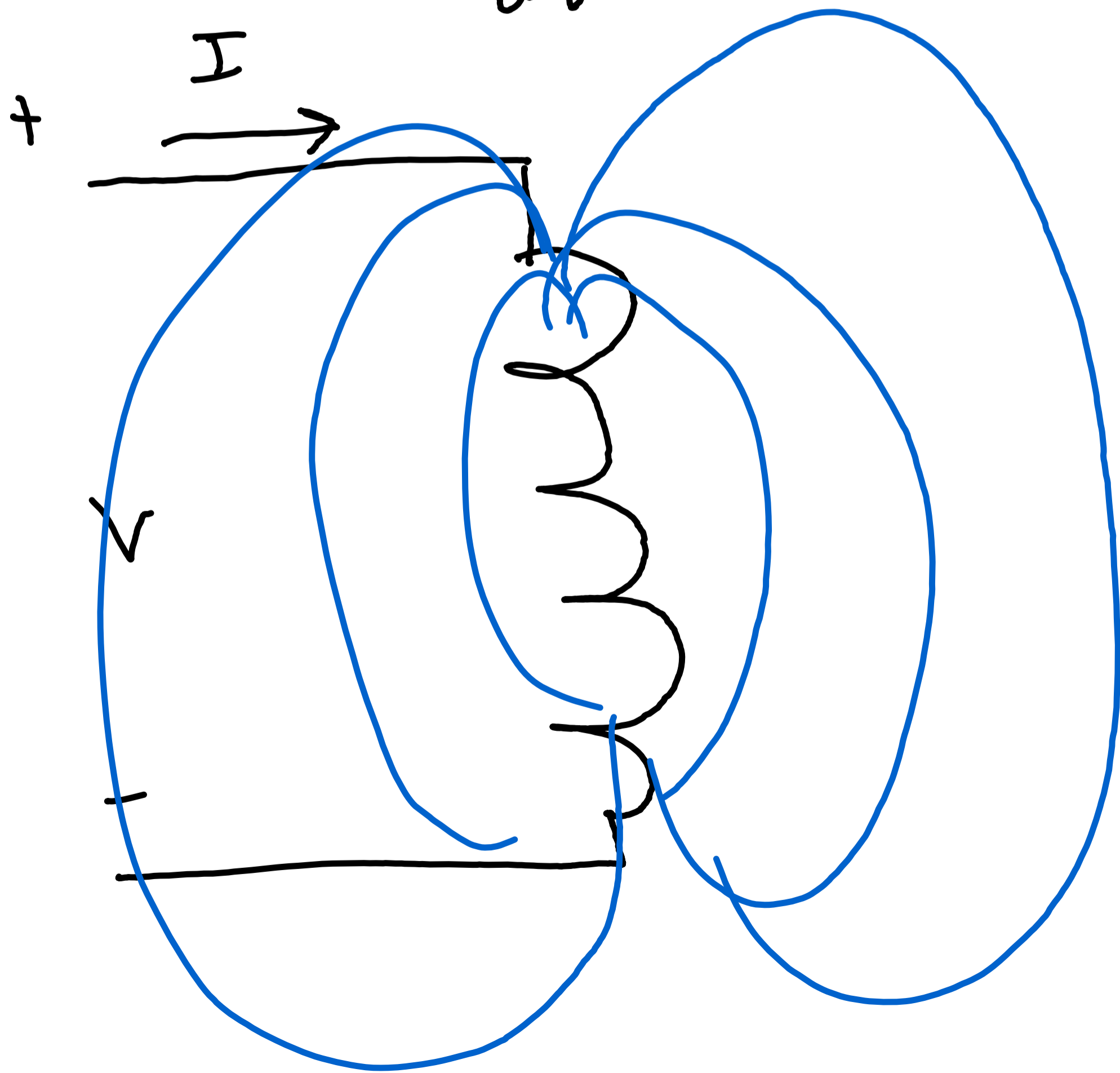

λ : magnetic flux


$$\lambda = L I$$

↑ inductance

$$V(t) = L \frac{dI}{dt} = L \dot{I}$$

Water Analogy for a inductor

Water Analogy for a inductor

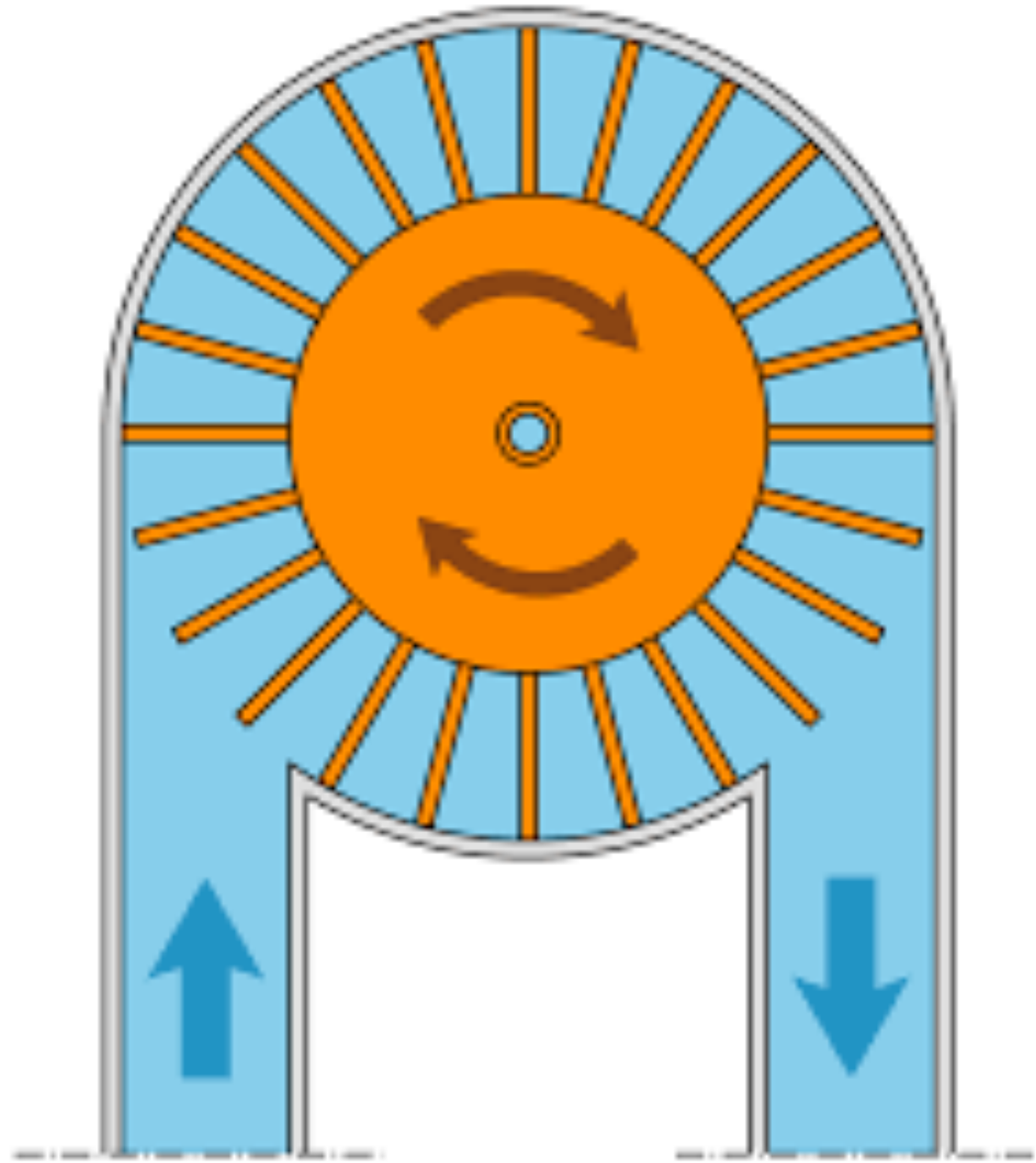


water wheels stores energy as inertia

Kirchhoff's voltage law (KVL)

Sum of voltages around a closed path is zero.


$$\sum_i^N V_i = 0$$

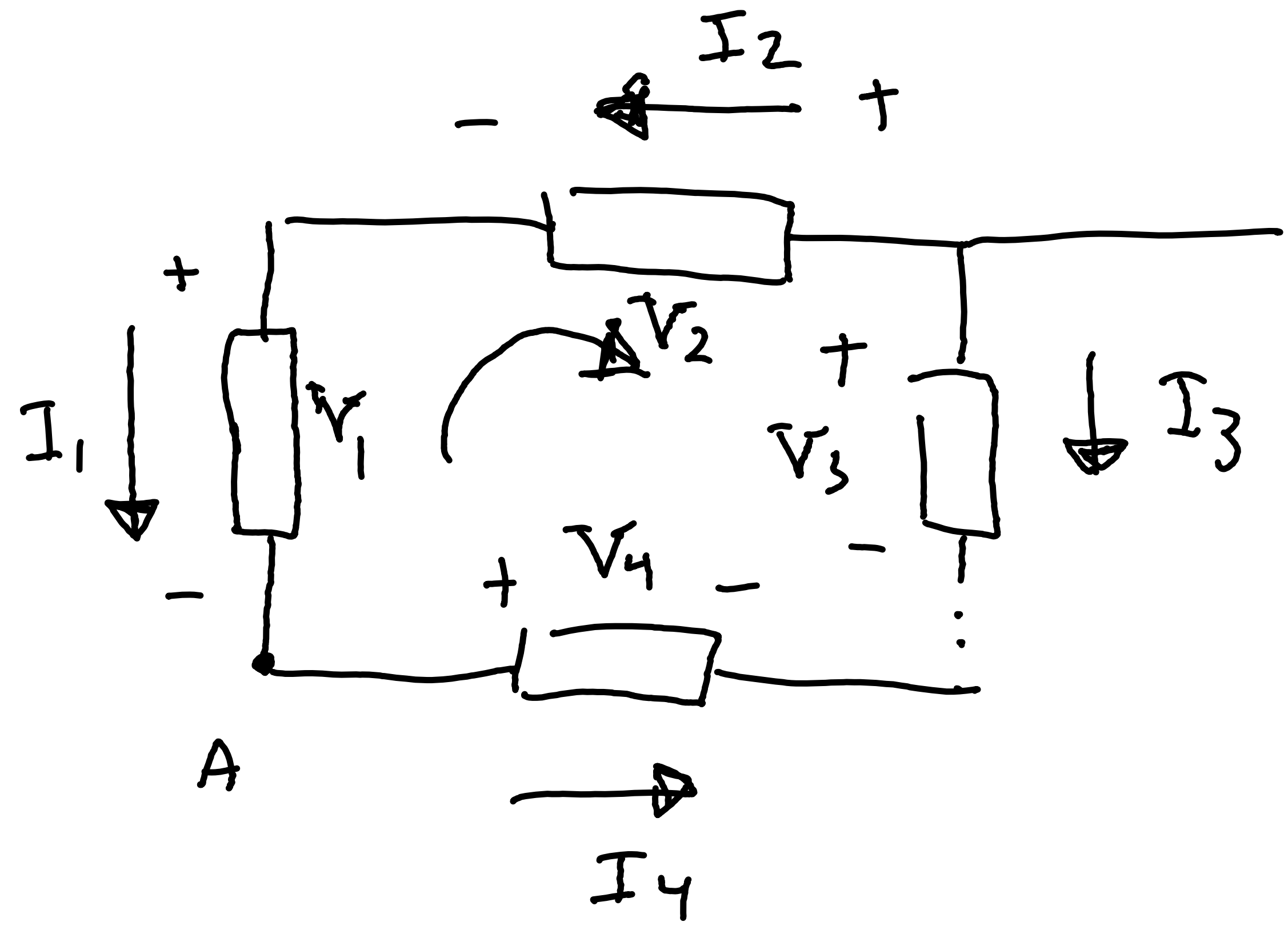

1. assume current direction
2. assign polarity
3. start loop from anywhere
4. sum all voltages


$$-V_1 - V_2 + V_3 + \dots + -V_y = 0$$

KVL Example (2.3 pg. 24)

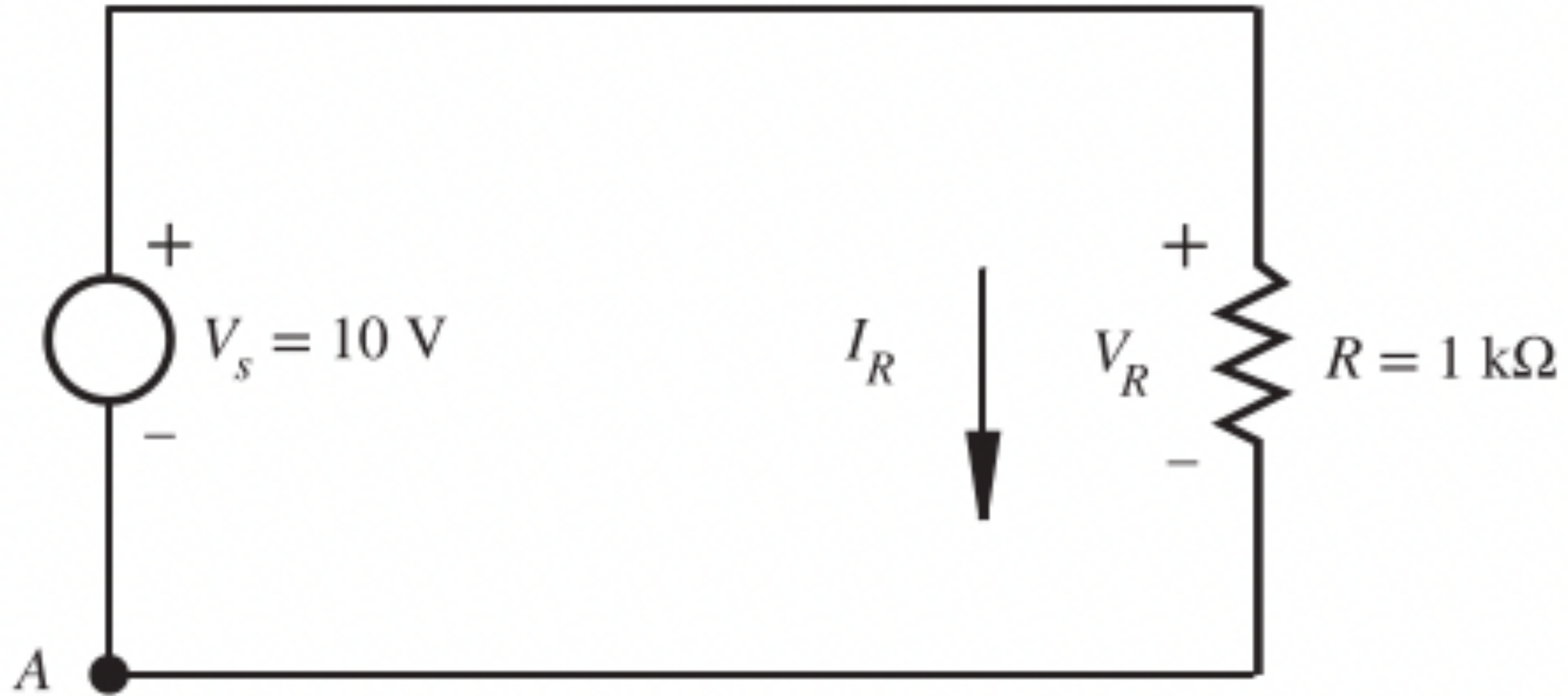

Find the current through the resistor.

KVL Example (2.3 pg. 24)

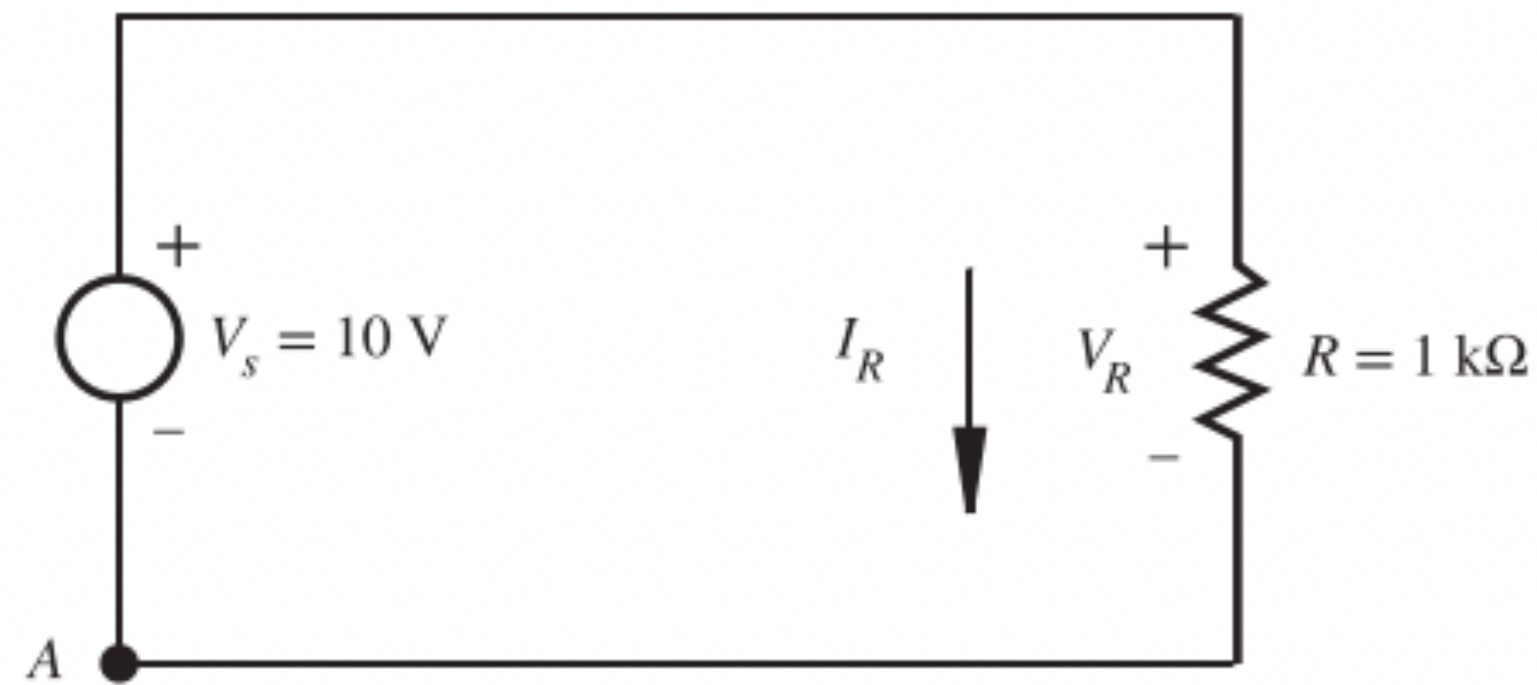

Find the current through the resistor.

$$\text{KVL: } -\bar{V}_s + \bar{V}_R = 0$$

$$\bar{V}_s = \bar{V}_R$$

$$I_R = \frac{V_s}{R} = \frac{10\text{ V}}{1\text{ k}\Omega}$$


$$= \underline{10\text{ mA}}$$

Kirchhoff's current law (KCL)

Sum of currents flow in/out of a node is

zero


$$\sum_i^N I_i = 0$$

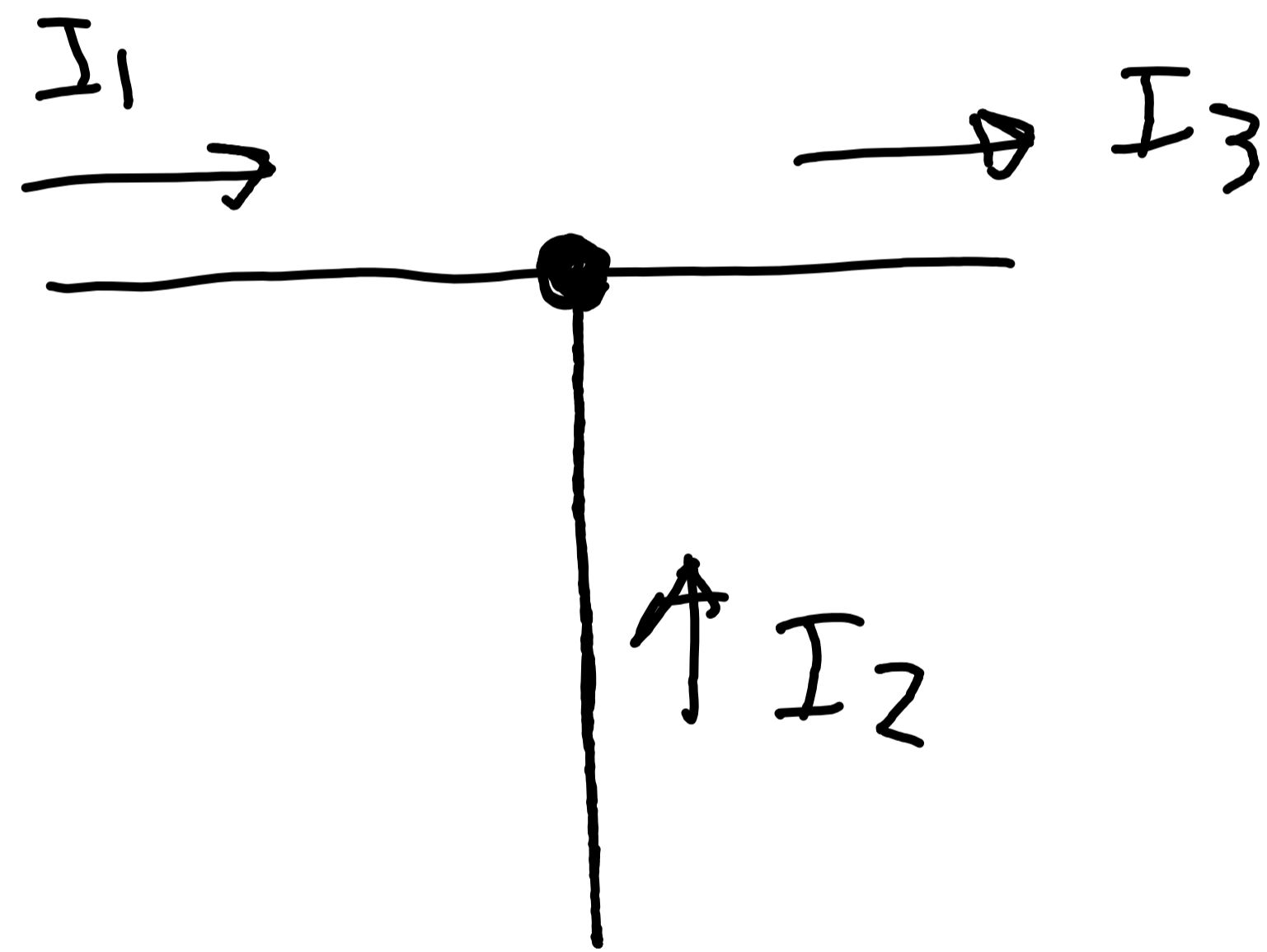

$$I_1 + I_2 = I_3$$


** often you must assume current direction. You have
assume voltage consistent with you current directions!
if after analysis the result are neg. that means
the result is opposite of your assumption.

Series Resistance

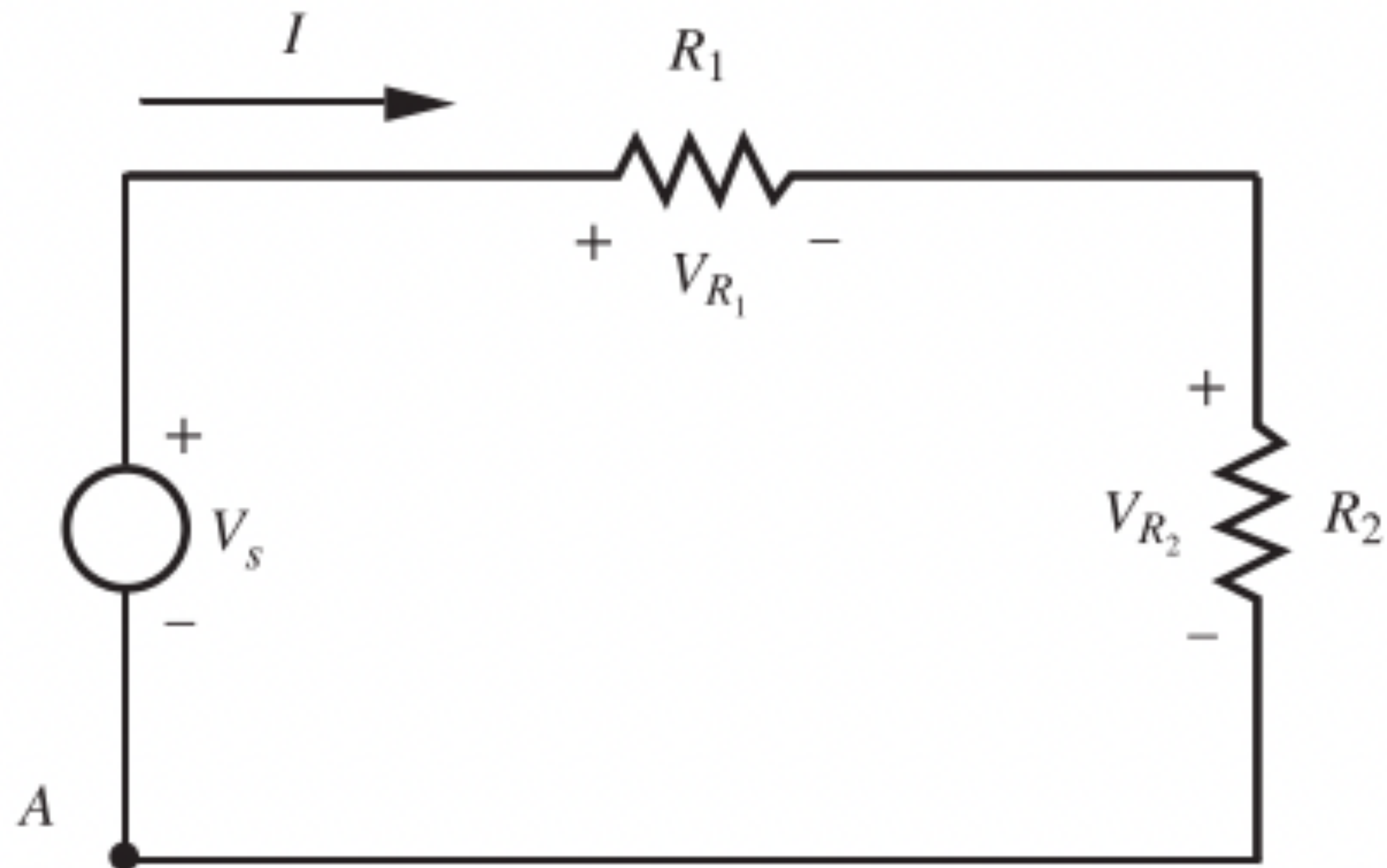

Find Req?

Series Resistance

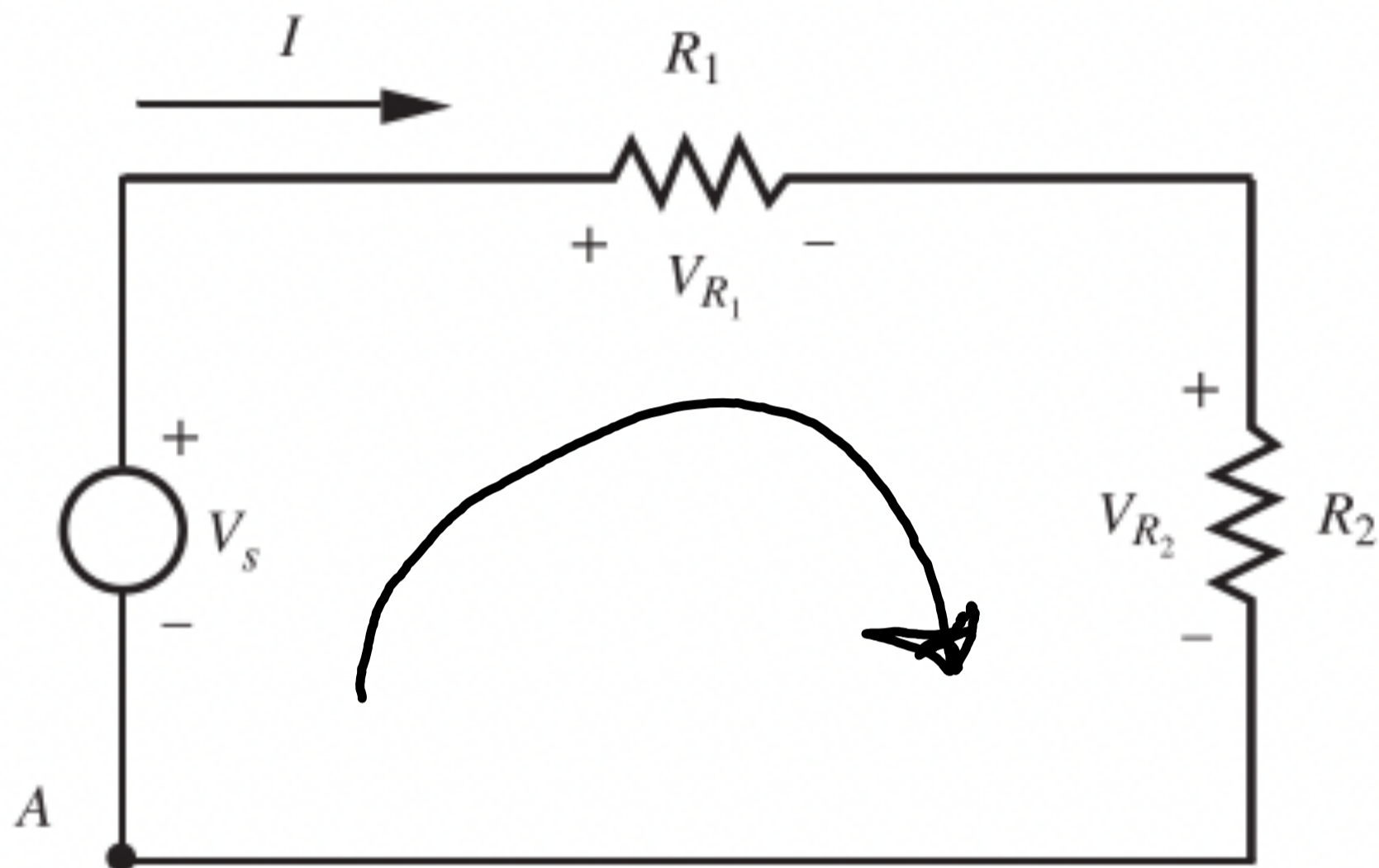

$$\text{KCL: } I = I_{R_1} = I_{R_2}$$

$$\text{KVL: } -V_s + V_{R_1} + V_{R_2} = 0$$

Ohm's
Law

$$V_{R_1} = IR_1$$


$$V_{R_2} = IR_2$$

$$-V_s + IR_1 + IR_2 = 0$$

$$V_s = (R_1 + R_2) I$$

Resistor in
series add!

Voltage Divider Circuit

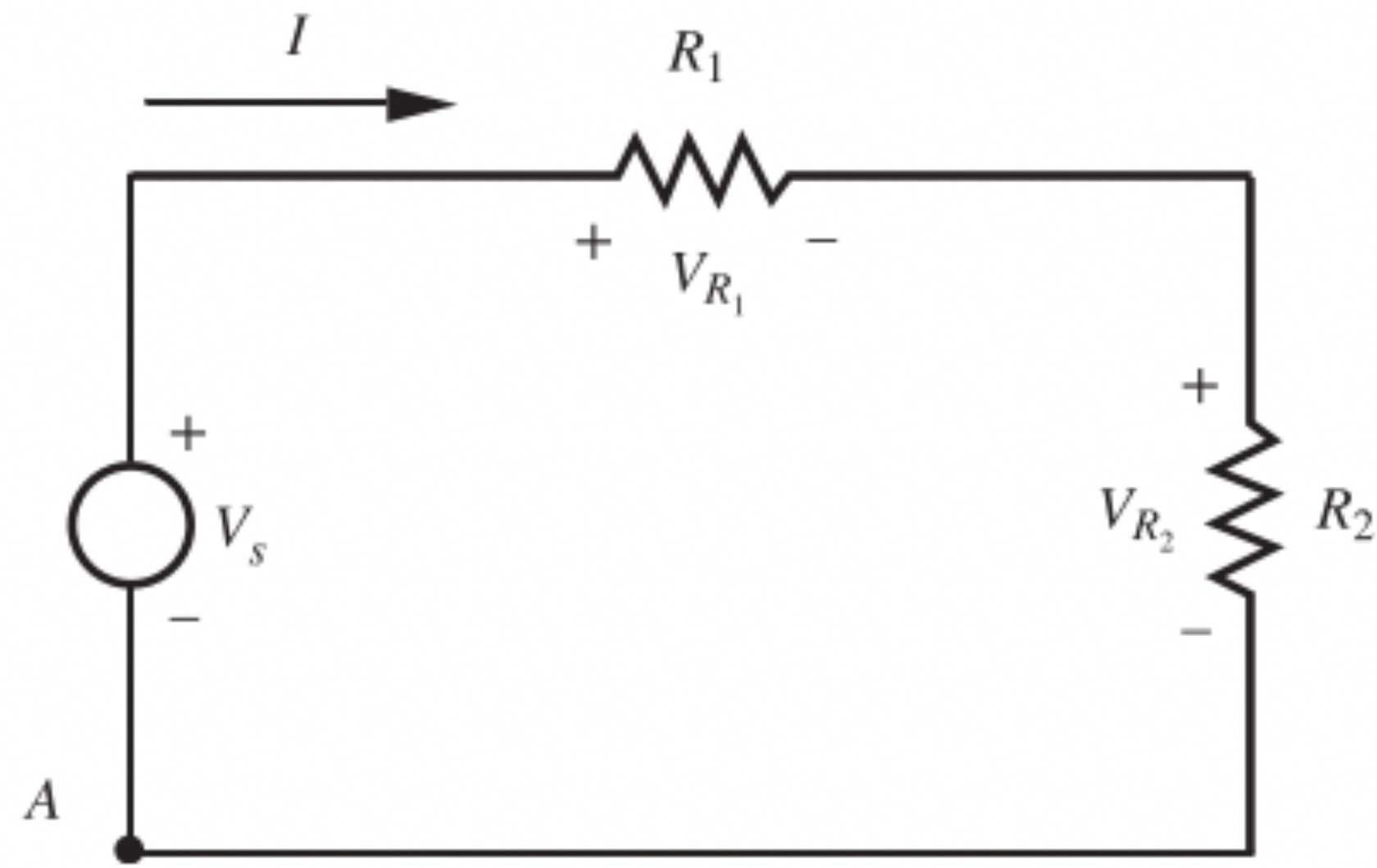

$$V_{R1} = \frac{R_1}{R_1 + R_2} V_s$$


$$V_{R2} = \frac{R_2}{R_1 + R_2} V_s$$

Why is this circuit useful?

> step down voltages

> simplest sensing circuit


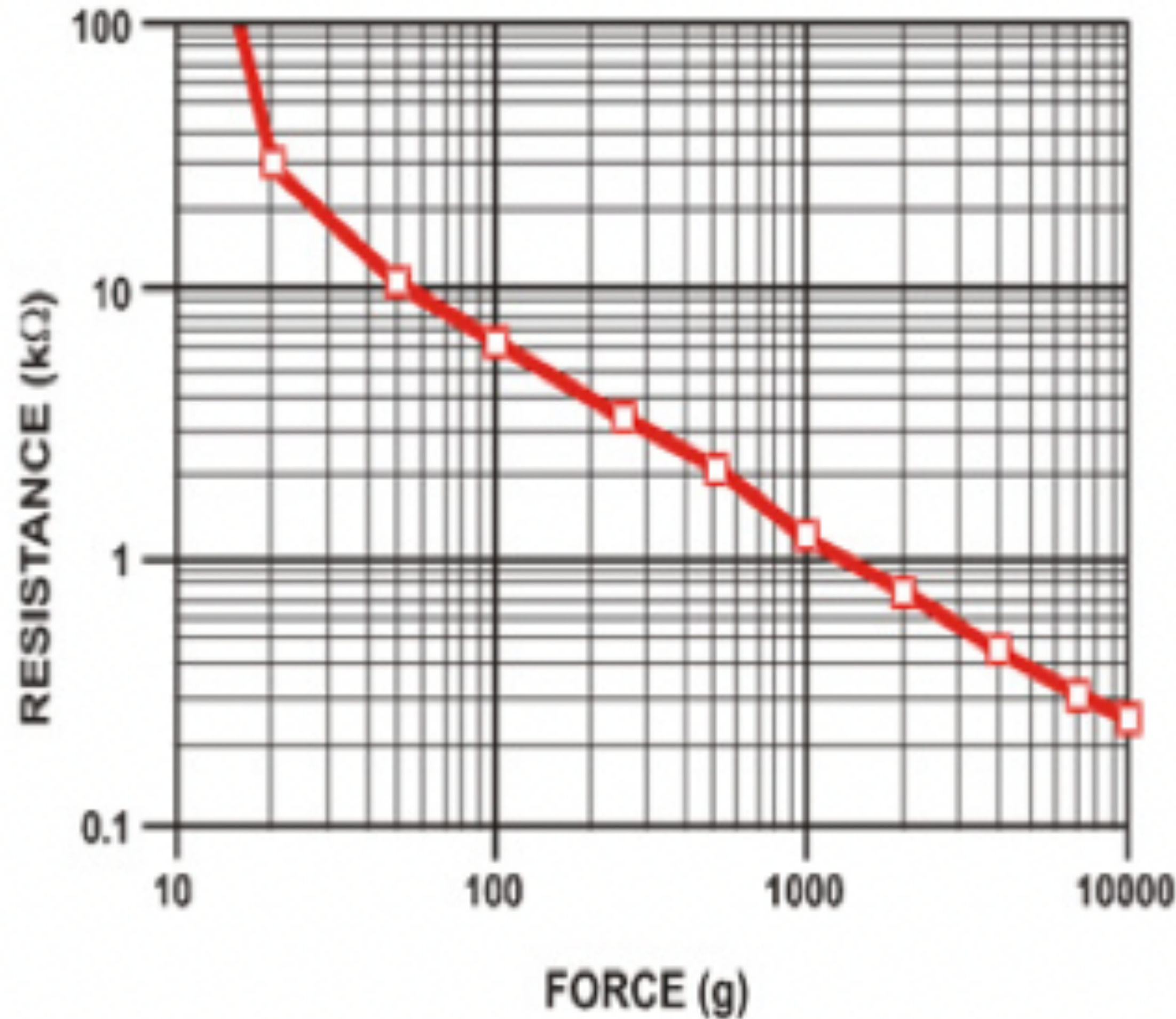
What if we have a sensor that changes a resistance with stimuli?



How can we
convert resistance
into something
we can measure
with a microcontroller
(Voltage!) ?



Force Sensitive Resistor

What if we have a sensor that changes a resistance with stimuli?

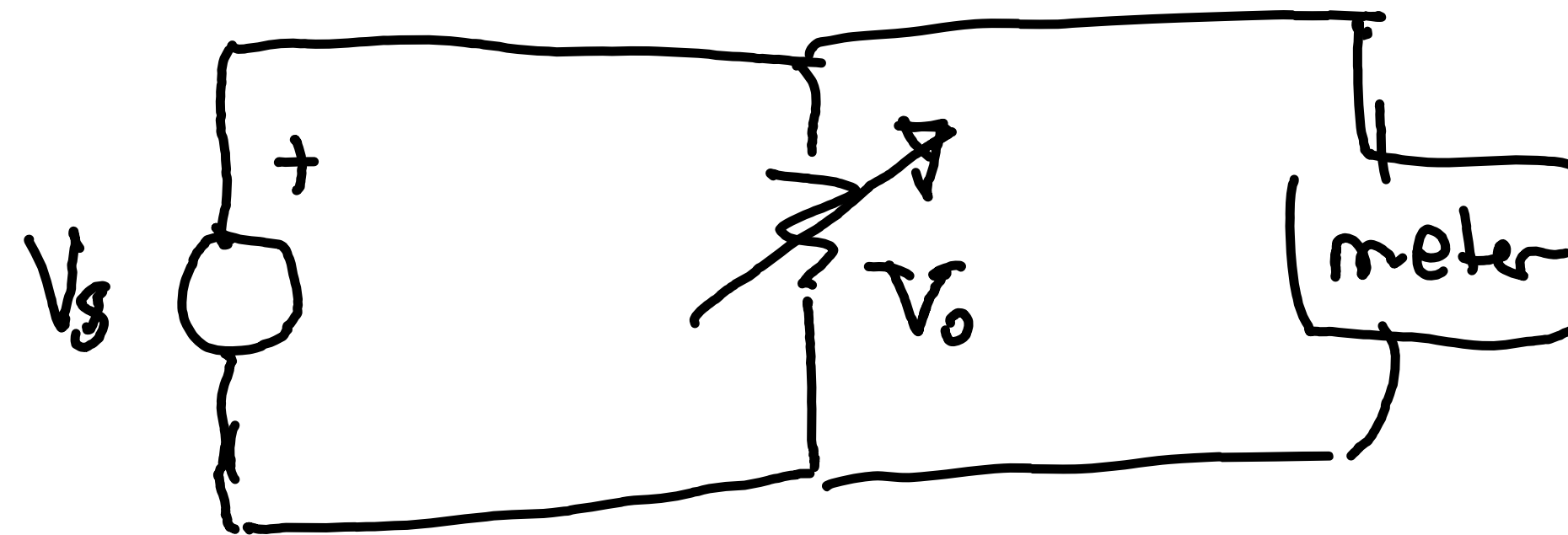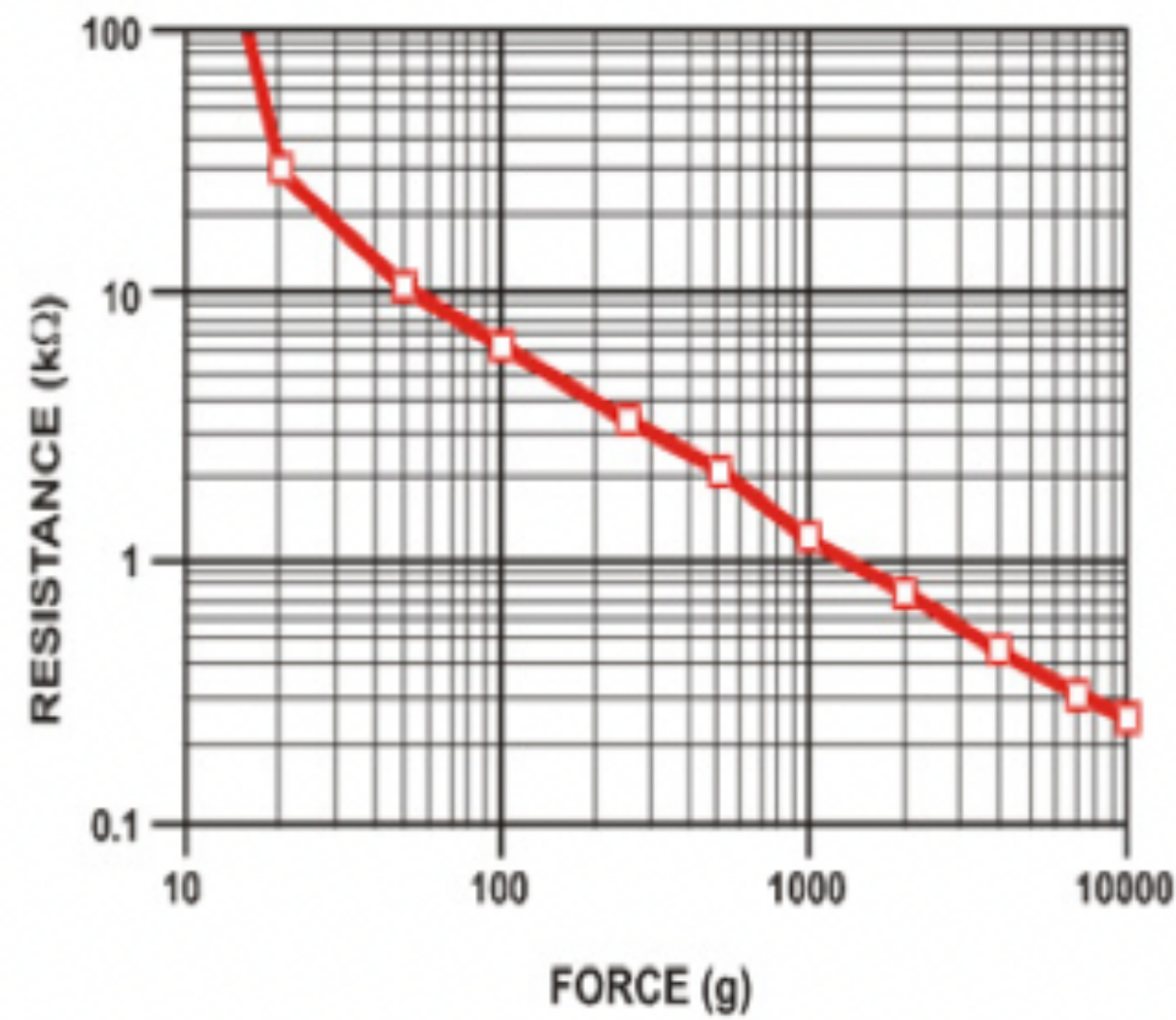


Idea 1: Would this work?

What if we have a sensor that changes a resistance with stimuli?

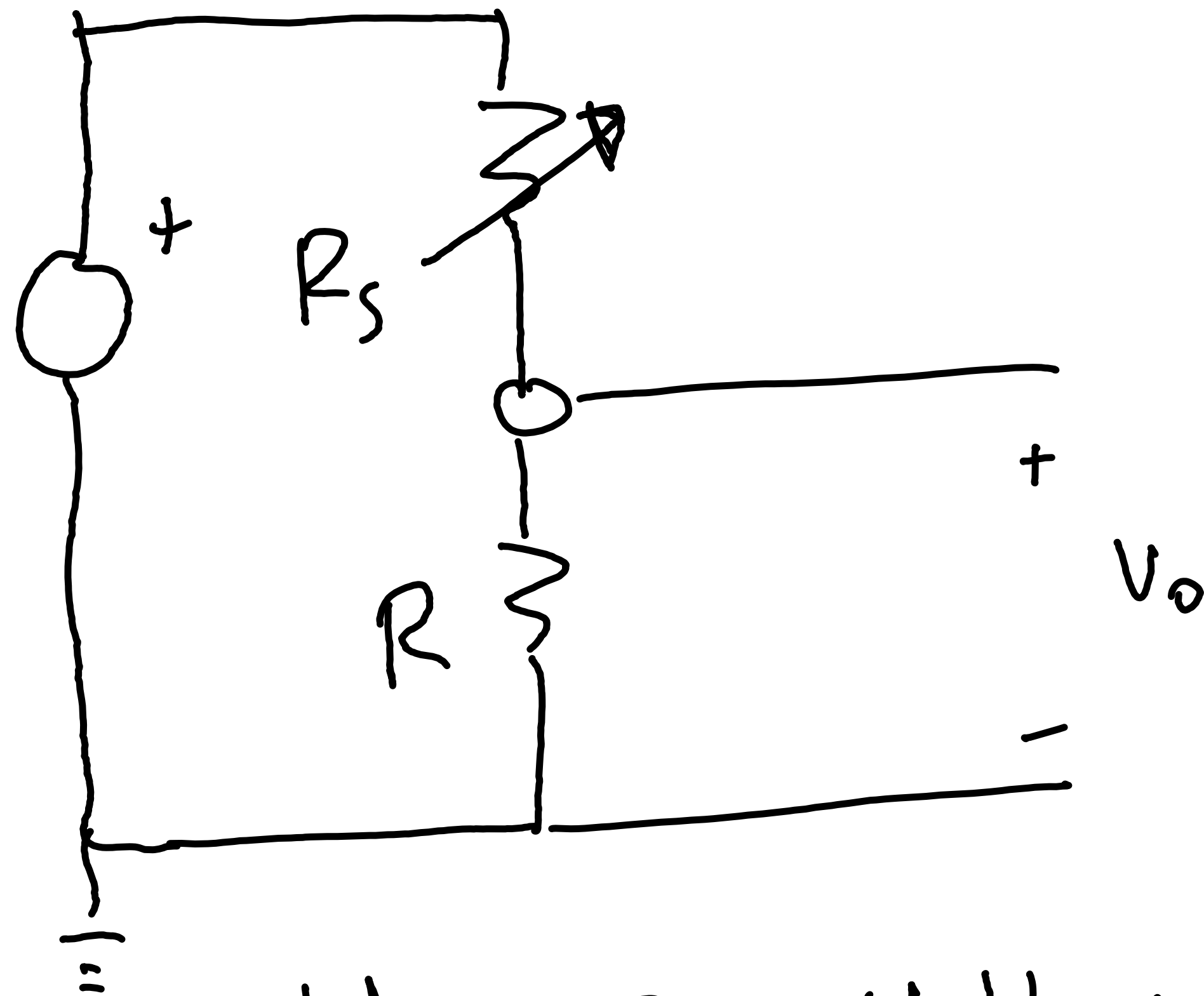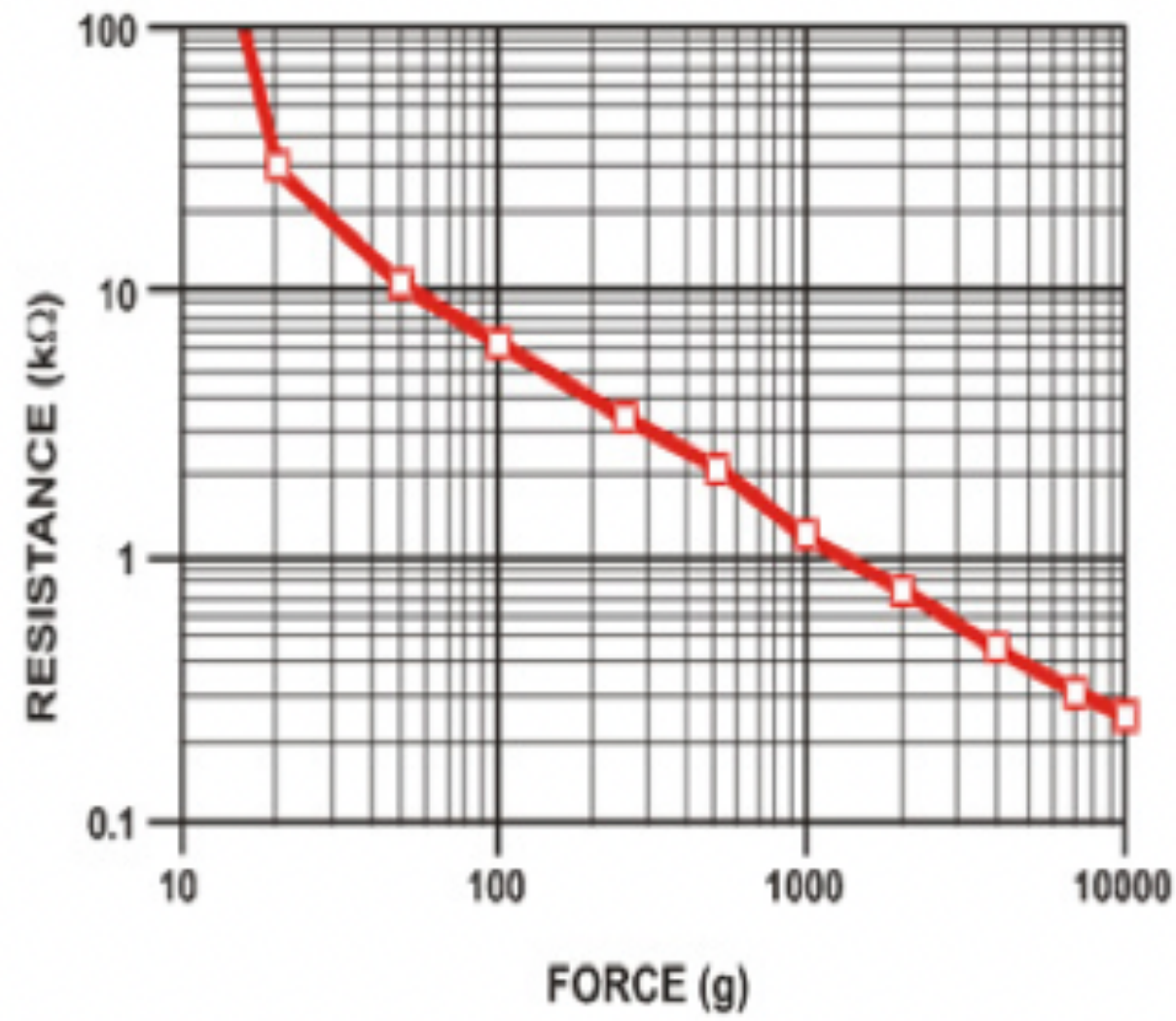

Idea 2: Voltage divider.

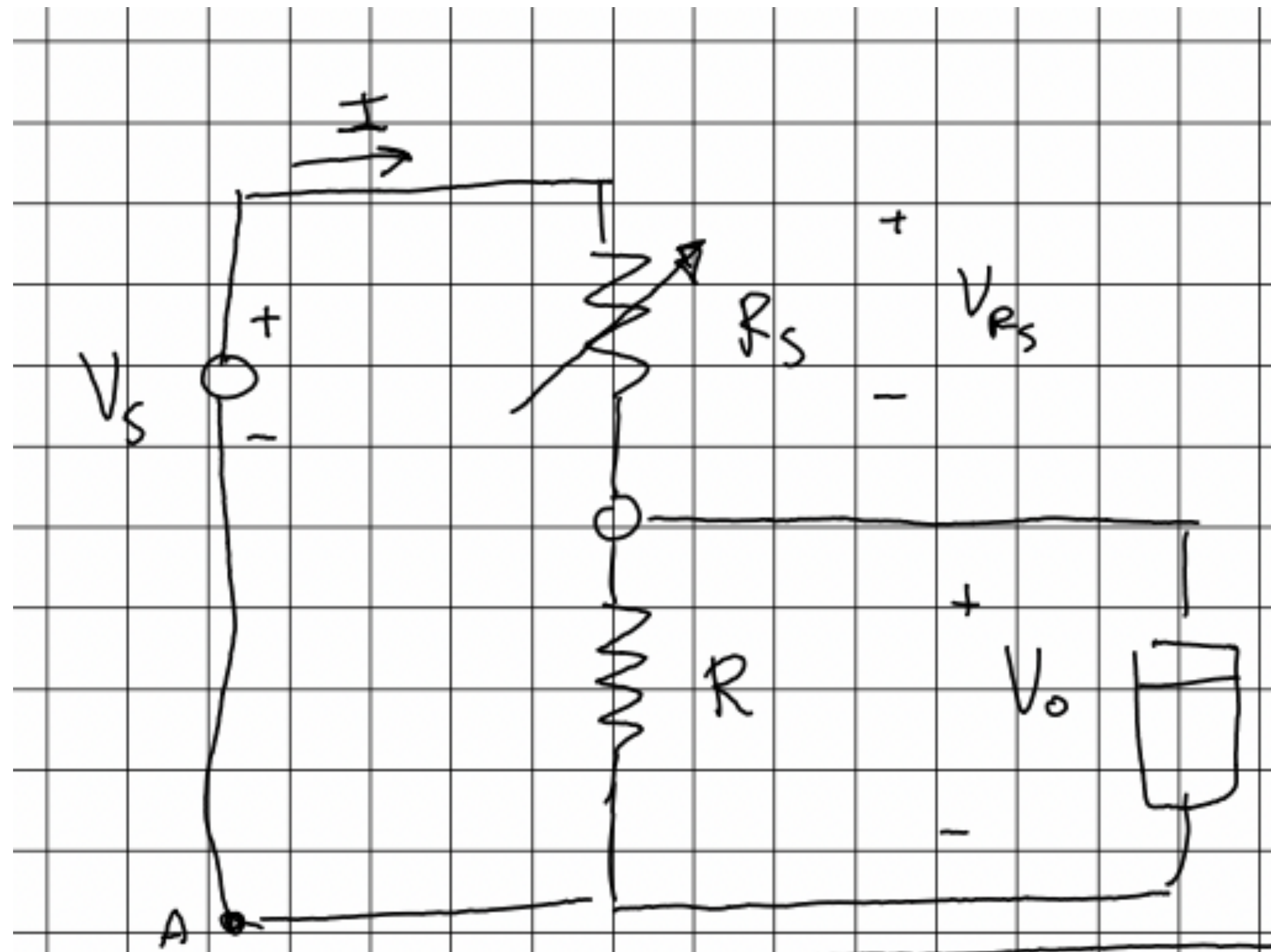What if we have a sensor that changes a resistance with stimuli?



$$\text{KCL: } \underline{I = I_{R_s} = I_R}$$

$$\text{KVL: } -V_s + V_{R_s} + V_o = 0$$


$$V_s = V_{R_s} + V_o$$

$$= I R_s + I R = I (R_s + R)$$


$$I = \frac{V_o}{R} \Rightarrow$$

$$\boxed{\frac{R}{R_s + R} V_s = V_o}$$

Let's look at the limits:

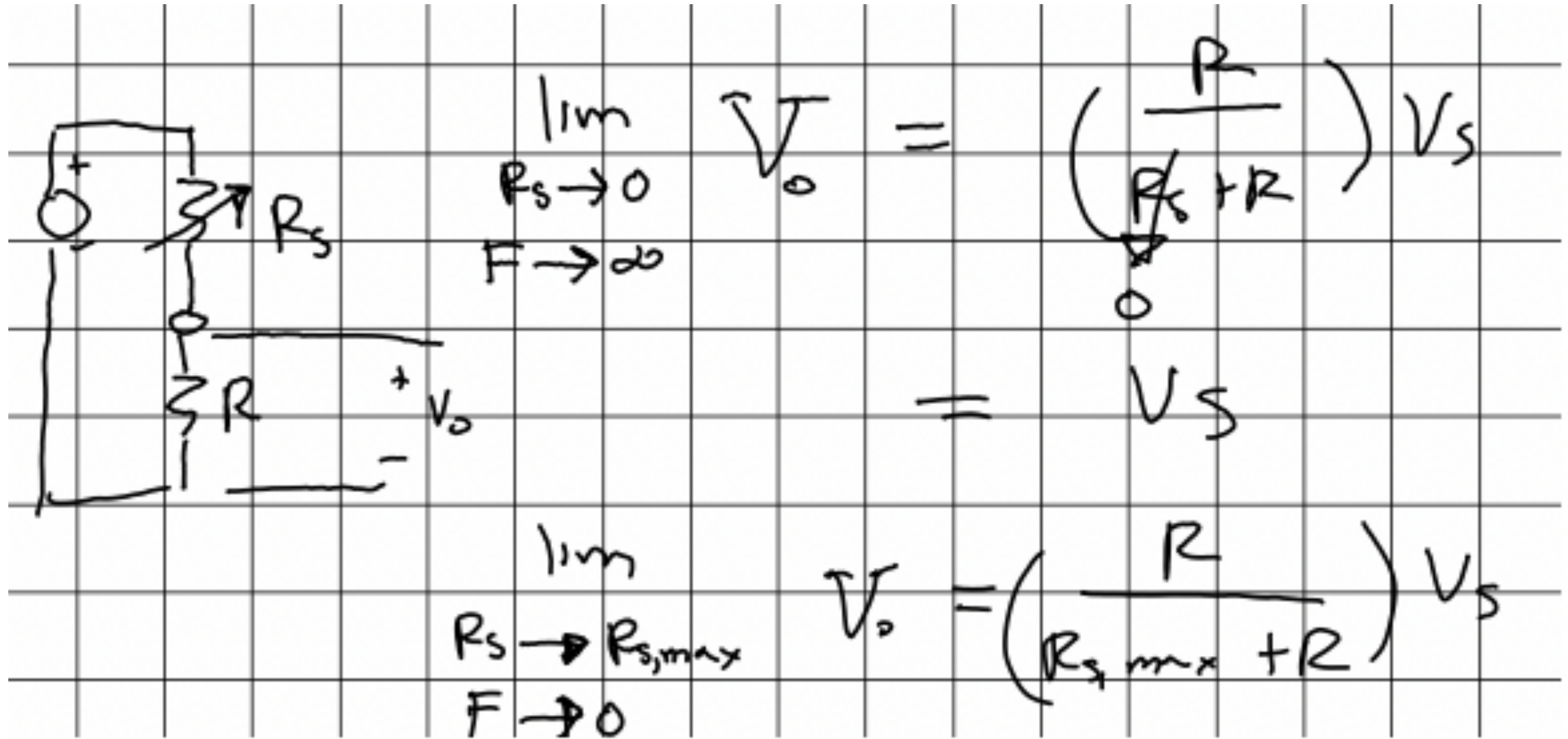

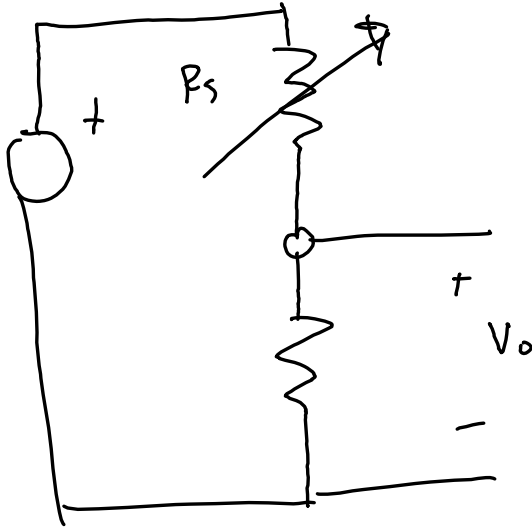
$$V_o = \left(\frac{R}{R_s + R} \right) V_s$$



$$\lim_{\substack{R_s \rightarrow 0 \\ F \rightarrow \infty}} \left(\frac{R}{R_s + R} \right) V_s = V_s$$

$$\lim_{\substack{R_s \rightarrow R_{s, \max} \\ F \rightarrow 0}} \left(\frac{R}{R_s + R} \right) V_s = 0$$

$$R_{s, \max} \gg R$$

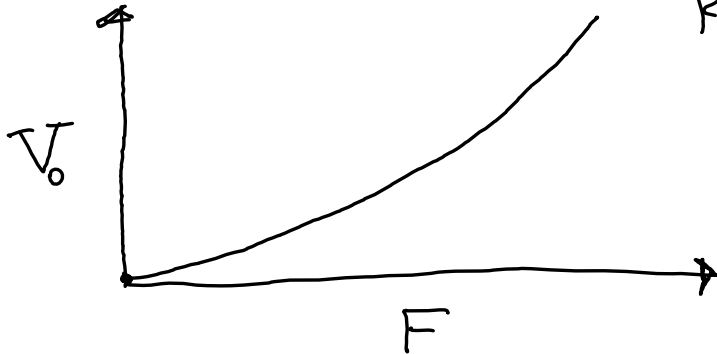

* multimeter
test on 1

Now we can *sample* the voltage from the voltage divider, which is proportional to the force

