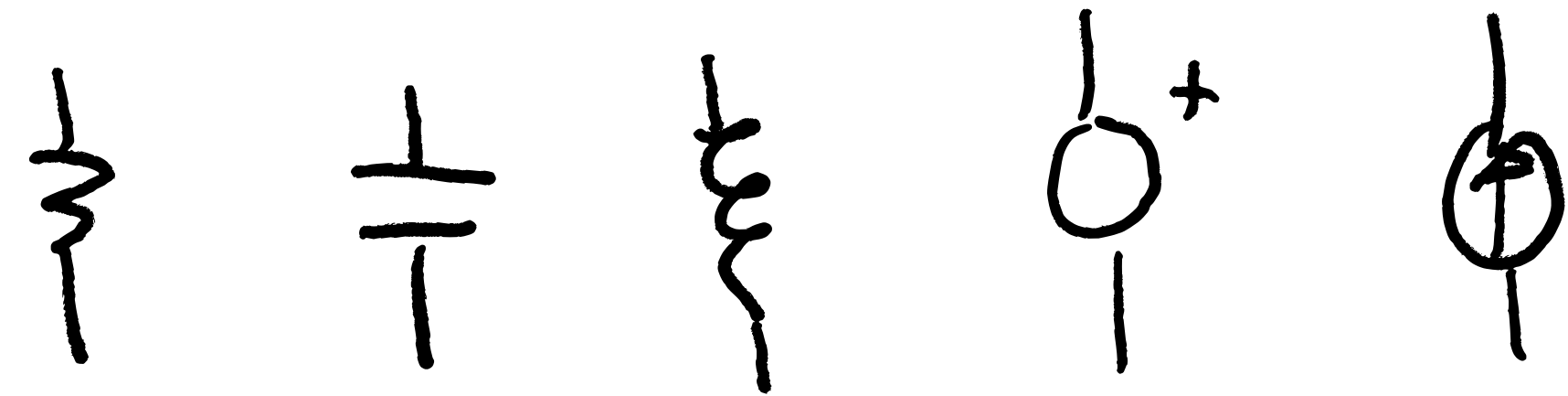


# ME133 Lecture 3

1/17/23  
~~1/12/23~~

Last time:


→ passive electrical elements



→ Ohm's Law  $V = IR$

Kirchoff's Laws

→ Voltage Divider

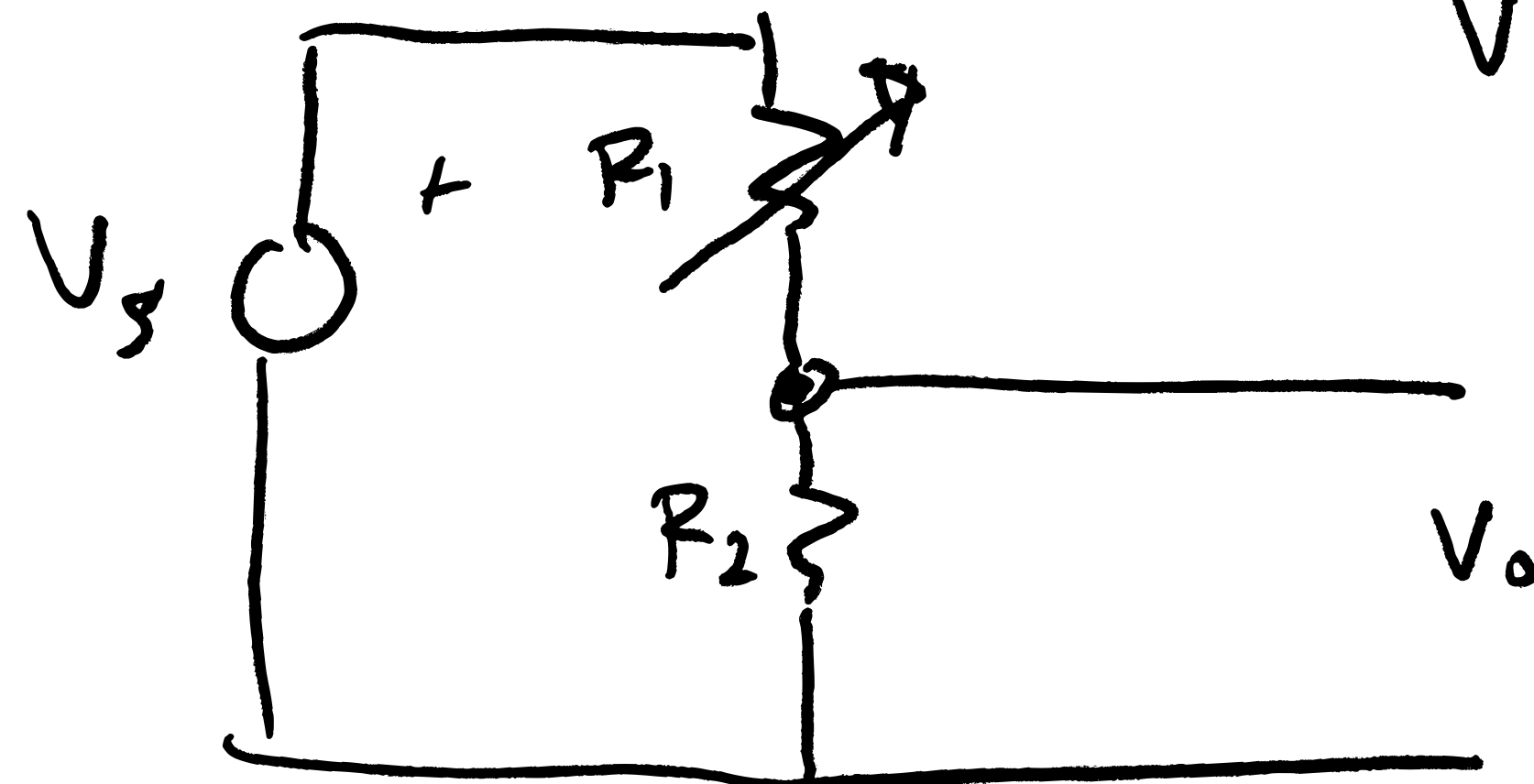

$$V_o = \left( \frac{R_2}{R_1 + R_2} \right) V_s$$


Today:

- Equivalent Series + Parallel circuits
- Sources ; meters
- Thevenin ; Norton Equivalent circuits
- Power
- Impedance

## ■ CLASS DISCUSSION ITEM 2.6
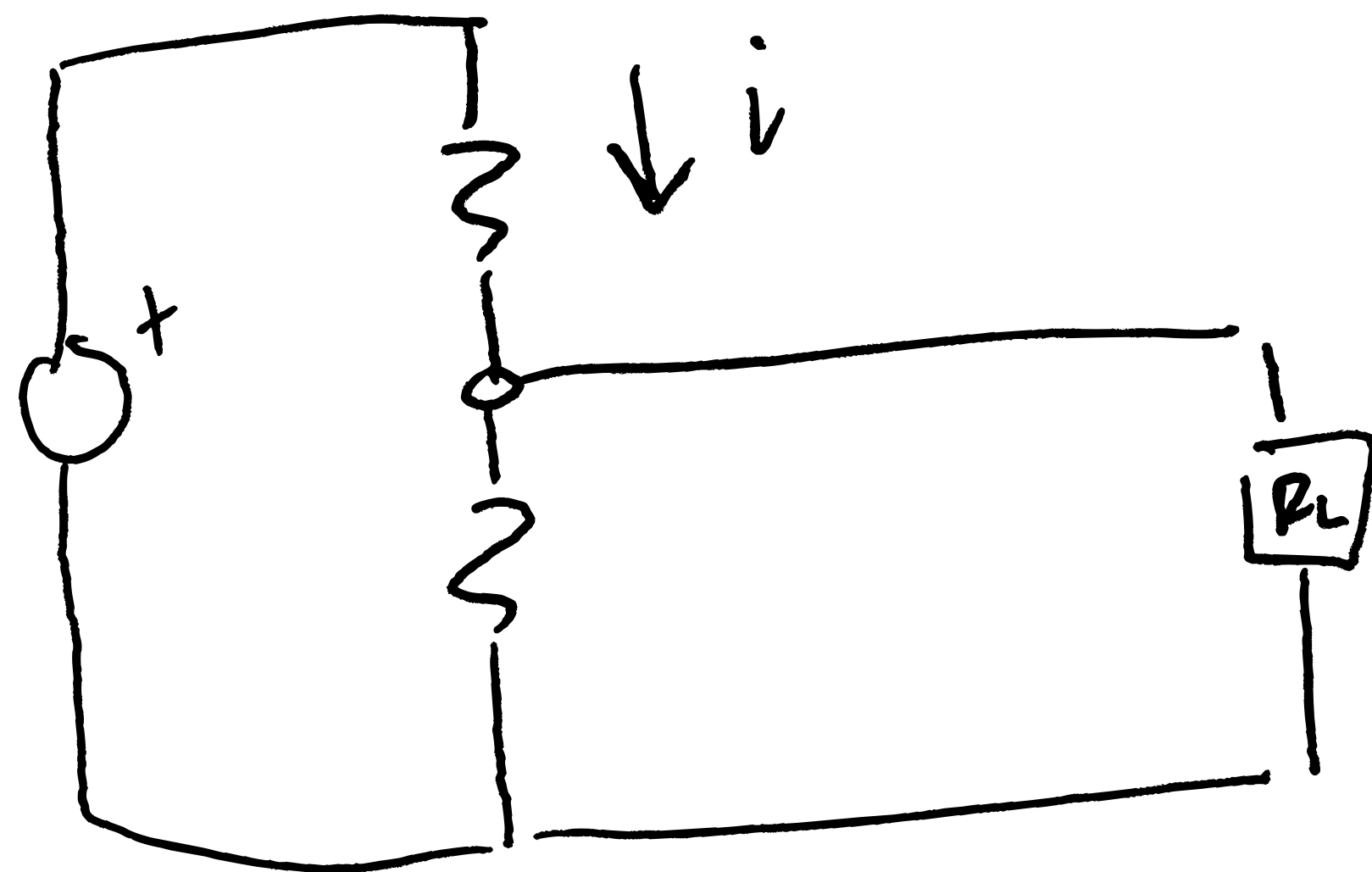
### *Improper Application of a Voltage Divider*


Your car has a 12 V battery that powers some circuits in the car at lower voltage levels. Why is it inappropriate to use a simple voltage divider to create a lower voltage level for circuits that might draw variable current?



→ load will mess up the  
voltage divider

"Load effect"

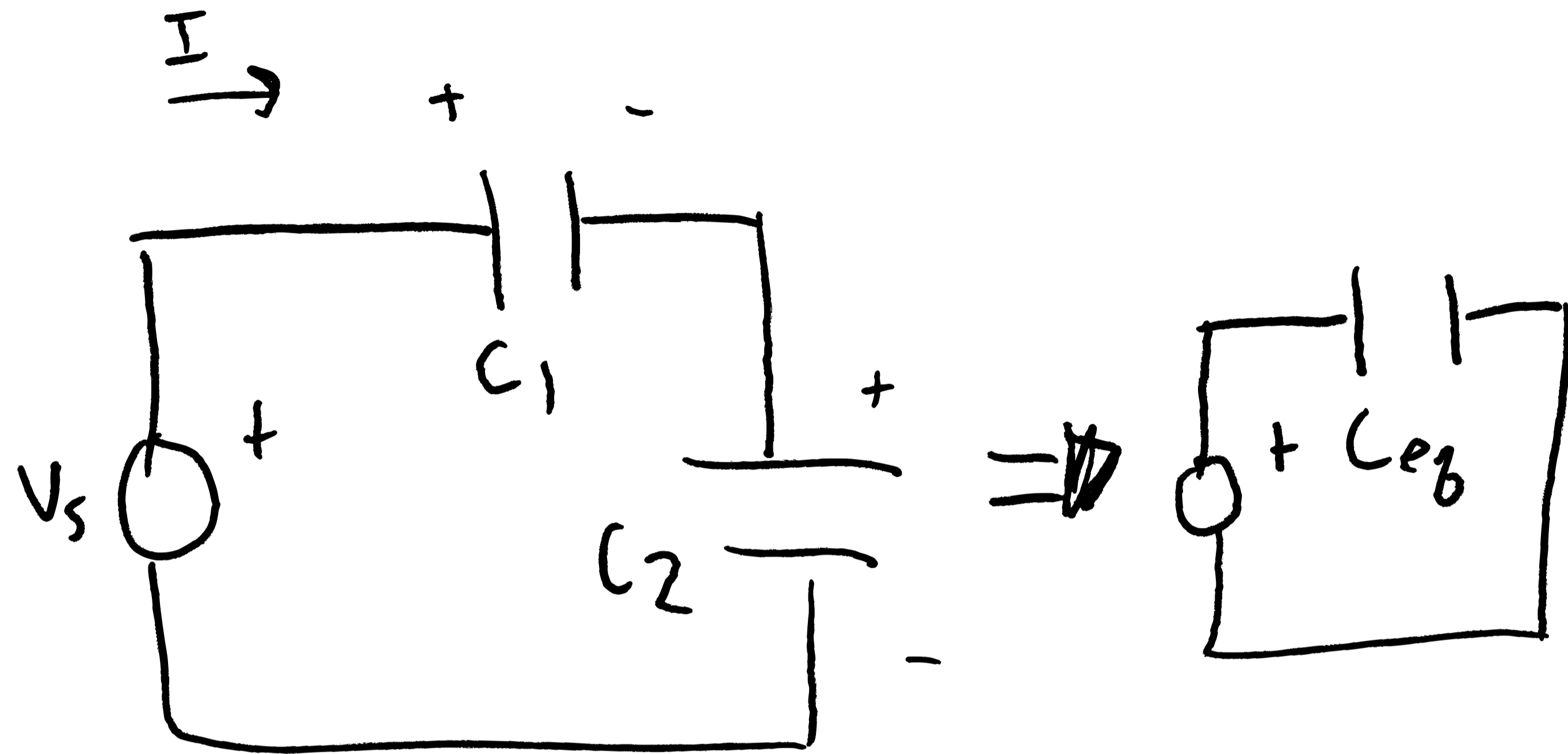Series capacitance: Find the equivalent capacitance



Find  $C_{eq}$ ?

KVL:  $V_s = V_1 + V_2$

$$I = C \dot{V}$$

$$\dot{V}_s = \dot{V}_1 + \dot{V}_2$$


$$\dot{V}_s = \frac{I_1}{C_1} + \frac{I_2}{C_2}$$

KCL:  $I = I_1 = I_2$

$$\dot{V}_s = \underbrace{\left( \frac{1}{C_1} + \frac{1}{C_2} \right)}_{\frac{1}{C_{eq}}} I$$

$$\therefore C_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}}$$

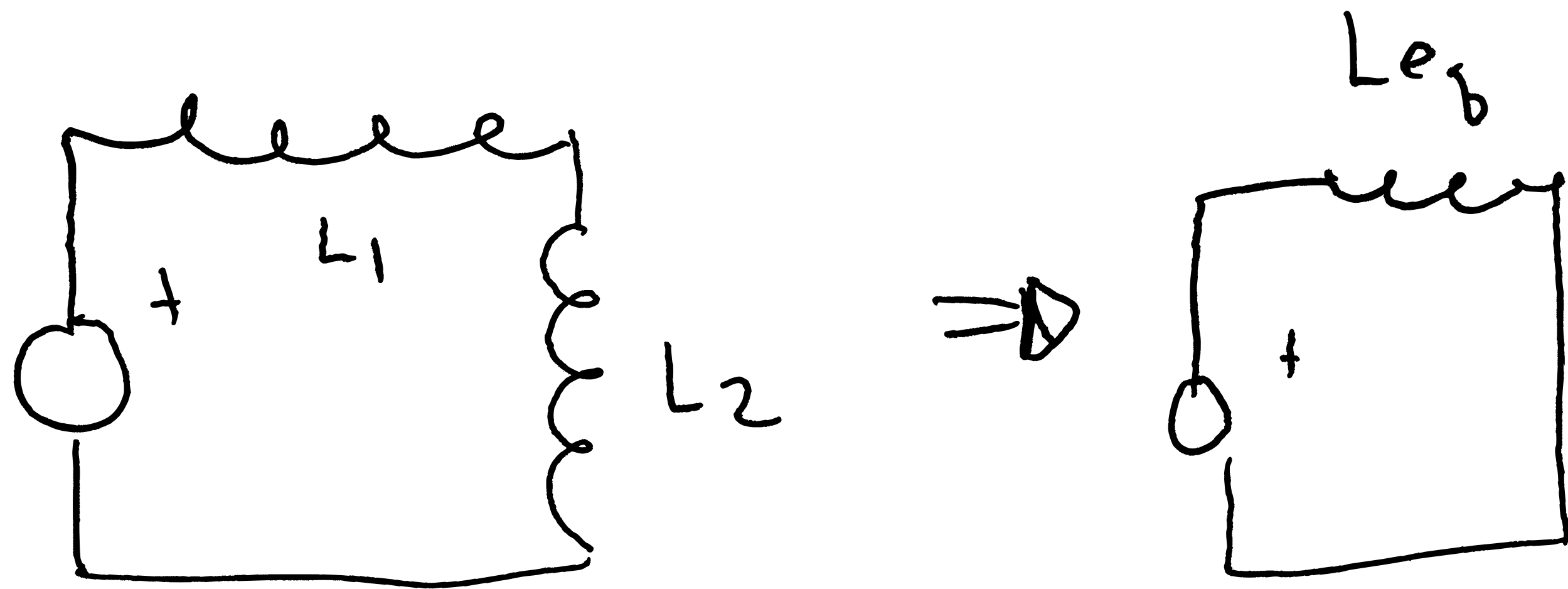Series inductance: Find the equivalent inductance




$$V = L \dot{I}$$
$$V = \underbrace{(L_1 + L_2)}_{L_{eq}} \dot{I}$$

$$\text{KVL: } V_s = V_1 + V_2$$

$$\text{KCL: } I = I_1 = I_2$$
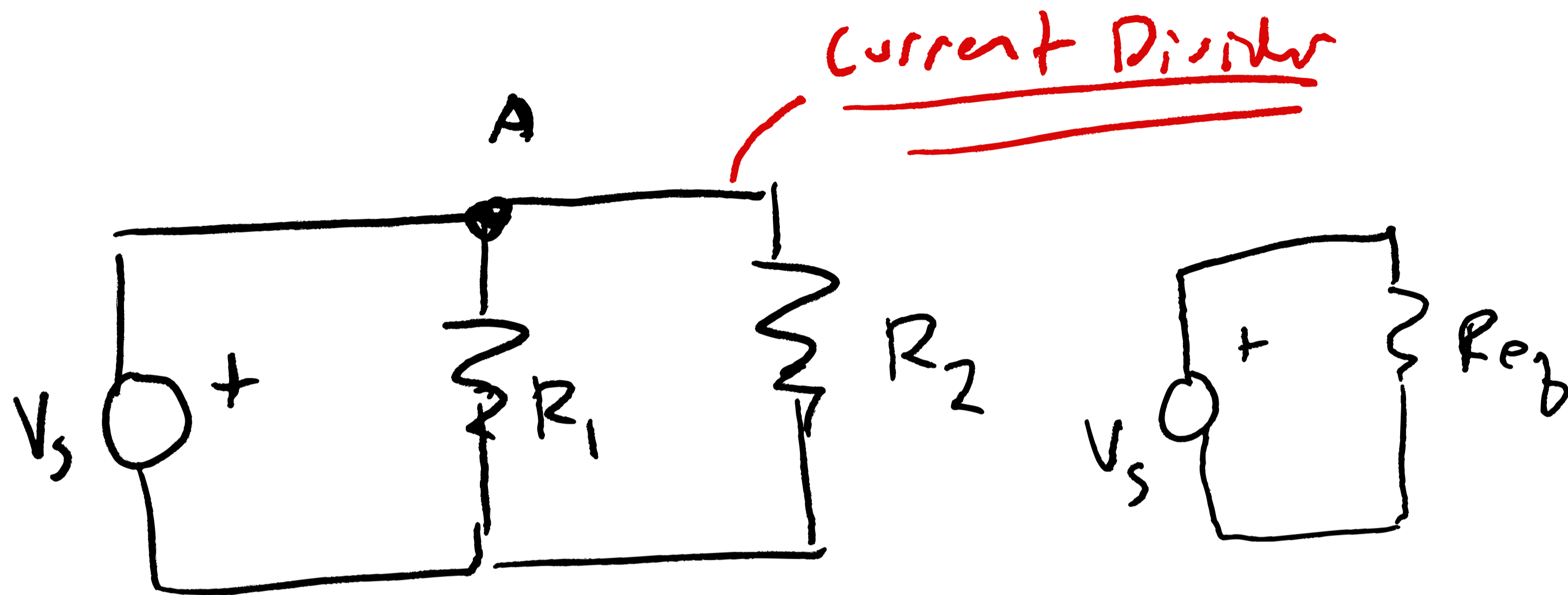
# Parallel resistance: Find the equivalent resistance



$$\text{KVL: } V_s = V_{R_1} = V_{R_2}$$

$$\text{KCL: } I = I_{R_1} + I_{R_2}$$

$$V = IR$$

$$I = I_{R_1} + I_{R_2}$$


→ Ohm's Law

$$I = \frac{V_{R_1}}{R_1} + \frac{V_{R_2}}{R_2}$$


$$I = \left( \frac{1}{R_1} + \frac{1}{R_2} \right) V_s$$

$$\frac{1}{R_{eq}} = \frac{R_1 + R_2}{R_1 R_2}$$

# Capacitors and Inductors in parallel

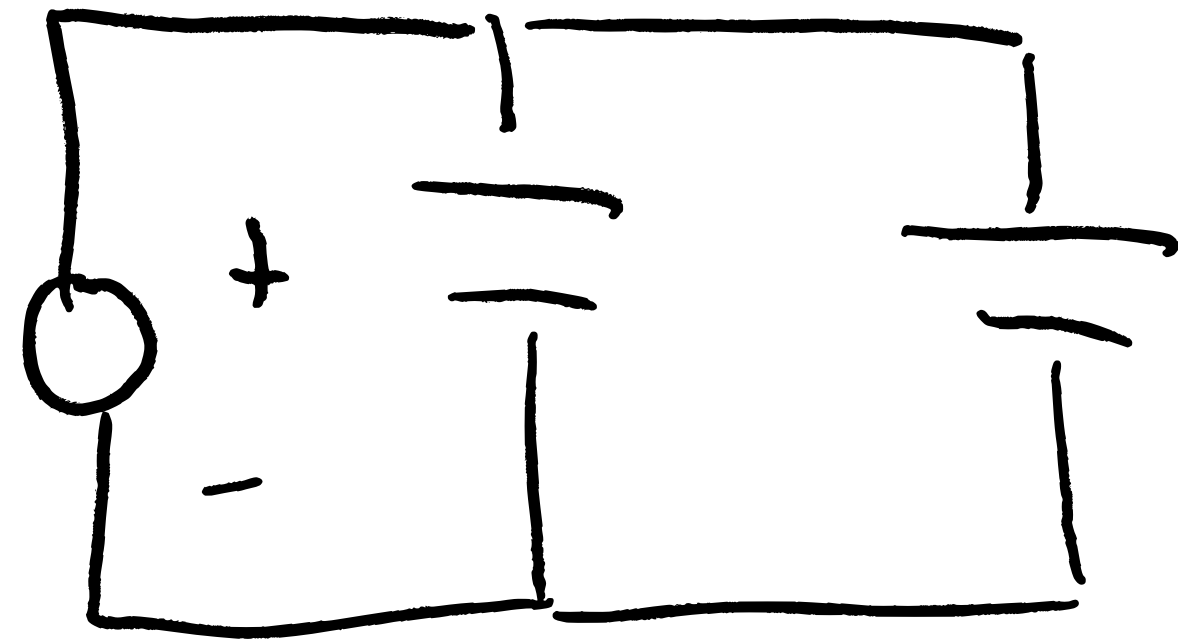


$$C_{eq} = C_1 + C_2$$

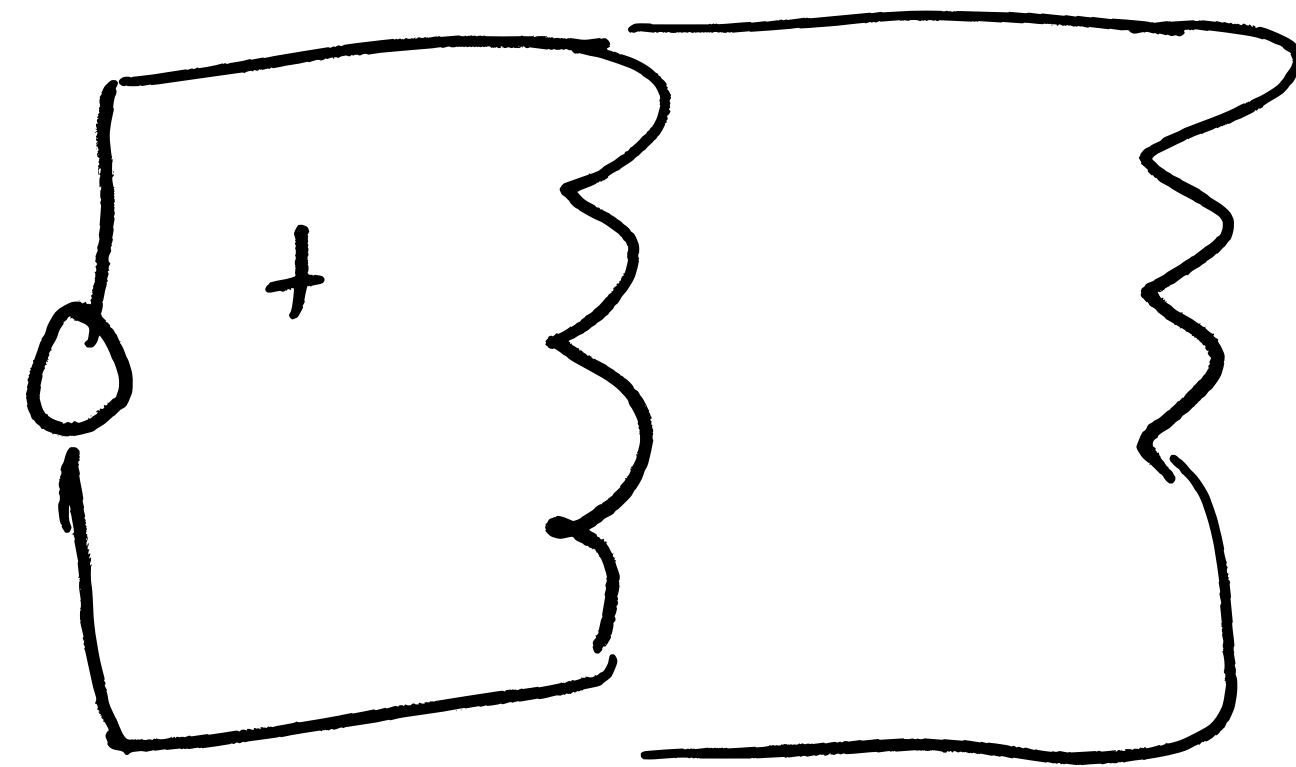

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2}$$
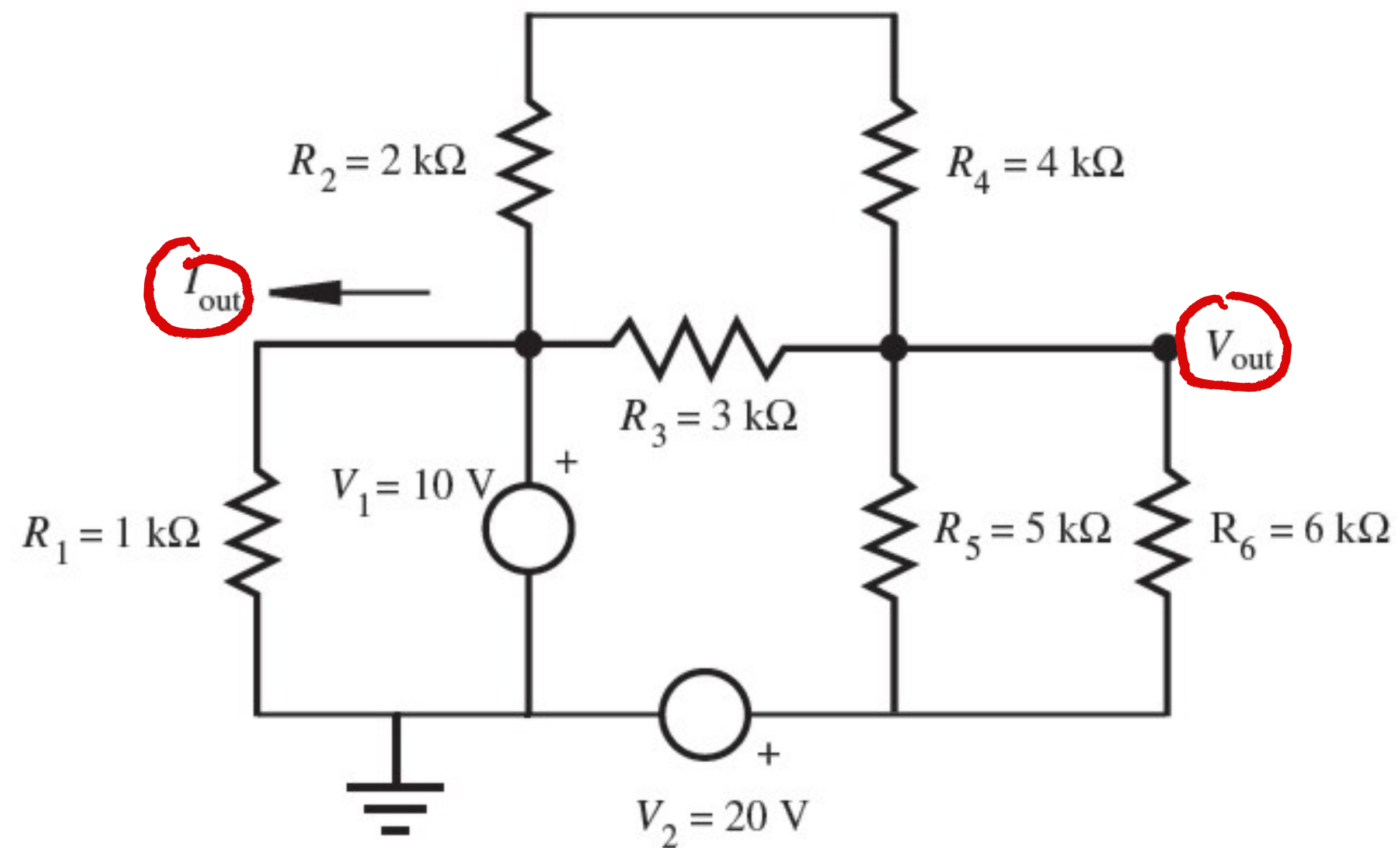
## Example 2.4: Find $I_{out}$ and $V_{out}$





What's our plan to solve?

1. Combine  $R_2$  ;  $R_3$  ;  $R_4$
2. Combine  $R_5$  ;  $R_6$


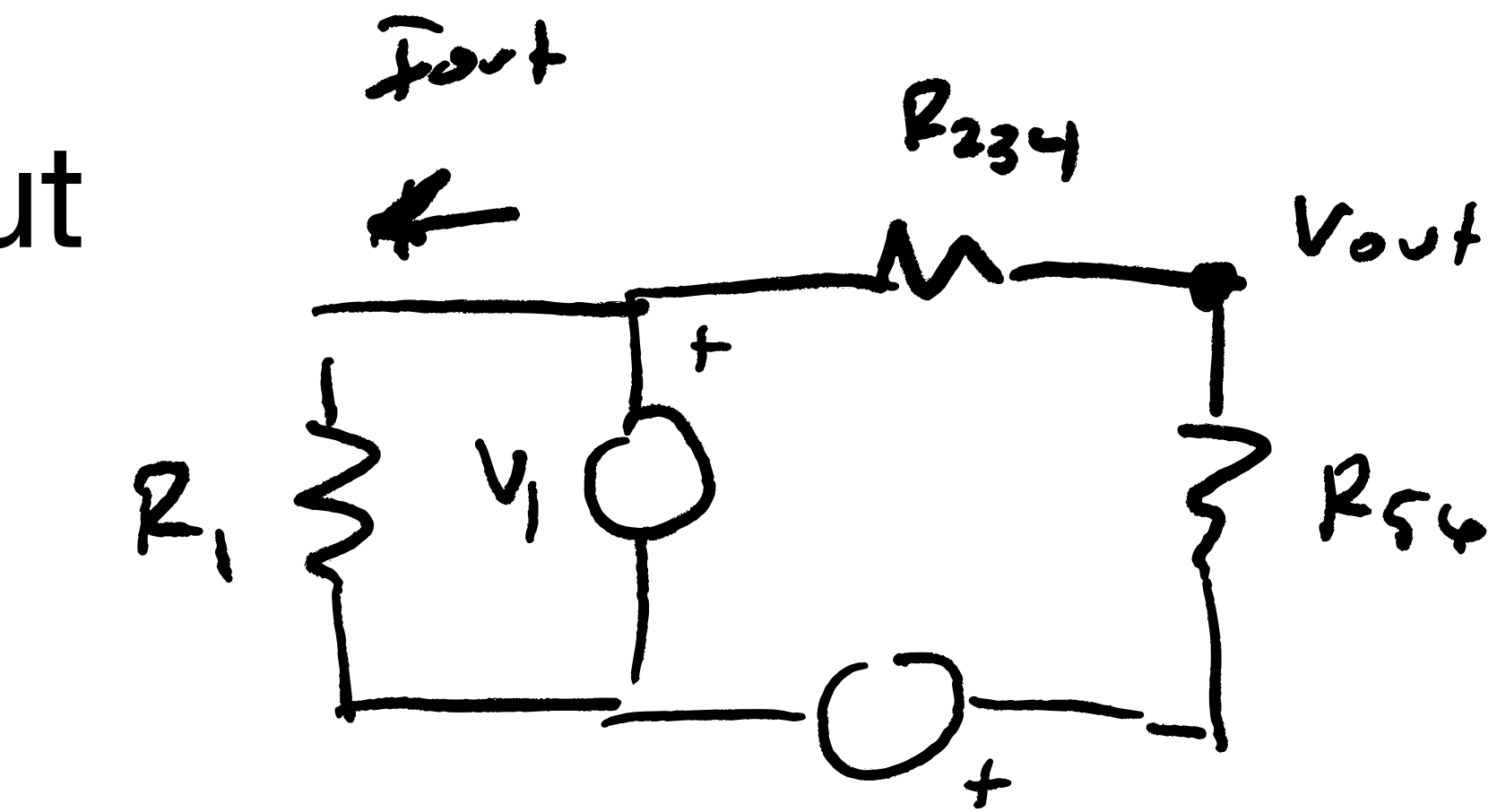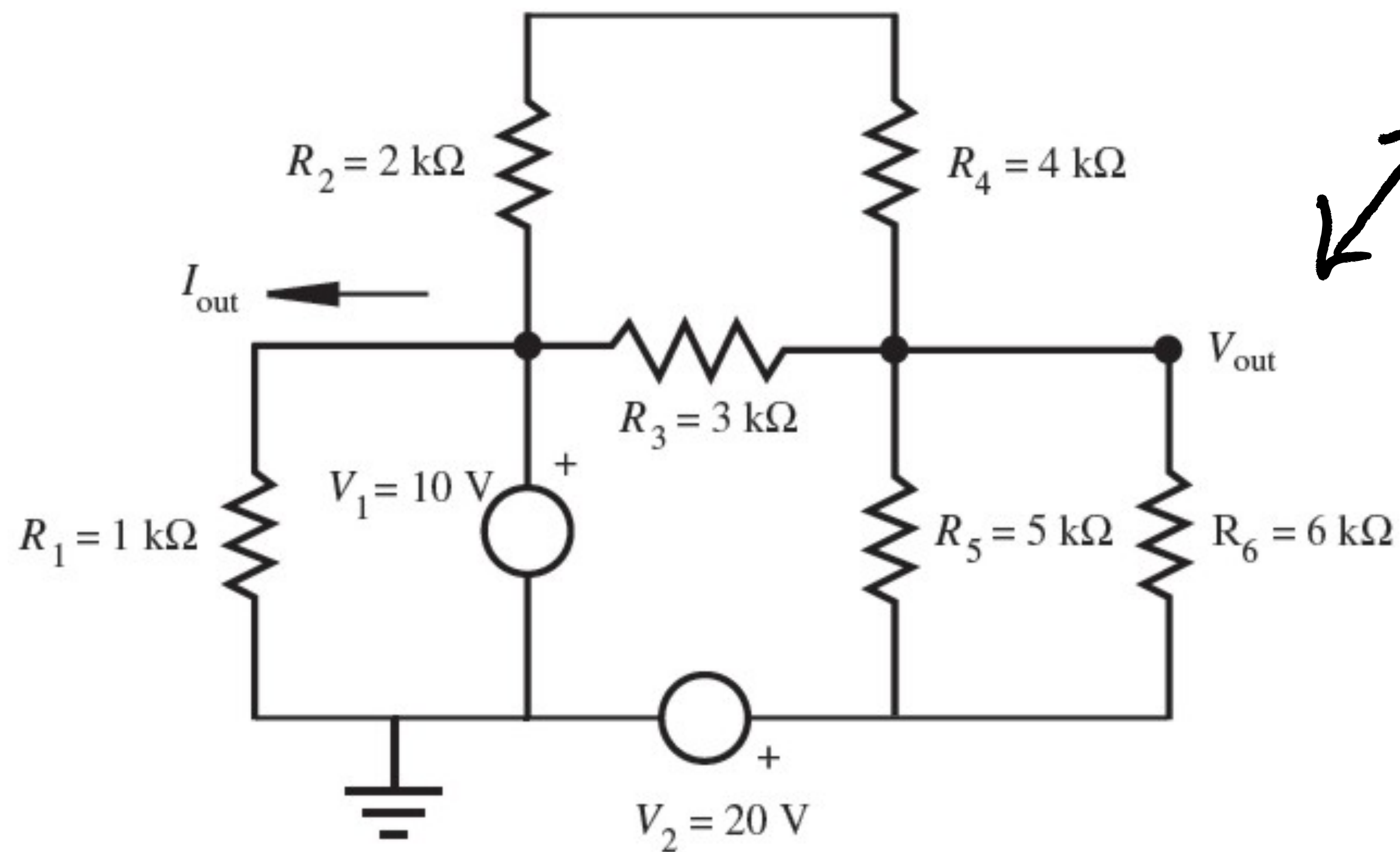
# Example 2.4: Find $I_{out}$ and $V_{out}$




$$(R_2 - R_4) \parallel R$$

$$R_{234} = \frac{(R_2 + R_4) \cdot R_3}{R_2 + R_3 + R_4}$$

$$R_5 \parallel R_6$$

$$R_{56} = \frac{R_5 R_6}{R_5 + R_6}$$
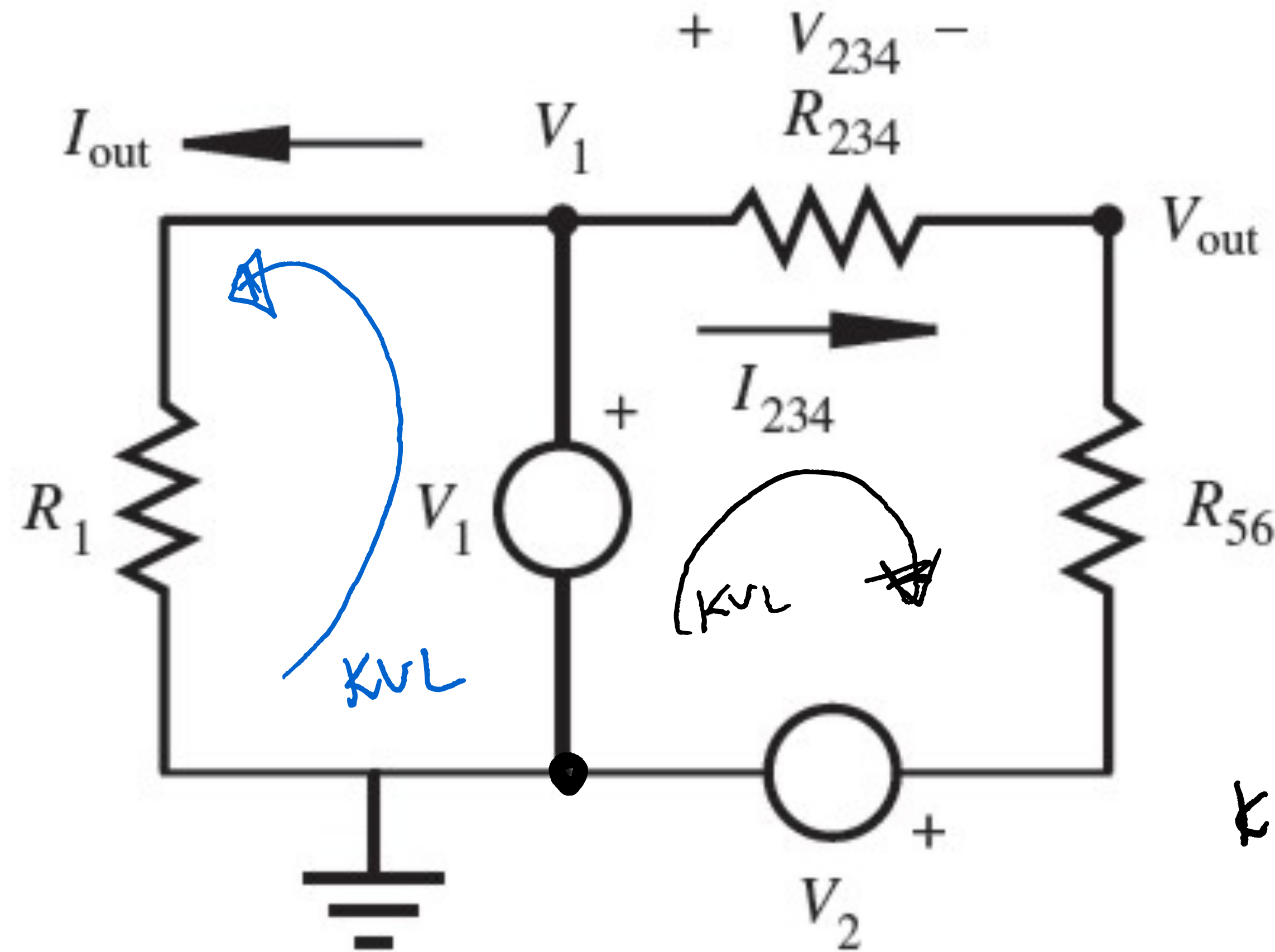
# Example 2.4: Find $I_{out}$ and $V_{out}$



KVL:  $V_1 = V_{R_1}$

Ohm's Law:  $V_{R_1} = I_{out} R_1$

$$I_{out} = \frac{V_1}{R_1}$$


KVL:  $-V_1 + \overbrace{V_{234} + V_{56}}^{V_{23456}} + V_2 = 0$

$$V_{23456} = V_1 - V_2$$

$$V_{234} = \left( \frac{R_{234}}{R_{234} + R_{56}} \right) (V_1 - V_2)$$

$$V_o = V_1 - V_{234}$$
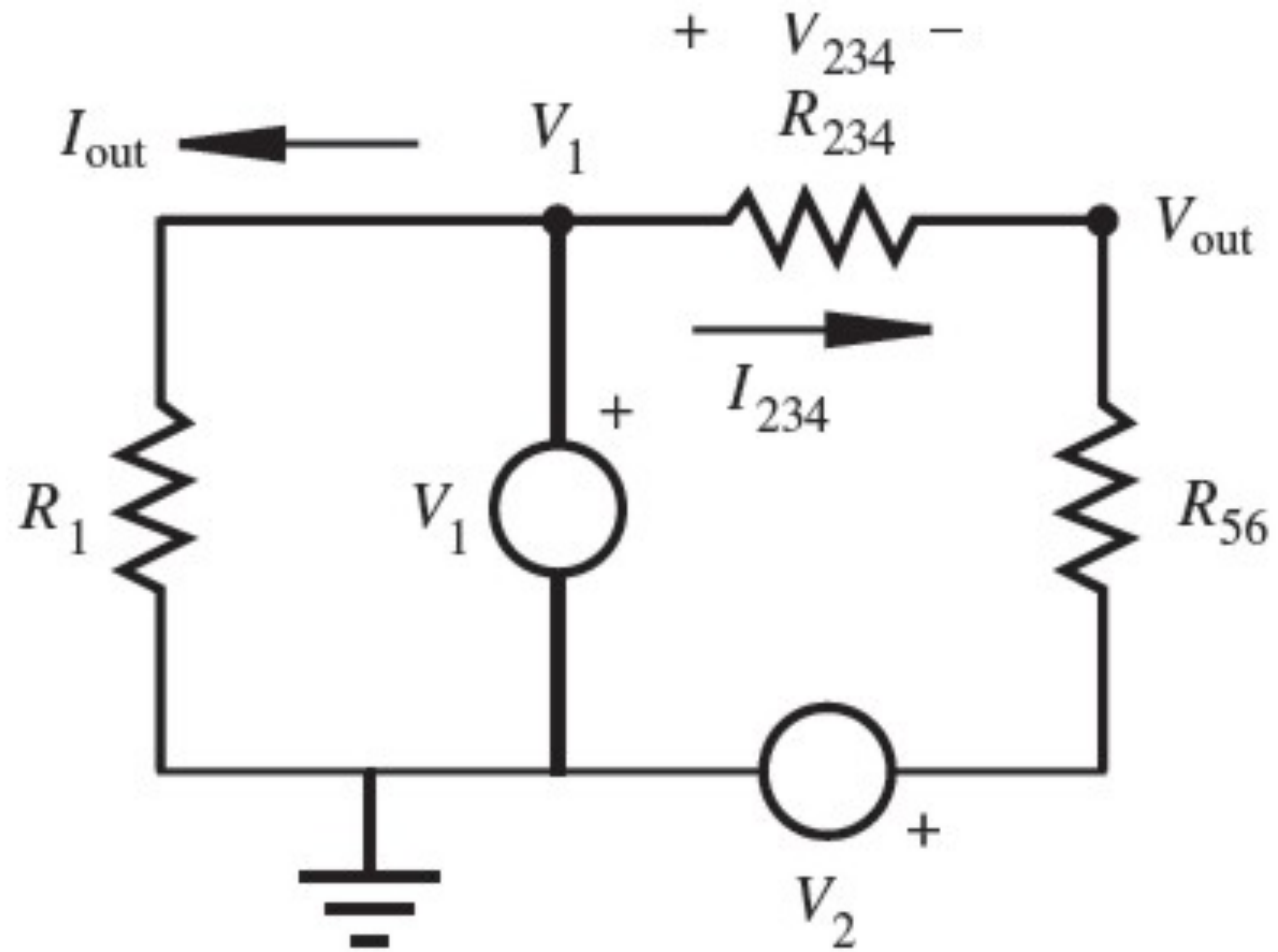
## Example 2.4: Find $I_{out}$ and $V_{out}$




# Sources and Meters

## Voltage Source


Power supply!

- ideal source
  - zero output impedance
  - sustain voltage @  $\infty$  current.

generalized resistance  $Z$

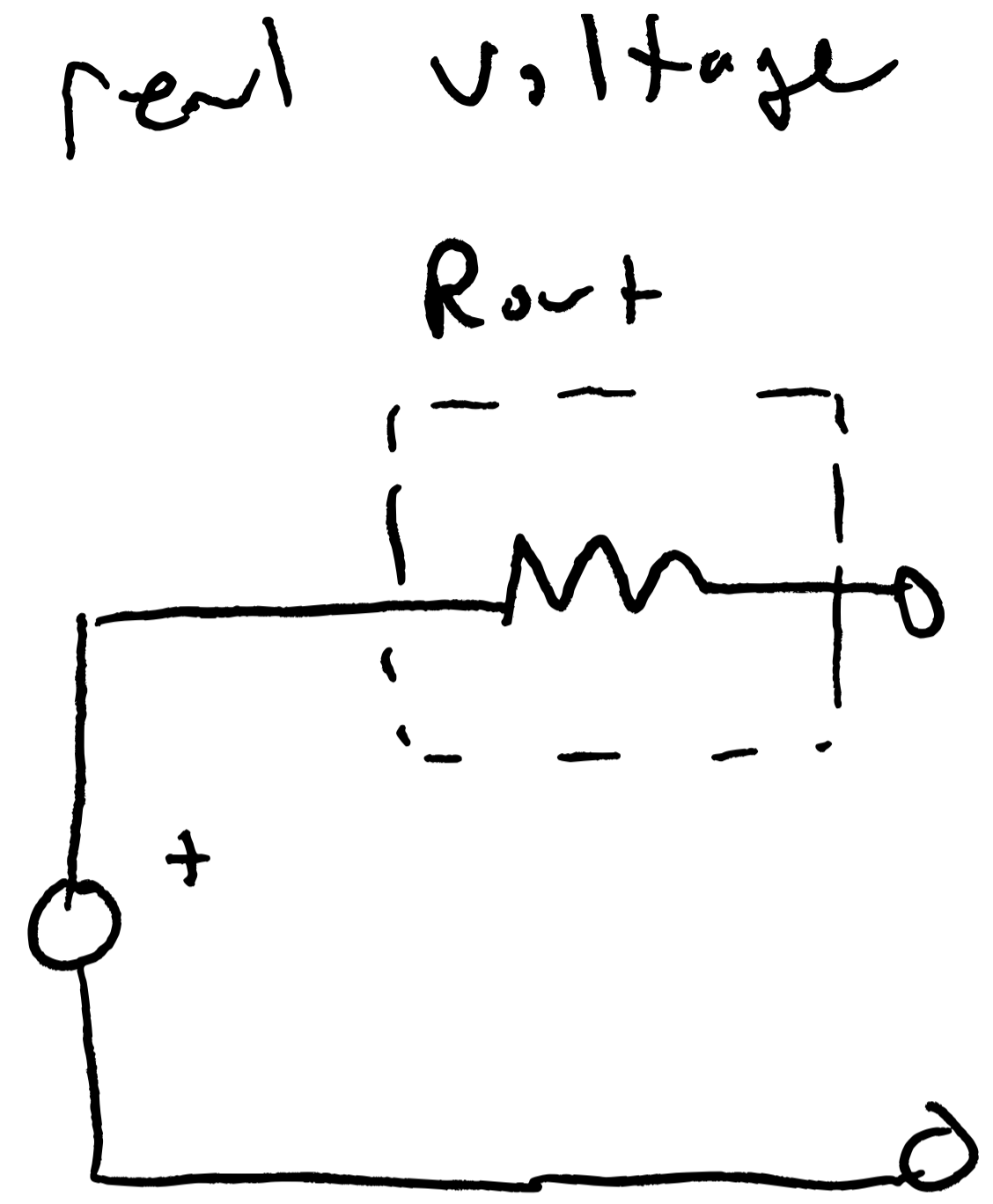

## Voltmeter

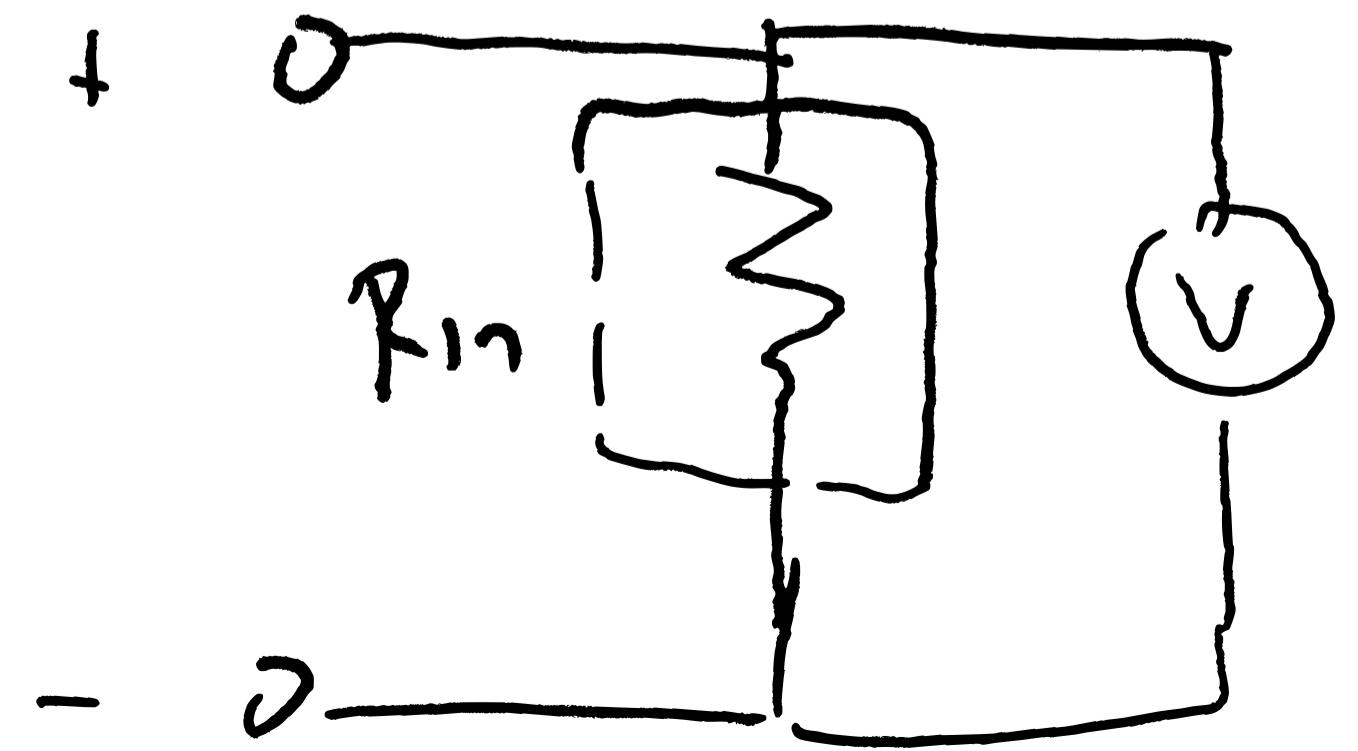


# Sources and Meters


## Current Source

- ideal current source  
→  $\infty$  output impedance  
→  $\infty$  voltage

Real Current Source

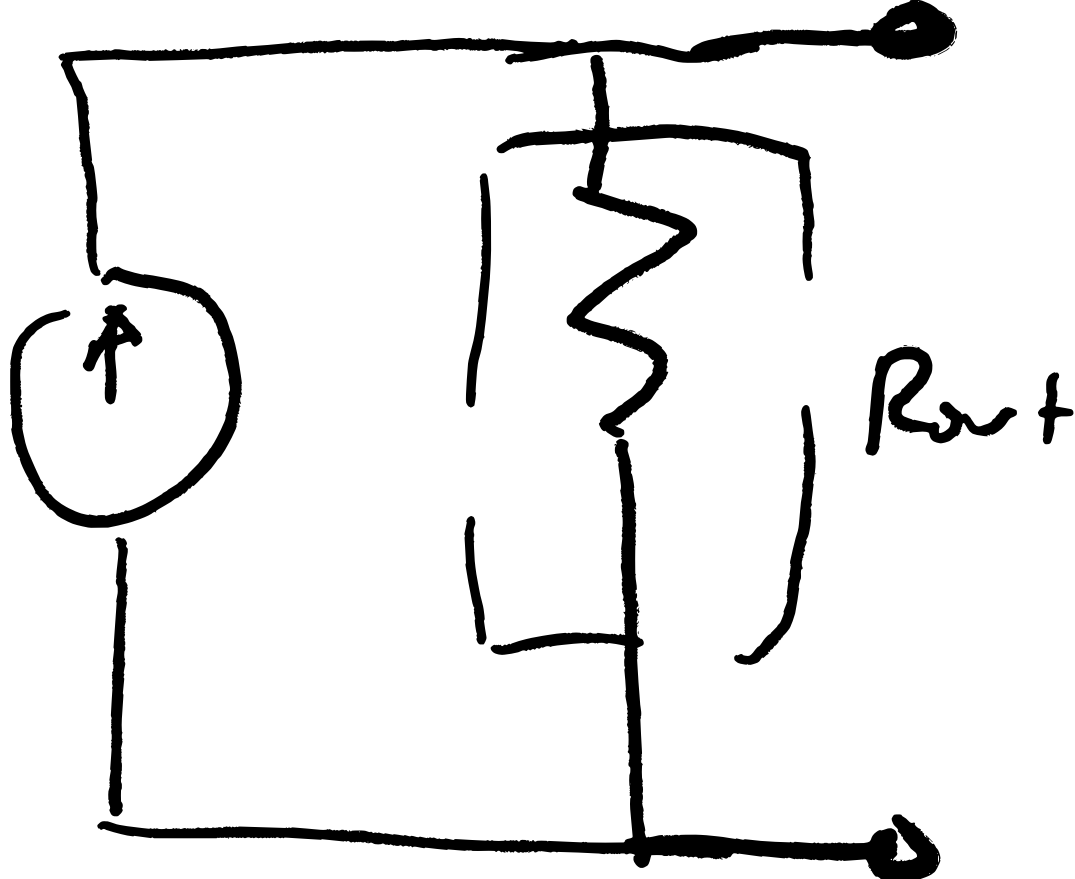

## Ammeter

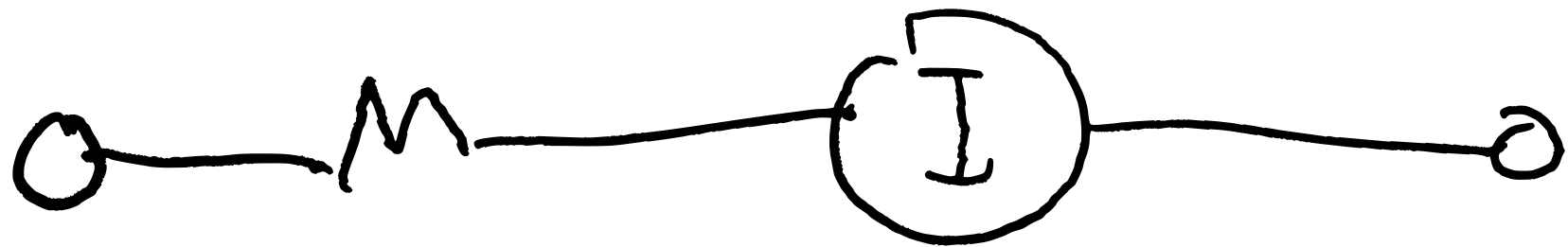

# How to use a multimeter?



Switch Position Or Symbols	Measurement Functions
$\tilde{V}$	AC Voltage
$\overline{V}$	DC Voltage
$A_{\overline{=}}$	DC Current
$\Omega$	Resistance (Ohms)
$\text{     }$	Continuity Beeper
$\rightarrow +$	Diode Test
OFF	ON/OFF Switch


Why should we care about input/output impedance?

Loading effect matters!

the effect on a measurement  
system  $\rightarrow$  can load rest of  
system?

Why should we care about input/output impedance?

Ideal case, what is  $V_m$ ?

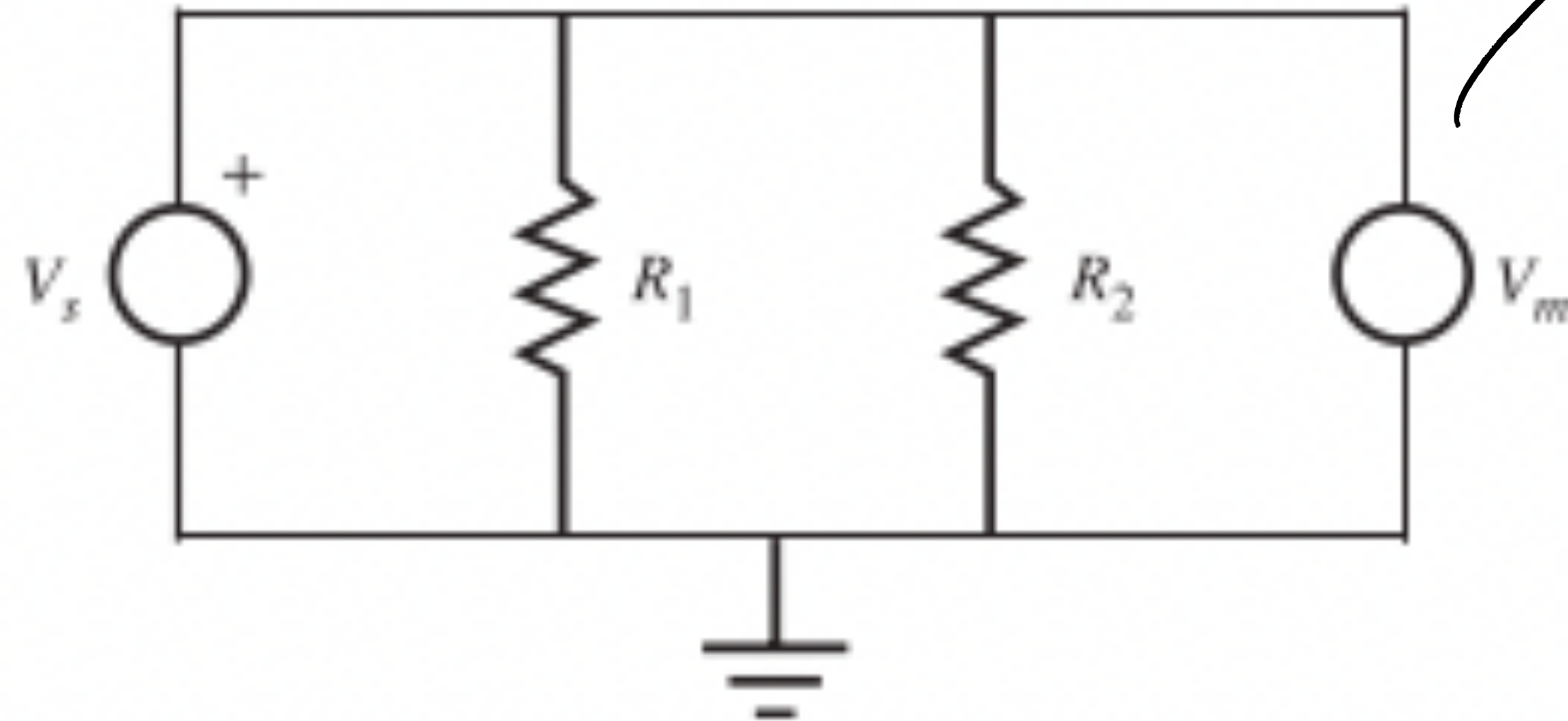


multimeter

$$\underline{\underline{V_m = V_s}}$$



Why should we care about input/output impedance?

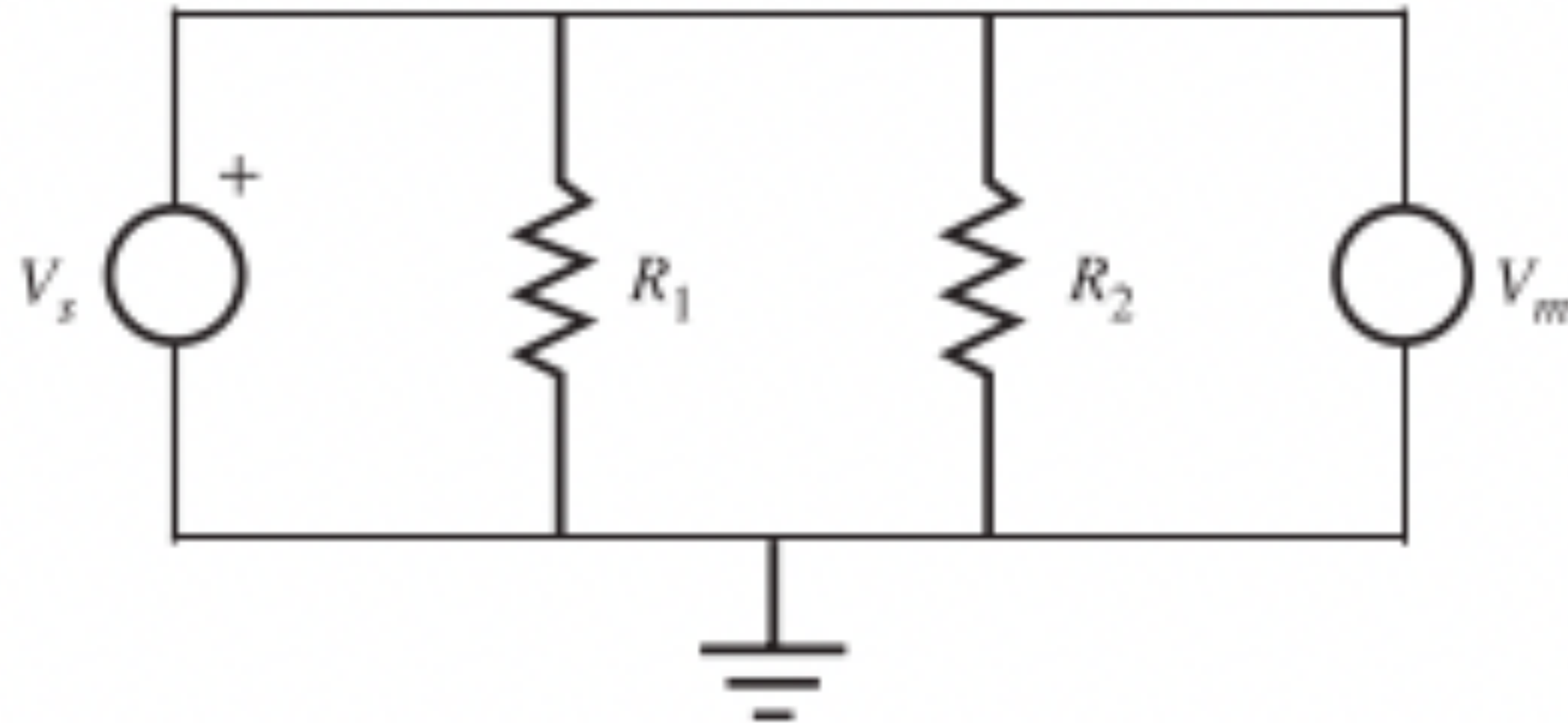
Actual case, with output/input impedance, what is  $V_m$ ?



Why should we care about input/output impedance?

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

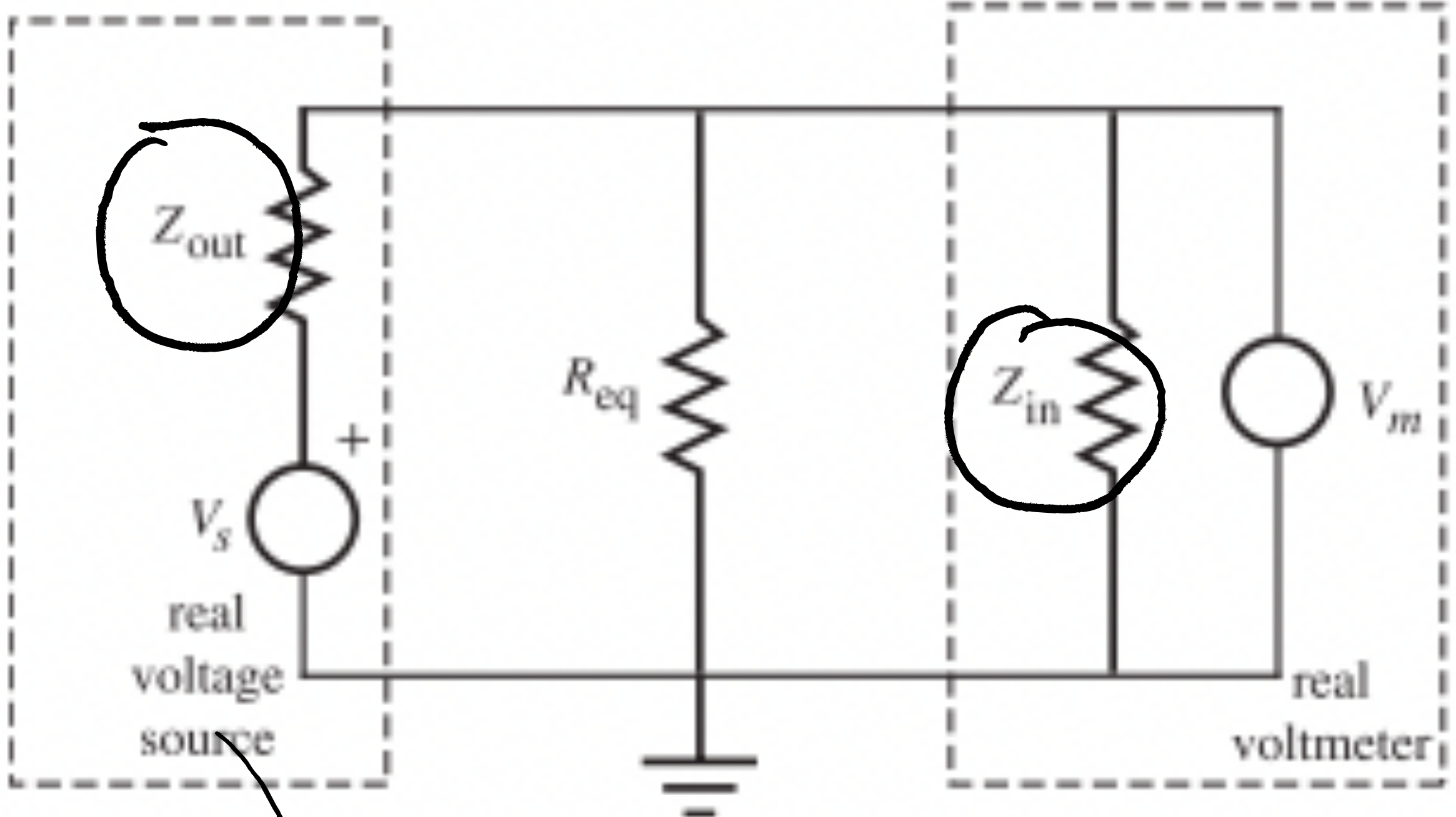Actual case, with output/input impedance, what is  $V_m$ ?





$$V_m = \frac{R_{eq} Z_{in}}{(R_{eq} + Z_{in}) + \frac{R_{eq} Z_m}{(R_{eq} + Z_{in})} + Z_{out}}$$

$V_s$

$$\underline{\underline{V_s \neq V_m}}$$

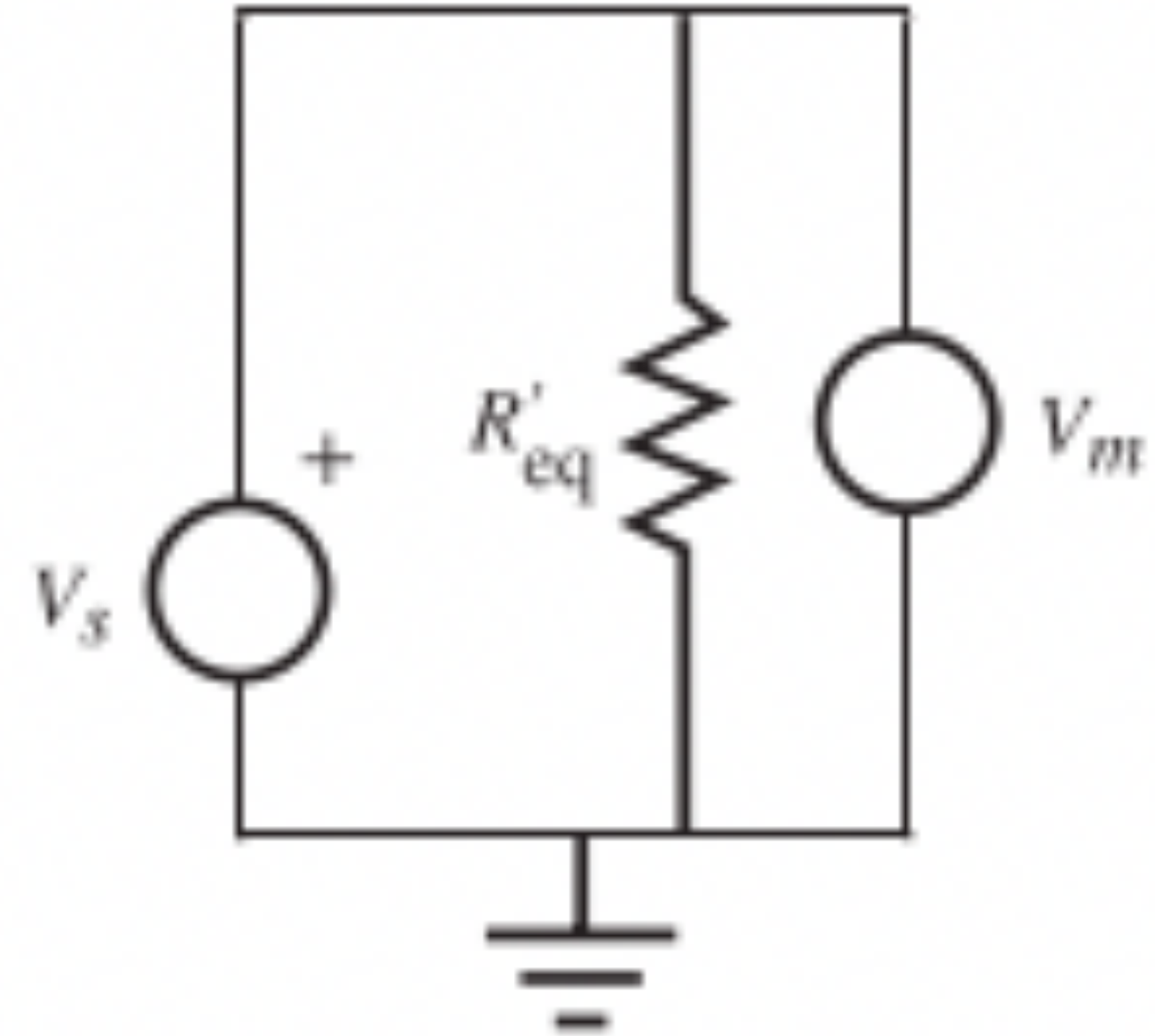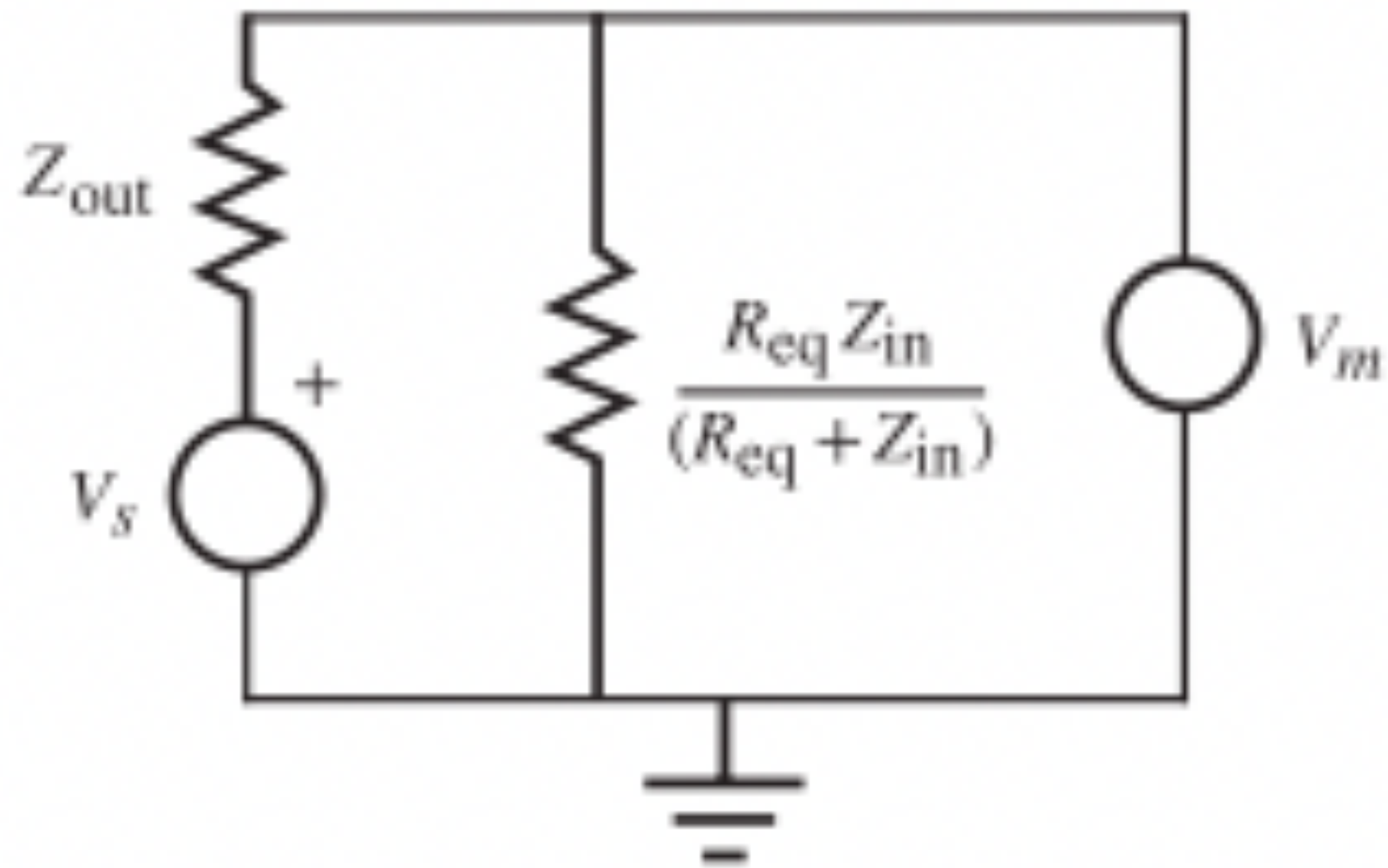Why should we care about input/output impedance?





# Thevenin Equivalent Circuits

What:

to simplify complex circuits  
by replacing w/ Eq. Source  
and Series Resistance

Why:



→ can help w/ designing  
circuits

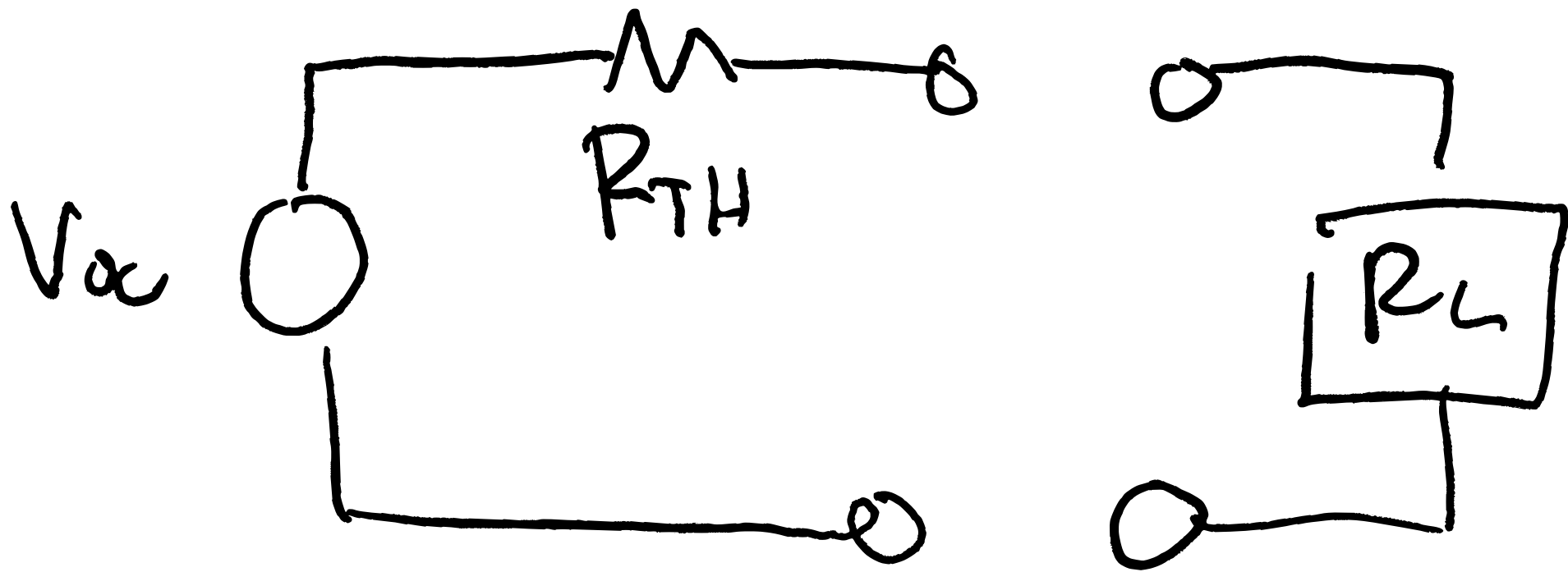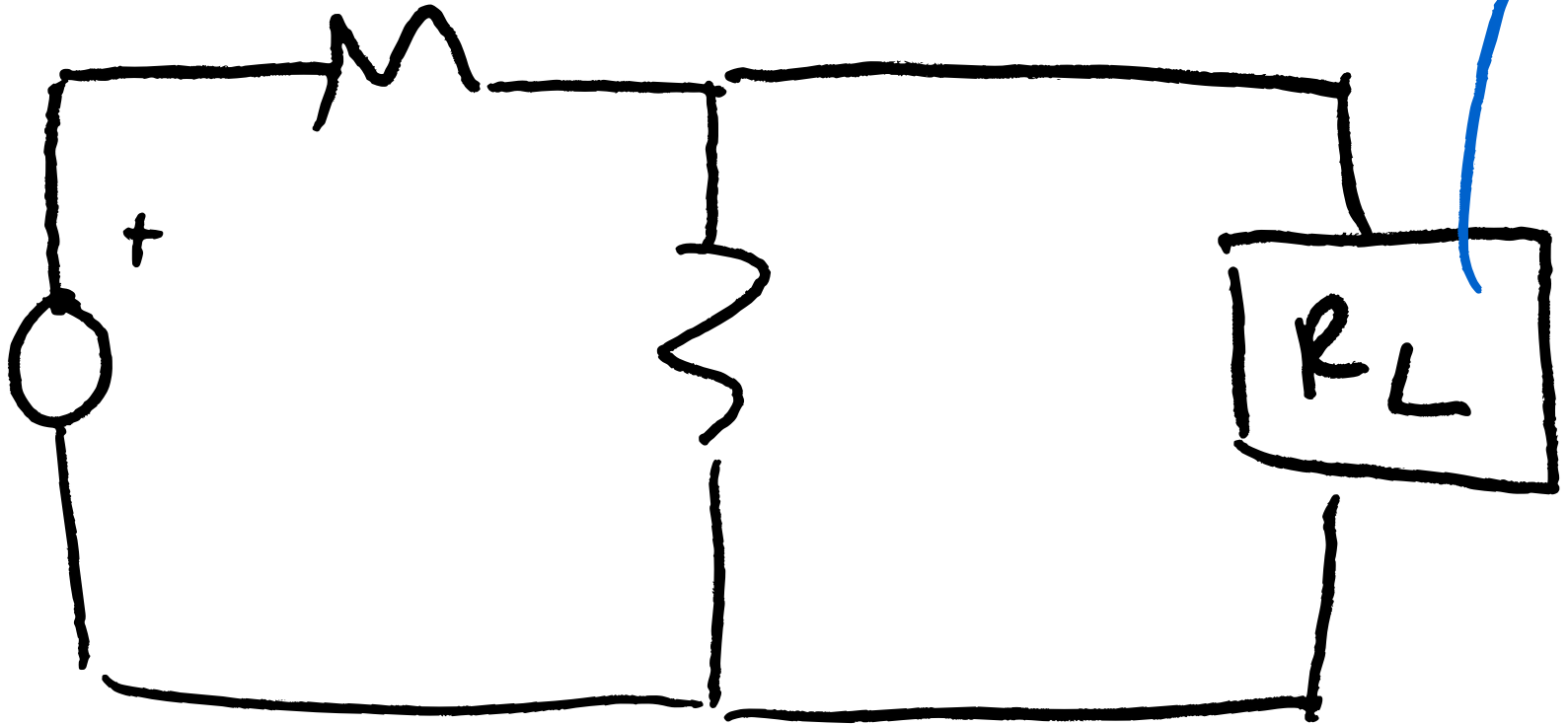

Goal

# Thevenin Equivalent Circuits: Step by Step

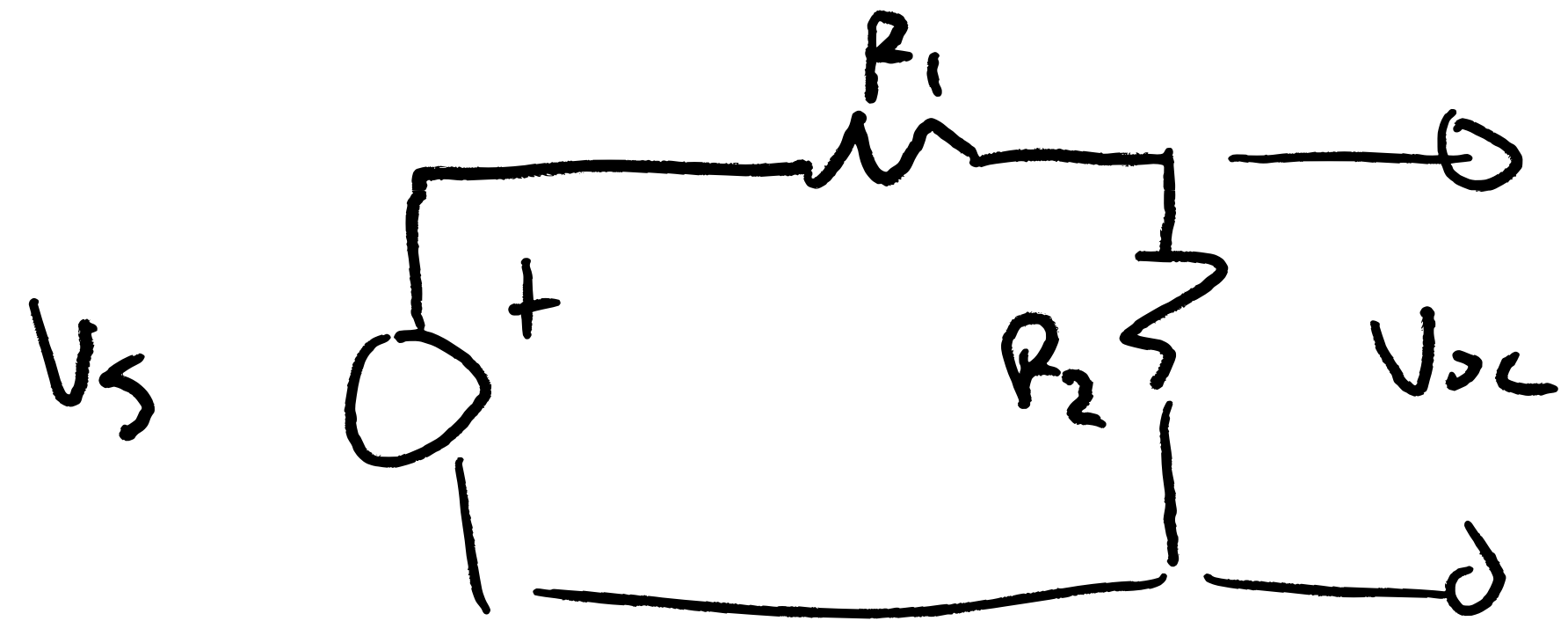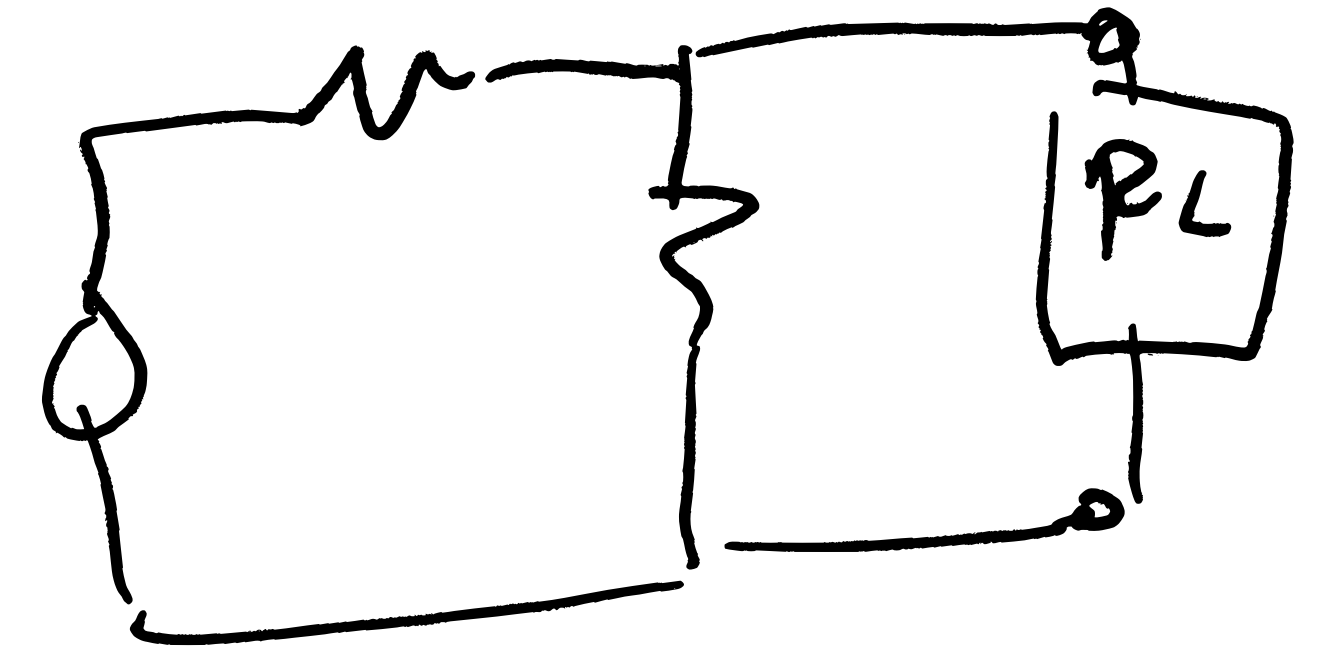1. Find open circuit voltage  $V_{oc}$ 
  - disconnect the load
  - find voltage across





$$V_{oc} = \left( \frac{R_2}{R_1 + R_2} \right) V_s$$

# Thevenin Equivalent Circuits: Step by Step

2. Find the Thevenin Eq. resistance



- short  $V_s$ .

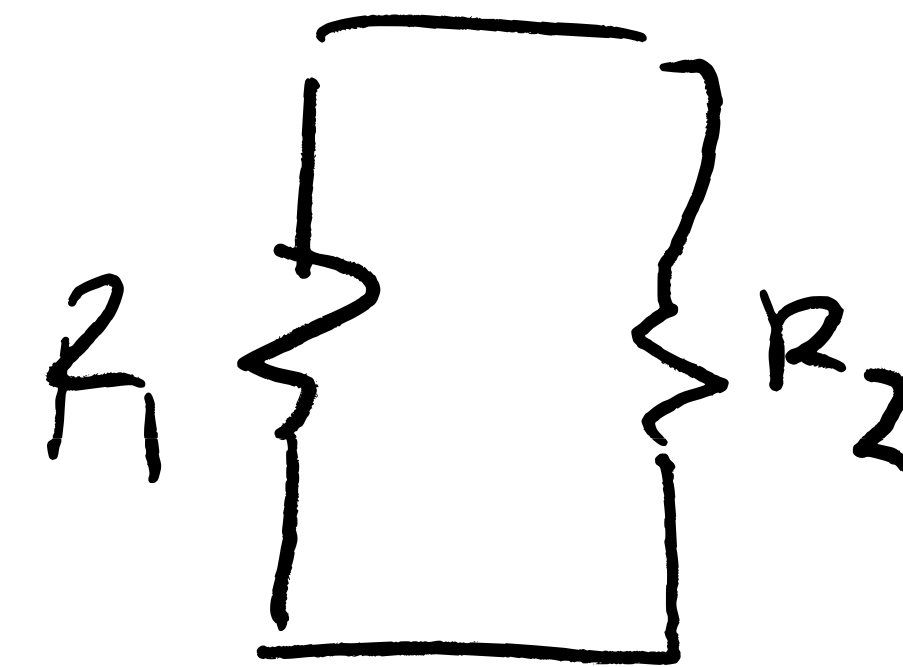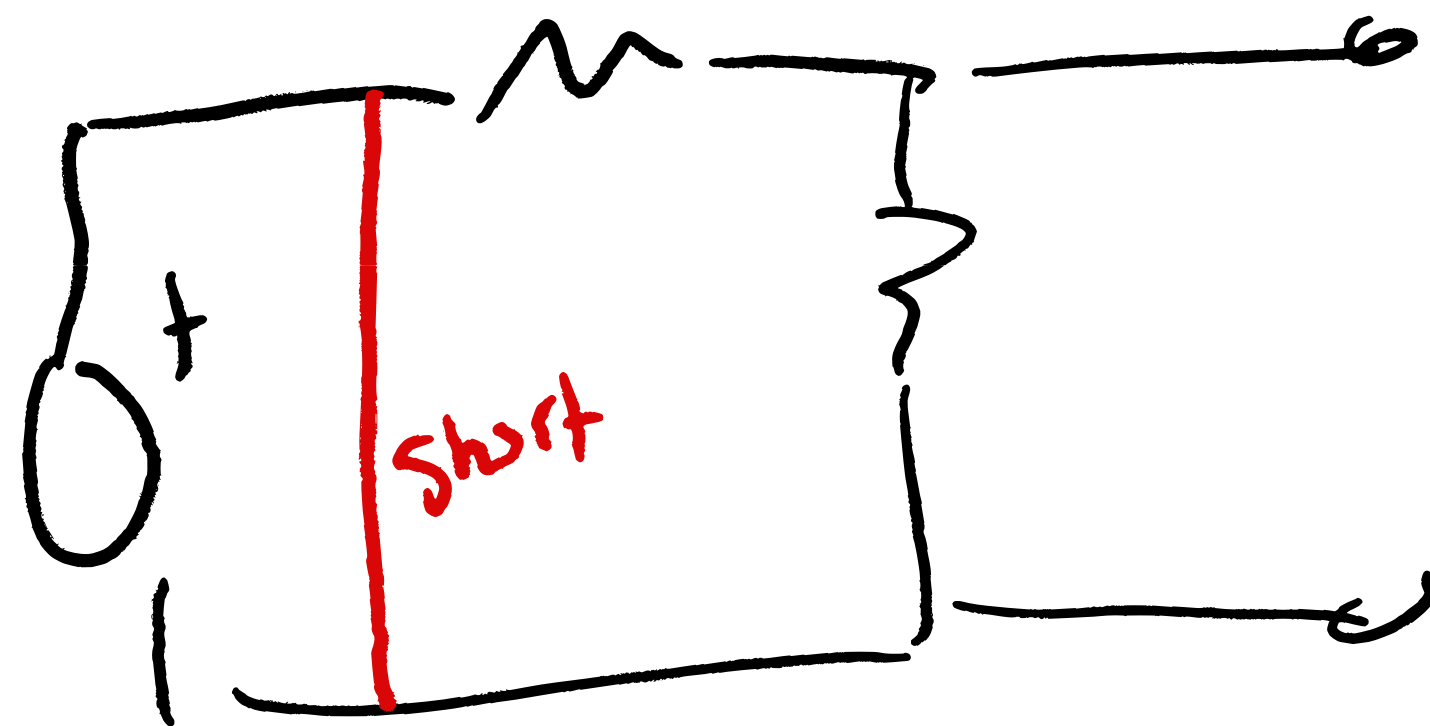

$$R_{Th} = \frac{R_1 R_2}{R_1 + R_2}$$

# Thevenin Equivalent Circuits: Step by Step

## 3. Analyze

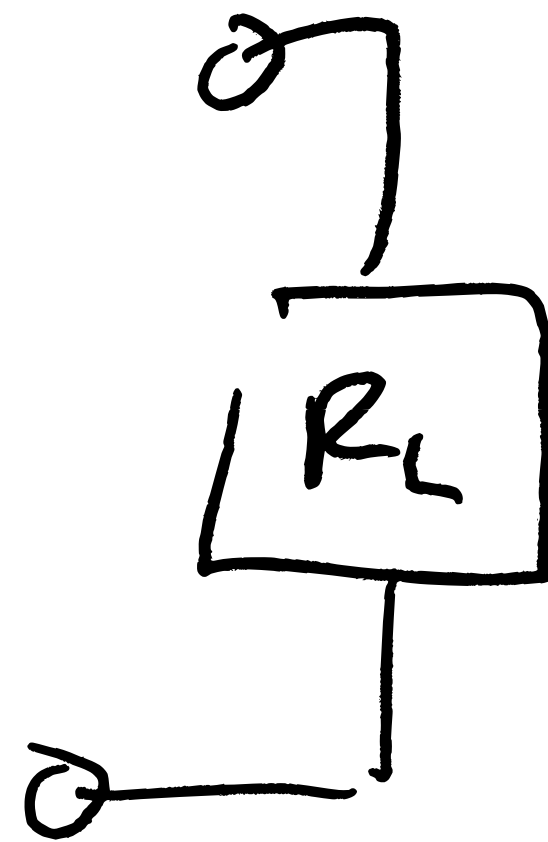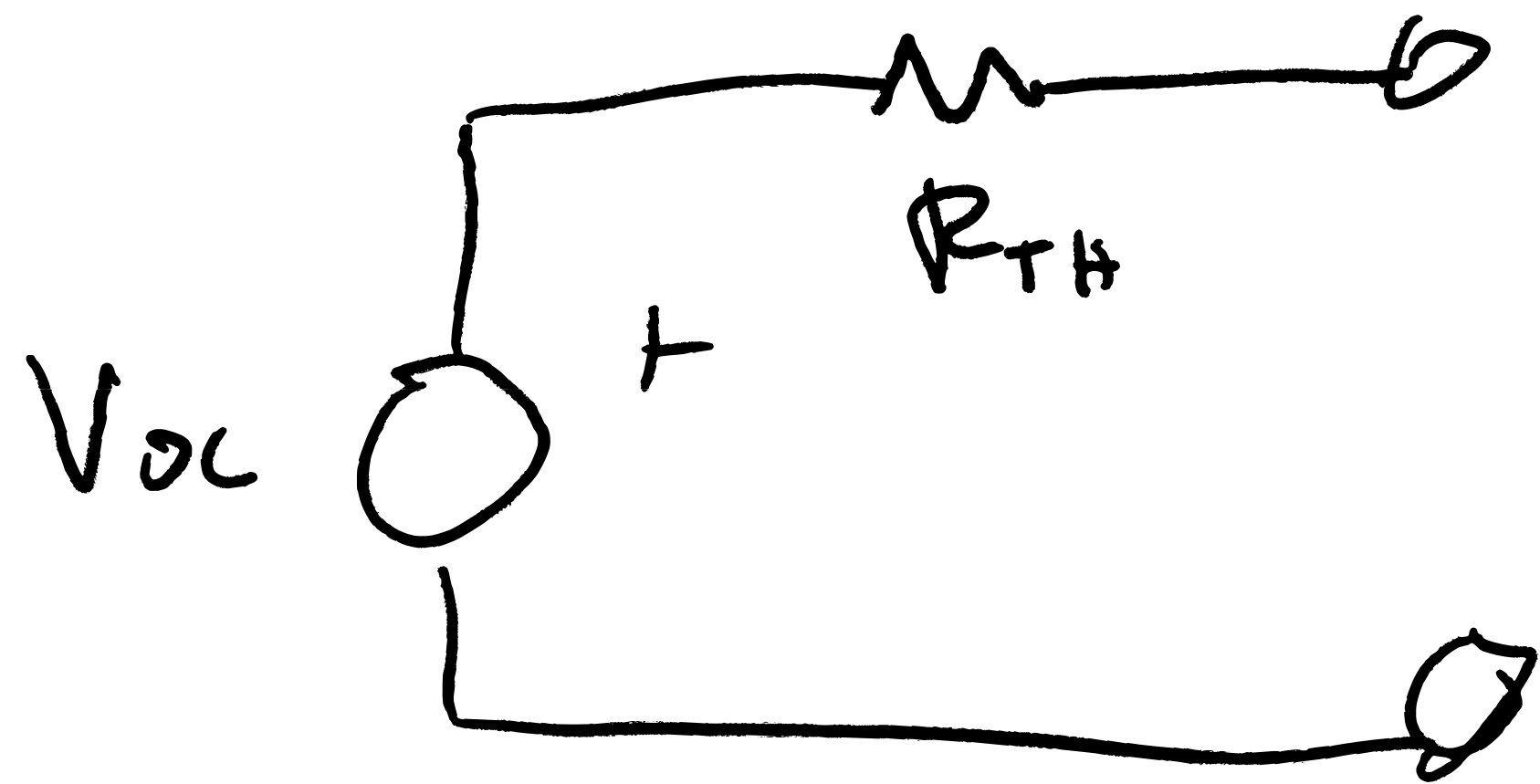

$$V_L = \left( \frac{R_L}{R_L + R_{TH}} \right) V_{oc}$$


# Norton Equivalent Circuits

What:

*same reason*

Why:

*same reason*

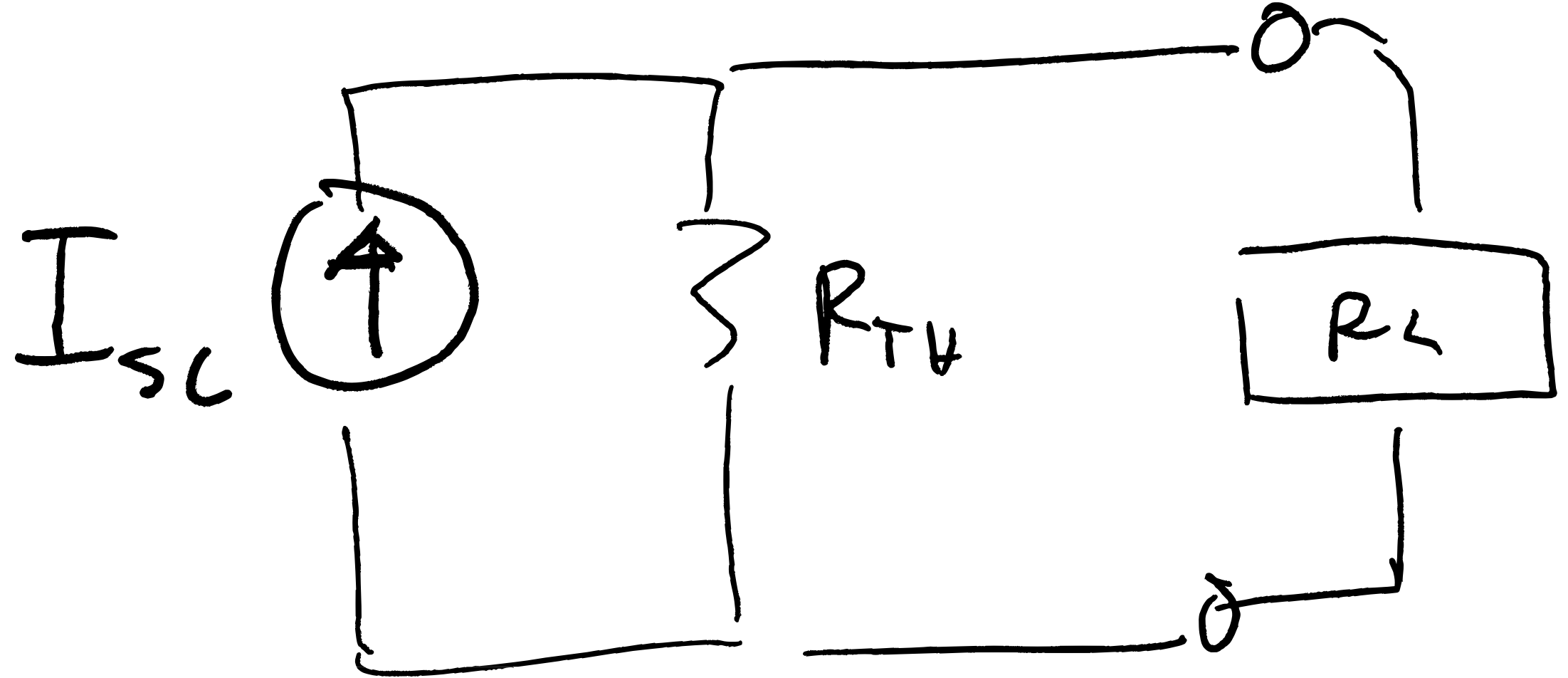





# Norton Equivalent Circuits: Step by Step

1. Find short circuit

- short the load

2. Find  $R_{TH}$   $\rightarrow$  same as Thevenin

3. Analyze

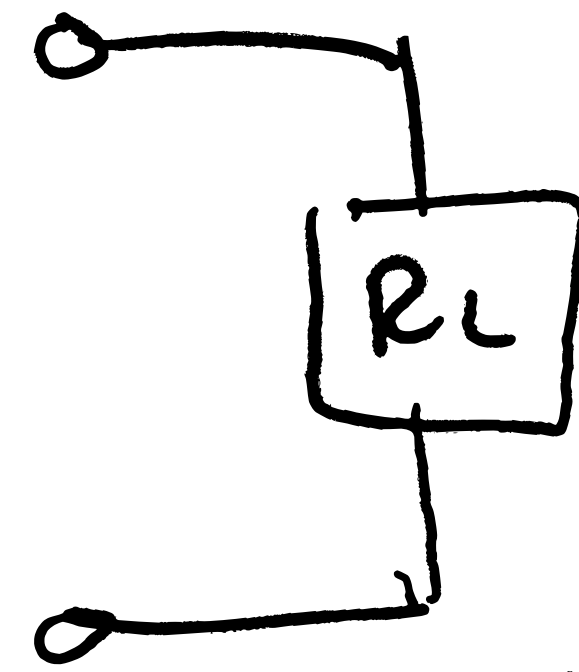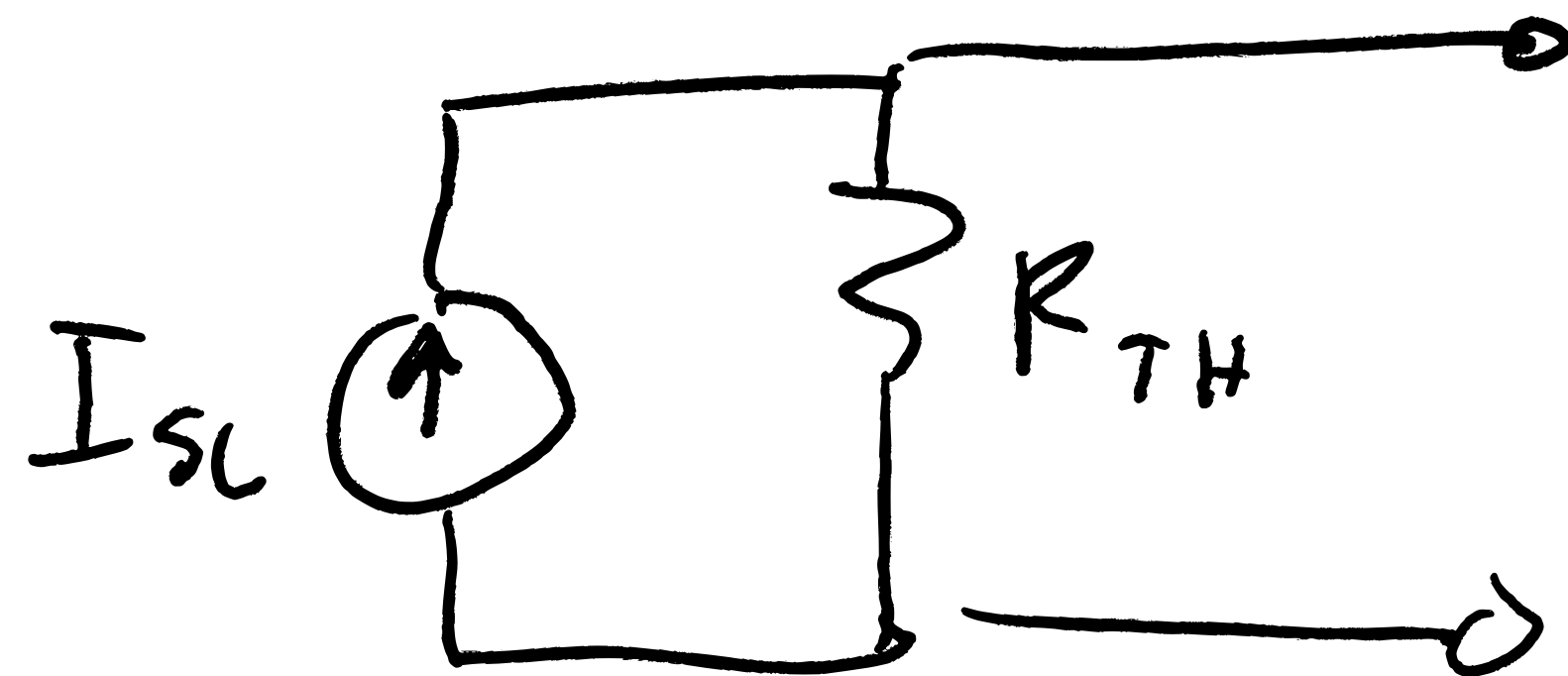

$$I_L = \left( \frac{R_{TH}}{R_{TH} + R_L} \right) I_{sc}$$

# Thevenin and Norton Equivalent Circuits: Why all the trouble?


- . Thevenin / Norton are independent of the load
- . we can make changes without reanalyzing whole circuit

# Electrical Power

All circuit elements either dissipate, store, or deliver power

→ physical interaction between charge & electromagnetic fields.

$$dW = V dq$$

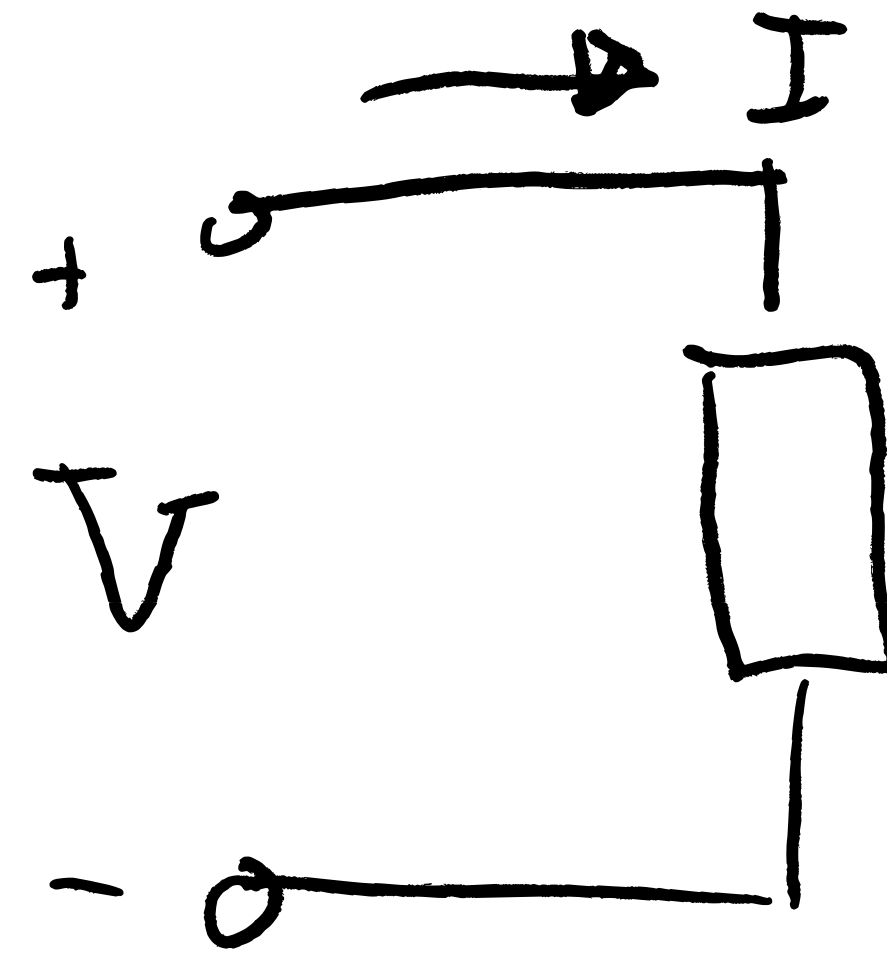


Power is the rate of work:

$$P = \frac{dW}{dt} = V \frac{dq}{dt} = \cancel{VI^2} = \frac{V^2}{R} \quad \underline{\underline{\text{check}}}$$

$$= VI = \frac{V^2}{R} = I^2 R$$


# Electrical Power

# Impedance Matching

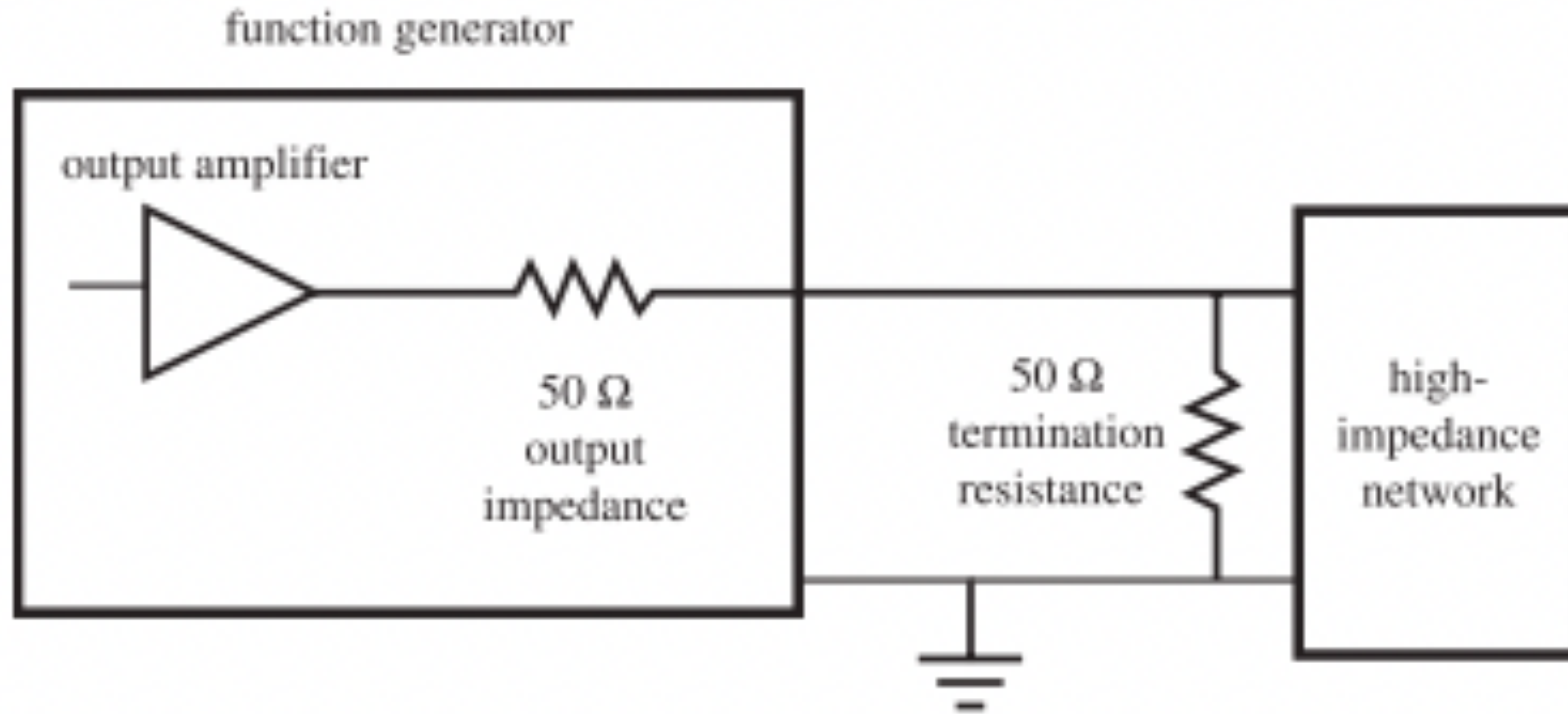

What does the termination resistant do?

# More on Impedance: String Analogy

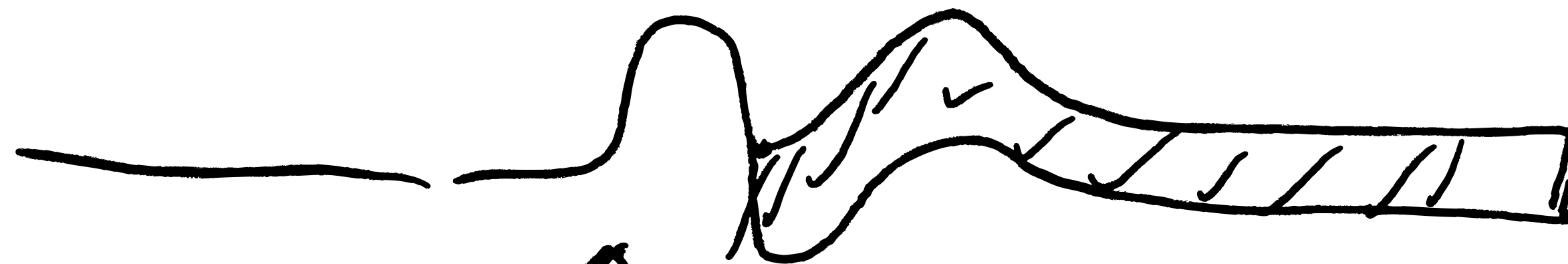

↑  
reflect!!

Impedance  
MIS match


# Discussion

## ■ CLASS DISCUSSION ITEM 2.12
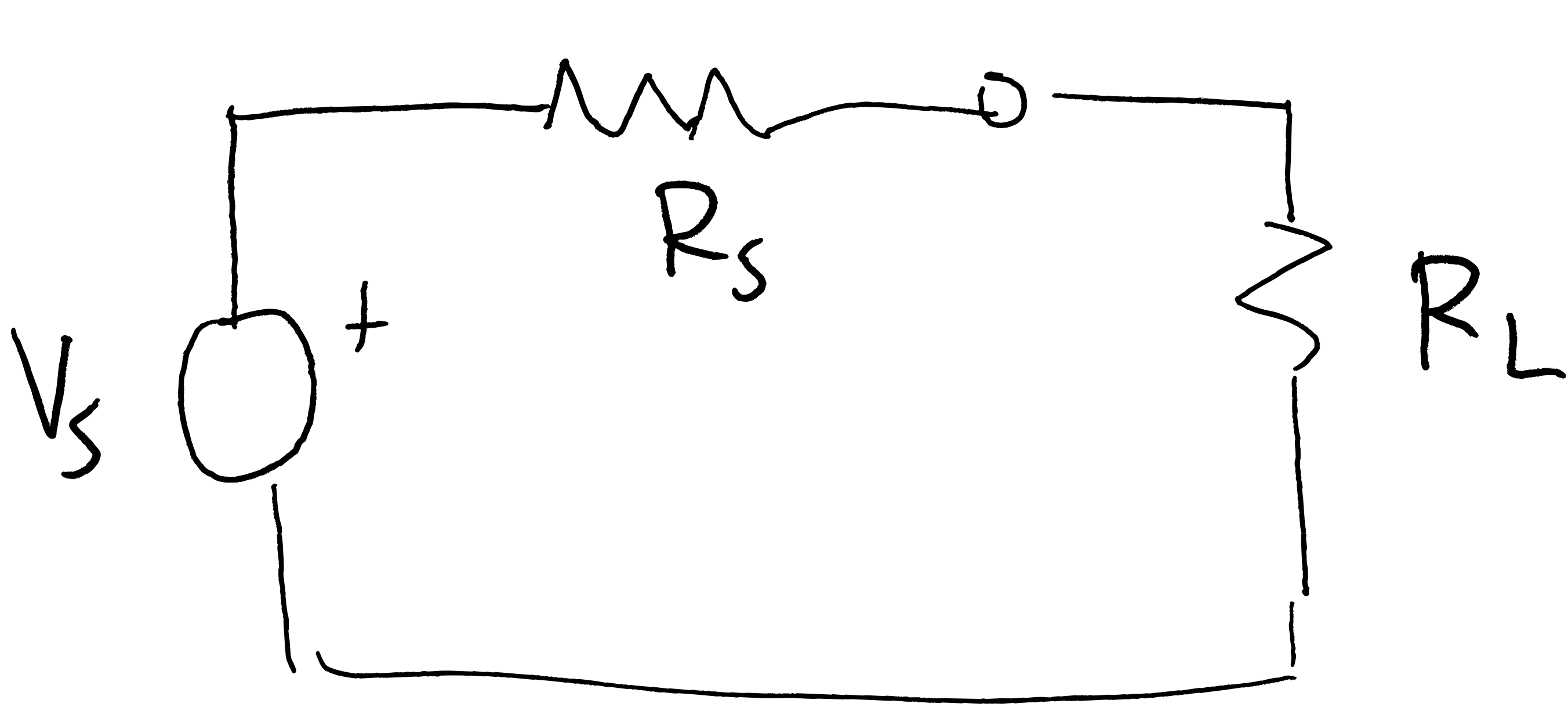
### *Audio Stereo Amplifier Impedances*

Why are audio stereo amplifier output impedances important specifications when selecting speakers?

Consider simple circuit. Find  $R_L$  to maximize power transfer



How to approach?

$$P_L(R_L)$$

$$\frac{dP_L}{dR_L} = 0$$

Solve for  $R_L$



Consider simple circuit. Find  $R_L$  to maximize power transfer