


Last time:

> series & parallel equivalent circuits

> source & meters  
→ loading effect

> output / input impedance

> Power.

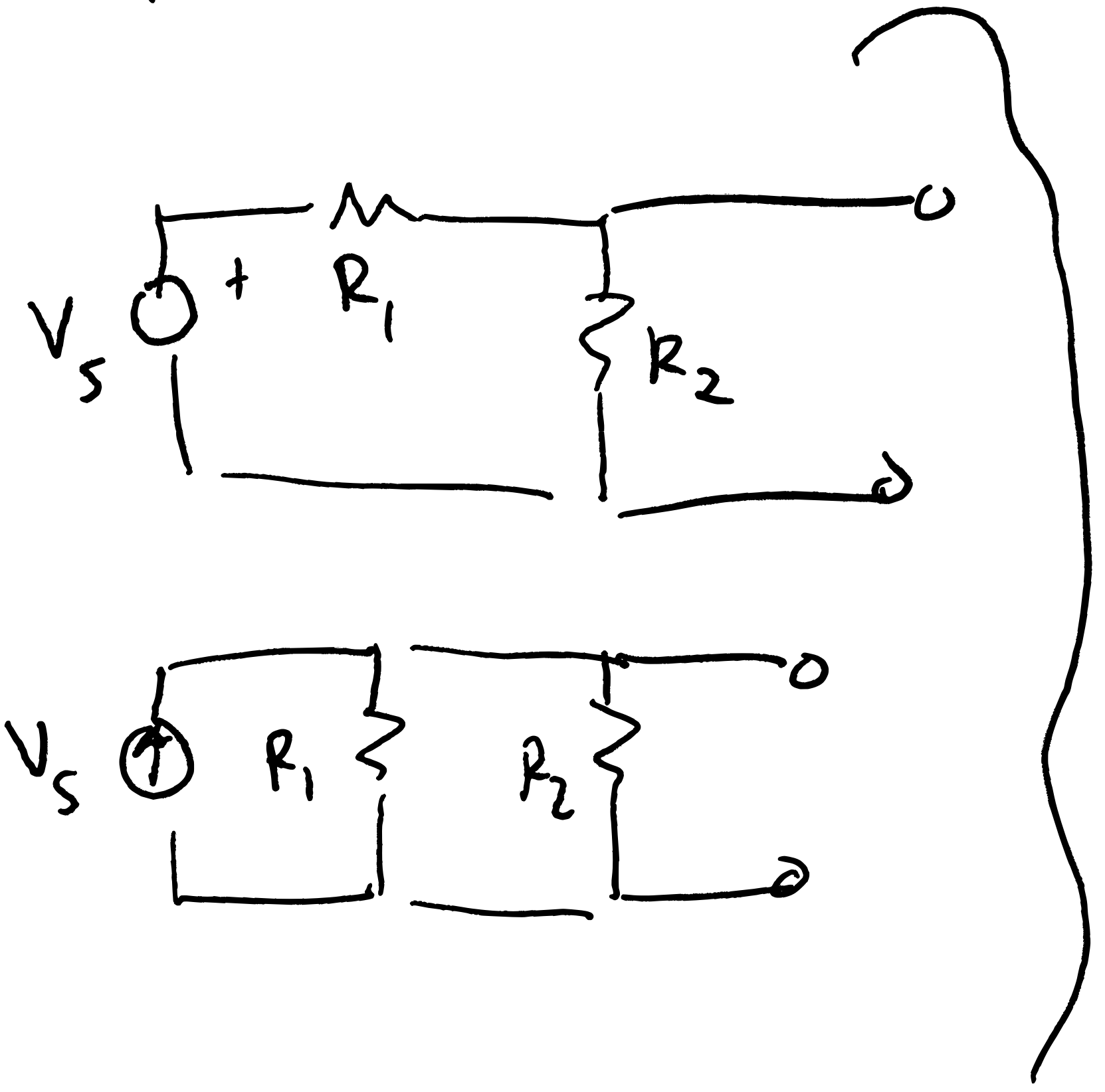

translate  
to  
the Norton  
& ( $I_{sc}$ )  
Thevenin  
( $V_{oc}$ )  
Eg.  
both  $R_{TH}$

# Electrical Power

All circuit elements either dissipate, store, or deliver power


> physical interactions between charge and electromagnetic fields

The amount of infinitesimal work done on/by an element by infinitesimal charge moving:

$$dW = V dq$$

Power is the rate of work:
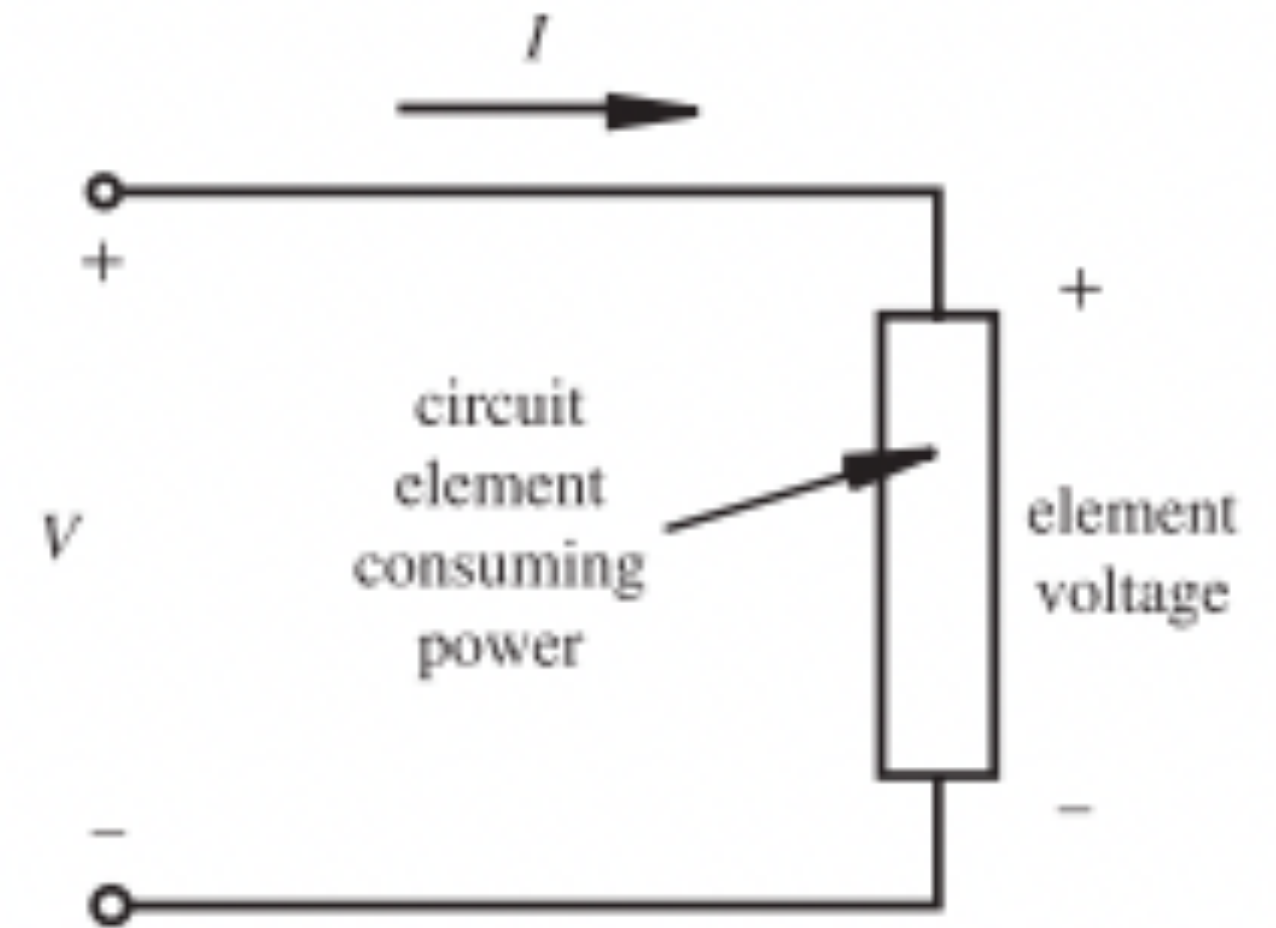
$$P = \frac{dW}{dt} = V \frac{dq}{dt} = \boxed{VI = I^2 R = \frac{V^2}{R}}$$



# Electrical Power

## Power on Circuits

$$P = VI$$

- for any element power consumed or generated is the product of voltage across it and current through that element

P negative : dissipation / storage

P positive : generation

Today:

- AC circuits
- Transformers

CH.2

- Intro to Semiconductors



CH.3

# AC circuits



Why?

- most electrical signals are not pure DC ( $V=C$ )
  - even when your system is powered by DC.
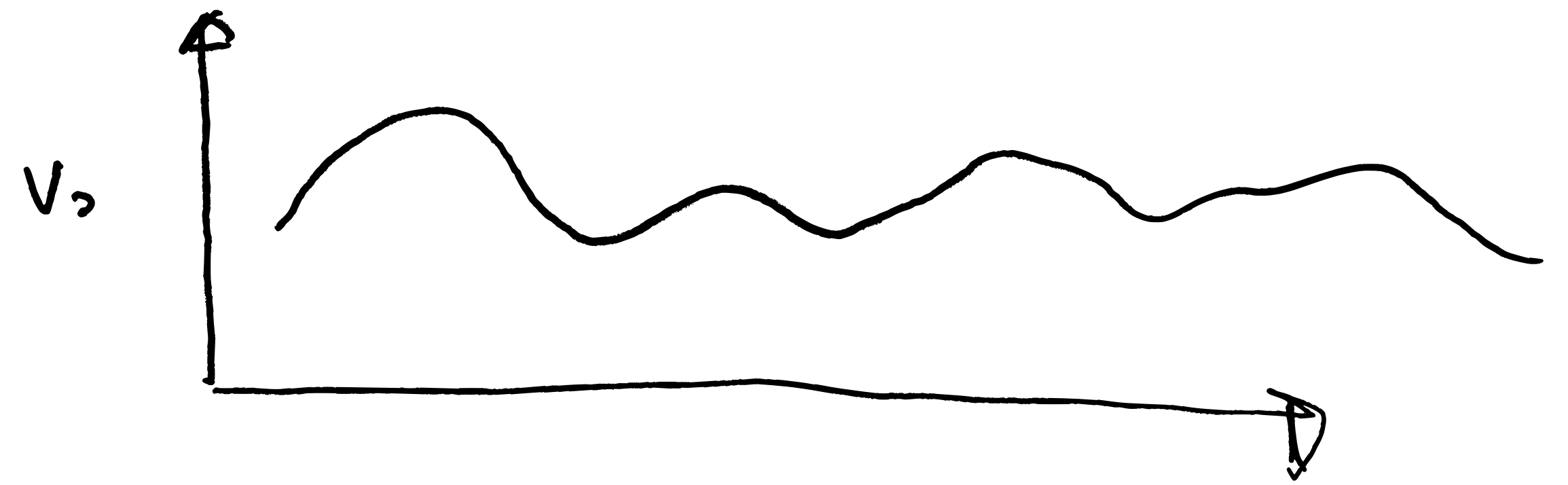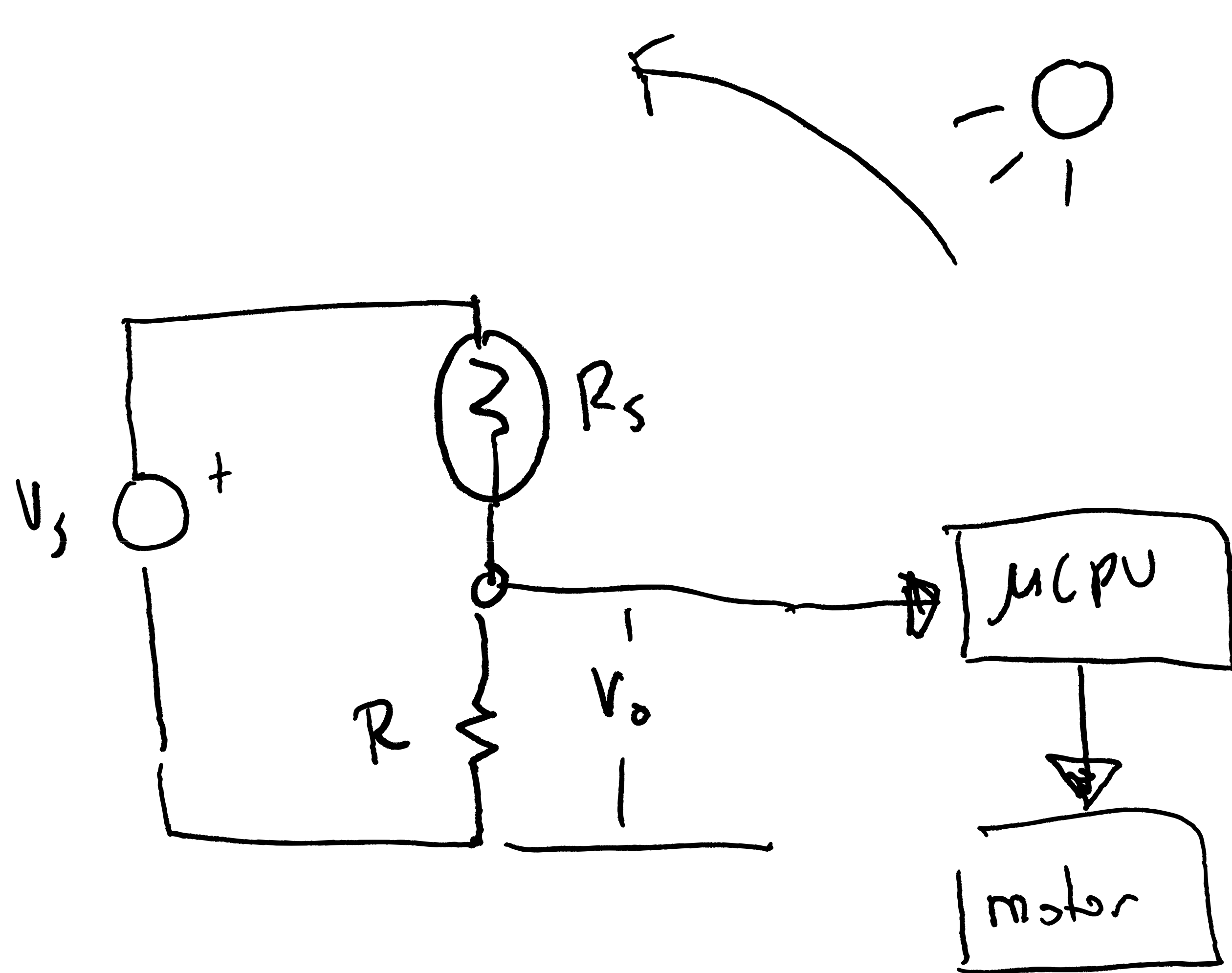
# Example: Photoresistor controls a motor


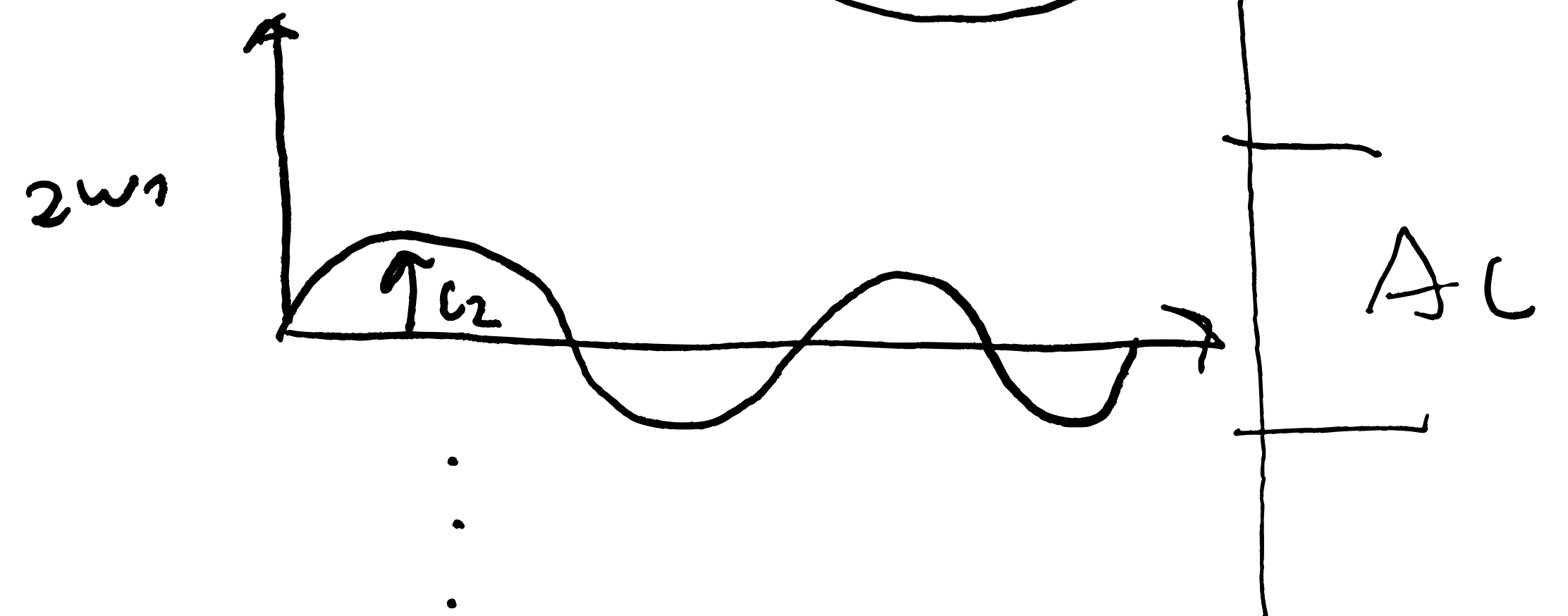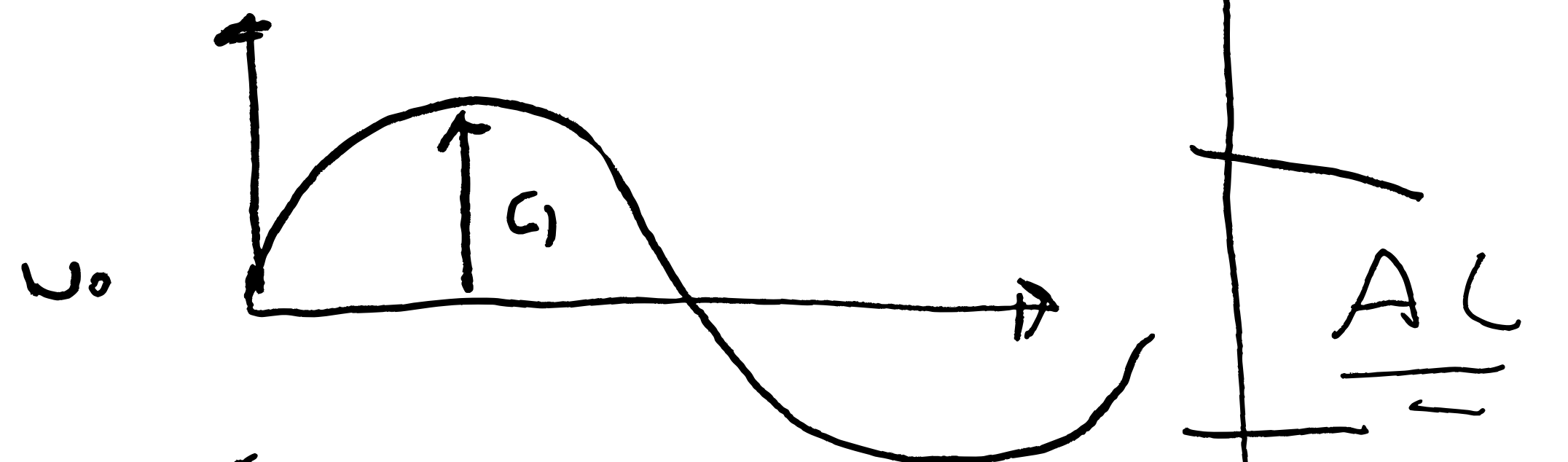
$$V_o(t) = C_0 + \sum_{n=1}^{\infty} C_n \cos(n\omega_0 t + \phi_n)$$



AC

AC



# AC Signal Definition (for a single freq.)


$$V(t) = V_m \sin(\omega t + \phi)$$

$V_m$ : amplitude

$\phi$ : phase

$\omega$ : freq. (rad/s)

$f = \frac{\omega}{2\pi}$  (Hz)

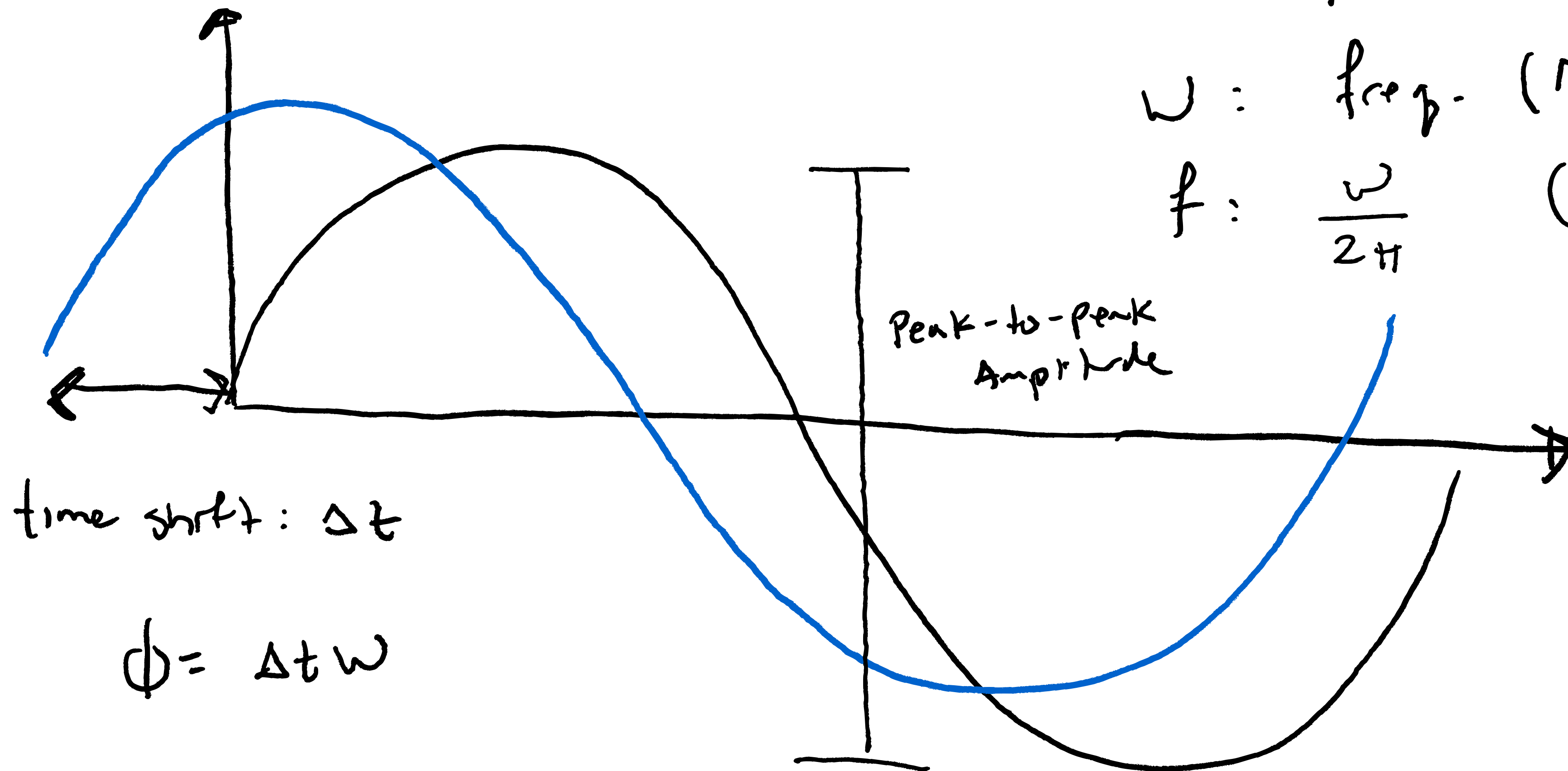

# Steady State Analysis

current  $i$ , voltage  $v$  of

every element are AC signals

with same freq. as

excitation freq.



# Euler's Formula

$$\underbrace{e^{j(\omega t + \phi)}}_{\text{exponential form}} = \underbrace{\cos(\omega t + \phi) + j \sin(\omega t + \phi)}_{\text{rectangular form}}$$

fundamental relationship between trig-  
functions & the complex exponential

# Phasors

We can treat  $V, I$  in AC

as phasors:


$$V = V_m e^{j(\omega t + \phi)}$$

exp. form

$$= V_m \angle \phi$$

phasor form
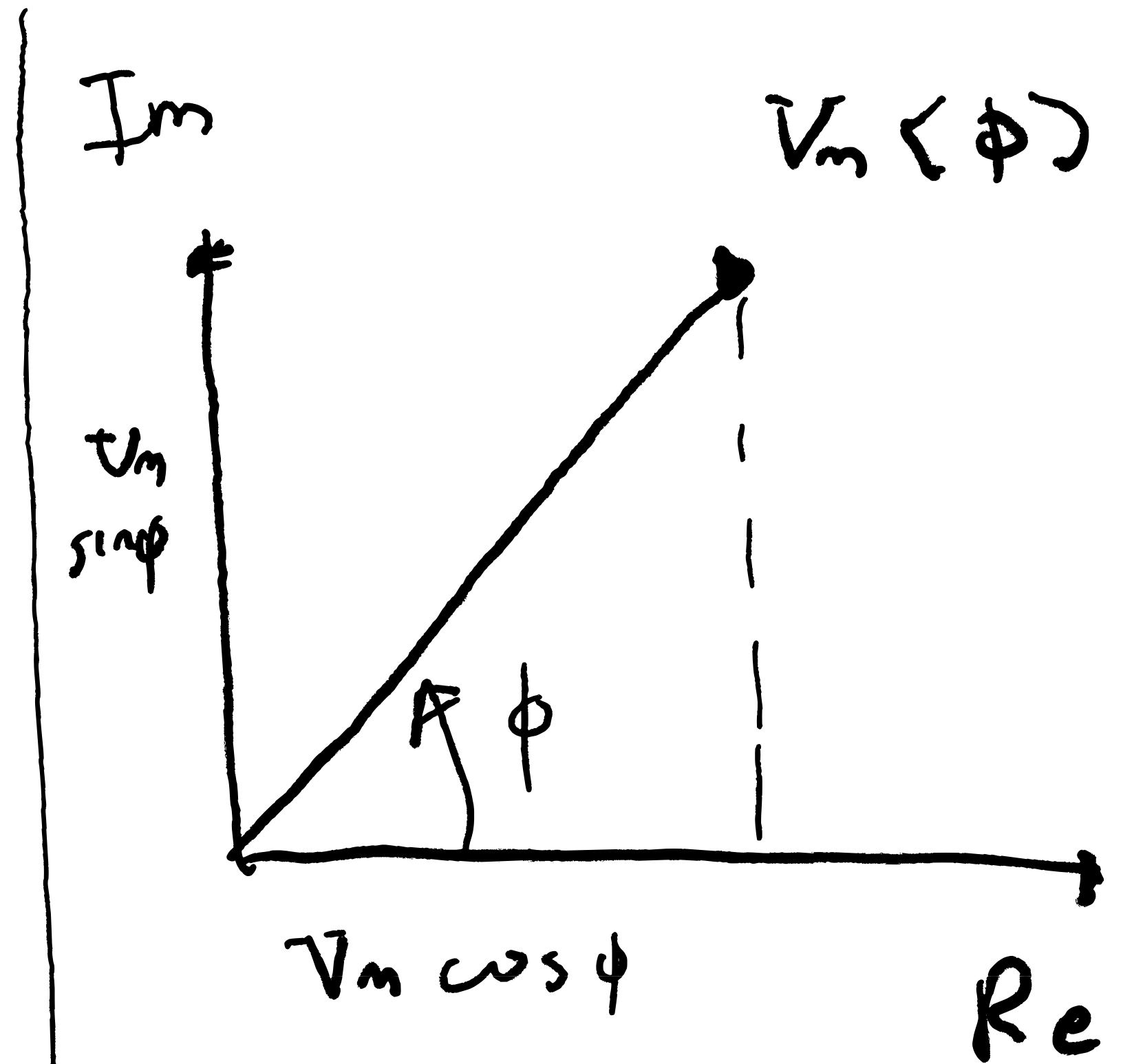
$$= V_m [\cos(\omega t + \phi) + j \sin(\omega t + \phi)]$$



---

Complex number =  $x + jy$

## Example 2.6

$$V(t) = 5.00 \sin(t - 1) \text{ V}$$

Find amplitude, frequency, and phase

$$V_m = 5 \text{ V}$$

$$f = \frac{1}{2\pi} \text{ Hz}$$

$$\phi = -1$$

## ■ CLASS DISCUSSION ITEM 2.7


### *Reasons for AC*


Justify and fully explain the reasons why AC power is used in virtually all commercial and public utility systems. Refer to the reasons just listed.

- \* AC power is easy to generate with rotating machinery.
- \* AC can power rotating machinery
- \* AC power is more efficient  
↳ step up to high voltage

# Generalized Ohm's Law

$$V = RI$$

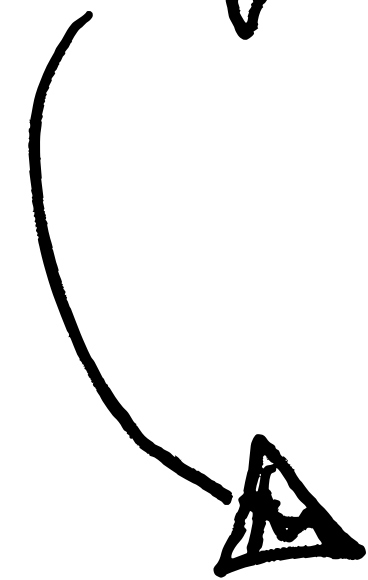
$$\triangle V = ZI$$

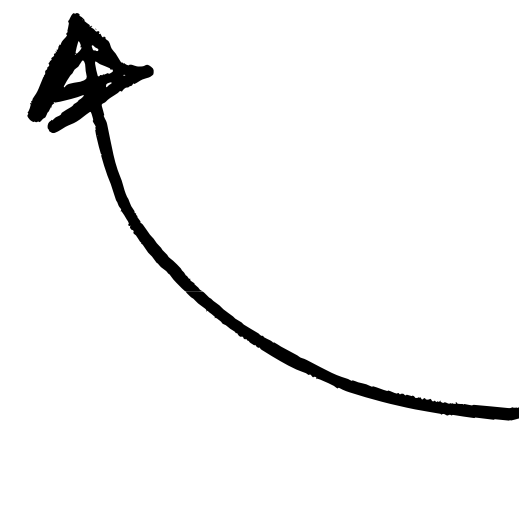
$$Z = f(\omega)$$

\* In general impedance is a function of frequency.

# Generalized Ohm's Law

What is the impedance of a resistor?

$$V = RI$$

$$\uparrow Z_R = R \quad (\text{no freq. dependence})$$

What is the impedance of an Inductor?

$$V = L \dot{I}$$

$$\rightarrow I = I_m e^{j(\omega t + \phi)}$$

$$\dot{I} = j\omega I_m e^{j(\omega t + \phi)}$$

$$\bar{V} = L j\omega \bar{I}_m e^{j(\omega t + \phi)}$$

$$\begin{aligned} V &= L \dot{I} \\ &= \underbrace{L j\omega}_{Z_L} \underbrace{I_m e^{j(\omega t + \phi)}}_I \end{aligned}$$

$$Z_L(\omega) = j\omega L$$

$$e^{j\phi} = (\cos(\phi) + j\sin(\phi))$$

$$\phi = 90^\circ$$

$$e^{j90^\circ} = 0 + j$$

$$\therefore Z_L = \omega L \angle 90^\circ$$


voltage leads current by  $90^\circ$

# Generalized Ohm's Law

$$Z_L = \omega L \langle 90^\circ \rangle$$

$$\omega \rightarrow 0 \quad Z_L = 0$$

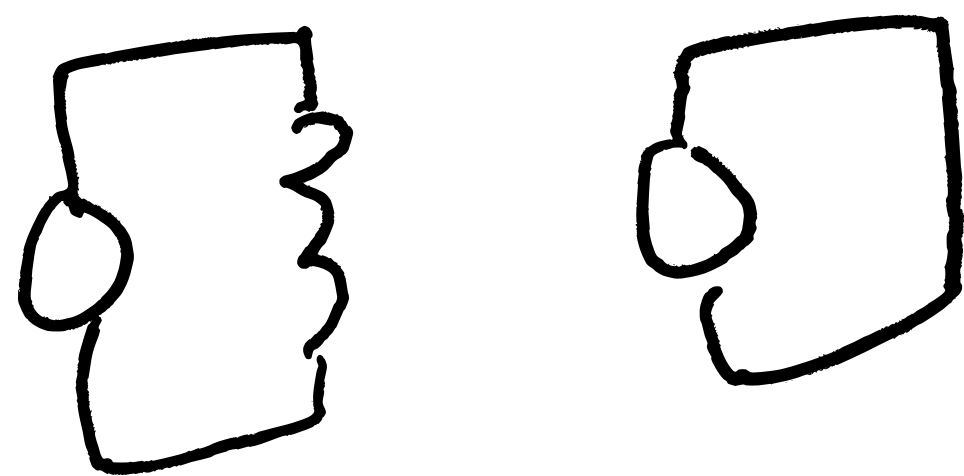inductor acts like a  
short circuit at low freq.



$$\omega \rightarrow \infty \quad Z_L = \infty \text{ open circuit}$$

What is the impedance of a Capacitor?

$$I = C \dot{V}$$

$$V = V_m e^{j(\omega t + \phi)}$$

$$\dot{V} = j\omega V_m e^{j(\omega t + \phi)}$$

$$I = j\omega C V$$

$$V = \frac{1}{j\omega C} I$$

$$Z_C = \frac{1}{\omega C} \langle -90^\circ \rangle$$


Voltage lags current by  $90^\circ$

$\omega \rightarrow 0$	$Z_C = \infty$
$\omega \rightarrow \infty$	$Z_C = 0$



# How to analyze AC circuits?


> same way as DC, except use  $Z_L$

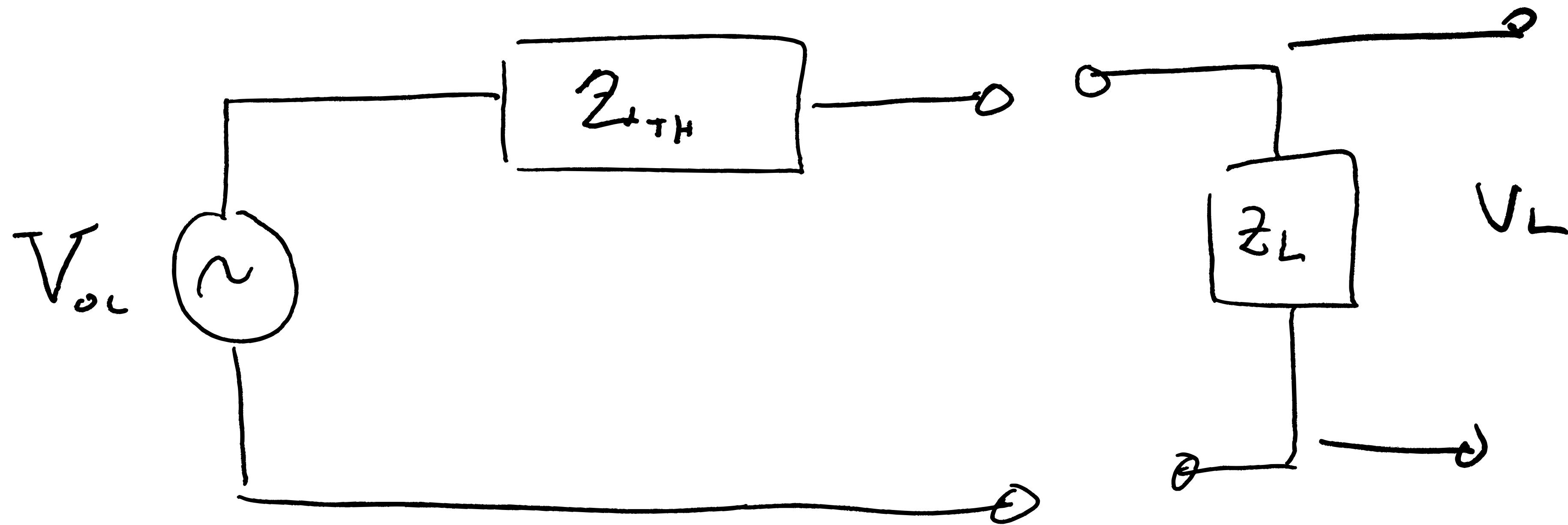

$$V_L = \left( \frac{Z_L}{Z_{TH} + Z_L} \right) V_{oc}$$

Transformers : only for AC.

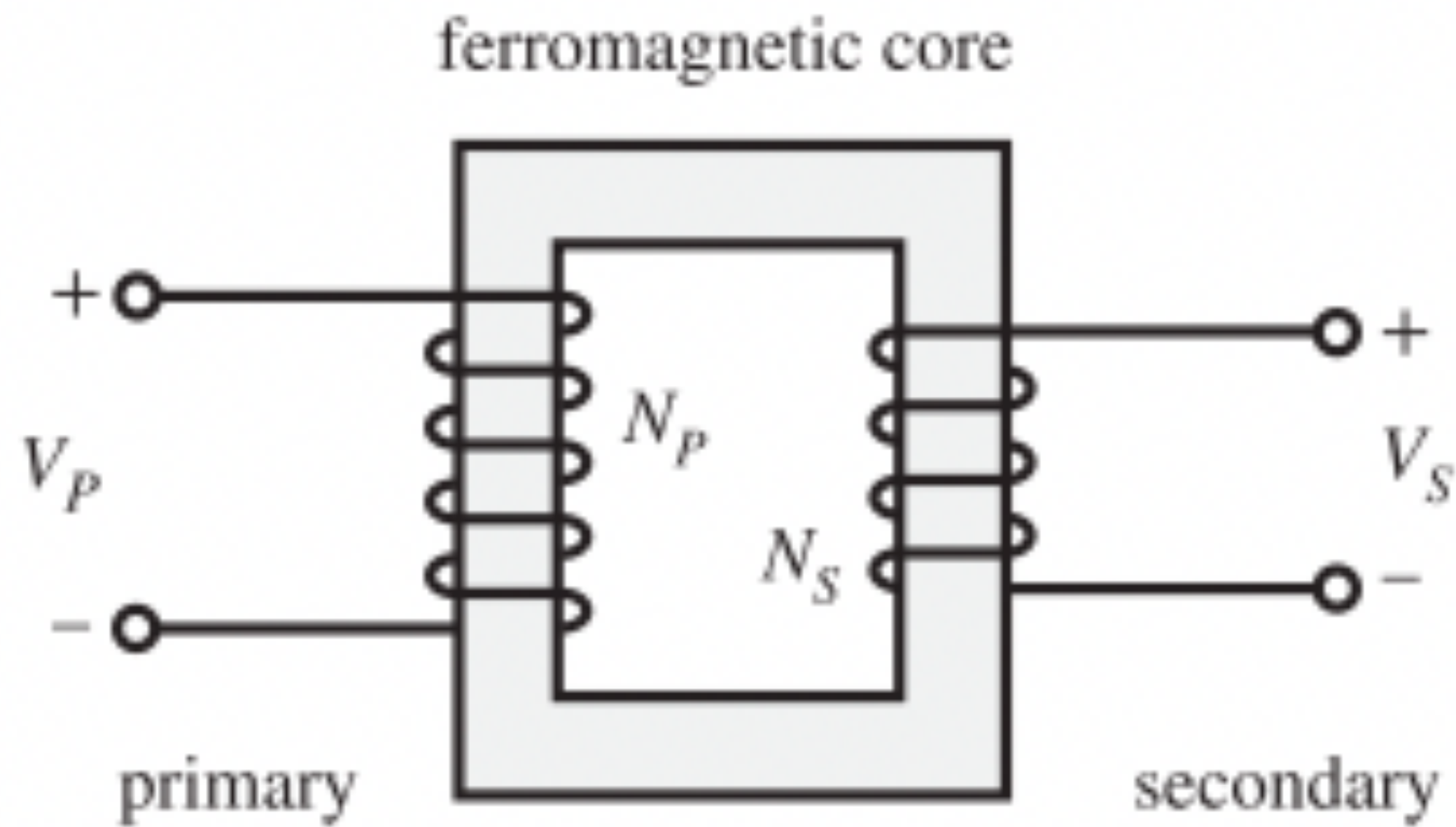• Change the relative amplitude of voltage / current in an AC circuit



$N_p$  : # of coils

$N_s$  : # of coils


$$\frac{V_p}{N_p} = \frac{V_s}{N_s} = \frac{-d\phi}{dt} \rightarrow \text{flux}$$

$$\therefore V_s = \underbrace{\frac{N_s}{N_p}}_{\text{like gens}} V_p$$

$N_s > N_p \rightarrow \frac{N_s}{N_p} > 1$  step-up

$N_s < N_p \rightarrow \frac{N_s}{N_p} < 1$  step down

# Transformers

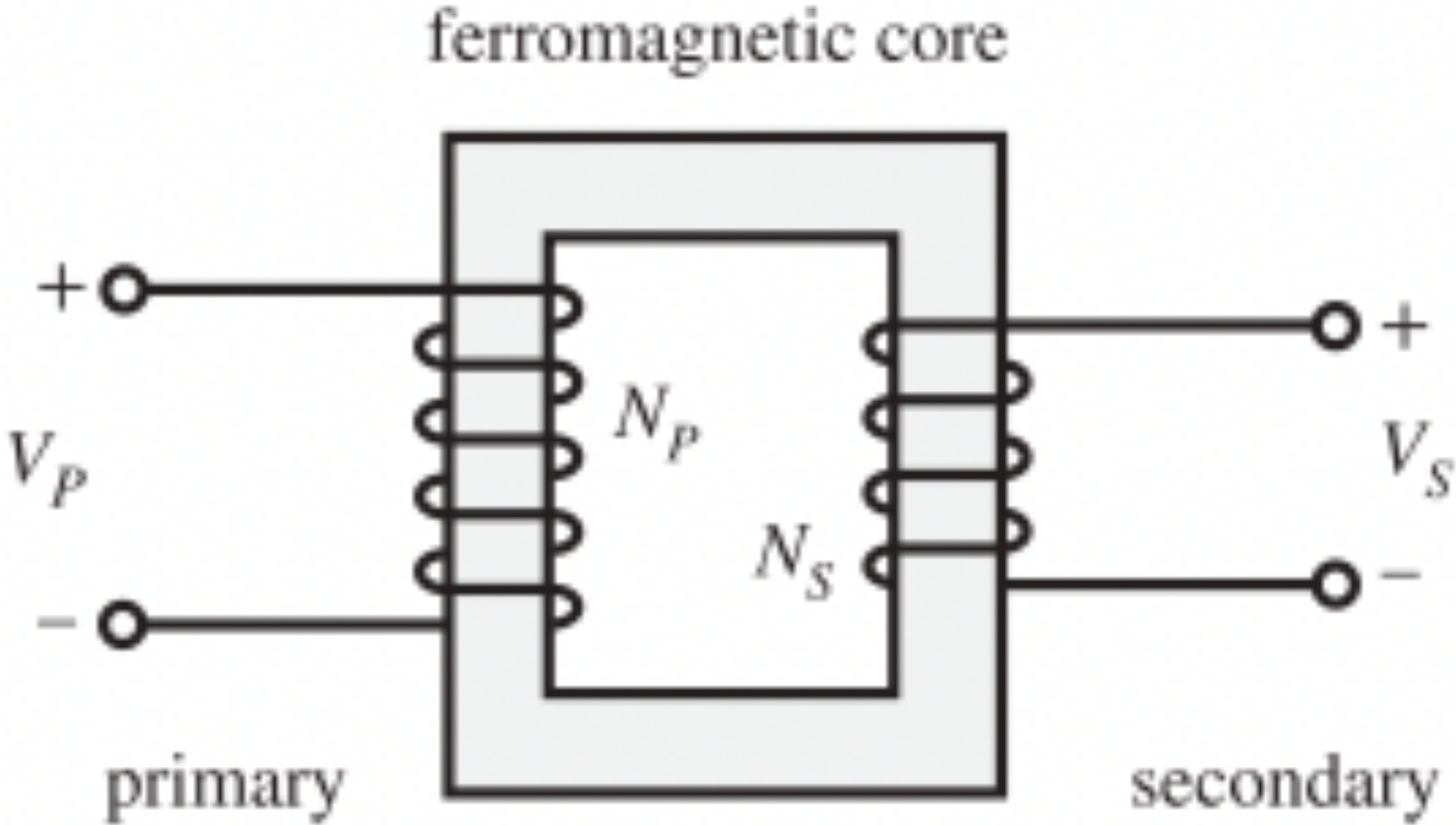

$P_{in} = P_{out}$   $\rightarrow \eta \approx P_{in} = P_{out}$

$V_p I_p = V_s I_s$  ideal

$I_s = \frac{V_p}{V_s} I_p$

$I_s = \frac{N_p}{N_s} I_p$

$V \uparrow$   $I \downarrow$

## Semiconductors — Ch.3

Sensors  
signal processing  
display (UI)

Focus: diodes  
transistor

## Semiconductor Physics

- metal (e.g. conductors) have  
a large number of weakly bound electrons

# Semiconductor Physics

- under an electric potential  
voltage

these electrons flow  
current

- other materials (insulators)  
have valence electrons,  
which tightly bound

- no flow, order potential  
for insulator.
- 

- Semiconductor  
have properties somewhere  
in between  
ex: silicon, germanium
- current-carrying characteristics  
depend on environment:  
temperature or light

\* properties of semiconductors can be significantly  
changed by doping: insert other elements onto  
lattice

# Semiconductor Physics: Types of dopants

• donor : enhances  
electron conductivity

n-type  
(negative)

• acceptor : reduces  
electron conductivity

p-type  
(positive)

The whole point of  
doping to control

# of charge carriers

- n-type : charge carrier  $e^-$

- p-type : charge carrier  $\oplus$

---

The interaction of p-  
i n-type areas within  
a single device is  
Basis for semiconductors

# Junction Diode: pn-junction



# Junction Diode: pn-junction

# Junction Diode: pn-junction

# Diode water analogy

# Semiconductor Intro Summary