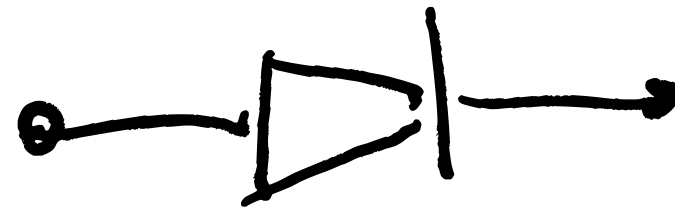


Last time:

> diode



on /off behavior

> diode circuits

Today:



Bipolar Junction Transistor (BJT)

■ CLASS DISCUSSION ITEM 3.4

Voltage Limiter

The diode portion of the following circuit is called a **voltage limiter**. Explain why. Sketch some input and output waveforms that illustrate the circuit's behavior. Note:

$$V_H > V_L$$

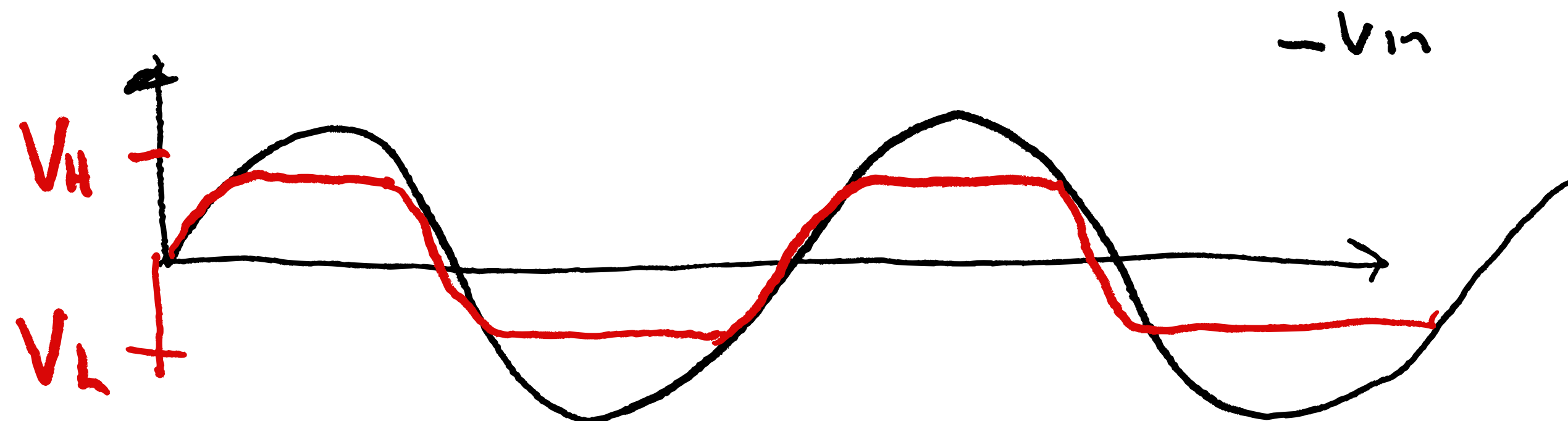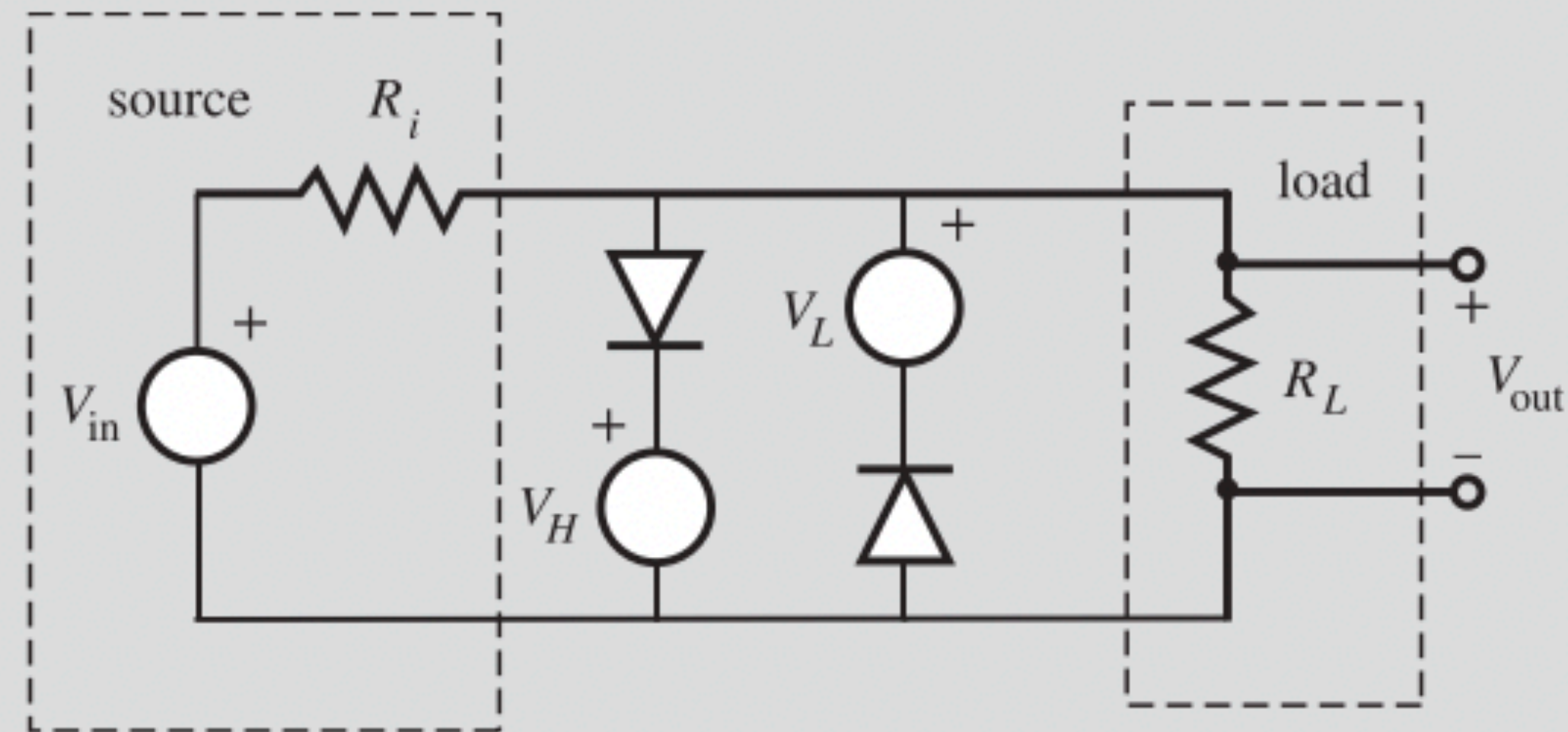

Zener Diode: Voltage regulator

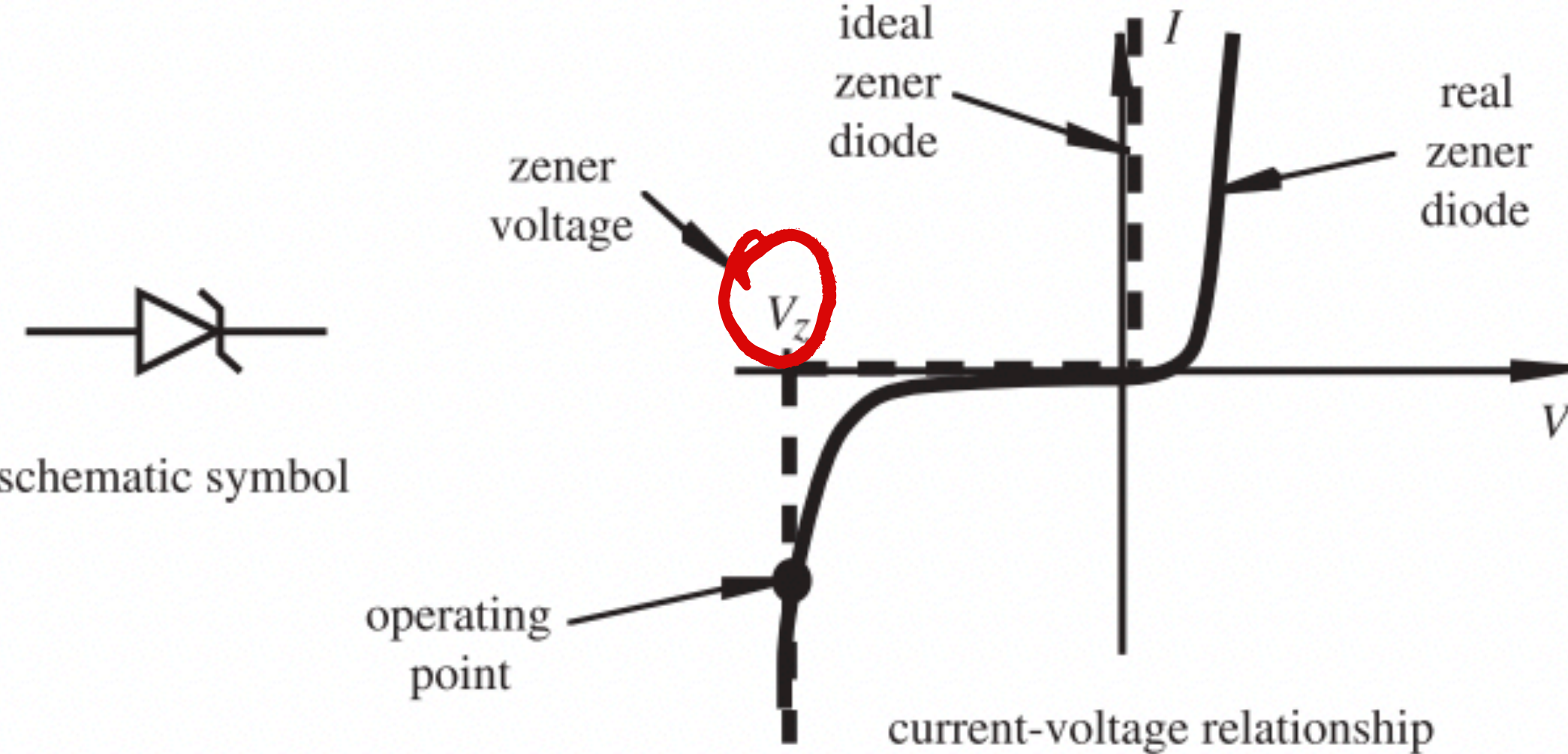


Figure 3.14 Zener diode symbol and current–voltage relationship.



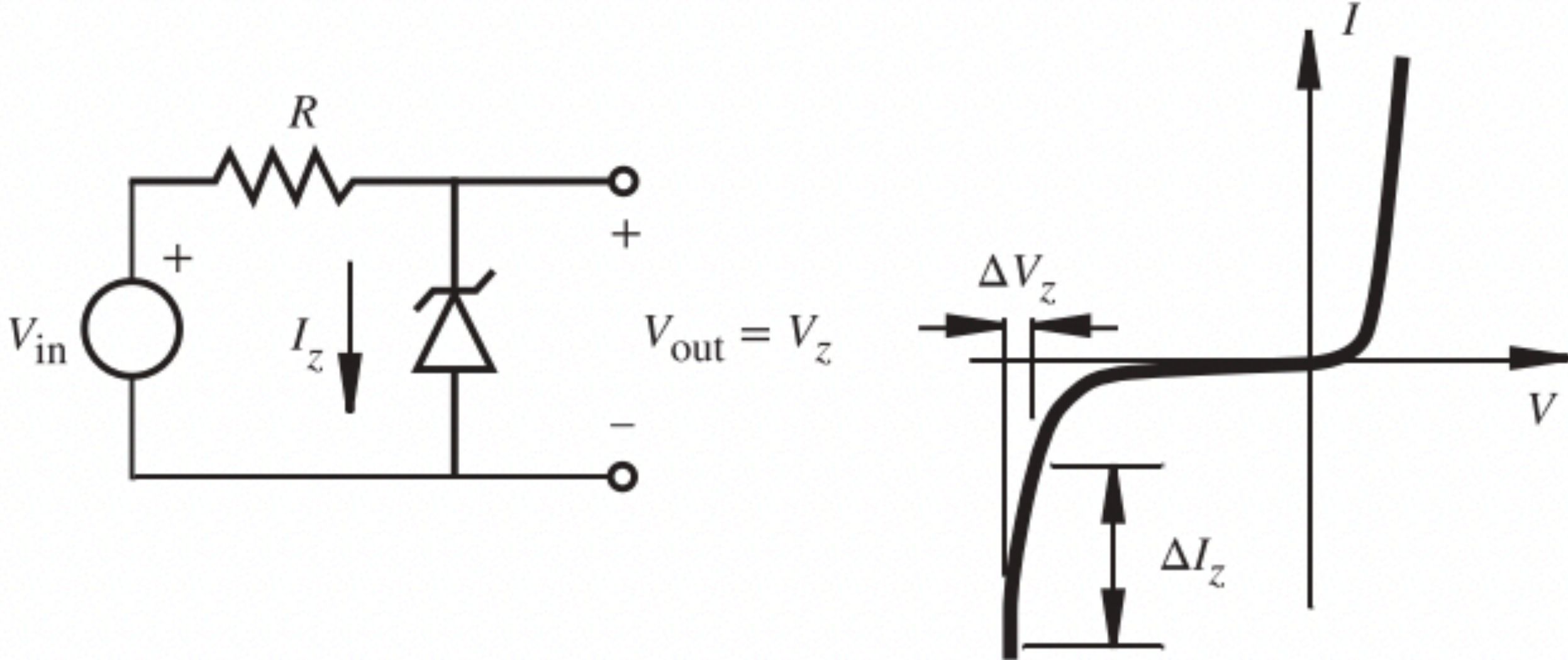
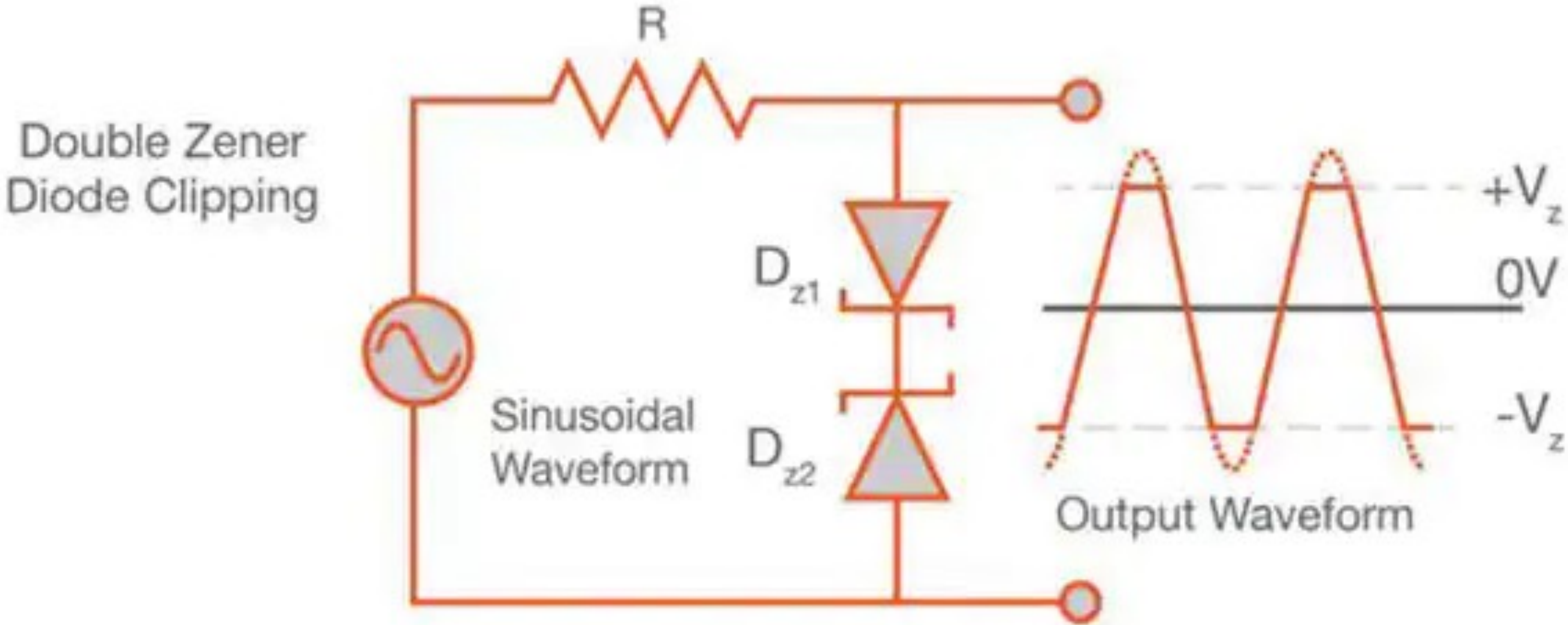
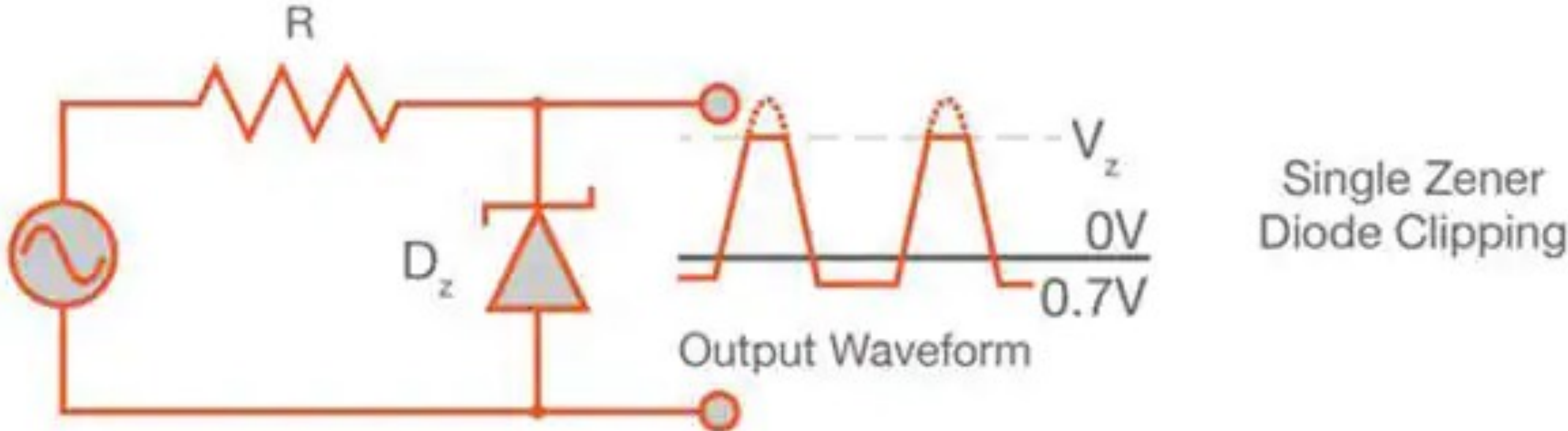


Figure 3.15 Zener diode voltage regulator.

Other Applications

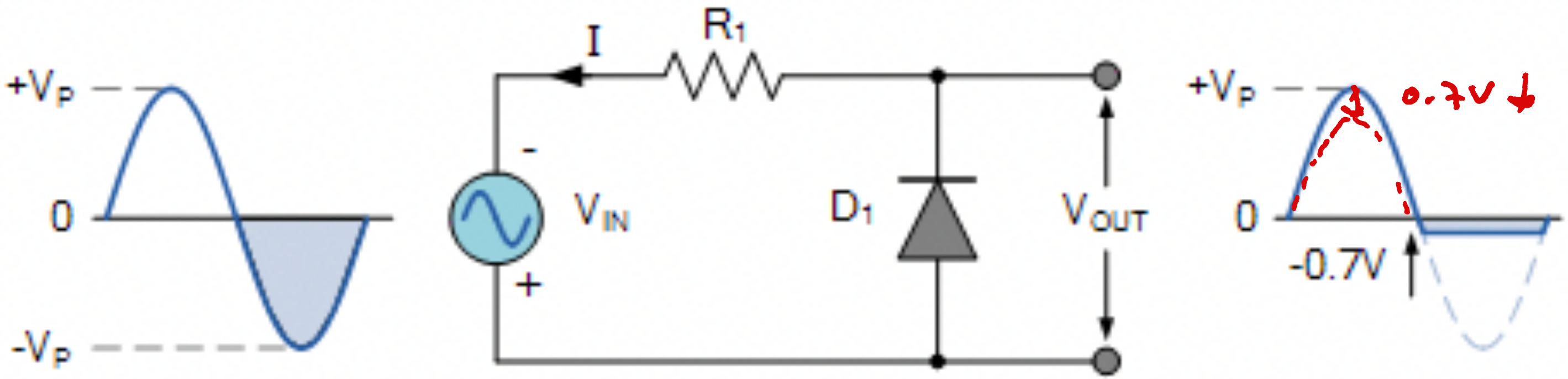

Compare with normal diode

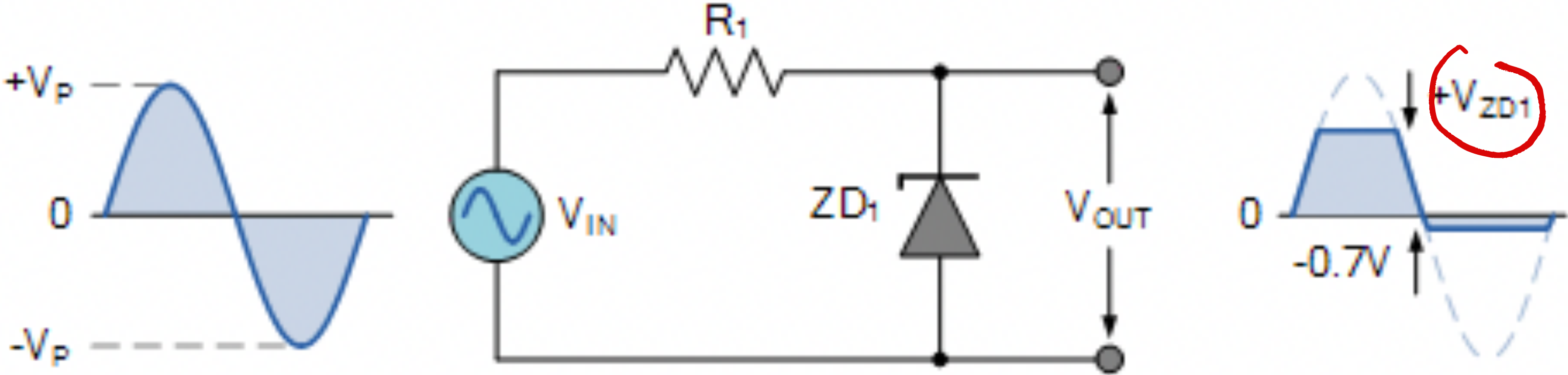

Transistors Overview

- these are the heart of nearly every electronic device
mechatronic devices
- the first transistor, BJT
invented in 1948
 - William Shockley, Bell Labs
- most important
tech. innovation in the 20th



Basically two functions

① Switching : control large voltage / current
using small voltage / current

② Amplification : magnify voltage / current
by transferring energy from
another source

Main Advantages

① Amplification : transmitting signal then amplify



② Switching : Build logic circuits

Ch. 6



Most Common Types of Transistors

Bipolar Junction	Field Effect
<ul style="list-style-type: none">• 3 terminal• Two PN junction	<ul style="list-style-type: none">• 3 terminal• Channel of doped semiconductor<ul style="list-style-type: none">→ conductivity channel



Bipolar Junction NPN transistor

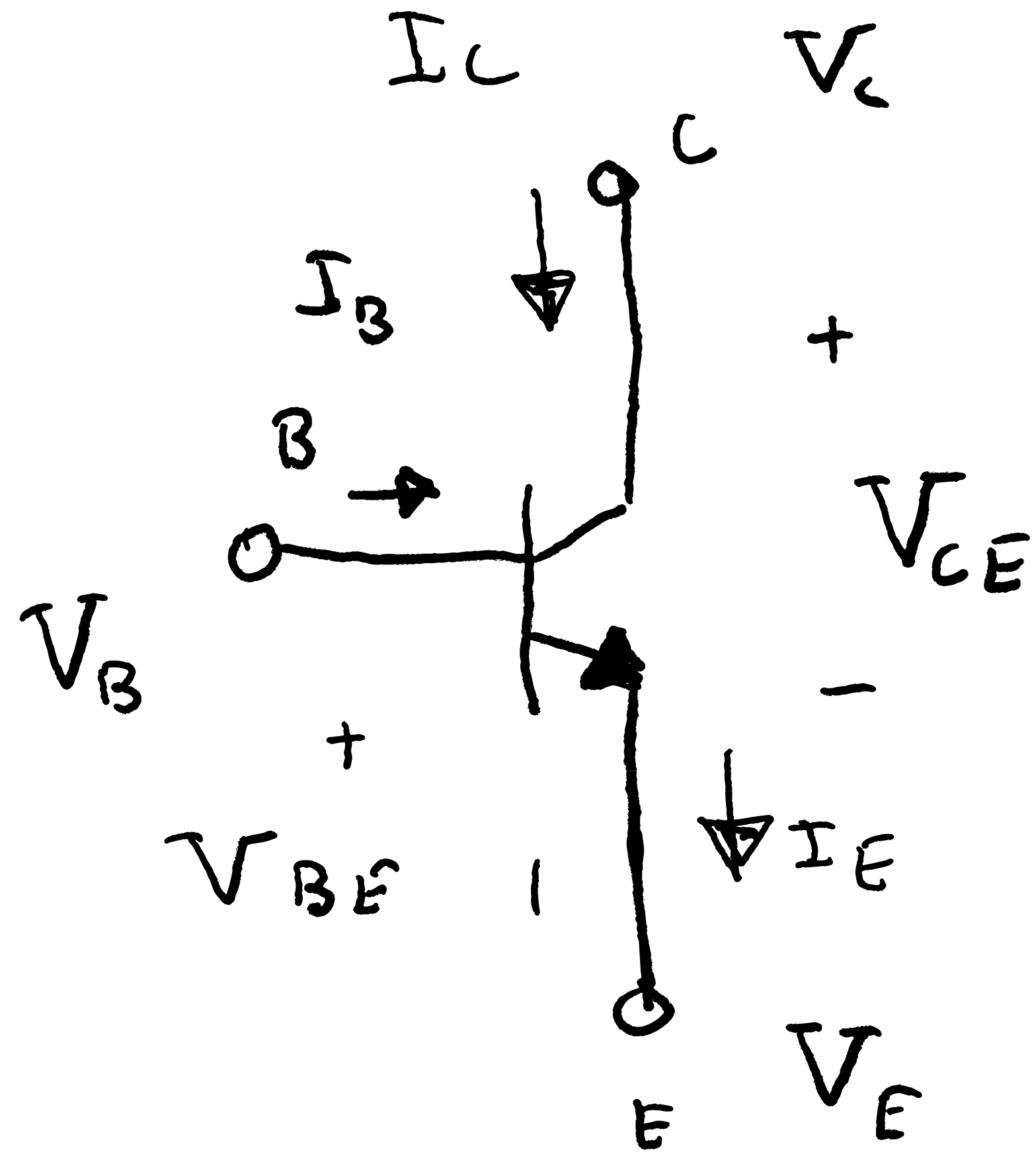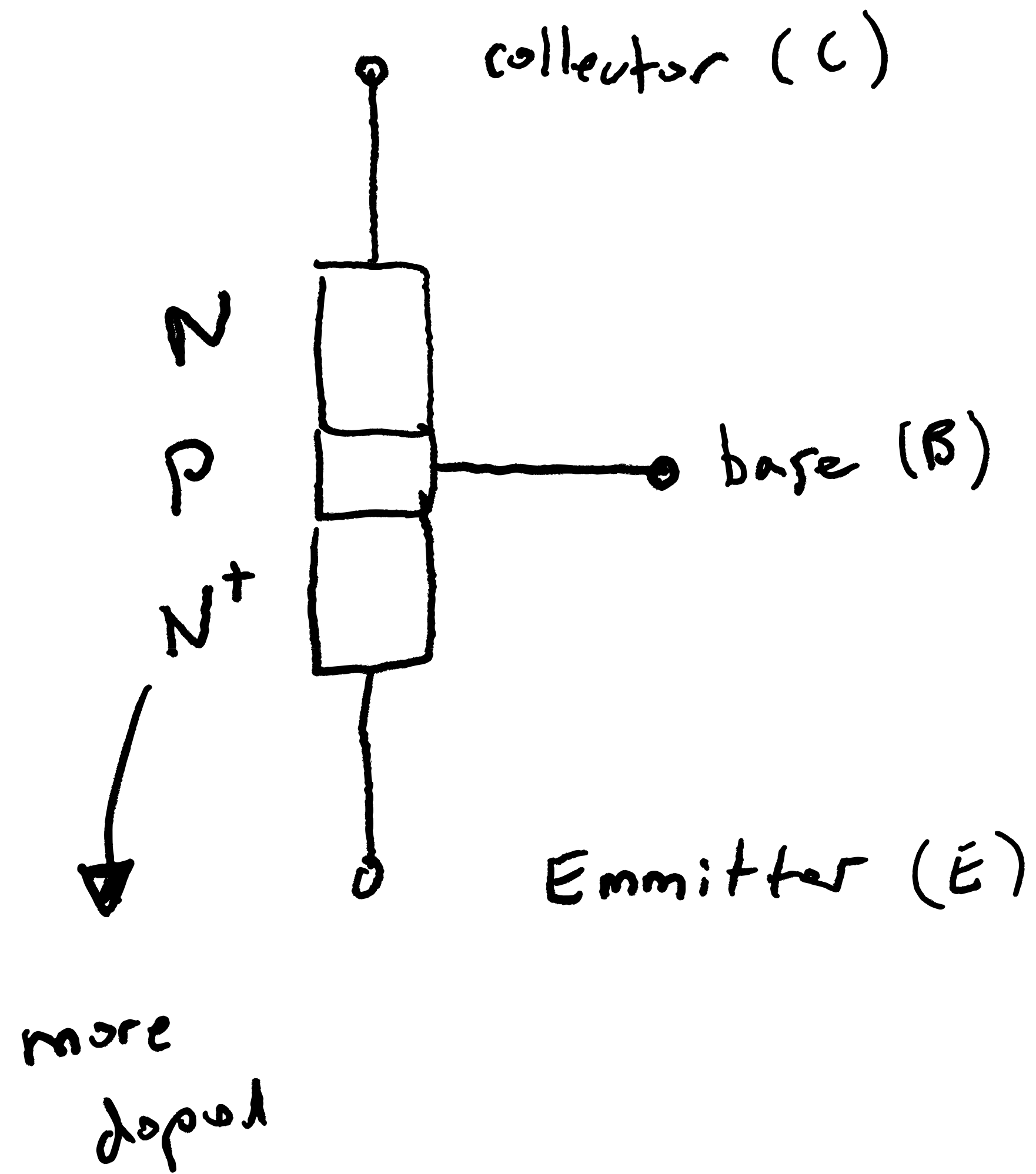

Bipolar Junction PNP transistor

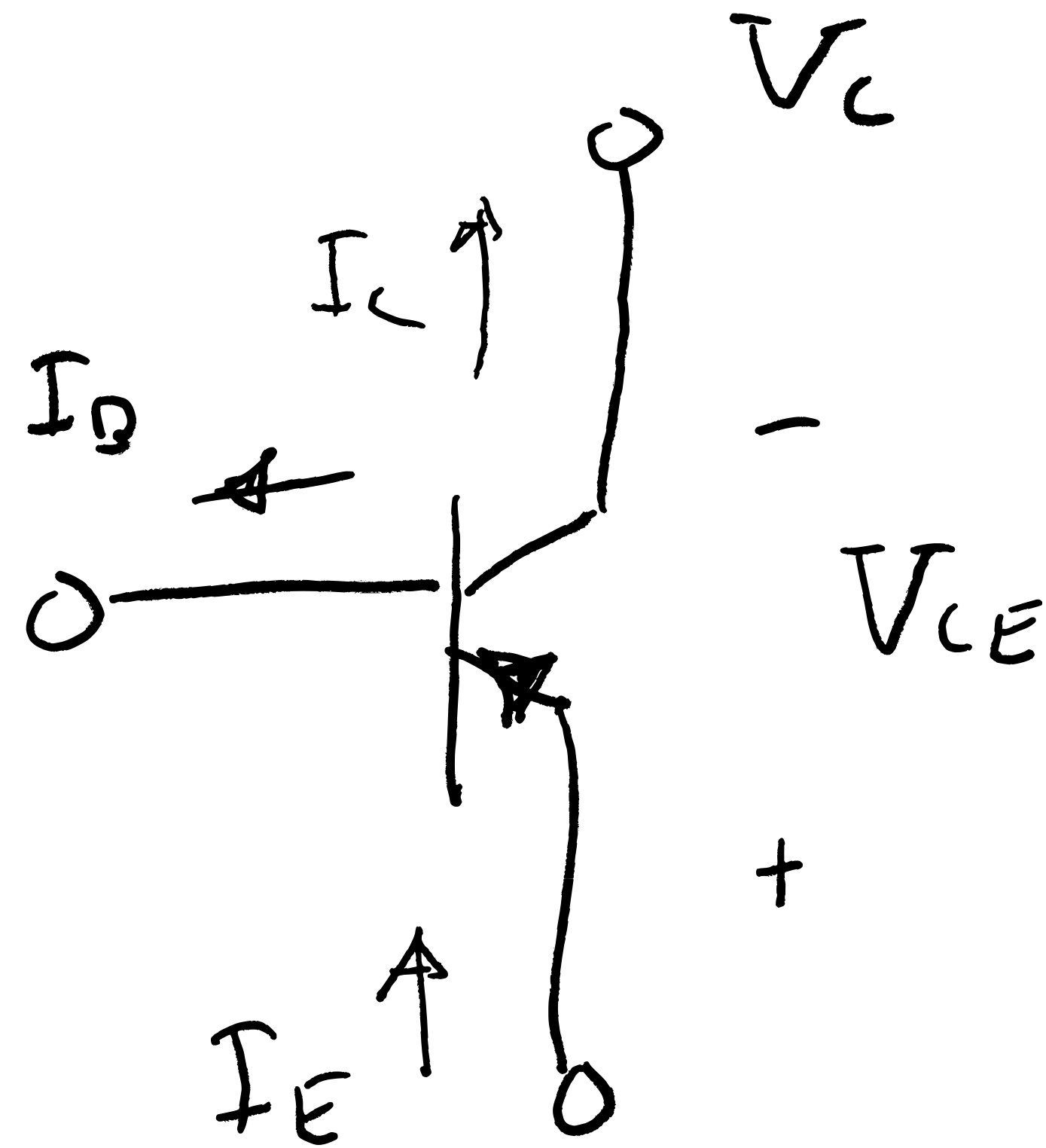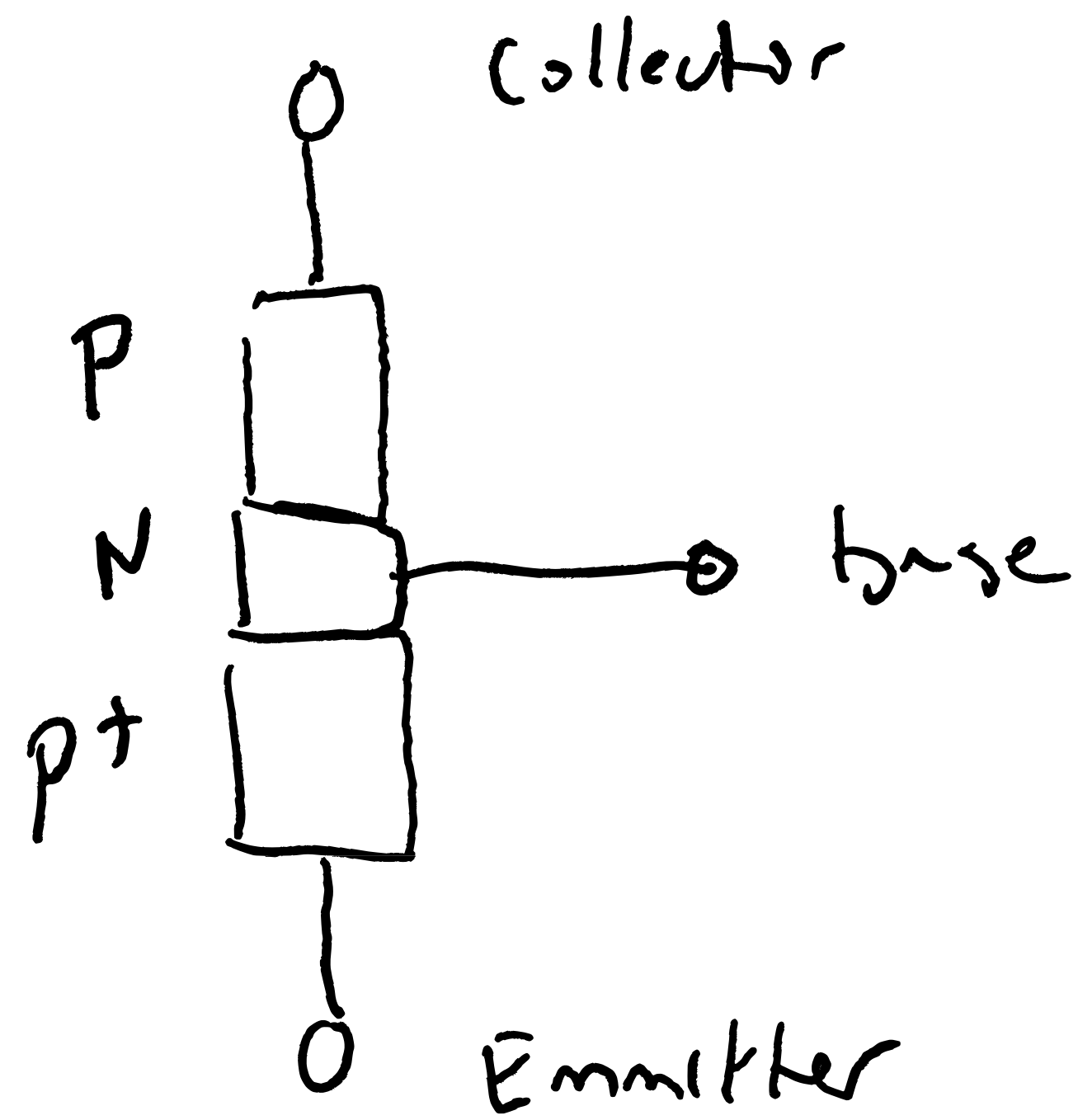


NPN Working Principle

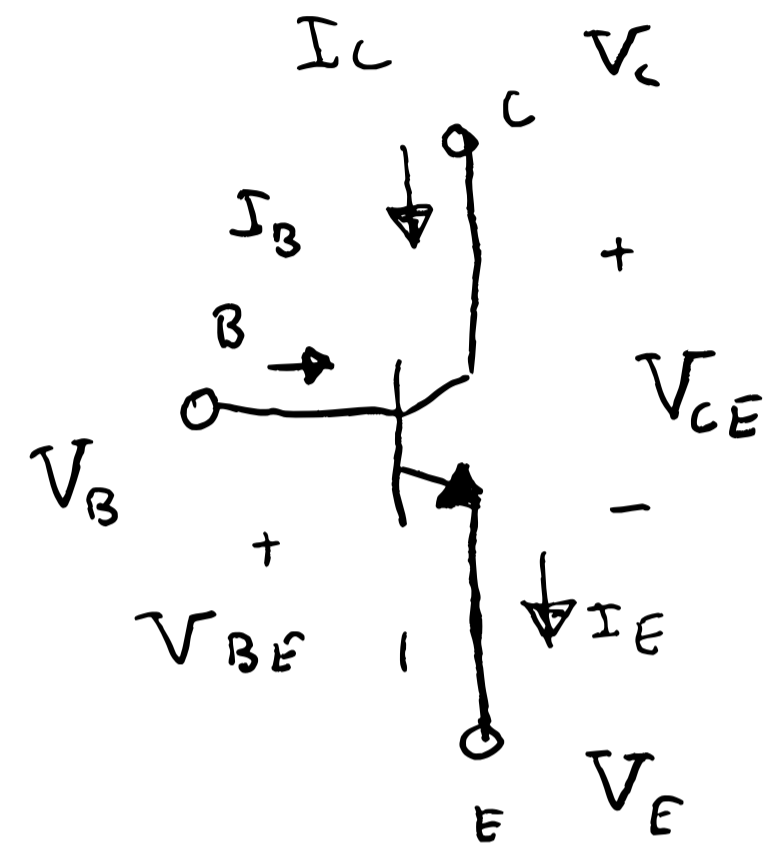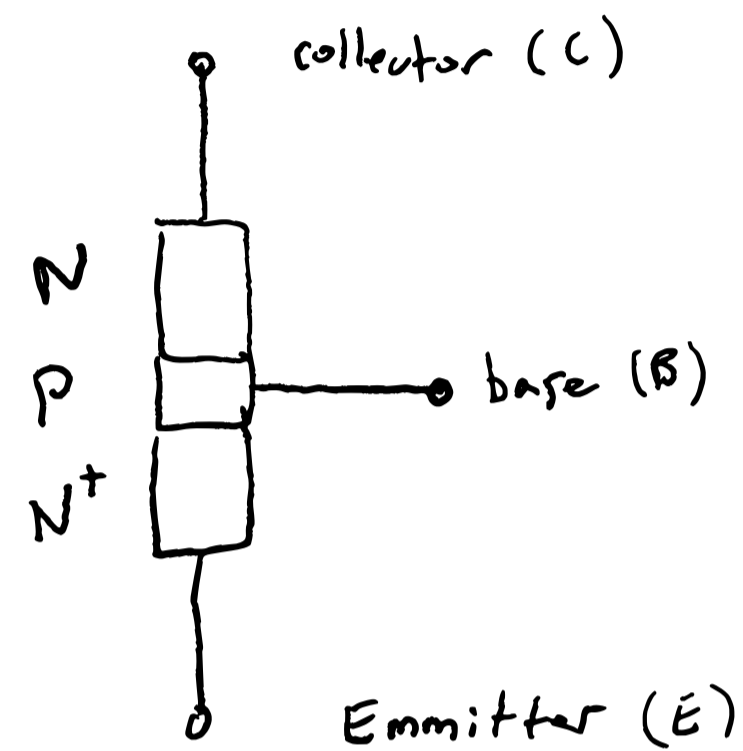

$$\begin{cases} I_E = I_C + I_B \\ V_{BE} = V_B - V_E \\ V_{CE} = V_C - V_E \end{cases}$$

Basic Idea

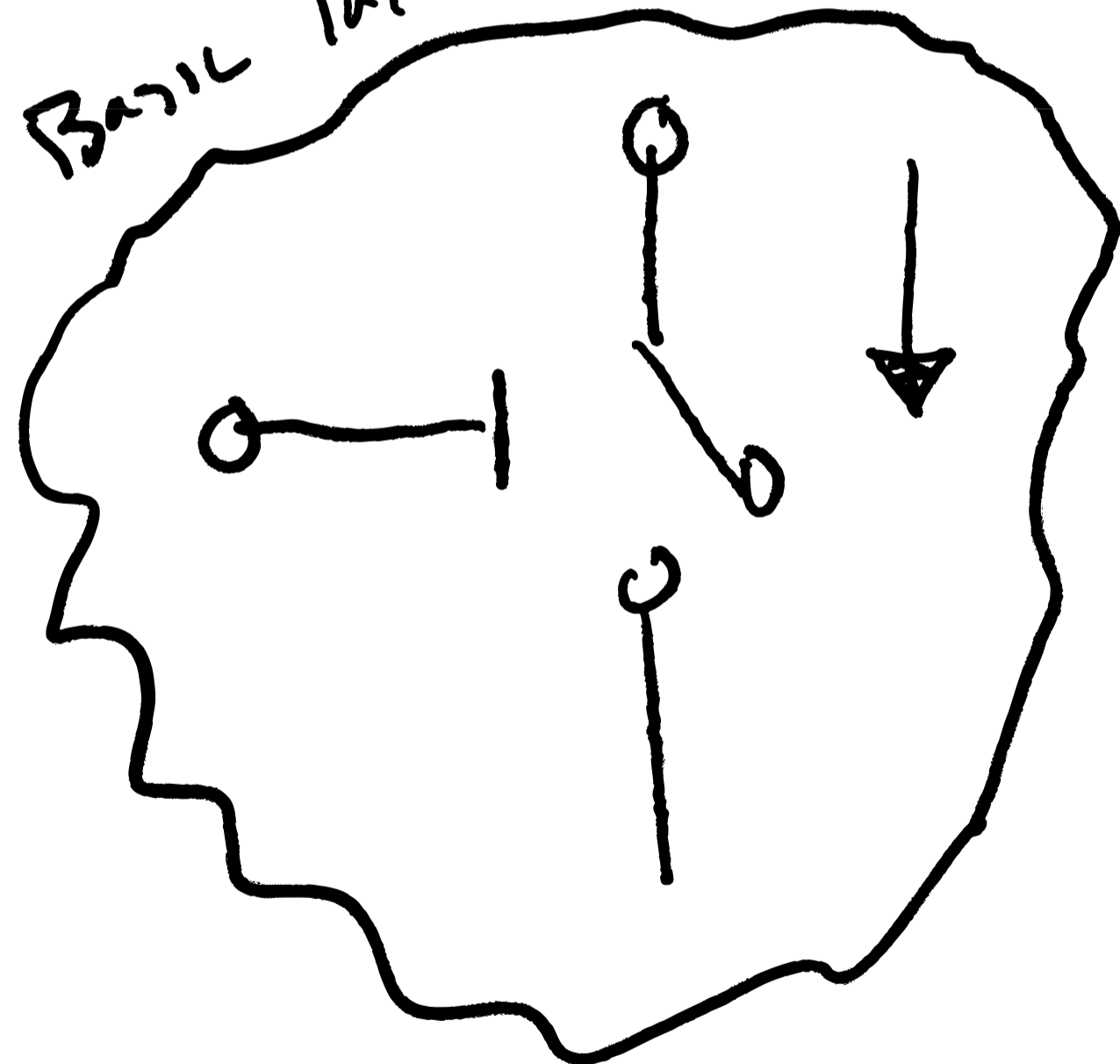

$$V_{BE} = 0.7V$$


For transistor to
be on
base-to-emitter
forward bias

→ Large collector
current (I_C) flows,
with only small (I_B)

$$I_B \ll I_C$$




• Voltage drop V_{CE} (0.2V)

Transistor Water Analogy

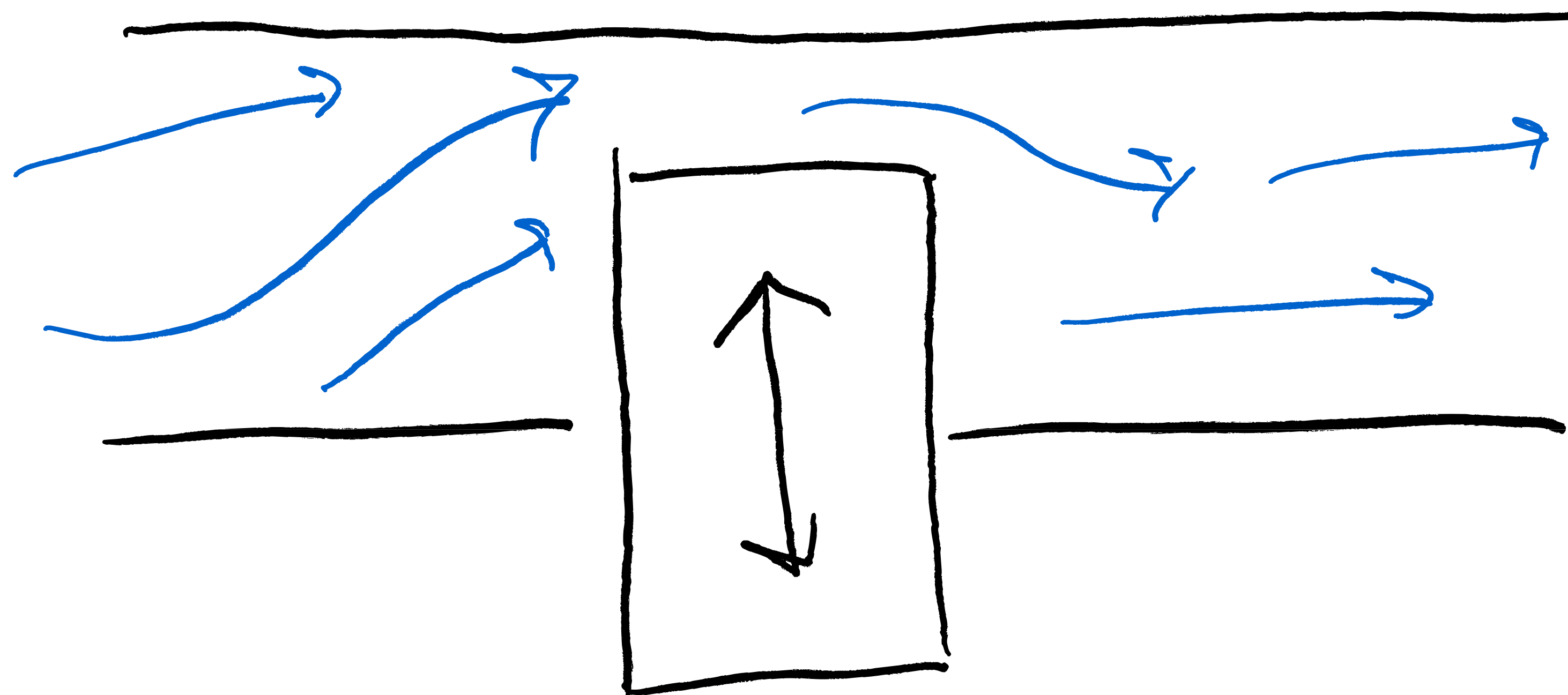


variable valve, controlled by I_B

Common Emitter Circuit

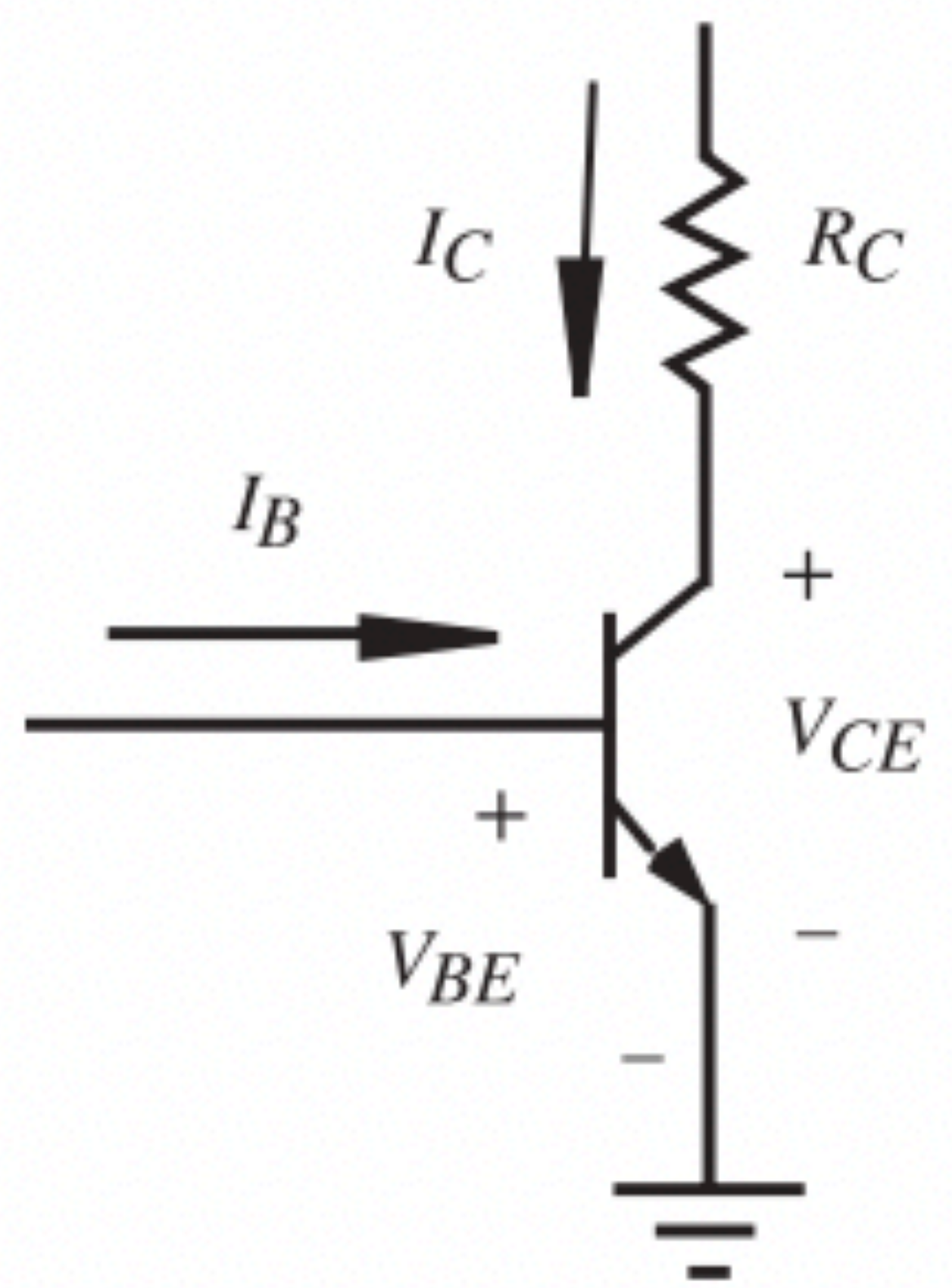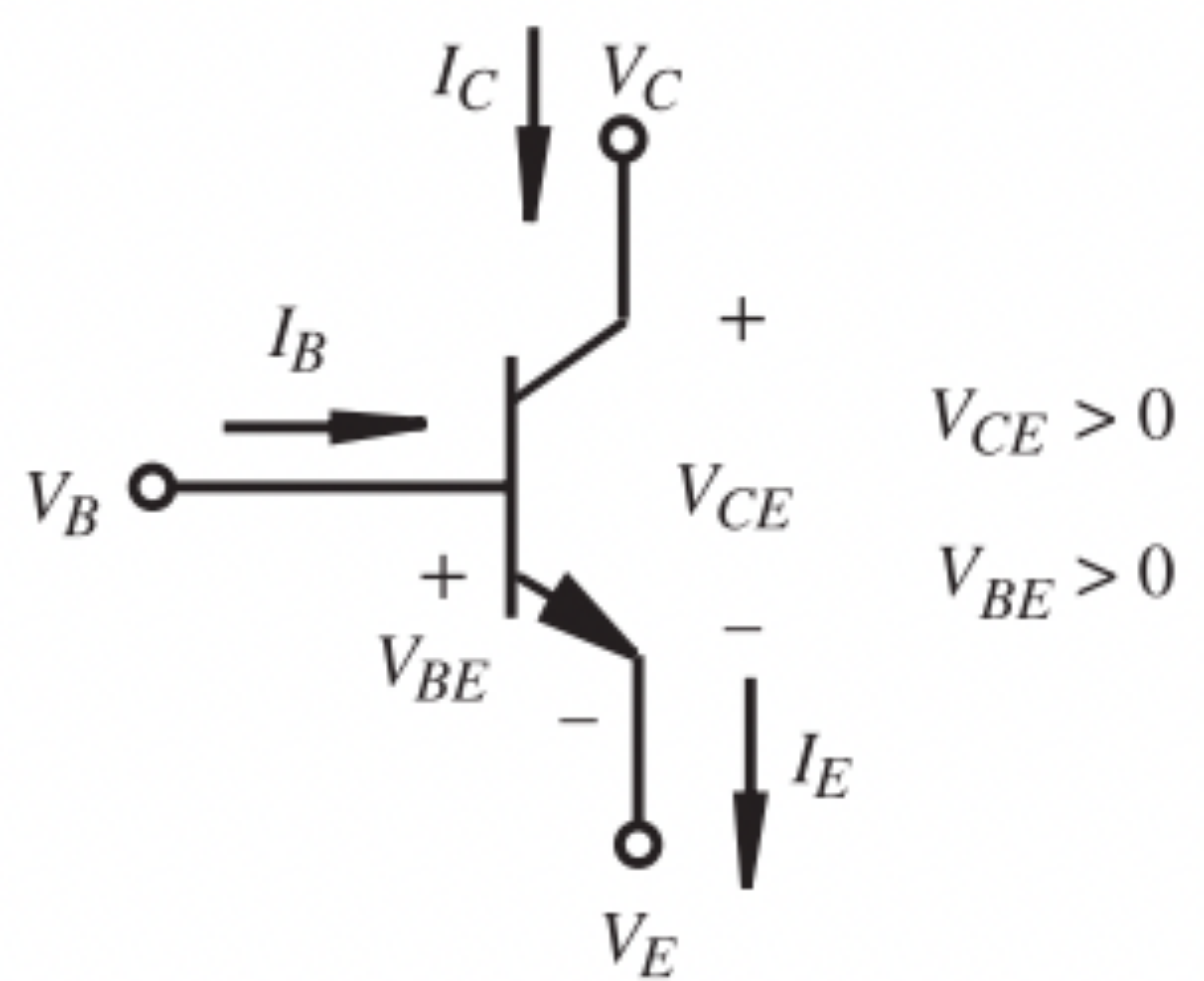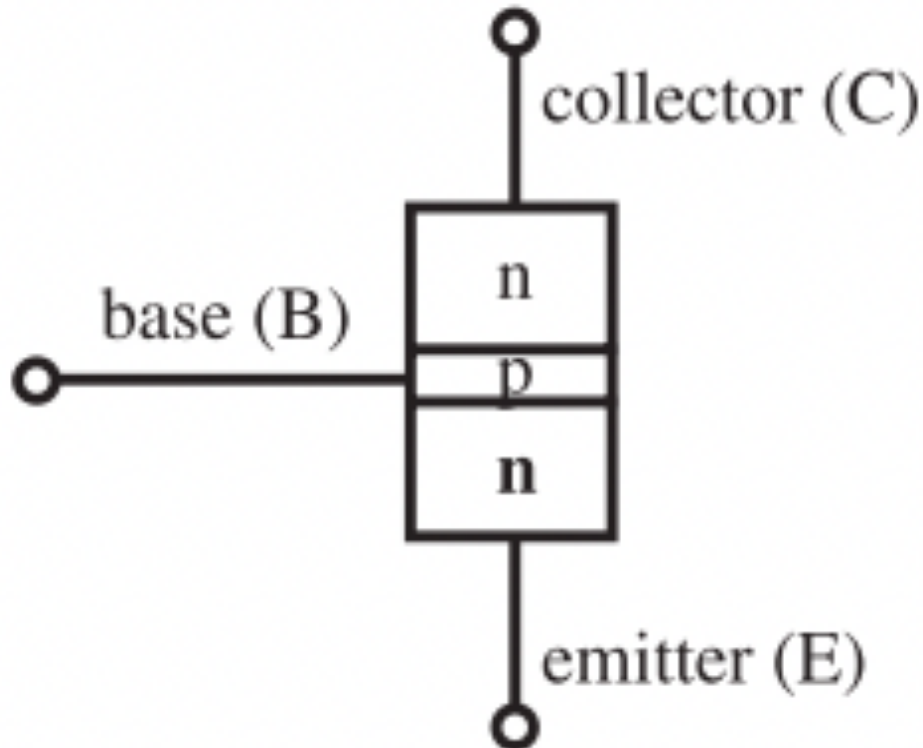

NPN Working Principle

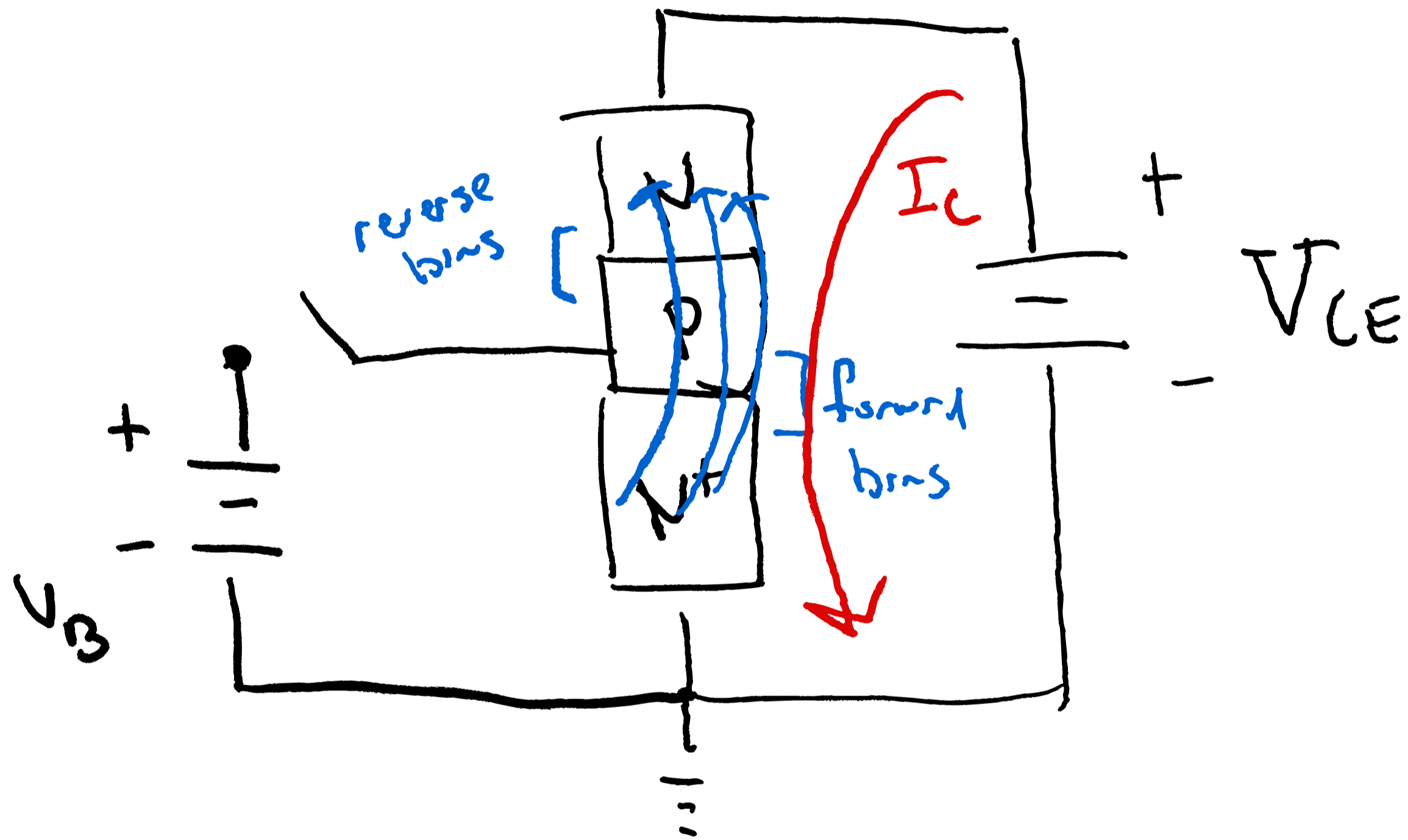Collector : collects e^- } When transistor is ON
 emitter : emits e^- }



$$V_B = V_E + 0.7V$$

P-section is small, e^- have enough momentum to cross over

Key idea

$$I_C = \beta I_B \quad \xrightarrow{100}$$

$h_{fe} \Rightarrow$ transistor data sheet

BJT Operation Modes Common Emitter

Active:

$\uparrow I_B \rightarrow \uparrow I_C$

- proportional currents

$$I_C = \beta I_B$$

amplifier

Saturation:


$V_{CE} \approx 0$;
max current flows

- $I_E \gg I_B$

$$I_B \approx I_C$$

- both junctions become forward

• behaves like short circuit


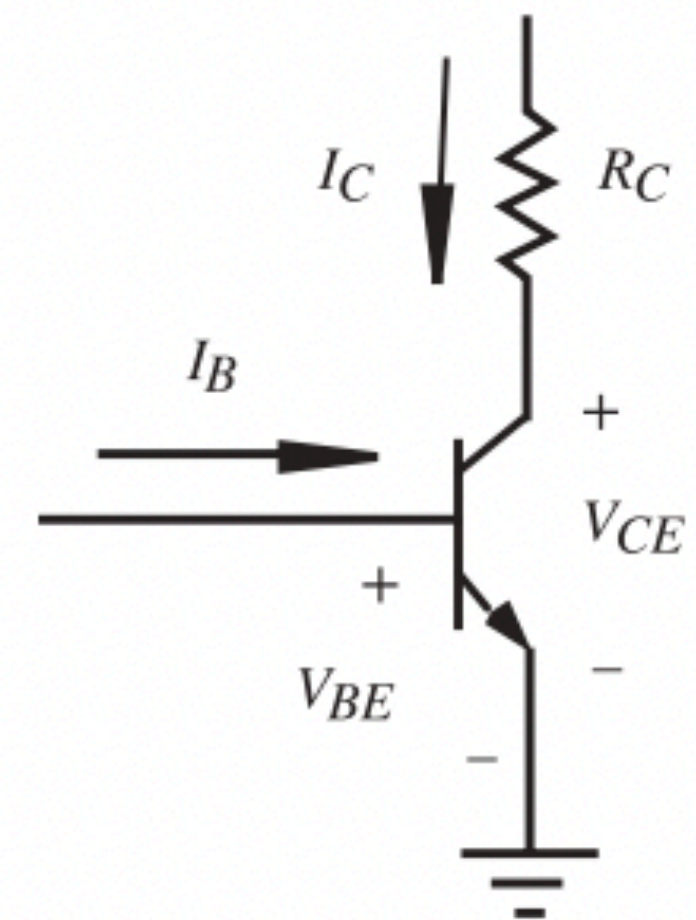


Cutoff:


- $V_{BE} \ll 0.7$

no current flow

open circuit

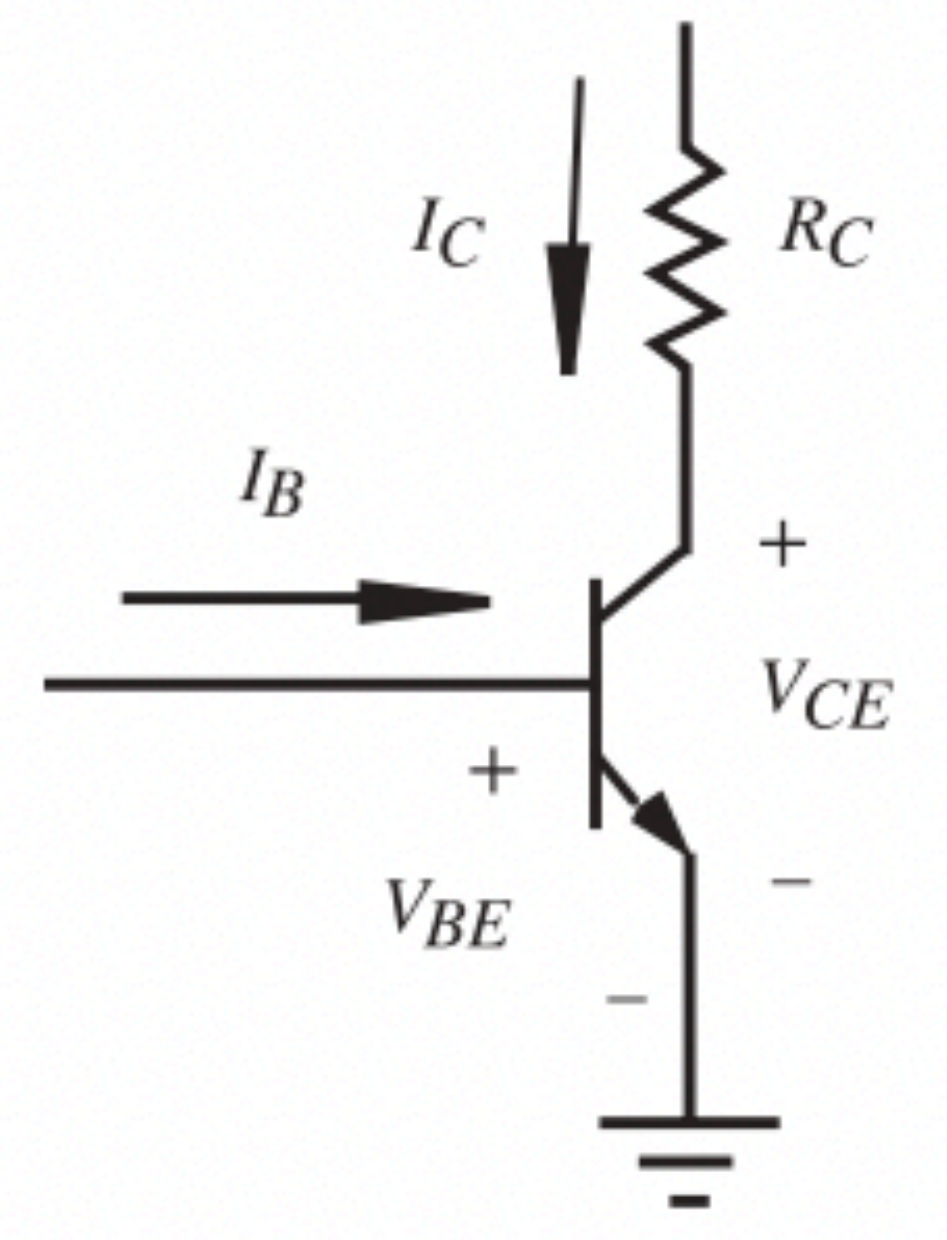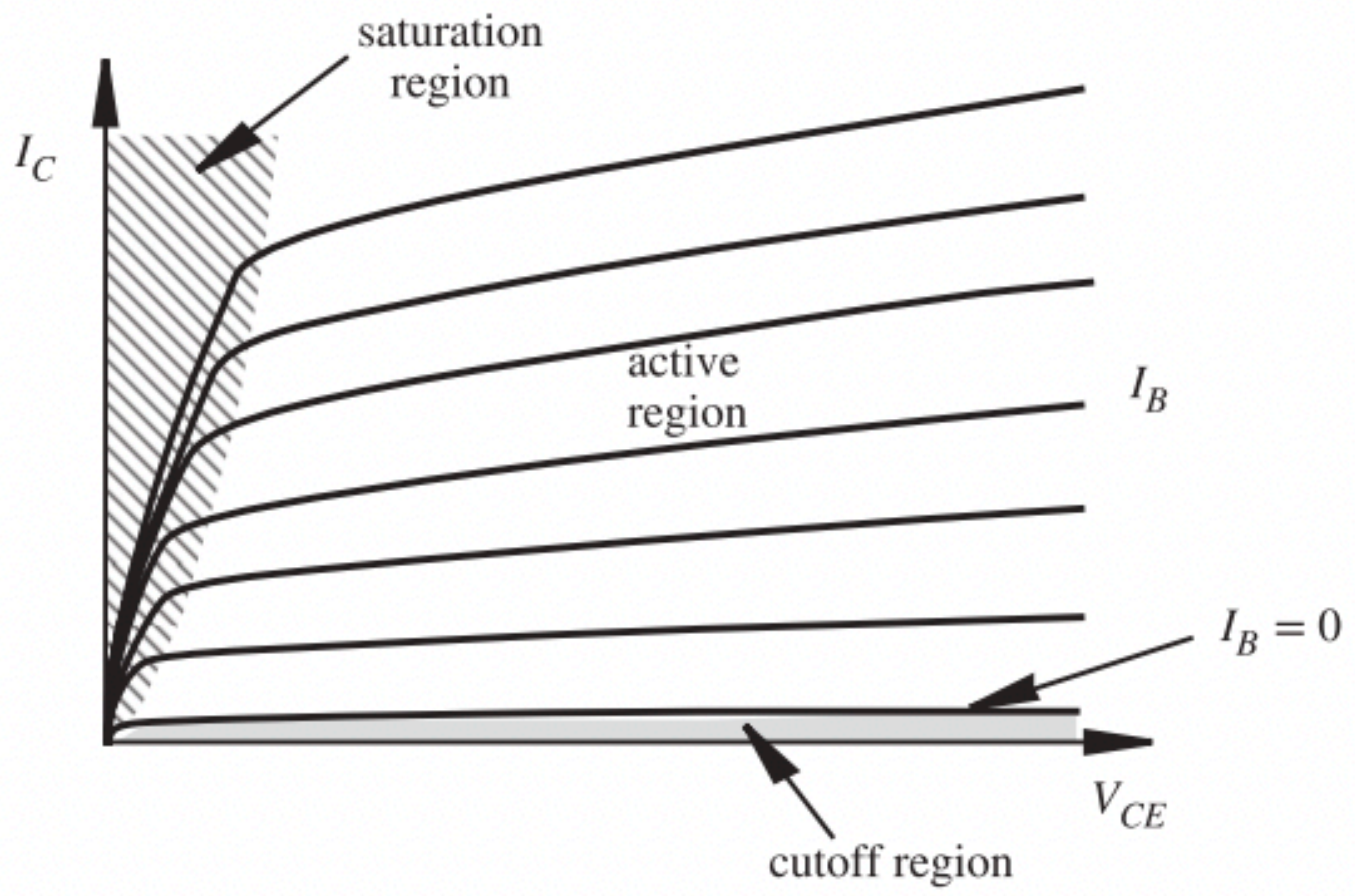

How to ensure saturation? (Example 3.4)

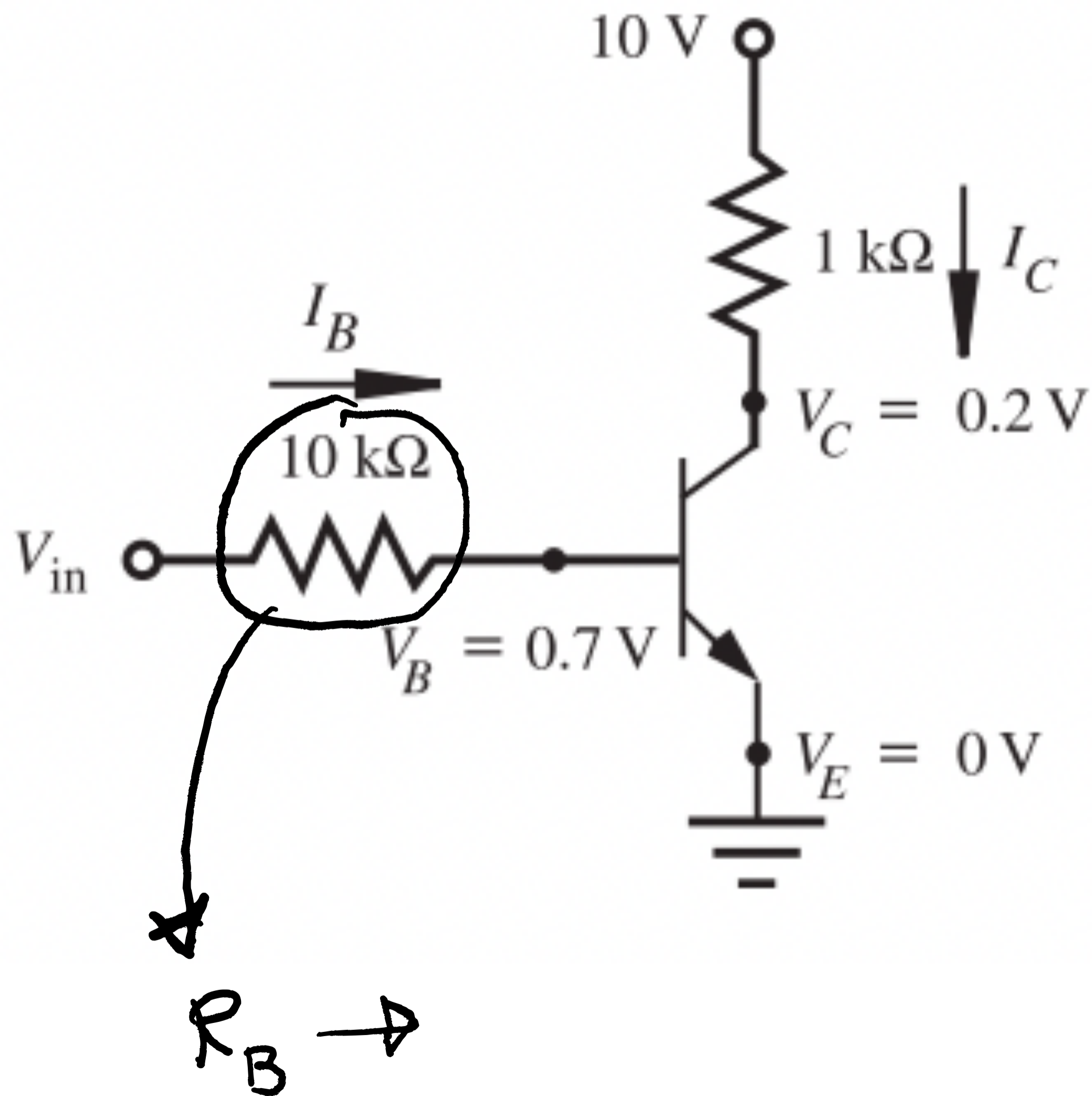

$$I_{C, \max} = 200\text{ mA}$$

$$V_{CE, \max} = 0.2\text{ V}$$

$$h_{FE} = \beta = 100$$

$$I_C = (10 - 0.2) / 1\text{ k}\Omega = 9.8\text{ mA}$$


$$I_C = \beta I_B \rightarrow I_B = 0.098\text{ mA}$$

$$V_{BE} = 0.7\text{ V}, \quad I_B = \frac{(V_{in} - V_{BE})}{10\text{ k}\Omega}$$


$$V_{in} = 0.78\text{ V} + 0.7\text{ V}$$

$$\boxed{V_{in} = 1.68\text{ V}} \times 2-5 \text{ times}$$


How to ensure saturation? (Example 3.4)

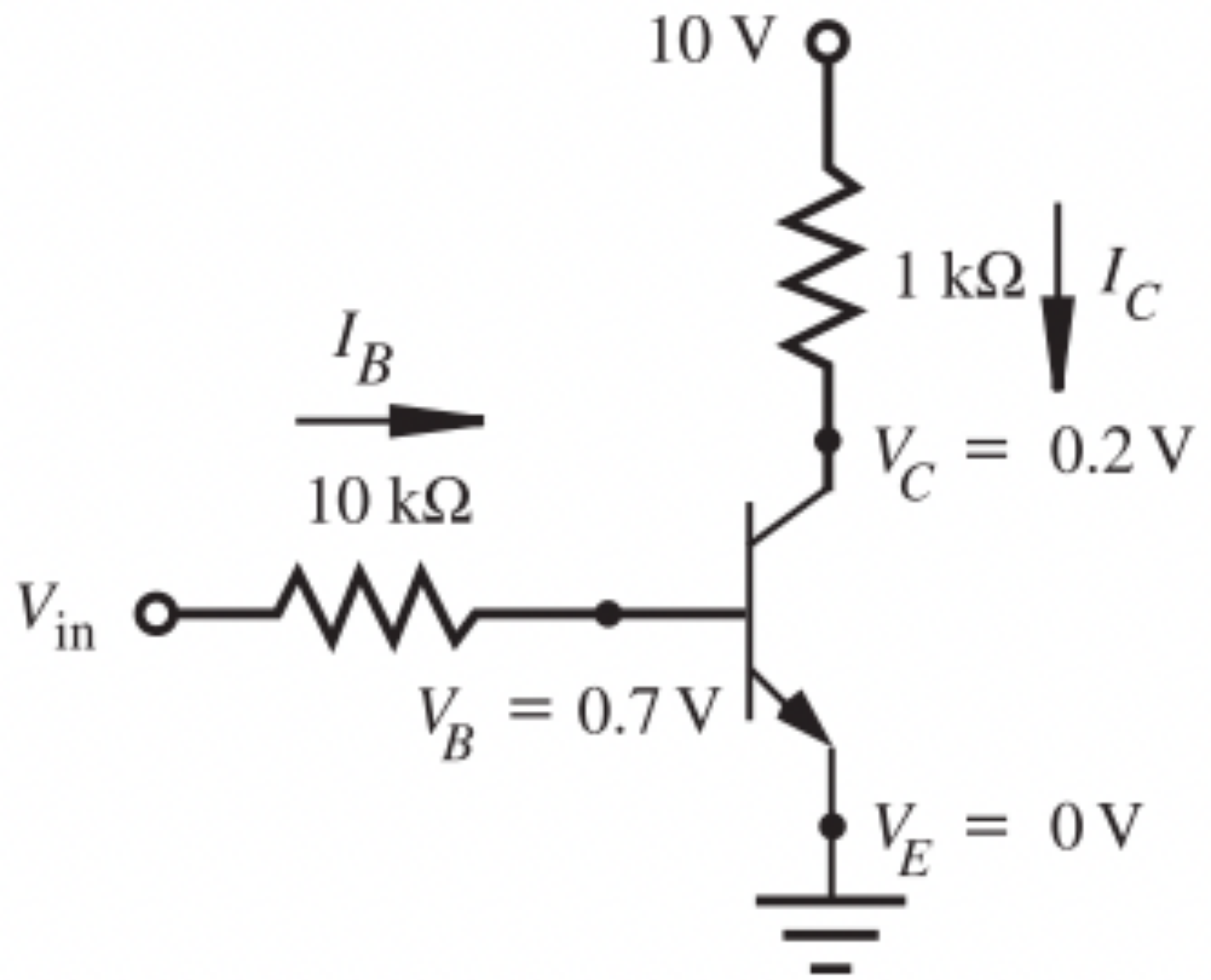


Real Data

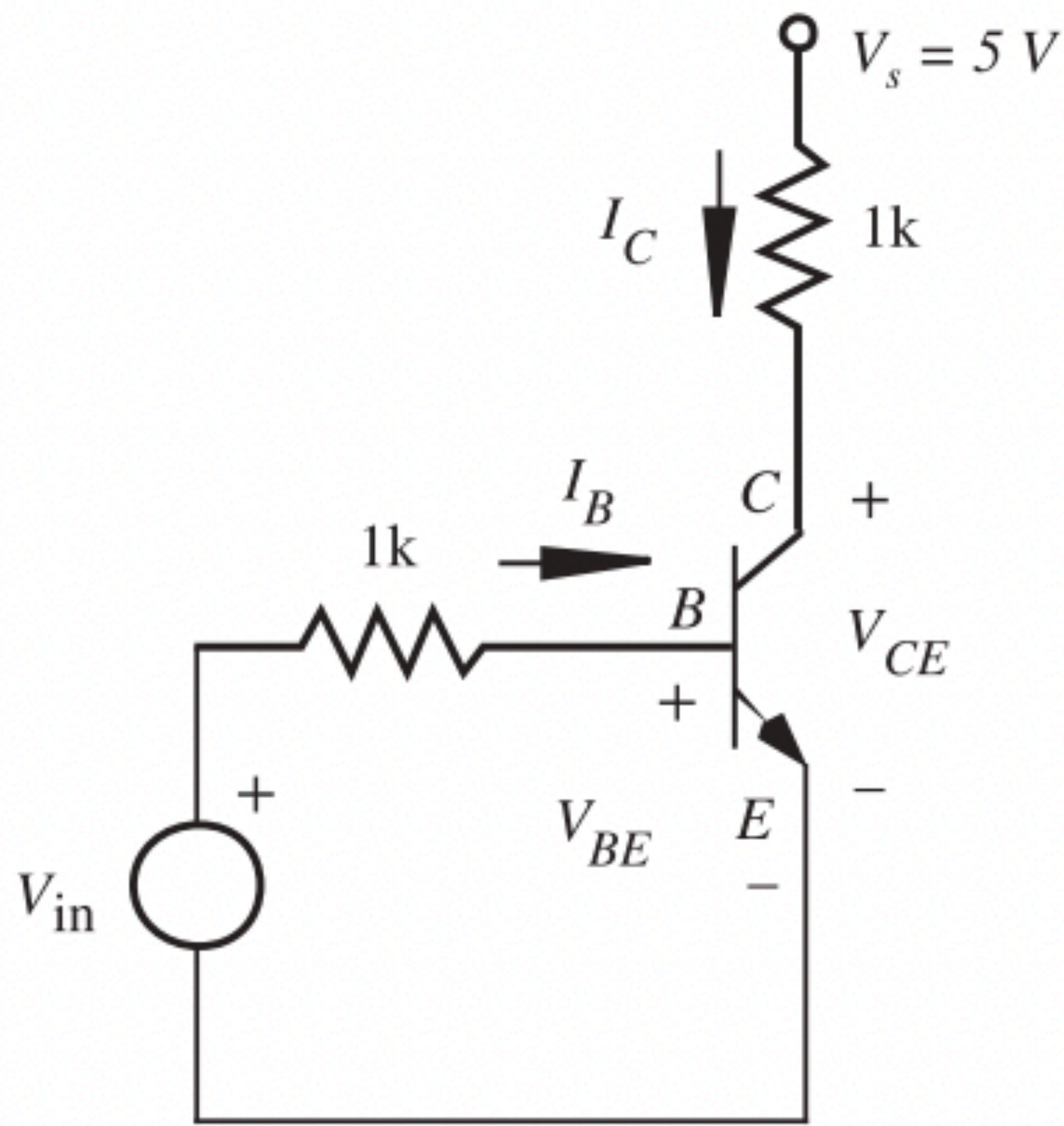

(a) common emitter



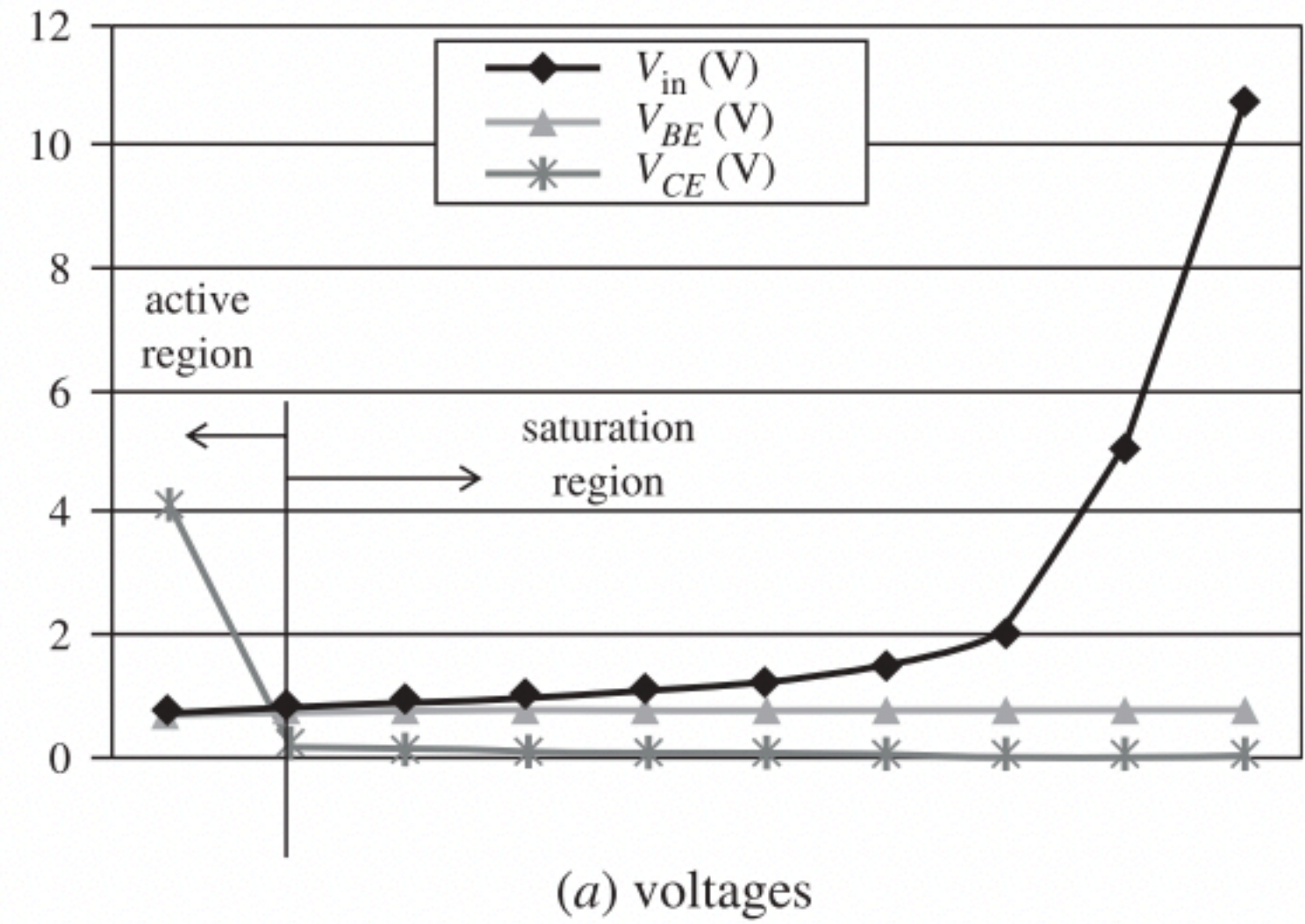


(a) voltages



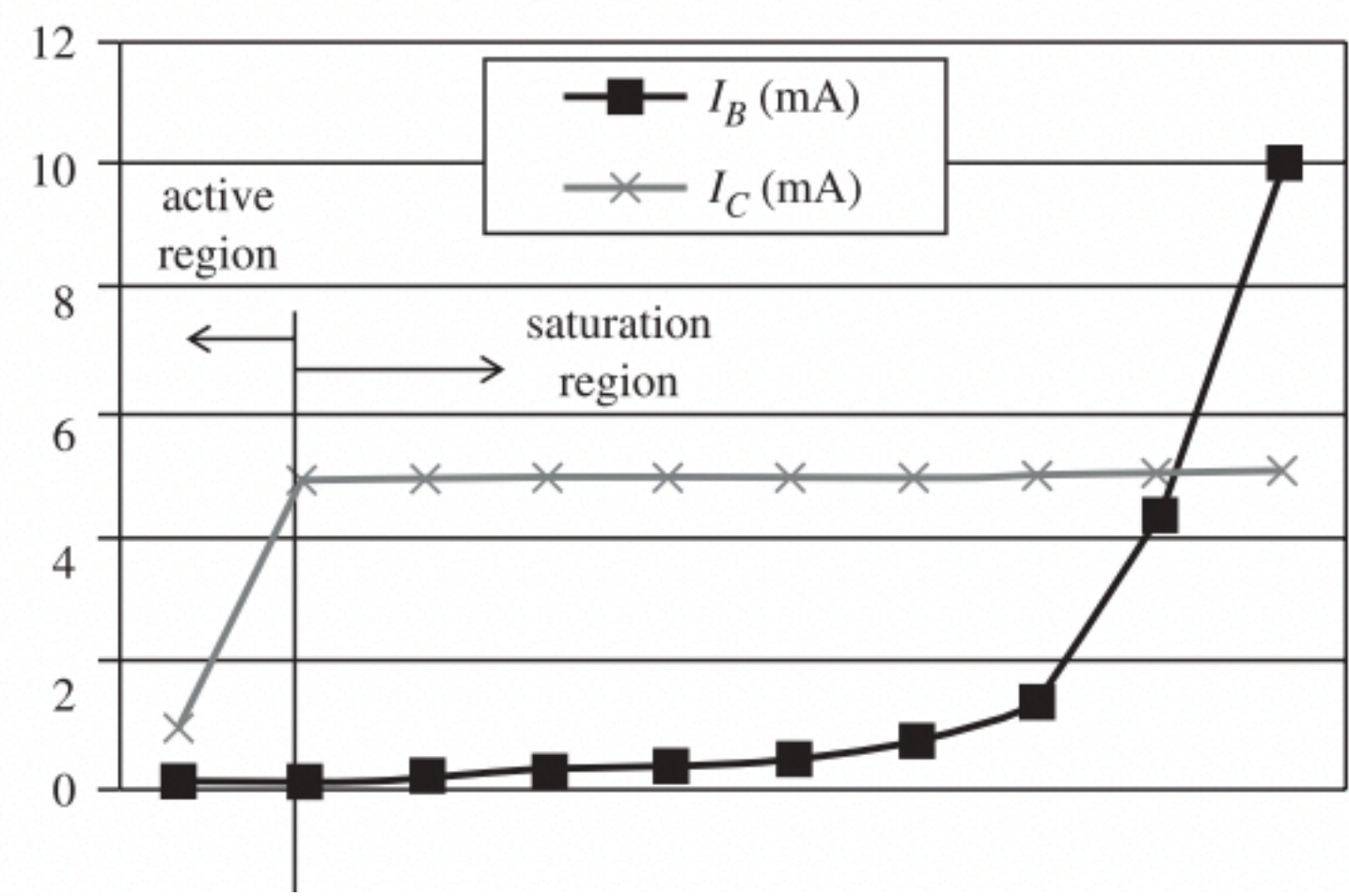


(b) currents

Real Data

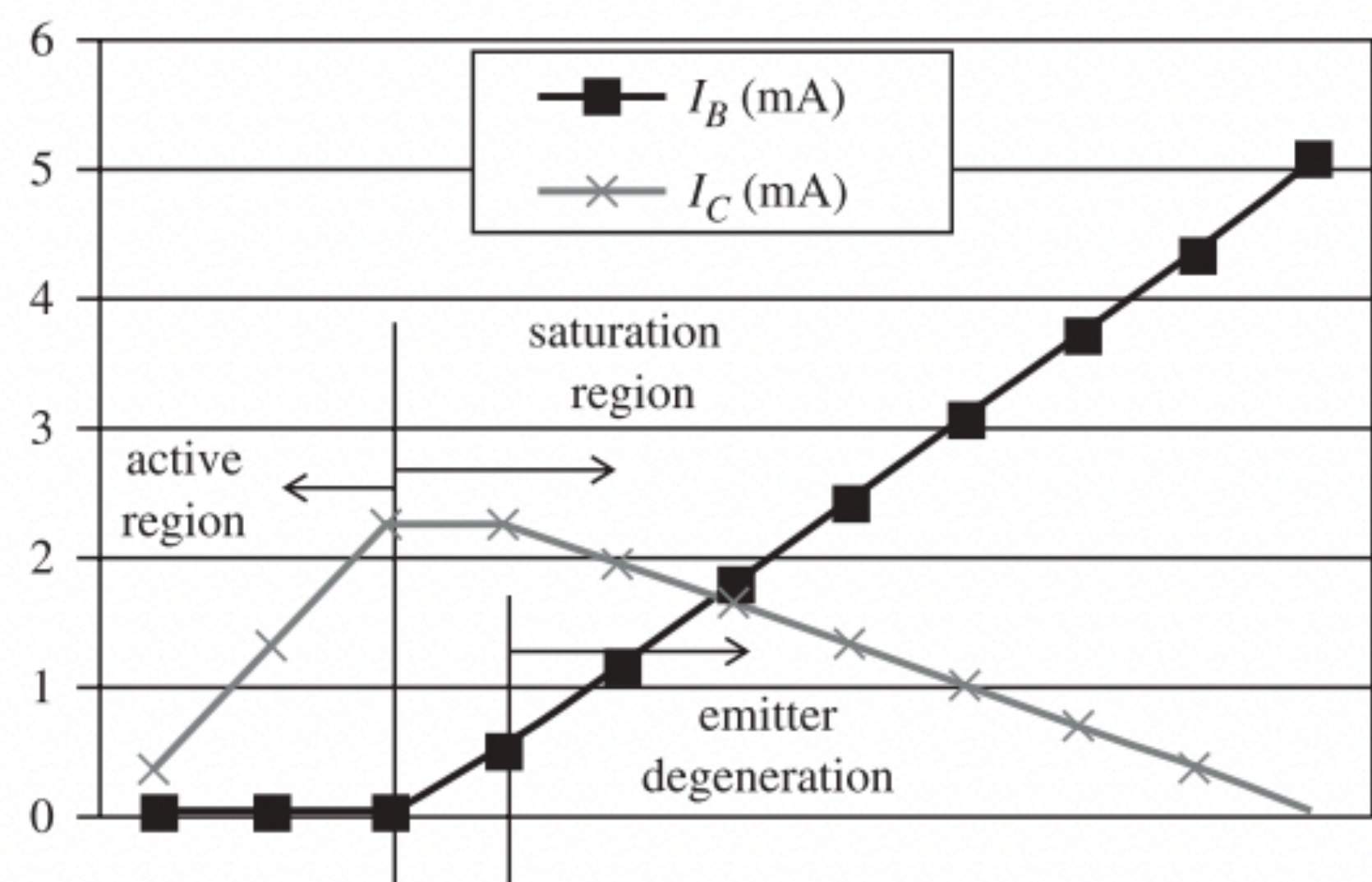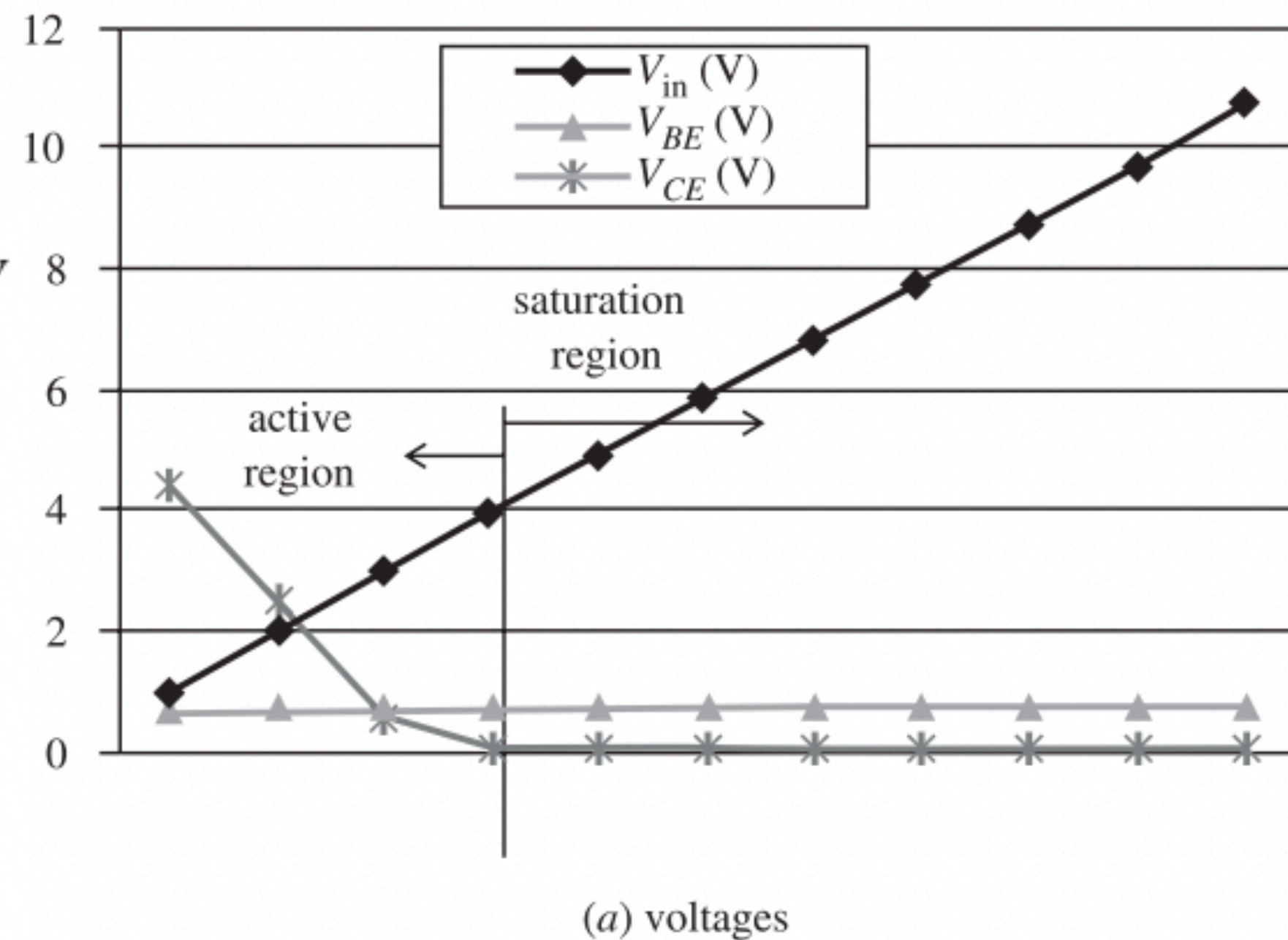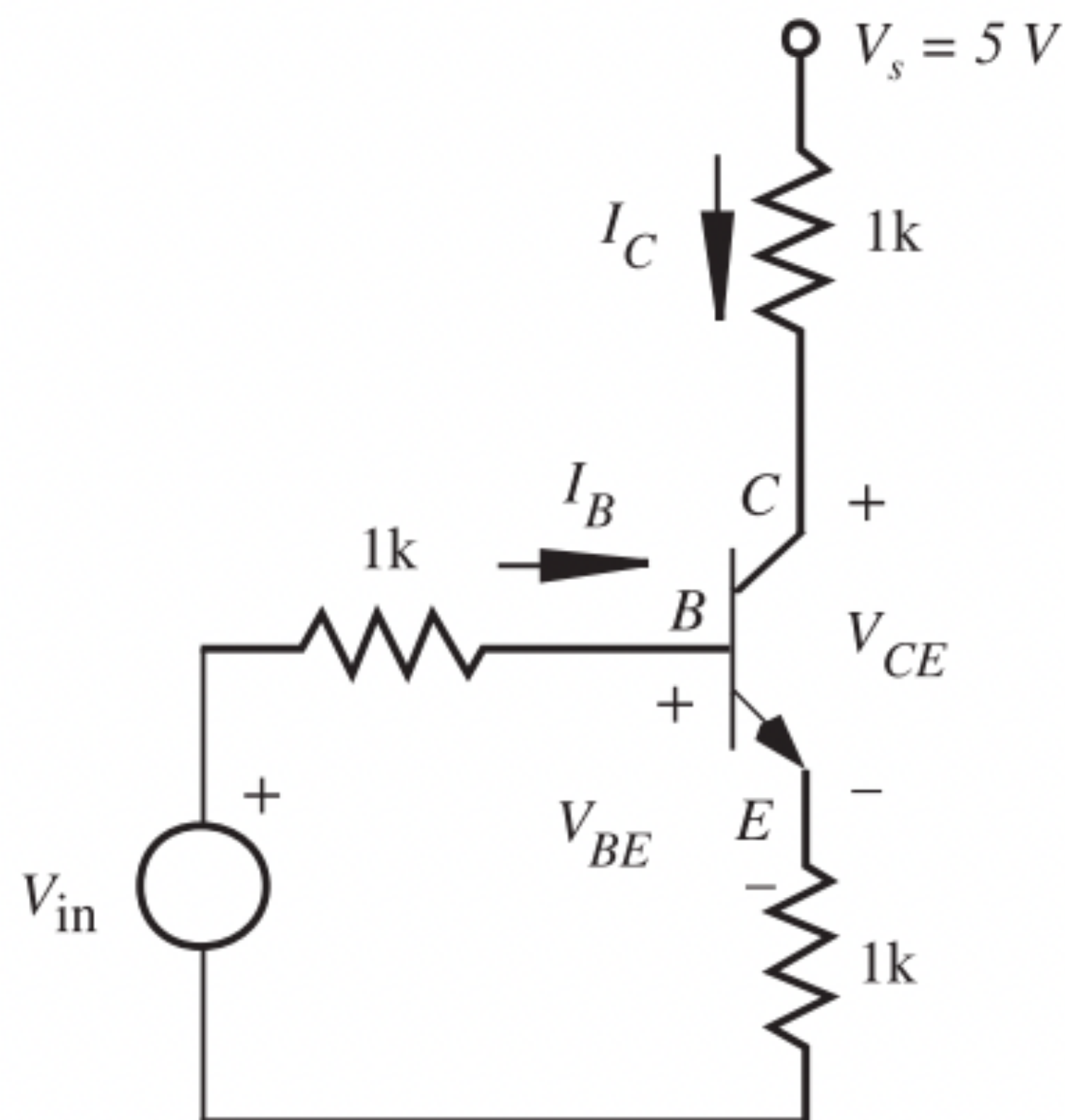

Summary of BJT Switch

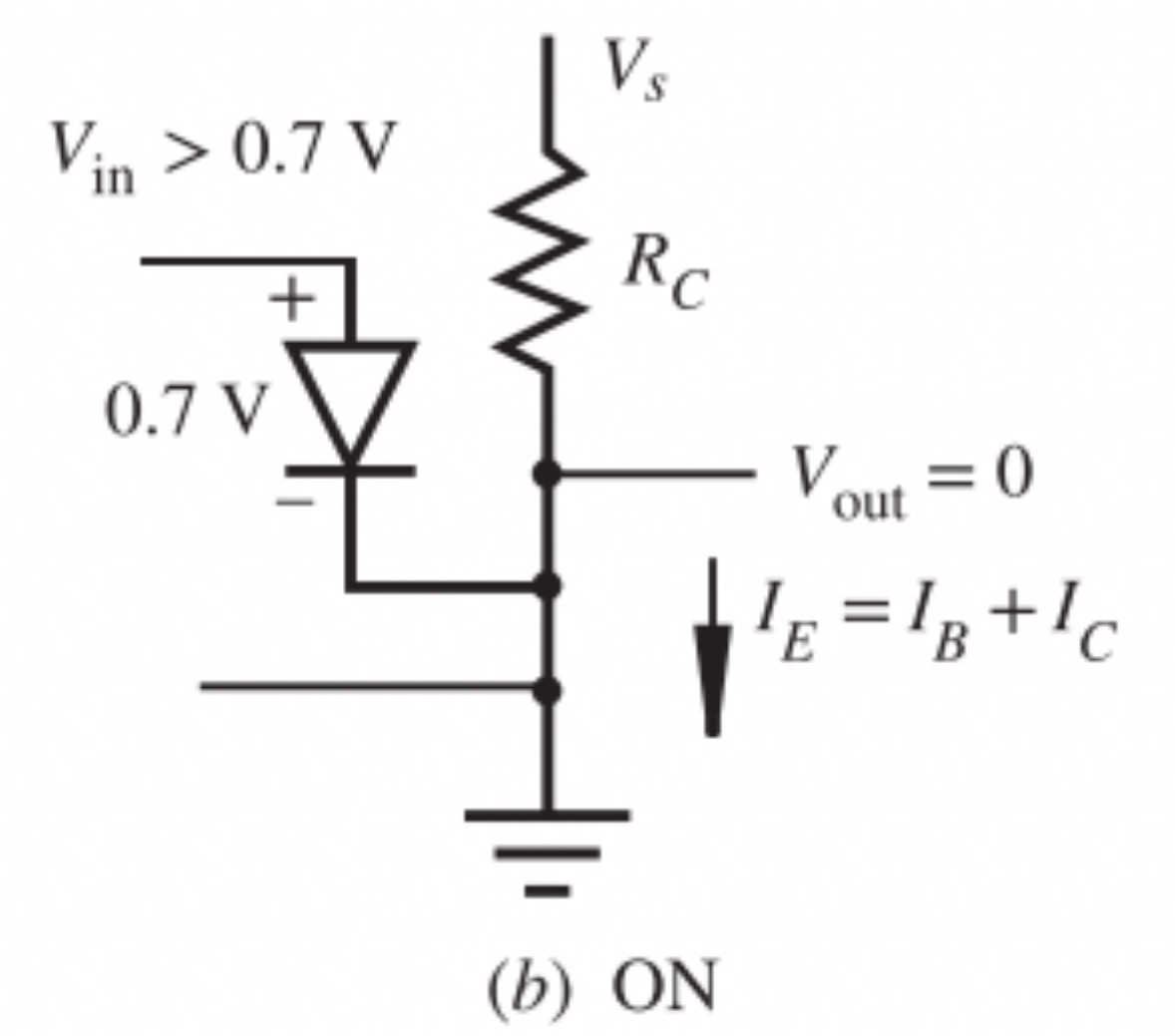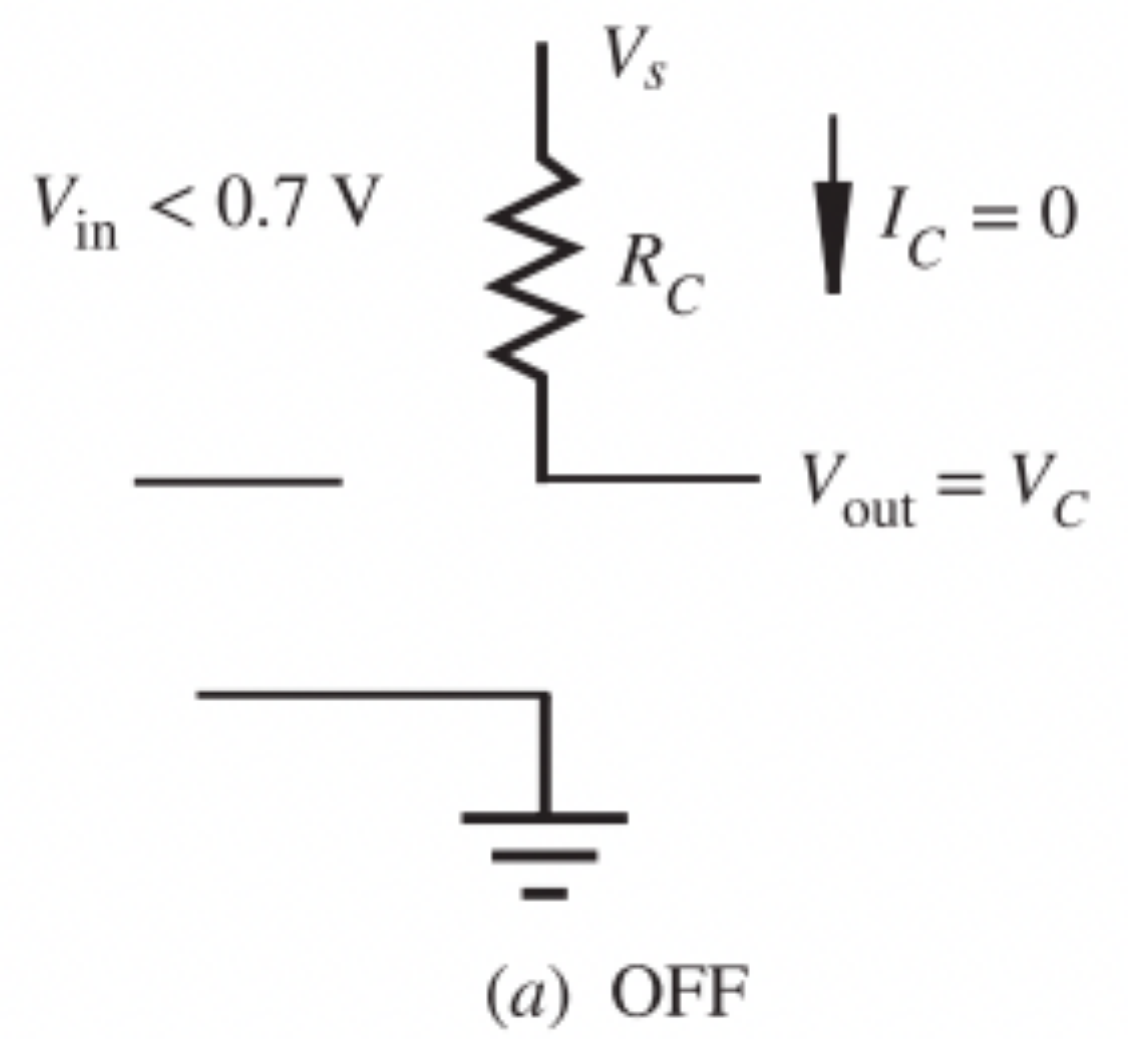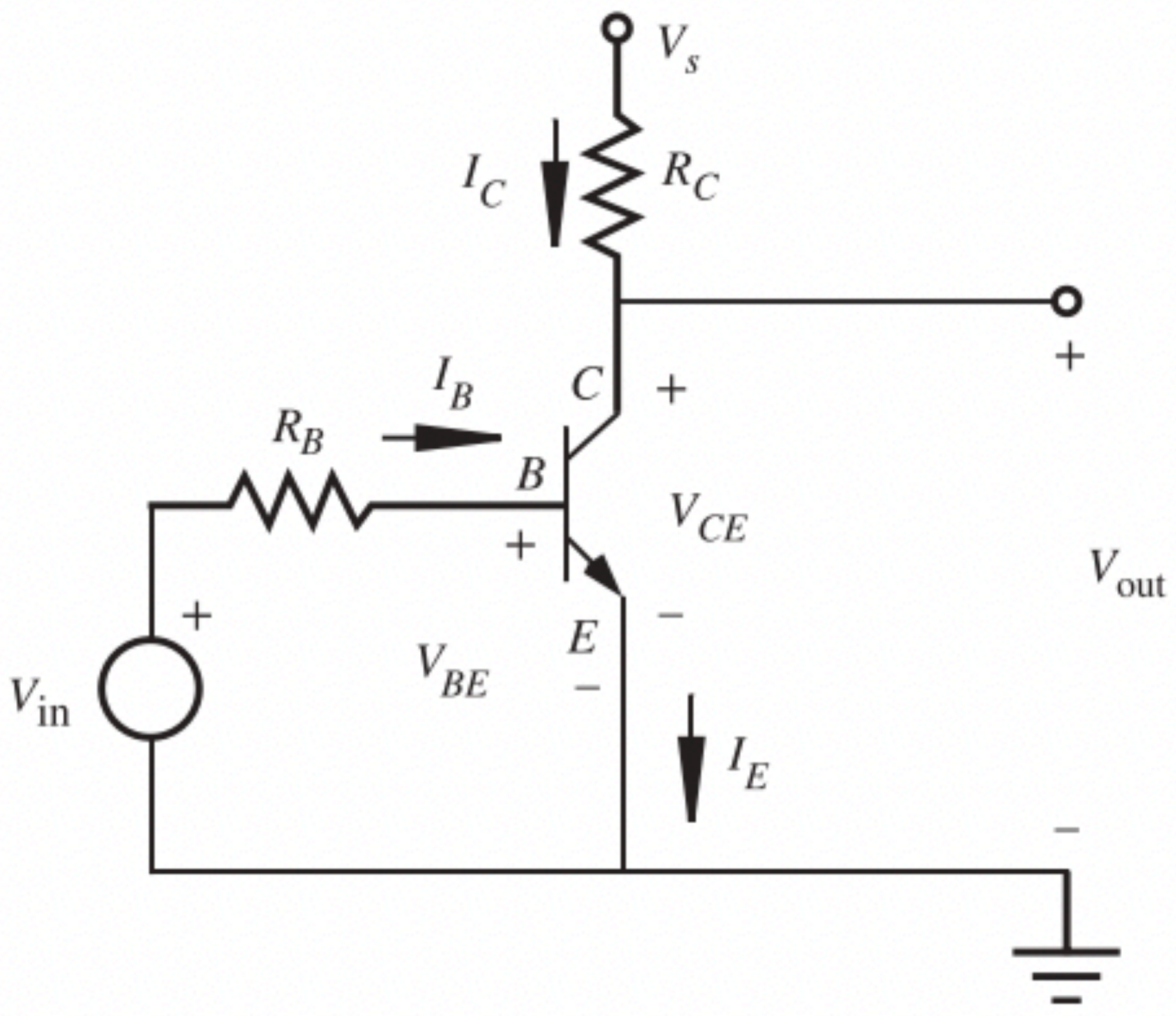

R_b is required

$$I_B = (V_{in} - V_B) / R_B$$

$$I_C = (V_s - V_C) / R_C$$

$$V_B = V_{BE} = 0.7 \text{ V}$$

$$V_C = V_{out} = 0.2 \text{ V}$$

Summary of BJT Switch

BJT Switch Applications

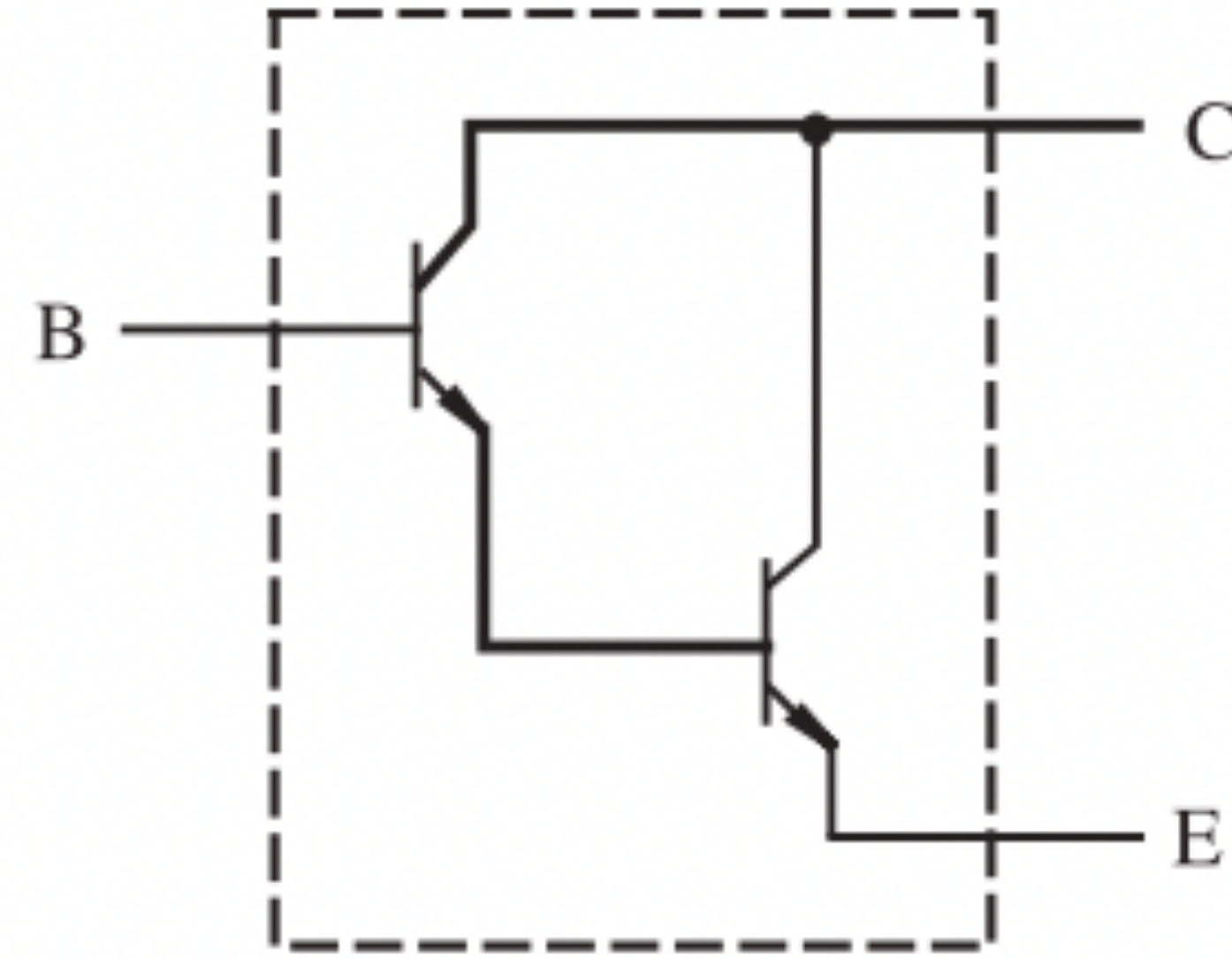
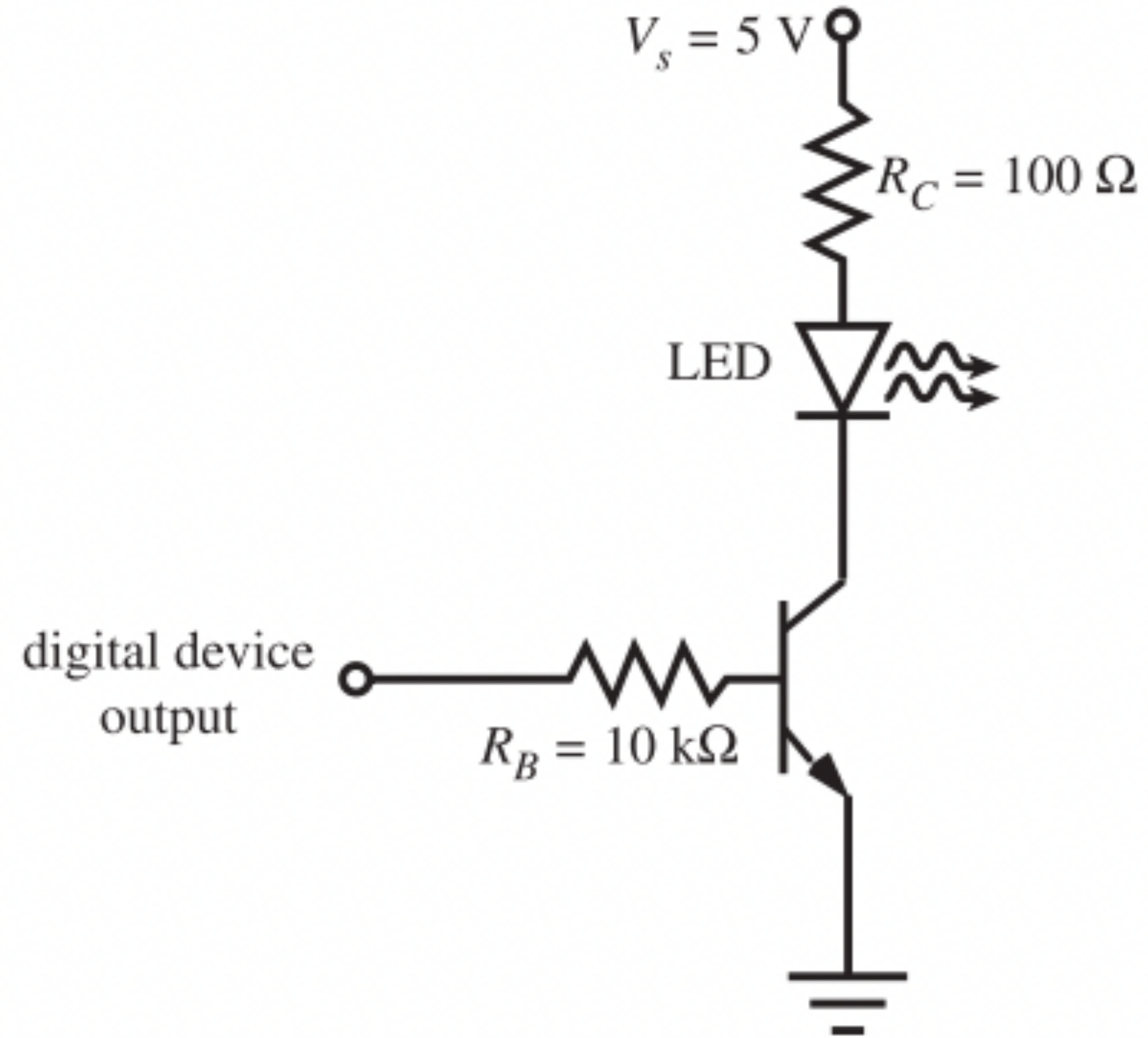


Figure 3.30 Darlington pair.

BJT Switch Applications

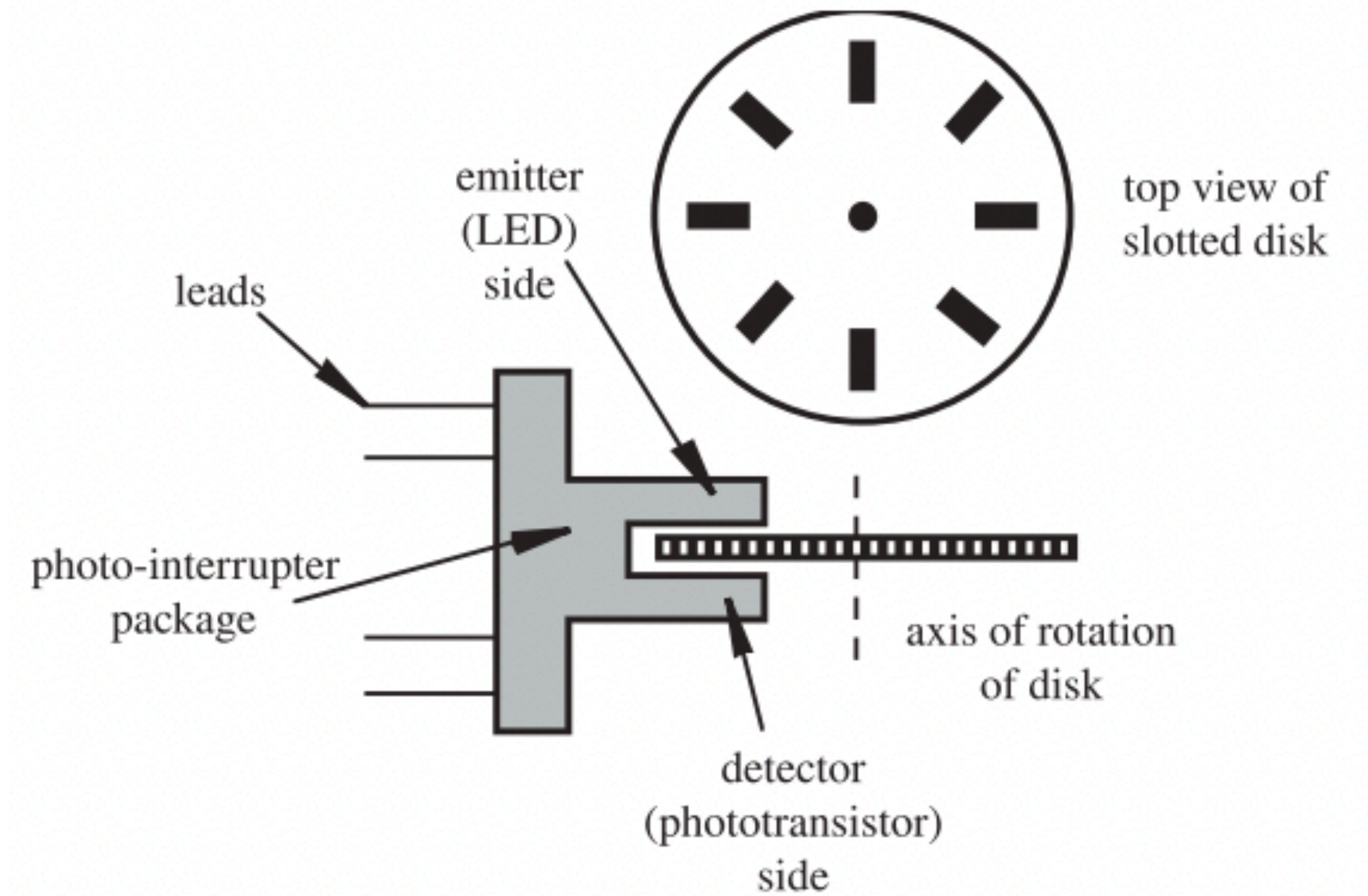
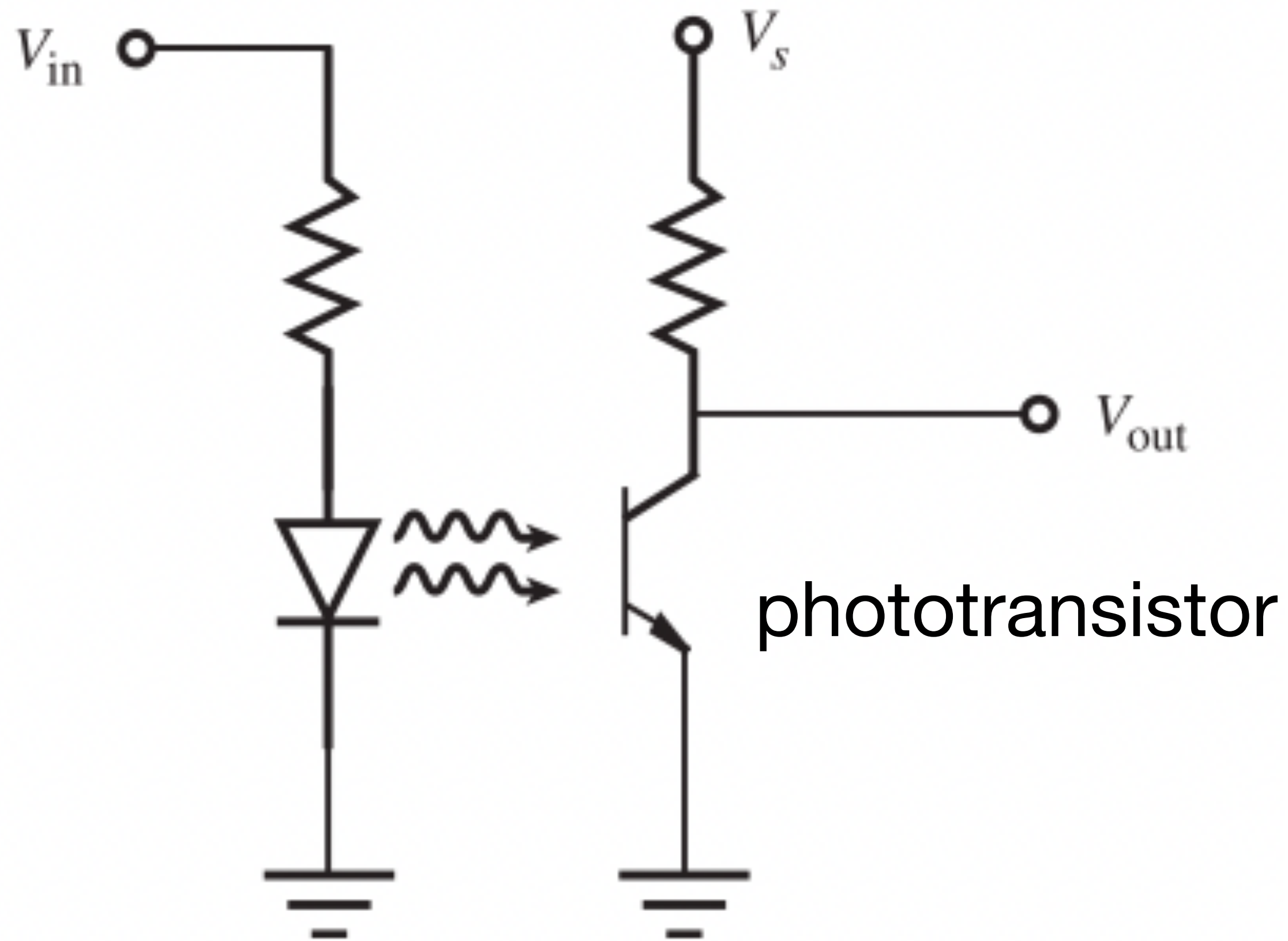



Figure 3.31 Optoisolator.

Types of optoisolators

Device type ^[note 5]	Source of light ^[7]	Sensor type ^[7]	Speed	Current transfer ratio
Resistive opto-isolator (Vactrol)	Incandescent light bulb	CdS or CdSe photoresistor (LDR)	Very low	<100% ^[note 6]
	Neon lamp		Low	
	GaAs infrared LED		Low	
Diode opto-isolator	GaAs infrared LED	Silicon photodiode	Highest	0.1–0.2% ^[22]
Transistor opto-isolator	GaAs infrared LED	Bipolar silicon phototransistor	Medium	2–120% ^[22]
		Darlington phototransistor	Medium	100–600% ^[22]
Opto-isolated SCR	GaAs infrared LED	Silicon-controlled rectifier	Low to medium	>100% ^[23]
Opto-isolated triac	GaAs infrared LED	TRIAC	Low to medium	Very high
Solid-state relay	Stack of GaAs infrared LEDs	Stack of photodiodes driving a pair of MOSFETs or an IGBT	Low to high ^[note 7]	Practically unlimited

BJT Packages

BJTs

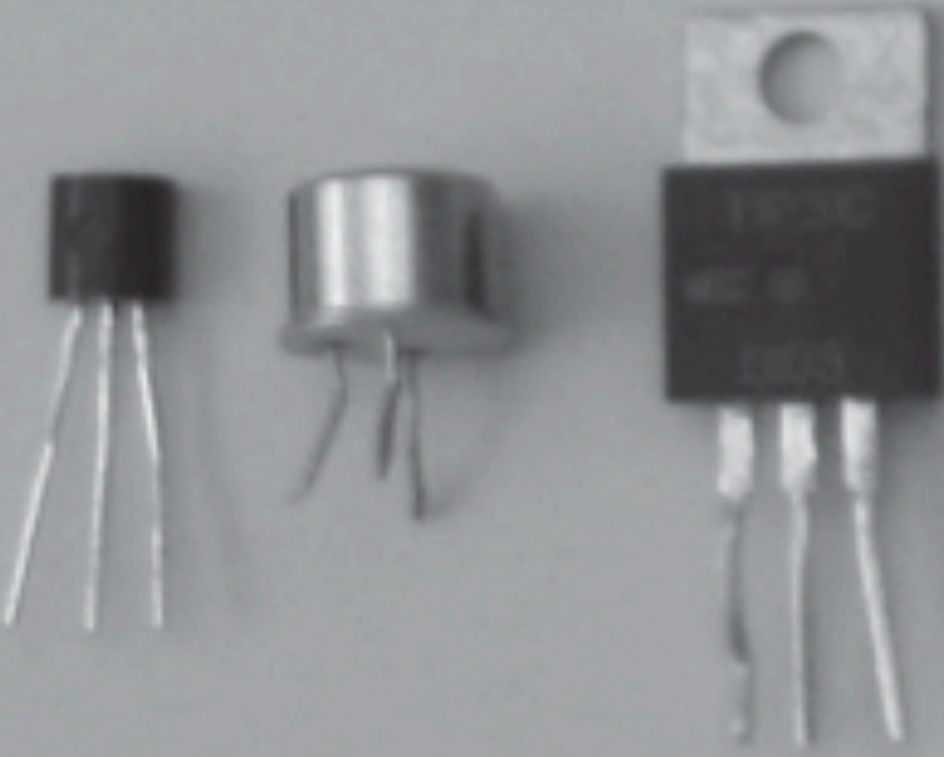

MOSFETs

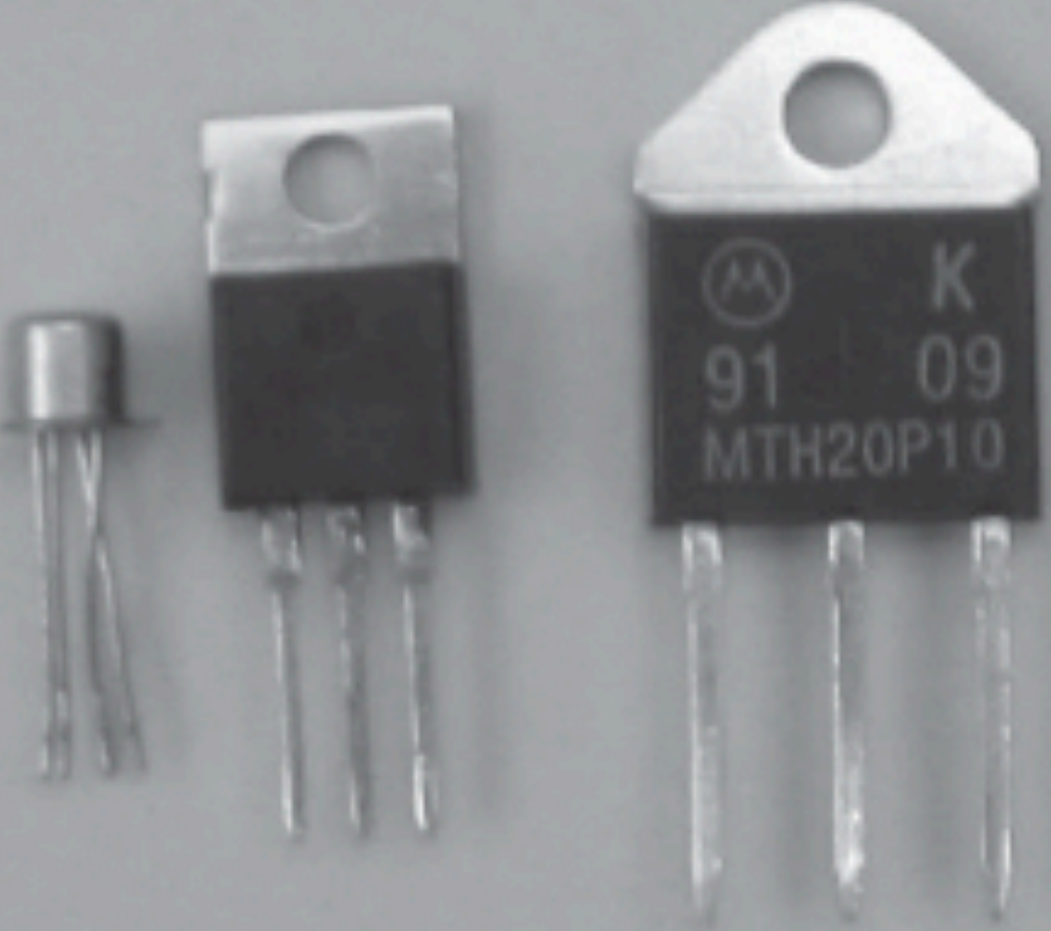


photo-interrupter

