

Last time:

- BJT - overview
- BJT as a switch


Polling:

```
while (1) {  
    digitalRead (pin)  
    if pin == High  
        break;  
}
```

Today:

- > Emitter Degeneration
- > FET , Field effect transistors

Recall npn BJT fundamentals

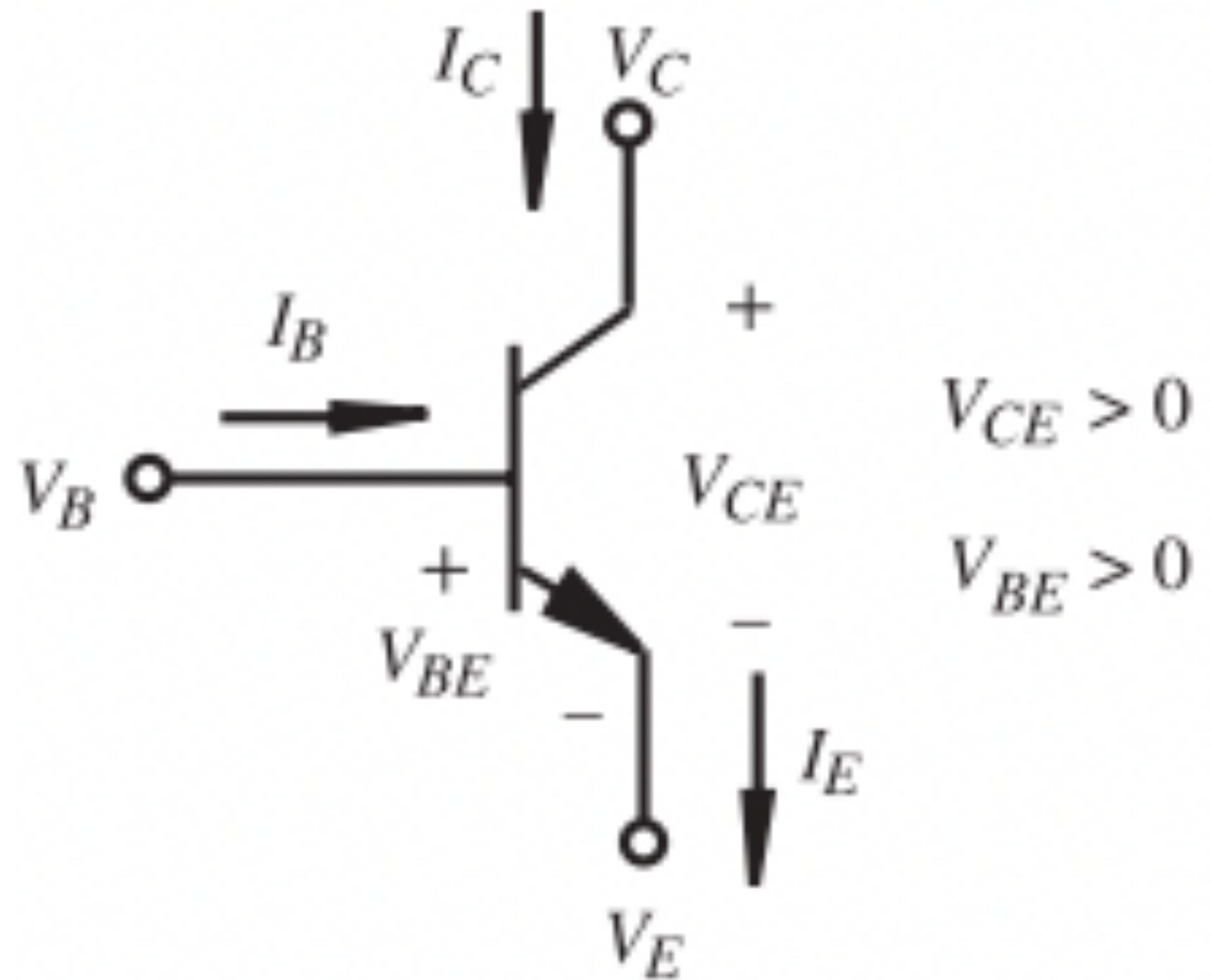


$$I_E = I_c + I_B$$

$$V_{BE} = V_B - V_E$$

$$V_{CE} = V_C - V_E$$

Recall npn BJT fundamentals

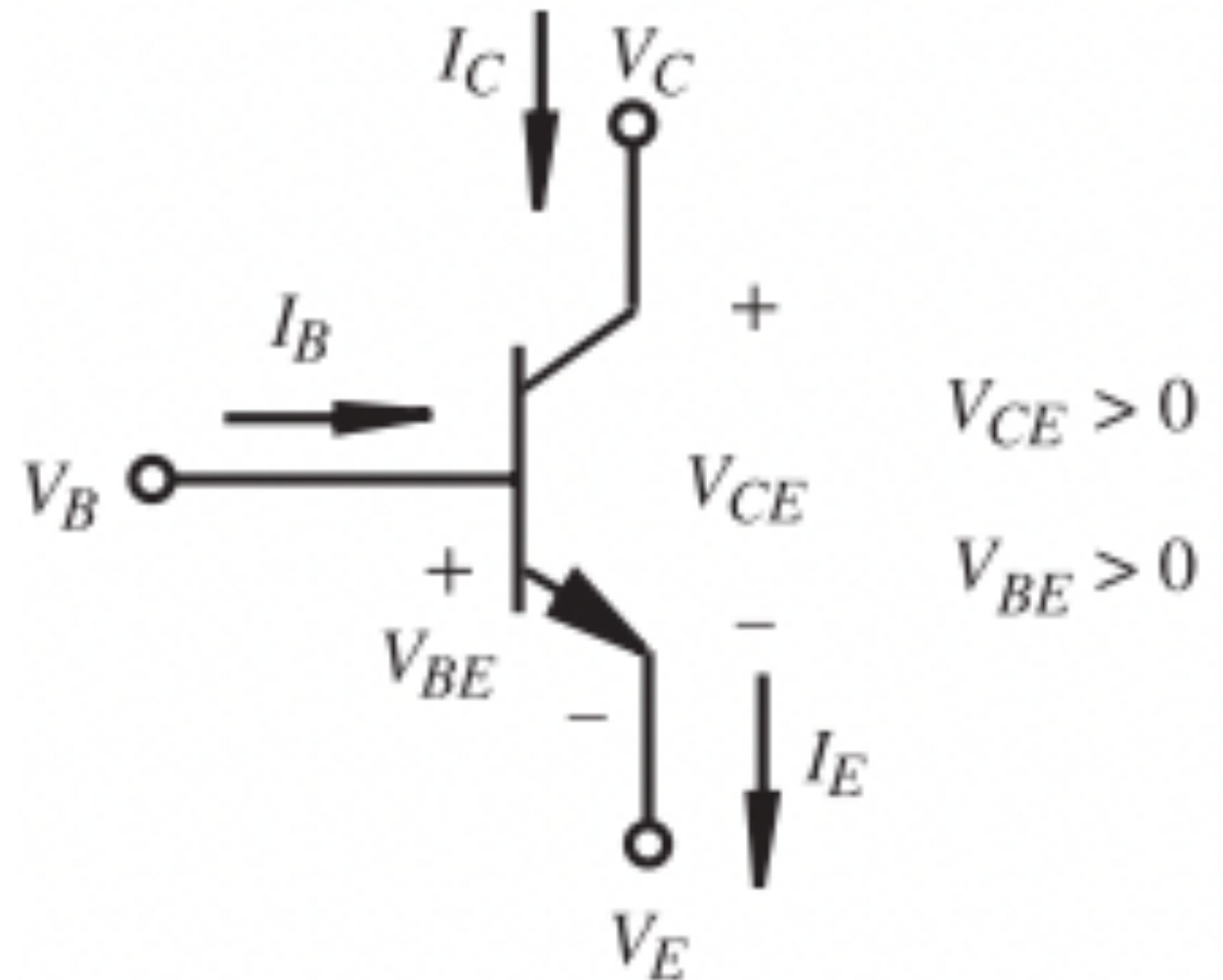


$$I_E = I_C + I_B$$


$$V_{BE} = V_B - V_E$$

$$V_{CE} = V_C - V_E$$


Real Data

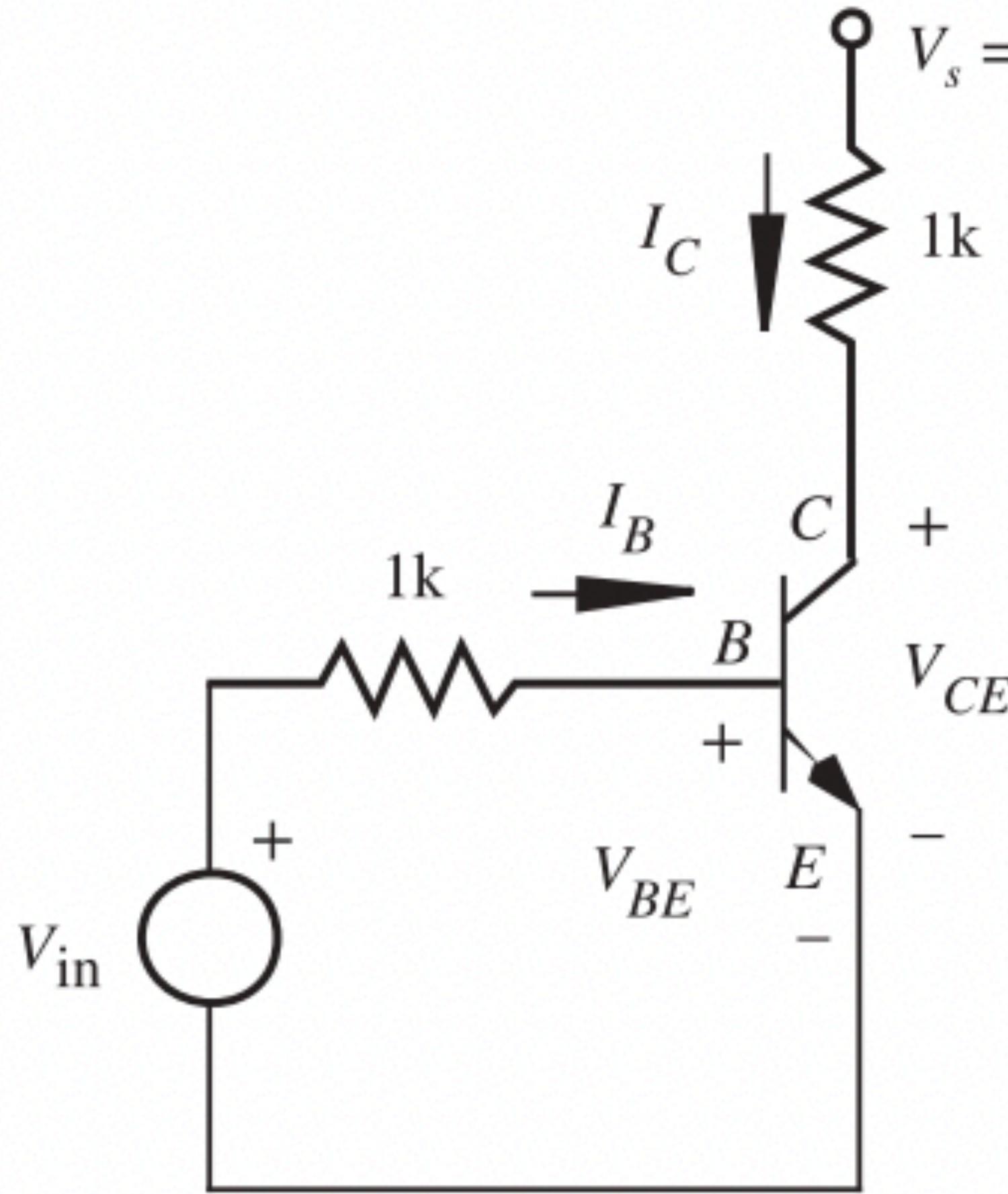


(a) common emitter

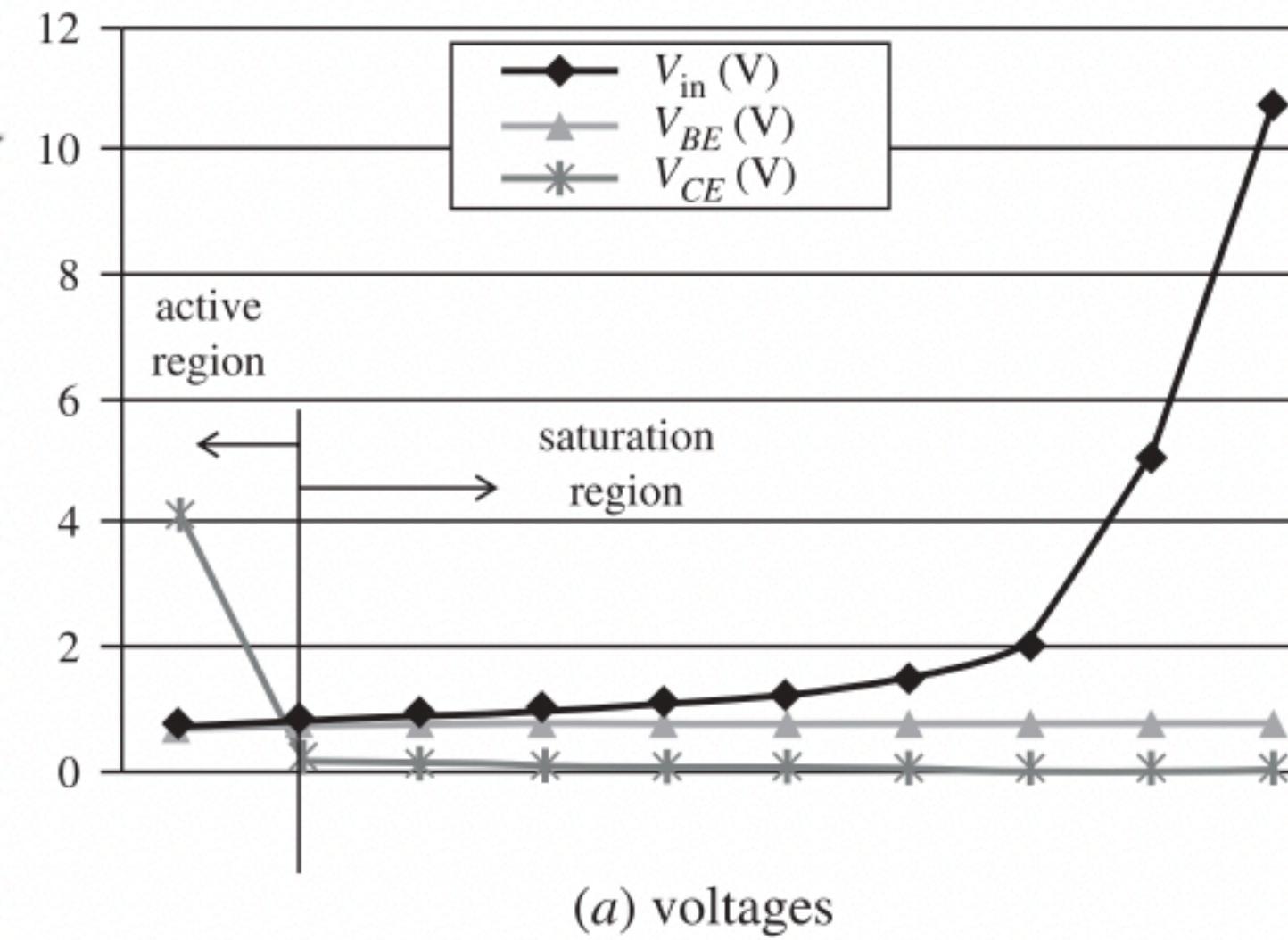

(a) voltages

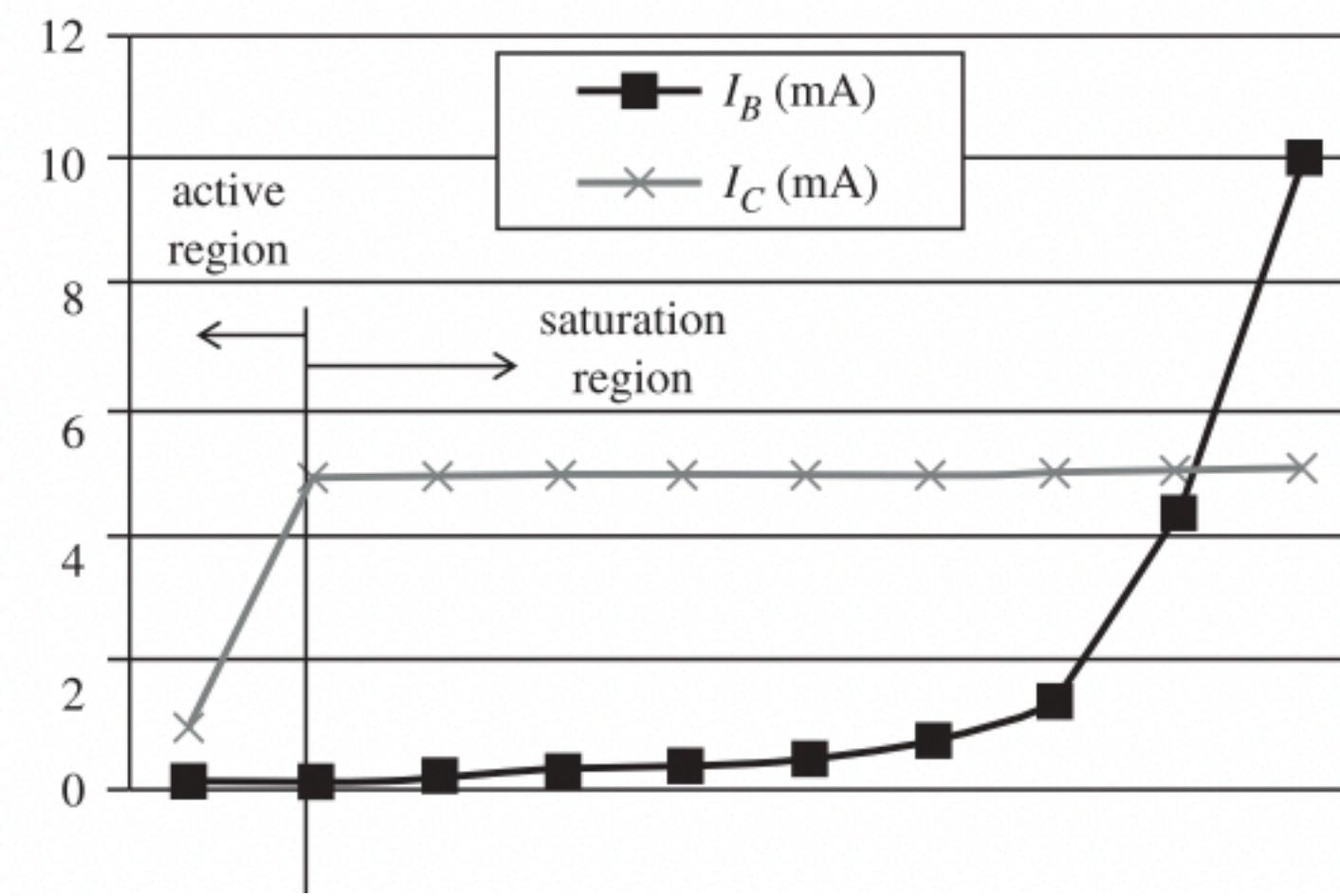

common emitter characteristics

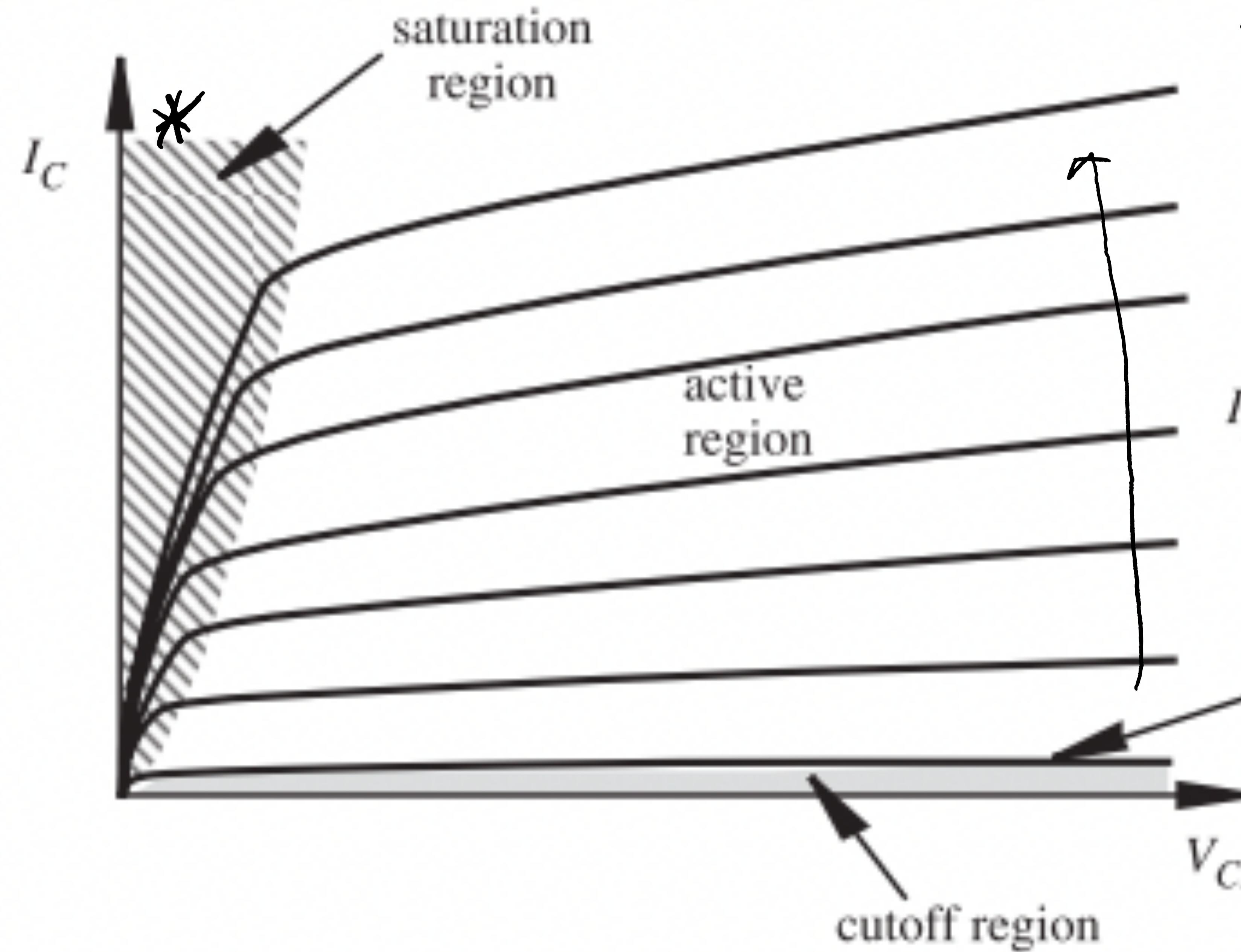

* Saturation Region

collector current is
stably controlled by
the collector circuit +
(load)


Active Region

Collector current
is proportional to
base current

cutoff

no collector
current .

Emitter Degeneration

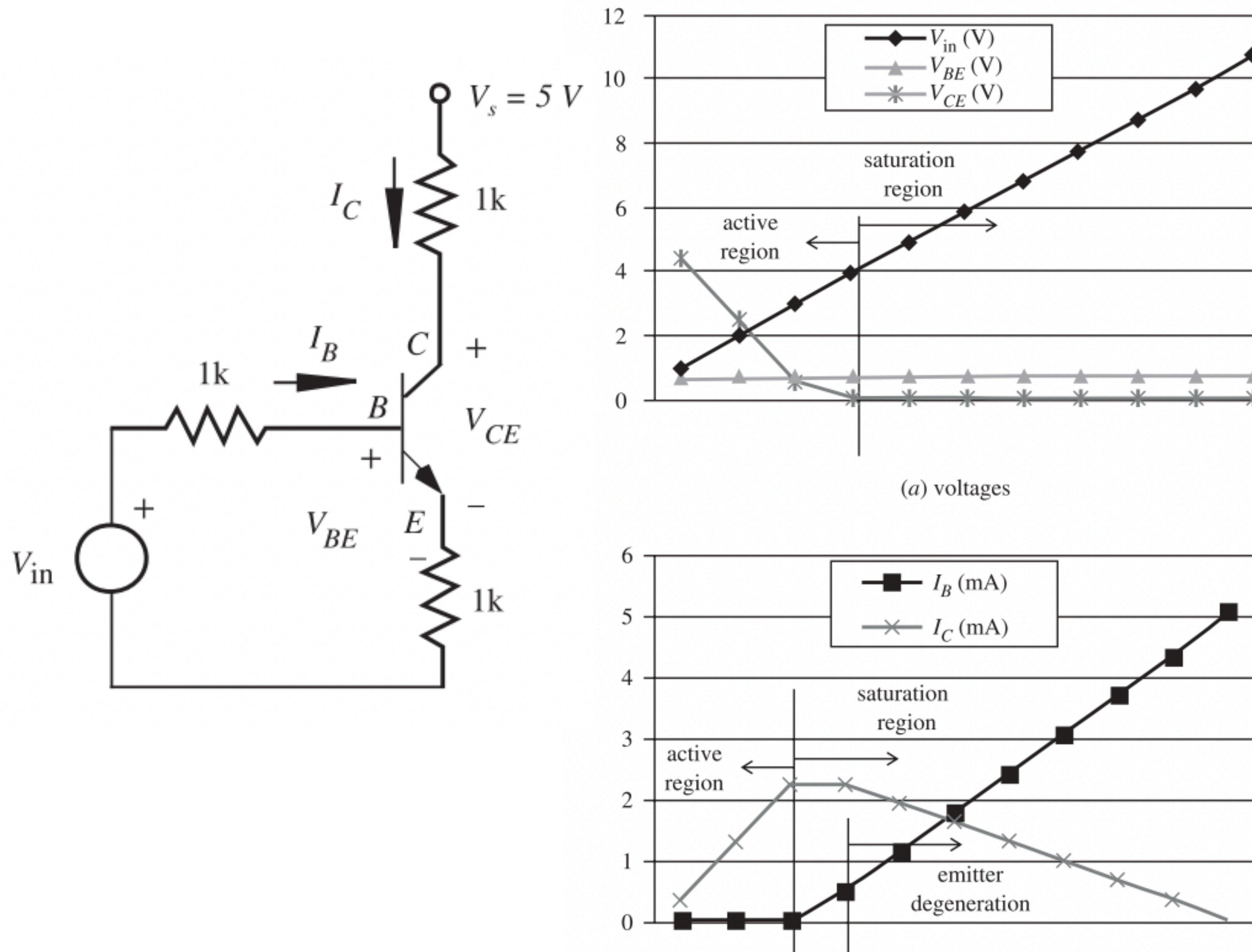

as base current is increased, the collector current drops, why?


$$I_E = I_C + I_B$$

creates a larger voltage across the emitter resistor

$$V_E = I_E R_E$$

this reduces the voltage across the collector resistor \rightarrow no voltage difference, \rightarrow no current flow

Summary of BJT Switch

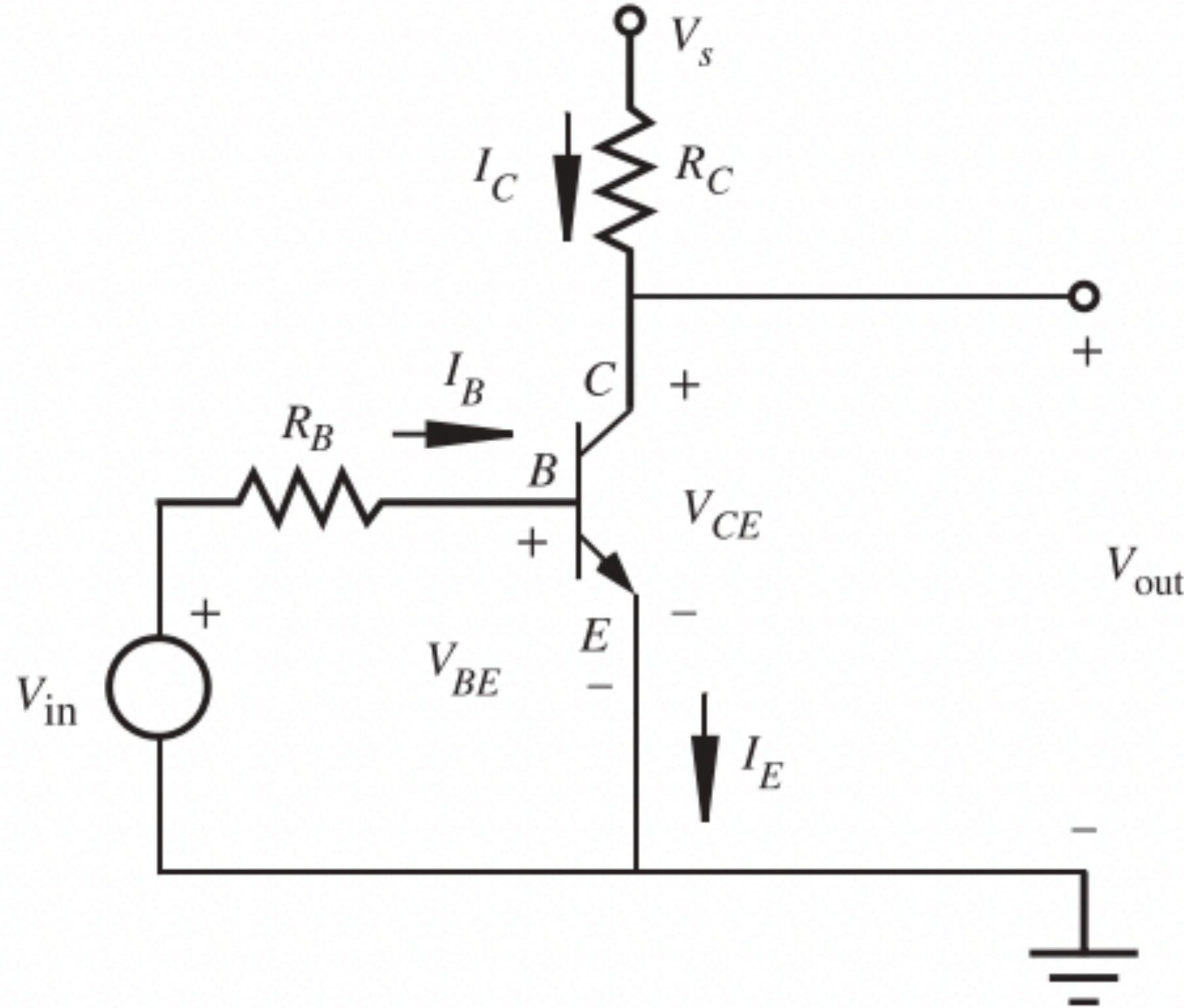


R_b is required

$$I_B = (V_{in} - V_B)/R_B$$


$$V_B = V_{BE} = 0.7 \text{ V}$$

$$I_C = (V_s - V_C)/R_C$$


$$V_C = V_{out} = 0.2 \text{ V}$$

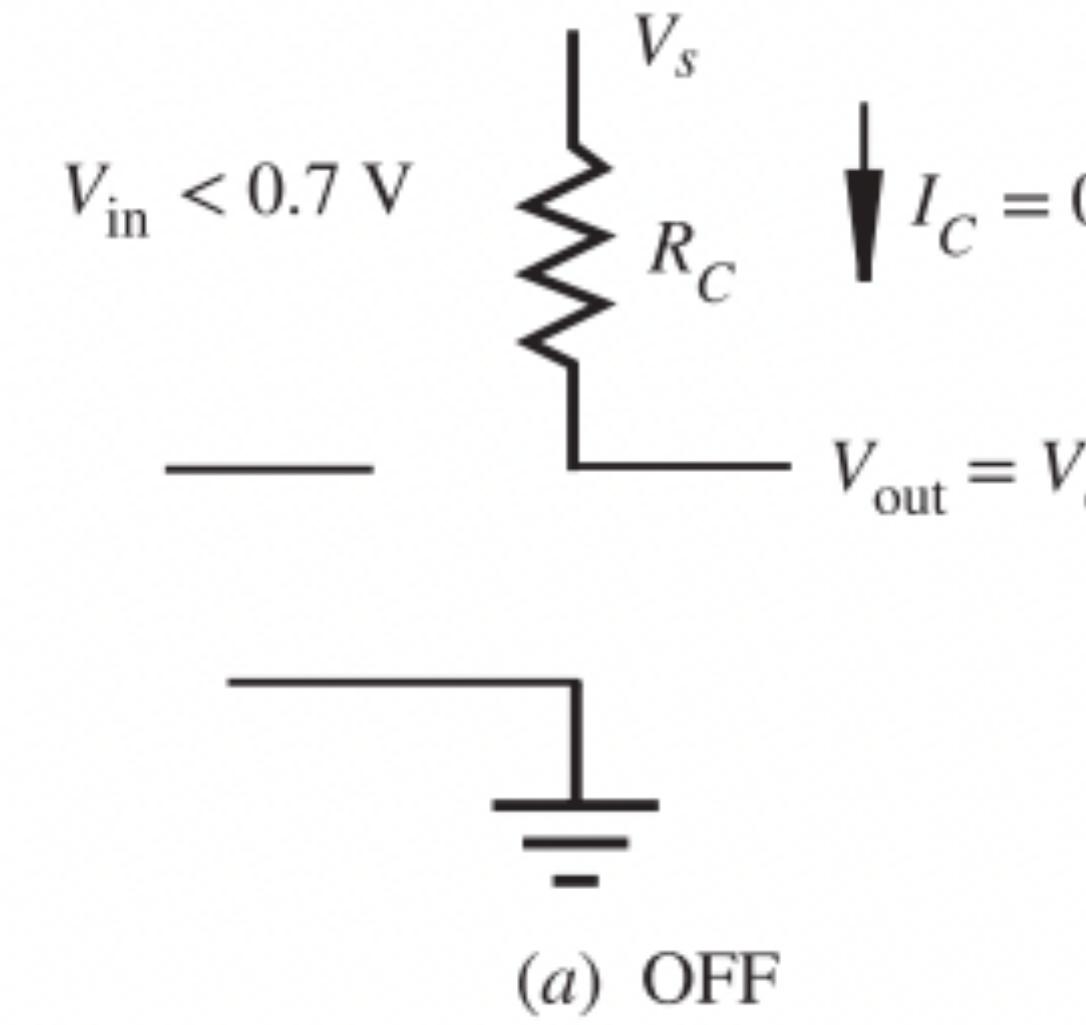

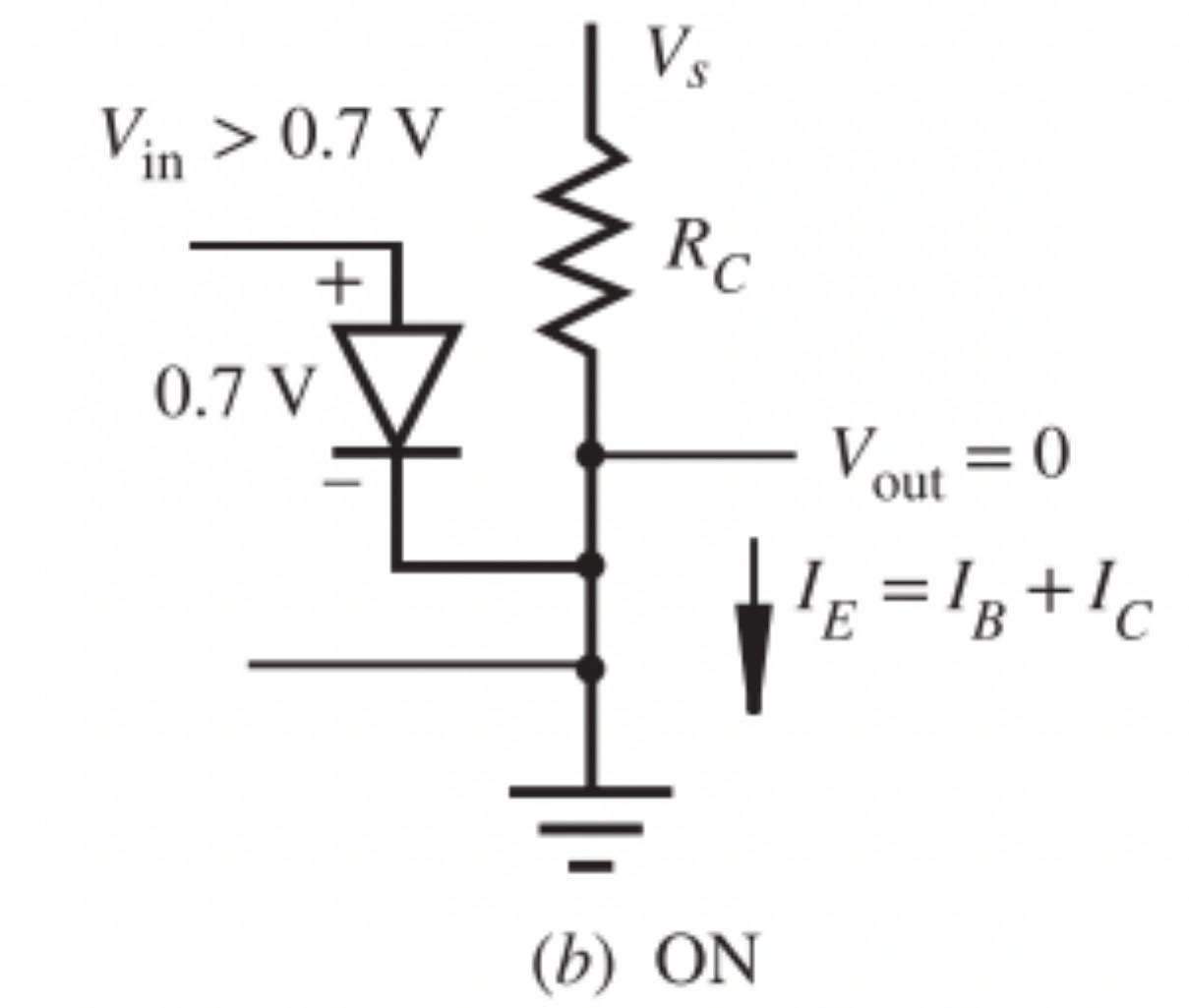For typical electronic applications
the common emitter configuration
is more appropriate because
it is easier to ensure
saturation \rightarrow max current flow



Summary of BJT Switch

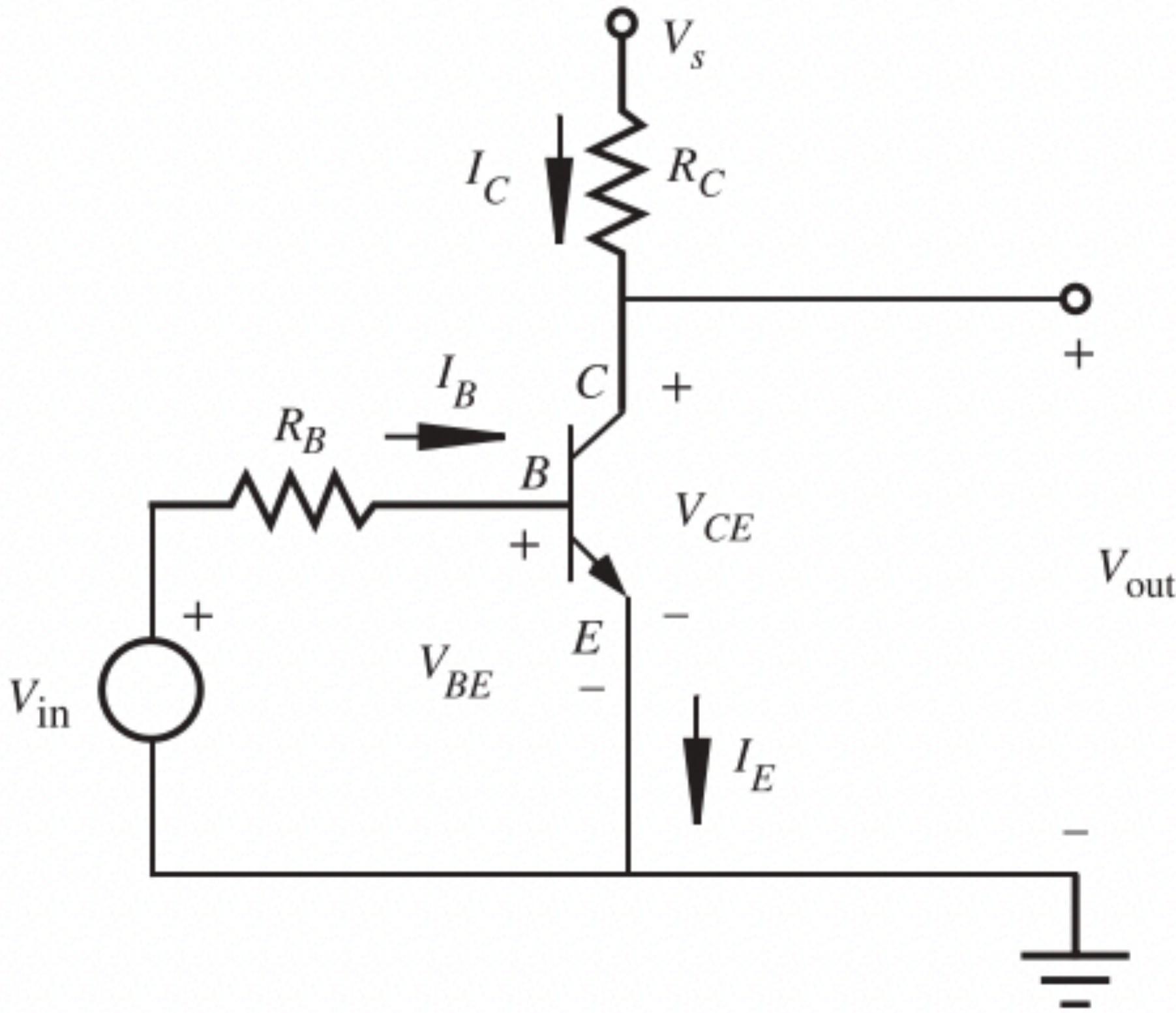



R_b is required

$$I_B = (V_{in} - V_B) / R_B$$

$$V_B = V_{BE} = 0.7 \text{ V}$$

$$I_C = (V_s - V_C) / R_C$$

$$V_C = V_{out} = 0.2 \text{ V}$$

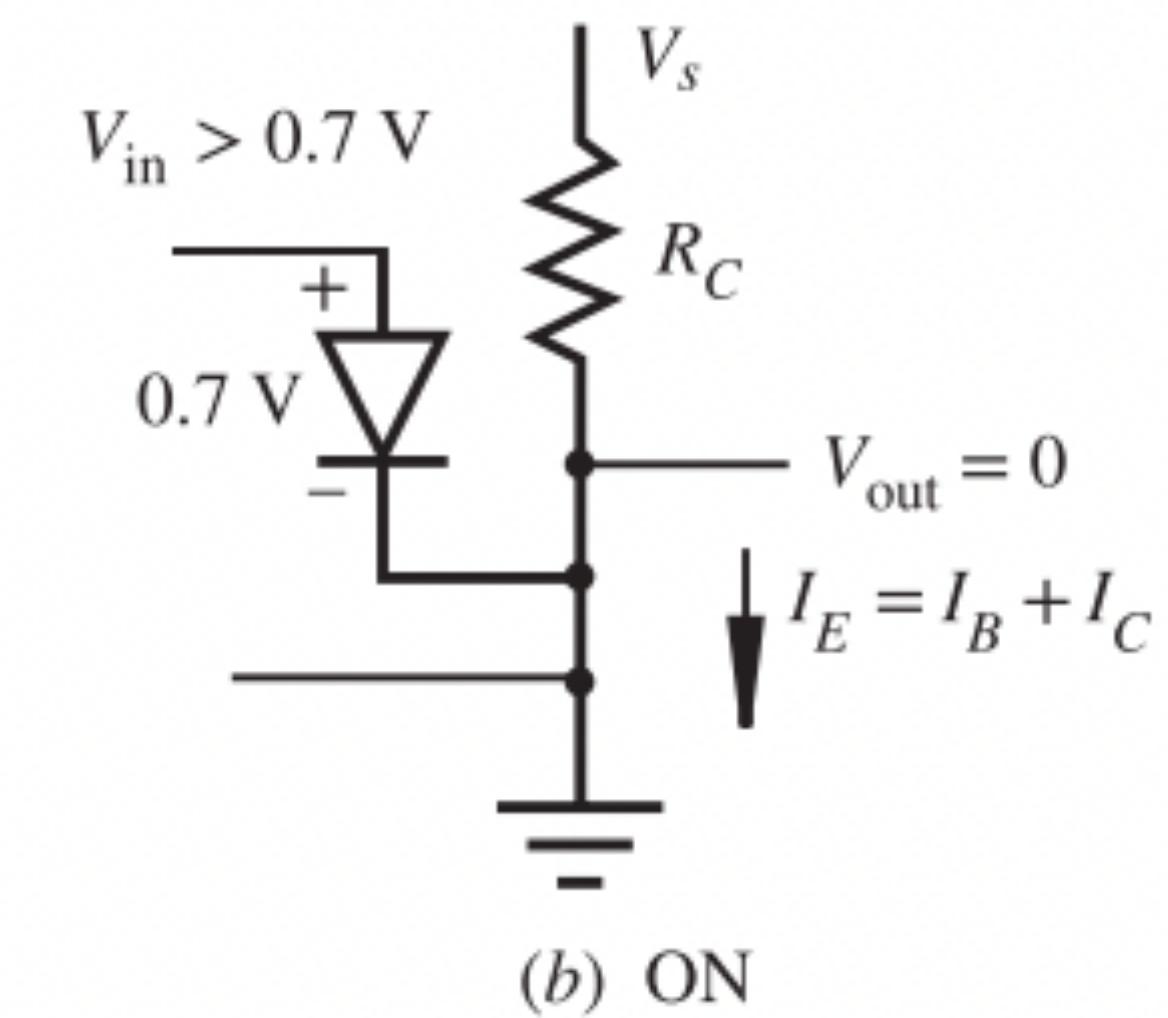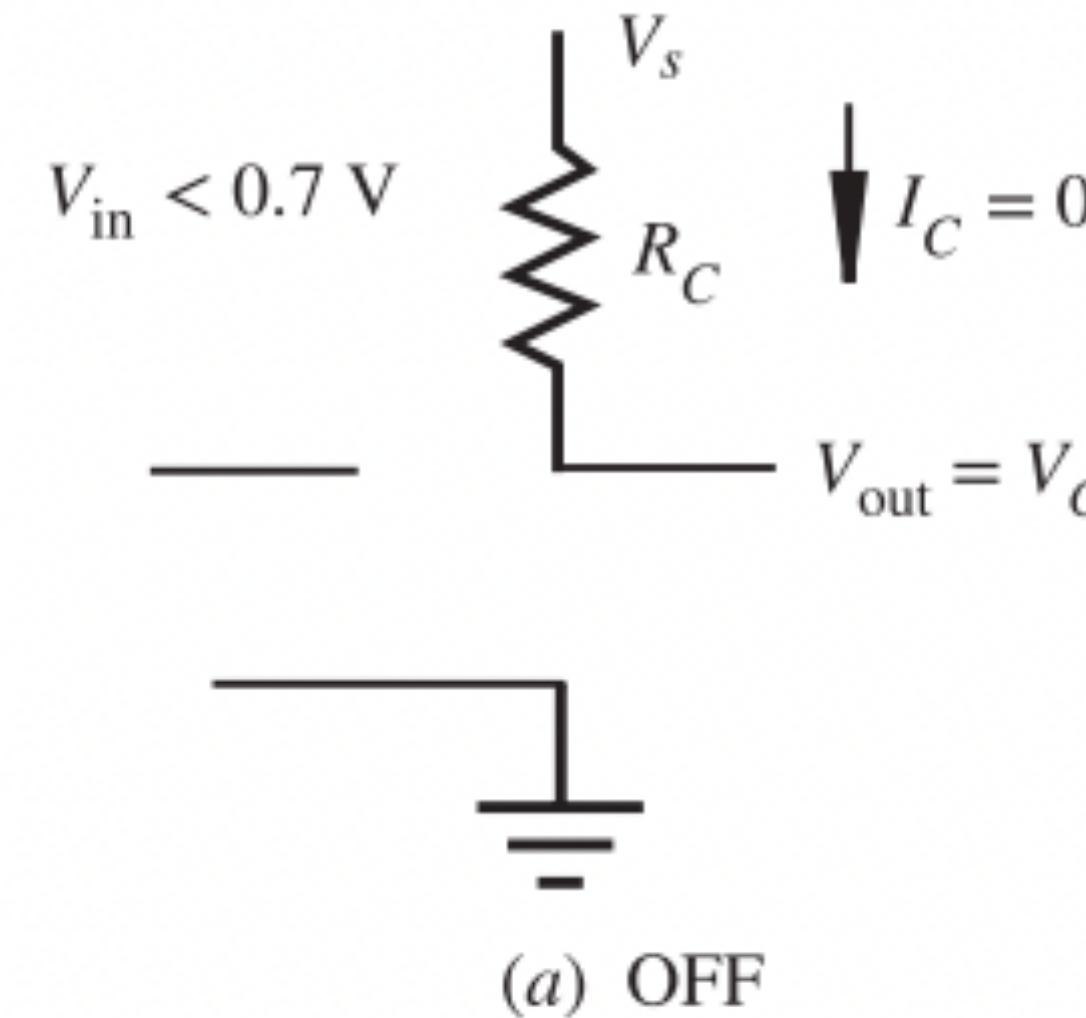

$$\textcircled{1} \quad V_C > V_B > V_E$$

Collector must be more positive
than base is emitter

$$\textcircled{2} \quad \text{To turn on } V_{BE} > 0.7 \text{ V}$$

$\textcircled{3} \quad I_C$ is independent of I_B , if saturation!

$\textcircled{4} \quad$ Minimum base current I_B for saturation
can be estimated $I_{B\min} \approx I_C / \beta$

$$I_B = 10 \cdot I_{B\min}$$

BJT Switch Applications

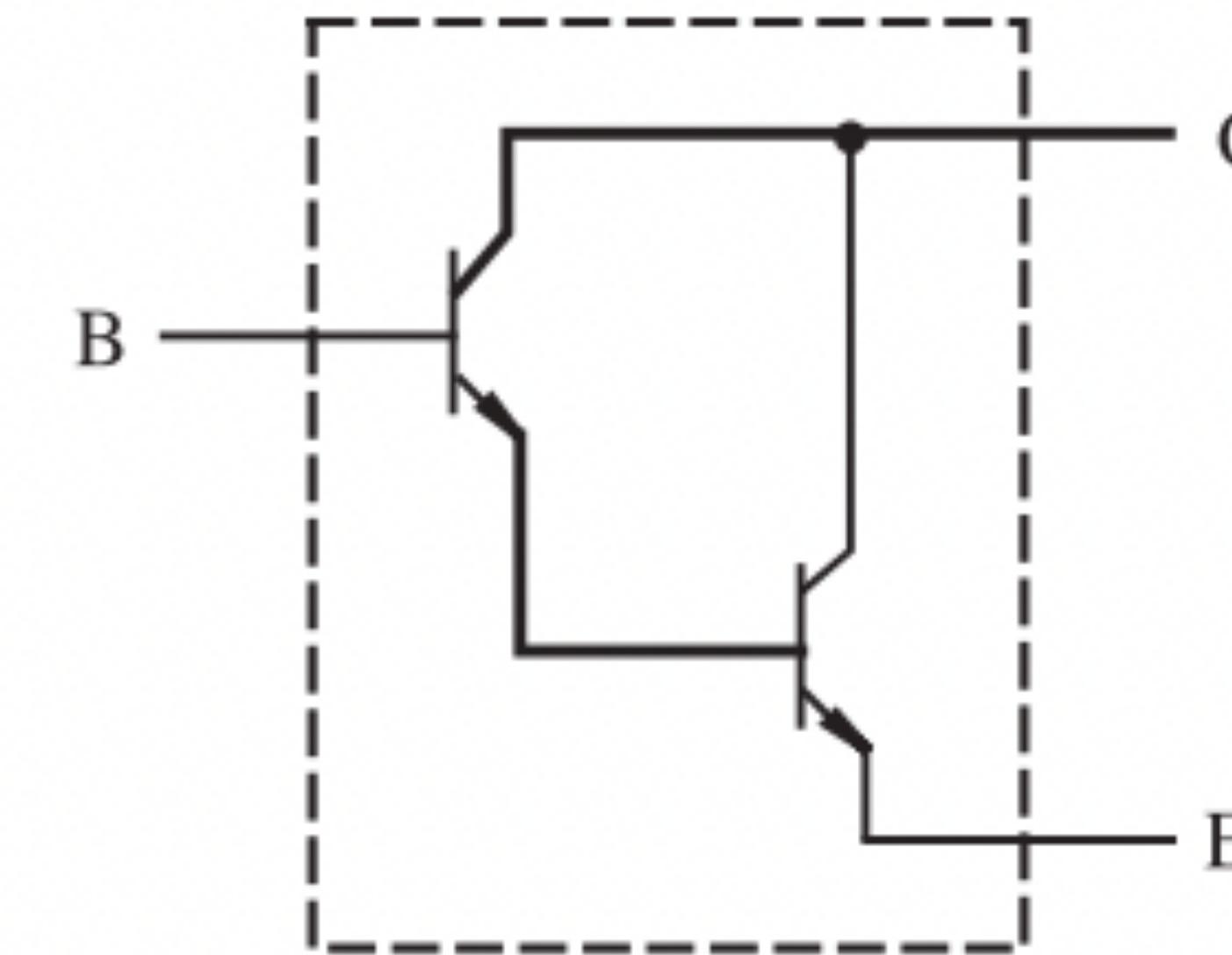
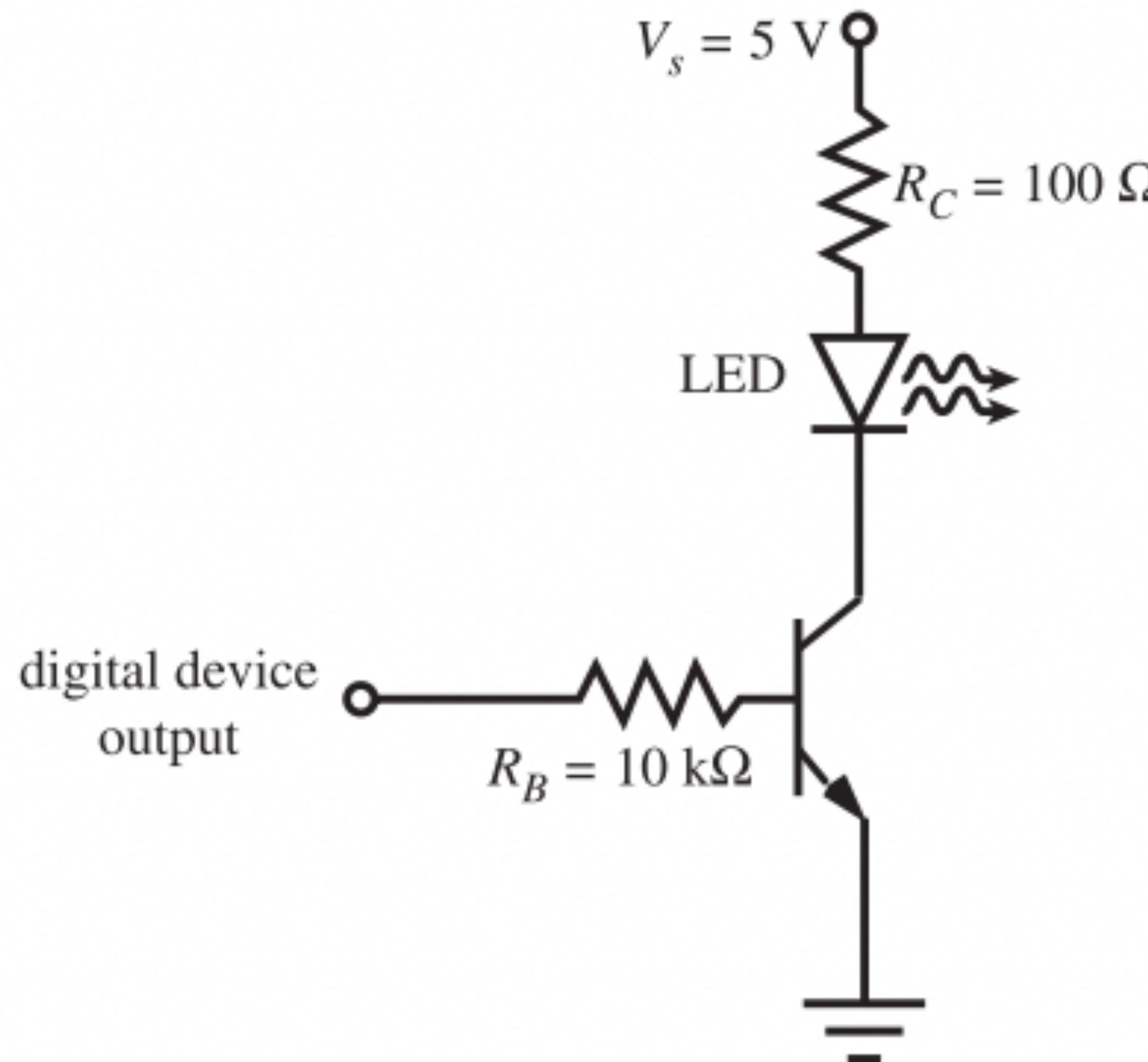


Figure 3.30 Darlington pair.

Current gain ~ 10000

BJT Switch Applications

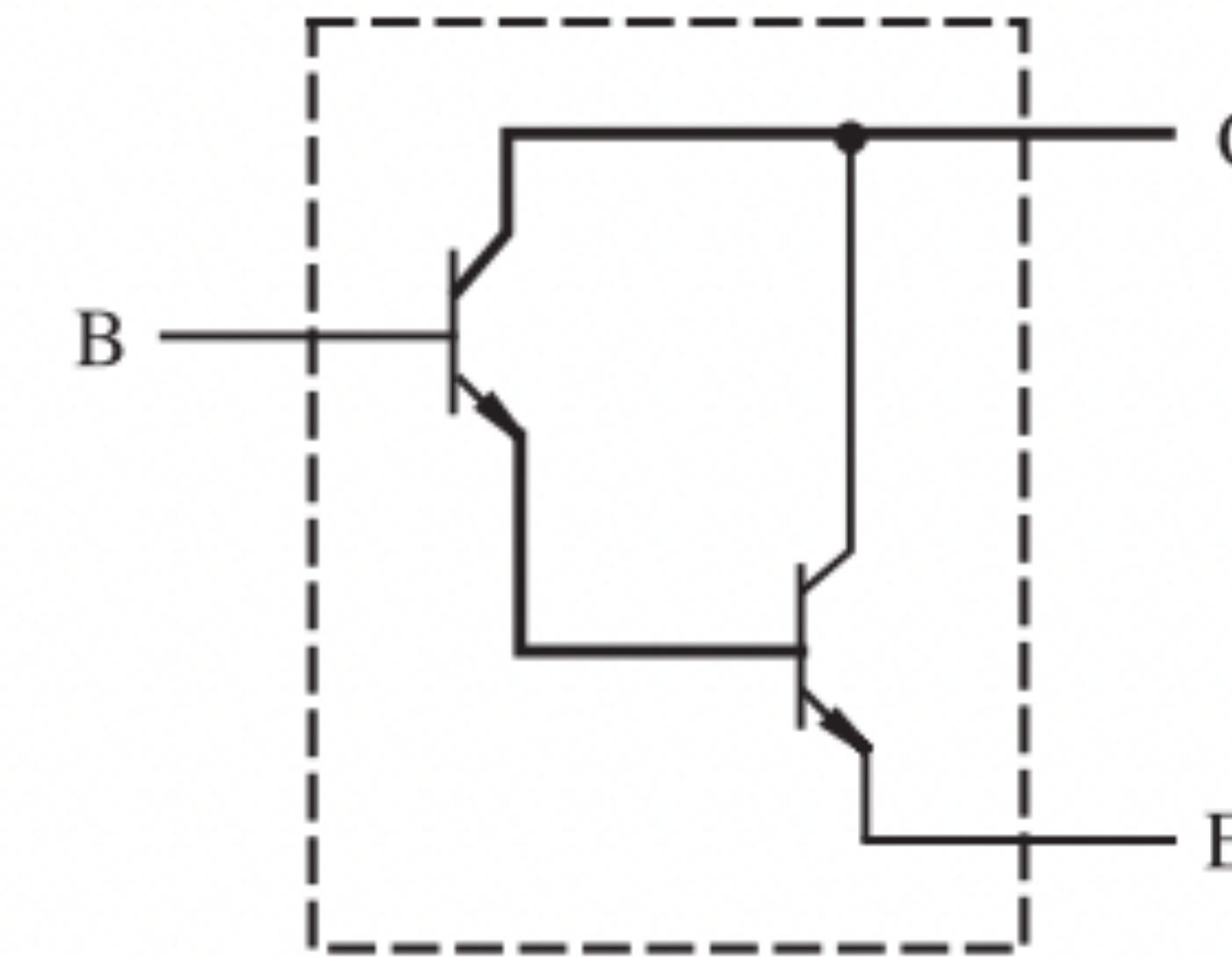
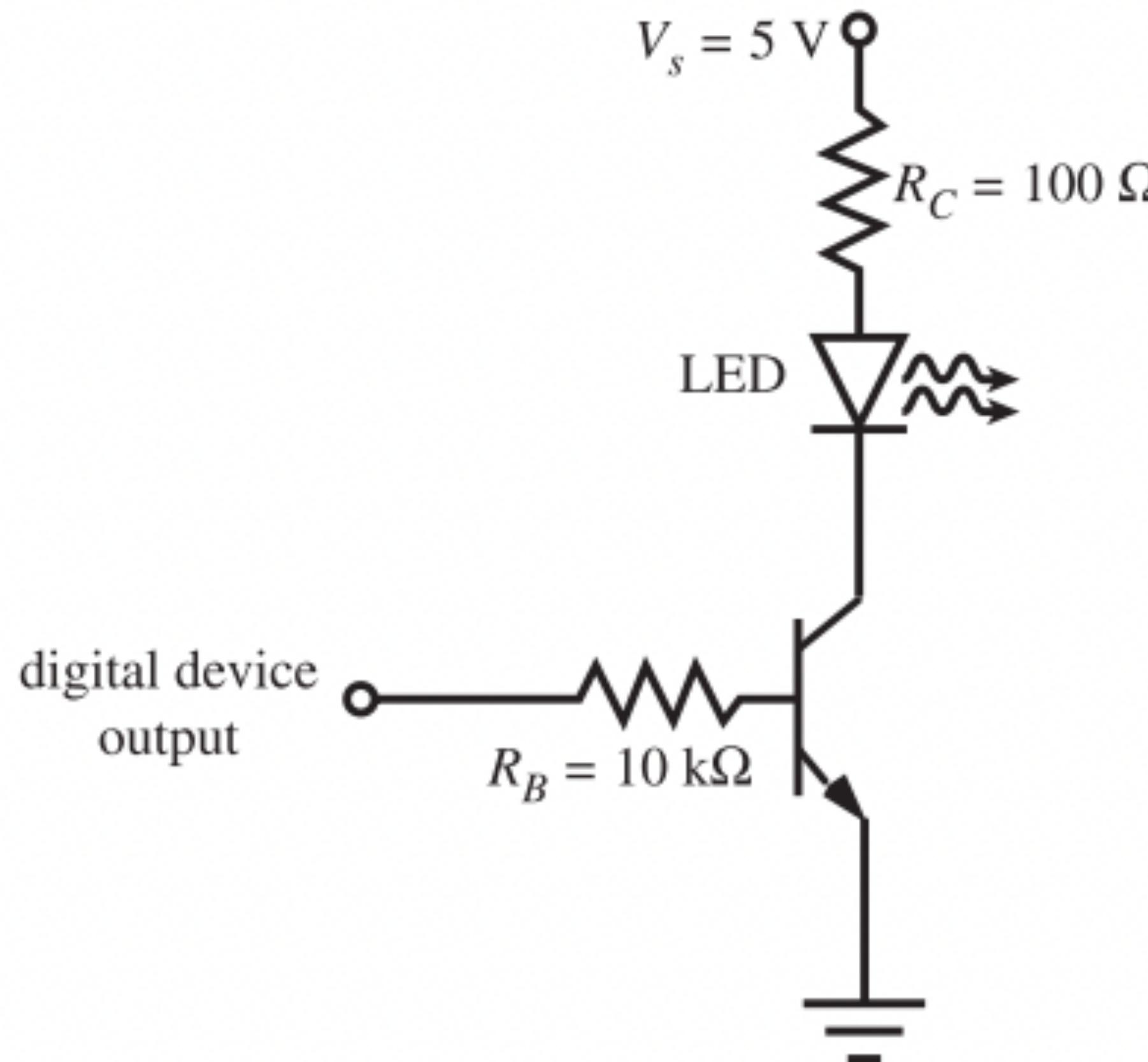


Figure 3.30 Darlington pair.

Current gain ~ 10000

BJT Switch Applications


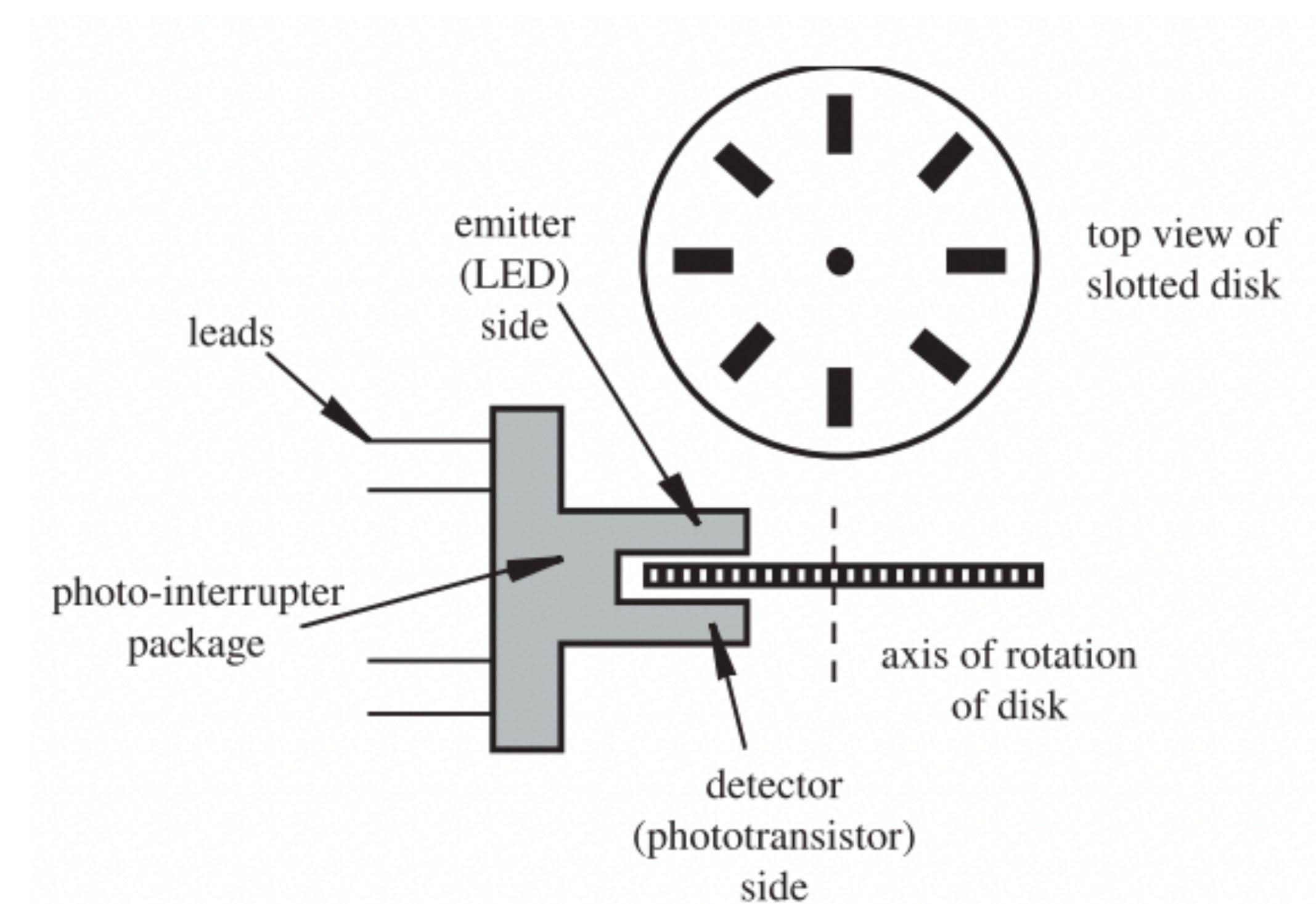
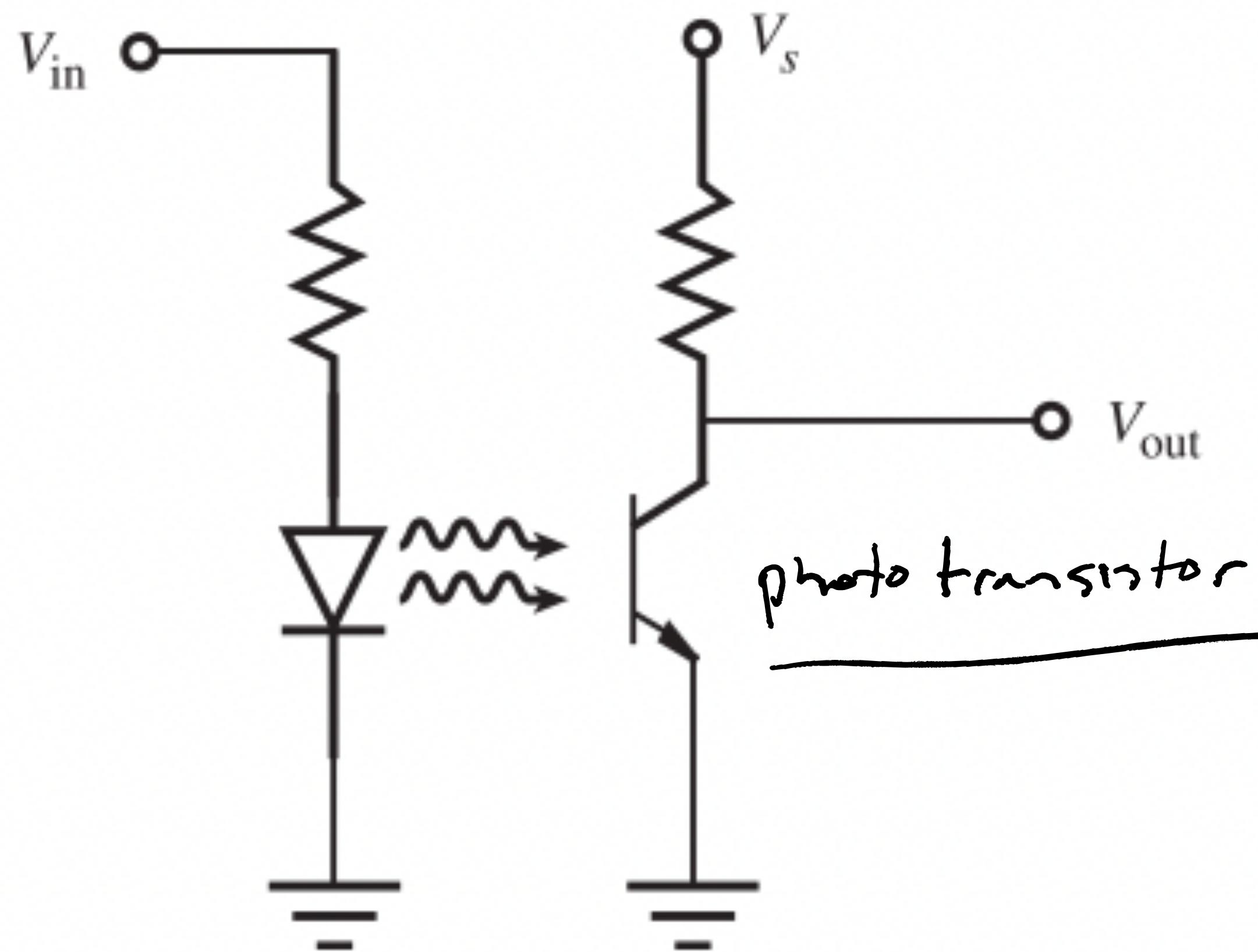


Figure 3.31 Optoisolator.

Types of optoisolators

Device type ^[note 5]	Source of light ^[7]	Sensor type ^[7]	Speed	Current transfer ratio
Resistive opto-isolator (Vactrol)	Incandescent light bulb	CdS or CdSe photoresistor (LDR)	Very low	<100% ^[note 6]
	Neon lamp		Low	
	GaAs infrared LED		Low	
Diode opto-isolator	GaAs infrared LED	Silicon photodiode	Highest	0.1–0.2% ^[22]
Transistor opto-isolator	GaAs infrared LED	Bipolar silicon phototransistor	Medium	2–120% ^[22]
		Darlington phototransistor	Medium	100–600% ^[22]
Opto-isolated SCR	GaAs infrared LED	Silicon-controlled rectifier	Low to medium	>100% ^[23]
Opto-isolated triac	GaAs infrared LED	TRIAC	Low to medium	Very high
Solid-state relay	Stack of GaAs infrared LEDs	Stack of photodiodes driving a pair of MOSFETs or an IGBT	Low to high ^[note 7]	Practically unlimited

BJT Packages

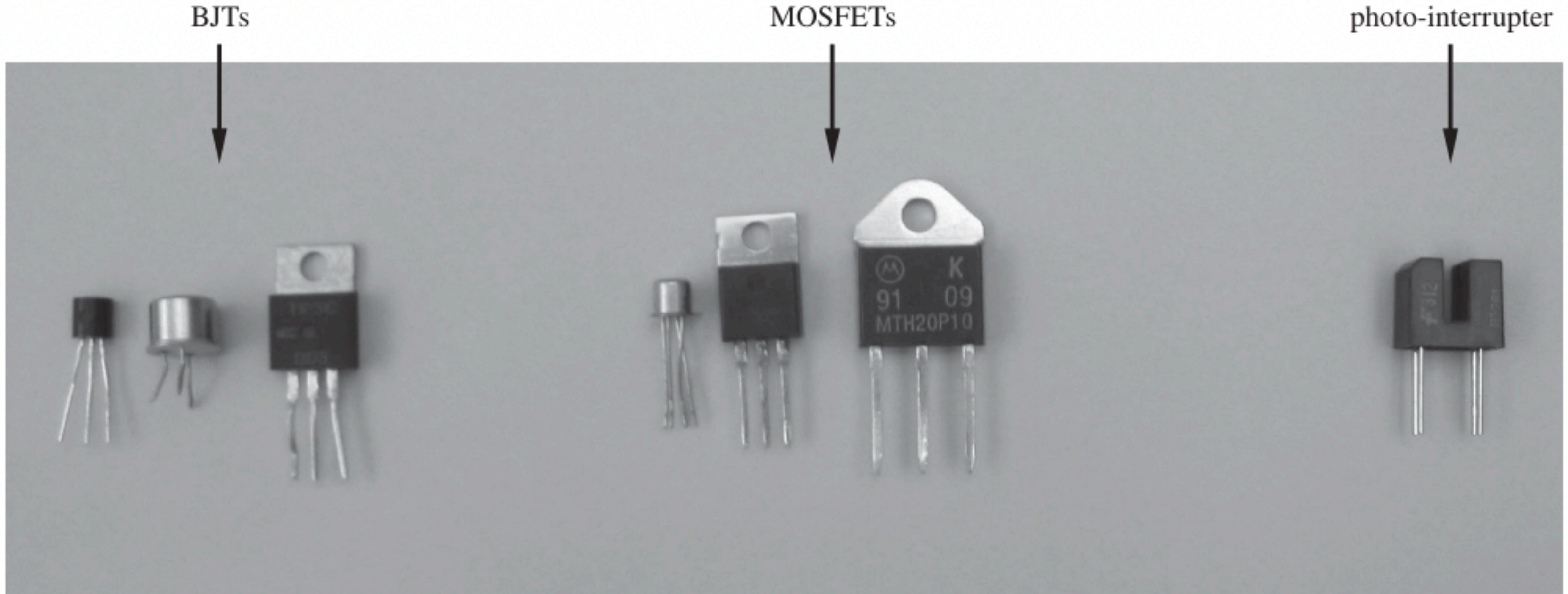

Field Effect Transistor (FET)

- Basic idea:

Voltage on one electrode
controls charge carriers
in a "channel"

- Channel: narrow region where current flows

- transconductance amplifier
→ output current is
controlled by input
voltage

(BJT is current-to-current amplifier
FET is voltage controlled current amplifier)

Flavors

enhancement / depletion mode
metal oxide semiconductor
(MOSFET)

Junction FET

waveform
Enhancement mode

→ off $V_g = 0$



Depletion mode

→ on $V_g = 0$

JFET are Dep.
mode

Application dependent

Field Effect Transistor (FET)

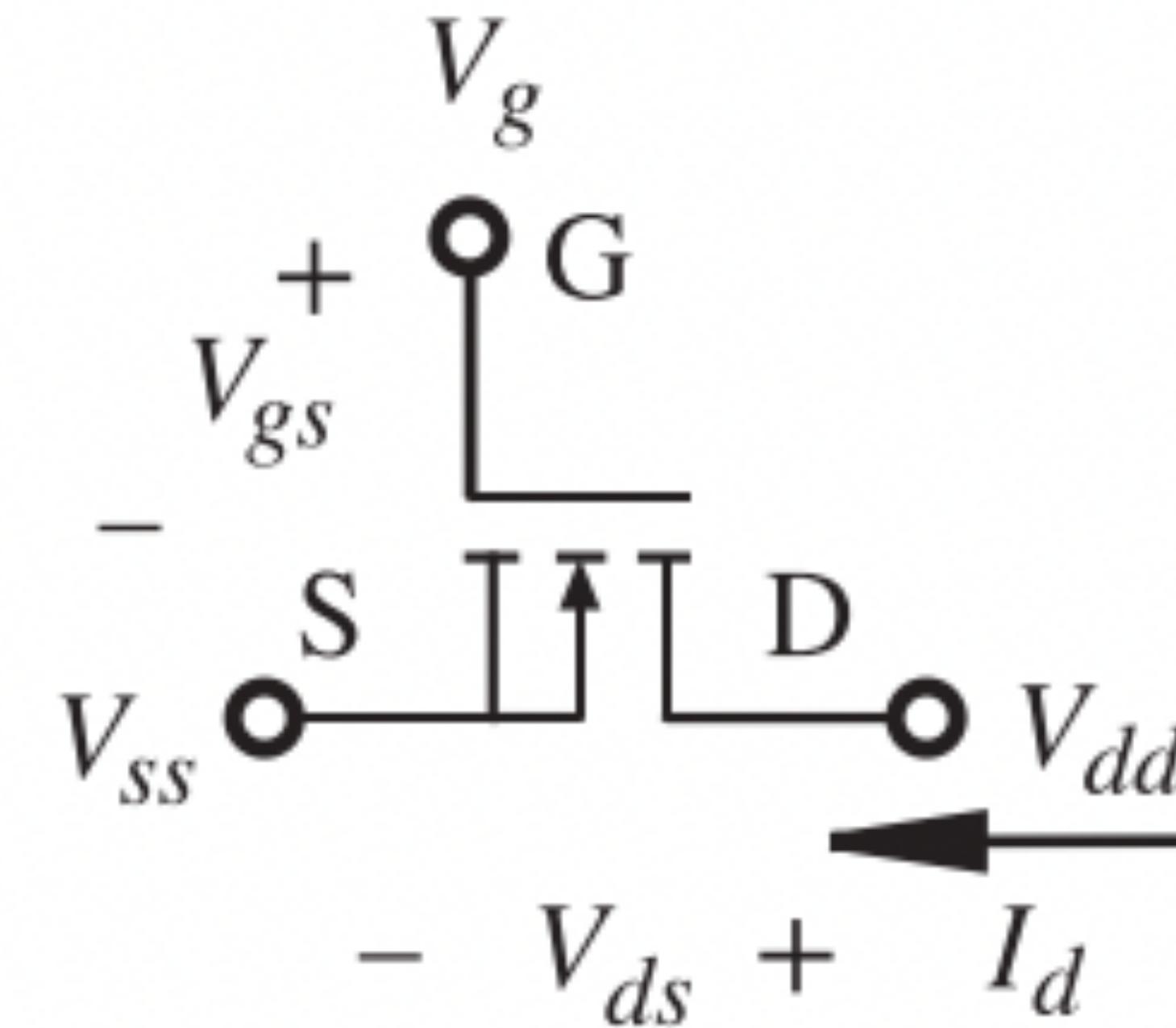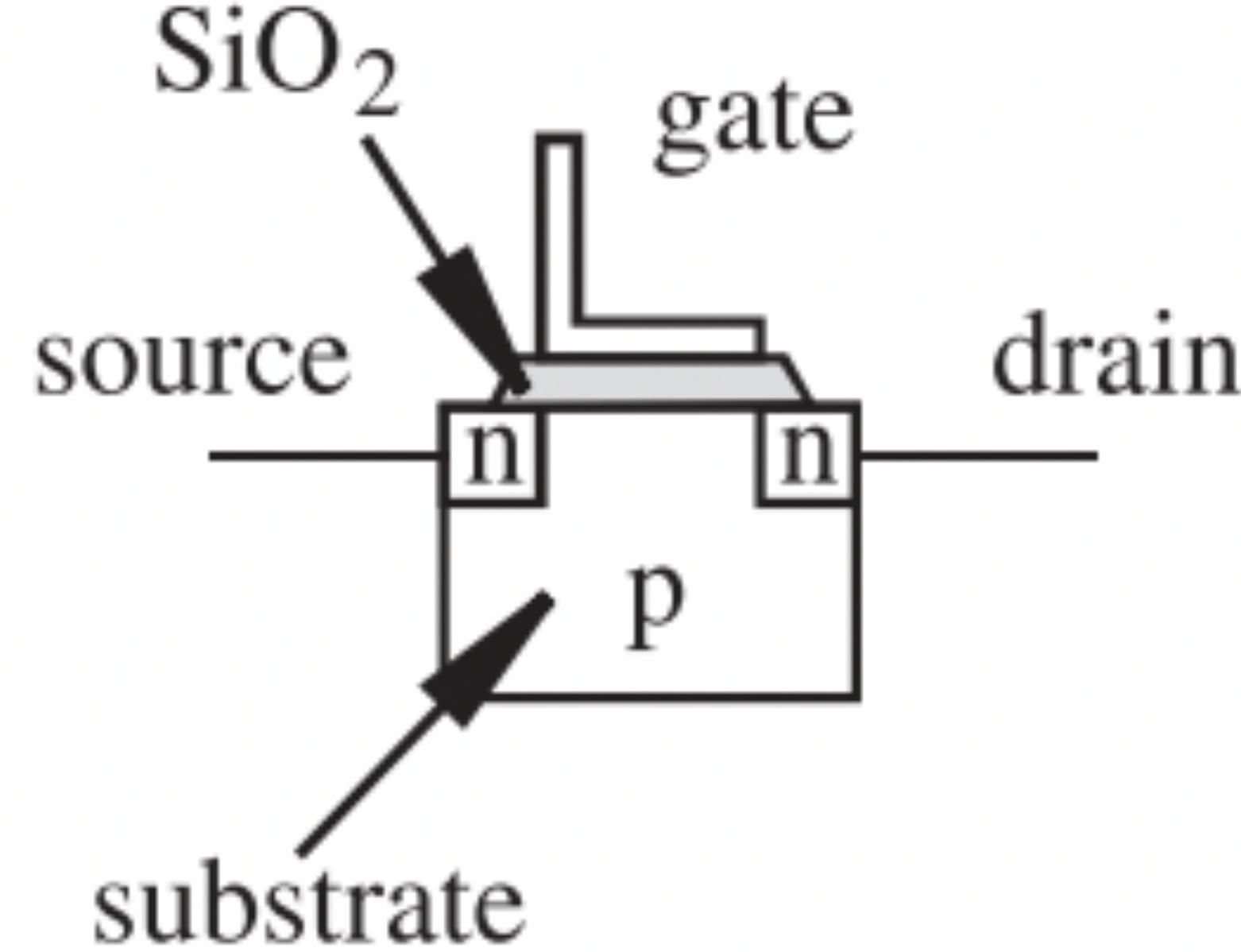


n - channel |

G - gate (base BJT)


D - drain (collector)

S - source (emitter)

Field Effect Transistor (FET)

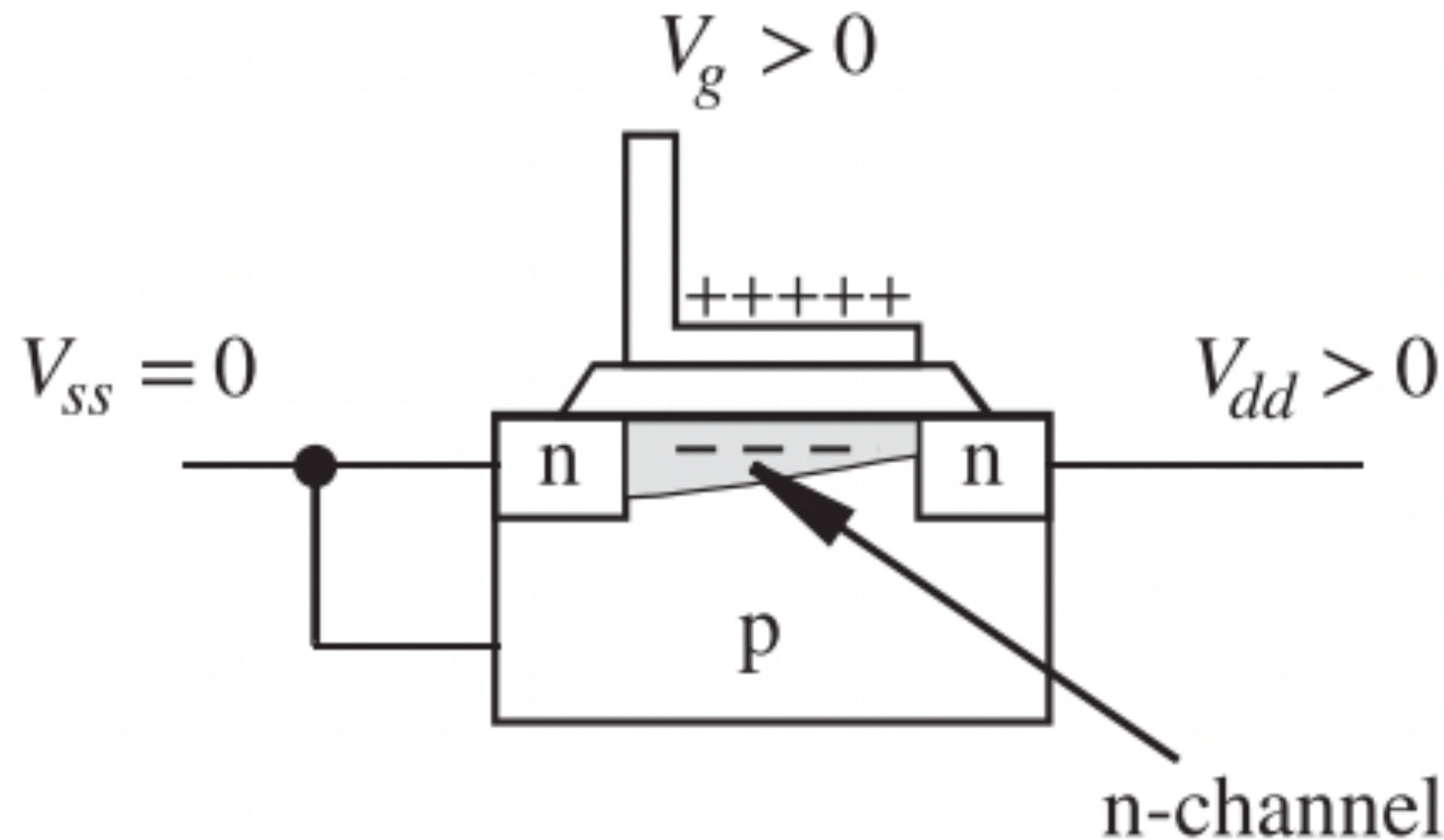

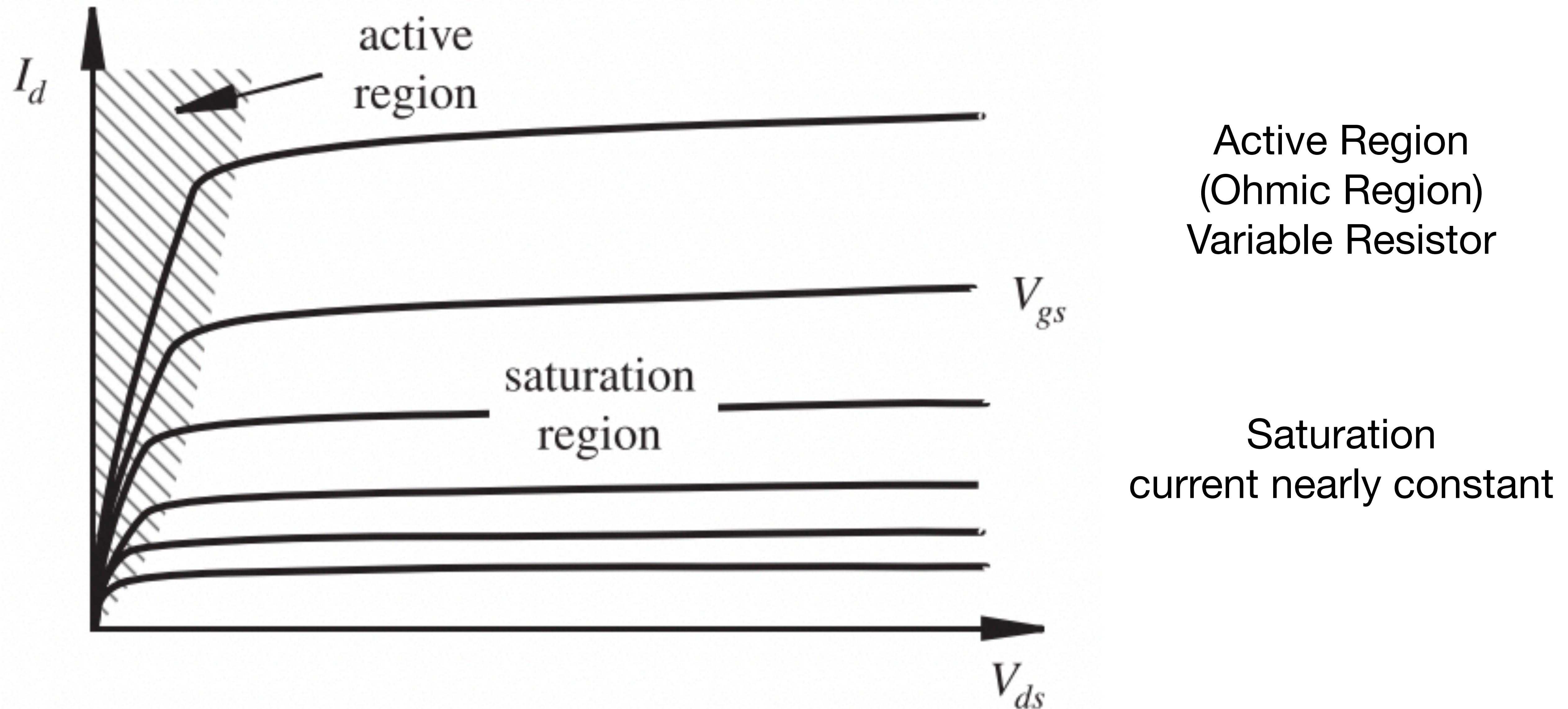n-Channel enhancement-mode MOSFET characteristic curves





amp, sign-in


What's good with MOSFETs?

- > High-current voltage controlled switch
- > analog switches (gates)
- > motor drives
- > operate @ much lower input current than BJT
 - less power, less heat
- > most common transistor in Integrated circuits (CPU, etc)
- > Can be fabricated extremely small, and
 - in complementary pair (n-channel & p-channel)
 - CMOS
 - symmetry allows for extreme compact fab

CMOS Teaser - Inverter

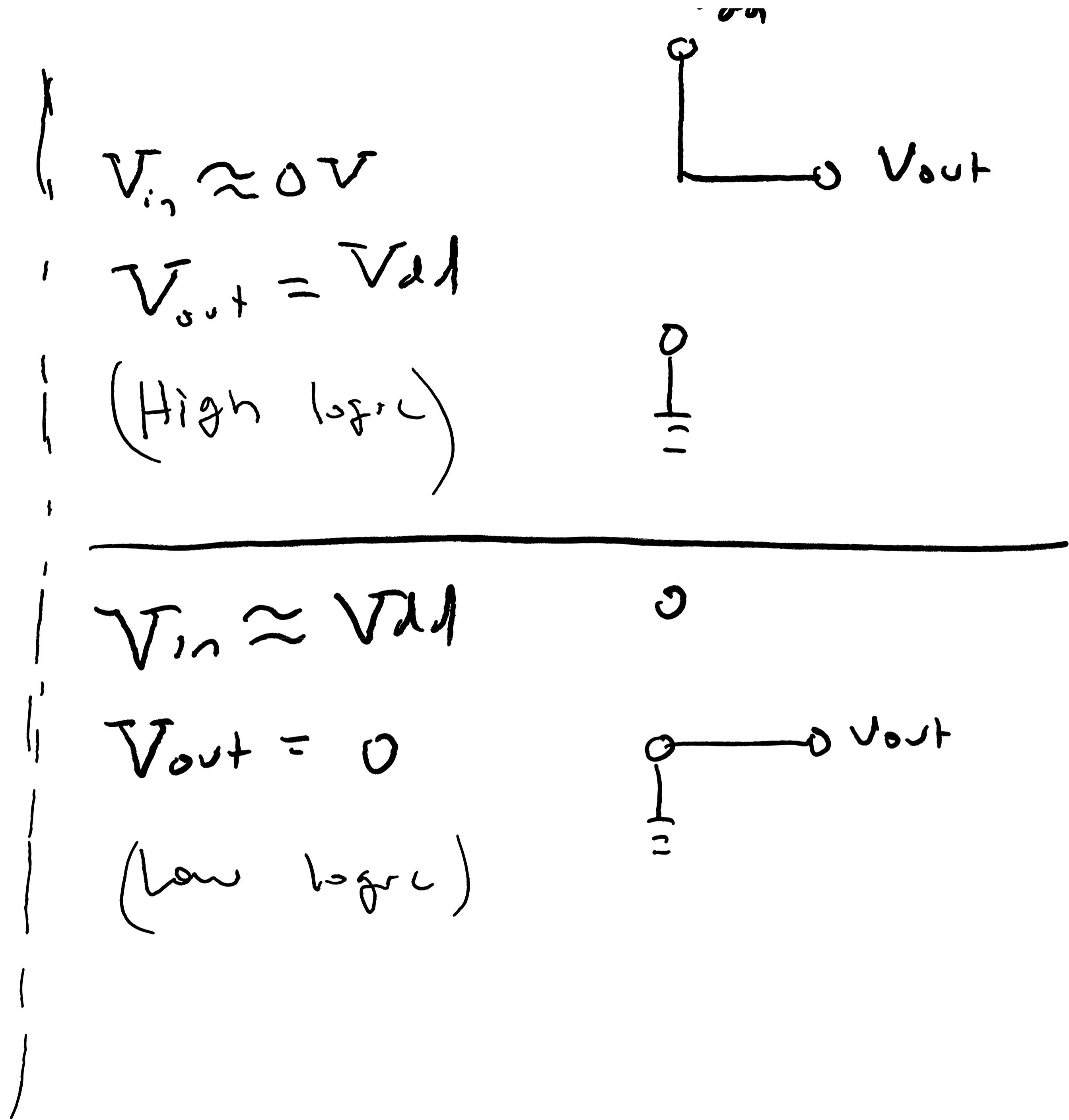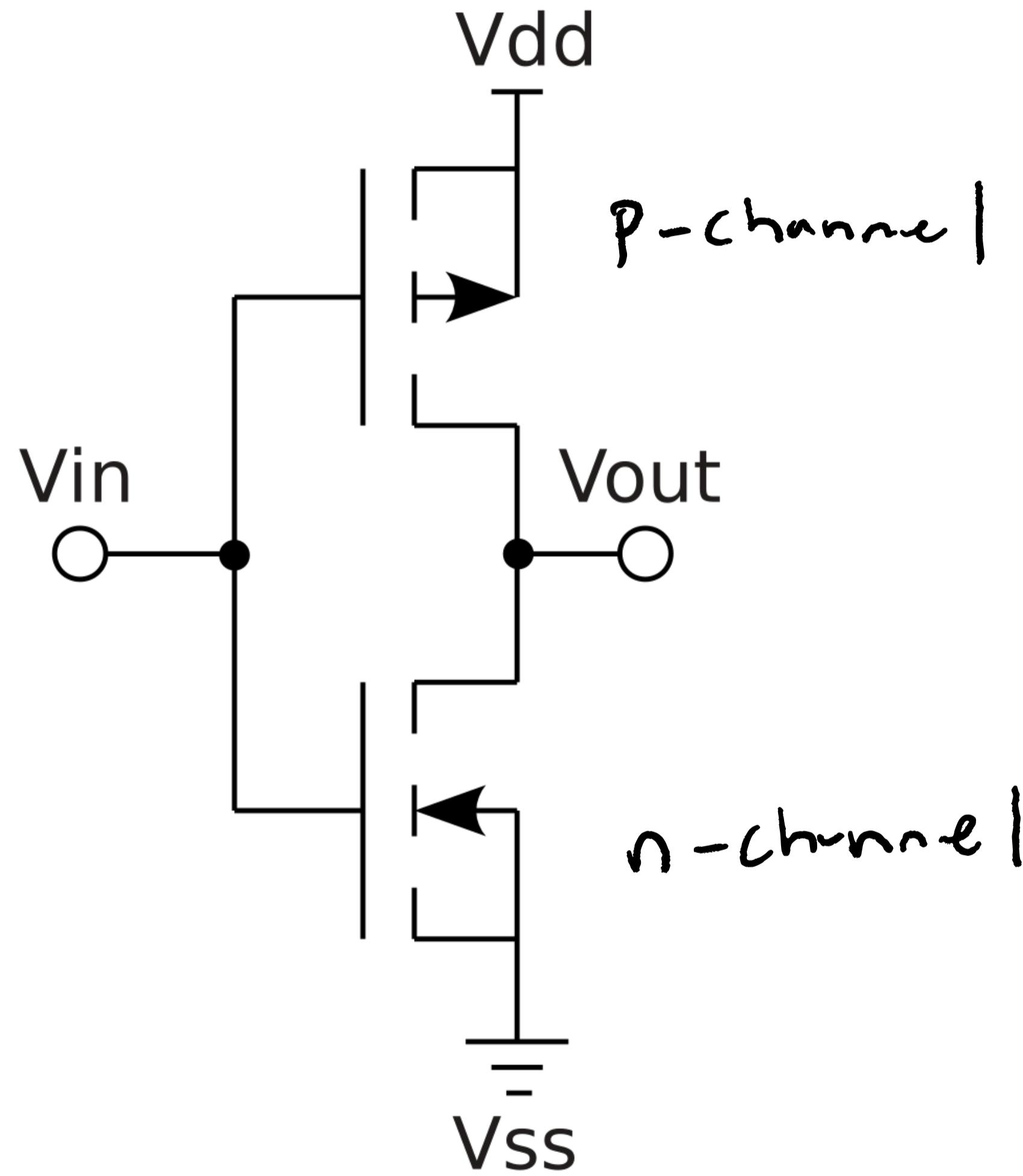


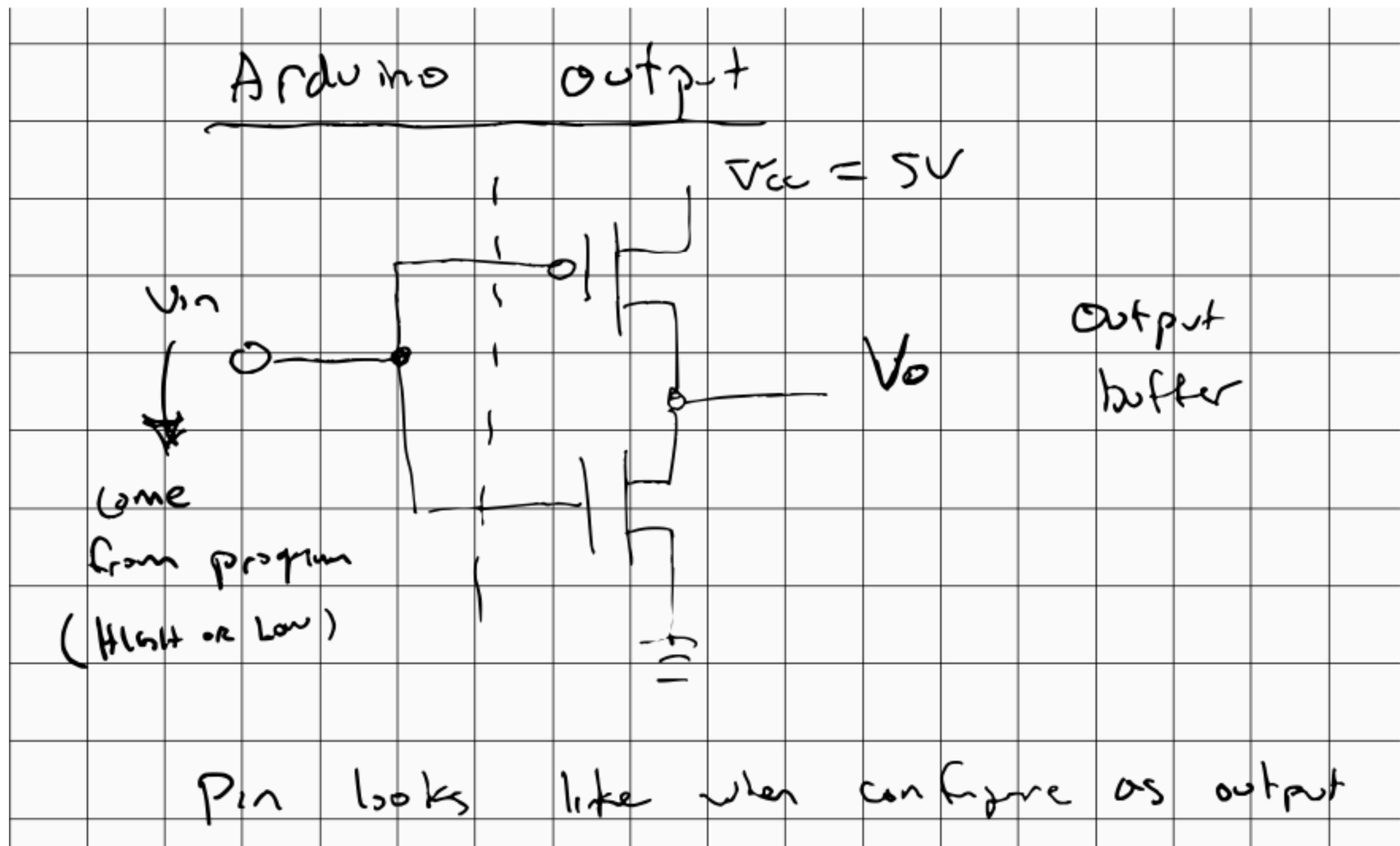Arduino output pins use **CMOS** architecture




- > power efficient
- > actively driven in both directions
- > very little power to hold state
- > most important: easy to fabricate


FET Symbols

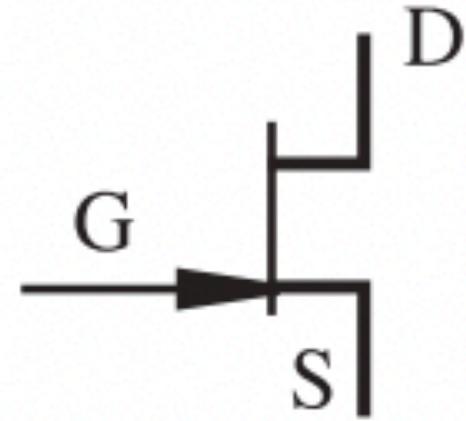


n-channel depletion-mode JFET

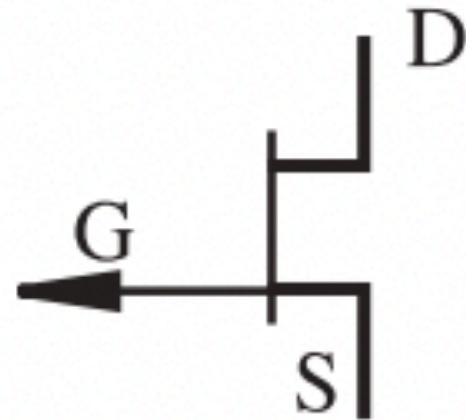

p-channel depletion-mode JFET

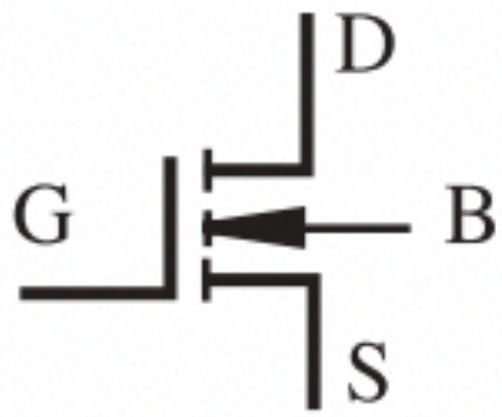

n-channel enhancement-mode MOSFET

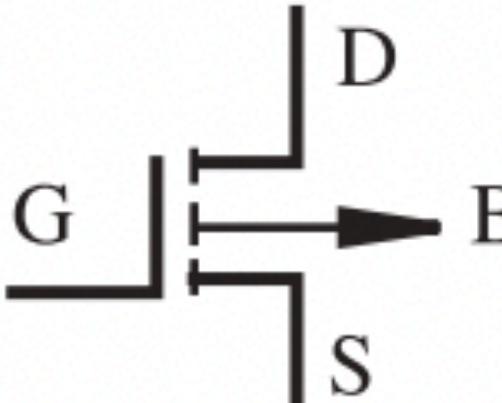


p-channel enhancement-mode MOSFET

① The direction of the arrow distinguishes between n- or p-channel



② A separation between gate & source is for MOSFET

③ A broken line indicates enhancement-mode

FET Power Switch

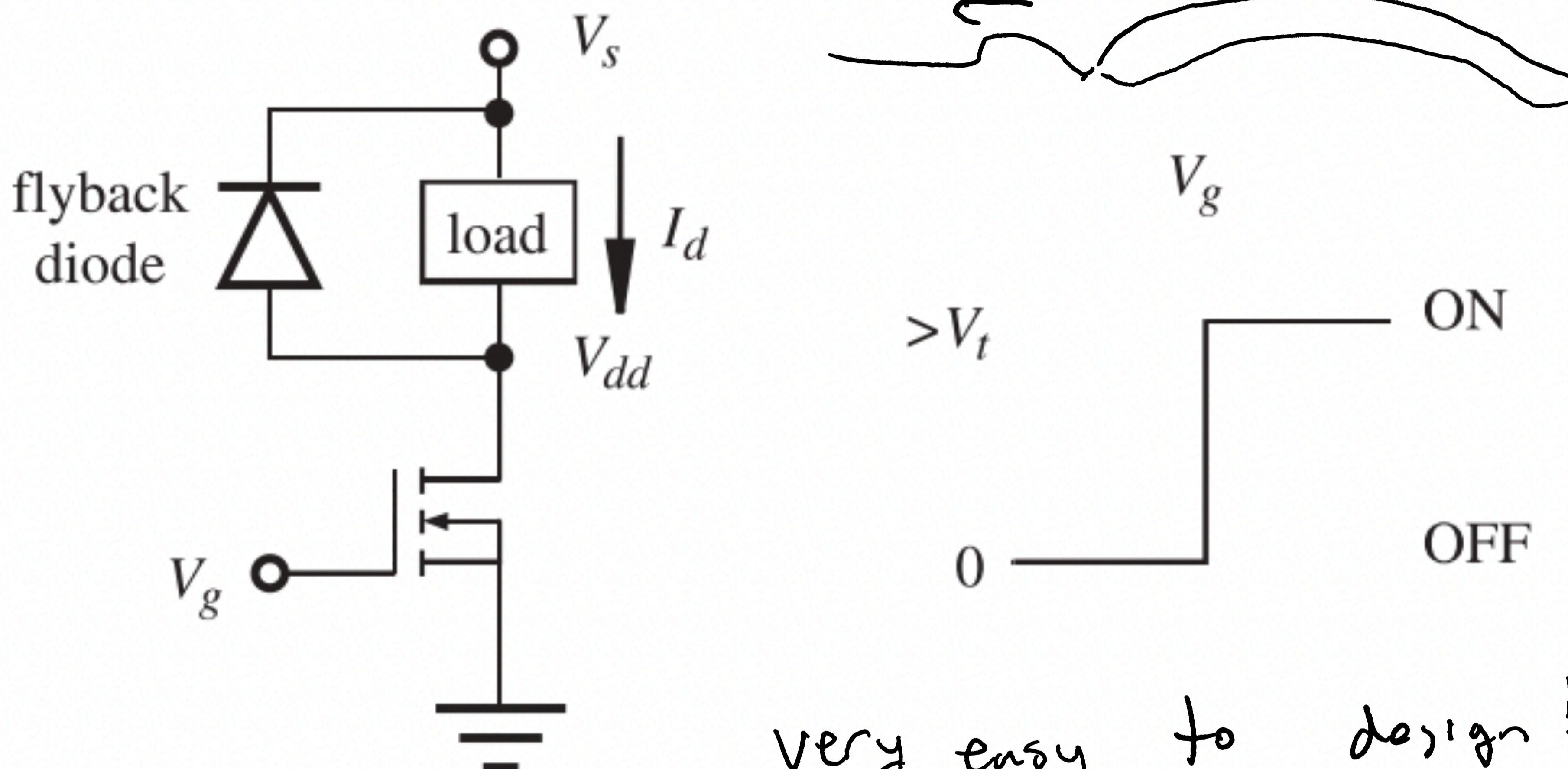

FET Analog Switch

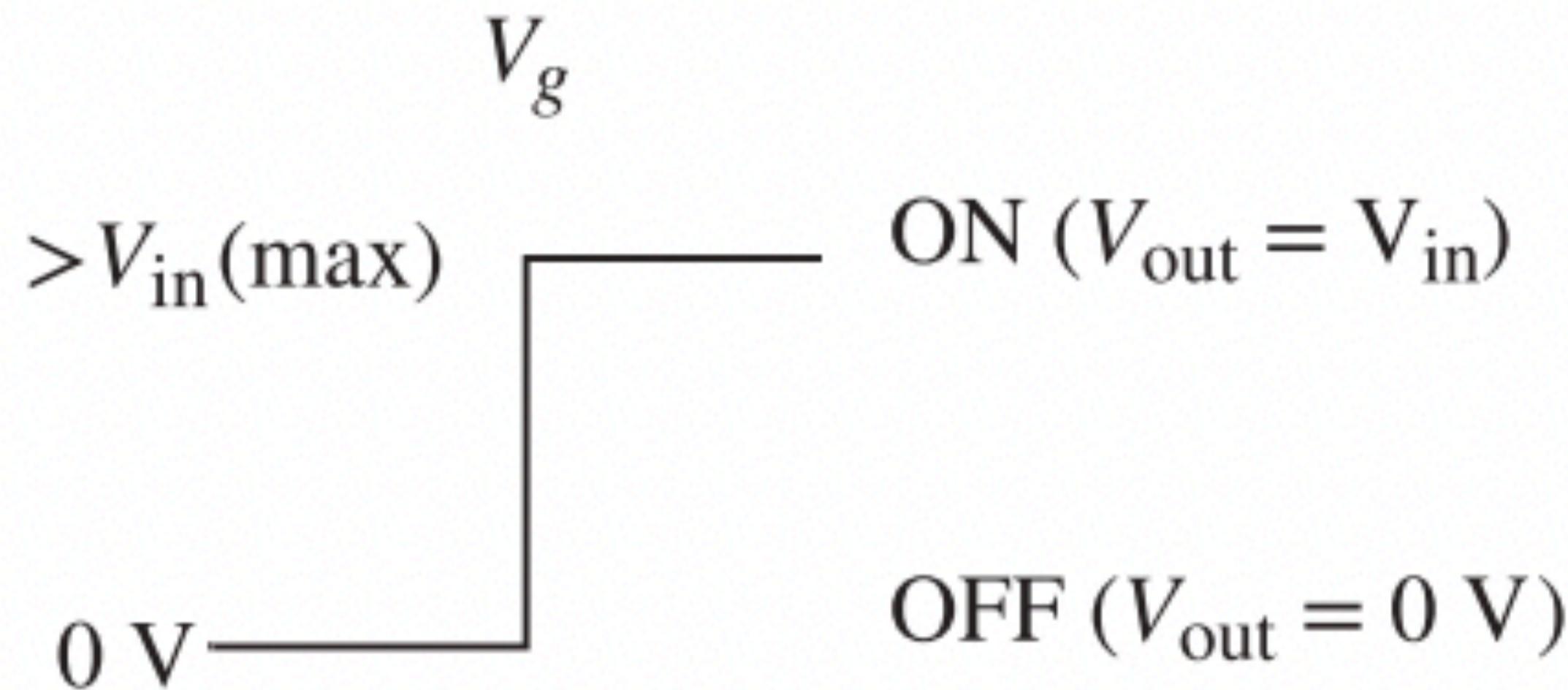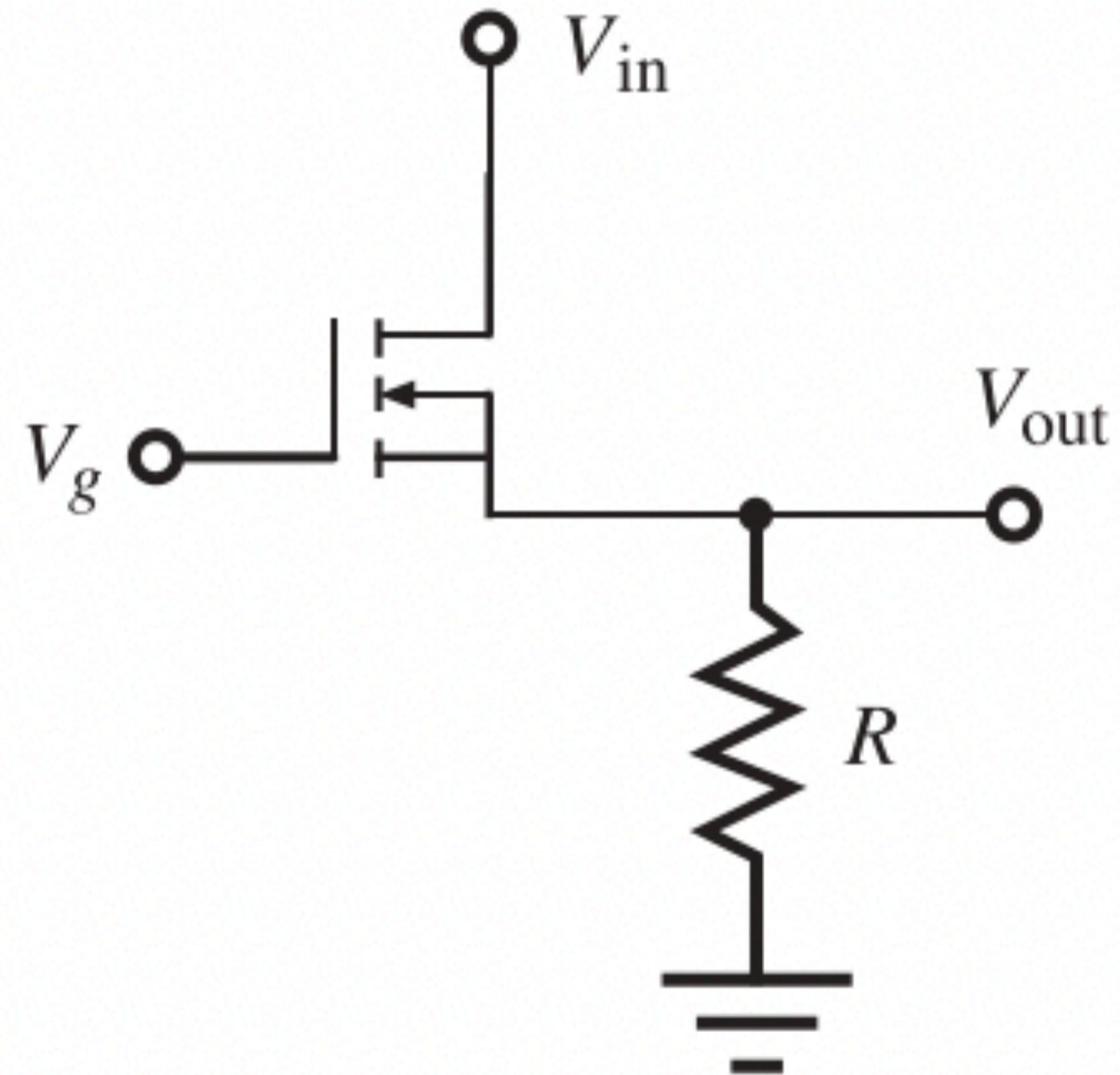

Pull-down
resistor \rightarrow ensure

$V_{out} \rightarrow 0$, when
transistor is off.

Summary BJT vs FET

Control

BJT: current controlled

FET: voltage controlled

Gain

BJT: larger current gain

FET: gain small

Size

BJT: large compared FET

FET: very tiny (Moore's Law)