

Digital Integrated Circuit (IC) Layout and Design - Week 4, Lecture 8

- <http://www.ee.ucr.edu/~rlake/EE134.html>
- HW 1 due next Tues.

Reading

- **Week 1 - Read Chapter 1 of text.**
- **Week 2 - Read Chapter 2 of text.**
- **Week 3 - Read Chapter 3 of text.**
- **Week 4 - Read Chapter 5 of text.**

Review/Finish

□ Inverter (Ch. 5)

- Voltage transfer curve (VTC)
- Switching Point


New

□ Inverter (Ch. 5)


- Capacitance
- Switching delay time



Simple Model versus SPICE

 

A Unified Model for Manual Analysis

 

define $V_{GT} = V_{GS} - V_T$

for $V_{GT} \leq 0$: $I_D = 0$

for $V_{GT} \geq 0$:

$$I_D = k' \cdot \frac{W}{L} \cdot \left(V_{GT} \cdot V_{\min} - \frac{V_{\min}^2}{2} \right) \cdot (1 + \lambda \cdot V_{DS})$$

with $V_{\min} = \min(V_{GT}, V_{DS}, V_{DSAT})$

Transistor Model for Manual Analysis

Table 3.2 Parameters for manual model of generic 0.25 μm CMOS process (minimum length device).


	V_{T0} (V)	γ ($\text{V}^{0.5}$)	V_{DSAT} (V)	k' (A/V^2)	λ (V^{-1})
NMOS	0.43	0.4	0.63	115×10^{-6}	0.06
PMOS	-0.4	-0.4	-1	-30×10^{-6}	-0.1

I keep all signs positive for PMOS and use V_{SG} , V_{SD} , I_{SD} .




Voltage Transfer Characteristic


CMOS Inverter Load Characteristics

 


CMOS Inverter VTC

 

 Switching Threshold as a function of Transistor Ratio



Determining V_{IH} and V_{IL}

 


A simplified approach


$$V_{IH} - V_{IL} = -\frac{(V_{OH} - V_{OL})}{g} = \frac{-V_{DD}}{g}$$

$$V_{IH} = V_M - \frac{V_M}{g} \quad V_{IL} = V_M + \frac{V_{DD} - V_M}{g}$$
 
$$NM_H = V_{DD} - V_{IH} \quad NM_L = V_{IL}$$





Inverter Gain

 


$$g = -\frac{1}{I_D(V_M)} \frac{k_n V_{DSATn} + k_p V_{DSATp}}{\lambda_n - \lambda_p}$$
$$\approx \frac{1+r}{(V_M - V_{Tn} - V_{DSATn}/2)(\lambda_n - \lambda_p)}$$

Gain as a function of VDD

  


Impact of Process Variations

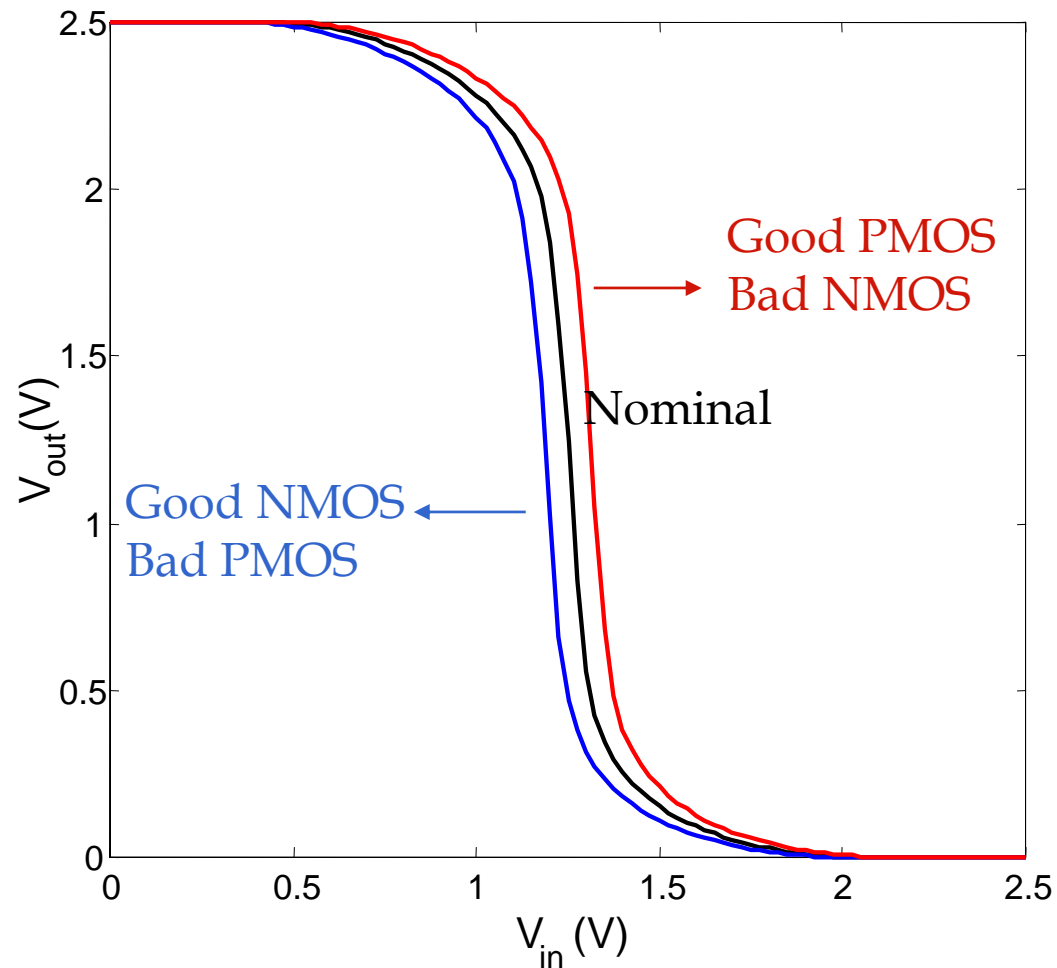


CMOS Inverter

First-Order DC Analysis

 


$$\begin{aligned} V_{OL} &= 0 \\ V_{OH} &= V_{DD} \\ V_M &= f(R_n, R_p) \end{aligned}$$

CMOS Inverter: Transient Response

 

(a) Low-to-high

 

(b) High-to-low

$$t_{pHL} = f(R_{on} \cdot C_L) = 0.69 R_n C_L$$