
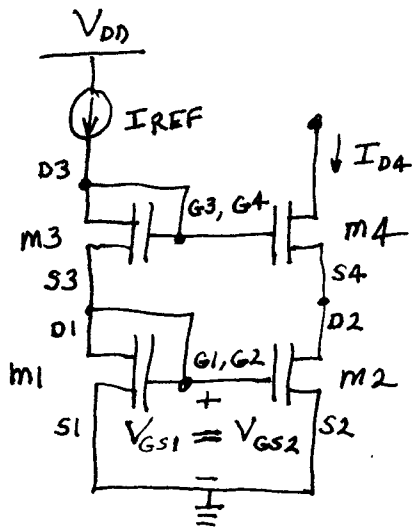


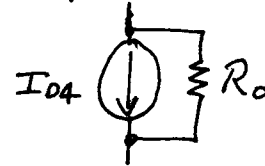Cascode Connection of 2 Current Mirrors (20.1.1)



MOTIVATION: Increase Output resistance (R_o)




Make a more ideal current source.





Drawback: Reduced output voltage swings.

OUTPUT RESISTANCE (low f)

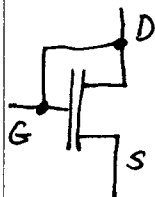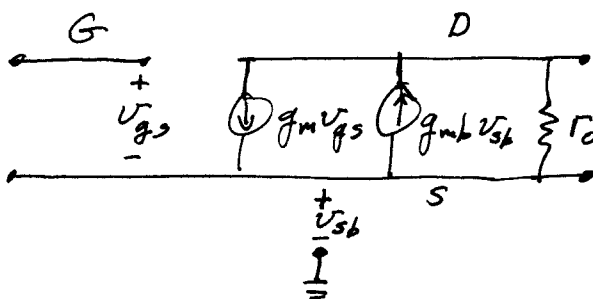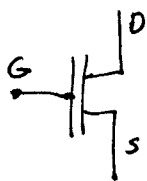



QUICK REVIEW

DIODE
CONNECTED
FET
 $D = G$

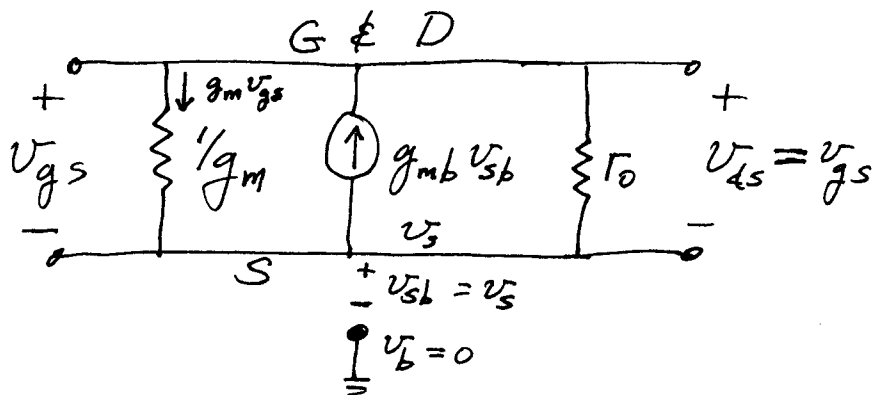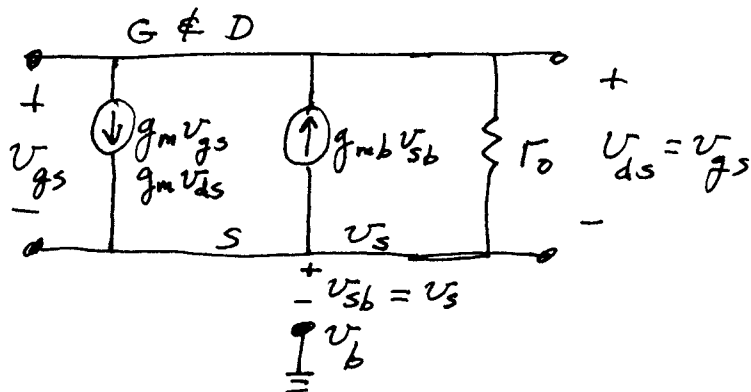CALCULATING OUTPUT RESISTANCE



1. "Kill" any input ac sources:
 - a. Short ac v -sources.
 - b. Open ac i -sources.
2. Apply ac voltage (current) source at output
3. Calculate current (voltage) at output.
4. Ratio is output resistance v_o/i_o .

Common SOURCE Output resistance (R_o)

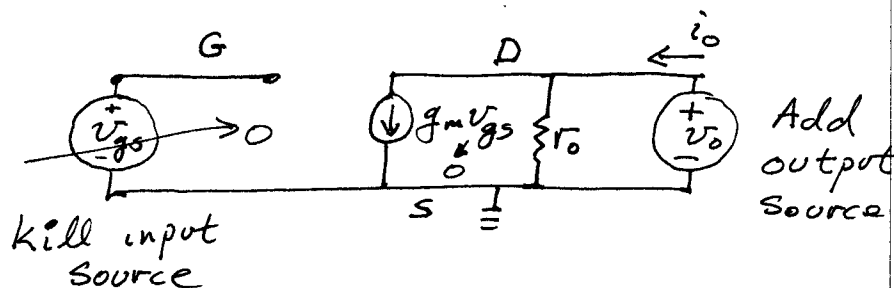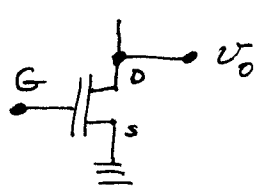

$$R_o = \frac{v_o}{i_o} = r_o$$

Common SOURCE with SOURCE Degeneration

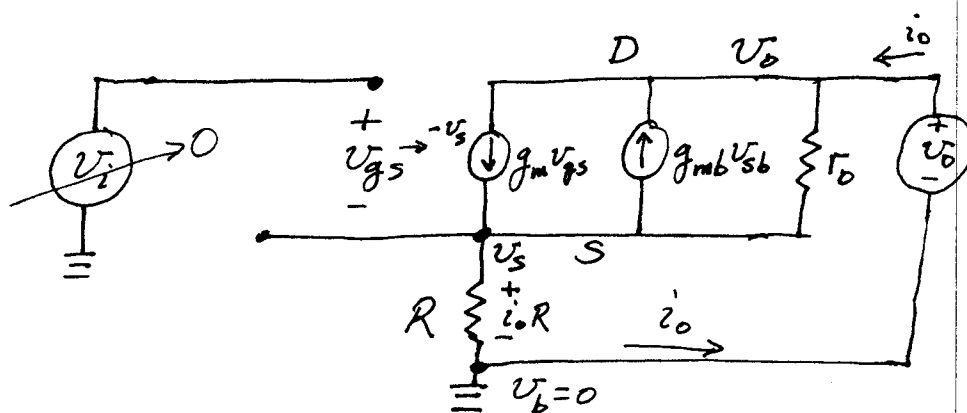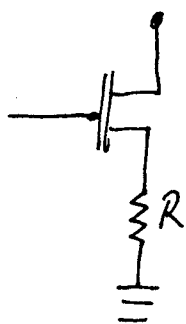

KCL at drain:


$$i_o - \frac{v_o - v_s}{r_o} + \underbrace{g_{mb} v_s}_{\chi g_m} + g_m v_s = 0$$

$$v_s = i_o R$$

$$i_o + i_o \frac{R}{r_o} + g_m (1 + \chi) i_o R = \frac{v_o}{r_o}$$

$$\boxed{\frac{v_o}{i_o} = r_o + R + g_m (1 + \chi) R r_o = R_{out}}$$

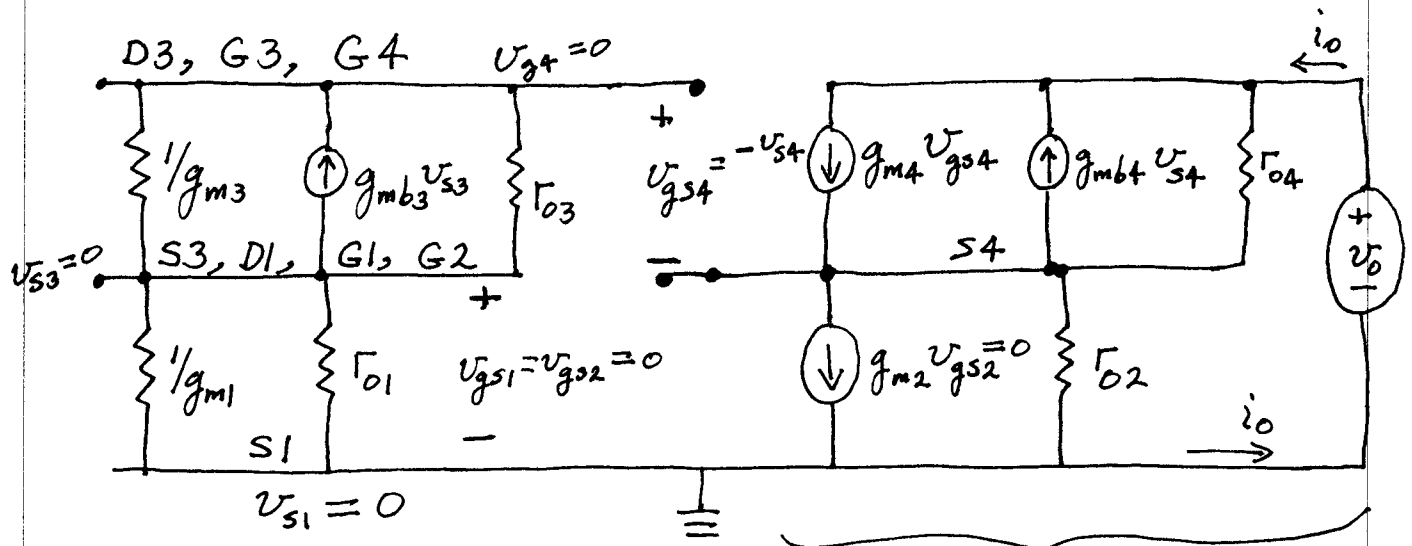SMALL SIGNAL EQUIVALENT CIRCUIT OF CASCODE CURRENT MIRROR p. L4.1



COMMON SOURCE with
SOURCE DEGENERATION
 $R = r_{o2}$

$$R_{out} = r_{o4} + r_{o2} + (g_{m4}(1+\chi) r_{o4} r_{o2})$$

This term dominates. $\gg r_o$
 $g_m r_o$ is the gain^(av) of a common source FET $\gg 1$

$$R_{out} \approx g_{m4}(1+\chi) r_{o4} r_{o2} \gg r_o$$

$$R_{out} \approx g_{m4} r_o^2. \quad \text{FOR simple current mirror, } R_{out} = r_o.$$

STACK 3 high Fig. 20.9

$$R_{o3} = r_o + R_{out,2} + g_m(1+\chi) r_o R_{out,2}$$

$$R_{o3} \approx g_m^2 r_o^3$$

BENEFIT INCREASED R_{out}

DRAWBACK REDUCED V_{D4} swing to keep $M4$ in saturation.

MINIMUM V_{D4} for $M4$ to stay in saturation?


$$V_{DS4} \geq V_{GS4} - V_{TH}$$

Choose (as before) $V_{GS1} = V_{GS2} = V_{GS3} = V_{GS4} = 1.2V$

$$V_{DS4} \geq V_{GS4} - V_{TH} = 1.2 - 0.83 = 0.37 \equiv \Delta V$$

ΔV is referred to as the excess gate voltage.
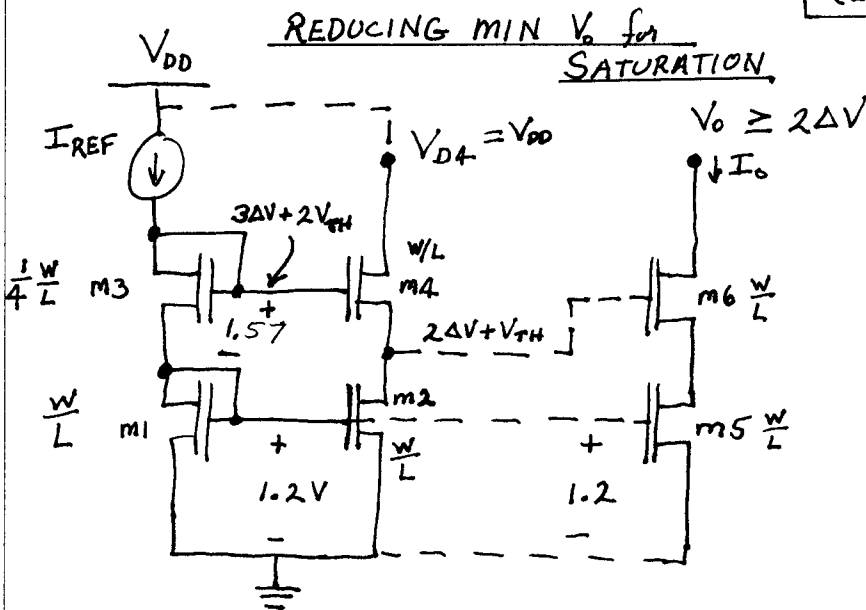
$$V_{D4} \geq \Delta V + V_{D2} = 0.37 + 1.2 = \boxed{1.57V} \quad \text{(The minimum for the current mirror is } \Delta V = 0.37V \text{.)}$$



Dotted lines:
Reduce $V_o \geq 2\Delta V$
where $\Delta V = V_{GS} - V_{TH}$.

• Reduce $\frac{W}{L}$ of $M3$ to $\frac{1}{4} \frac{W}{L}$

$$I_{REF} = \frac{1}{4} KP \frac{W}{L} (V_{GS3} - V_{THN})^2 = KP \frac{W}{L} (\underbrace{V_{GS1} - V_{TH}}_{1.2V})^2$$

$$V_{GS3} - V_{TH} = 2(V_{GS1} - V_{TH}) = 2\Delta V$$

where $\Delta V = 0.37$ as before.

$$V_{GS3} = 2\Delta V + V_{TH} = 2(0.37) + 0.83 = 1.57V$$

$$V_{G3} = V_{GS3} + V_{GS1} = 2\Delta V + V_{TH} + (V_{GS1} - V_{TH}) + V_{TH} = 3\Delta V + 2V_{TH}$$

$$V_{G3} = 3\Delta V + 2V_{TH}$$


$$\begin{aligned} \bullet V_{S4} = V_{G6} = V_{G3} - V_{GS3} &= 3\Delta V + 2V_{TH} - (\Delta V + V_{TH}) \\ V_{G6} &= 2\Delta V + V_{TH} \end{aligned}$$

$$\bullet V_{S6} = V_{G6} - V_{GS1} = 2\Delta V + V_{TH} - (\Delta V + V_{TH}) = \Delta V = 0.37V$$


$$\therefore V_{D6} = V_o \geq 2\Delta V = 0.74V$$

NOTE

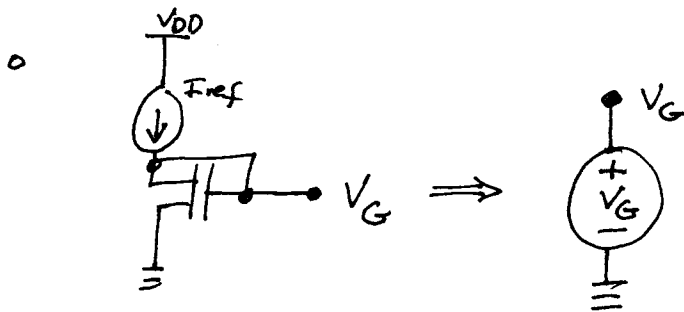
- $M4$ is used to drop down the gate voltage on $M6$ by $V_{GS} = 1.2V$.




Acts like a constant voltage source.

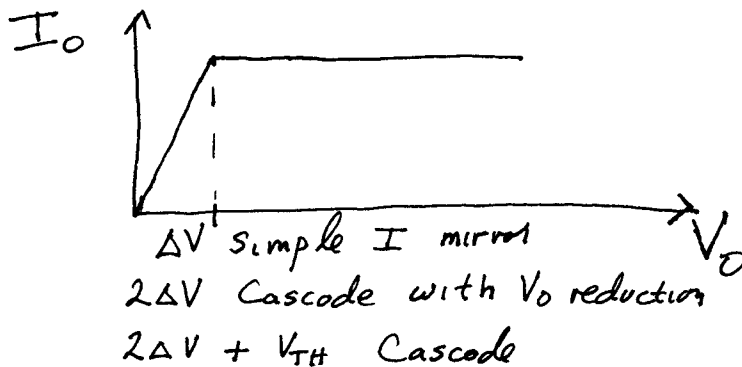


TRANSIENT RESPONSE of CURRENT MIRROR

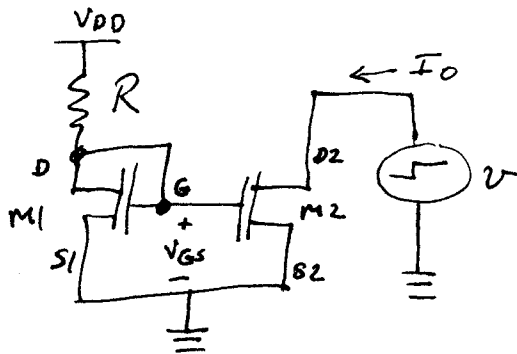

Small SIGNAL

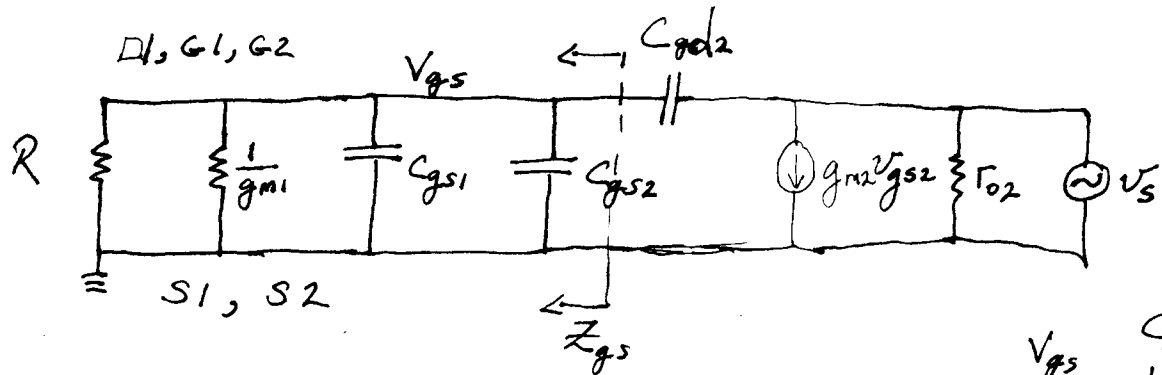
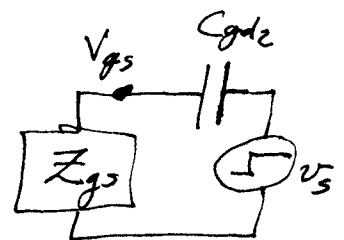
$$Z_{gs} = \frac{R \parallel \frac{1}{g_{m1}}}{1 + j\omega R \parallel \frac{1}{g_{m1}} (C_{gs1} + C_{gs2})}$$



$$v_{gs} = v_s \frac{Z_{gs}}{Z_{gs} + \frac{1}{j\omega C_{gd2}}} =$$


$$= v_s \frac{1}{1 + \frac{1 + j\omega R_{eq} (C_{gs1} + C_{gs2})}{j\omega R_{eq} C_{gd2}}} \quad R_{eq} \equiv R \parallel \frac{1}{g_m}$$

$$v_{gs} = v_s \frac{j\omega R_{eq} C_{gd2}}{1 + j\omega R_{eq} (C_{gs1} + C_{gs2} + C_{gd2})}$$

For instantaneous v_s (i.e. $\omega \rightarrow \infty$)

$$v_{gs} = v_s \frac{C_{gd2}}{C_{gs1} + C_{gs2} + C_{gd2}}$$

$$i_o = g_{m2} v_{gs}$$

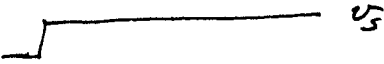Now v_s is held fixed  v_s
i.e. DC.
 $\omega = 0$

How long does it take v_{gs} to decay to DC value V_{GS} ?

1) For $v_s < 0$, $v_{gs} < 0$. ~~Current~~ Current flows thru R to recharge gate node to V_{GS} (DC value).

$$\Rightarrow \tau = RC = R(C_{gs1} + C_{gs2} + C_{gd2})$$

2) For $v_s > 0$, $v_{gs} > 0$. Current flows thru $1/g_m$ to discharge gate node to V_{GS} .

$$\tau = \frac{1}{g_m} (C_{gs1} + C_{gs2} + C_{gd2})$$