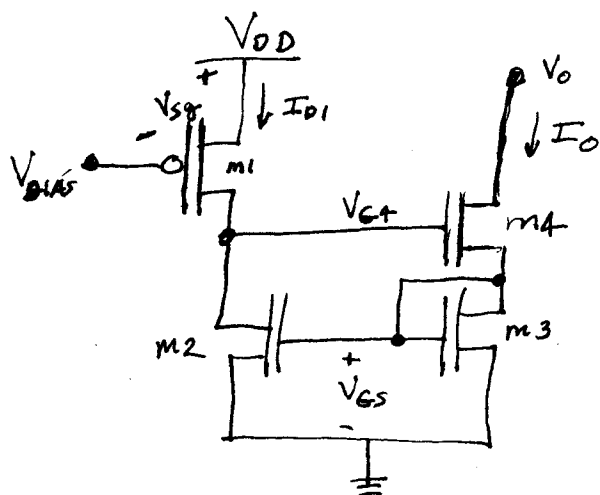


Sec. 20.2

WILSON CURRENT MIRROR

Negative feedback ^{to improve} ~~for~~ stability.

• Let I_{D1} be stable reference

• Assume $V_O \uparrow$

• $\Rightarrow I_O \uparrow$

$\Rightarrow I_{d3} \uparrow$

$\Rightarrow I_{d2} \uparrow$

• But I_{D1} fixed by V_{BIAS}

$\Rightarrow I_{D2}$ discharges $G4 \Rightarrow V_{G4} \downarrow \Rightarrow I_O \downarrow$

$$R_{out} \approx r_o + g_{m2} r_o^2/2$$

$$V_O(\min) = V_{GS3} + V_{DS4,sat} = V_{GS3} + V_{GS4} - V_{THN}$$




$$\approx 1.2 + 0.37$$

$$= 1.57 \text{ (cascode)}$$

$$I_O = \frac{\beta_3}{2} (V_{GS3} - V_{TH})^2$$

$$\sqrt{\frac{2I_O}{\beta_3}} + V_{TH3} = V_{GS3}$$

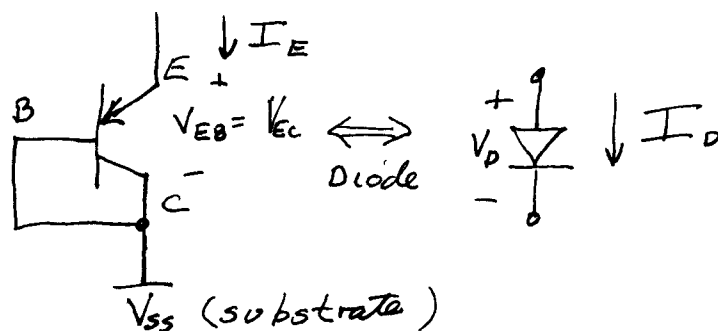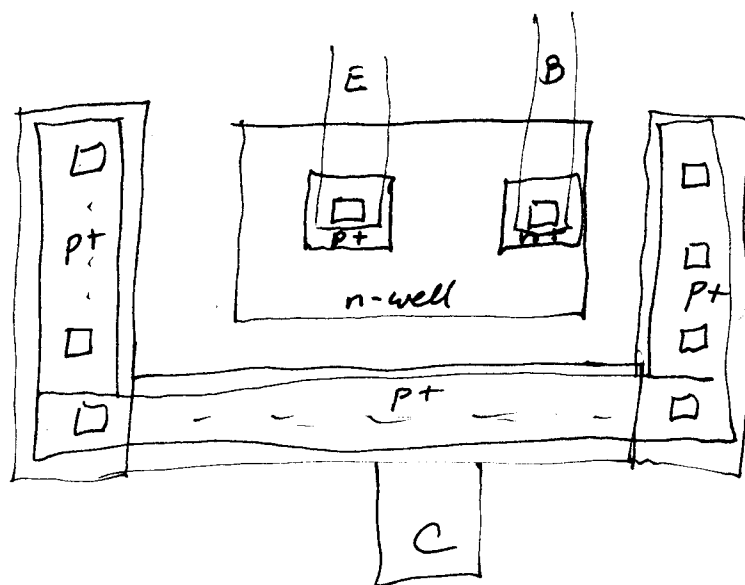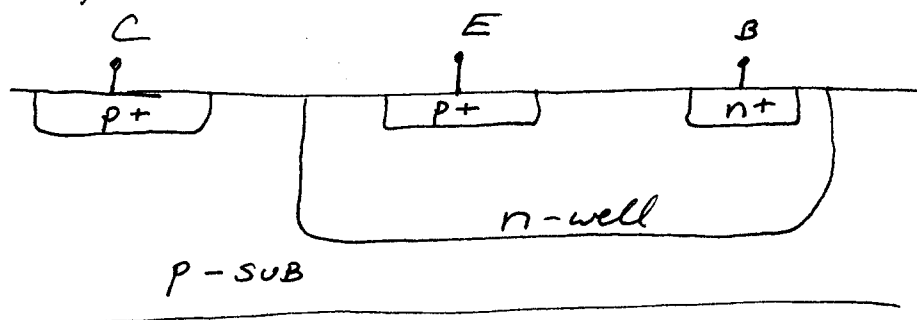(21.2.2) Diode Referenced Self Biasing.
USE parasitic PNP BJTs



Forward voltage reference, (V_{EB}) @ fixed I_E // $26\text{mV @ } 300\text{K}$
 $I_D = I_S e^{V_d / n V_T}$ ($V_T = kT/q$)

$I_S \propto \text{Emitter area}$


For given I_D , V_d is strongly T dependent.

W4

Thermal voltage ($V_T = \frac{kT}{q}$) referenced self biasing (21.2.3) ¹¹

Cascode forcing
same I thru
both arms.

FIG 21.12

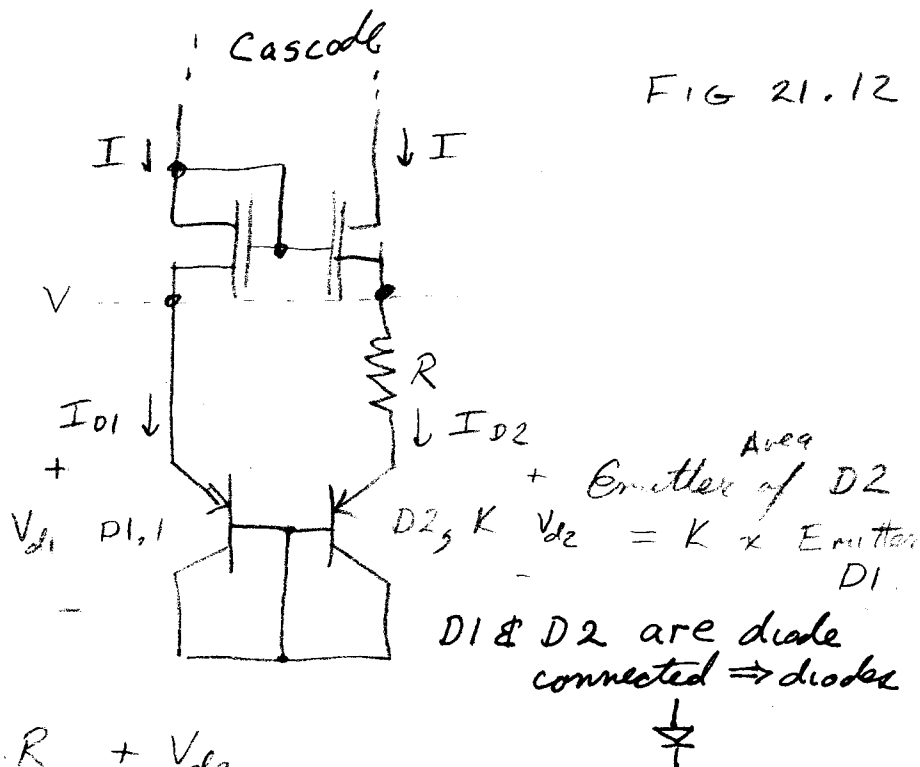

$$V_{D1} = I_{D2} R + V_{D2}$$

$$I_{D1} = I_S e^{V_{D1}/nV_T} \Rightarrow V_{D1} = nV_T \ln\left(\frac{I_{D1}}{I_S}\right)$$

$$I_{D2} = K I_S e^{V_{D2}/nV_T} \Rightarrow V_{D2} = nV_T \ln\left(\frac{I_{D2}}{K I_S}\right)$$

$$nV_T \ln\left(\frac{I}{I_S}\right) = IR + nV_T \ln\left(\frac{I}{K I_S}\right)$$

$$\ln\left(\frac{I/I_S}{I/K I_S}\right) = \ln K = \frac{IR}{nV_T}$$

$$R = \frac{nV_T \ln K}{I}$$

$$I = \frac{n \ln K}{g R} k_B T =$$

Temp Coeff

$$TC_I = \frac{1}{I} \frac{dI}{dT} = \frac{1}{T} - \frac{1}{R} \frac{\partial R}{\partial T} \approx 1000 \frac{\text{ppm}}{^\circ\text{C}}$$


3300 $\frac{\text{ppm}}{^\circ\text{C}}$ 2000 $\frac{\text{ppm}}{^\circ\text{C}}$ >0 cancellation

W4

Thermal voltage ($V_T = \frac{kT}{q}$) referenced self biasing (21.2.3) ¹¹

Cascode forcing
same I thru
both arms.

FIG 21.12

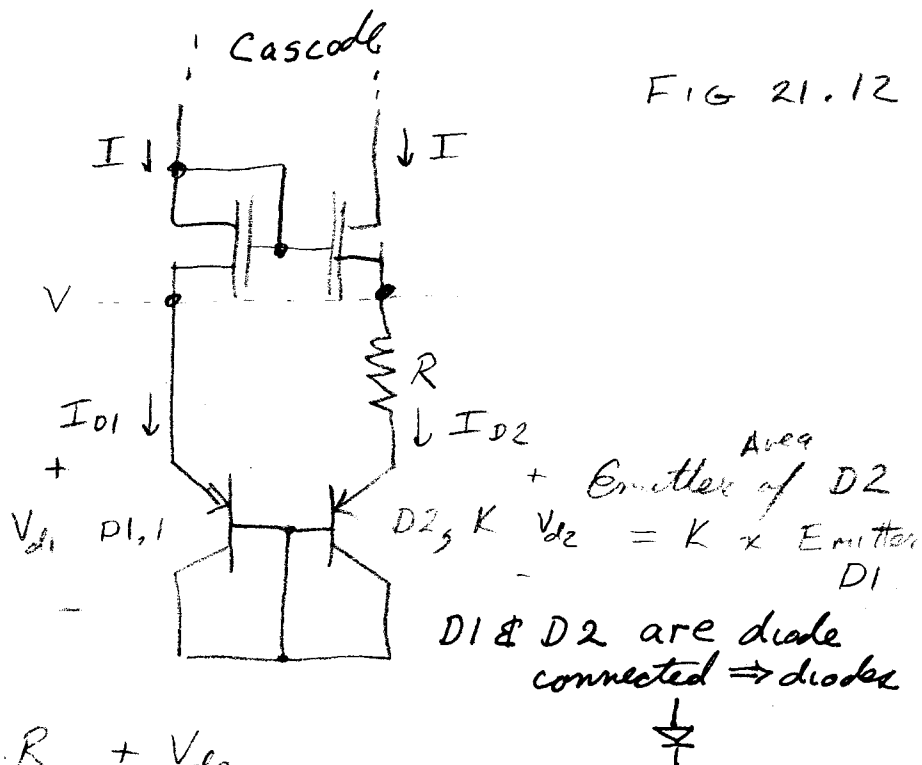

$$V_{d1} = I_{d2} R + V_{d2}$$

$$I_{d1} = I_s e^{V_{d1}/nV_T} \Rightarrow V_{d1} = nV_T \ln\left(\frac{I_{d1}}{I_s}\right)$$

$$I_{d2} = K I_s e^{V_{d2}/nV_T} \Rightarrow V_{d2} = nV_T \ln\left(\frac{I_{d2}}{K I_s}\right)$$

$$nV_T \ln\left(\frac{I}{I_s}\right) = IR + nV_T \ln\left(\frac{I}{K I_s}\right)$$

$$\ln\left(\frac{I/I_s}{I/K I_s}\right) = \ln K = \frac{IR}{nV_T}$$

$$R = \frac{nV_T \ln K}{I}$$


$$I = \frac{n \ln K}{g R} k_B T =$$

Temp Coeff

$$TC_I = \frac{1}{I} \frac{dI}{dT} = \frac{1}{T} - \underbrace{\frac{1}{R} \frac{\partial R}{\partial T}}_{>0} \approx 1000 \frac{\text{ppm}}{^\circ\text{C}}$$

3300 $\frac{\text{ppm}}{^\circ\text{C}}$ 2000 $\frac{\text{ppm}}{^\circ\text{C}}$ cancellation

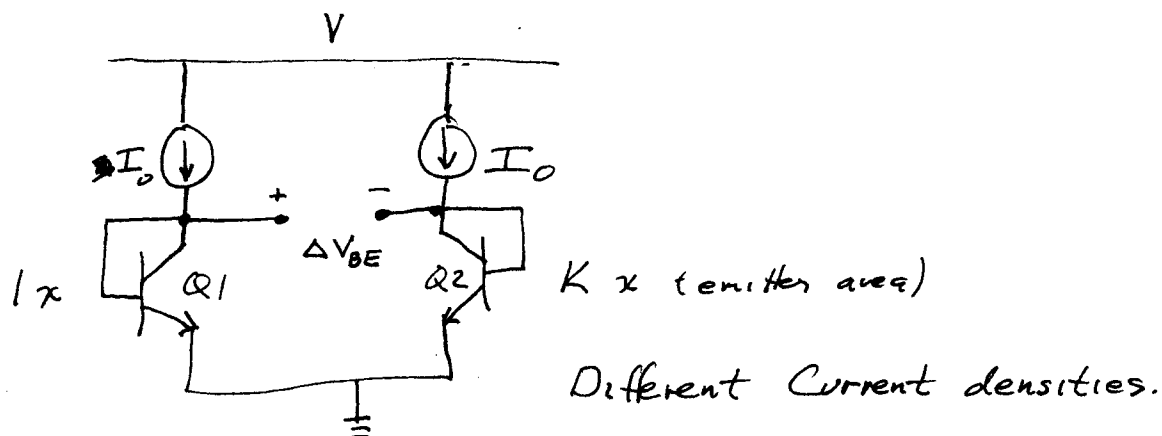Underlying Principle of thermal voltage (V_T) ref.



$$\Delta V_{BE} = V_{BE1} - V_{BE2}$$

$$= V_T \ln \left(\frac{I_0}{I_{S1}} \right) - V_T \ln \left(\frac{I_0}{K I_{S1}} \right)$$


$$\Delta V_{BE} = V_T \ln K = \frac{k_B T}{q} \ln(K)$$

$$\Delta V_{BE} \propto T \quad \& \quad \text{independent of } I$$

(2.1.3) BAND GAP V REFERENCE

Combine + TC of thermal Voltage (V_T) w/
- TC of diode forward V. (V_d).

To achieve a V_{ref} with 0 TC.

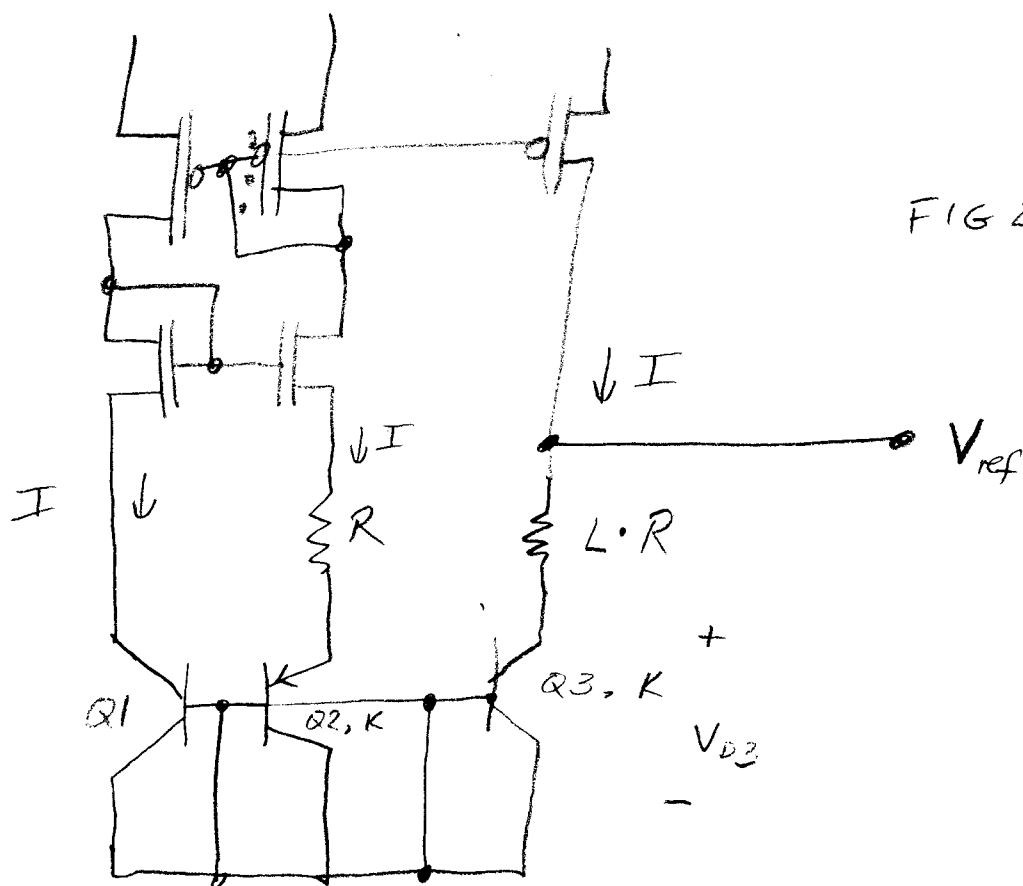

$$I = \frac{nV_T \ln K}{R}$$

$$V_{ref} = I L R + V_{D3}$$

$$V_{ref} = \underbrace{nV_T}_{\text{Thermal } V} (\ln K) L + \underbrace{V_{D3}}_{\text{Diode forward } V}$$

$$\frac{\partial V_{ref}}{\partial T} = n L \ln K \underbrace{\frac{\partial V_T}{\partial T}}_{0.085 \text{ mV}/^\circ\text{C}} + \underbrace{\frac{\partial V_{D3}}{\partial T}}_{-2 \text{ mV}/^\circ\text{C}} = 0$$

Choose L & K :

$$n L \ln K = \frac{2}{0.085} = 23.5$$


$$n=1, K=8, L=11.3 \text{ for } TC=0$$

$V_{G2} \sim 0 \Rightarrow$ ^{done} m5 turns on & pulls V_{G2} up to $2V_{GS}$.

(pt A) (Desired op. pt.)
When $V_{G2} = 2V_{GS}$, $V_{GS5} = 0$ & m5 shuts off.

21.4 BETA MULTIPLIER REFERENCED SELF BIASING

FIG 21.16

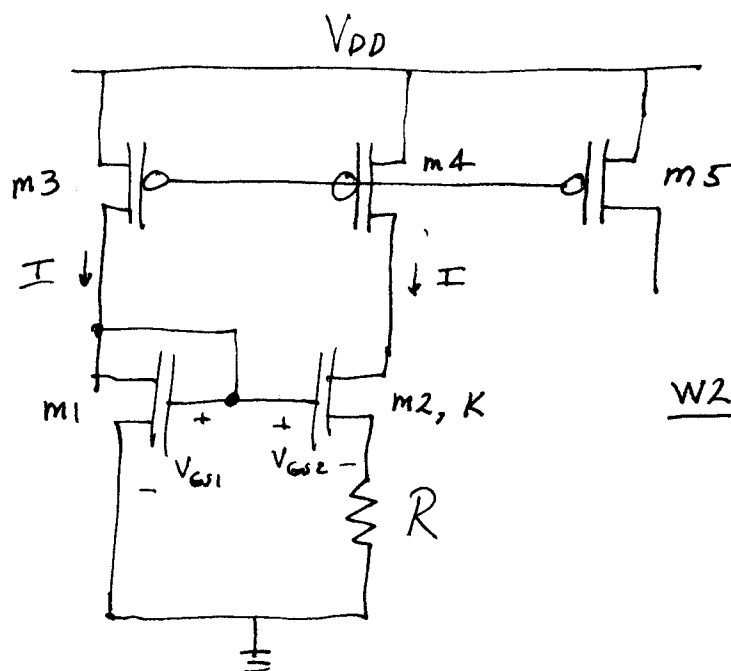

$$W2 = K \cdot W1$$

$$L_1 = L_2 \text{ \& } W_2 = K W_1 \Rightarrow \beta_2 = K \beta_1$$

$$V_{GS1} = V_{GS2} + IR$$

$$V_{GS1} = \sqrt{\frac{2I}{\beta_1}} + V_{THN}$$

$$V_{GS2} = \sqrt{\frac{2I}{K\beta_1}} + V_{THN}$$

$$\sqrt{\frac{2I}{\beta}} = \sqrt{\frac{2I}{K\beta}} + IR$$

$$\sqrt{\frac{2I}{\beta}} \left(1 - \frac{1}{\sqrt{K}}\right) = IR$$

$$\frac{2I}{\beta} \left(1 - \frac{1}{\sqrt{K}}\right)^2 = I^2 R^2$$

$$(I \neq 0)$$

$$I = \frac{2}{R^2 \beta} \left(1 - \frac{1}{\sqrt{K}}\right)^2 \quad (K > 1) \quad \text{Needs start up circuitry Fig. 21.17.}$$

$$\begin{aligned} TC_I &= \frac{1}{I} \frac{\partial I}{\partial T} = \frac{1}{I} \left(\frac{\partial I}{\partial R} \frac{\partial R}{\partial T} + \frac{\partial I}{\partial \beta} \frac{\partial \beta}{\partial T} \right) \\ &= \frac{R^2 \beta}{\cancel{I}} \left(-\frac{2}{R^3 \beta} \frac{\partial R}{\partial T} + \frac{-1}{R^2 \beta^2} \frac{\partial \beta}{\partial T} \right) \\ &= \left(-\frac{2}{R} \frac{\partial R}{\partial T} - \frac{1}{\beta} \frac{\partial \beta}{\partial T} \right) \\ &\quad -4000 \frac{\text{ppm}}{^\circ\text{C}} + \frac{1.5}{T} \end{aligned}$$

$$= \begin{cases} 0 & @ T = 375 K \\ 1000 \frac{\text{ppm}}{^\circ\text{C}} & @ 300 K \end{cases}$$

$$\begin{aligned} \beta &= \mu_n C_{ox} \frac{W}{L} \\ L &= \mu(T_0) \left(\frac{T}{T_0}\right)^{-1.5} \\ \beta &= \beta_0 \left(\frac{T}{T_0}\right)^{-1.5} \end{aligned}$$

(21.4-1) β Multiplier Voltage Ref

$$V_{ref} = V_{GS1} = V_{GS2} + IR$$

$$= \underbrace{\sqrt{\frac{2I}{K\beta_1}} + V_{THN}}_{V_{GS2}} + \underbrace{\frac{2}{R\beta_1} \left(1 - \frac{1}{\sqrt{K}}\right)^2}_{IR}$$

$$= \frac{2}{R\beta_1 \sqrt{K}} \left(1 - \frac{1}{\sqrt{K}}\right) + V_{THN} + \frac{2}{R\beta_1} \left(1 - \frac{1}{\sqrt{K}}\right)^2$$

$\left(\frac{1}{\sqrt{K}} - \frac{1}{K}\right)$
 $1 - 2\frac{1}{\sqrt{K}} + \frac{1}{K}$

$$= \frac{2}{R\beta_1} \left(1 - \frac{1}{\sqrt{K}}\right) + V_{THN}$$

$$\frac{dV_{ref}}{dT} = \underbrace{\frac{dV_{THN}}{dT}}_{-2.4 \frac{mV}{^{\circ}C}} - \frac{2}{R\beta_1} \left(1 - \frac{1}{K}\right) \left[\underbrace{\frac{1}{R} \frac{\partial R}{\partial T}}_{\frac{2000 \text{ ppm}}{^{\circ}C}} + \underbrace{\frac{1}{\beta} \frac{\partial \beta}{\partial T}}_{-\frac{1.5}{T}} \right]$$

$$\left. \frac{dV_{ref}}{dT} \right|_{300K} = 0 \text{ when } \frac{2}{R\beta_1} \left(1 - \frac{1}{K}\right) = \frac{-0.0024}{[0.002 - 0.005]}$$

Let $K=4$:

$$= 0.8$$

$$R = \frac{1}{(0.8)\beta_1} \quad V_{ref} = \frac{0.8\beta_1}{\beta_1} 2\left(\frac{1}{2}\right) + V_{THN}$$

$$\boxed{V_{ref} = V_{GS1} = 0.8 + V_{THN}} = 1.63V$$

Notes:

- Error in V_{ref}

- process variations (ΔV_{THN} , ΔR , $\Delta \beta$)

- ∇T

- Body Effect


- Less precise than BJT bandgap V_{ref}

- Laser trimming of R .

CN20 Table A.7

N-well R_{sq} 2000 - 3000 $\frac{\Omega}{\square}$

- Fuses

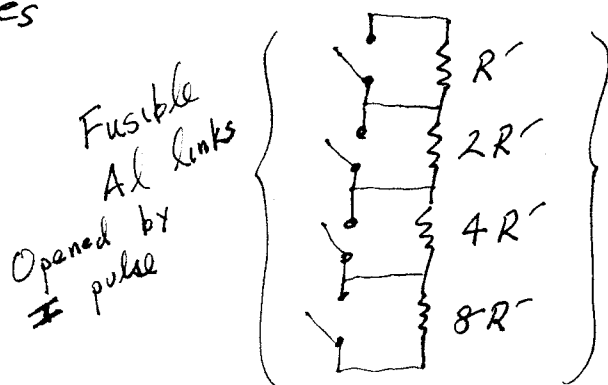

2^n values of R_{TOT}
for n R_s .


LOW I SOURCE (Subthreshold)

- Want $I_{\bullet} = 100 \text{ nA}$.

Simple I Mirror

Choose $V_{GS} = 1 \text{ V}$

$V_{DD} = 2 \text{ V}$

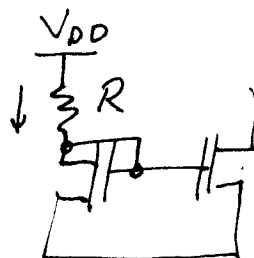

$$I = \frac{1 \text{ V}}{R} = 1 \text{ e-}7 \text{ A}$$

$$R = 10 \text{ M}\Omega \quad (\text{not available})$$

- USE β multiplier in subthreshold (Widlar)

$$I \approx I_{D0} \frac{W}{L} e^{(V_{GS} - V_{THN})/nV_T} \quad (\text{Same form as diode equation})$$

$$V_{GS1} = nV_T \ln \left[\frac{I L}{I_{D0} W} \right] + V_{THN}$$

SEE FIG 21.16

$$V_{GS2} = nV_T \ln \left[\frac{I L}{K I_{D0} W} \right] + V_{THN}$$

$$V_{GS1} = V_{GS2} + IR$$

$$nV_T \ln(K) = IR$$

$$I = \frac{nV_T}{R} \ln(K)$$

Thermal Voltage referenced

~~Use this to create a~~

$$n = 1$$

$$K = 2$$

$$V_T = 0.026 \text{ V}$$

$$R = 180 \text{ k}\Omega$$